

10/55

$$V_o(s) = \frac{R_2 + \frac{1}{sC_1}}{\frac{1}{sC_1}} V_2(s)$$

$$\Rightarrow V_o(s) = (sC_1 R_2 + 1) V_2(s)$$

KCL  $V_o$ :

$$V_o \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_2 \right) = \frac{V_1(s)}{R_1} + V_2(s) \left( sC_2 + \frac{1}{R_2} \right)$$

$$V_2(s) (sC_1 R_2 + 1) \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_2 \right) - V_2(s) \left( sC_2 + \frac{1}{R_2} \right) = \frac{V_1(s)}{R_1}$$


$$V_2(s) \left( \frac{sC_1 R_2}{R_1} + sC_1 + s^2 C_1 C_2 R_2 + \frac{1}{R_1} + \cancel{\frac{1}{R_2}} + \cancel{sC_2} - \cancel{sC_2} - \cancel{\frac{1}{R_2}} \right) = \frac{V_1(s)}{R_1}$$

$$\therefore V_1(s) = V_2(s) (sC_1 R_2 + sC_1 R_1 + s^2 C_1 C_2 R_1 R_2 + 1)$$

and


$$\frac{V_2(s)}{V_1(s)} = \boxed{T(s) = \frac{(C_1 C_2 R_1 R_2)^{-1}}{s^2 + s[(C_2 R_1)^{-1} + (C_2 R_2)^{-1}] + (C_1 C_2 R_1 R_2)^{-1}}}$$
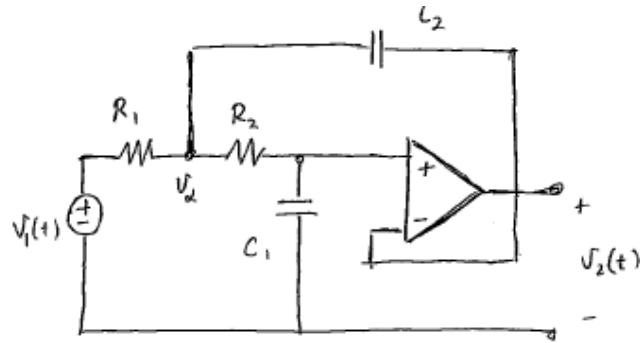
$$\left( \text{equivalently } T(s) = \frac{1}{C_1 C_2 R_1 R_2 s^2 + (R_2 + R_1) C s + 1} \right)$$



11.3, 11.8, 11.9

11.5

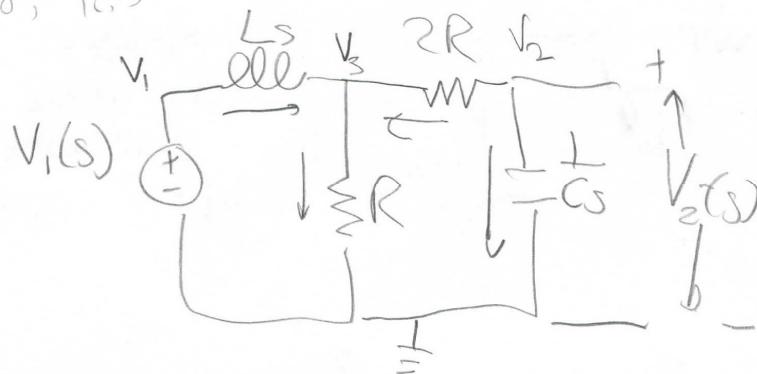

$$\frac{V_1 - V_3}{Ls} - \frac{V_3}{R} + \frac{V_2 - V_3}{2R} = 0$$

$$\textcircled{1} \quad \frac{V_2}{2R} - \left( \frac{1}{Ls} + \frac{1}{R} + \frac{1}{2R} \right) V_3 = -\frac{V_1}{Ls}$$


$$-\frac{V_2 - V_3}{2R} - \frac{V_2}{Cs} = 0$$

$$\textcircled{2} \quad -\left(\frac{1}{2R} + Cs\right)V_2 + \frac{V_3}{2R} = 0$$

$$\begin{bmatrix} \frac{1}{2R} & -\left(\frac{1}{Ls} + \frac{1}{R} + \frac{1}{2R}\right) \\ -\left(\frac{1}{2R} + Cs\right) & \frac{1}{2R} \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -\frac{V_1}{Ls} \\ 0 \end{bmatrix}$$

using Matlab,  $V_2 = \frac{R \cdot V_1}{3CLRs^2 + (2CR^2 + L)s + R}$
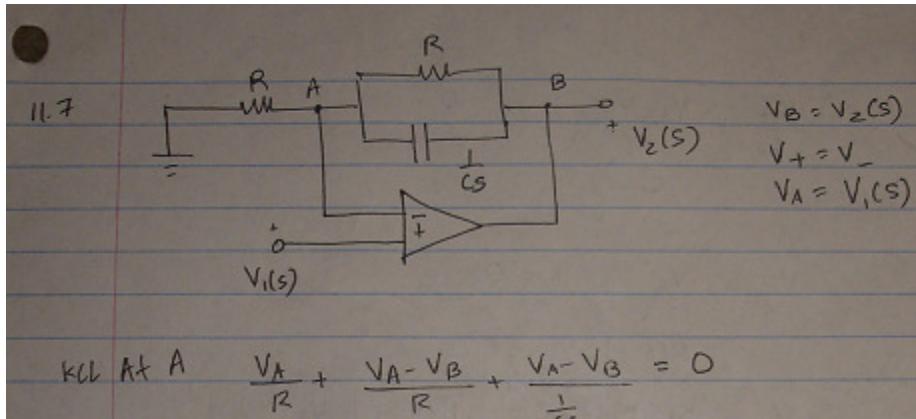
$$\boxed{\frac{V_2}{V_1} = \frac{R}{3CLRs^2 + (2CR^2 + L)s + R}}$$



$$\text{KCL at } A \quad \frac{V_A}{R} + \frac{V_A - V_B}{R} + \frac{V_A - V_B}{\frac{1}{CS}} = 0$$

$$\frac{V_A}{R} + \frac{V_A - V_B}{\frac{R(\frac{1}{CS})}{R + \frac{1}{CS}}} = 0$$

$$\frac{V_A}{R} + \frac{V_A - V_B}{\frac{R}{RCS+1}} = 0$$

$$\frac{V_A}{R} + \frac{\frac{RCS+1}{R} V_A}{\frac{R}{RCS+1}} = \frac{\frac{RCS+1}{R} V_B}{R}$$

$$V_1(s) \left[ \frac{1}{R} + \frac{RCS+1}{R} \right] = \frac{RCS+1}{R} V_B$$

$$V_1(s) \left[ \frac{RCS+2}{R} \right] = \frac{RCS+1}{R} V_2(s)$$

$$\frac{V_2(s)}{V_1(s)} = \frac{(RCS+2)R}{R(RCS+1)} = \frac{RCS+2}{RCS+1}$$

pole at  $-1k \text{ rad/s}$

$$RCS+1=0 \Rightarrow S = \frac{-1}{RC} = -1k$$

$R = 1k$
$C = 1MF$

$$[1/8] \quad T_I(s) = \frac{I_2(s)}{I_1(s)} = \frac{R}{3R + sL} \quad (\text{immediate from source transformation})$$

$$\boxed{T_I(s) = \frac{R/L}{s + 3R/L}}$$

e.g.  $\boxed{R = \frac{500}{3} \Omega, L = 1 H}$

This answer is non-unique

11-28



$$i_1(s) = \frac{s}{s+\beta^2}$$

$$i_1(s) = \frac{10s}{s+\beta^2} \cdot 10^{-3}$$

 $\beta = 500$ 

$$R_2 i_2 - L s i_2 - R_1 (i_2 - i_1) = 0$$

$$R_1 i_1 - (R_1 + R_2 + L s) i_2 = 0$$

$$\begin{bmatrix} 1 & 0 \\ R_1 & -(R_1 + R_2 + L s) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \frac{10s}{s+\beta^2} \\ 0 \end{bmatrix}$$

for  $\beta = 500$ 

$$i_2(s) = \frac{10^2 R_1 s}{L s^3 + (R_1 + R_2)s^2 + \beta^2 L s + \beta^2 (R_1 + R_2)}$$

$$i_2(s) = \frac{s}{s^3 + 500s^2 + 25000s + 125 \times 10^8}$$

$$i_2(s) = \frac{-0.002}{s+5000} + \frac{.001 - .0001i}{s - 500i} + \frac{.001 + .0001i}{s + 500i}$$

$$i_2(t) = -.002 e^{-5000t} + (.001 - .0001i) e^{500it} + (.001 + .0001i) e^{-500it}$$

decays to zero  $+ (.001 - .0001i)(\cos 500t + i \sin 500t) + (.001 + .0001i)(\cos 500t - i \sin 500t)$

$$i_2(t) = -2 \left( \cos 500t + \frac{\sin 500t}{10} \right) \text{ mA} \approx -2 \cos(500t - 0.0997)$$

$$\text{for } \beta = 5000, i_2(s) = \frac{s}{s^3 + 500s^2 + 2.5 \times 10^6 + 1.25 \times 10^{10}} = \frac{-0.001}{s+5000} + \frac{+5 \times 10^{-4} + 5 \times 10^{-4}i}{s+5000i} + \frac{5 \times 10^{-4} - 5 \times 10^{-4}i}{s-5000i}$$

$$i_2(t) = -.001 e^{-5000t} + (5 \times 10^{-4} + 5 \times 10^{-4}i) e^{5000it} + (5 \times 10^{-4} - 5 \times 10^{-4}i) e^{-5000it}$$

decays to zero

$$i_{2ss}(t) = -(\cos 5000t + \sin 5000t) \text{ mA} = -\sqrt{2} \cos(5000t - \frac{\pi}{4})$$

$$11.7) \quad T_V(s) = \pm \frac{2 \times 10^5}{(s+100)(s+10000)}$$

Case i)

$$T_V(s) = \frac{k_1}{s+100} - \frac{k_2}{s+10000} - \frac{k_3}{s}$$

$$\frac{k_1}{s+100} = \frac{k_1/s}{1+100/s} = \frac{\bar{Z}_2(s)}{\bar{Z}_1(s) + \bar{Z}_2(s)}$$

$$\bar{Z}_2(s) = \frac{k_1}{s} \quad \bar{Z}_1(s) = 1 + \frac{100}{s} - \frac{k_1}{s}$$

$$\boxed{\bar{Z}_2 = \frac{100}{s} \quad \bar{Z}_1(s) = 1} \quad = 1 + \frac{(100 - k_1)}{s}$$

$$k_1 = 100 \Rightarrow 10^2$$

$$\frac{k_3}{s+10000} = \frac{\bar{Z}_2(s)}{\bar{Z}_1(s) + \bar{Z}_2(s)} = \frac{k_3/s}{1 + 10000/s}$$

$$\bar{Z}_2(s) = \frac{k_3}{s} \quad \bar{Z}_1(s) = 1 + \frac{10000 - k_3}{s}$$

$$k_3 = 10000 \Rightarrow 10^3$$

$$\boxed{\bar{Z}_2(s) = \frac{10^3}{s} \quad \bar{Z}_1(s) = 1 + \frac{10000}{s}}$$

$$\text{Case (i): } k_1 k_2 k_3 = +2 \times 10^5$$


$$C < 1 \mu F = 10^{-6}$$

$$R > 10k = 10^4$$

$$10^5 k_2 = 2 \times 10^5$$

$$k_2 = \frac{Z}{\cancel{Z}} = \cancel{-2} = \frac{Z_1 + Z_2}{Z_2} \quad \begin{matrix} Z_1 + Z_2 = \cancel{10^4} \\ \cancel{Z_2 = 0} \end{matrix}$$

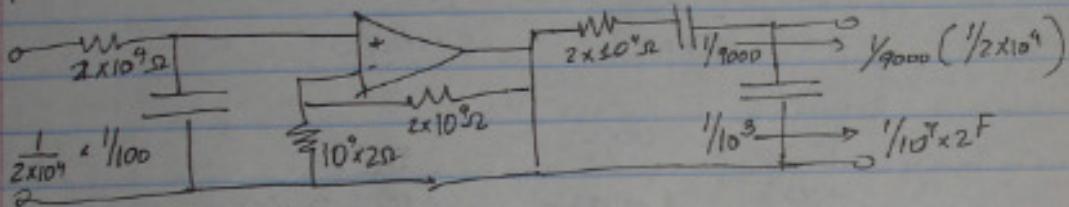using scaling factor  $k_m = 10^4 \times 2$




$$(Ans (ii)) \quad k_1, k_2, k_3 = 2 \times 10^5$$

$$10^5 k_2 = -2 \times 10^5$$

$$\Rightarrow k_2 = -2$$
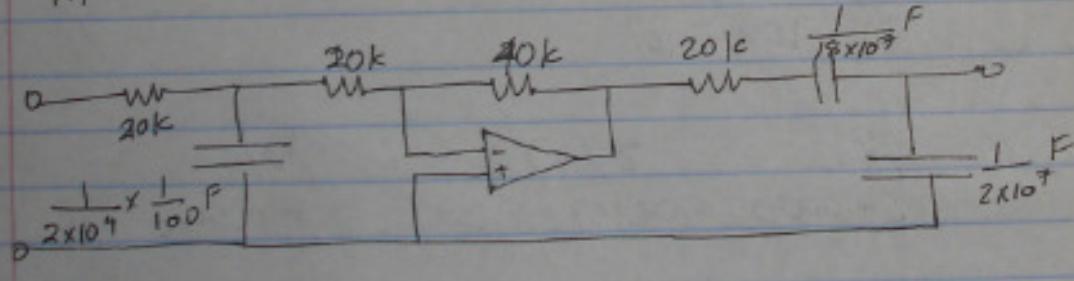
$$\frac{-R_2}{R_1} = -2 \Rightarrow R_2 = 2R_1$$



11/58a cct 1:  $v_i(s) = v_p(s)$

$$v_p(s) \cdot \left( \frac{1}{10k} + \frac{1}{10k} + (100n)s \right) = v_2(s) \left( \frac{1}{10k} + (100n)s \right)$$

$$v_i(s) = \left( 2 \cdot 10^{-4} + 10^{-7}s \right) = v_2(s) \left( 10^{-4} + 10^{-7}s \right)$$

$$\frac{v_2(s)}{v_i(s)} = T_V(s) = \left( \frac{s + 2000}{s + 1000} \right) \quad \blacksquare$$

cct 2:  $v_2(s) = \frac{10k + (50n \cdot s)^{-1} v_i(s)}{20k + (50n \cdot s)^{-1}}$


$$\begin{aligned} \frac{v_2(s)}{v_i(s)} &= T_V(s) = \frac{(10k)(50n)s + 1}{(20k)(50n)s + 1} \\ &= \frac{\frac{1}{2}s + 1000}{s + 1000} \times \frac{2}{2} \end{aligned}$$

$$T_V(s) = \frac{1}{2} \left( \frac{s + 2000}{s + 1000} \right) \quad \blacksquare$$

11/58b Since loading, especially for impedances of less than  $10\text{k}\Omega$ , changes the  $v_i$  to  $v_2$  characteristic of circuit 2, circuit 1 is clearly superior.

11/58c An input impedance changes the  $v_i$  to  $v_2$  characteristic of circuit 2, so circuit 1 is superior; ~~however~~ however, one may argue that the  $100\text{\Omega}$  input impedance has negligible influence on the transfer function of circuit 2~~2~~ (considering tolerances of practical components), so, because circuit 2 uses fewer & cheaper parts, it is superior.

11/58d This assertion is true. Note that the transfer function of circuit 1 is unaffected by both input and output impedances. ~~as~~ The transfer function of circuit 2 may be affected by input or output impedances; however, circuit 1 introduces neither (this may be verified by a straightforward ~~argument~~ argument using Thevenin's Theorem... but only if you're feeling really anal). Hence the circuits may be connected in either order.

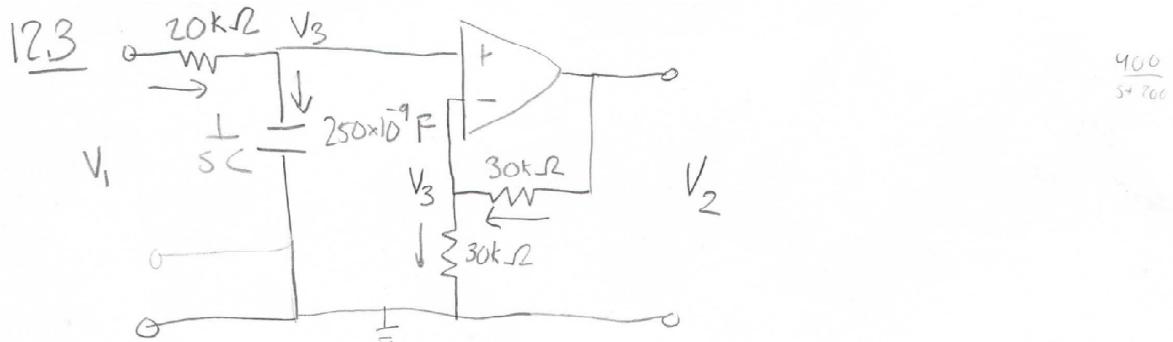

$$\frac{V_1 - V_3}{20k} - V_3 sC = 0$$

$$\frac{1}{20k} V_1 + 0V_2 - \left( \frac{1}{20k} + sC \right) V_3 = 0$$

$$\frac{1}{20k} \cdot \left( \frac{V_1}{\frac{1}{20k} + sC} \right) = V_3$$

$$V_3 = \frac{2}{20k} \cdot \frac{V_1}{\frac{1}{20k} + sC} = \frac{2}{20k} \cdot \frac{V_1}{\frac{1}{20k} + \frac{1}{20k} sC} = \frac{2}{1 + 20ksC}$$

$$\frac{V_2 - V_3}{30k} - \frac{V_3}{30k} = 0$$

$$0V_1 + \frac{1}{30k} V_2 - \left( \frac{1}{30k} \right) V_3 = 0$$

$$V_2 = 2V_3$$

$$\frac{V_2}{V_1} = \frac{2}{1 + 20ksC} = \frac{V_2}{V_1} = \frac{400}{s+200}$$


a)

DC gain: 2

Infinite frequency gain: 0

$$\sqrt{\omega^2 + 200^2} = \frac{2}{\sqrt{2}} \Rightarrow \frac{400^2}{2} = \omega^2 + 200^2 \quad [\omega_c = 200 \text{ rad/s}]$$

low pass filter

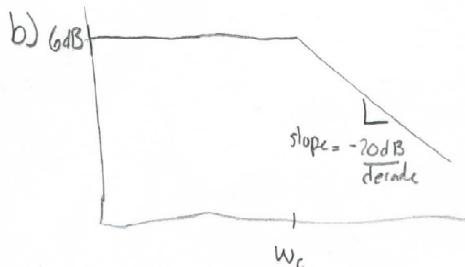

c) gain at  $0.5\omega_c$ :

$$\frac{400}{\sqrt{100^2 + 200^2}} = \boxed{1.789}$$


gain at  $\omega_c$ :

$$\boxed{1.414}$$

gain at  $2\omega_c$ :

$$\boxed{1.8944}$$

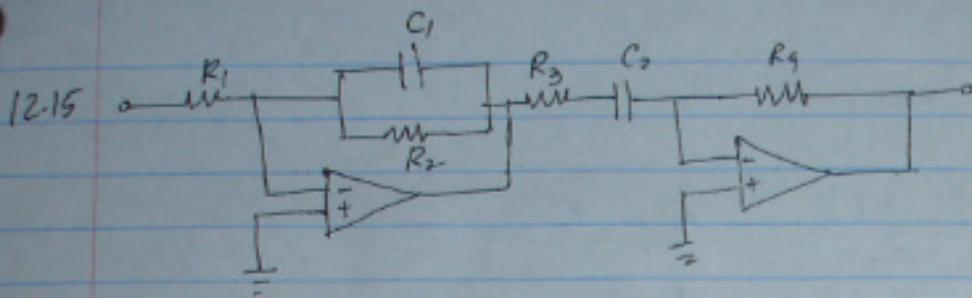e) increase the horizontal  $30\text{k}\Omega$  resistor to a  $270\text{k}\Omega$  resistor



$$\text{Bandpass gain} = 30$$

$$\omega_{c1} = 100 \text{ rad/s} \quad \omega_{c2} = 2500 \text{ rad/s}$$

$$R \geq 10k \quad C \leq 1\text{NF}$$

Stage 1: Inverter

$$K_1 = -\frac{R_2}{R_1} = -\frac{\frac{1}{C_1 s \cdot R_2}}{R_1 + \frac{1}{C_1 s}} = \frac{-R_2}{(R_2 C_1 s + 1) R_1}$$

Stage 2:

$$K_2 = -\frac{R_4}{R_3} = -\frac{R_4}{R_3 + \frac{1}{C_2 s}} = \frac{-R_4 C_2 s}{R_3 C_2 s + 1}$$

$$T_V(s) = \frac{-R_2}{R_1(R_2 C_1 s + 1)} \cdot \frac{-R_4 C_2 s}{(R_3 C_2 s + 1)}$$

$$T(s) = \left( \frac{R_2 / R_1 R_2 C_1}{s + \frac{R_1}{R_1 R_2 C_1}} \right) \cdot \left( \frac{\frac{R_4 C_2 s}{R_3 C_2}}{s + \frac{1}{R_3 C_2}} \right)$$

~~$$\omega_{c1} = \frac{1}{R_2 C_1} \quad \omega_{c2} = \frac{1}{R_3 C_2} \quad K_1 = \frac{R_2}{R_1 C_1}$$~~

$$\omega_{c1} = \frac{1}{R_2 C_1} \quad \omega_{c2} = \frac{1}{R_3 C_2} \quad K_1 = \frac{R_2}{R_1 C_1}$$

$$K_2 = \frac{R_4}{R_3}$$

band pass filter

$$\frac{|k_1 k_2|}{d_2} = \frac{\frac{1}{R_1 C_1} \cdot \frac{R_4}{R_3}}{\frac{1}{R_3 C_2}}$$

$$\Rightarrow \frac{R_4 C_2}{R_1 C_1} = 30$$

$$\frac{1}{R_3 C_2} = 100 \text{ rad/s} \Rightarrow$$

$$\frac{1}{R_2 C_1} = 2500$$

$$C_1 = \frac{1}{2500 R_2} \quad C_2 = \frac{1}{100 R_3}$$

$$R_2 = 10\text{k}$$

$$C_1 = 4 \times 10^{-9} \text{ F}$$

$$R_3 = 10\text{k}$$

$$C_2 = \cancel{10^{-9}} \cdot 10^{-7} \text{ F}$$

$$\frac{R_4}{R_1} \cdot \frac{10^{-7}}{4 \times 10^{-9}} < 30$$

$$\frac{R_4}{R_1} = \frac{6}{5} \Rightarrow R_4 = 60\text{k}$$

$$R_1 = 50\text{k}$$

12/57] 1<sup>st</sup> cut: filter characteristics

$$v_p(s) = \frac{1k}{100m + \frac{1}{400ns} + 1k} V_1(s) = \frac{10k}{100k} V_2(s)$$

$$\begin{aligned} \frac{V_2(s)}{V_1(s)} &= T_1(s) = \frac{10k}{s100m + \frac{1}{s400n} + 1k} \\ &= \frac{(10k)(400n)s}{s^2(100m)(400n) + (1k)(400n)s + 1} \\ &= \frac{10^5 s}{s^2 + 10^4 s + 25 \times 10^6} \\ &= \frac{10^5 s}{(s+5000)(s+5000)} \end{aligned}$$

The so-called pass-band gain is attained at roughly  $\boxed{\omega_0 = 5000 \text{ rad/s}}$  (the center frequency)

$$|T(5000j)| = \left| \frac{10^5 (5000j)}{2(5000)(5000)} \right| = |10j| = \frac{10}{\sqrt{2}}$$

$$\Rightarrow \boxed{|T(\omega_0 j)| = 10} \quad (\text{pass-band gain})$$

The cut-off frequencies are

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} =$$

$$B = \omega_{c2} - \omega_{c1} = \boxed{10 \text{ krad/s} = B} \quad (\text{bandwidth})$$

Filter 1 meets specs almost exactly. ~~Filter 2~~  
 Because it is also a superior design when comparing part count & use of standard components, there is no reason to investigate the filter specs of circuit 2 (though there is nothing wrong with doing so.)  
 Hence, filter 1 is the better design  
 (Should be worth half of points)