

# HW #1 solutions

1-17.

$$i = e^v - 10$$

$$p = iv$$

for  $v = -2$ ,  $P = -2 \cdot (e^{-2} - 10) = 19.73 \text{ W}$ , absorbing

for  $v = 2$ ,  $P = 2 \cdot (e^2 - 10) = -5.22 \text{ W}$ , delivering

for  $v = 3$ ,  $P = 3 \cdot (e^3 - 10) = 30.26 \text{ W}$ , absorbing.


1-20

$i = 2 \text{ A}$ ,  $T = 4 \text{ hrs}$ ,  $v(t) = 12 - 2e^{-t}$

$$W = \int_0^T P dt = \int_0^T iv dt = 2 \int_0^4 (12 - 2e^{-t}) dt$$

$$= 2 \cdot (12t + 2e^{-t}) \Big|_0^4 = 2 \left[ 48 + \frac{2}{e^4} - 2 \right] = 92.1 \text{ J}$$

1-24

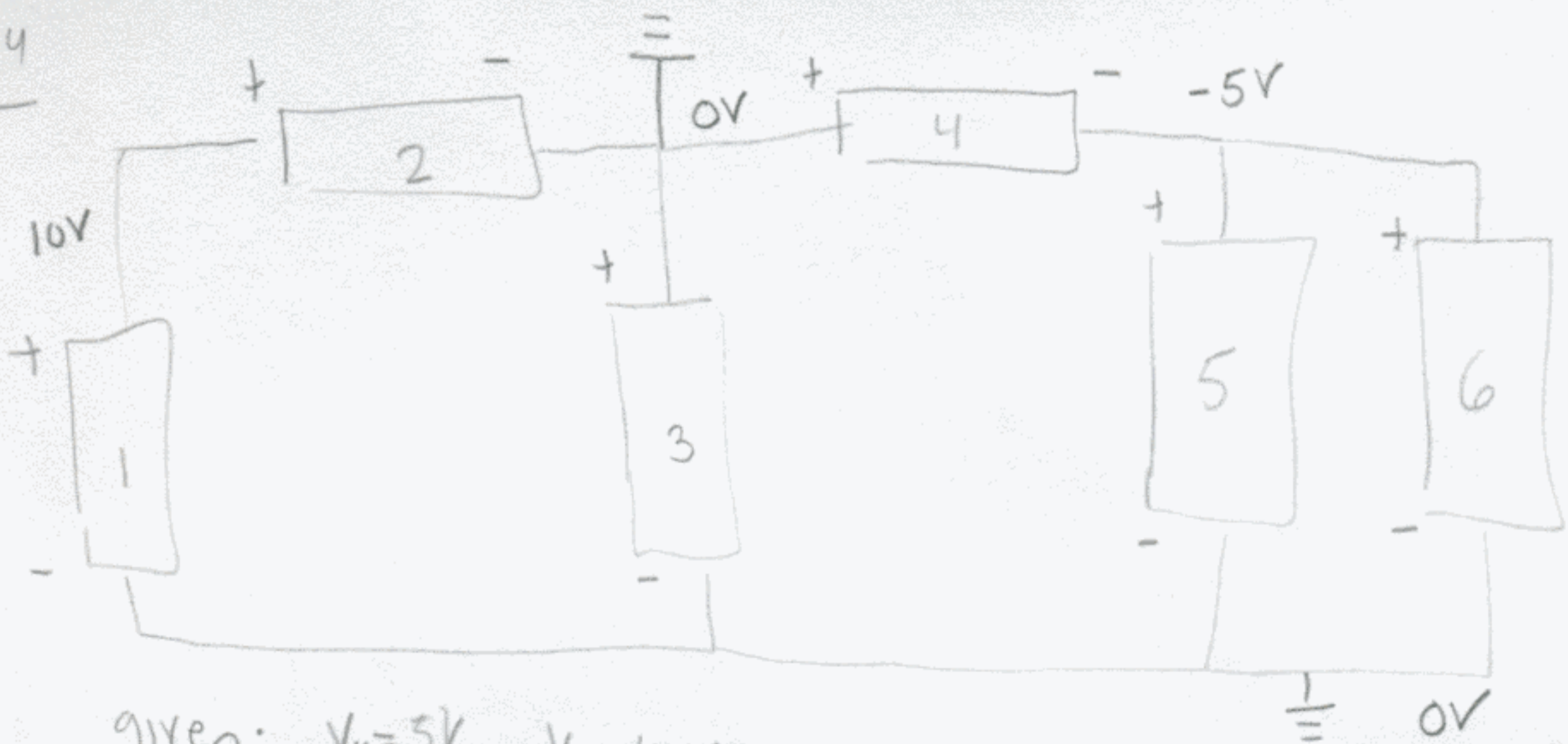

given:  $V_4 = 5V$ ,  $V_1 = 10V$

$$V_2 = 10V$$

$$V_3 = 0V$$

$$V_5 = V_6 = -5V$$

2.2

$$P = I^2 R, \quad P = 12 \times 10^{-3} \text{ W}, \quad R = 6.2 \times 10^3$$

$$I = \sqrt{\frac{P}{R}} = \sqrt{\frac{12 \times 10^{-3}}{6.2 \times 10^3}} = \boxed{1.39 \text{ mA}}$$

2.8


$$R \in [10, 100 \times 10^6], \quad V_{\text{max}} = 500 \text{ V}, \quad P_{\text{max}} = \frac{1}{4} \text{ W}$$

$$P = \frac{V^2}{R} \quad R_{\text{crit}} = \frac{V_{\text{max}}^2}{P_{\text{max}}} = \frac{4 \cdot (500)^2}{1/4} = 10^6 = \boxed{1 \text{ M}\Omega = R_{\text{crit}}}$$

for  $R < R_{\text{crit}}$ ,  $\frac{V_{\text{max}}^2}{R} > P_{\text{max}}$ , so power is the limiting rating

for  $R > R_{\text{crit}}$ ,  $R \cdot P_{\text{max}} > V_{\text{max}}^2$ , so voltage is the limiting rating

2.14

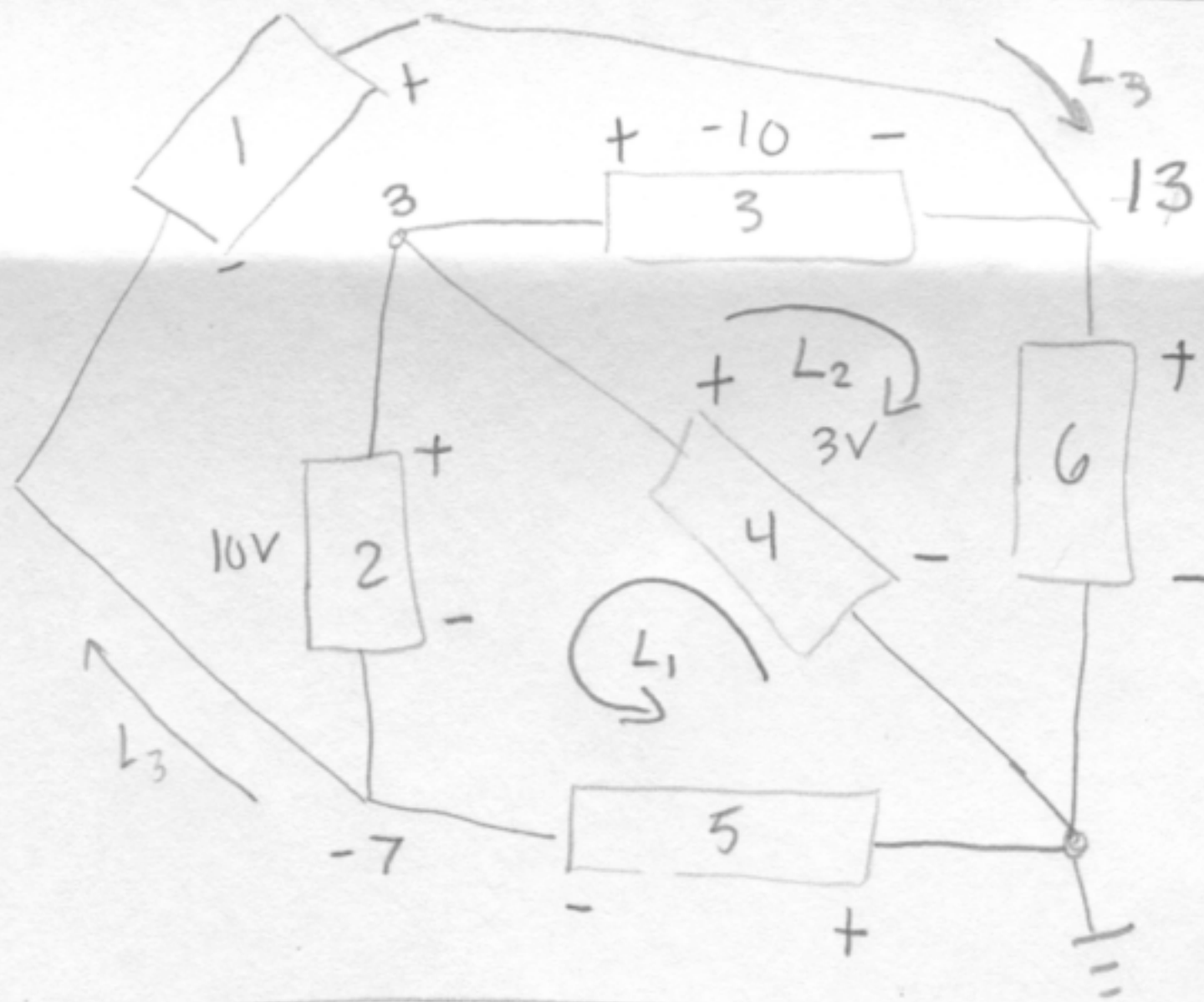

Given:  $V_2 = 10 \text{ V}$   
 $V_3 = -10 \text{ V}$   
 $V_4 = 3 \text{ V}$

Find:  $V_1, V_5, V_6$

$$\boxed{V_1 = 20 \text{ V}, \quad V_5 = 7 \text{ V}, \quad V_6 = 13 \text{ V}}$$


$$\text{KVL for } L_1: \quad -V_4 + V_2 - V_5 = 0 \quad \Rightarrow V_5 = 7 \text{ V}$$

$$\text{KVL for } L_2: \quad -V_4 + V_3 + V_6 = 0 \quad \Rightarrow V_6 = 13 \text{ V}$$

$$\text{KVL for } L_3: \quad -V_1 + V_6 + V_5 = 0 \quad \Rightarrow V_1 = 20 \text{ V}$$

(perimeter)

2-17

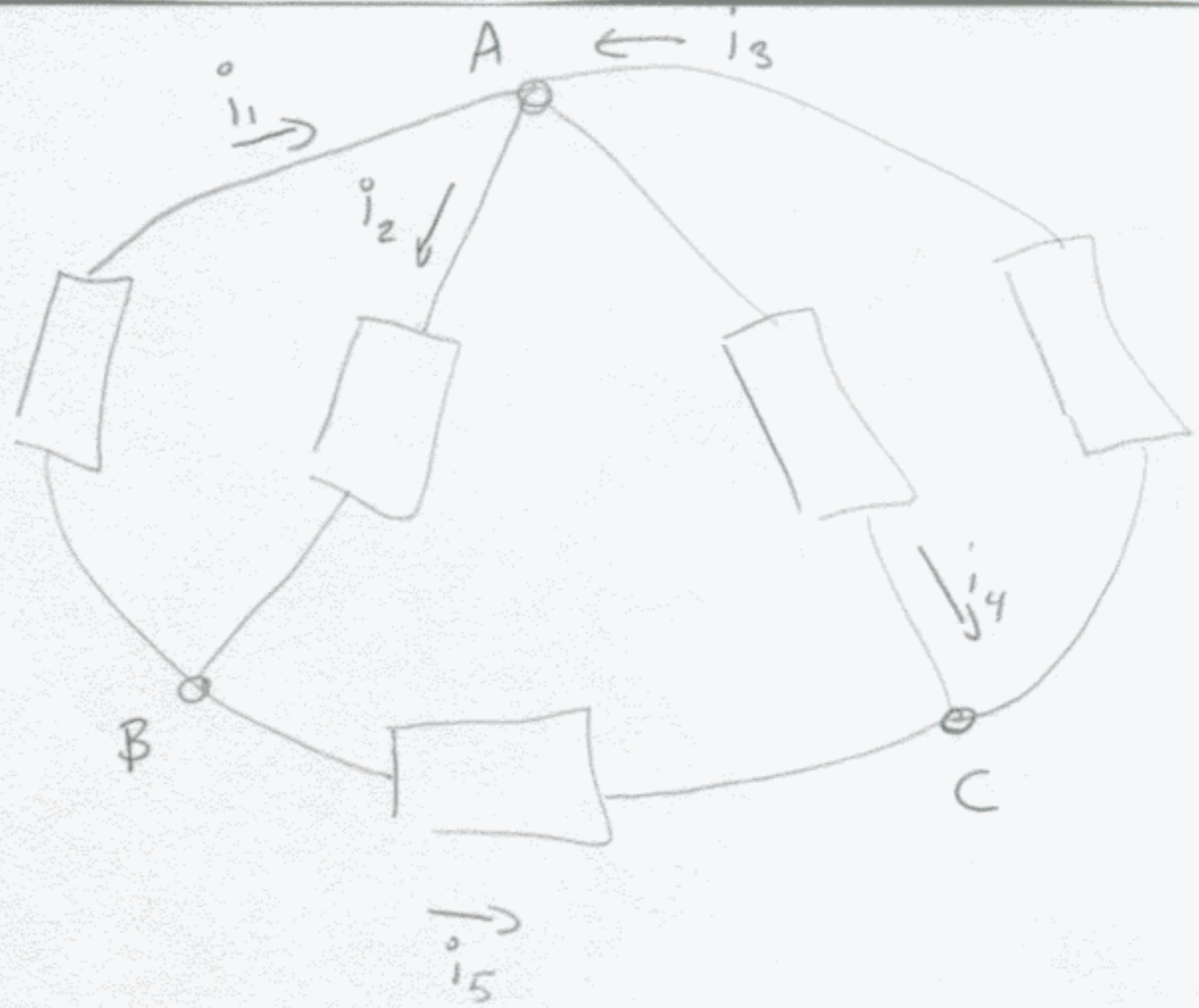


$i_2 = 10 \text{ mA}$ ,  $i_3 = -15 \text{ mA}$ ,  $i_4 = 5 \text{ mA}$  Find  $i_1$  &  $i_5$

at A:  $i_{in} = i_{out}$   $i_1 + i_3 = i_2 + i_4$   
 $i_1 - 15 = 10 + 5 \Rightarrow i_1 = 30 \text{ mA}$

at B:  $i_{in} = i_{out}$   $i_2 = i_1 + i_5$   
 $10 = 30 + i_5 \Rightarrow i_5 = -20 \text{ mA}$

2-23

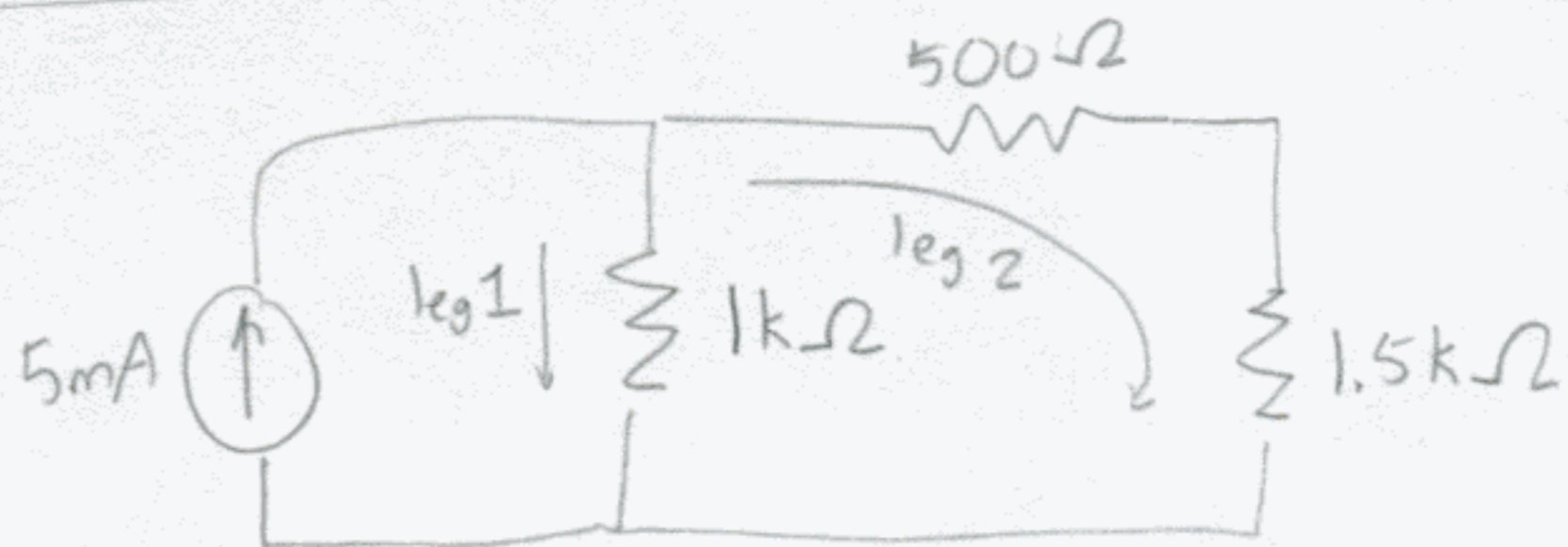

Find the power dissipated in the  $1.5 \text{ k}\Omega$  resistor.


$$R_{eq} = \frac{1}{\frac{1}{1000} + \frac{1}{2000}} = \frac{1}{\frac{2}{2000} + \frac{1}{2000}} = \frac{2000}{3} = 666.67 \Omega$$

$$V = IR = 5 \times 10^{-3} \cdot 666.67 = 3.33 \text{ V dropped across each leg}$$

current through leg 2:  $I = \frac{V}{R} = \frac{3.33}{2000} = 1.67 \text{ mA}$

power through resistor:  $P = I^2 R = (1.67 \times 10^{-3})^2 \cdot 1.5 \times 10^3 = 4.167 \text{ mW}$

2-25

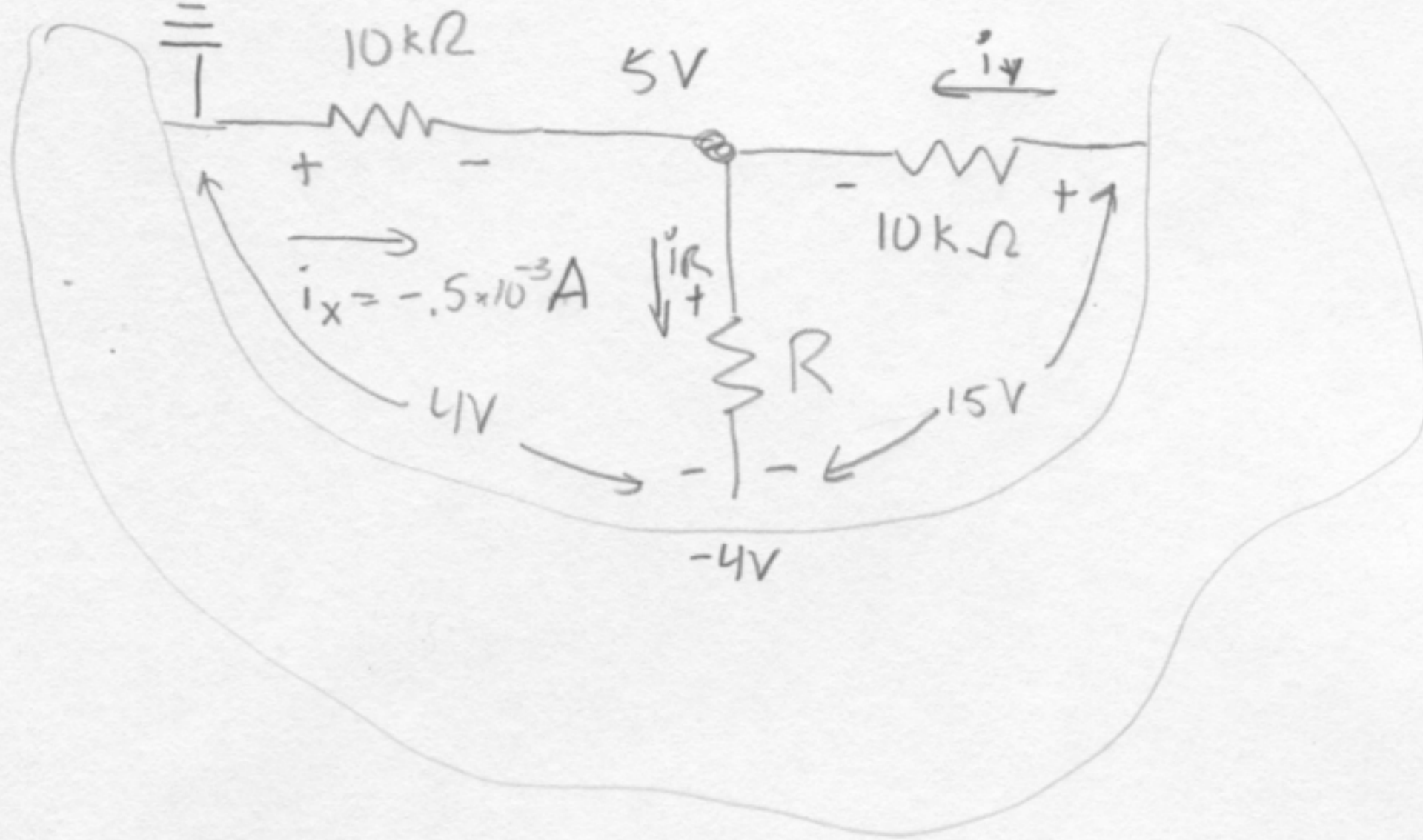

Find R.

voltage across left resistor  $V = iR = -0.5 \times 10^{-3} \times 10 \times 10^3 = -5V$

(Ohm's)

voltage across R is  $5 - (-4) = 9V$

(KVL)

voltage across right resistor  $V_R + V_{right} = 15$   $V_{right} = 6$

(KVL)

current through right resistor:  $i = \frac{V}{R} = \frac{6}{10 \times 10^3} = 6 \times 10^{-4} A$

(Ohm's)

current through R:  $i_{in} = i_{out}$

(KCL)



$$i_R = i_y + i_x$$

$$= -0.5 \times 10^{-3} + 0.6 \times 10^{-3}$$


$$= 0.1 \times 10^{-3} A$$

$$R = \frac{V}{I} = \frac{9}{0.1 \times 10^{-3}} = 90 k\Omega$$

2-28 Find Req

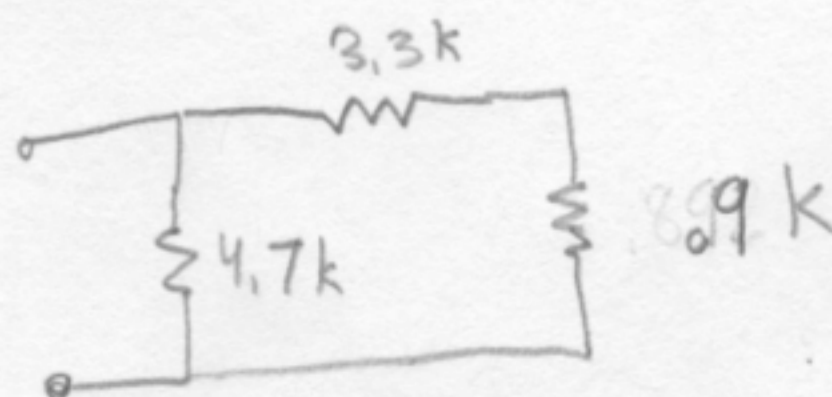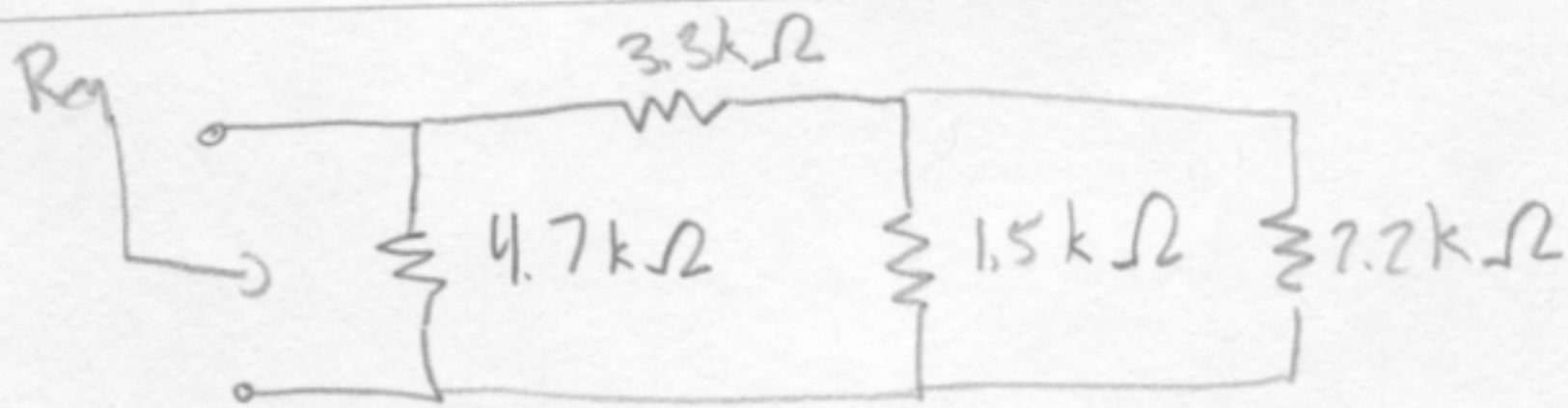
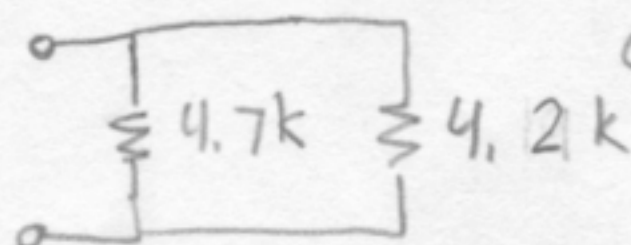
$$\frac{1}{\frac{1}{1.5k} + \frac{1}{2.2k}}$$



$$R_{eq} = \frac{1}{\frac{1}{4.2k} + \frac{1}{4.7k}} = 2.2k\Omega$$

