


HW #6: solutions

Problem 4-20:

Goal: Achieve $v_{out} = -100v_s$ by using circuits (1) & (2).

Possibilities: to either have [source - circuit 2 - circuit 1] or [source - circuit 1 - circuit 2]

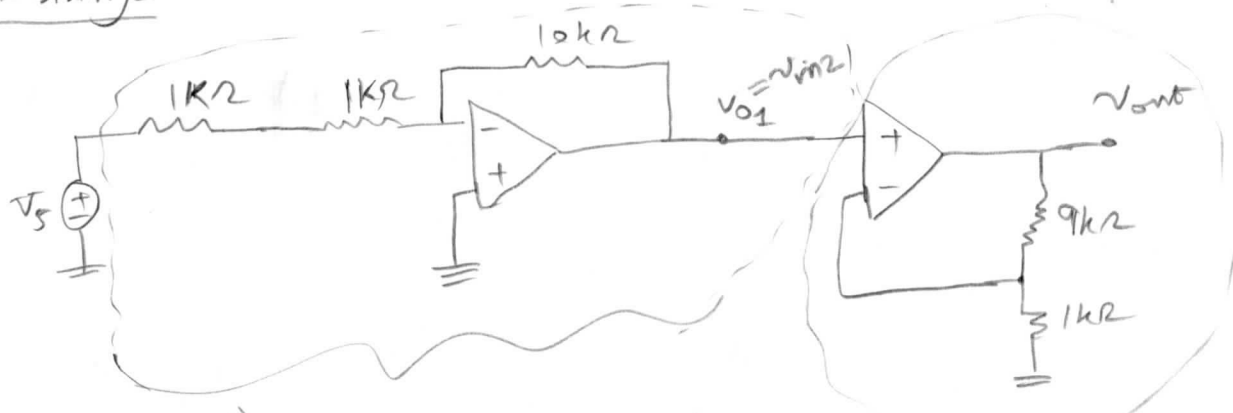possibility 1: source - circuit 2 - circuit 1:



acts as an inverting op-amp

w/ $R_1 = 2k\Omega$ & $R_2 = 10k\Omega$

$$v_{o1} = -\frac{10}{2} v_s = -5v_s$$

acts as a non-inverting op-amp


w/ $R_1 = 9k\Omega$ & $R_2 = 1k\Omega$

$$v_{out} = \frac{9+1}{1} v_{in2} = 10v_{in2}$$

$$v_{out} = -50v_s$$

It's not appropriate, we need -100 as our total gain

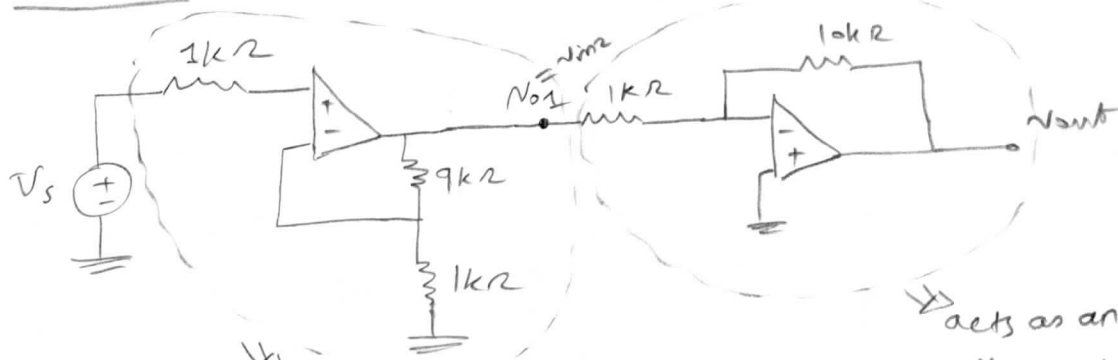possibility 2: source - circuit 1 - circuit 2:



acts as a non-inverting op-amp

w/ $R_1 = 9k\Omega$ & $R_2 = 1k\Omega$

$$v_{o1} = \frac{9+1}{1} v_s = 10v_s$$

acts as an inverting op-amp


w/ $R_1 = 1k\Omega$, $R_2 = 10k\Omega$

$$v_{out} = -\frac{10}{1} v_{in2}$$

$v_{out} = -100v_s$ ✓ it's appropriate design

4-22°

find range of gain v_o/v_s °

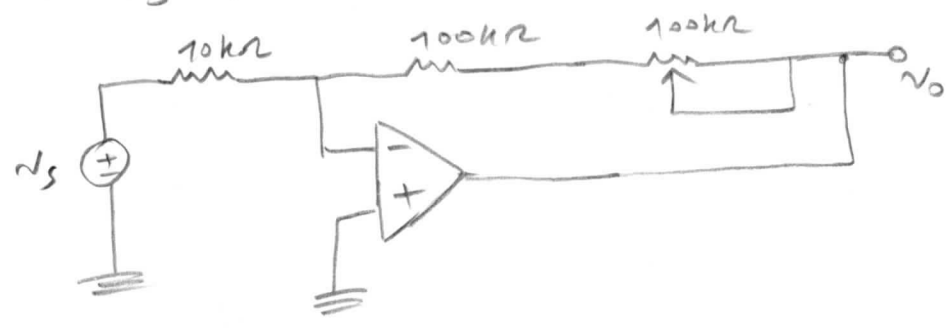


≡ inverting op-amp
 $R_1 = 10k\Omega$
 $R_2 = 100 + \alpha k\Omega$
 where $\alpha \in [0, 100]k\Omega$

$$\Rightarrow \frac{v_o}{v_s} = - \left(\frac{100 + \alpha}{10} \right) = -10 - \frac{\alpha}{10} \Rightarrow \begin{cases} \max(\frac{v_o}{v_s}) = -10 - \frac{\alpha}{10} \Big|_{\alpha=0} = -10 \\ \min(\frac{v_o}{v_s}) = -10 - \frac{\alpha}{10} \Big|_{\alpha=100} = -20 \end{cases}$$

$$\Rightarrow \boxed{-20 \leq \frac{v_o}{v_s} \leq -10} : \text{range of gain}$$

4-24° [one way]

Given:

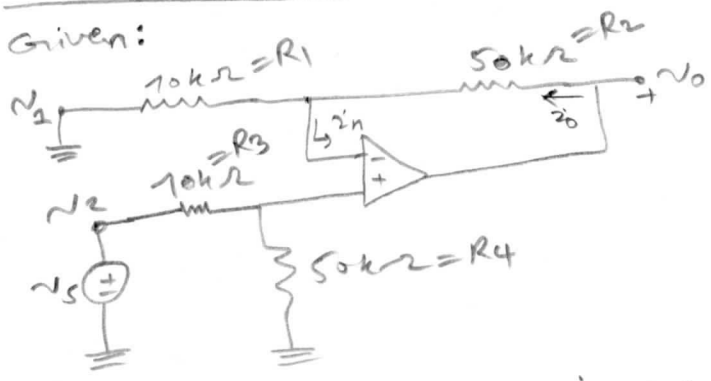

find v_o in terms of v_s
 - find i_o for $v_s = 2V$

(a) we note that this circuit is a subtractor, so we have:

$$\begin{matrix} v_1 \rightarrow & \boxed{k_1} & \oplus & \rightarrow & v_o \\ v_2 \rightarrow & \boxed{k_2} & \oplus & \rightarrow & \end{matrix} \quad \text{where: } k_1 = -\frac{R_2}{R_1} = -\frac{50}{10} = -5$$


$$k_2 = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) = \left(\frac{10 + 50}{10} \right) \left(\frac{50}{10 + 50} \right)$$

$$\Rightarrow k_2 = 5$$

$$\Rightarrow v_o = k_1 v_1 + k_2 v_2 = 5v_2 - 5v_1 \quad \left. \begin{matrix} \text{where } v_1 = 0 \\ v_2 = v_s \end{matrix} \right\} \Rightarrow \boxed{v_o = 5v_s}$$

(b) $i_{in} = 0$ (basic op-amp property) $\Rightarrow i_o = \frac{v_o}{R_1 + R_2} = \frac{v_o}{10 + 50} \xrightarrow{v_o = 5v_s} i_o = \frac{5}{60} v_s \xrightarrow{v_s = 2V} \boxed{i_o = \frac{1}{6} mA}$

4-24° [Alternative way]

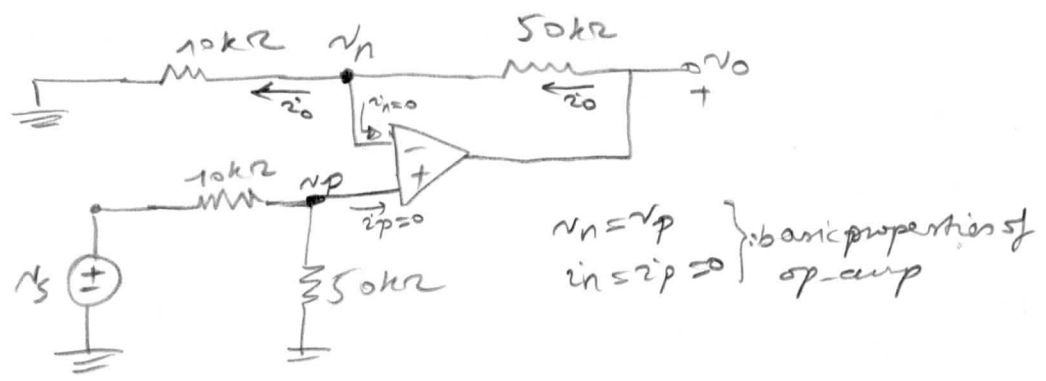

We find v_p by using voltage division trick:

$$v_p = \frac{50}{50+10} v_s = \frac{5}{6} v_s \Rightarrow \boxed{v_n = v_p = \frac{5}{6} v_s} \quad (1)$$

Having found v_n , we can find i_o , noting that 10kR is grounded:

$$i_o = \frac{+v_n}{10} \xrightarrow{(1)} \boxed{i_o = +\frac{5}{60} \frac{v_s}{\text{mA}}} \quad (2)$$

on the other hand voltage drop across 50kR:



$$i_o \times 50 = v_o - v_n \Rightarrow v_o = v_n + 50 i_o \xrightarrow{(1)} \frac{(2)}{(2)} \frac{5}{6} v_s + 50 \left(\frac{5}{60} v_s \right)$$

$$\Rightarrow v_o = \left(\frac{5}{6} + \frac{25}{6} \right) v_s \Rightarrow \boxed{v_o = 5 v_s}$$

Therefore, given $v_s = 2 \text{ [V]} \Rightarrow i_o = \frac{5}{60} \times 2 \Rightarrow \boxed{i_o = \frac{1}{6} \text{ mA}}$

4-27

3 input inverting summer:

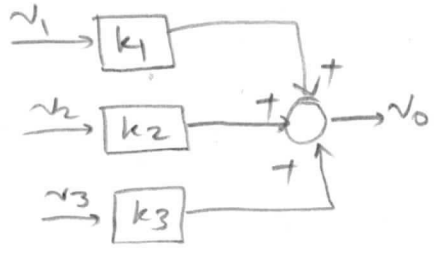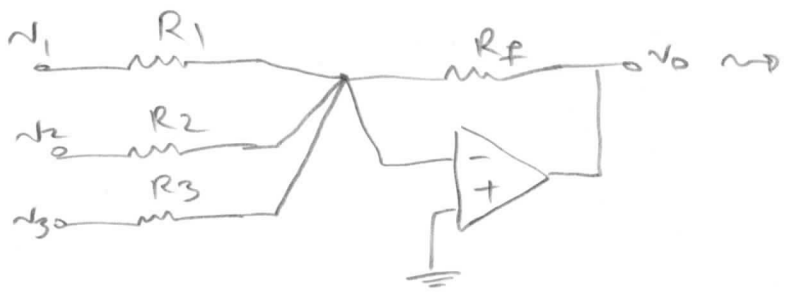

$$\Rightarrow v_0 = k_1 v_1 + k_2 v_2 + k_3 v_3 = -\frac{R_f}{R_1} v_1 - \frac{R_f}{R_2} v_2 - \frac{R_f}{R_3} v_3$$

$$\Rightarrow v_0 = -R_f \left(\frac{1}{R_1} v_1 + \frac{1}{R_2} v_2 + \frac{1}{R_3} v_3 \right)$$


given: $\left\{ \begin{array}{l} R_f = 100 \text{ k}\Omega \\ v_0 = -[v_1 + 10v_2 + 100v_3] \end{array} \right.$

$$\Rightarrow \frac{R_f}{R_1} = 1 \Rightarrow R_1 = 100 \text{ k}\Omega$$


$$\frac{R_f}{R_2} = 10 \Rightarrow R_2 = 10 \text{ k}\Omega$$

$$\frac{R_f}{R_3} = 100 \Rightarrow R_3 = 1 \text{ k}\Omega$$

4-28

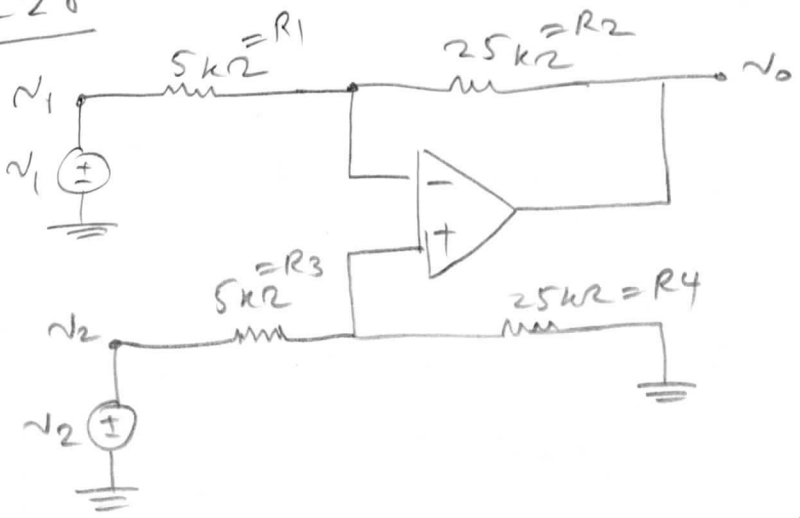

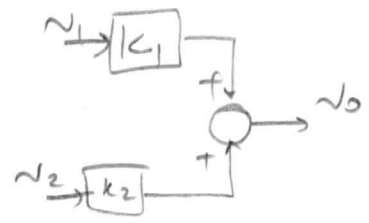note that it is a subtractor circuit, i.e., differential op-amp, so we get:



$$\text{where } k_1 = -\frac{R_2}{R_1} = -\frac{25}{5} = -5$$


$$k_2 = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) = \left(\frac{5 + 25}{5} \right) \left(\frac{25}{5 + 25} \right)$$

$$\Rightarrow k_2 = 5$$

$$\Rightarrow v_0 = k_1 v_1 + k_2 v_2 = 5v_2 - 5v_1$$

4-31°

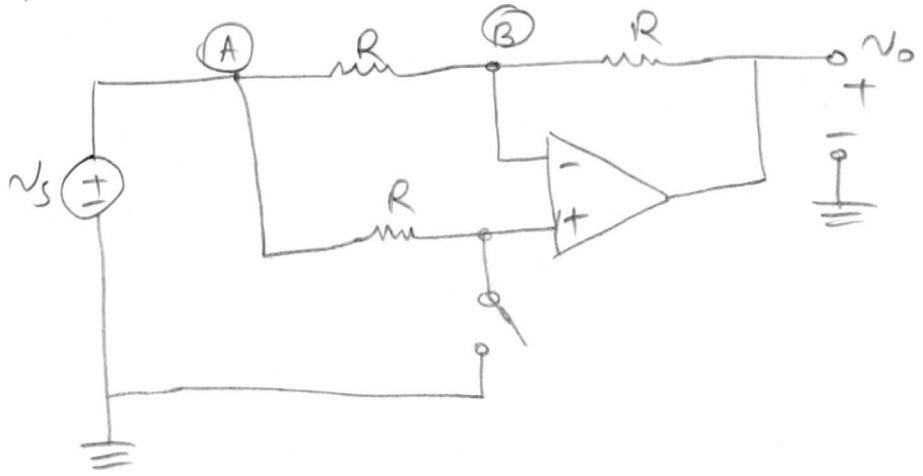The claim is false, as it is discussed below:



Switch is open:

basic op-amp properties: $v_n = v_p$, $i_p = i_n = 0 \Rightarrow \left. \begin{aligned} v_A = v_B = v_s \\ \frac{v_B - v_o}{R} = 0 \Rightarrow v_B = v_o \end{aligned} \right\} \Rightarrow v_o = v_s$


It disproves the 2nd statement of the claim

Switch is closed:

$v_p = v_n = v_B = 0$
 $(i_n = 0 \Rightarrow \frac{v_A - v_B}{R} = \frac{v_B - v_o}{R})$
 $v_A = v_s$

$\Rightarrow v_o = -v_s$ → It disproves the 1st statement of the claim

4-32°

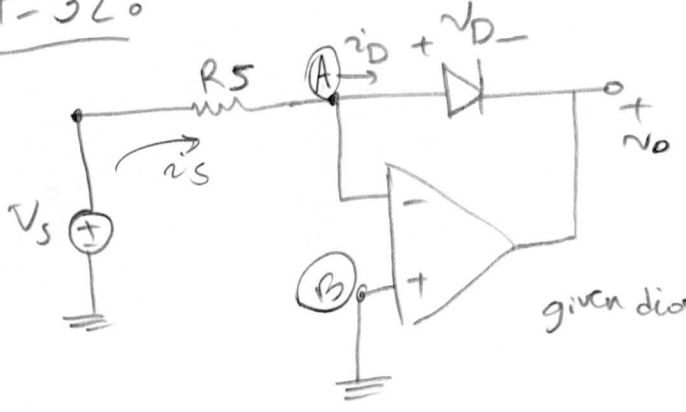

$i_n = i_p = 0 \Rightarrow v_s = v_o$
 $v_p = v_n \Rightarrow v_A = v_B = 0$

$i_s = \frac{v_s - v_o}{R_s}$

given diode eqn: $i_D = I_0 (e^{v_D/V_T} - 1)$


$\Rightarrow \frac{v_s}{R_s} = I_0 (e^{\frac{v_D}{V_T}} - 1)$
 $v_D = v_A - v_o = 0 - v_o$

$\frac{v_s}{R_s} = I_0 (e^{-\frac{v_o}{V_T}} - 1) (*)$

from eq'n (*) : $\frac{V_s}{I_0 R_s} = e^{-\frac{V_0}{V_T}} - 1 \Rightarrow -\frac{V_0}{V_T} = \ln\left(\frac{V_s}{I_0 R_s} + 1\right)$

$\Rightarrow V_0 = -V_T \ln\left(\frac{V_s}{R_s I_0} + 1\right)$

4-36:

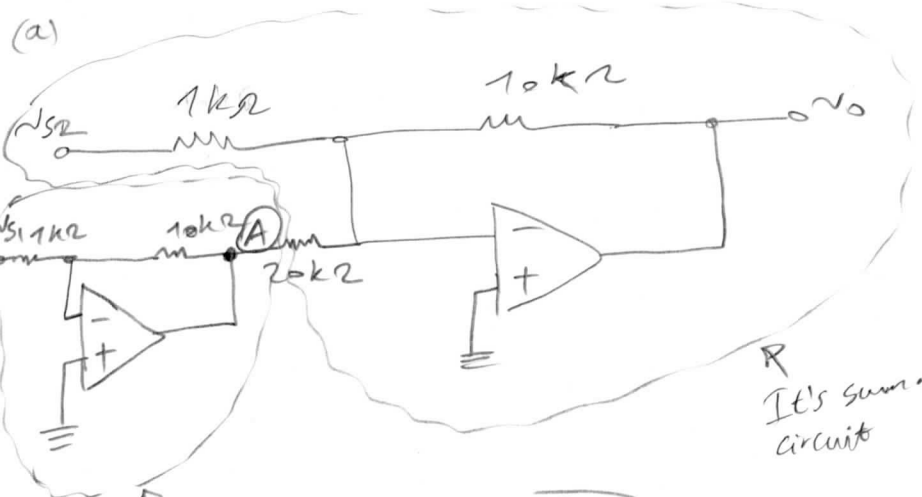

It's an inverting op-amp $\Rightarrow V_A = -\frac{10}{1} V_{S1}$

It's summer circuit


$\Rightarrow V_0 = \left(-\frac{10}{1}\right) V_{S2} + \left(\frac{-10}{20}\right) V_A$
 $= -10V_{S2} - \frac{1}{2} V_A$

$\Downarrow V_A = -10V_{S1}$

$V_0 = -10V_{S2} - \frac{1}{2} (-10V_{S1})$

$\Downarrow V_0 = 5V_{S1} - 10V_{S2} \quad (*)$

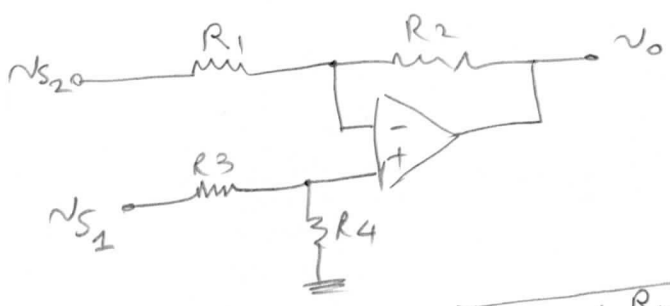(b) As an alternative way, we can use subtractor circuit :



for which we have :

$V_0 = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{S1} - \left(\frac{R_2}{R_1}\right) V_{S2} \quad (**)$

Comparing eqns (*) & (**):


$$5 = \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \Rightarrow 5 = \left(\frac{R_1 + 10R_1}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \Rightarrow \boxed{\frac{R_3}{R_4} = \frac{6}{5}} \quad (**)$$

$$-1 = -\frac{R_2}{R_1} \Rightarrow \boxed{R_2 = 10R_1} \quad (*)$$

therefore, subtractor circuit w/ $R_1 = 1 \text{ k}\Omega$; $R_2 = 10 \text{ k}\Omega$; $R_3 = 6 \text{ k}\Omega$; $R_4 = 5 \text{ k}\Omega$, would yield the same result. [these values are some typical values, so any values which satisfy (*) & (**) are correct]

4-41

let's consider an inverting op-amp:

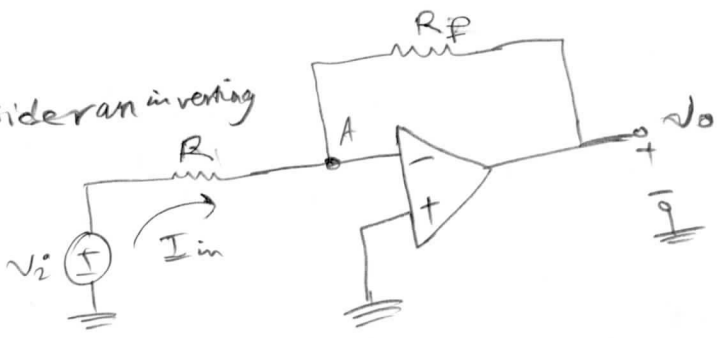

for this opamp we have:

$$K = \frac{V_o}{V_i} = -\frac{R_f}{R}$$

From which

The restrictions of the problem are:

- $R > 10 \text{ k}\Omega$
- R, R_f : 5% resistance values $< 300 \text{ k}\Omega$
- voltage gain: $K = -\frac{R_f}{R} = -10$

therefore, we can pick:

$$R_f = 200 \text{ k}\Omega < 300 \text{ k}\Omega$$

and so, $R = 20 \text{ k}\Omega$, which is a 5% resistance value $> 10 \text{ k}\Omega$ which also satisfies $R_f/R = 10$.


[In order to pick 5% resistor values refer to standard values ^{table} at the end of book].

Other values for R & Rf are not unique, so long as the requirements are met, it is fine

4-45°

goal: using 2 op-amps w/ inputs v_1, v_2, v_3 ;
to get: $v_o = -3v_1 + 2v_2 - 5v_3$

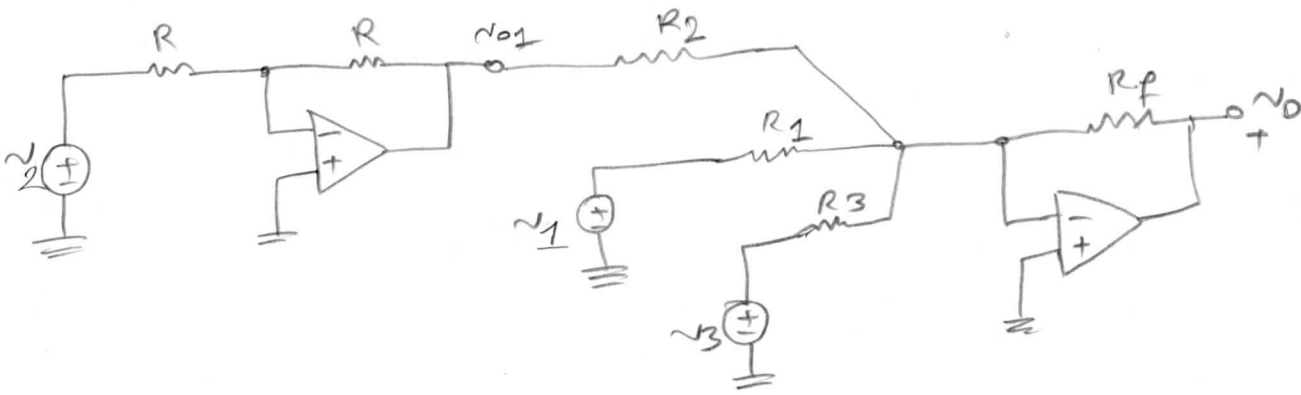one possibility is to put one inverting & one summer in series:



$$v_{o1} = -\frac{R}{R} v_2 = -v_2$$

$$v_o = \left(-\frac{R_f}{R_2}\right) v_{o1} + \left(-\frac{R_f}{R_1}\right) v_1 + \left(-\frac{R_f}{R_3}\right) v_3$$

$$\Rightarrow v_o = +\frac{R_f}{R_2} v_2 - \frac{R_f}{R_1} v_1 - \frac{R_f}{R_3} v_3$$

Need: $v_o = 2v_2 - 3v_1 - 5v_3$

$$\Rightarrow \frac{R_f}{R_2} = 2; \quad \frac{R_f}{R_1} = 3; \quad \frac{R_f}{R_3} = 5$$

So, we can pick:

- $R = 1 \text{ k}\Omega$
- $R_f = 30 \text{ k}\Omega$
- $R_2 = 15 \text{ k}\Omega$
- $R_1 = 10 \text{ k}\Omega$
- $R_3 = 6 \text{ k}\Omega$

[these are some typical values, so long as the fractions are satisfied, it would be fine]