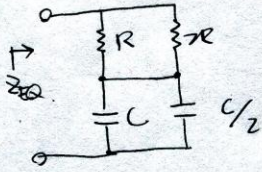


10.2



By observing the circuit: we have  $R$  &  $2R$  in parallel  
 $C$  &  $C/2$  in parallel


$$R // 2R = \frac{2R^2}{R+2R} = \frac{2R}{3}$$

$$\frac{1}{Cs} // \frac{2}{Cs} = \frac{\frac{1}{Cs} \cdot \frac{2}{Cs}}{\frac{1}{Cs} + \frac{2}{Cs}} = \frac{2}{3Cs}$$


$$Z_{EQ} = \frac{2R}{3} + \frac{2}{3Cs} = \frac{2RCs + 2}{3Cs}$$

poles:  $s = 0$

zeros:  $s = \frac{-1}{RC}$

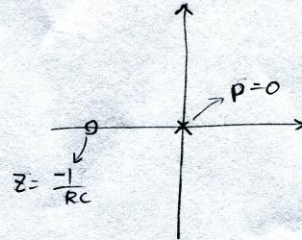

10.4

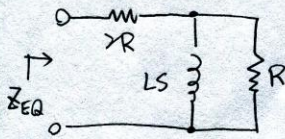


$$LS // R = \frac{LRS}{LS+R}$$


$$Z_{EQ} = 2R + \frac{LRS}{LS+R} = \frac{3LRS + 2R^2}{LS+R}$$

Poles:  $s = \frac{-R}{L}$

zeros:  $s = \frac{-2R}{3L}$

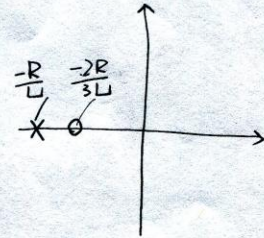

10.6

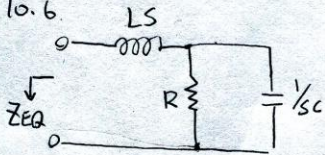

$$Z_{EQ} = LS + R // \frac{1}{Cs}$$

$$= LS + \frac{R}{RCs+1}$$


$$= \frac{LRCs^2 + LS + R}{RCs+1} = \frac{10^{-3}s^2 + 2s + 10^3}{5 \times 10^{-4}s + 1}$$

Poles:  $s = -\frac{1}{RC} = -2 \times 10^3$

Poles of  $Z_{EQ}$ :  $s = -2 \times 10^3$

Zeros:  $s = -1000, -1000$



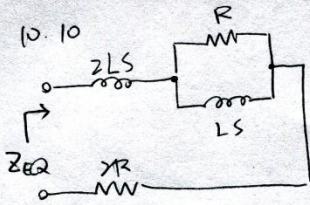

$$Z_{EQ} = 2LS + R // LS + 2R$$

$$= \frac{2L^2S^2 + 5LRS + 2R^2}{LS + R} = \frac{(LS + 2R)(2LS + R)}{LS + R}$$


Poles @  $S = -\frac{R}{L}$

Zeros @  $S = -\frac{2R}{L}$ , &  $-\frac{R}{2L}$

Select value to set  $S = -\frac{R}{L} = -2000 \Rightarrow R = 2000L$

We can choose  $L = 1H$  &  $R = 2k\Omega$

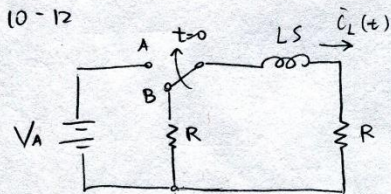
Zeros of  $Z_{EQ}$  will be:  $-4000$  &  $-1000$  rad/s respectively



$Z = LS + R$       $I_L(S) = \frac{V_A}{Z} = \frac{V_A}{LS + R} = \frac{V_A/L}{S + R/L}$

The switch has been in B for a long time  $\Rightarrow \dot{i}_L(0^-) = 0$

Change switch to A, circuit becomes:

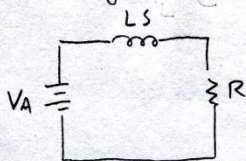

$V_A(S) = \frac{V_A}{S}$   
 $Z = LS + R$

$I_L(S) = \frac{V_A(S)}{LS + R} = \frac{V_A}{S \cdot (LS + R)} = \frac{A}{S} + \frac{B}{S + \frac{R}{L}}$


A =  $I_L(S) \cdot S \Big|_{S=0} = \frac{V_A}{R}$

B =  $I_L(S) \cdot (S + \frac{R}{L}) \Big|_{S = -\frac{R}{L}} = -\frac{V_A}{R}$

$\Rightarrow \dot{i}_L(t) = \frac{V_A}{R} (1 - e^{-\frac{R}{L}t}) u(t)$




10.17

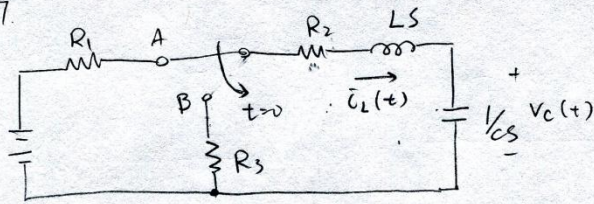

Switch @ A for a long time  $\rightarrow \tilde{i}_L(0) = 0, V_C(0) = V_A$

(a) Switch to B circuit become :

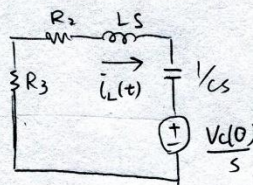

$$Z_{eq} = R_2 + R_3 + LS + \frac{1}{CS} = \frac{LCS^2 + (R_2 + R_3)CS + 1}{CS}$$

$$I_L(s) = -\frac{V_C(0)}{s} / Z_{eq} = \frac{-V_A \cdot CS}{LCS^2 + (R_2 + R_3)CS + 1}$$

(c) For  $R_1 = R_3 = 500 \Omega, R_2 = 1 \text{ k}\Omega, L = 250 \text{ mH}, C = 4 \mu\text{F}, V_A = 15 \text{ V}$ .


$$I_L(s) = \frac{-6 \times 10^{-5}}{10^{-6} s^2 + 6 \times 10^{-3} s + 1} = \frac{-60}{s^2 + 6 \times 10^3 s + 10^6} = \frac{A}{s + 5828.5} + \frac{B}{s + 171.6}$$

solve the equation we have:  $A = 10.61$  &  $B = -10.61$

$$\tilde{i}_L(t) = 10.61 [e^{-5828.5t} - e^{-171.6t}] u(t) \text{ mA}$$



10-19.

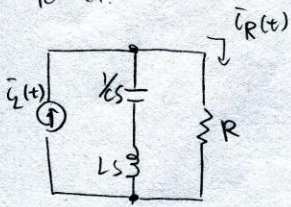


$$\frac{I_R(s)}{I_L(s)} = \frac{LCs^2 + 1}{LCs^2 + RCs + 1}$$

look for formula of current division


$$I_R(s) = I_L(s) \cdot \frac{1/R}{1/R + 1/(Cs + Ls)}$$

$$= I_L(s) \cdot \frac{1/R}{1/R + Cs/LCs^2 + 1} = I_L(s) \cdot \frac{LCs^2 + 1}{LCs^2 + RCs + 1}$$

10-24

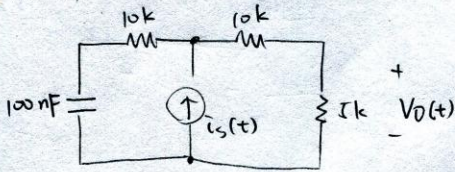

↓

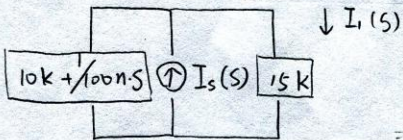

$$I_1(s) = I_S(s) \cdot \frac{1/5k}{1/5k + 1/(10k + 100nFs)} = I_S \cdot \frac{10^{-3}s + 1}{2.5 \times 10^3 s + 1}$$

$$V_O(s) = I_1(s) \cdot \frac{0.4s + 400}{s + 400}$$

$$= \frac{10^{-3}s + 1}{(s + 400)^2} = \frac{10^{-3}}{s + 400} + \frac{0.6}{(s + 400)^2}$$

$$i_S(t) = 2.5 e^{-400t} \times 10^{-3} u(t)$$


$$I_S(s) = \frac{2.5 \times 10^{-3}}{s + 400}$$

$$V_O(s) = I_1(s) \cdot 5k = \frac{5}{s + 400} + \frac{3 \times 10^3}{(s + 400)^2}$$


$$V_O(t) = [5 e^{-400t} + 3 \times 10^3 \cdot t \cdot e^{-400t}] \cdot u(t)$$



10.27

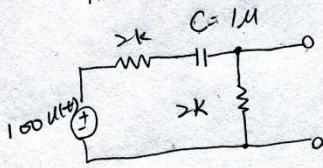

Short circuit:

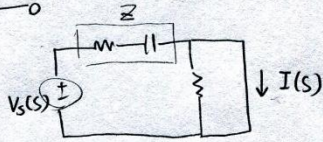


where  $V_S(s) = \frac{100}{s}$

$$Z = 2k + \frac{1}{1\mu S} = \frac{2 \times 10^{-3} s + 1}{10^{-6} s}$$

$$I_N(s) = \frac{V_S(s)}{Z} = \frac{100 \cdot 10^{-6} s}{s(2 \times 10^{-3} s + 1)} = \frac{0,05}{s + 500}$$


Open circuit:

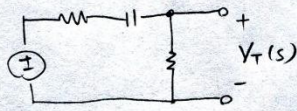

$$V_T(s) = V_S \cdot \frac{2k}{2k + 2k + \frac{1}{1\mu S}} = \frac{50}{s + 250}$$

$$Z = \frac{V_T(s)}{I_N(s)} = \frac{10000(s + 500)}{s + 250}$$


⇒ Thevenin

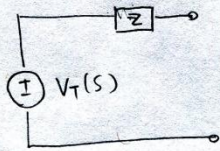

where  $V_T = \frac{50}{s + 250}$

$$Z = \frac{10000(s + 500)}{s + 250}$$

10.28

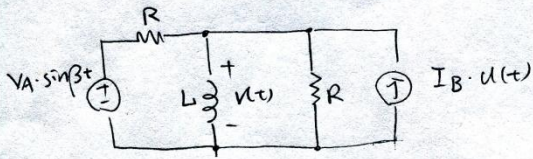


$$V_S(s) = V_A \cdot \frac{\beta}{s^2 + \beta^2}$$

$$I_S(s) = \frac{I_B}{s}$$

no. initial energy using superposition.


① turn on  $V_S$  turn off  $I_S$

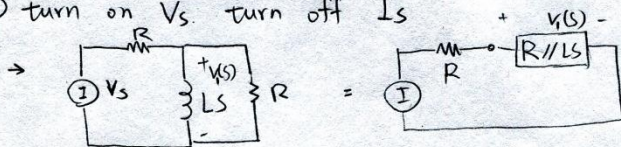

$$V_L(s) = V_S \cdot \frac{R // LS}{R + R // LS} = \frac{V_A \beta}{s^2 + \beta^2} \cdot \frac{LS}{2LS + R}$$



② turn on  $I_s$  turn off  $V_s$

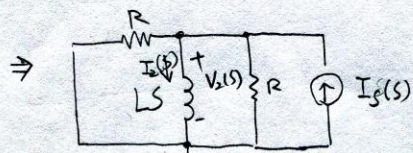

$$I_2(s) = I_s \cdot \frac{1/LS}{1/LS + 1/R + 1/R}$$

$$= \frac{I_B}{s} \cdot \frac{R}{2LS + R}$$

$$V_2(s) = I_2(s) \cdot LS = \frac{I_B \cdot L \cdot R}{2LS + R}$$

Apply superposition :

$$V(s) = V_1(s) + V_2(s)$$

$$= \frac{V_A \beta}{s^2 + \beta^2} \cdot \frac{LS}{2LS + R} + \frac{I_B LR}{2LS + R}$$

$$= \frac{I_B LR s^2 + V_A \beta L s + I_B LR \beta^2}{(2LS + R)(s^2 + \beta^2)}$$

forced poles :  $s = \pm j\beta$

Natural pole :  $s = -\frac{R}{2L}$