

MAE 140 HW 1. solution

1-15.
$$\bar{i}(t) = \begin{cases} 0 & t < 0 \\ 3e^{-2t} & t \geq 0 \end{cases}$$


for $t > 0$, $q(t) = \int_0^t 3e^{-2\tau} d\tau = -\frac{3}{2}e^{-2\tau} \Big|_0^t = \frac{3}{2}(1 - e^{-2t})$ (C)

1-18. $P = i \cdot V$ (power = current \times voltage)

$W = P \cdot t$ (Energy = power \times time)

$$\Rightarrow t = \frac{W}{P} = \frac{W}{\bar{i} \cdot V} = \frac{237.5 \times 10^3}{15 \times 10^{-3} \times 6} = 2.64 \times 10^6 \text{ (s)} = 30.5 \text{ days}$$

1-21

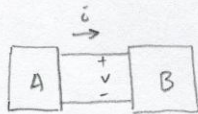

use passive sign convention.

$P_B = \bar{i} \cdot V$ $P_A = -\bar{i} \cdot V$

Power is transferred

a) $V = 11V, \bar{i} = -1.1A$ $P_A = 12.1W, P_B = -12.1W$

B \rightarrow A

b) $V = 80V, \bar{i} = 20mA$ $P_A = -1.6W, P_B = 1.6W$

A \rightarrow B

c) $V = -120V, \bar{i} = -12mA$ $P_A = -1.44W, P_B = 1.44W$

A \rightarrow B

d) $V = -1.5V, \bar{i} = -600\mu A$ $P_A = -0.9mW, P_B = 0.9mW$

A \rightarrow B

2-3

$P = \bar{i}^2 \cdot R$ $\bar{i} = \sqrt{\frac{P}{R}} = 1 \text{ mA}$

2-9

$P = \frac{V^2}{R} < 0.125W \Rightarrow |V| < \sqrt{0.125 \cdot R} = 111.8V$

2-12

resistance temperature

5 k Ω

$> 5^\circ C$

$\frac{5000 - 1000}{25 - x} = \frac{5000 - 340}{25 - 100}$

340 Ω

100 $^\circ C$


$\Rightarrow x = 89.4$

1 k Ω

$x^\circ C$


$\Rightarrow x = 89.4$

MAE 140 HW 1 Solution

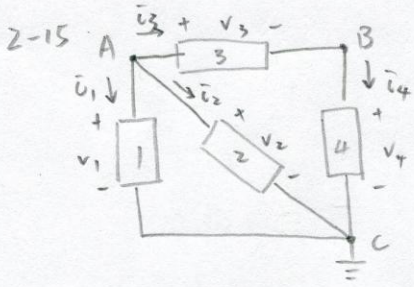

a) nodes : A, B, C.

loops :

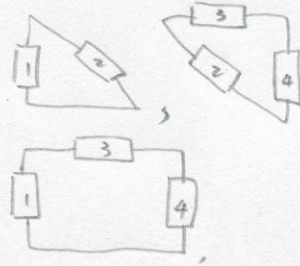

(just 2 of them will be enough)

b) series : 3, 4
parallel : 1, 2

c) KCL: $-\dot{i}_1 - \dot{i}_2 - \dot{i}_3 = 0$,
 $\dot{i}_3 - \dot{i}_4 = 0$
 $\dot{i}_1 + \dot{i}_2 + \dot{i}_4 = 0$


(just two of them will be enough)

KVL: $V_1 - V_2 = 0$

$-V_2 + V_3 + V_4 = 0$


$-V_1 + V_3 + V_4 = 0$

(just two of them will be enough)

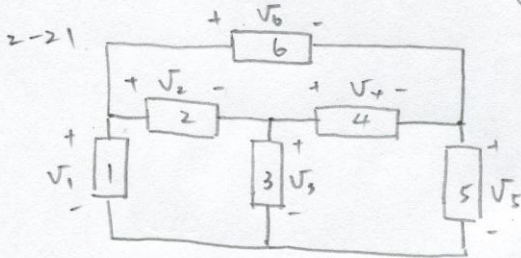

$V_2 = 10, V_4 = 5, V_5 = 15$
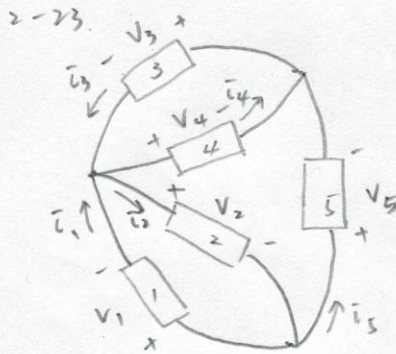
$$\left. \begin{aligned} V_2 + V_4 - V_6 &= 0 \\ V_4 + V_5 - V_3 &= 0 \\ V_2 + V_3 - V_1 &= 0 \end{aligned} \right\} \Rightarrow \begin{aligned} V_6 &= 15 \text{ V} \\ V_3 &= 20 \text{ V} \\ V_1 &= 30 \text{ V} \end{aligned}$$




a) KVL: $V_3 + V_4 = 0$
 $V_1 + V_2 = 0$
 $V_2 + V_5 - V_4 = 0$

$V_1 - V_3 - V_5 = 0$

$V_4 = 0 \Rightarrow V_3 = 0$

$V_2 = -V_5 = -V_1$

MAE 140. HW1. Solution

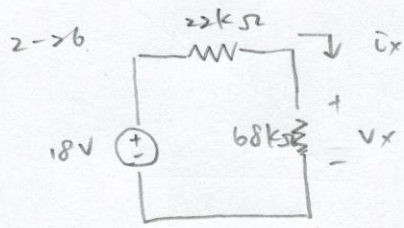

$$i_x = \frac{V}{R_{total}} = \frac{18}{22k + 68k} = 0.2 \text{ mA}$$

$$V_x = 18V \cdot \frac{68k}{68k + 22k} = 13.6 \text{ V.}$$