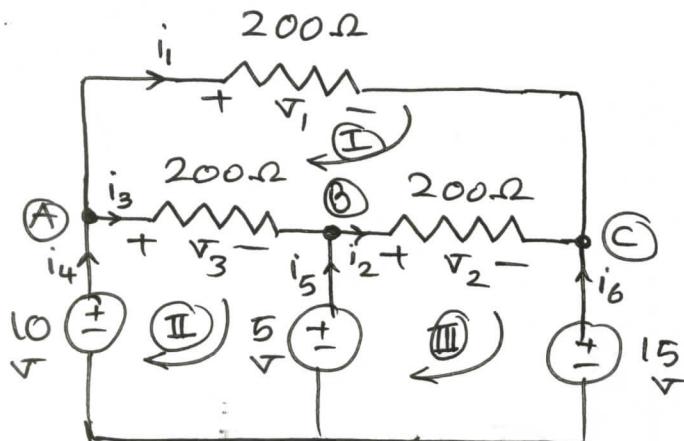


HW #2
MAE140
Fall 2013

2-30

a)



b) Loop I: $V_1 - V_2 - V_3 = 0$

Loop II: $V_3 + 5 - 10 = 0 \Rightarrow V_3 = 5V$

Loop III: $V_2 + 15 - 5 = 0 \Rightarrow V_2 = -10V$

$$\left. \begin{array}{l} \\ \\ \end{array} \right\} \Rightarrow V_1 = -5V$$

c) $V_1 = 200i_1 \Rightarrow i_1 = \frac{-5}{200} = -0.025A$

$$V_2 = 200i_2 \Rightarrow i_2 = \frac{-10}{200} = -0.05A$$


$$V_3 = 200i_3 \Rightarrow i_3 = \frac{5}{200} = 0.025A$$

d) KCL at Node A: $i_4 = i_1 + i_3 = 0A$

KCL at Node B: $i_2 = i_3 + i_5 \Rightarrow i_5 = -0.075A$

KCL at Node C: $i_1 + i_2 + i_6 = 0 \Rightarrow i_6 = 0.075A$

2-32

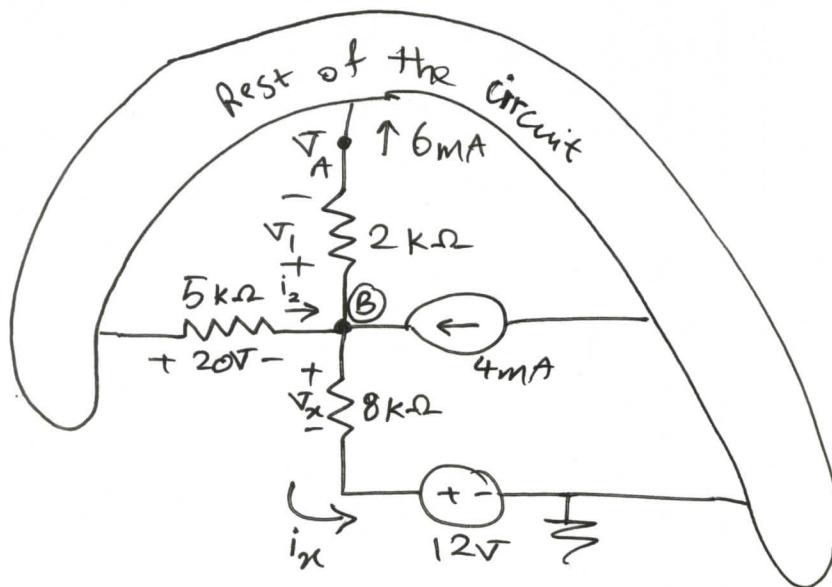

(a) Elements equations

$$\left\{ \begin{array}{l} V_1 = 2 \text{k}\Omega \times 6 \text{mA} = 12 \text{V} \\ 20 \text{V} = 5 \text{k}\Omega i_2 \Rightarrow i_2 = 4 \text{mA} \\ V_x = 8 \text{k}\Omega i_x \end{array} \right.$$

KCL at Node B: $-6 \text{mA} + i_2 + 4 \text{mA} - i_x = 0$
 $\Rightarrow i_x = 2 \text{mA}$

Thus, $V_x = 8 \text{k}\Omega \times 2 \text{mA} = 16 \text{V}$

(b) Sum of the currents into the rest of the circuit is as;


$$6 \text{mA} - i_2 - 4 \text{mA} + i_x = 6 \text{mA} - 4 \text{mA} - 4 \text{mA} + 2 \text{mA} = 0 \text{mA}$$

(c) $V_1 = 2 \times 6 = 12 \text{V}$ Voltage across the $2 \text{k}\Omega$ resistor

V_A with respect to the ground ($\frac{1}{2}$) is as;

$$V_A = -V_1 + V_x + 12 = -12 + 16 + 12 = 16 \text{V}$$


2-38

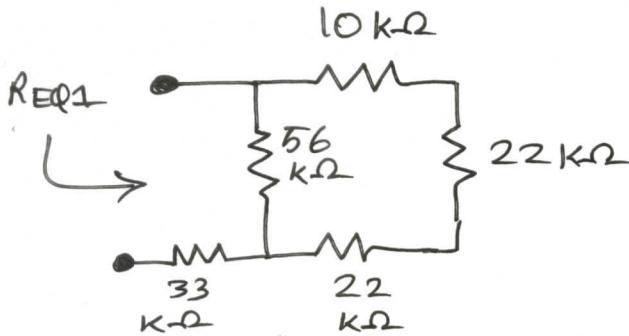

$$10 + 22 + 22 = 54 \text{ k}\Omega$$

$$56/54 = \frac{56 \times 54}{56 + 54} = 27.49 \text{ k}\Omega$$

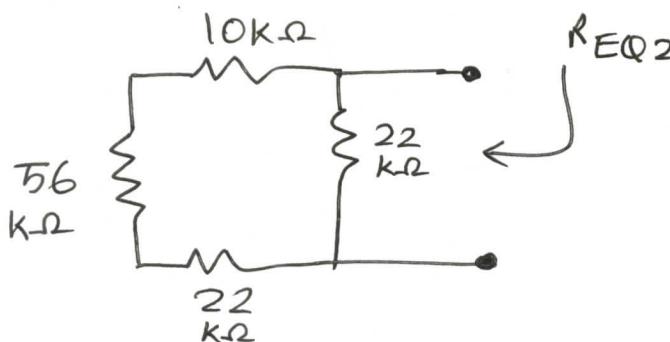
$$\Rightarrow R_{EQ1} = 27.49 + 33 = 60.49 \text{ k}\Omega$$




$$56 + 10 + 22 = 88 \text{ k}\Omega$$

$$\Rightarrow R_{EQ2} = 88 \parallel 22 = 17.6 \text{ k}\Omega$$


2-43

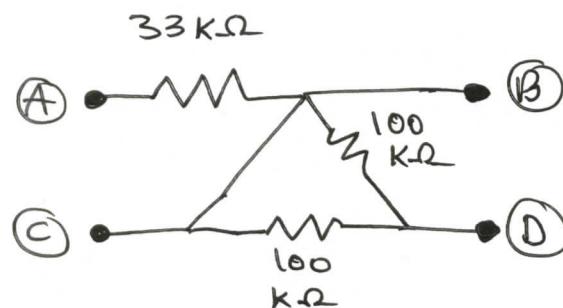

$$A-B: R_{AB} = 33 \text{ k}\Omega$$

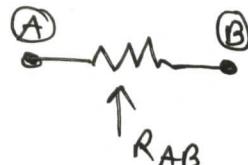

$$A-C:$$

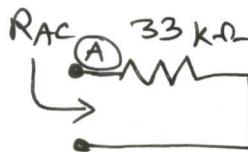


$$\Rightarrow R_{AC} = 33 \text{ k}\Omega$$

$$A-D:$$




$$\Rightarrow R_{AD} = (100 \parallel 100) + 33 = 83 \text{ k}\Omega$$

$$B-C:$$

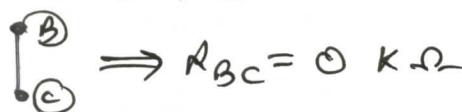


$$\Rightarrow R_{BC} = 0 \text{ k}\Omega$$



B-D:

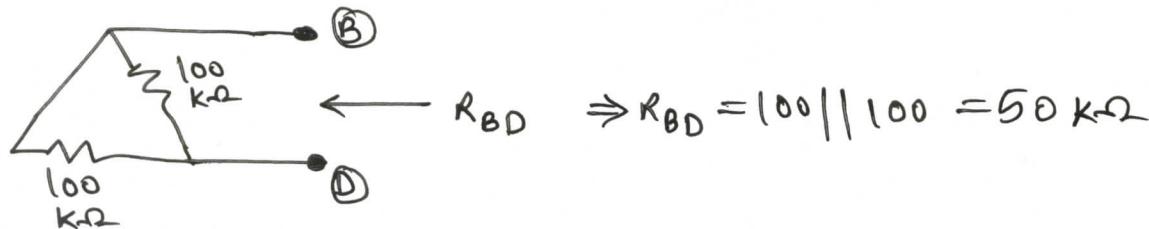

C-D:

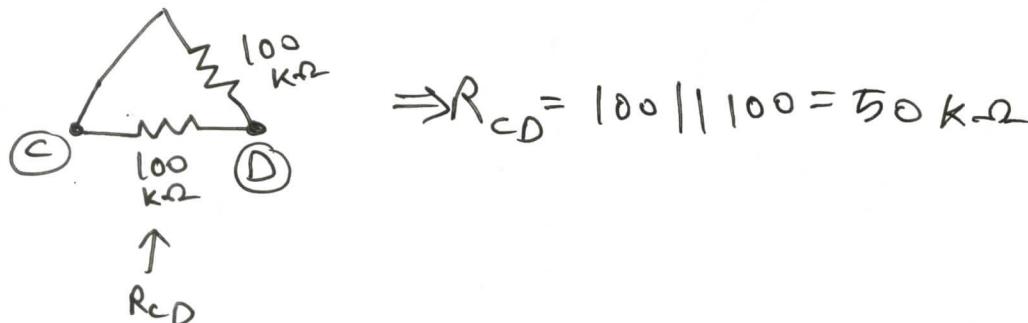

2-56

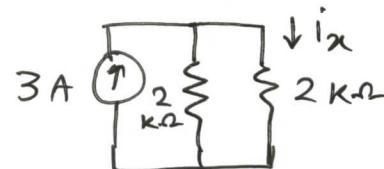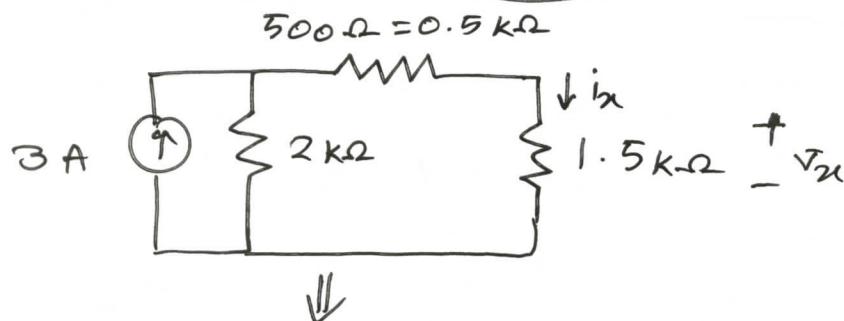



Current division:

$$i_x^o = \frac{2 \times 3}{2+2} = 1.5 \text{ A}$$

$$V_x = 1.5 \times 10^3 \Omega \times i_x^o = 2.25 \times 10^3 \text{ V}$$

✓

2-59

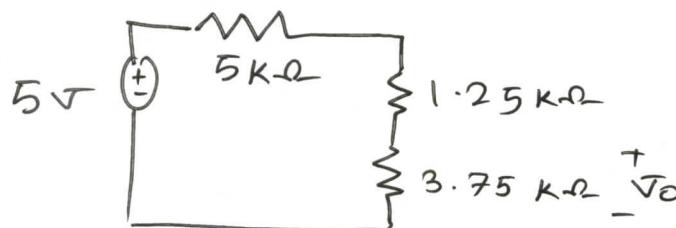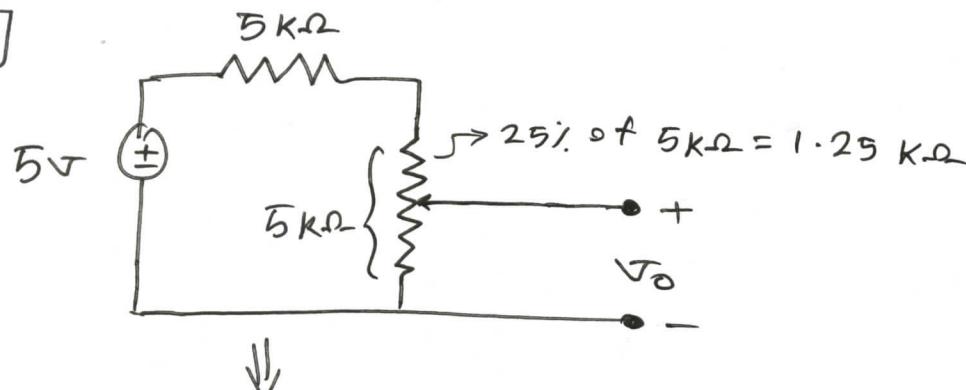


Voltage division:

$$V_o = \frac{3.75}{5+1.25+3.75} \times 5$$

$$= 1.875 \text{ V}$$



2-66

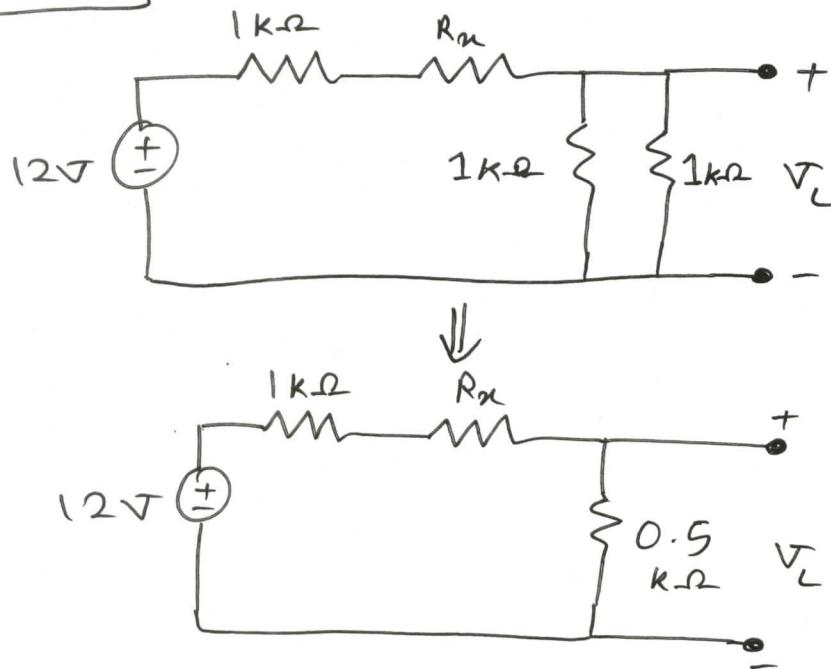

Voltage division:

$$\begin{aligned} V_L &= \frac{0.5}{1+R_m+0.5} \times 12 \\ V_L &= 2 \end{aligned} \quad \left. \begin{array}{l} \Rightarrow 2 = \frac{0.5}{1+R_m+0.5} \times 12 \\ \Rightarrow R_m = 1.5 \text{ k}\Omega \end{array} \right.$$

2-70

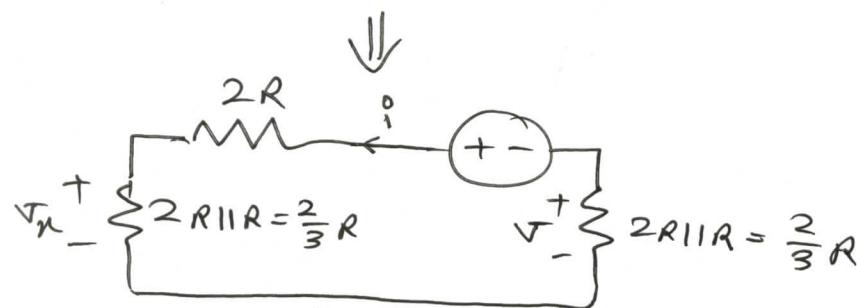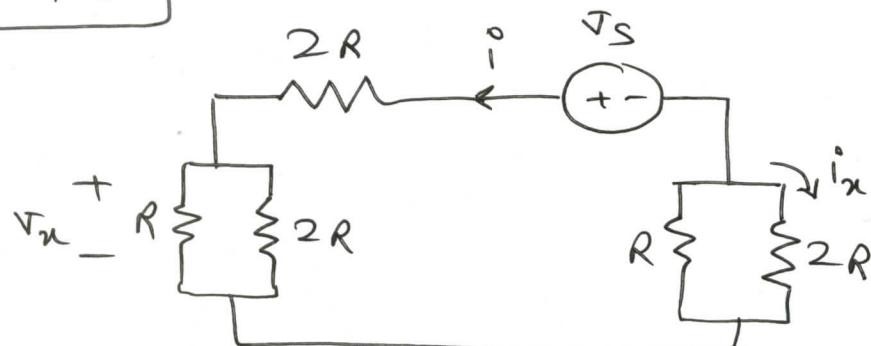


Voltage division: $V_{L2} = \frac{2/3 R}{2R + 2/3 R + 2/3 R} \times V_S = 0.2 V_S$

Note that $\text{J} = -\text{J}_x = -0.2 \text{ V}_s$

$$\Rightarrow i_x = -\frac{0.2 \text{ V}_s}{2R} = \frac{-\text{V}_s}{10R}$$

2-74

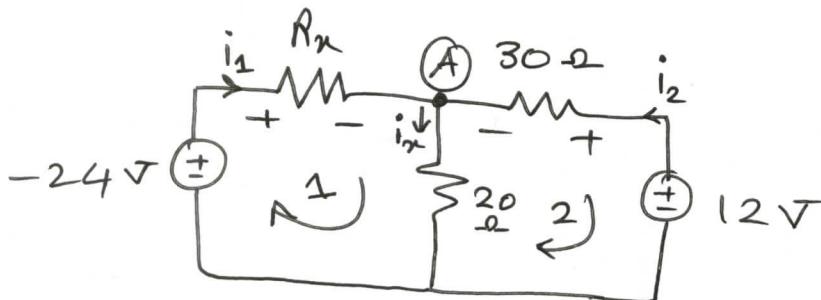

$$\text{Loop 1: } R_x i_1 + 0 - (-24) = 0 \quad (*)$$


$$\text{Loop 2: } -30i_2 + 12 - 0 = 0 \Rightarrow 30i_2 - 12 = 0 \Rightarrow i_2 = \frac{12}{30} \quad (I)$$

$$\text{Node A: } i_1 + i_2 = i_x = 0 \Rightarrow i_1 = -i_2 \quad (**)$$

$$(*) \text{ & } (**) \Rightarrow R_x(-i_2) = -24 \Rightarrow R_x i_2 = 24 \quad (II)$$


$$(I) \text{ & } (II) \Rightarrow R_x = 60 \Omega$$

2-78

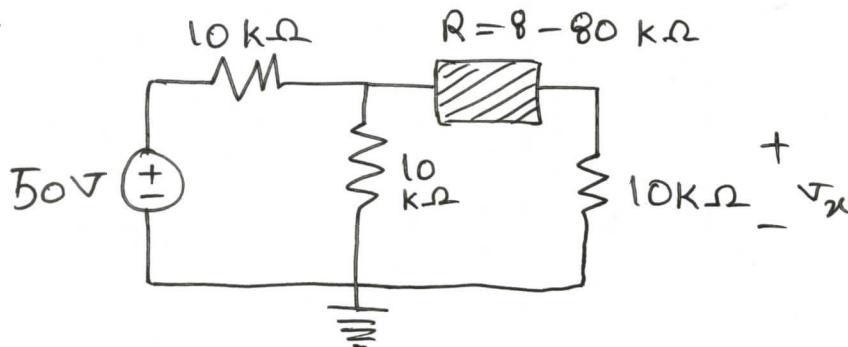


Using Source transformation;

$$R = 8 - 80 \text{ k}\Omega$$

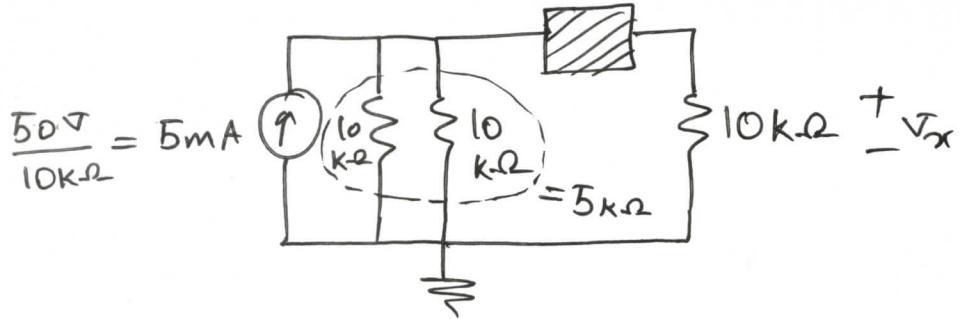

↓ (using another Source transformation)

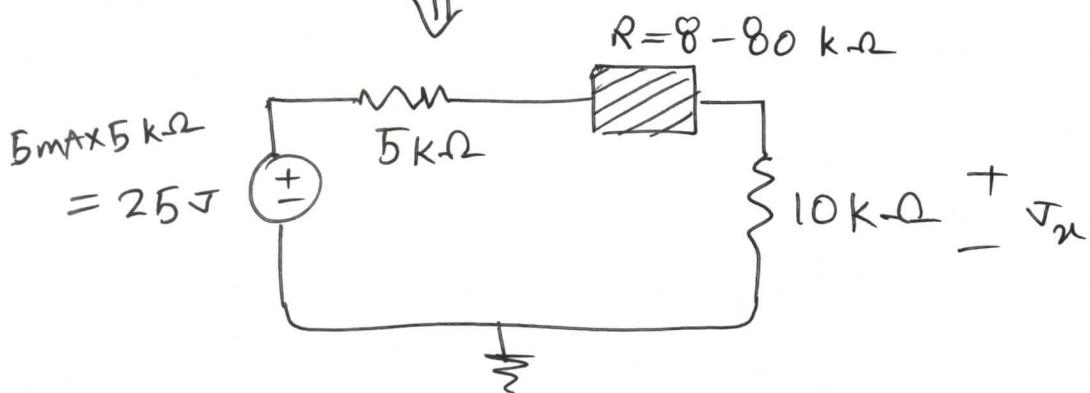

Voltage division: $V_x = \frac{10}{5+R+10} \times 25 \text{ V}$

$$R = 8 \text{ k}\Omega \Rightarrow V_x = 10.86 \text{ V}$$

$$R = 80 \text{ k}\Omega \Rightarrow V_x = 2.63 \text{ V} \Rightarrow V_x = 2.63 - 10.86 \text{ V}$$