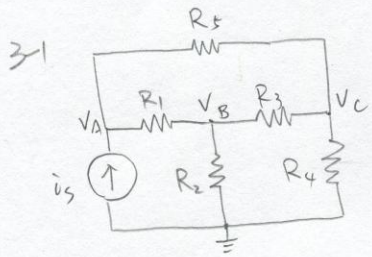



# MAE 140 HW3 Solution



$$G_1 = 1/R_1, G_2 = 1/R_2, G_3 = 1/R_3, G_4 = 1/R_4, G_5 = 1/R_5$$

Formulate eqs by inspection:
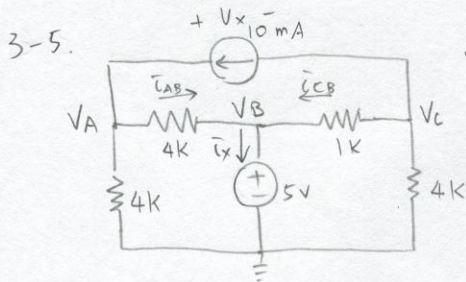
$$\begin{bmatrix} G_1 + G_5 & -G_1 & -G_5 \\ -G_1 & G_1 + G_2 + G_3 & -G_3 \\ -G_5 & -G_3 & G_3 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}$$



a) Use Method 2: carefully choose a ground.

$$V_B = 5$$

Formulate eqs of nodes A and C by inspection:


$$\begin{bmatrix} \frac{1}{4k} + \frac{1}{4k} & -\frac{1}{4k} & 0 \\ 0 & -\frac{1}{1k} & \frac{1}{4k} + \frac{1}{1k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 10 \text{ mA} \\ 5 \\ -10 \text{ mA} \end{bmatrix}$$

b) Plug in  $V_B = 5$  we get:

$$\begin{bmatrix} 0.5 \times 10^{-3} & 0 \\ 0 & 1.25 \times 10^{-3} \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 11.25 \times 10^{-3} \\ -5 \times 10^{-3} \end{bmatrix} \Rightarrow \begin{matrix} V_A = 22.5 \text{ V} \\ V_C = -4 \text{ V} \end{matrix}$$

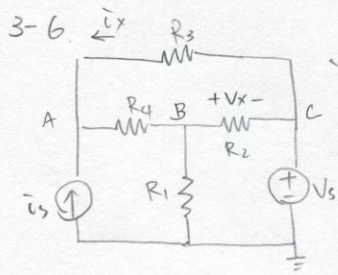c)  $V_x = V_A - V_C = 26.5 \text{ V}$ .

$$i_x = i_{AB} + i_{CB} = \frac{V_A - V_B}{4k} + \frac{V_C - V_B}{1k} = -4.625 \text{ mA}$$



a) Choose a ground as shown:

$$V_C = V_S$$

Formulate eqs of nodes A and B by inspection


$$\begin{bmatrix} \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} & \frac{1}{R_5} \\ -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_2} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}$$

b) Plug in  $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}$ ,  $V_S = 25$ ,  $i_s = 1 \text{ mA}$

$$\begin{bmatrix} 0.2 \times 10^{-3} & -0.1 \times 10^{-3} \\ -0.1 \times 10^{-3} & 0.3 \times 10^{-3} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 3.5 \times 10^{-3} \\ 2.5 \times 10^{-3} \end{bmatrix} \Rightarrow \begin{matrix} V_A = 26 \text{ V} \\ V_B = 17 \text{ V} \end{matrix}$$

P1

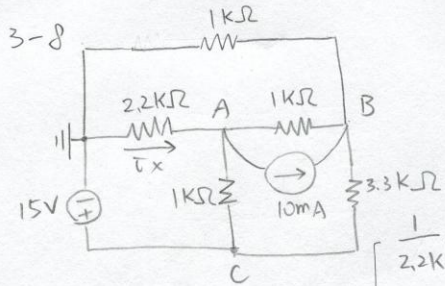3-6 (cont.)  $V_x = V_B - V_C = -8V$ ,  $i_x = \frac{V_C - V_A}{R_3} = -0.1 \text{ mA}$



a) Choose a ground as shown:


$$V_C = 15 \text{ V} \quad \#$$

Formulate eqs of nodes A and B by inspection

$$\begin{bmatrix} \frac{1}{2.2k} + \frac{1}{1k} + \frac{1}{1k} & -\frac{1}{1k} & -\frac{1}{1k} \\ -\frac{1}{1k} & \frac{1}{1k} + \frac{1}{1k} + \frac{1}{3.3k} & -\frac{1}{3.3k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -10 \text{ mA} \\ 10 \text{ mA} \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 2.45 & -1 \\ -1 & 2.3 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 5 \\ 15 \end{bmatrix} \quad V_A = 5.7 \text{ V}, \quad V_B = 9 \text{ V}$$

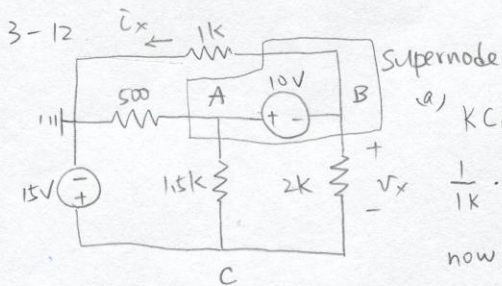b)  $V_x = V_B - V_C = 9 \text{ V} \quad \#$   $i_x = \frac{0 - V_A}{2.2k} = -2.6 \text{ mA} \quad \#$




a) KCL for the supernode A & B

$$\frac{1}{1k} \cdot V_B + \frac{1}{500} \cdot V_A + \frac{1}{1.5k} (V_A - V_C) + \frac{1}{2k} (V_B - V_C) = 0$$

now use  $V_C = 15$ ,  $V_A = V_B + 10$

$$\Rightarrow V_A = 7.8 \text{ V}, \quad V_B = -2.2 \text{ V}$$

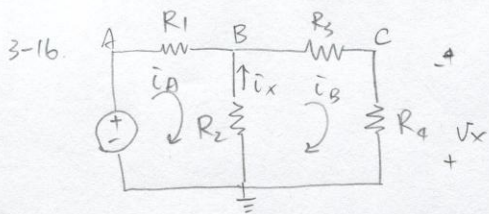b)  $V_x = V_B - V_C = -17.2 \text{ V} \quad \#$   $i_x = \frac{V_B}{1k} = -2.2 \text{ mA} \quad \#$



(a)  $V_A = V_s$   
Formulate eqs for nodes B and C:

$$\Rightarrow \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & \frac{1}{R_3} \\ \frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{V_s}{R_1} \\ 0 \end{bmatrix}$$


$$V_B = \frac{V_s R_2 (R_3 + R_4)}{R_1 R_2 + R_2 R_3 + R_1 R_3 + R_2 R_4} \quad V_C = \frac{V_s R_2 R_4}{R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4}$$

b) set Den =  $R_1 R_2 + R_1 R_3 + R_1 R_4 + R_2 R_3 + R_2 R_4$

$$\bar{i}_A = \frac{V_A - V_B}{R_1} = \frac{V_s (R_2 + R_3 + R_4)}{\text{Den}} \quad \bar{i}_B = \frac{V_C}{R_4} = \frac{V_s R_2}{\text{Den}}$$

$$c) \quad V_x = 0 - V_C = \frac{-V_s R_2 R_4}{\text{Den}} \quad \bar{i}_x = -\bar{i}_A + \bar{i}_B = \frac{V_s (-R_3 - R_4)}{\text{Den}}$$

3-6

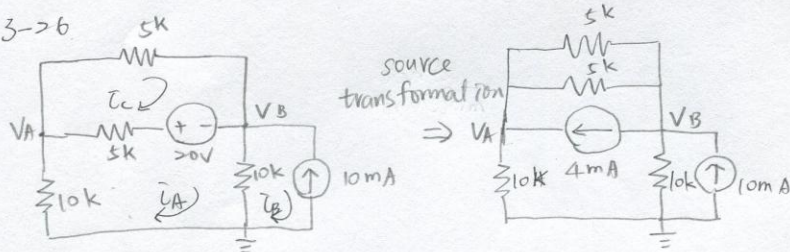

$$\bar{i} = \frac{V}{R} = \frac{20}{5k} = 4 \text{ mA}$$

Formulate eqs by inspection:


$$\begin{bmatrix} \frac{1}{5k} + \frac{1}{5k} + \frac{1}{10k} & \frac{1}{5k} \\ \frac{1}{5k} & \frac{1}{5k} + \frac{1}{10k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4 \times 10^{-3} \\ 10 \times 10^{-3} - 4 \times 10^{-3} \end{bmatrix} \Rightarrow \begin{matrix} V_A = 48.9 \text{ V} \\ V_B = 51.1 \text{ V} \end{matrix}$$

$$\bar{i}_A = \frac{-V_A}{10k} = -4.89 \text{ mA}$$

$$\bar{i}_B = -10 \text{ mA}$$

$$\bar{i}_C = \frac{V_A - V_B}{5k} = -0.44 \text{ mA}$$

3-26 (Another way)

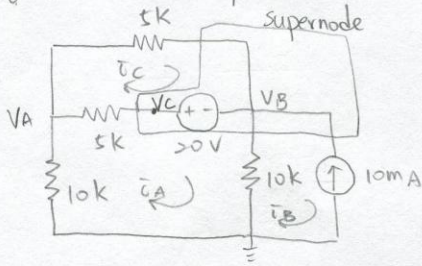

Formulate eqs by using a supernode BSC



$$V_C - V_B = 20$$

$$\frac{1}{5k}(V_B - V_A) + \frac{1}{5k}(V_C - V_A) + \frac{1}{10k}(V_B) = 10 \text{ mA}$$

$$\frac{1}{5k}(V_A - V_B) + \frac{1}{5k}(V_A - V_C) + \frac{1}{10k}(V_A) = 0$$

Replace  $V_C$  by  $V_C = V_B + 20$
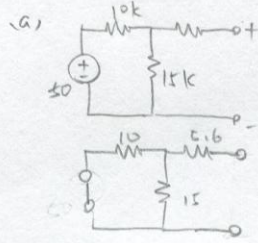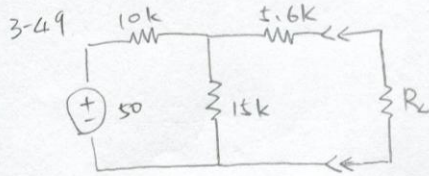
$$\Rightarrow \begin{bmatrix} \frac{1}{5k} + \frac{1}{5k} + \frac{1}{10k} & -\frac{1}{5k} - \frac{1}{5k} \\ -\frac{1}{5k} - \frac{1}{5k} & \frac{1}{5k} + \frac{1}{5k} + \frac{1}{10k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 4 \times 10^{-3} \\ 6 \times 10^{-3} \end{bmatrix} \Rightarrow \begin{cases} V_A = 48.9 \text{ V} \\ V_B = 51.1 \text{ V} \end{cases}$$




$$V_{oc} = 50 \cdot \frac{15}{15+10} = 30 \text{ V}$$


$$R_{eq} = 10k // 15k + 5.6k = 6k + 5.6k = 11.6k$$

$$\bar{i}_N = \frac{V_{oc}}{R_{eq}} = \frac{30}{11.6} = 2.586 \text{ mA}$$


Thévenin :

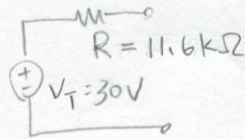

Norton :

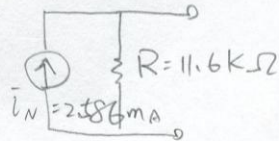


(b) Use Norton equivalent :

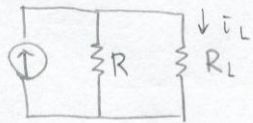




$$\bar{i}_L = \bar{i}_N \cdot \frac{\frac{1}{R_L}}{\frac{1}{R} + \frac{1}{R_L}} = 0.893 \text{ mA}$$

3-50

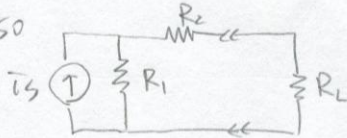


Use source transformation :

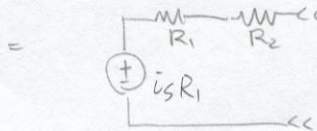

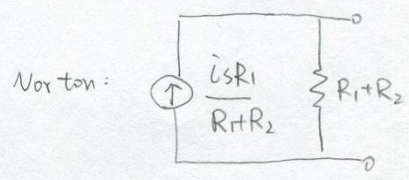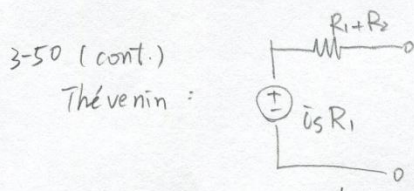




b) Use Norton equivalent

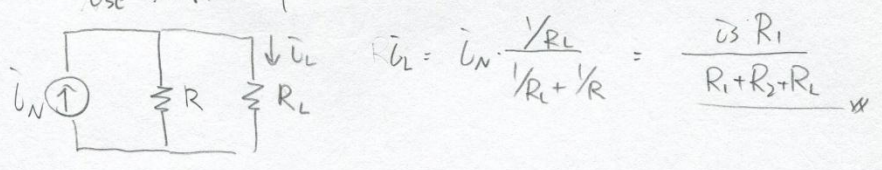

c) current division:

$$u_L = u_s \cdot \frac{1/R_2 + R_L}{1/R_1 + 1/R_2 + R_L} = \frac{u_s R_1}{R_1 + R_2 + R_L} \#$$

3-57.

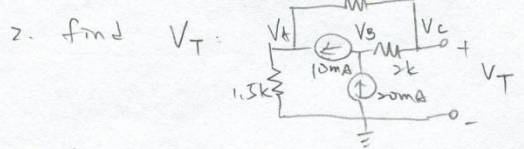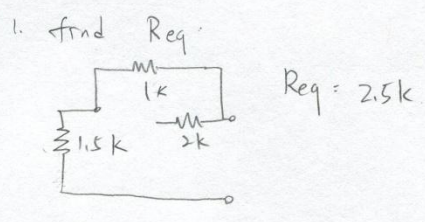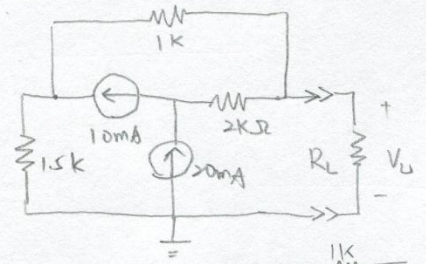

$$\begin{bmatrix} \frac{1}{1.5k} + \frac{1}{1k} & 0 & \frac{1}{1k} \\ 0 & \frac{1}{2k} & \frac{1}{2k} \\ \frac{1}{1k} & \frac{1}{2k} & \frac{1}{1k} + \frac{1}{2k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 10 \text{ mA} \\ 10 \text{ mA} \\ 0 \end{bmatrix} \Rightarrow \begin{matrix} V_A = 30 \text{ V} \\ V_B = 60 \text{ V} \\ V_C = 40 \text{ V} \end{matrix}, V_T = V_C = 40 \text{ V}$$

