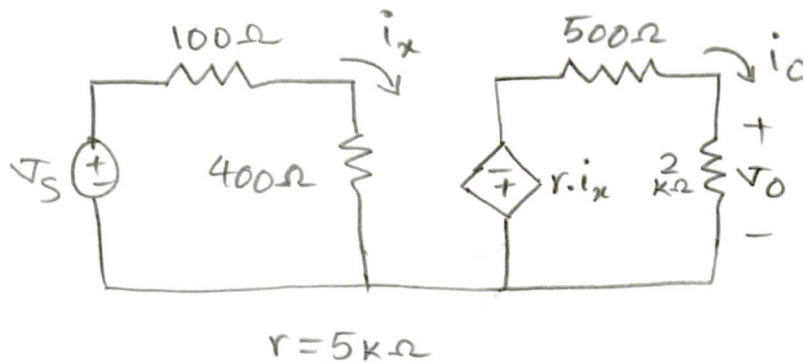


HW #5

MAE140

Fall 2013

4-1



$$\text{KVL in left loop: } i_x = \frac{V_S}{0.1 \times 10^3 + 0.4 \times 10^3} = 2 V_S \text{ mA}$$


$$\text{KVL in right loop: } i_o = \frac{-r \cdot i_x}{0.5 \times 10^3 + 2 \times 10^3} = \frac{-5 \times 10^3 i_x}{2.5 \times 10^3} = -2 i_x$$

Voltage division:

$$V_o = \frac{-2 \times 10^3 (r \cdot i_x)}{0.5 \times 10^3 + 2 \times 10^3} = \frac{-2 \times 10^3 (5 \times 10^3 \cdot i_x)}{2.5 \times 10^3} = -4 i_x \times 10^3$$

$$\left\{ \begin{array}{l} \frac{V_o}{V_S} = \frac{-4 i_x \times 10^3}{V_S} = \frac{-4 (2 V_S \times 10^{-3}) \times 10^3}{V_S} = -8 \\ \frac{i_o}{i_x} = \frac{-2 i_x}{i_x} = -2 \end{array} \right.$$

4-9

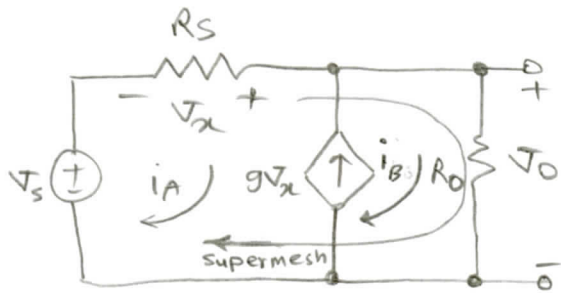

We can use a supermesh in the above circuit as;

$$-V_s + R_s i_A + R_o i_B = 0 \quad \text{Ⓘ}$$


$$\text{Also, we have; } \left. \begin{array}{l} i_B - i_A = gV_x \\ V_x = -R_s i_A \end{array} \right\} \Rightarrow i_A = \frac{i_B}{1 - gR_s} \quad \text{Ⓢ}$$

$$\begin{aligned} \text{Ⓘ} \text{ \& \text{Ⓢ}} &\Rightarrow -V_s + R_s \frac{i_B}{1 - gR_s} + R_o i_B = 0 \\ &\Rightarrow i_B = \frac{V_s}{\frac{R_s}{1 - gR_s} + R_o} \end{aligned}$$

$$V_o = R_o i_B = \frac{R_o V_s}{\frac{R_s}{1 - gR_s} + R_o}$$

$$\frac{V_o}{V_s} = \frac{R_o}{R_o + \frac{R_s}{1 - gR_s}} = \frac{R_o(1 - gR_s)}{R_o + R_s - gR_o R_s}$$

4-23

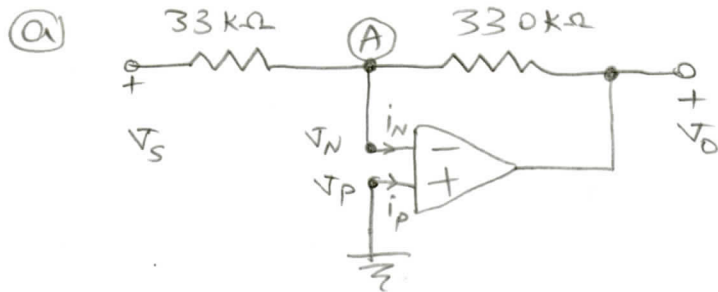


Based on the  $i-v$  relationships of the ideal model of the Op Amp, we have;

$$\begin{cases} V_p = V_n \\ i_p = i_n = 0 \end{cases}$$

$$\Rightarrow V_p = V_n = 0$$

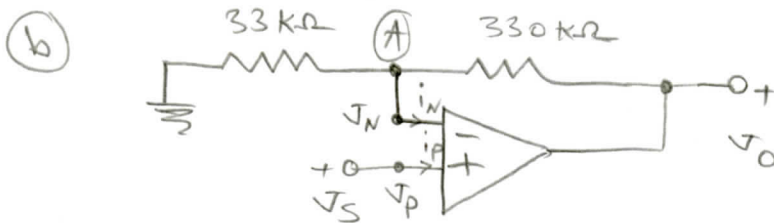
Kcl at (A):  $\frac{0 - V_s}{33 \times 10^3} + \frac{0 - V_o}{330 \times 10^3} = 0 \Rightarrow \frac{V_o}{V_s} = -10$



Again we have;  $V_p = V_n \Rightarrow V_n = V_p = V_s$   
 $i_p = i_n = 0$

Kcl at (A):  $\frac{V_s}{33 \times 10^3} + \frac{V_s - V_o}{330 \times 10^3} = 0 \Rightarrow \frac{V_o}{V_s} = 11$

4-28

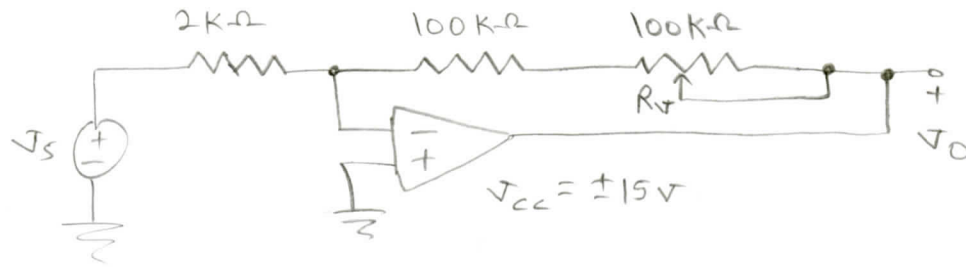

The variable resistor is denoted by  $R_v$  which is in the range of;  $0 \leq R_v \leq 100\text{ k}\Omega$


The above circuit is an inverting amplifier with a gain of;

$$K = \frac{V_o}{V_s} = -\frac{100 \times 10^3 + R_v}{2 \times 10^3}$$

$0 \leq R_v \leq 100\text{ k}\Omega$ , thus the gain is in the range of;

$$-100 \leq K = \frac{V_o}{V_s} \leq -50$$

4-30

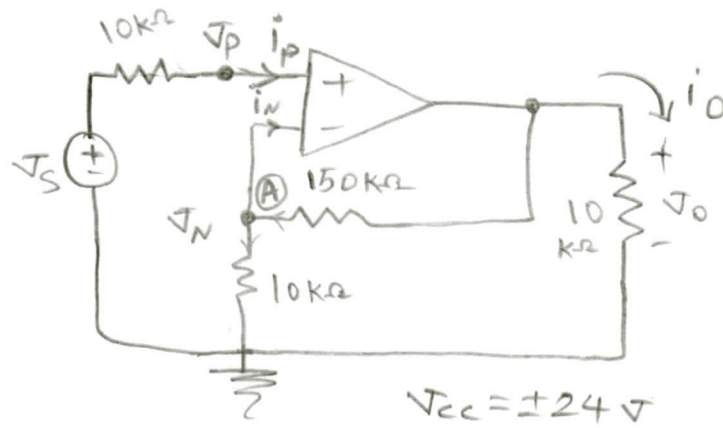

(a)  $i_p = i_n = 0 \Rightarrow V_p = V_S$   
 Also  $V_p = V_n \Rightarrow V_n = V_S$

KCL at (A):  $\frac{V_n}{10 \times 10^3} = \frac{V_o - V_n}{150 \times 10^3} \xrightarrow{V_n = V_S} \frac{V_o}{V_S} = 16$


(b)  $V_S = 1V \Rightarrow V_o = 16 \times 1 = 16V$

$V_S = 3V \Rightarrow V_o = 16 \times 3 = 48V$

In this case, the OP Amp becomes saturated, thus

$V_o = +24V$  (coming from  $V_{CC} = \pm 24V$ )

4-32

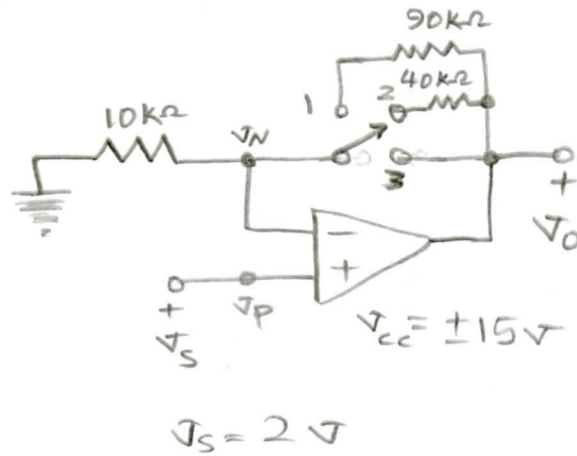

Amplification by a factor of 1  $\Rightarrow$  connect switch "3"

because  $V_P = V_N$   
 $V_P = V_S \Rightarrow V_O = V_S = 2\text{ V}$   
 $V_N = V_O$

Amplification by a factor of 5  $\Rightarrow$  connect switch "2"

because in this case, the circuit acts like a noninverting amplifier with a gain of  $K = \frac{V_O}{V_S} = \frac{40 \times 10^3 + 10 \times 10^3}{10 \times 10^3} = 5$   
 $\Rightarrow V_O = 5 \times V_S = 10\text{ V}$

Amplification by a factor of 10  $\Rightarrow$  connect switch "1"

because again in this case, the circuit acts like


a noninverting amplifier with a gain of;

$$K = \frac{V_O}{V_S} = \frac{90 \times 10^3 + 10 \times 10^3}{10 \times 10^3} = 10$$

$$\Rightarrow V_O = 10 \times V_S = 20\text{ V}$$


Due to  $V_{CC} = \pm 15\text{ V}$ , the Op Amp becomes saturated and thus  $V_O$  can have a maximum value of  $V_O = 15\text{ V}$ . Therefore, another recommendation to fix the circuit for this case is to increase  $V_{CC} = \pm 15\text{ V}$  to  $V_{CC} = \pm 20\text{ V}$ .

4-36

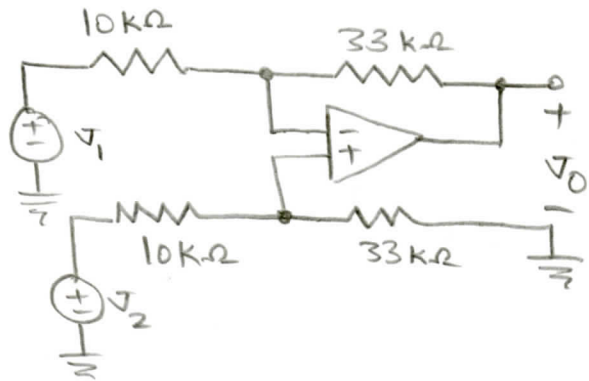

Using superposition to find  $V_O$ :

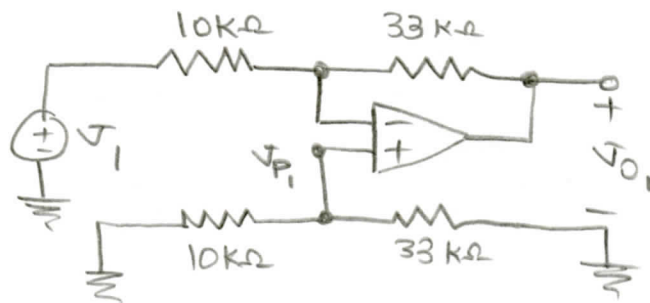
(I) First set  $V_2 = 0$  (turn off  $V_2$ );



In above circuit,  $V_p = 0$ . Therefore the circuit acts like an inverting amplifier with the result that

$$V_{O1} = - \frac{33 \times 10^3}{10 \times 10^3} V_1$$

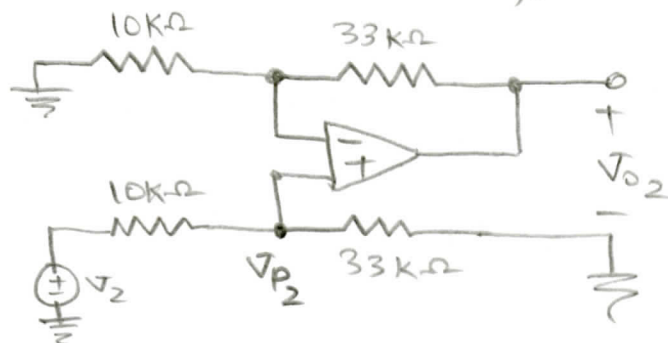(II) Second set  $V_1 = 0$  (turn off  $V_1$ );



The circuit looks like a noninverting amplifier with a voltage divider connected at its input.

$$\left. \begin{array}{l} \text{Voltage division: } V_{P_2} = \frac{33 \times 10^3}{10 \times 10^3 + 33 \times 10^3} V_2 \\ \text{Noninverting amplifier: } V_{O_2} = \frac{33 \times 10^3 + 10 \times 10^3}{10 \times 10^3} V_{P_2} \end{array} \right\} \Rightarrow V_{O_2} = \frac{33}{10} V_2$$


$$V_O = V_{O_1} + V_{O_2} = -\frac{33}{10} V_1 + \frac{33}{10} V_2$$

$$\Rightarrow V_O = \frac{33}{10} (V_2 - V_1)$$

As we can see, the output voltage is proportional to the difference between the two inputs. Thus, such a circuit is called differential amplifier or subtractor.

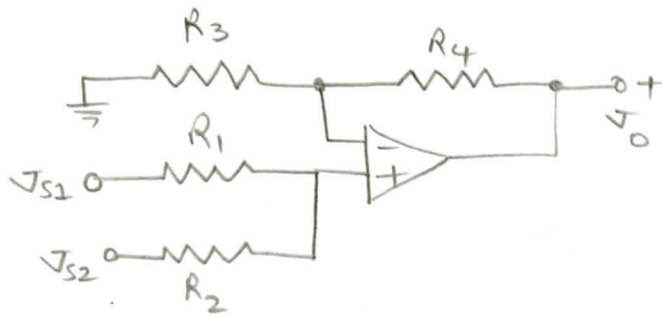
In page 195 of a book, we can see the general equation for gain of a subtractor circuit.





Using superposition to find  $V_0$ ;

(I) First Set  $V_{S2} = 0$ ;

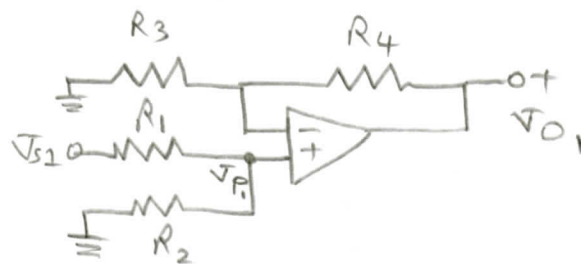


Circuit looks like a noninverting amplifier with a voltage divider connected at its input.

$$\text{Voltage division: } V_{P1} = \frac{R_2 V_{S1}}{R_1 + R_2}$$

$$\text{Noninverting amplifier: } V_{O1} = \frac{R_3 + R_4}{R_3} V_{P1} = \frac{R_3 + R_4}{R_3} \cdot \frac{R_2 V_{S1}}{R_1 + R_2}$$

(II) Second Set  $V_{S1} = 0$ ;

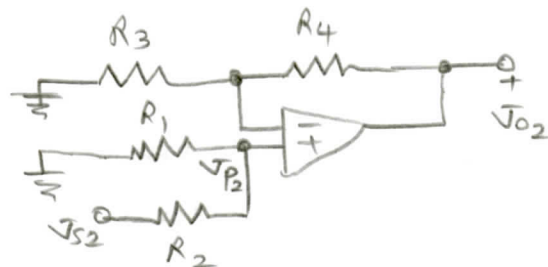

The same as case (I);

$$V_{P2} = \frac{R_1 V_{S2}}{R_1 + R_2}, \quad V_{O2} = \frac{R_3 + R_4}{R_3} V_{P2}$$

$$\Rightarrow V_{O2} = \frac{R_3 + R_4}{R_3} \cdot \frac{R_1 V_{S2}}{R_1 + R_2}$$

$$V_0 = V_{O1} + V_{O2} = \left( \frac{R_3 + R_4}{R_3} \right) \left( \frac{1}{R_1 + R_2} \right) (R_2 V_{S1} + R_1 V_{S2})$$