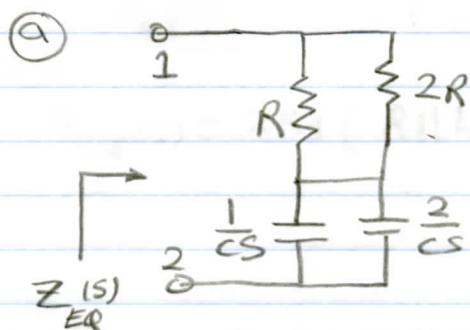


HW#7  
MAE140  
Fall 2013

10-4




$$Z_{EQ}(s) = (R \parallel 2R) + \left( \frac{1}{Cs} \parallel \frac{2}{Cs} \right) = \frac{2}{3}R + \frac{2}{3} \frac{1}{Cs}$$

$$\Rightarrow Z_{EQ}(s) = \frac{2}{3} \left( \frac{RCs+1}{Cs} \right)$$

Zero:  $RCs+1=0 \Rightarrow s = -\frac{1}{RC}$

Pole:  $Cs=0 \Rightarrow s=0$

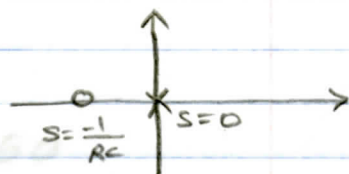


(b) Zero:  $s = -33 \text{ krad/s} = -33 \times 10^3 \text{ rad/s}$

$$s = -\frac{1}{RC} = -33 \times 10^3 \Rightarrow \frac{1}{RC} = 33 \times 10^3$$

We can choose  $R = 10 \text{ k}\Omega$

$$\Rightarrow C = 0.003 \text{ }\mu\text{F}$$

10-66

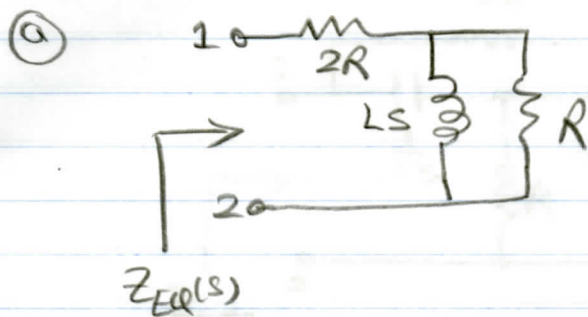


$$Z_{EQ}(s) = 2R + (R \parallel LS) = 2R + \frac{RLS}{R+LS}$$

$$= \frac{3RLS + 2R^2}{R+LS}$$

zero:  $3RLS + 2R^2 = 0 \Rightarrow s = -\frac{2R}{3L}$

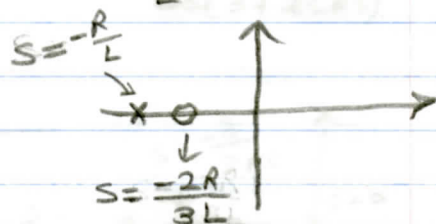pole:  $R + LS = 0 \Rightarrow s = -\frac{R}{L}$



(b) pole:  $s = -150 \text{ rad/s}$


$$s = -\frac{R}{L} = -150 \Rightarrow \frac{R}{L} = 150$$

we can select  $R = 10 \text{ k}\Omega$

$$\Rightarrow L = 0.06 \times 10^{-3} \text{ H}$$

zero:  $s = -\frac{2}{3} \frac{R}{L} = -\frac{2}{3} (150) \text{ rad/s} = -100 \text{ rad/s}$

16-10

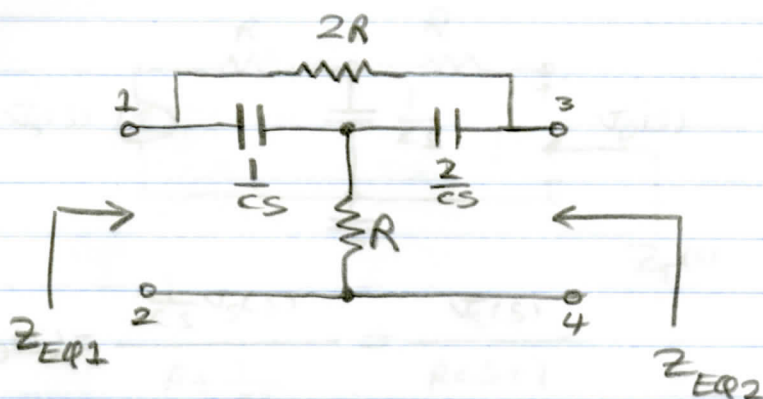


$$Z_{EQ1} = \left[ \left( \frac{2}{cS} + 2R \right) \parallel \frac{1}{cS} \right] + R$$

$$= \frac{\left( \frac{2}{cS} + 2R \right) \left( \frac{1}{cS} \right)}{\frac{2}{cS} + 2R + \frac{1}{cS}} + R = \frac{2(1+RCs)}{cS(3+2CRS)} + R$$

$$= \frac{2(CR)^2 s^2 + 5CRS + 2}{cS(3+2CRS)}$$

Zeros:  $s = -\frac{1}{2RC}$  and  $s = -\frac{2}{RC}$

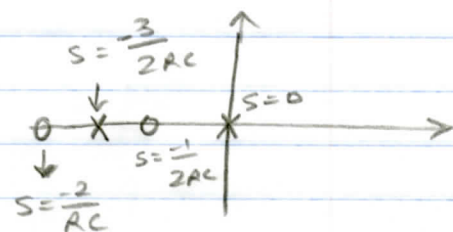Poles:  $s = 0$  and  $s = -\frac{3}{2RC}$




$$Z_{EQ2} = \left[ \left( \frac{1}{cS} + 2R \right) \parallel \frac{2}{cS} \right] + R$$

$$= \frac{\left( \frac{1}{cS} + 2R \right) \left( \frac{2}{cS} \right)}{\frac{1}{cS} + 2R + \frac{2}{cS}} + R = \frac{2(1+2RCs)}{cS(3+2RCs)} + R$$


$$= \frac{2(CR)^2 s^2 + 7CRS + 2}{cS(3+2RCs)}$$

Zeros:  $s = \frac{-7 \pm \sqrt{33}}{4RC}$

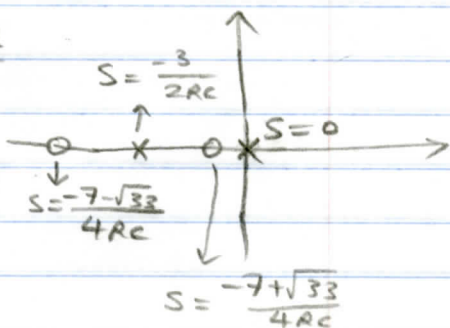Poles:  $s = 0$  and  $s = -\frac{3}{2RC}$




10-14

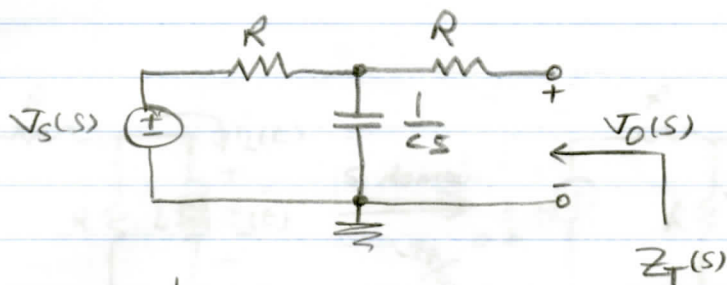

$$(a) \quad V_O(s) = \frac{\frac{1}{cS} V_S(s)}{R + \frac{1}{cS}} = \frac{V_S(s)}{RCs + 1}$$

$$(b) \quad Z_T(s) = \left( R \parallel \frac{1}{cS} \right) + R = \frac{R \frac{1}{cS}}{R + \frac{1}{cS}} + R = \frac{R(RCs + 2)}{RCs + 1}$$

10-18

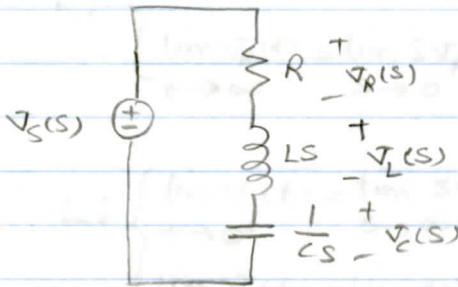

$$V_S(t) = u(t) \Rightarrow V_S(s) = \frac{1}{s}$$

(a) using voltage division:

$$V_R(s) = \frac{R V_S(s)}{R + LS + \frac{1}{cS}} = \frac{R}{LS^2 + RS + \frac{1}{c}}$$

$$V_L(s) = \frac{LS V_S(s)}{R + LS + \frac{1}{cS}} = \frac{LCS}{LCS^2 + RCS + 1} = \frac{LS}{LS^2 + RS + \frac{1}{c}}$$

$$V_C(s) = \frac{\frac{1}{cS} V_S(s)}{R + LS + \frac{1}{cS}} = \frac{1}{CLS^3 + CRS^2 + S} = \frac{\frac{1}{cS}}{LS^2 + RS + \frac{1}{c}}$$

(b)  $V_R(s)$ : two poles

$V_L(s)$ : one zero & two poles

$V_C(s)$ : three poles

Note that the denominator is the same for all  $V_R$ ,  $V_L$ , and  $V_C$

}  $\Rightarrow$  the two poles are the same for all  $V_R, V_L, V_C$ .  
And the zero for  $V_L$  is due to impedance of  $L$  and pole for  $V_C$  is due to impedance of  $C$ .



①


$$R: \begin{cases} \lim_{t \rightarrow 0^+} V_R(t) = \lim_{s \rightarrow \infty} sV_R(s) = 0 \text{ V, initial value} \\ \lim_{t \rightarrow \infty} V_R(t) = \lim_{s \rightarrow 0} sV_R(s) = 0 \text{ V, final value} \end{cases}$$

$$L: \begin{cases} \lim_{t \rightarrow 0^+} V_L(t) = \lim_{s \rightarrow \infty} sV_L(s) = 1 \text{ V, initial value} \\ \lim_{t \rightarrow \infty} V_L(t) = \lim_{s \rightarrow 0} sV_L(s) = 0 \text{ V, final value} \end{cases}$$

$$C: \begin{cases} \lim_{t \rightarrow 0^+} V_C(t) = \lim_{s \rightarrow \infty} sV_C(s) = 0 \text{ V, initial value} \\ \lim_{t \rightarrow \infty} V_C(t) = \lim_{s \rightarrow 0} sV_C(s) = 1 \text{ V, final value} \end{cases}$$

Because the input voltage is  $v_s(t) = u(t)$ , therefore at  $t=0$ , the whole input voltage drops across  $L$ . But at  $t=\infty$ , the whole input voltage drops across  $C$ . At  $t=0$  and  $t=\infty$ , there is no voltage drop across  $R$ .

10-23

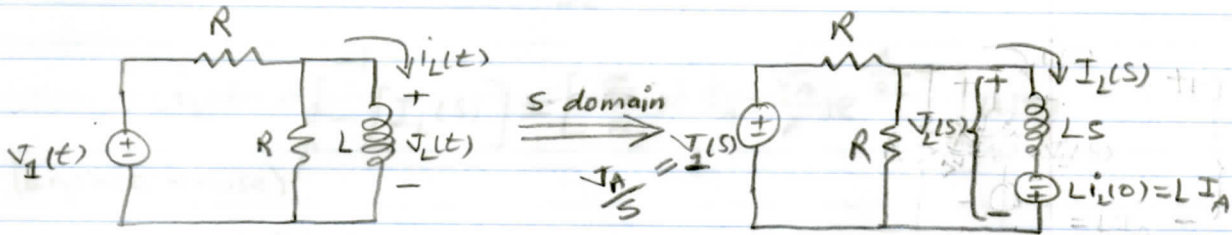


$$V_2(t) = V_A u(t)$$

$$i_L(0) = I_A$$

Using superposition as:

(I) turn off  $L I_A$

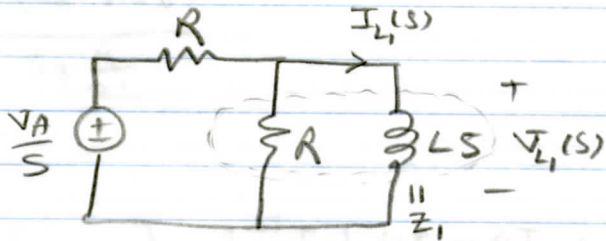


$$I_{L_1}(s) = \frac{V_{L_1}(s)}{LS}$$

voltage division:  $V_{L_1}(s) = \frac{Z_2 \left( \frac{V_A}{s} \right)}{R + Z_1} \Rightarrow I_{L_1}(s) = \frac{V_A}{s(R + 2LS)}$

$$Z_1 = \frac{LRS}{R + LS} \Rightarrow I_{L_1}(s) = \frac{V_A}{2L \left( s \left( s + \frac{R}{2L} \right) \right)}$$

(II) turn off  $\frac{V_A}{s}$

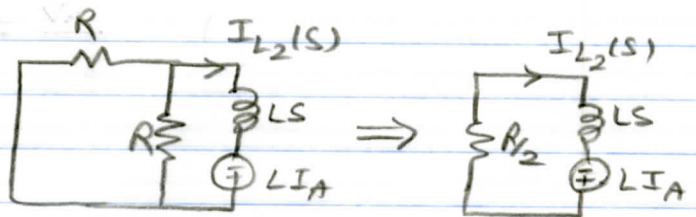

$$\Rightarrow I_{L_2}(s) = \frac{L I_A}{\frac{R}{2} + LS} = \frac{I_A}{s + \frac{R}{2L}}$$

$$I_L(s) = I_{L_1}(s) + I_{L_2}(s) = \frac{V_A}{2L \left( s \left( s + \frac{R}{2L} \right) \right)} + \frac{I_A}{s + \frac{R}{2L}}$$

$$\Rightarrow I_L(s) = \frac{\frac{V_A}{R}}{s} + \frac{I_A - \frac{V_A}{R}}{s + \frac{R}{2L}}$$

$$i_L(t) = \mathcal{L}^{-1} [I_L(s)] = \left[ \frac{V_A}{R} + \left( I_A - \frac{V_A}{R} \right) e^{-\frac{R}{2L}t} \right] u(t)$$

(Laplace inverse) ↑

$$V_L(s) = (Ls)I_L(s) - LI_A =$$

$$= Ls \left[ \frac{\frac{V_A}{R}}{s} + \frac{I_A - \frac{V_A}{R}}{s + \frac{R}{2L}} \right] - LI_A$$


$$= \frac{\frac{1}{2}(V_A - RI_A)}{s + \frac{R}{2L}}$$

$$v_L(t) = \mathcal{L}^{-1} [V_L(s)] = \mathcal{L}^{-1} \left[ \frac{\frac{1}{2}(V_A - RI_A)}{s + \frac{R}{2L}} \right]$$

$$\Rightarrow v_L(t) = \frac{1}{2}(V_A - RI_A) e^{-\frac{R}{2L}t} u(t)$$



10-28

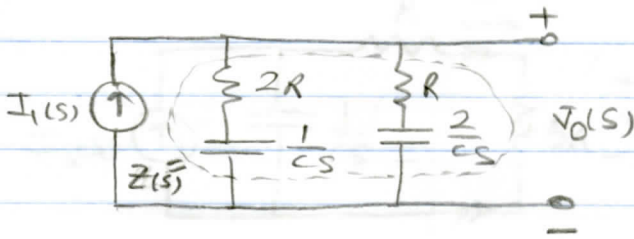

$$V_0(s) = Z(s) I_1(s) \Rightarrow \frac{V_0(s)}{I_1(s)} = Z(s)$$

$$Z(s) = \left( 2R + \frac{1}{cS} \right) \parallel \left( R + \frac{2}{cS} \right)$$



$$= \frac{\left( 2R + \frac{1}{cS} \right) \left( R + \frac{2}{cS} \right)}{2R + \frac{1}{cS} + R + \frac{2}{cS}}$$

$$\Rightarrow Z(s) = \frac{(2RcS + 1)(RcS + 2)}{3cS(RcS + 1)}$$


$$\text{zeros: } \begin{cases} 2RcS + 1 = 0 \Rightarrow s = -\frac{1}{2Rc} \\ RcS + 2 = 0 \Rightarrow s = -\frac{2}{Rc} \end{cases}$$

$$\text{poles: } \begin{cases} cS = 0 \Rightarrow s = 0 \\ RcS + 1 = 0 \Rightarrow s = -\frac{1}{Rc} \end{cases}$$


10-34

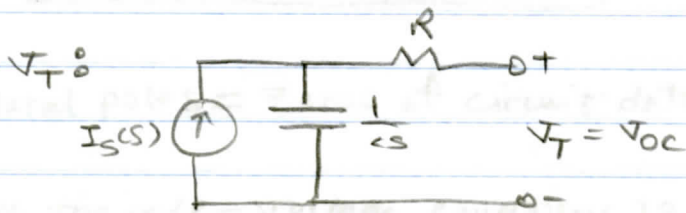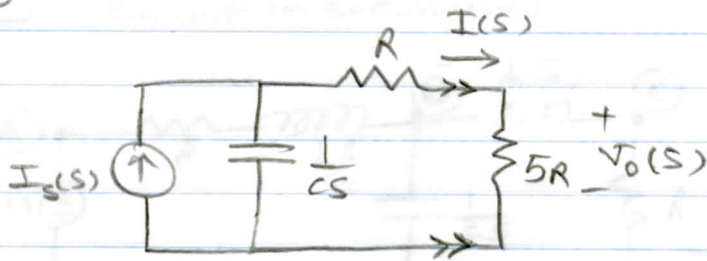

$$V_T = V_{oc} = \frac{I_s(s)}{cS}$$

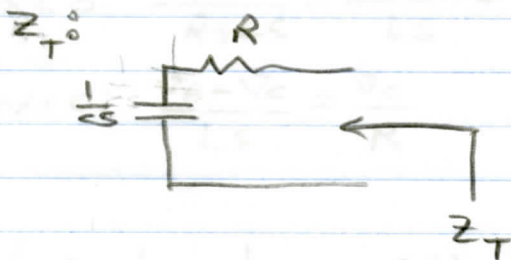
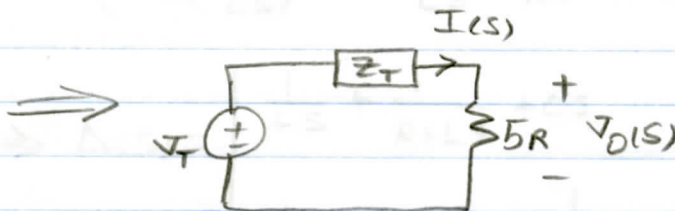
$$Z_T = R + \frac{1}{cS} = \frac{RcS + 1}{cS}$$




$$I(s) = \frac{V_T}{Z_T + 5R} \Rightarrow I(s) = \frac{I_s(s)}{cS \left( \frac{RcS + 1}{cS} + 5R \right)}$$



$$\Rightarrow \frac{I(s)}{I_s(s)} = \frac{1}{6RcS + 1}$$

10-62

Circuit in s-domain:

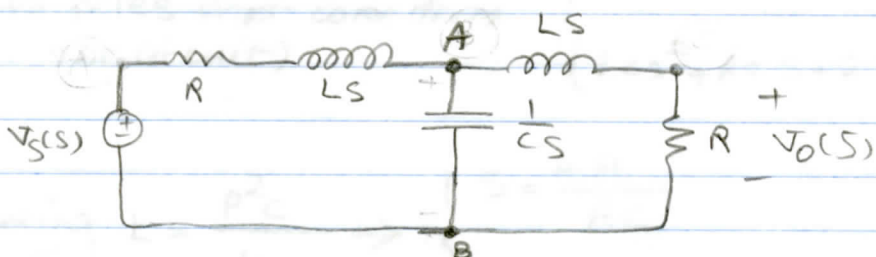

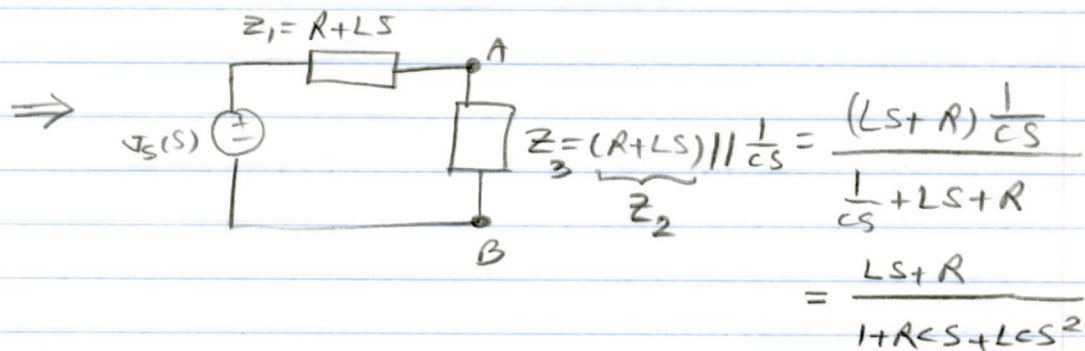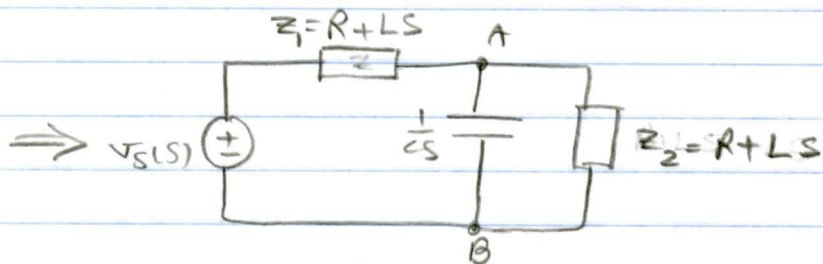First, we calculate  $V_o(s)$  using circuit reduction and voltage division as:



Using voltage division: 
$$V_{AB} = \frac{Z_3 V_s(s)}{Z_3 + Z_1}$$

inserting  $Z_1$  and  $Z_3 \Rightarrow V_{AB} = \frac{V_s(s)}{2 + RcS + LcS^2}$

using another voltage division:

$$V_o(s) = \frac{R}{LS + R} V_{AB} \xrightarrow[\text{inserting } V_{AB}]{\text{inserting}} V_o(s) = \frac{R V_s(s)}{(LS + R)(LcS^2 + RcS + 2)}$$

Natural poles for  $V_o(s)$ :  
(the poles that come from  
the circuit)


$$\begin{cases} Ls + R = 0 \\ Lcs^2 + Rcs + 2 = 0 \end{cases}$$

inserting  $L = \frac{R^2 C}{4} \Rightarrow$

$$\begin{cases} s = \frac{-4}{RC} \\ s = \frac{2}{RC} (-1 \pm j) \end{cases}$$

10-67

a

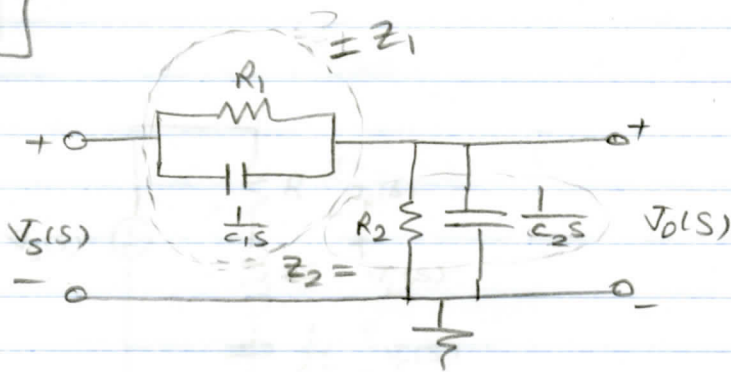

$$Z_1 = R_1 \parallel \frac{1}{C_1 s} = \frac{R_1 \frac{1}{C_1 s}}{R_1 + \frac{1}{C_1 s}} = \frac{R_1}{R_1 C_1 s + 1}$$

$$Z_2 = R_2 \parallel \frac{1}{C_2 s} = \frac{R_2 \frac{1}{C_2 s}}{R_2 + \frac{1}{C_2 s}} = \frac{R_2}{R_2 C_2 s + 1}$$

voltage division:

$$V_O(s) = \frac{Z_2 V_S(s)}{Z_1 + Z_2} = \frac{R_2 (R_1 C_1 s + 1) V_S(s)}{R_1 (C_2 R_2 s + 1) + R_2 (C_1 R_1 s + 1)}$$

$$\Rightarrow \frac{V_O(s)}{V_S(s)} = \frac{R_1 R_2 C_1 s + R_2}{(R_1 R_2 C_2 + R_1 R_2 C_1) s + R_1 + R_2}$$

b

$$R_2 = 15 \text{ M}\Omega$$

$$C_2 = 3 \text{ pF}$$

$$\frac{V_O(s)}{V_S(s)} = \frac{1}{2} \Rightarrow \frac{R_1 R_2 C_1 s + R_2}{(R_1 R_2 C_2 + R_1 R_2 C_1) s + R_1 + R_2} \stackrel{\text{Text}}{=} \frac{1}{2}$$

$$\Rightarrow R_1 R_2 C_2 s + R_1 = R_1 R_2 C_1 s + R_2$$

$$\Rightarrow \left. \begin{array}{l} R_1 = R_2 \\ C_1 = C_2 \end{array} \right\} \Rightarrow \begin{array}{l} R_1 = 15 \text{ M}\Omega \\ C_1 = 3 \text{ pF} \end{array}$$