

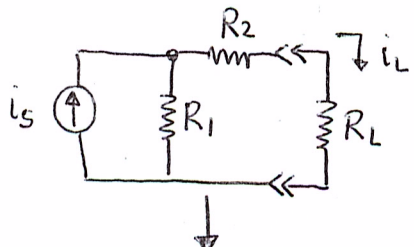


3.50 3.51 3.56 3.3 3.4 3.7 3.11 3.14 3.22 3.24

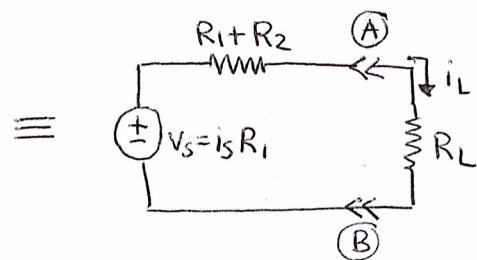
3.50 (a) Find the Thévenin or Norton equivalent circuit seen by R_L



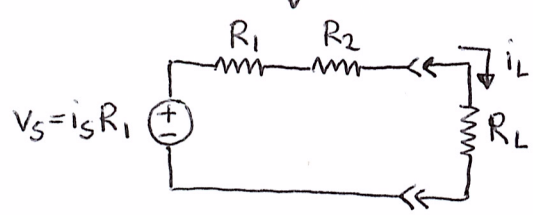Use source transformation to transform the current source into a voltage source, i.e.



Thevenin equivalent circuit

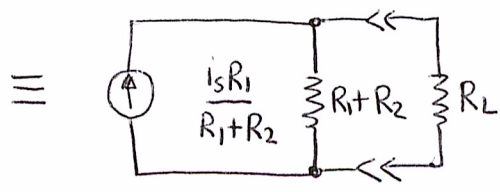

Norton equivalent circuit


(b) Use (a) to find i_L in terms of R_1, R_2 and R_L
 Using the Thévenin equivalent circuit from (a) and KVL we can write

$$-v_s + i_L(R_1 + R_2) + i_L R_L = 0$$

$$-i_s R_1 + i_L(R_1 + R_2 + R_L) = 0$$

$$i_L = \frac{R_1}{R_1 + R_2 + R_L} i_s$$

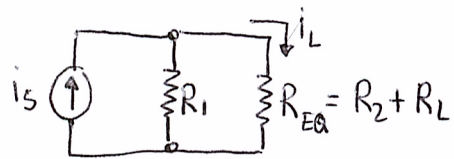(c) Check your answer in (b) using current division.



$$i_L = \frac{G_{eq}}{G_1 + G_{eq}} i_s = \frac{\frac{1}{R_{eq}}}{\frac{1}{R_1} + \frac{1}{R_{eq}}} i_s = \frac{R_1}{R_1 + R_{eq}} i_s$$

$$i_L = \frac{R_1}{R_1 + R_2 + R_L} i_s$$


Note: You can solve for i_L directly using the following rule

$$i_L = i_s \frac{R_1}{R_1 + R_2 + R_3}$$
 ← resistance of the 'other' path
 ← total resistance of the loop

3.51

Find Thévenin equivalent circuit seen by R_L and V_L

2/9

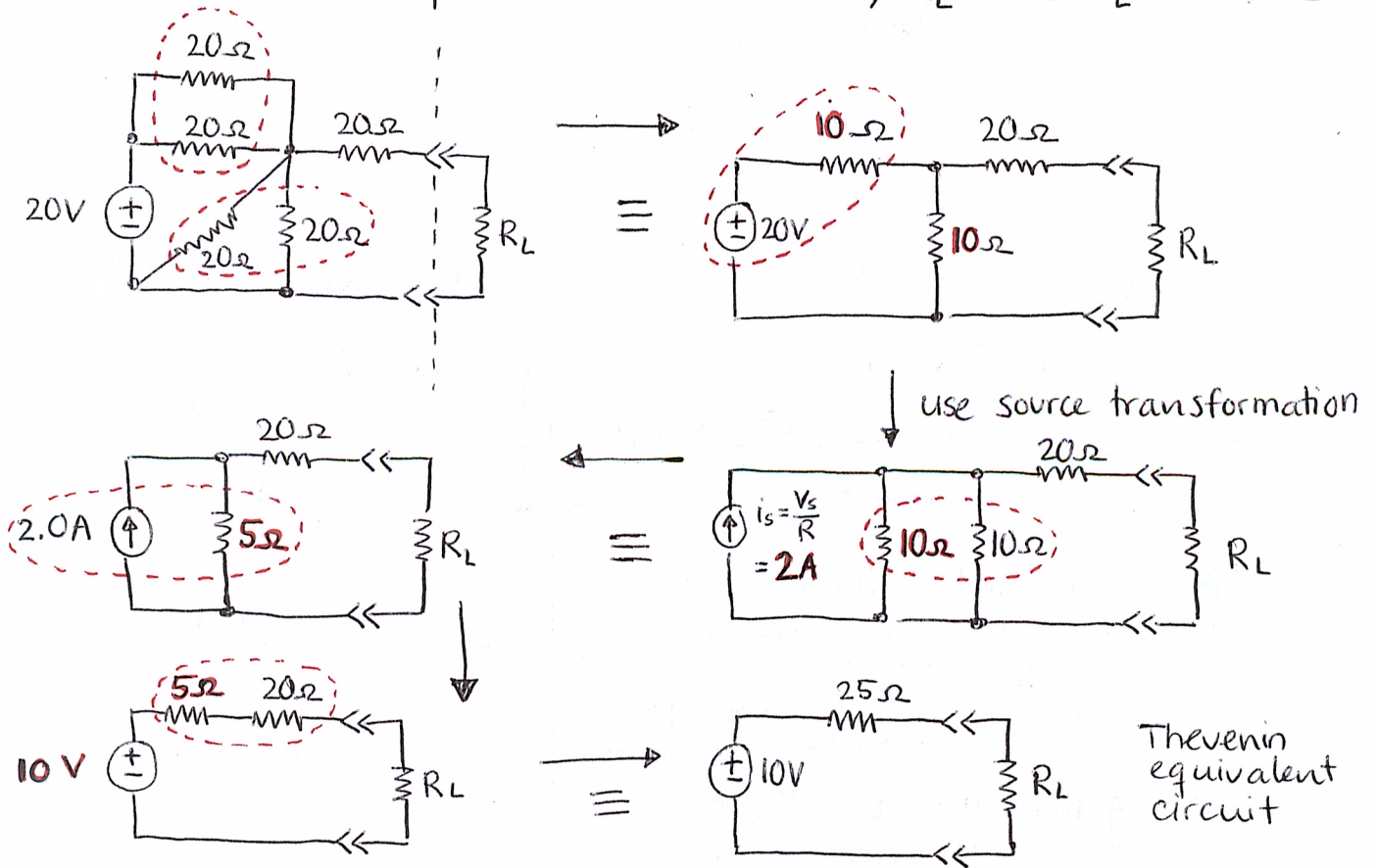


Use voltage divider to find voltage across R_L

$$V_L = \frac{R_L}{R_L + 25\Omega} 10V$$


$V_L (R_L = 5\Omega) =$	1.67 V
$V_L (R_L = 10\Omega) =$	2.86 V
$V_L (R_L = 20\Omega) =$	4.44 V

3,56

3/9

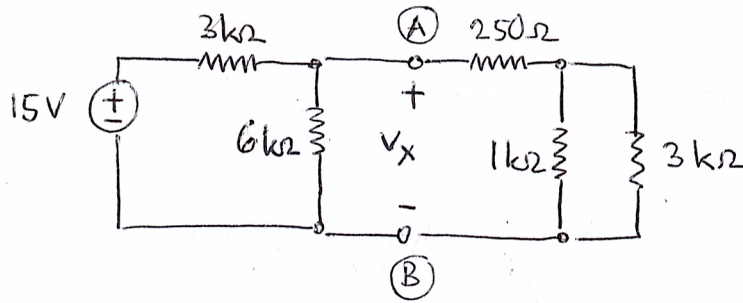

To the left of A and B

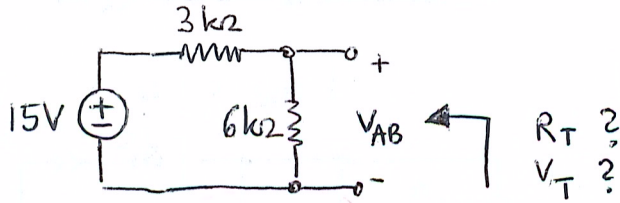




Open circuit yields Thévenin voltage, so using voltage division we obtain

$$V_T = V_{AB} = \frac{6 \text{ k}\Omega}{3 \text{ k}\Omega + 6 \text{ k}\Omega} 15 \text{ V} = \underline{\underline{10 \text{ V}}}$$


Looking from A and B, the two resistors are in parallel so

$$R_T = 3 \text{ k}\Omega \parallel 6 \text{ k}\Omega = \frac{3 \text{ k}\Omega \cdot 6 \text{ k}\Omega}{(3+6) \text{ k}\Omega} = \underline{\underline{2 \text{ k}\Omega}}$$


To the right of A and B

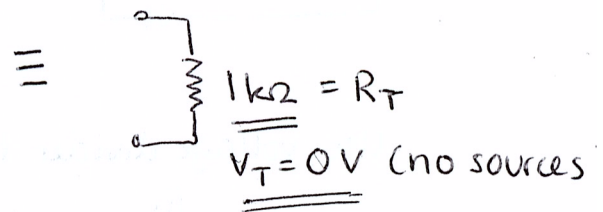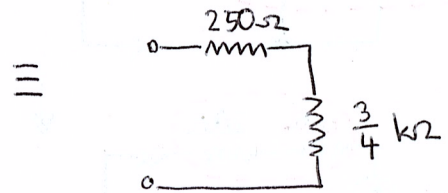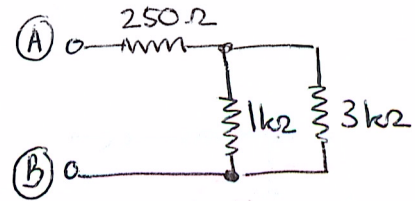

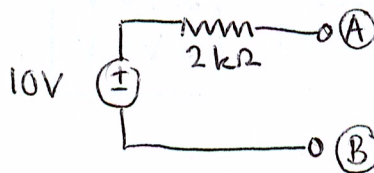Thus, we have for the Norton equ. circuit



connecting both

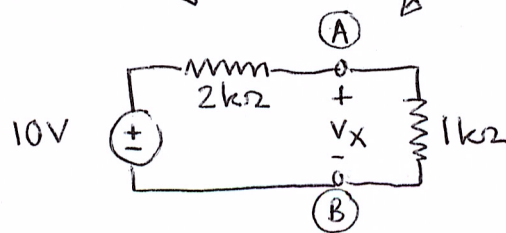


Using voltage division we have

$$V_x = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 2 \text{ k}\Omega} 10 \text{ V}$$

$$\boxed{V_x = 3.33 \text{ V}}$$

3.3 a) Node voltage equation

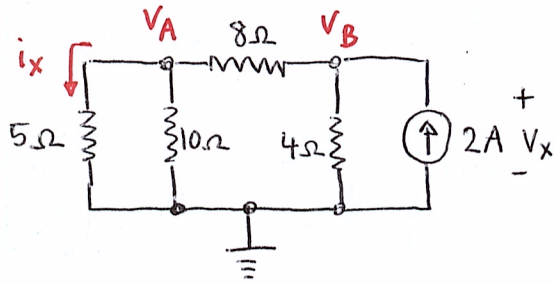

By inspection we can write

$$\begin{bmatrix} \frac{1}{5\Omega} + \frac{1}{10\Omega} + \frac{1}{8\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & \frac{1}{8\Omega} + \frac{1}{4\Omega} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 2A \end{bmatrix} \Leftrightarrow \underbrace{\begin{bmatrix} 0.425\frac{1}{\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & 0.375\frac{1}{\Omega} \end{bmatrix}}_A \underbrace{\begin{bmatrix} V_A \\ V_B \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 0 \\ 2A \end{bmatrix}}_b$$

b) Solve for V_A and V_B . Using Cramer's rule we have

$$V_A = \frac{\begin{vmatrix} 0 & -\frac{1}{8\Omega} \\ 2A & \frac{3}{8\Omega} \end{vmatrix}}{|A|} = \frac{0.25 \frac{A^2}{V}}{0.14375 \frac{A^2}{V^2}} = \boxed{1.74 V}$$


$$V_B = \frac{\begin{vmatrix} 0.425\frac{1}{\Omega} & 0 \\ -\frac{1}{8\Omega} & 2A \end{vmatrix}}{|A|} = \frac{0.85 \frac{A^2}{V}}{0.14375 \frac{A^2}{V^2}} = \boxed{5.91 V}$$

c) Find i_x and v_x

$$i_x = \frac{V_A}{5\Omega} = \boxed{347.8 \text{ mA}}$$

$$v_x = V_B = \boxed{5.91 V}$$

3.4 a)

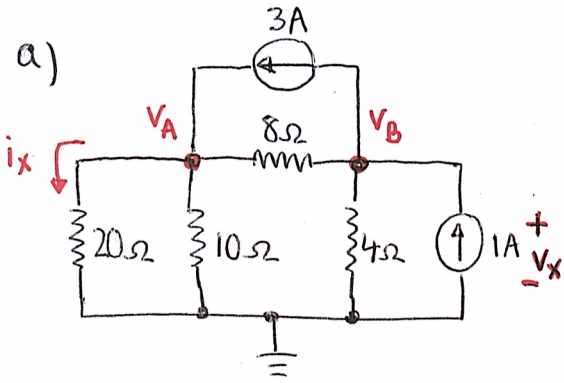

5/9

$$\begin{bmatrix} \frac{1}{20\Omega} + \frac{1}{10\Omega} + \frac{1}{8\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & \frac{1}{8\Omega} + \frac{1}{4\Omega} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 3A \\ 1A - 3A \end{bmatrix}$$

$$\Leftrightarrow \begin{bmatrix} 0.275 \frac{1}{\Omega} & -\frac{1}{8\Omega} \\ -\frac{1}{8\Omega} & 0.375 \frac{1}{\Omega} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 3A \\ -2A \end{bmatrix}$$

$$b) \quad V_A = \frac{\begin{vmatrix} 3A & -\frac{1}{8\Omega} \\ -2A & \frac{3}{8\Omega} \end{vmatrix}}{|A|} = \frac{0.875 \frac{A^2}{V}}{0.0875 \frac{A^2}{V^2}} = \boxed{10V}$$

$$V_B = \frac{\begin{vmatrix} 0.275 \frac{1}{\Omega} & 3A \\ -\frac{1}{8\Omega} & -2A \end{vmatrix}}{|A|} = \frac{-0.175 \frac{A^2}{V}}{0.0875 \frac{A^2}{V^2}} = \boxed{-2V}$$

c) Find i_x and V_x .

$$i_x = \frac{V_A}{20\Omega} = \boxed{0.5A}$$


$$V_x = V_B = \boxed{-2V}$$

3.7 Draw the circuit that is represented by the following equations.


$$\begin{bmatrix} 1 & 0 & 0 \\ -\frac{1}{R_1} & \left(\frac{1}{R_1} + \frac{1}{R_2}\right) & -\frac{1}{R_2} \\ -\frac{1}{R_3} & -\frac{1}{R_2} & \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}\right) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} V_S \\ i_S \\ 0 \end{bmatrix}$$

$V_D = 0$ (GND!)

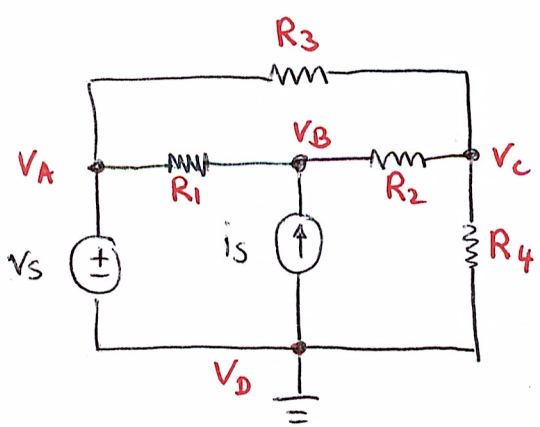means that the circuit contains a voltage source between node A and GND



3.11 a) Formulate node-voltage equations

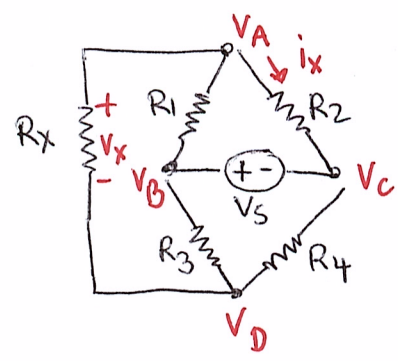

Since the circuit does not have a ground designated, we choose node C as our ground.

Thus, $v_B = v_S$.

Using method 2 (see book p.85) we can write by inspection

$$\begin{array}{c}
 \text{node A} \quad \text{node B} \quad \text{node D} \\
 \text{node A} \quad \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x} & -\frac{1}{R_1} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_x} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_D \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \\
 \text{node D}
 \end{array}$$

and $v_B = v_S$

This can be further reduced to

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_x} \end{bmatrix} \begin{bmatrix} v_A \\ v_D \end{bmatrix} = \begin{bmatrix} \frac{v_S}{R_1} \\ \frac{v_S}{R_3} \end{bmatrix}$$

A x = b

b) Solve for v_x and i_x .

First we solve for v_A and v_D using Cramer's rule or matrix inversion and obtain


$$\begin{aligned}
 v_A &= 5.3266 \text{ V} \\
 v_B &= 9.6774 \text{ V}
 \end{aligned}$$

$$i_x = \frac{v_A}{R_2} = \boxed{10.6452 \text{ mA}}$$

$$v_x = v_A - v_B = \boxed{-4.3548 \text{ V}}$$

3.14 a) Formulate node-voltage equations

7/9

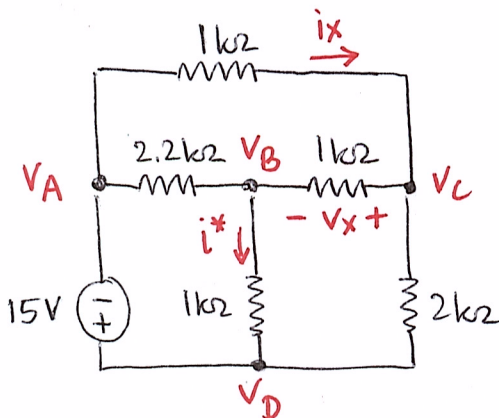

We choose node A as our ground and thus $v_D = +15V$. Using method 2 (see book page 85) we can write by inspection

$$\begin{array}{c} \text{node B} \quad \text{node C} \quad \text{node D} \\ \text{node B} \\ \text{node C} \end{array} \begin{bmatrix} \frac{1}{2.2k} + \frac{1}{1k} + \frac{1}{1k} & -\frac{1}{1k} & -\frac{1}{1k} \\ -\frac{1}{1k} & \frac{1}{1k} + \frac{1}{1k} + \frac{1}{2k} & -\frac{1}{2k} \end{bmatrix} \begin{bmatrix} v_B \\ v_C \\ v_D \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

and $v_D = 15V$

Rearranging yields

$$\underbrace{\begin{bmatrix} \frac{1}{2.2k} + \frac{1}{1k} + \frac{1}{1k} & -\frac{1}{1k} \\ -\frac{1}{1k} & \frac{1}{1k} + \frac{1}{1k} + \frac{1}{2k} \end{bmatrix}}_A \underbrace{\begin{bmatrix} v_B \\ v_C \end{bmatrix}}_x = \underbrace{\begin{bmatrix} \frac{v_D}{1k} \\ \frac{v_D}{2k} \end{bmatrix}}_b$$

b) solve for i_A , i_B and i_C .

First, we solve for v_B and v_C using matrix inversion ($x = A^{-1}b$)

$$v_B = 8.7611 V$$

$$v_C = 6.5044 V$$

$$i_C = i_x = \frac{v_A - v_C}{1k\Omega} = \frac{-6.5044V}{1000 \frac{V}{A}} = \boxed{-6.5044 \text{ mA}}$$

$$i_B = \frac{v_C - v_D}{2k\Omega} = \frac{6.5044V - 15V}{2000 \frac{V}{A}} = \boxed{-4.25 \text{ mA}}$$

$$i^* = \frac{v_B - v_D}{1k\Omega} = i_A - i_B \rightarrow i_A = i_B + \frac{8.7611V - 15V}{1000 \frac{V}{A}} = \boxed{-10.4889 \text{ mA}}$$


c) Find v_x and i_x

$$i_x = i_C = \boxed{-6.5044 \text{ mA}}$$

$$v_x = v_C - v_B = \boxed{-2.2567 V}$$

3.22 b) formulate node-voltage equations

8/9

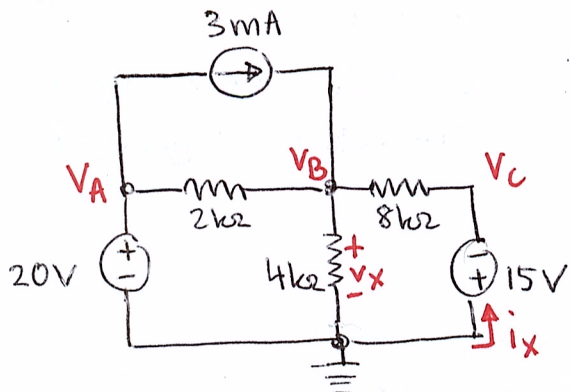

Because of the two voltage sources in the circuit we know that

$$V_A = 20V \quad \text{and} \quad V_C = -15V$$

Thus, we can write by inspection

$$\begin{array}{c} \text{node A} \quad \text{node B} \quad \text{node C} \\ \text{node B} \end{array} \begin{bmatrix} -\frac{1}{2k\Omega} & \frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{8k\Omega} & -\frac{1}{8k\Omega} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = 3mA$$

with $V_A = 20V$
 $V_C = -15V$

Rearranging yields

$$\left[\frac{1}{2k\Omega} + \frac{1}{4k\Omega} + \frac{1}{8k\Omega} \right] V_B = 3mA + \frac{V_A}{2k\Omega} + \frac{V_C}{8k\Omega}$$


d) Find v_x and i_x .

First we have to solve for V_B : $V_B = 12.7143V$

$$V_x = V_B = 12.7143V$$

$$i_x = \frac{V_C - V_B}{8k\Omega} = \frac{-15V - 12.7143V}{8000 \frac{V}{A}} = -3.5mA$$

3.24

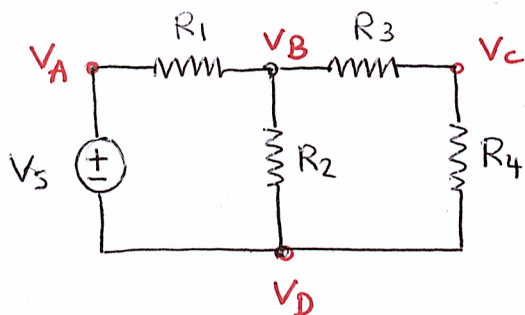

9/9

$$R_1 = R_2 = R_3 = R_4 = 1 \text{ k}\Omega$$

$$V_S = 10 \text{ V}$$

$V_C = -2 \text{ V}$ when V_B is connected to ground

Note that we already know the voltage at node C [$V_C = -2 \text{ V}$] and that $V_A - V_D = V_S = 10 \text{ V}$.

Thus, we can write by inspection (using method 3)
↳ 'supernode'

$$\begin{array}{c} \text{node A} \quad \text{node C} \quad \text{node D} \\ \text{node C} \end{array} \begin{bmatrix} 0 & \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_C \\ V_D \end{bmatrix} = 0$$

$$\begin{aligned} V_A - V_D &= V_S \\ V_C &= -2 \text{ V} \end{aligned}$$

Rearranging yields

$$\left[-\frac{1}{R_4} \right] V_D = -\left(\frac{1}{R_3} + \frac{1}{R_4} \right) V_C$$

$$V_D = \frac{0.002}{0.001} (-2 \text{ V})$$

$$\boxed{V_D = -4 \text{ V}}$$

$$V_A = V_D + V_S = -4 \text{ V} + 10 \text{ V}$$

$$\boxed{V_A = 6 \text{ V}}$$