

MAE 140 Hw 4 Solutions

3-2

a) Formulate mesh current to get $A\vec{x} = \vec{b}$ form!


Using mesh current analysis, we can get:

$$\begin{aligned} \bar{i}_s &= \bar{i}_\alpha \\ \bar{i}_1 &= \bar{i}_\alpha - \bar{i}_\beta \\ \bar{i}_2 &= \bar{i}_\beta \\ \bar{i}_3 &= \bar{i}_\beta - \bar{i}_\gamma \\ \bar{i}_x &= \bar{i}_\gamma \end{aligned}$$

Using KVL, we can get:

$$\text{KVL } \bar{i}_\beta \rightarrow -\bar{i}_1 R_1 + \bar{i}_2 R_2 + \bar{i}_3 R_3 = 0$$
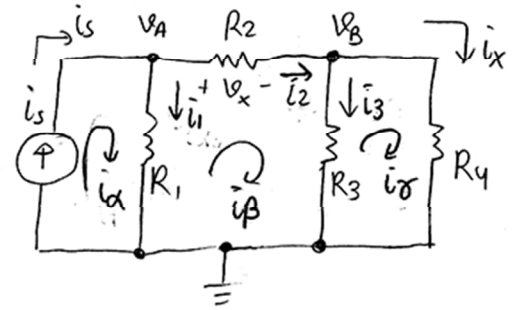
$$\text{KVL } \bar{i}_\gamma \rightarrow -\bar{i}_3 R_3 + \bar{i}_x R_4 = 0$$



Combining both, we can get:

$$\begin{aligned} \bar{i}_\alpha &= i_s \\ -(\bar{i}_\alpha - \bar{i}_\beta) R_1 + \bar{i}_\beta R_2 + (\bar{i}_\beta - \bar{i}_\gamma) R_3 &= 0 \\ -(\bar{i}_\beta - \bar{i}_\gamma) R_3 + \bar{i}_\gamma R_4 &= 0 \end{aligned} \rightarrow \begin{bmatrix} 1 & 0 & 0 \\ -R_1 & R_1 + R_2 + R_3 & -R_3 \\ 0 & -R_3 & R_3 + R_4 \end{bmatrix} \begin{bmatrix} \bar{i}_\alpha \\ \bar{i}_\beta \\ \bar{i}_\gamma \end{bmatrix} = \begin{bmatrix} \bar{i}_s \\ 0 \\ 0 \end{bmatrix}$$

$\hookrightarrow A\vec{x} = \vec{b}$

b) Solve for v_A and v_B !Using $\bar{i}_\alpha = i_s$, we can reduce the matrix into =

$$\begin{bmatrix} R_1 + R_2 + R_3 & -R_3 \\ -R_3 & R_3 + R_4 \end{bmatrix} \begin{bmatrix} \bar{i}_\beta \\ \bar{i}_\gamma \end{bmatrix} = \begin{bmatrix} R_1 i_s \\ 0 \end{bmatrix} \rightarrow A_2 \vec{x}_2 = \vec{b}_2$$

Solving for $\vec{x}_2 = A_2^{-1} \vec{b}_2$, we can get:

$$\begin{bmatrix} \bar{i}_\beta \\ \bar{i}_\gamma \end{bmatrix} = \frac{1}{(R_1 + R_2 + R_3)(R_3 + R_4) - R_3^2} \begin{bmatrix} R_3 + R_4 & R_3 \\ R_3 & R_1 + R_2 + R_3 \end{bmatrix} \begin{bmatrix} R_1 i_s \\ 0 \end{bmatrix}$$

$$\hookrightarrow \begin{bmatrix} \hat{i}_\beta \\ \hat{i}_\gamma \end{bmatrix} = \frac{\hat{i}_s}{(R_1+R_2)(R_3+R_4)+R_3R_4} \begin{bmatrix} R_1(R_3+R_4) \\ R_1R_3 \end{bmatrix}$$

Then $V_A = \hat{i}_1 R_1 = (\hat{i}_\alpha - \hat{i}_\beta) R_1$

$$V_A = i_s \left(1 - \frac{R_1(R_3+R_4)}{(R_1+R_2)(R_3+R_4)+R_3R_4} \right) R_1 = \frac{R_2(R_3+R_4)+R_3R_4}{(R_1+R_2)(R_3+R_4)+R_3R_4} R_1 i_s$$

$$V_B = i_x R_4 = \hat{i}_\gamma R_4 \rightarrow V_B = \frac{i_s R_1 R_3 R_4}{(R_1+R_2)(R_3+R_4)+R_3R_4}$$

c) Solve for V_x and i_x !

$$V_x = V_A - V_B = i_s \left[\frac{R_1 R_2 (R_3+R_4)}{(R_1+R_2)(R_3+R_4)+R_3R_4} \right]$$

$$\hat{i}_x = \hat{i}_\gamma = \frac{i_s R_1 R_3}{(R_1+R_2)(R_3+R_4)+R_3R_4}$$

3-4

a) Formulate mesh current!


$$\hat{i}_x = -\hat{i}_\beta \quad 1A = -\hat{i}_\gamma$$

$$3A = -\hat{i}_\alpha$$

$$\hat{i}_1 = \hat{i}_\beta - \hat{i}_\gamma$$

$$\hat{i}_2 = \hat{i}_\gamma - \hat{i}_\alpha = \hat{i}_\gamma + 3A$$
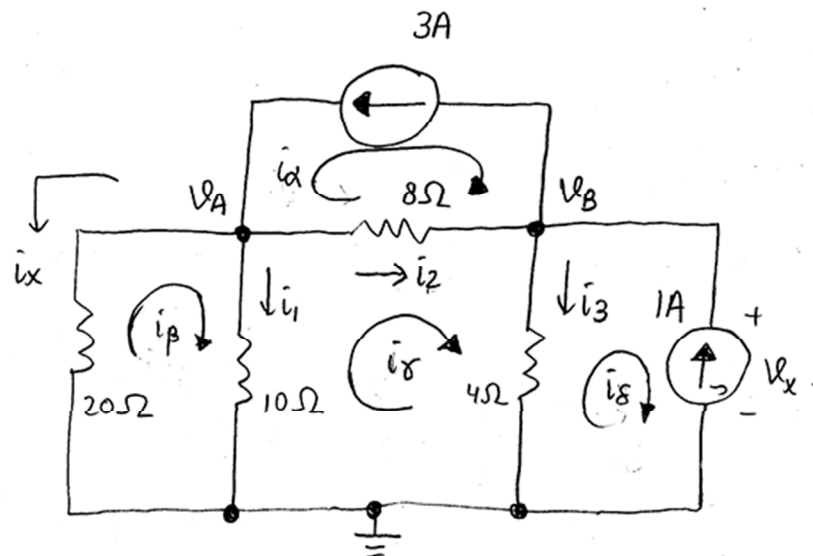
$$\hat{i}_3 = -\hat{i}_\gamma - \hat{i}_\beta = \hat{i}_\gamma + 1A$$



→ Unknowns: $\hat{i}_\beta, \hat{i}_\gamma$

$$\text{KVL } i_\beta \rightarrow -i_4(10\Omega) - i_x(20\Omega) = 0$$

$$-(i_\beta - i_x)(10\Omega) + i_\beta(20\Omega) = 0 \rightarrow -(20\Omega + 10\Omega)i_\beta + (10\Omega)i_x = 0$$

$$\text{KVL } i_x \rightarrow -i_3(4\Omega) + i_2(8\Omega) - i_4(10\Omega) = 0$$

$$-(i_x + 1A)(4\Omega) + (i_x + 3A)(8\Omega) + (i_\beta - i_x)(10\Omega) = 0$$

$$(-10\Omega)i_\beta + (4\Omega + 8\Omega + 10\Omega)i_x = -4V - 24V$$

So, we have:

$$\begin{bmatrix} 30\Omega & -10\Omega \\ -10\Omega & 22\Omega \end{bmatrix} \begin{bmatrix} i_\beta \\ i_x \end{bmatrix} = \begin{bmatrix} 0 \\ -28V \end{bmatrix} \rightarrow \begin{bmatrix} i_\beta \\ i_x \end{bmatrix} = \begin{bmatrix} -0.5A \\ -1.5A \end{bmatrix}$$

b) Solve for V_A and V_B !

$$V_A = (-i_\beta)(20\Omega) = (0.5A)(20\Omega) = \underline{\underline{10V}}$$

$$V_B = i_3(4\Omega) = (1A - 1.5A)4\Omega = \underline{\underline{-2V}}$$

c) Solve for V_x and i_x !


$$V_x = V_B = -2V$$

$$i_x = -i_\beta = 0.5A$$

3-9

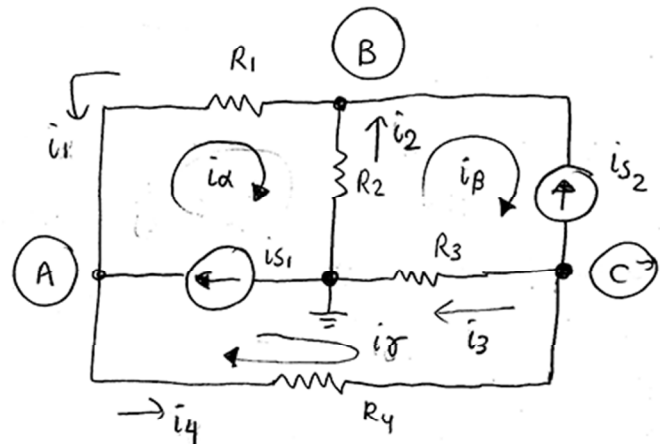a) Formulate mesh current!

$$\begin{aligned} -i_{s1} &= i_\alpha - i_x & i_4 &= +i_x \\ i_{s2} &= -i_\beta \\ i_1 &= -i_\alpha \\ i_2 &= i_\beta - i_\alpha \\ i_3 &= i_\beta - i_x \end{aligned}$$




4/11

You might want to avoid the current sources for the KVL

$$\hookrightarrow -(\dot{i}_4 R_4 + \dot{i}_3 R_3 + \dot{i}_2 R_2 + \dot{i}_1 R_1) = 0$$
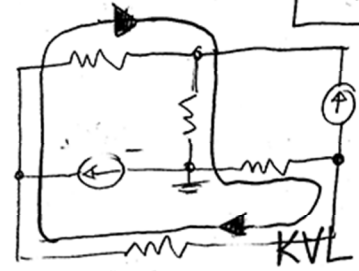
$$(\dot{i}_\alpha) R_1 + (\dot{i}_\alpha - \dot{i}_\beta) R_2 + (\dot{i}_\beta - \dot{i}_\gamma) R_3 + (\dot{i}_\gamma) R_4 = 0$$



So, we have :

$$\begin{bmatrix} +1 & 0 & -1 \\ 0 & -1 & 0 \\ R_1+R_2 & -R_2-R_3 & R_3+R_4 \end{bmatrix} \begin{bmatrix} \dot{i}_\alpha \\ \dot{i}_\beta \\ \dot{i}_\gamma \end{bmatrix} = \begin{bmatrix} \dot{i}_{s1} \\ \dot{i}_{s2} \\ 0 \end{bmatrix}$$

b) Solve symbolically with Matlab for the node voltages!

$$\hookrightarrow \begin{bmatrix} \dot{i}_\alpha \\ \dot{i}_\beta \\ \dot{i}_\gamma \end{bmatrix} = \begin{bmatrix} \frac{-\dot{i}_{s2}(R_2+R_3) + \dot{i}_{s1}(R_3+R_4)}{R_1+R_2+R_3+R_4} \\ -\dot{i}_{s2} \\ \frac{-\dot{i}_{s1}(R_1+R_2) + \dot{i}_{s2}(R_2+R_3)}{R_1+R_2+R_3+R_4} \end{bmatrix}$$

$$\begin{aligned} \text{KVL } \dot{i}_\alpha &\rightarrow -V_B + \dot{i}_1 R_1 + V_A = 0 \rightarrow V_A = V_B + \dot{i}_\alpha R_1 \\ V_B &= -\dot{i}_2 R_2 = -(\dot{i}_\alpha - \dot{i}_\beta) R_2 \\ V_C &= \dot{i}_3 R_3 = (\dot{i}_\beta - \dot{i}_\gamma) R_3 \end{aligned} \quad \left. \vphantom{\begin{aligned} \text{KVL } \dot{i}_\alpha \\ V_B \\ V_C \end{aligned}} \right\} V_A = \dot{i}_\alpha (R_1 + R_2) - \dot{i}_\beta R_2$$

$$\hookrightarrow \begin{aligned} V_A &= -(R_1 + R_2) \dot{i}_\alpha + R_2 \dot{i}_\beta \\ V_B &= R_2 (\dot{i}_\alpha - \dot{i}_\beta) \\ V_C &= R_3 (\dot{i}_\beta - \dot{i}_\gamma) \end{aligned}$$

c) Solve for V_A, V_B, V_C using $R_1 = 1.5 \text{ k}\Omega, R_2 = 2.2 \text{ k}\Omega, R_3 = 3.3 \text{ k}\Omega, R_4 = 4.7 \text{ k}\Omega, \dot{i}_{s1} = \dot{i}_{s2} = 2 \text{ mA}$!

$$\dot{i}_\alpha = -0.427 \text{ mA}$$

$$\dot{i}_\beta = -2 \text{ mA}$$

$$\dot{i}_\gamma = -1.6 \text{ mA}$$

→

$$V_A = 5.9812 \text{ V}$$

$$V_B = 5.3402 \text{ V}$$

$$V_C = -1.4103 \text{ V}$$

3-11

a) Formulate mesh-current!

$$\bar{i}_1 = i_\beta - i_\alpha \quad \bar{i}_4 = -i_\gamma$$

$$\bar{i}_x = -i_\beta \quad \bar{i}_5 = -i_\alpha$$

$$\bar{i}_3 = i_\gamma - i_\alpha$$

$$\text{KVL } i_\alpha \rightarrow -i_1 R_1 + \bar{i}_3 R_3 + \bar{i}_5 R_x = 0$$

$$(i_\alpha - i_\beta) R_1 + (i_\alpha - i_\gamma) R_3 + i_\alpha R_x = 0$$

$$\text{KVL } i_\beta \rightarrow +i_x R_2 + i_1 R_1 - \bar{v}_s = 0$$

$$-i_\beta R_2 + (i_\beta - i_\alpha) R_1 = +\bar{v}_s$$

$$\text{KVL } i_\gamma \rightarrow +\bar{i}_3 R_3 + i_4 R_4 + \bar{v}_s = 0$$

$$(i_\gamma - i_\alpha) R_3 + i_\gamma R_4 = -\bar{v}_s$$

$$\hookrightarrow \begin{bmatrix} R_1 + R_3 + R_x & -R_1 & -R_3 \\ -R_1 & R_2 + R_1 & 0 \\ -R_3 & 0 & R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \\ i_\gamma \end{bmatrix} = \begin{bmatrix} 0 \\ +\bar{v}_s \\ -\bar{v}_s \end{bmatrix}$$

b) Solve for \bar{v}_x , i_x using $R_1 = R_4 = 2k\Omega$, $R_2 = R_3 = 500\Omega$, $R_x = 750\Omega$, $\bar{v}_s = 15V$!

Matrix becomes:

$$\begin{bmatrix} 3250\Omega & -2000\Omega & -500\Omega \\ -2000\Omega & 2500\Omega & 0 \\ -500\Omega & 0 & 2500\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 0 \\ -15V \\ -15V \end{bmatrix}$$



(with Matlab)

$$\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -5.8 \text{ mA} \\ 10.6 \text{ mA} \\ -4.8 \text{ mA} \end{bmatrix}$$

$$\bar{v}_x = i_5 R_x = (-i_\alpha) R_x = (-5.8 \text{ mA})(750\Omega)$$

$$\rightarrow \bar{v}_x = -4.35V$$
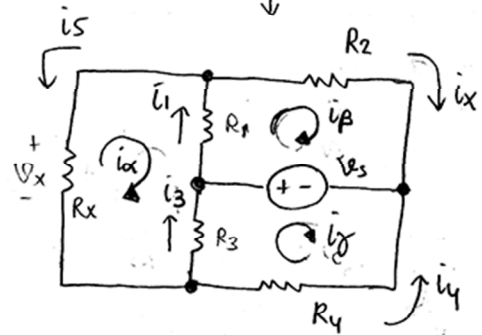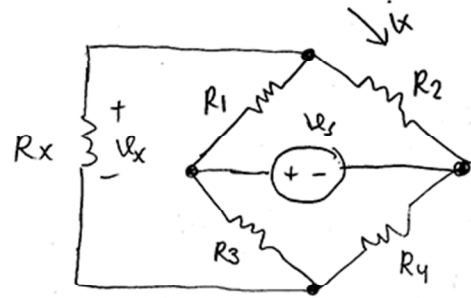
$$\bar{i}_x = i_\beta \rightarrow \bar{i}_x = 10.6 \text{ mA}$$



3-17

a) Formulate mesh-current!

$$\bar{i}_1 = \bar{i}_B - \bar{i}_A$$

$$\bar{i}_4 = \bar{i}_C$$

$$\bar{i}_2 = \bar{i}_C - \bar{i}_A$$

$$\bar{i}_x = -\bar{i}_B$$

$$\bar{i}_3 = \bar{i}_C - \bar{i}_B$$

mesh KVL =

$$\text{KVL } \bar{i}_A \rightarrow -V_S - \bar{i}_2 R_A - \bar{i}_1 R_B = 0 \rightarrow (\bar{i}_A - \bar{i}_C) R_A + (\bar{i}_A - \bar{i}_B) R_B = V_S$$

$$\text{KVL } \bar{i}_B \rightarrow \bar{i}_1 R_B - \bar{i}_3 R_C - \bar{i}_x R_D = 0 \rightarrow (\bar{i}_B - \bar{i}_A) R_B + (\bar{i}_B - \bar{i}_C) R_C + \bar{i}_B R_D = 0$$

$$\text{KVL } \bar{i}_C \rightarrow \bar{i}_4 R_E + \bar{i}_2 R_A + \bar{i}_3 R_C = 0 \rightarrow \bar{i}_C R_E + (\bar{i}_C - \bar{i}_A) R_A + (\bar{i}_C - \bar{i}_B) R_C = 0$$

Matrix form

↳

$$\begin{bmatrix} R_A + R_B & -R_B & -R_A \\ -R_B & R_B + R_C + R_D & -R_C \\ -R_A & -R_C & R_A + R_C + R_E \end{bmatrix} \begin{bmatrix} \bar{i}_A \\ \bar{i}_B \\ \bar{i}_C \end{bmatrix} = \begin{bmatrix} V_S \\ 0 \\ 0 \end{bmatrix}$$

c) Which set of equations would be easier and why?


For nodal vs mesh analysis, the nodal analysis can be easier to solve if you choose V_D to be your ground. Then you have a known V_A and V_B , leading to only 2 node equations. mesh still needs 3 equations, so nodal is easier.

d) Using Matlab, find v_x and i_x in terms of mesh current variables!

Using Matlab,

$$\begin{bmatrix} \bar{i}_A \\ \bar{i}_B \\ \bar{i}_C \end{bmatrix} = \frac{1}{\det(A)} \begin{bmatrix} V_S (R_A (R_B + R_C + R_D) + R_C (R_B + R_D + R_E) + R_E (R_D + R_B)) \\ V_S (R_A (R_B + R_C) + R_B (R_C + R_E)) \\ V_S (R_A (R_B + R_C + R_D) + R_B R_C) \end{bmatrix}$$
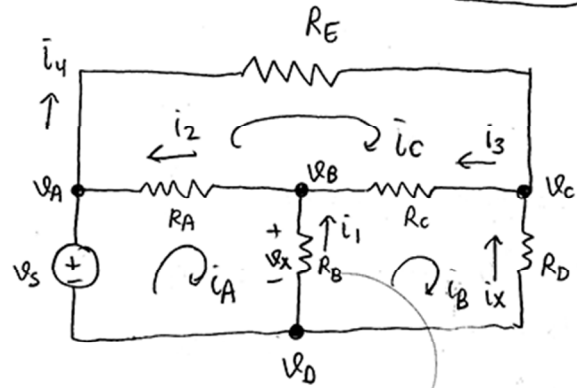
$$\det(A) = R_A (R_B R_D + R_B R_E + R_C R_D + R_C R_E + R_D R_E) + R_B (R_C R_D + R_C R_E + R_D R_E)$$



Now, we have:

$$\bar{i}_x = -i_\beta \rightarrow$$

$$\bar{i}_x = - \frac{R_A(R_B + R_C) + R_B(R_C + R_E)}{\det(A)} \cdot v_s$$

$$v_x = (\bar{i}_x - i_\beta) R_B \rightarrow$$

$$v_x = \frac{R_A R_D + R_C(R_D + R_E) + R_E R_D}{\det(A)} \cdot R_B v_s$$

3-23

Use mesh current to find R_{in} !

$$\begin{aligned} i_1 &= \bar{i}_\alpha & i_4 &= \bar{i}_\alpha - i_\gamma \\ i_2 &= i_\beta & i_5 &= i_\gamma - i_\beta \\ i_3 &= \bar{i}_\alpha - i_\beta & i_6 &= i_\gamma \end{aligned}$$

$$\begin{aligned} \text{KVL } i_\alpha &\rightarrow -v_s + i_1 R + i_3 R + i_4 R = 0 \\ &R(i_\alpha + i_\alpha - i_\beta + i_\alpha - i_\gamma) = v_s \end{aligned}$$

$$\begin{aligned} \text{KVL } i_\beta &\rightarrow -i_3 R + i_2 R - i_5 R = 0 \\ &R(i_\beta - i_\alpha + i_\beta + i_\beta - i_\gamma) = 0 \end{aligned}$$

$$\begin{aligned} \text{KVL } i_\gamma &\rightarrow -i_4 R + i_5 R + i_6 R = 0 \\ &R(i_\gamma - i_\alpha + i_\gamma - i_\beta + i_\gamma) = 0 \end{aligned}$$


$$\text{By definition, } R_{in} = \frac{v_s}{i_1} = \frac{v_s}{\bar{i}_\alpha}$$

Solving \bar{i}_α using Matlab \rightarrow

$$\bar{i}_\alpha = \frac{v_s}{2R}$$

Therefore,

$$R_{in} = 2R$$

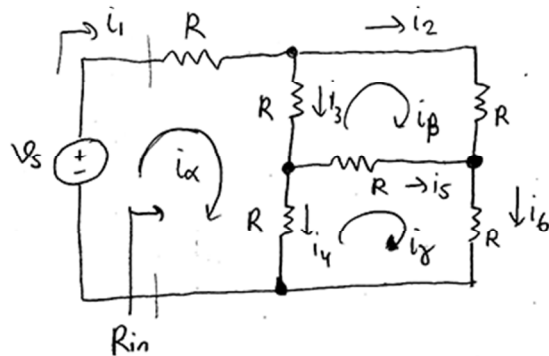


Matrix form:

$$\begin{bmatrix} 3R & -R & -R \\ -R & 3R & -R \\ -R & -R & 3R \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \\ i_\gamma \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \\ 0 \end{bmatrix}$$

3-24

$$R_1 = 1\text{k}\Omega, V_s = 10\text{V}, V_c = -2\text{V} \text{ when } V_B = 0$$

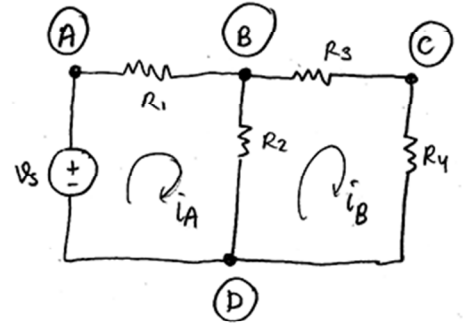Find V_A, V_D, i_A, i_B !

$$\text{mesh A} \rightarrow -V_s + i_A R_1 + (i_A - i_B) R_2 = 0$$

$$\text{mesh B} \rightarrow (i_B - i_A) R_2 + (R_3 + R_4) i_B = 0$$

Matrix form \rightarrow

$$\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$

Plugging in the values \rightarrow

$$\begin{bmatrix} 2\text{k}\Omega & -1\text{k}\Omega \\ -1\text{k}\Omega & 3\text{k}\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 10\text{V} \\ 0 \end{bmatrix}$$

$$i_A = 6\text{mA}$$

$$i_B = 2\text{mA}$$

$$\rightarrow V_A = i_A R_1 = 6\text{mA}(1\text{k}\Omega) = \underline{\underline{6\text{V}}}$$

$$V_D = (i_B - i_A) R_2 = (2\text{mA} - 6\text{mA})(1\text{k}\Omega) = \underline{\underline{-4\text{V}}}$$

(Note that we can solve i_B directly because V_B and V_C are known)

3-25

$$\rightarrow i_B = -\frac{V_C - V_B}{R_3} \rightarrow (R_1 + R_2) i_A = V_s + R_2 i_B \rightarrow \text{alternative sol.}$$

a) Use Matlab to find symbolic expression for i_A for Prob 3-24!

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \frac{V_s}{\det(A)} \begin{bmatrix} R_2 + R_3 + R_4 \\ R_2 \end{bmatrix}$$

$$\det(A) = R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)$$

$$\rightarrow i_A = \frac{R_2 + R_3 + R_4}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2} V_s$$

or use $i_B = -\frac{V_C - V_B}{R_3}$ and solve for


$$i_A = \frac{V_s + R_2 i_B}{R_1 + R_2}$$

mentioned
above

b) Compute ratio of \bar{i}_A/v_s !

$$\frac{\bar{i}_A}{v_s} = \frac{R_2 + R_3 + R_4}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

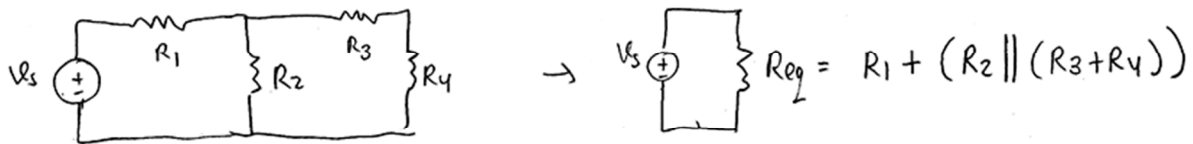c) Find symbolic expression for equivalent circuit using series/parallel resistance!



$$\rightarrow R_{eq} = R_1 + \left(\frac{1}{R_2} + \frac{1}{R_3 + R_4} \right)^{-1} = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}$$

$$= \frac{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)}{R_1 + R_2 + R_3} = \frac{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}{R_1 + R_2 + R_3}$$

$$\frac{\bar{i}_A}{v_s} = \frac{1}{R_{eq}} = \frac{R_1 + R_2 + R_3}{(R_1 + R_2)(R_3 + R_4) + R_1 R_2}$$

→ Same as b)


3-92

Find the power delivered to the load with & without the attenuator!

Using mesh, we have:

$$i_x = i_\beta, \quad \text{mesh } \alpha \rightarrow -v_s + i_\alpha(600\Omega + 300\Omega + 450\Omega) - i_\beta(450\Omega) = 0$$
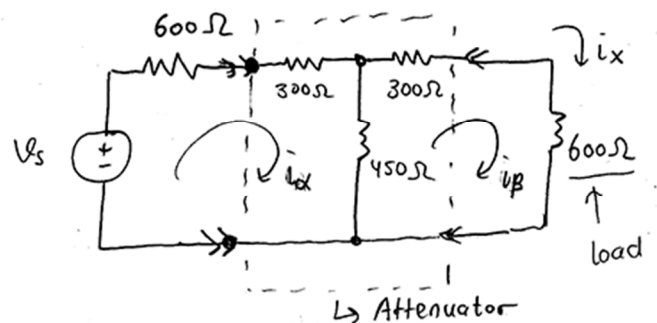
$$\text{mesh } \beta \rightarrow i_\beta(450\Omega + 300\Omega + 600\Omega) - i_\alpha(450\Omega) = 0$$



$$\rightarrow \begin{bmatrix} 1350 \Omega & -450 \Omega \\ -450 \Omega & 1350 \Omega \end{bmatrix} \begin{bmatrix} i_x \\ i_\beta \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix} \rightarrow \begin{bmatrix} i_x \\ i_\beta \end{bmatrix} = \begin{bmatrix} V_s / 1200 \Omega \\ V_s / 3600 \Omega \end{bmatrix}$$

So, we have $P_w = i_x^2 \cdot R_{load} = (V_s / 3600 \Omega)^2 (600 \Omega) = \boxed{\frac{1}{21600 \Omega} V_s^2}$

Without attenuator, the circuit is simply \rightarrow

$$i_x = \frac{V_s}{1200 \Omega} \rightarrow P_{w/o} = i_x^2 R_{load} = \left(\frac{V_s}{1200 \Omega}\right)^2 (600 \Omega)$$



$$P_{w/o} = \frac{1}{2400 \Omega} V_s^2$$

$$\frac{P_w}{P_{w/o}} = \frac{1/21600}{1/2400} = \boxed{\frac{1}{9}}$$

Attenuator reduces power by



$$\log_{10} (1/9) \cdot 20 \text{ dB} = \boxed{-19.08 \text{ dB}}$$

3-96


Want $P = 25 \text{ mW} \pm 10\%$ to the R_L . Which one is better? What if $P = 25 \text{ mW} \pm 5\%$?

Note that the source can be simplified.

So, we have

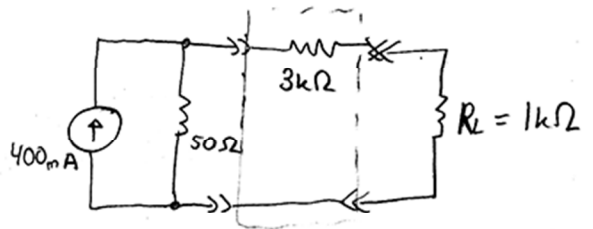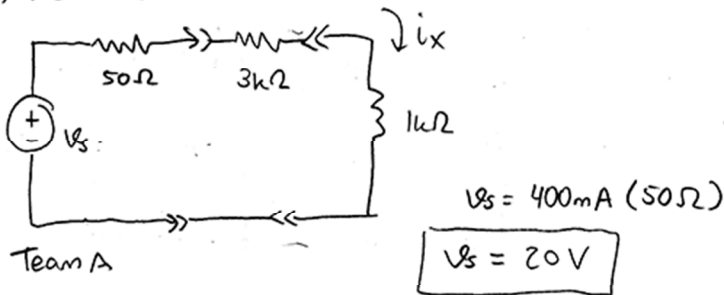

Team A

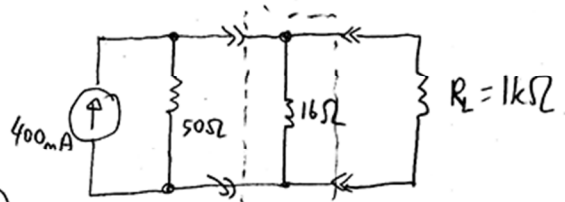

Team B

11/11


So, we have =

Team A
$$i_x = \frac{V_s}{50\Omega + 3k\Omega + 1k\Omega} = \underline{4.9 \text{ mA}} \rightarrow P_A = i_x^2 R_L = (4.9 \text{ mA})^2 (1k\Omega)$$

$P_A = 24.4 \text{ mW}$

Team B

Using mesh, we have:

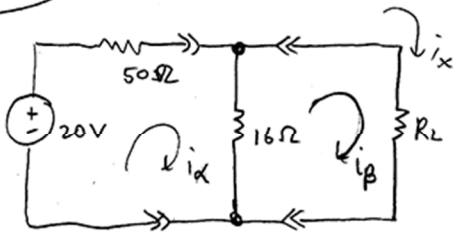

$$i_A \rightarrow -20V + (50\Omega + 16\Omega) i_A - (16\Omega) i_B = 0$$

$$i_B \rightarrow (16\Omega + 1k\Omega) i_B - (16\Omega) i_A = 0$$

$$\rightarrow \begin{bmatrix} 66\Omega & -16\Omega \\ -16\Omega & 1016\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 20V \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 0.3042 \text{ A} \\ 4.8 \text{ mA} \end{bmatrix}$$

$$\rightarrow i_x = 4.8 \text{ mA}$$

$$P_B = i_x^2 R_L = (4.8 \text{ mA})^2 (1k\Omega)$$

$$P_B = 23 \text{ mW}$$

For $P = 25 \text{ mW} \pm 10\%$, we have a range of $P_1 \in [22.5 \text{ mW}, 27.5 \text{ mW}]$

For $P = 25 \text{ mW} \pm 5\%$, we have a range of $P_2 \in [23.75 \text{ mW}, 26.25 \text{ mW}]$

Both team uses the same amount of components. Both team fulfilled the $\pm 10\%$ power requirement, but team B's design used less power. The $\pm 5\%$ power requirement is only fulfilled by team A.

\rightarrow Choose Team B for $\pm 10\%$, Team A for $\pm 5\%$