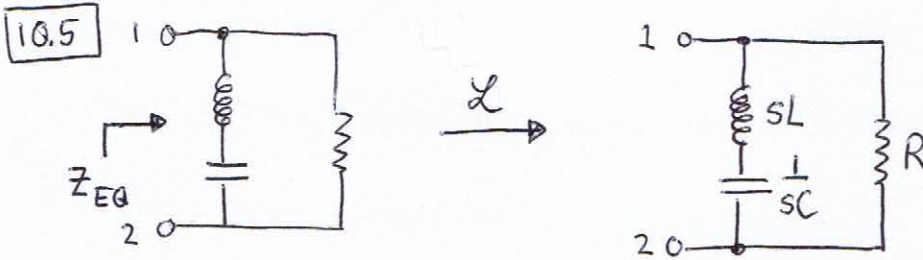


10.5 10.7 10.9 10.15 10.18 10.22 10.27 10.32 10.58 10.68



$$a) Z_{EQ} = (sL + \frac{1}{sC}) \parallel R = \left(\frac{1 + s^2LC}{sC} \right) \parallel R$$

$$= \frac{\frac{(1 + s^2LC)R}{sC}}{\frac{1 + s^2LC}{sC} + R} = \frac{R + s^2LCR}{1 + sRC + s^2LC} = Z_{EQ}$$

$$Z_{EQ} = \frac{s^2R + \frac{R}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$\rightarrow \text{zeros: } s_{1/2} = \pm j\sqrt{\frac{1}{LC}}$$

$$\text{poles: } s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$s_{1/2} = -\frac{RC \pm \sqrt{R^2C^2 - 4LC}}{2LC}$$

b) $R = 2k\Omega$ and $C = 0.1\mu F$
 want zeros at $\pm j5000 \text{ rad/s}$

$$(5000)^2 = \frac{1}{LC}$$


$$L = \frac{1}{C \cdot 5000^2} = \frac{1}{0.1 \cdot 10^{-6} \cdot 25 \cdot 10^6} = 0.4 \text{ H} = L$$

$$c) s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

$$= -\frac{2 \cdot 10^3}{2 \cdot 0.4} \pm \sqrt{\frac{4 \cdot 10^6}{4 \cdot 0.16} - 5000^2}$$

$$s_{1/2} = -2.5 \cdot 10^3 \pm j4330.1$$

10.7

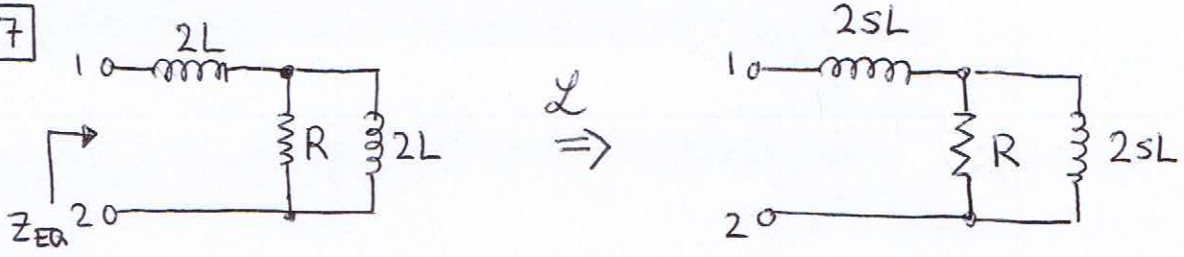

a) $Z_{EQ} = 2sL + R \parallel (2sL) = 2sL + \frac{2sLR}{2sL + R}$

$Z_{EQ} = \frac{4sLR + 4s^2L^2}{2sL + R} = \frac{4sL(R + sL)}{2sL + R} = Z_{EQ}$

zeros: $s_1 = 0$
 $s_2 = -\frac{R}{L}$


poles: $s = -\frac{R}{2L}$

b) Want pole at -2000 rad/s

$2000 = \frac{R}{2L} \Rightarrow L = \frac{R}{4000}$

$L (R = 1k\Omega) = 0.25 H = 250 mH$
 zeros at $s_1 = 0 \quad s_2 = -4000$

10.9

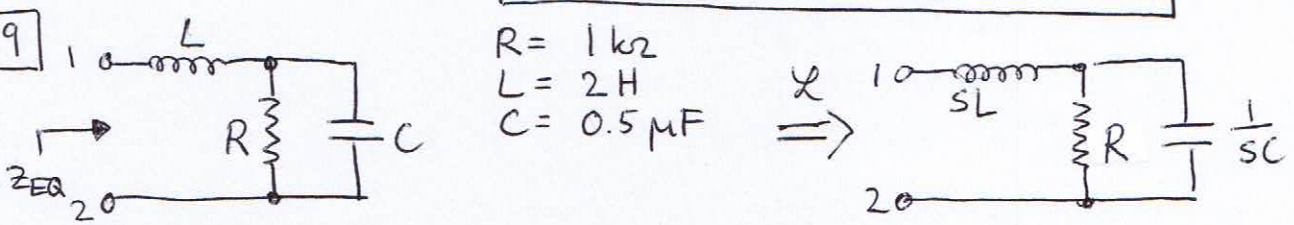

$R = 1k\Omega$
 $L = 2H$
 $C = 0.5 \mu F$

a) $Z_{EQ} = sL + R \parallel \frac{1}{sC} = sL + \frac{\frac{R}{sC}}{\frac{1}{sC} + R} = sL + \frac{R}{1 + sCR} = \frac{R + sL + s^2LCR}{1 + sCR}$

zeros: $s_{1/2} = -\frac{1}{2CR} \pm \sqrt{\frac{1}{4C^2R^2} - \frac{1}{LC}}$

$s_{1/2} = -1000 \pm \sqrt{10^6 - 10^6} \Rightarrow s_1 = s_2 = -1000$

poles: $s = -\frac{1}{CR} = -2000 \text{ rad/s} = s$

b) $L = 5H$


zeros $s_{1/2} = -1000 \pm \sqrt{10^6 - 0.4 \cdot 10^6} = -1000 \pm 774.6$

$s_1 = -1774.6 \quad s_2 = -225.4 \text{ rad/s}$

poles $s = -2000 \text{ rad/s}$ (unchanged)

10.15

3/11

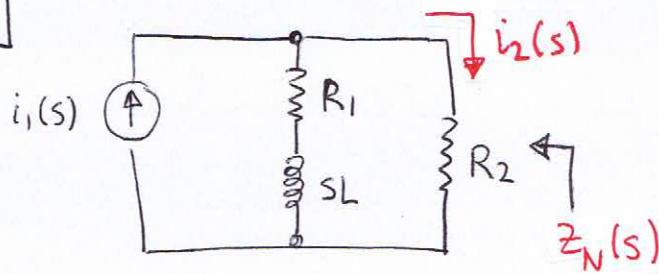


$$a) \frac{i_2(s)}{i_1(s)} = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_1 + sL}} = \frac{\frac{1}{R_2}}{\frac{R_1 + sL + R_2}{R_2(R_1 + sL)}} = \frac{sL + R_1}{R_1 + R_2 + sL}$$

$$\boxed{i_2(s) = \frac{sL + R_1}{sL + R_1 + R_2} i_1(s)}$$

$$b) Z_N(s) = R_2 \parallel (R_1 + sL) = \frac{R_2(R_1 + sL)}{sL + R_1 + R_2} = Z_N(s)$$

10.18

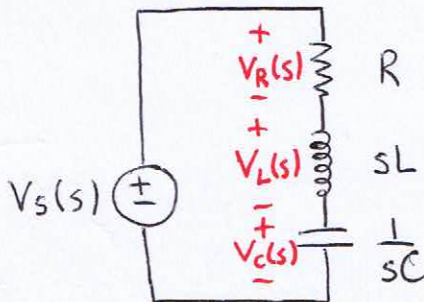

with input $V_s(t) = u(t) \rightarrow \boxed{V_s(s) = \frac{1}{s}}$

a) Using voltage division we can write

$$V_R(s) = \frac{R}{R + sL + \frac{1}{sC}} V_s(s) = \frac{\frac{R}{L}}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$V_L(s) = \frac{s^2}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \cdot \frac{1}{s} = \frac{s}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

$$V_C(s) = \frac{\frac{1}{LC}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \cdot \frac{1}{s} = \frac{\frac{1}{LC}}{s(s^2 + s\frac{R}{L} + \frac{1}{LC})}$$

	zeros	poles
$V_R(s)$	$s_1 = s_2 = \infty$	$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{L^2C^2}}$
$V_L(s)$	$s_1 = 0 \quad s_2 = \infty$	$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{L^2C^2}}$
$V_C(s)$	$s_1 = s_2 = s_3 = \infty$	$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{L^2C^2}}$ $s_3 = 0$

c) Initial and final value theorem

$$\lim_{t \rightarrow 0} v(t) = \lim_{s \rightarrow \infty} sV(s)$$

$$\lim_{t \rightarrow \infty} v(t) = \lim_{s \rightarrow 0} sV(s)$$

R) $\lim_{t \rightarrow 0} v_R(t) = \lim_{s \rightarrow \infty} sV_R(s) = \boxed{0V}$ initial value

$\lim_{t \rightarrow \infty} v_R(t) = \lim_{s \rightarrow 0} sV_R(s) = \boxed{0V}$ final value

L) $\lim_{t \rightarrow 0} v_L(t) = \boxed{1V}$ initial value

$\lim_{t \rightarrow \infty} v_L(t) = \boxed{0V}$ final value

C) $\lim_{t \rightarrow 0} v_C(t) = \boxed{0V}$ initial value


$\lim_{t \rightarrow \infty} v_C(t) = \boxed{1V}$ final value

With input voltage $v_s(t) = u(t)$ the entire voltage drops across L at $t=0$.


At $t=\infty$, the entire voltage drop is observed across the capacitor.

So depending on where you connect the terminals, you can use an RLC circuit to change the output voltage from 0 to 1, 1 to 0, or keep it at 0V.

10.22

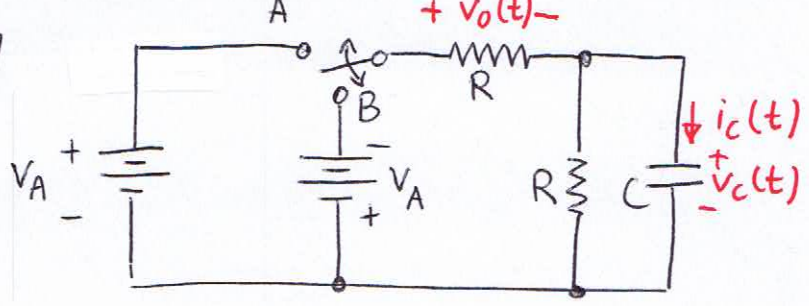

Initial condition (switch in position B)

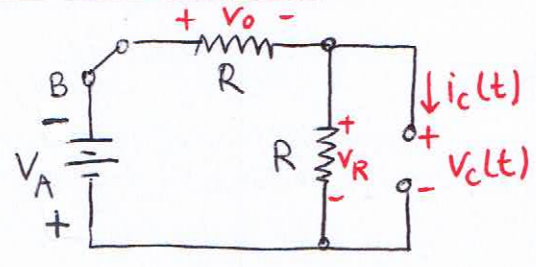


For $t < 0$ the circuit is in DC-steady-state condition and the capacitor acts like an open circuit. Consequently,

$$i_c(0) = 0$$

$$v_c(0) = v_R(t) = \frac{R}{R+R}(-V_A) = -\frac{1}{2}V_A$$

$$v_0(0) = -\frac{1}{2}V_A$$

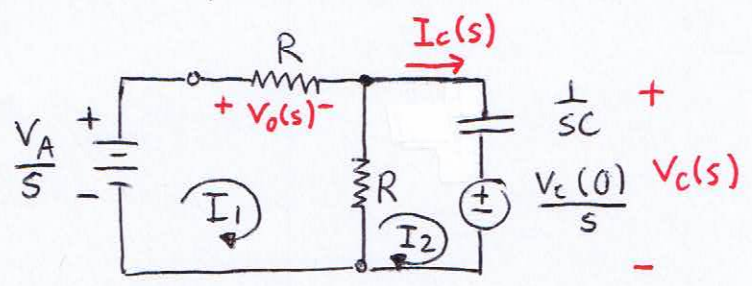Now, transform the circuit into the s-domain for $t > 0$ (switch in position A)



Using mesh-current analysis we can write

$$\underbrace{\begin{bmatrix} R+R & -R \\ -R & R+\frac{1}{sC} \end{bmatrix}}_A \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_X = \underbrace{\begin{bmatrix} \frac{V_A}{s} \\ -\frac{v_c(0)}{s} \end{bmatrix}}_b = \begin{bmatrix} \frac{V_A}{s} \\ \frac{V_A}{2s} \end{bmatrix}$$

$$A^{-1} = \frac{sC}{R(2+sRC)} \begin{bmatrix} \frac{1+sRC}{sC} & R \\ R & 2R \end{bmatrix} \quad \text{(using MATLAB symbolic expressions)}$$

$$X = A^{-1}b = \frac{sC}{R(2+sRC)} \begin{bmatrix} \frac{V_A}{s} \left(\frac{1+sRC}{sC} + \frac{R}{2} \right) \\ \frac{V_A}{s} (R + R) \end{bmatrix}$$

$$\Rightarrow I_1(s) = \frac{sC}{R(2+sRC)} \cdot \frac{V_A}{s} \cdot \frac{1+1.5sRC}{sC} = \frac{1+1.5sRC}{sR(2+sRC)} V_A$$

$$\Rightarrow I_2(s) = \frac{\cancel{RC}}{R(2+sRC)} \cdot \frac{V_A}{\cancel{s}} \cdot \cancel{2R} = \frac{2C}{2+sRC} V_A = \frac{\frac{2}{R}}{s + \frac{2}{RC}} V_A$$

$$I_2(s) = \frac{2}{R} \left(\frac{1}{s + \frac{2}{RC}} \right) V_A$$

Now we can solve for $V_o(s)$, $v_o(t)$, $V_c(s)$ and $v_c(t)$

$$\rightarrow V_o(s) = R I_1(s) = \boxed{\frac{1+1.5sRC}{s(2+sRC)} V_A}$$

$$\rightarrow v_o(t) = \mathcal{L}^{-1}\{V_o(s)\} = \mathcal{L}^{-1}\left\{ \left(\frac{k_1}{s} + \frac{k_2}{s + \frac{2}{RC}} \right) V_A \right\}$$

$$k_1 = s V_o(s) \Big|_{s=0} = \frac{1}{2}$$

$$k_2 = \left(s + \frac{2}{RC} \right) V_o(s) \Big|_{s = -\frac{2}{RC}} = 1$$

$$v_o(t) = \mathcal{L}^{-1}\left\{ \left(\frac{0.5}{s} + \frac{1}{s + \frac{2}{RC}} \right) V_A \right\} = \boxed{\left(\frac{1}{2} + e^{-\frac{2t}{RC}} \right) V_A u(t)}$$

$$\rightarrow V_c(s) = \frac{1}{sC} I_2(s) + \frac{V_c(0)}{s} = \frac{2}{RC} \left(\frac{1}{s(s + \frac{2}{RC})} \right) V_A - \frac{1}{2s} V_A$$

$$= \frac{2}{RC} \left[\frac{k_1}{s} + \frac{k_2}{s + \frac{2}{RC}} \right] V_A - \frac{1}{2s} V_A$$

$$k_1 = \frac{1}{s + \frac{2}{RC}} \Big|_{s=0} = \frac{RC}{2}$$



$$k_2 = \frac{1}{s} \Big|_{s = -\frac{2}{RC}} = -\frac{RC}{2}$$

$$V_c(s) = \left[\frac{1}{s} - \frac{1}{s + \frac{2}{RC}} \right] V_A - \frac{1}{2s} V_A = \boxed{\left[\frac{1}{2s} - \frac{1}{s + \frac{2}{RC}} \right] V_A}$$

$$\rightarrow v_c(t) = \mathcal{L}^{-1}\{V_c(s)\} = \mathcal{L}^{-1}\left\{ \left(\frac{1}{2s} - \frac{1}{s + \frac{2}{RC}} \right) V_A \right\}$$

$$v_c(t) = \boxed{\frac{V_A}{2} \left(1 - 2e^{-\frac{2t}{RC}} \right) u(t)}$$

10.27

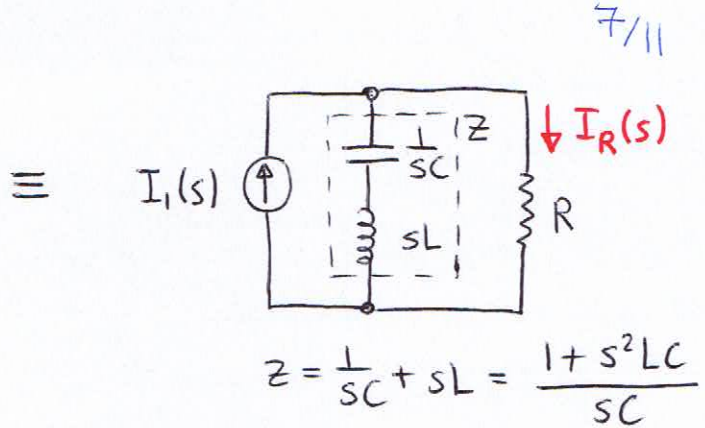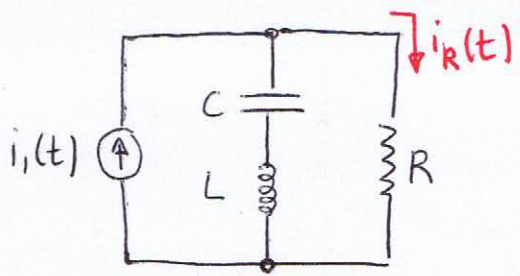

Using current division we can write


$$\frac{I_R(s)}{I_1(s)} = \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{Z}} = \frac{Z}{R+Z} = \frac{\frac{1+s^2 LC}{sC}}{\frac{1+s^2 LC}{sC} + R} = \boxed{\frac{1+s^2 LC}{1+sRC+s^2 LC}}$$

zeros: $s = \pm j\sqrt{\frac{1}{LC}}$


poles: $s^2 + s\frac{R}{L} + \frac{1}{LC} = 0$

$$s_{1/2} = -\frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} - \frac{1}{LC}}$$

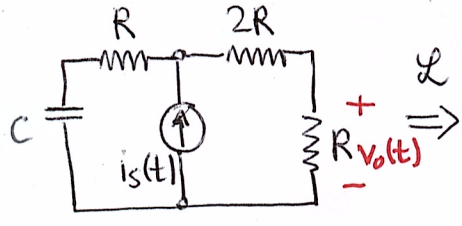10.32 Compute $v_o(t)$ using current division (no initial conditions)



$i_s(t) = 5e^{-500t} u(t) \text{ mA}$

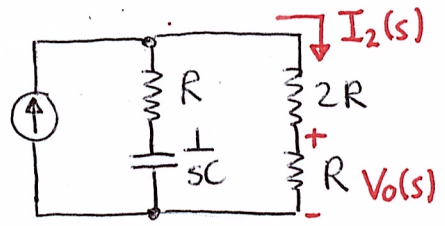

$R = 5 \text{ k}\Omega$
 $C = 0.2 \mu\text{F}$

$I(s) = \frac{0.005}{s+500}$

Using element voltage-current relation we know

$V_o(s) = R I_2(s) \tag{1}$

Calculate $I_2(s)$ using current division

$$\frac{I_2(s)}{I_s(s)} = \frac{\frac{1}{3R}}{\frac{1}{3R} + \frac{1}{R + \frac{1}{sC}}} = \frac{R + \frac{1}{sC}}{3R + R + \frac{1}{sC}} = \frac{R + \frac{1}{sC}}{4R + \frac{1}{sC}} = \frac{s + \frac{1}{RC}}{s + \frac{1}{4RC}} \cdot \frac{1}{4}$$

substituting the expression for $I_2(s)$ in (1) yields

$V_o(s) = \frac{R}{4} \cdot \frac{s + \frac{1}{RC}}{s + \frac{1}{4RC}} \cdot \frac{0.005}{s+500}$

Note: $\frac{1}{RC} = \frac{1}{5 \cdot 10^3 \cdot 0.2 \cdot 10^{-6}} = 10^3$

$V_o(s) = \frac{25}{4} \cdot \frac{s+1000}{(s+250)(s+500)} = \frac{k_1}{s+250} + \frac{k_2}{s+500}$

$k_1 = \lim_{s \rightarrow -250} \frac{25}{4} \cdot \frac{s+1000}{s+500} = \frac{25}{4} \cdot \frac{750}{250} = \frac{75}{4} = 18.75$

$k_2 = \lim_{s \rightarrow -500} \frac{25}{4} \cdot \frac{s+1000}{s+250} = \frac{25}{4} \cdot \frac{500}{-250} = -\frac{50}{4} = -12.5$

$V_o(s) = \frac{18.75}{s+250} - \frac{12.5}{s+500}$

\Rightarrow forced pole at $s = -500 \text{ rad/s}$ *
natural pole at $s = -250 \text{ rad/s}$ **


$V_o(t) = \left\{ 18.75 e^{-250t} - 12.5 e^{-500t} \right\} u(t)$

natural response forced response

* forced by the input $I(s)$

** comes from the transfer function $T(S) = \frac{V_o(s)}{I(s)}$

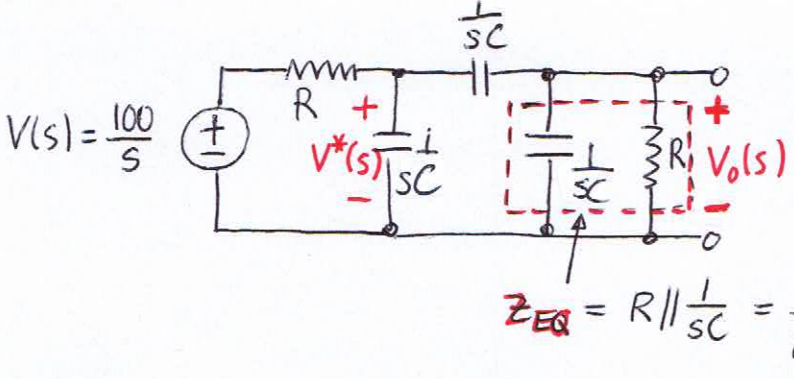10.58 Solve for $V_o(s)$ and $v_o(t)$ (no energy in the circuit)



$$R = 1 \text{ k}\Omega$$

$$C = 0.2 \mu\text{F}$$

$$RC = 0.2 \cdot 10^{-3}$$

$$\frac{1}{RC} = 5000$$

$$Z_{EQ} = R \parallel \frac{1}{sC} = \frac{\frac{R}{sC}}{R + \frac{1}{sC}} = \frac{R}{1 + sRC}$$

$$V_o(s) = \frac{Z_{EQ}}{Z_{EQ} + \frac{1}{sC}} V^*(s) = \frac{\frac{R}{1 + sRC}}{\frac{R}{1 + sRC} + \frac{1}{sC}} V^*(s)$$

$$V_o(s) = \frac{sRC}{1 + 2sRC} V^*(s)$$

Note: You can also use source transformation (see next page)

$$V^*(s) = \frac{\frac{1}{sC} \parallel (\frac{1}{sC} + Z_{EQ})}{\frac{1}{sC} \parallel (\frac{1}{sC} + Z_{EQ}) + R} V(s)$$

$$\frac{1}{sC} \parallel (\frac{1}{sC} + \frac{R}{1 + sRC}) = \frac{1}{sC} \parallel \frac{1 + 2sRC}{sC(1 + sRC)} = \frac{\frac{1}{sC} \cdot \frac{1 + 2sRC}{sC(1 + sRC)}}{\frac{1}{sC} + \frac{1 + 2sRC}{sC(1 + sRC)}}$$

$$= \frac{\frac{1 + 2sRC}{sC(1 + sRC)}}{1 + \frac{1 + 2sRC}{1 + sRC}} = \frac{1 + 2sRC}{sC(1 + sRC + 1 + 2sRC)} = \frac{1 + 2sRC}{sC(2 + 3sRC)}$$

$$V^*(s) = \frac{\frac{1 + 2sRC}{sC(2 + 3sRC)}}{\frac{1 + 2sRC}{sC(2 + 3sRC)} + R} V(s) = \frac{1 + 2sRC}{sCR(2 + 3sRC) + 2sRC + 1} V(s)$$

$$\Rightarrow V_o(s) = \frac{sRC}{1 + 2sRC} \cdot \frac{1 + 2sRC}{sCR[2 + 3sRC + 2 + \frac{1}{sCR}]} \cdot \frac{100}{s}$$

$$V_o(s) = \frac{1}{3sRC + 4 + \frac{1}{sRC}} \cdot \frac{100}{s} = \frac{100}{0.6 \cdot 10^{-3} s^2 + 4s + 5000} \cdot \frac{100}{s}$$

$$V_o(s) = \frac{10^5}{0.6s^2 + 4000s + 5 \cdot 10^6} = \frac{10^5}{\frac{3}{5}(s^2 + s \frac{20}{3} 10^3 + \frac{25}{3} 10^6)}$$

$$V_o(s) = \frac{5}{3} 10^5 \left[\frac{1}{s^2 + \frac{20}{3} 10^3 s + \frac{25}{3} 10^6} \right]$$

$$s_{1/2} = -\frac{10}{3} 10^3 \pm \sqrt{\frac{100}{9} - \frac{75}{9}} 10^3$$

$$\rightarrow s_1 = -\frac{15}{3} 10^3 = -5000$$

$$\rightarrow s_2 = -\frac{5}{3} 10^3 = -1667$$

$$V_o(s) = \frac{5}{3} 10^5 \left[\frac{k_1}{(s+5000)} + \frac{k_2}{s+1667} \right]$$



$$k_1 = \lim_{s \rightarrow -5000} \frac{1}{s+1667} = -30 \cdot 10^{-5}$$

$$k_2 = \lim_{s \rightarrow -1667} \frac{1}{s+5000} = +30 \cdot 10^{-5}$$

$$V_o(s) = 50 \left[\frac{1}{s+1667} - \frac{1}{s+5000} \right]$$


$$V_o(t) = 50 \left[e^{-1667t} - e^{-5000t} \right] u(t)$$

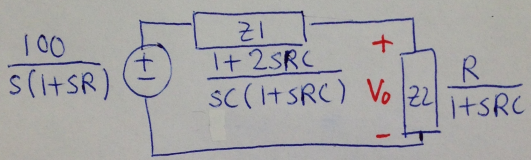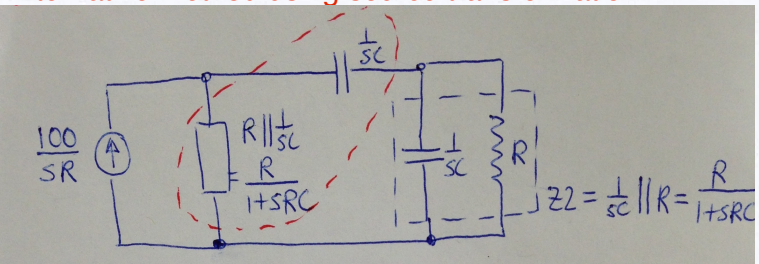Alternative method using source transformation




$$\begin{aligned} \Rightarrow V_o(s) &= \frac{Z_2}{Z_1 + Z_2} \cdot \frac{100}{s(1+SR)} = \frac{\frac{R}{1+SR}}{\frac{R}{1+SR} + \frac{1+2sRC}{sC(1+SR)}} \cdot \frac{100}{s(1+SR)} \\ &= \frac{sRC}{(sRC + 1 + 2sRC)} \cdot \frac{100}{s(1+SR)} \\ &= \frac{100}{3RC} \frac{1}{\left(s + \frac{1}{3RC}\right) \left(s + \frac{1}{RC}\right)} = \frac{5}{3} 10^5 \frac{1}{(s+1667)(s+5000)} \end{aligned}$$

10.68

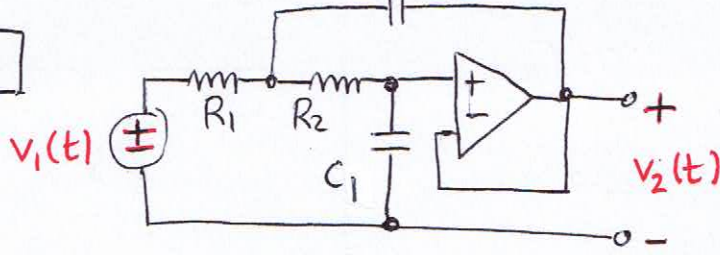

Transforming into s-domain yields

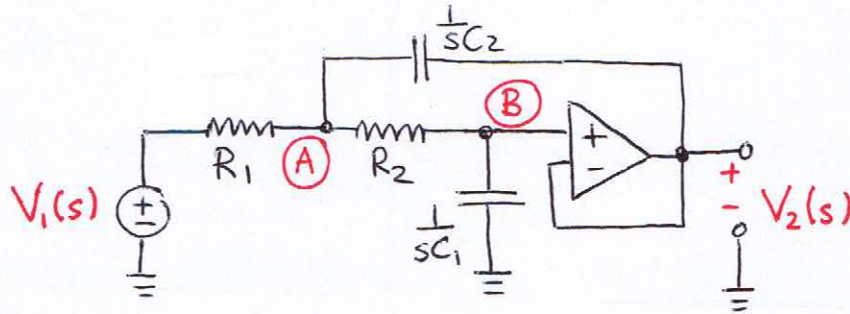

Note that
 $i^+ = i^- = 0$ and thus
 $V^+ = V^- = V_2(s)$

Using KCL at node A yields

$$\frac{V_1(s) - V_A(s)}{R_1} = \frac{V_A(s) - V_2(s)}{\frac{1}{sC_2}} + \frac{V_A(s) - 0V}{R_2 + \frac{1}{sC_1}}$$

$$\frac{1}{R_1} V_1(s) + sC_2 V_2(s) = \left[\frac{1}{R_1} + sC_2 + \frac{sC_1}{1 + sC_1 R_2} \right] V_A \quad (1)$$

Using KCL at node B yields

$$\frac{V_A(s) - V^+(s)}{R_2} = \frac{V^+(s) - 0V}{\frac{1}{sC_1}} \quad V^+ = V^- = V_2(s)$$

$$V_A(s) = (1 + sC_1 R_2) V_2(s) \quad (2)$$

Substitute (2) in (1)

$$\frac{1}{R_1} V_1(s) + sC_2 V_2(s) = \left[\frac{1 + sR_1 C_2}{R_1} + \frac{sC_1}{1 + sR_2 C_1} \right] (1 + sR_2 C_1) V_2(s)$$

$$\frac{1}{R_1} V_1(s) = \left[\frac{1}{R_1} (1 + sR_1 C_2) (1 + sR_2 C_1) + sC_1 - sC_2 \right] V_2(s)$$

$$\frac{V_1(s)}{V_2(s)} = 1 + s^2 R_1 R_2 C_1 C_2 + s(R_1 C_2 + R_2 C_1) + sR_1(C_1 - C_2)$$

$$\frac{V_2(s)}{V_1(s)} = \frac{1}{s^2 R_1 R_2 C_1 C_2 + sC_1(R_1 + R_2) + 1}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{(R_1 R_2 C_1 C_2)^{-1}}{s^2 + s\left(\frac{1}{C_2 R_2} + \frac{1}{C_2 R_1}\right) + \frac{1}{R_1 R_2 C_1 C_2}}$$