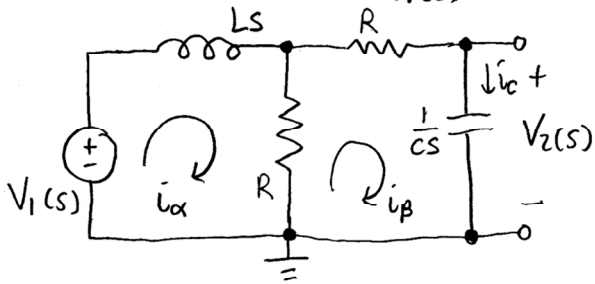


11-9 Find $T_V(s) = \frac{V_2(s)}{V_1(s)}$!



Circuit is already in the impedance form.
Treat each non-source components like resistors.

Mesh Current:

$$\begin{bmatrix} Ls+R & -R \\ -R & R+R+\frac{1}{Cs} \end{bmatrix} \begin{bmatrix} i_\alpha \\ i_\beta \end{bmatrix} = \begin{bmatrix} V_1(s) \\ 0 \end{bmatrix}$$

Solve the mesh current equation (find $i_\beta = \bar{i}_c$ to calculate $V_2(s)$)

$$\rightarrow -Ri_\alpha + (2R + \frac{1}{Cs})i_\beta = 0 \rightarrow i_\alpha = (2 + \frac{1}{RCs})i_\beta$$



$$\rightarrow (Ls+R)i_\alpha - Ri_\beta = 0 \rightarrow (Ls+R)(2 + \frac{1}{RCs})i_\beta - Ri_\beta = V_1(s)$$

$$\bar{i}_\beta = \frac{V_1(s)}{(Ls+R)(2 + \frac{1}{RCs}) - R} = \frac{RCs}{(Ls+R)(1+2RCs) - R^2Cs} \cdot V_1(s)$$

Then $V_2(s) = \frac{1}{Cs} \cdot \bar{i}_\beta = \frac{1}{Cs} \cdot \frac{RCs}{(Ls+R)(1+2RCs) - R^2Cs} \cdot V_1(s)$

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{R}{2LCRs^2 + (L+CR^2)s + R}$$

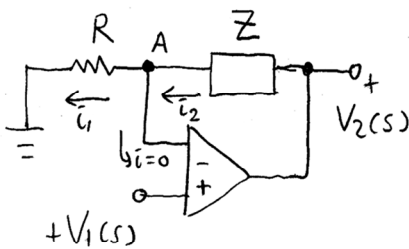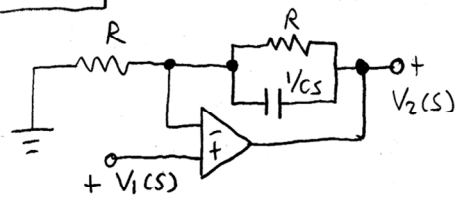11-11 Find $T_V(s) = \frac{V_2(s)}{V_1(s)}$! Select R and C s.t. $T_V(s)$ has a pole at $s = -100 \text{krad/s}$!



$$Z = R \parallel \frac{1}{Cs} = \left(\frac{1}{R} + Cs\right)^{-1} = \frac{R}{1+RCs}$$

Using nodal analysis at node A ($V_A(s) = V_1(s)$)

$$\bar{i}_1 + 0 = \bar{i}_2 \rightarrow \frac{V_A(s) - 0}{R} = \frac{V_2(s) - V_A(s)}{Z}$$

$$\frac{R}{1+RCs} V_1(s) + V_1(s) = V_2(s)$$


$$T_V(s) = \frac{V_2(s)}{V_1(s)} = 1 + \frac{1}{1+RCs} = \frac{2+RCs}{1+RCs}$$

↳ Non-inverting OP-Amp Circuit

Pole at $s = -\frac{1}{RC}$ → Want $\frac{1}{RC} = 100 \text{ krad/s} = 10^5 \text{ rad/s}$

C is usually in the μF (10^{-6}) or pF (10^{-9}) range, so $C = 10 \text{ pF}$ and $R = 1 \text{ k}\Omega$ works.

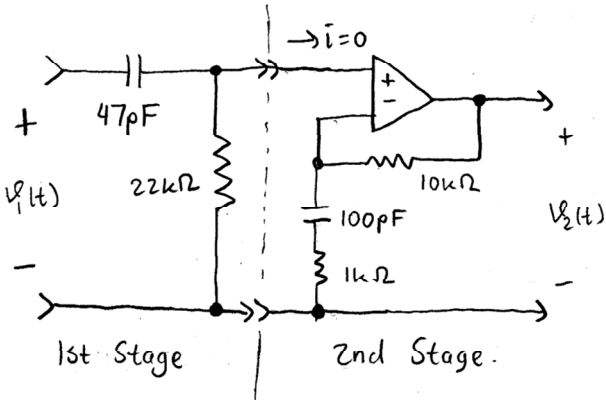
11-15 Find $T_V(s) = \frac{V_2(s)}{V_1(s)}$! Locate the poles and zeros of $T_V(s)$!



Note that this is a cascade of 2 circuits = Voltage divider and non-inverting OP-Amp.

We can use chain rule because the 2nd stage is not loading the first one because of the infinite input impedance of the OP Amp.

1st Stage

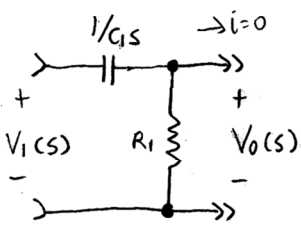


Volt. Divider

$$\frac{V_0(s)}{V_1(s)} = \frac{R_1}{R_1 + \frac{1}{C_1 s}} = \frac{s}{s + \frac{1}{R_1 C_1}} = \frac{s}{s + \frac{1}{(22 \text{ k}\Omega)(47 \text{ pF})}}$$

$$\frac{V_0(s)}{V_1(s)} = \frac{s}{s + 967.1}$$

2nd Stage

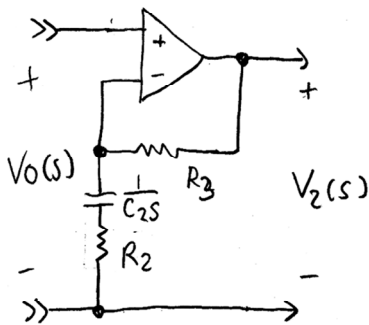

Non-inverting OP-Amp

$$\frac{V_2(s)}{V_0(s)} = 1 + \frac{R_3}{\left(\frac{1}{C_2 s} + R_2\right)} = 1 + \frac{R_3/R_2 s}{s + \frac{1}{C_2 R_2}} = 1 + \frac{\frac{10 \text{ k}\Omega}{1 \text{ k}\Omega} s}{s + \frac{1}{100 \text{ pF} \cdot 1 \text{ k}\Omega}}$$


$$\frac{V_2(s)}{V_0(s)} = 1 + \frac{10s}{s + 10000} = \frac{11s + 10000}{s + 10000}$$

$$\hookrightarrow \frac{V_2(s)}{V_1(s)} = \left(\frac{V_0(s)}{V_1(s)}\right) \left(\frac{V_2(s)}{V_0(s)}\right) = \left(\frac{s}{s + 967.1}\right) \left(\frac{11s + 10000}{s + 10000}\right)$$

$$\text{Zeros} = \left\{ 0, -\frac{10^4}{11} \right\} \text{ rad/s}, \text{ Poles} = \left\{ -967.1, -10^4 \right\} \text{ rad/s}$$

11-35

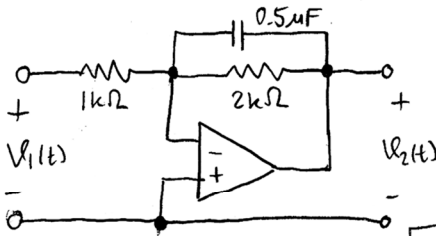Find $v_{2ss}(t)$ using $v_1(t) = 10 \cdot \cos(\omega t)$ V, $\omega = \{500, 1k, 10k\}$ rad/s!
Where is the pole?



Inverting OP - Amp Circuit

$$\frac{V_2(s)}{V_1(s)} = \frac{-\left(\frac{1}{0.5\mu F \cdot s} \parallel 2k\Omega\right)}{1k\Omega} = -\frac{\left(\frac{1}{2k\Omega} + 0.5\mu F \cdot s\right)^{-1}}{1k\Omega}$$

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{-2}{1 + 10^{-3}s} = \frac{-2000}{s + 1000}$$

$$\rightarrow \text{Pole} = -1000 \text{ rad/s}$$

For $v_1(t) = 10 \cdot \cos \omega t \rightarrow$ Sinusoidal input, we can use $T_V(j\omega)$ to find the $v_{2ss}(t)$.

$$T_V(j\omega) = \frac{-2000}{j\omega + 1000} = \frac{-2000(-j\omega + 1000)}{\omega^2 + 10^6} \rightarrow T_V(\omega j) = \frac{-2 \cdot 10^6 + 2000\omega j}{\omega^2 + 10^6}$$

$$v_{2ss}(t) = 10 \cdot |T_V(j\omega)| \cdot \cos(\omega t + \angle T_V(j\omega))$$

$$\hookrightarrow \omega = 500 \text{ rad/s}$$

$$|T_V(j\omega)| = 1.789, \quad \angle T_V(j\omega) = 2.678 \text{ rad}$$

$$v_{2ss}(t) = 17.89 \cos(500t + 2.678 \text{ rad}) \text{ V} = (-16 \cos 500t - 8 \sin 500t) \text{ V}$$

$$\hookrightarrow \omega = 1k \text{ rad/s}$$

$$|T_V(j\omega)| = 1.414, \quad \angle T_V(j\omega) = 2.356 \text{ rad}$$

$$v_{2ss}(t) = 14.14 \cos(1kt + 2.356 \text{ rad}) \text{ V} = -10(\cos 1kt + \sin 1kt) \text{ V}$$

$$\hookrightarrow \omega = 10k \text{ rad/s}$$


$$|T_V(j\omega)| = 0.1990, \quad \angle T_V(j\omega) = 1.670 \text{ rad}$$

$$v_{2ss}(t) = 1.99 \cos(10kt + 1.670 \text{ rad}) \text{ V} = (-0.198 \cos 10kt - 1.98 \sin 10kt) \text{ V}$$

11-37

$R_1 = 100\Omega, R_2 = 400\Omega, L = 100\text{mH}$

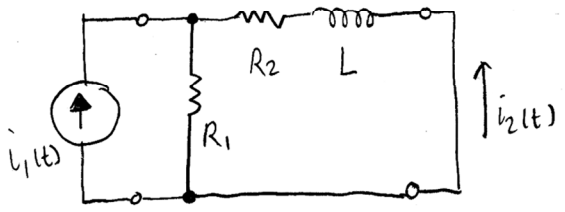Find $\hat{i}_{2ss}(t)$ for $i_1(t) = 10 \cos(\omega t) \text{ mA}$, $\omega = \{50 \text{krad/s}, 5 \text{krad/s}\}$!
Find poles!



This is a current divider circuit.

$$\frac{-I_2(s)}{I_1(s)} = \frac{(R_2 + Ls)^{-1}}{R_1^{-1} + (R_2 + Ls)^{-1}} = \frac{R_1}{R_1 + (R_2 + Ls)}$$

$$= \frac{100\Omega}{100\Omega + 400\Omega + 100\text{mH} \cdot s} = \frac{100}{0.1s + 500}$$

$$T_I(s) = \frac{I_2(s)}{I_1(s)} = \frac{-1000}{s + 5000}$$

→ Pole = -5000 rad/s

$$i_1(t) = 10 \cdot \cos(\omega t) \text{ mA} \rightarrow \hat{i}_{2ss}(t) = 10 \cdot |T_I(j\omega)| \cos(\omega t + \angle T_I(j\omega)) \text{ mA}$$

$\omega = 50 \text{krad/s} \rightarrow |T_I(j\omega)| = 0.0199, \angle T_I(j\omega) = 1.670 \text{ rad}$


$$\hat{i}_{2ss}(t) = 0.199 \cos(50kt + 1.670) \text{ mA} = (-0.0198 \cos 50kt - 0.198 \sin 50kt) \text{ mA}$$

$\omega = 5 \text{krad/s} \rightarrow |T_I(j\omega)| = 0.1414, \angle T_I(j\omega) = 2.356 \text{ rad}$

$$\hat{i}_{2ss}(t) = 1.414 \cos(5kt + 2.356) \text{ mA} = -0.1 (\cos 5kt + \sin 5kt) \text{ mA}$$

11-80

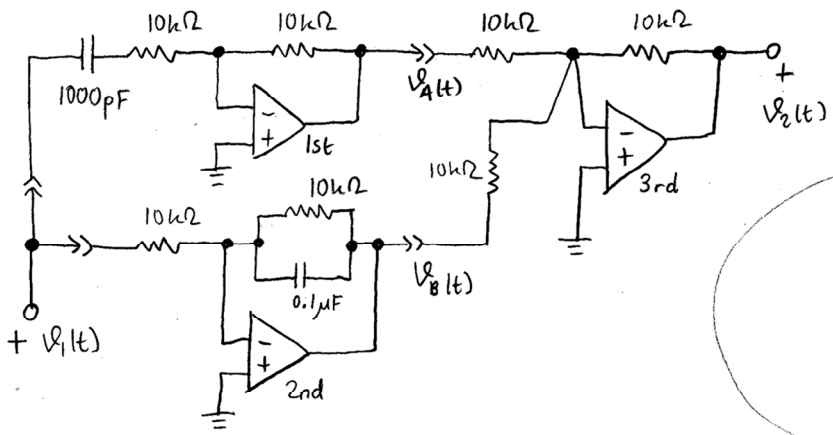Interconnection of 3 basic OP Amp modules (all are inverting OP Amp).



All $R = 10\text{k}\Omega$,
 $C_1 = 1000 \text{ pF}$
 $C_2 = 0.1 \mu\text{F}$

5/12

a) Does this interconnection involve loading?

(No) → OP Amp circuits do not involve loading.

b) Find the overall TF and locate its poles and zeros!

1st OP Amp → Inverting OP Amp

$$T_1(s) = \frac{V_A(s)}{V_1(s)} = \frac{-R}{R + \frac{1}{C_1 s}} = \frac{-s}{s + \frac{1}{RC_1}} = \frac{-s}{s + \frac{1}{10k\Omega \cdot 1000pF}} \rightarrow T_1(s) = \frac{-s}{s+100}$$

2nd OP Amp → Inverting OP Amp

$$T_2(s) = \frac{V_B(s)}{V_1(s)} = \frac{-(R \parallel \frac{1}{C_2 s})}{R} = \frac{-(\frac{1}{R} + C_2 s)^{-1}}{R} = \frac{-1}{1 + RC_2 s} = \frac{-1}{1 + 10k\Omega \cdot 0.1\mu F \cdot s} = \frac{-1}{1 + 10^{-3}s}$$

3rd OP Amp → Inverting OP Amp summing junction.

$$\rightarrow T_2(s) = \frac{-1000}{s+1000}$$

$$V_2(s) = -\frac{R}{R} V_A(s) - \frac{R}{R} V_B(s) = -(V_A(s) + V_B(s)) = -(T_1(s) V_1(s) + T_2(s) V_1(s))$$

$$= -\left(\frac{-s}{s+100} - \frac{1000}{s+1000}\right) V_1(s) = \frac{s(s+1000) + 1000(s+100)}{(s+100)(s+1000)} V_1(s)$$

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{s^2 + 2000s + 10^5}{(s+100)(s+1000)} = \frac{(s+1948.7)(s+51.3167)}{(s+100)(s+1000)}$$

$$\rightarrow \text{Zeros} = \{-1948.7, -51.3167\} \text{ rad/s}, \quad \text{Poles} = \{-100, -1000\} \text{ rad/s}$$

c) Find $v_{2ss}(t)$ when $v_1(t) = \cos \omega t$ V, $\omega = \{500, 10k, 200k\}$ rad/s!

Same method as 11-35 and 11-37

$$\rightarrow v_{2ss}(t) = |T_V(j\omega)| \cdot \cos(\omega t + \angle T_V(j\omega)) \text{ V}$$

$$\omega = 500 \text{ rad/s} \rightarrow |T_V(j\omega)| = 1.774, \quad \angle T_V(j\omega) = -0.1174 \text{ rad}$$

$$v_{2ss}(t) = 1.774 \cos(500t - 0.1174) \text{ V} = (1.7615 \cos 500t + 0.2077 \sin 500t) \text{ V}$$

$$\omega = 10 \text{ rad/s} \rightarrow |T_V(j\omega)| = 1.014, \quad \angle T_V(j\omega) = -0.0879 \text{ rad}$$

$$V_{2SS}(t) = 1.014 \cos(10kt - 0.0879) \text{ V} = (1.010 \cos 10kt + 0.0890 \sin 10kt) \text{ V}$$

$$\omega = 200 \text{ rad/s} \rightarrow |T_V(j\omega)| = 1, \quad \angle T_V(j\omega) = -0.0045 \text{ rad}$$


$$V_{2SS}(t) = \cos(200kt - 0.0045) \text{ V} = (\cos 200kt + 0.0045 \sin 200kt) \text{ V}$$

d) Can you think of a use for this circuit?

We have the input signal passed to 2 different OP Amps and then the output from each of these OP Amps are summed by the 3rd OP Amp. The 1st OP Amp is a differentiator which attenuates at high frequency while the 2nd OP Amp is a low pass filter.

↳ Differentiator + Low pass → Proportional Differentiator (PD) Circuit which rejects high frequency noise

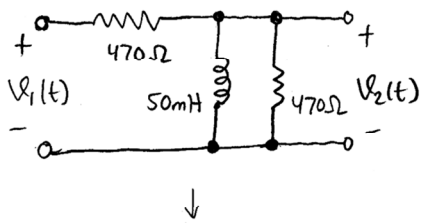
12-5 Find $T_V(s) = \frac{V_2(s)}{V_1(s)}$ $R = 470 \Omega, L = 50 \text{ mH}$



This is a voltage divider.

$$Z = (L \parallel R) = \left(\frac{1}{Ls} + \frac{1}{R} \right)^{-1} = \frac{RLs}{R+Ls}$$
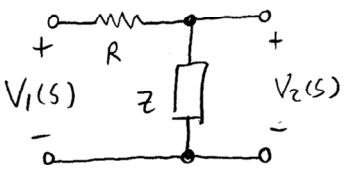
$$T_V(s) = \frac{Z}{Z+R} = \frac{\frac{RLs}{R+Ls}}{\frac{RLs}{R+Ls} + R} = \frac{RLs}{RLs + R^2 + RLs} = \frac{s}{2\left(s + \frac{R}{2L}\right)}$$



$$T_V(s) = \frac{s}{2\left(s + \frac{470 \Omega}{2 \cdot 0.05 \text{ H}}\right)} = \frac{s}{2(s + 4700)}$$

a) Find DC Gain, ∞ freq. gain, cutoff freq.! Identify the type of gain response!

DC Gain → $G_{DC} = \lim_{s \rightarrow 0} T_V(s) = \frac{0}{2(0+4700)} \rightarrow G_{DC} = 0$

∞ Gain → $G_{\infty} = \lim_{s \rightarrow \infty} T_V(s) = \lim_{s \rightarrow \infty} \frac{1}{2\left(1 + \frac{4700}{s}\right)} \rightarrow G_{\infty} = \frac{1}{2}$

Cutoff frequency ω_c where $|T_V(j\omega_c)| = \frac{1}{\sqrt{2}} T_{Vmax}$, $T_{Vmax} = 1/2$ in this case

$$T_V(j\omega) = \frac{j\omega}{2(j\omega + 4700)} = \frac{j\omega(-j\omega + 4700)}{2(\omega^2 + 4700^2)} = \frac{\omega^2 + 4700j\omega}{2(\omega^2 + 4700^2)}$$

$$\hookrightarrow |T_V(j\omega)| = \frac{\sqrt{\omega^4 + \omega^2 \cdot 4700^2}}{2(\omega^2 + 4700^2)} = \frac{1}{2} \frac{\omega}{\sqrt{\omega^2 + 4700^2}}$$


$$\hookrightarrow |T_V(j\omega_c)| = \frac{1}{\sqrt{2}} \cdot \frac{1}{2} = \frac{1}{2} \frac{\omega_c}{\sqrt{\omega_c^2 + 4700^2}} \rightarrow \frac{1}{8} = \frac{\omega_c^2}{4} \cdot \frac{1}{(\omega_c^2 + 4700^2)}$$

$$\hookrightarrow \omega_c^2 + 4700^2 = 2\omega_c^2 \rightarrow \omega_c^2 = 4700^2 \rightarrow \boxed{\omega_c = 4700 \text{ rad/s}}$$

Same as the magnitude of the pole!

$$T_V(s) = \frac{s}{s + 4700} \rightarrow \boxed{\text{High pass filter}}$$

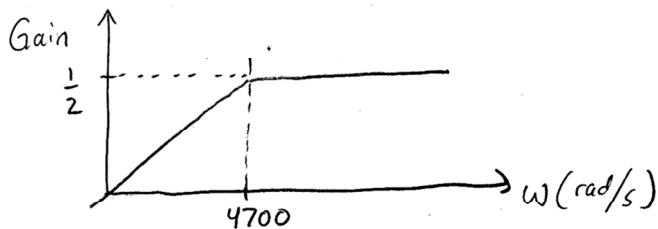b) Sketch the straight line approximate of the gain response!



c) Calculate gain at $\omega = \{0.5\omega_c, \omega_c, 2\omega_c\}$!

Using gain = $|T_V(j\omega)|$ and $\omega_c = 4700 \text{ rad/s} \rightarrow$

$$|T_V(0.5\omega_c)| = 0.2236$$

$$|T_V(\omega_c)| = 0.3536 = \frac{1}{\sqrt{2} \cdot 2}$$

$$|T_V(2\omega_c)| = 0.4472$$

d) Plot the bode plot! \rightarrow (Matlab Plot at the end)

e) How many dB down the passband is the filter one octave below the ω_c ?

One octave lower $\rightarrow \omega = 0.5\omega_c$.

$$\text{Gain at } \omega_c \rightarrow G_{\omega_c} = 20 \cdot \log_{10}\left(\frac{1}{\sqrt{2} \cdot 2}\right) = \underline{\underline{-9.03 \text{ dB}}}$$


$$\text{Gain at } \omega = 0.5\omega_c \rightarrow G_{\omega} = 20 \cdot \log_{10}(0.2236) = \underline{\underline{-13.01 \text{ dB}}}$$

$$\hookrightarrow \boxed{3.98 \text{ dB lower}}$$

12-9

We need a low-pass filter with $\omega_c = 1 \text{ krad/s}$ and gain of -5 .

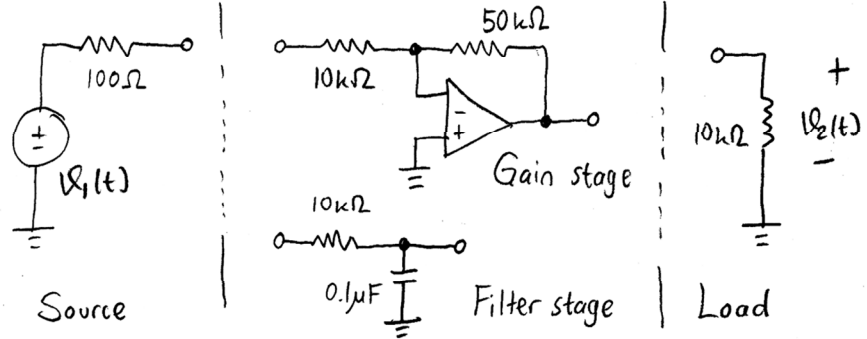
The filter must fit in between the source and load circuit. The following circuits can never get the desired result no matter how you connect them. Explain why and suggest a way to get the desired result!



We have 2 configurations =
 a) Gain then filter
 b) Filter then gain

Individually, the gain and filter circuits seem to do what they are supposed to do:


Gain stage \rightarrow Inverting OP Amp.

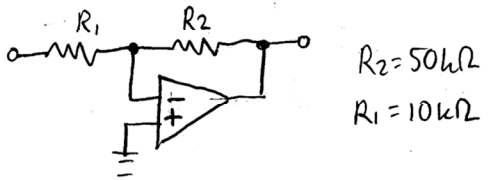

$R_2 = 50 \text{ k}\Omega$
 $R_1 = 10 \text{ k}\Omega$

$$T_G(s) = -\frac{R_2}{R_1} = -\frac{50 \text{ k}\Omega}{10 \text{ k}\Omega} = \underline{\underline{-5}}$$

Filter Stage \rightarrow Voltage divider

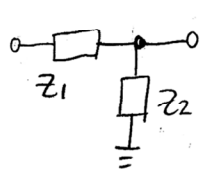

$Z_1 = 10 \text{ k}\Omega$

$Z_2 = (0.1 \mu\text{F} \cdot s)^{-1}$


$$T_F(s) = \frac{Z_2}{Z_1 + Z_2} = \frac{\frac{1}{0.1 \mu\text{F} \cdot s}}{10 \text{ k}\Omega + \frac{1}{0.1 \mu\text{F} \cdot s}}$$

$$= \frac{1000}{s + 1000} \rightarrow \text{DC Gain} = \underline{\underline{1}}$$

$\hookrightarrow \omega_c = 1000 \text{ rad/s}$

However, when plugged into the circuit, the source internal resistance and the load resistance will affect the transfer functions in a bad way.

Configuration a)

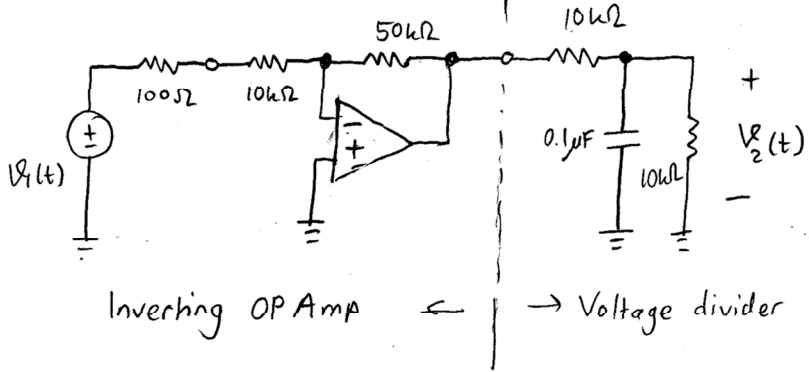

This configuration will have

$$R_1 = 100 \Omega + 10 \text{ k}\Omega$$

$$R_2 = 50 \text{ k}\Omega$$

$$Z_1 = 10 \text{ k}\Omega$$

$$Z_2 = (10 \text{ k}\Omega \parallel \frac{1}{0.1 \mu\text{F} \cdot s})$$

9/12

$$T_{G_a}(s) = -\frac{R_2}{R_1} = \frac{-50k\Omega}{10.1k\Omega} = \underline{\underline{-4.95}}$$

$$T_{F_a}(s) = \frac{z_2}{z_1 + z_2} = \frac{\left(\frac{1}{10k\Omega} + 0.1\mu F \cdot s\right)^{-1}}{10k\Omega + \left(0.1\mu F \cdot s + \frac{1}{10k\Omega}\right)^{-1}} = \frac{\frac{1}{1+10^{-3}s}}{1 + \frac{1}{1+10^{-3}s}} = \frac{1}{2+10^{-3}s} = \underline{\underline{\frac{1000}{s+2000}}}$$


We can do the chain rule because the OP Amp circuit is not loading to the volt. divider.

$$\hookrightarrow T_{V_a}(s) = T_{G_a}(s) \cdot T_{F_a}(s) = -4.95 \cdot \frac{1000}{(s+2000)}$$

$$\begin{aligned} \omega_c &= 2000 \text{ rad/s} \\ \text{DC gain} &= -4.95 \cdot \frac{1000}{2000} \\ &= -2.475 \end{aligned}$$

Wrong gain and wrong ω_c !

Configuration b)

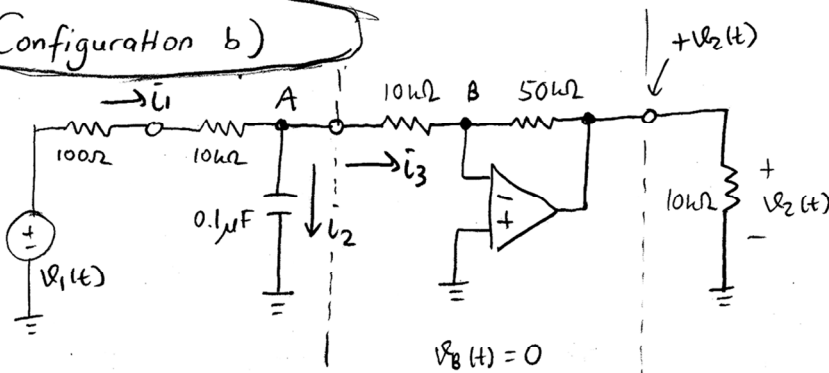

- Note that we lose the voltage divider because $i_3 \neq 0$.
- Need to do a nodal analysis at node A to find V_A , then use V_A as the input to the OP Amp.
- Note that $V_2(t)$ = the OP Amp's output.

Find V_A !

$$\text{Node A} \rightarrow \bar{i}_1 = i_2 + i_3$$

$$\frac{V_1(s) - V_A(s)}{10k\Omega + 100\Omega} = \frac{V_A(s) - 0}{(0.1\mu F \cdot s)^{-1}} + \frac{V_A(s) - 0}{10k\Omega} = \left(\frac{1}{10k\Omega} + 0.1\mu F \cdot s\right) V_A(s)$$

$$\frac{V_1(s)}{10.1k\Omega} = \left(\frac{1}{10k\Omega} + \frac{1}{10.1k\Omega} + 0.1\mu F \cdot s\right) V_A(s) \rightarrow \frac{V_A(s)}{V_1(s)} = \frac{1/10.1k\Omega}{\left(\frac{1}{10k\Omega} + \frac{1}{10.1k\Omega} + 0.1\mu F \cdot s\right)}$$

$$T_{F_b}(s) = \frac{V_A(s)}{V_1(s)} = \frac{1}{\left(\frac{10.1}{10} + 1 + 0.00101s\right)} = \frac{1}{(2.01 + 0.00101s)}$$


$$T_{G_b}(s) = \frac{V_2(s)}{V_A(s)} = \frac{-50k\Omega}{10k\Omega} = \underline{\underline{-5}}$$

So, we have:

$$T_{V_b}(s) = \frac{V_2(s)}{V_1(s)} = \frac{V_A(s)}{V_1(s)} \cdot \frac{V_2(s)}{V_A(s)} = \left(\frac{1}{2.01 + 0.00101s} \right) (-5) \rightarrow \begin{cases} \omega_c = 1990 \text{ rad/s} \\ \text{DC Gain} = -2.488 \end{cases}$$


So, the loading and source resistances significantly altered the gain and ω_c . We need to take these resistances into account when designing the circuits.

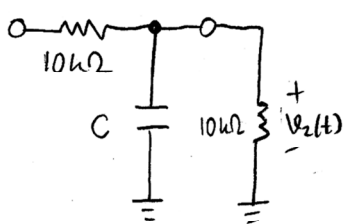I think configuration a) is easier to fix.



$$T_{F_a}(s) = \frac{(\frac{1}{Cs} \parallel 10k\Omega)}{10k\Omega + (\frac{1}{Cs} \parallel 10k\Omega)} = \frac{(\frac{1}{10k\Omega} + Cs)^{-1}}{10k\Omega + (\frac{1}{10k\Omega} + Cs)^{-1}} = \frac{\frac{10k\Omega}{1 + 10k\Omega \cdot Cs}}{10k\Omega + \frac{10k\Omega}{1 + 10k\Omega \cdot Cs}}$$
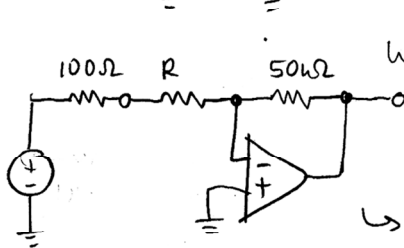
$$= \frac{1}{1 + 10k\Omega \cdot Cs + 1} = \frac{1}{2 + 10k\Omega \cdot Cs}$$



Want: $\omega_c = \frac{2}{10k\Omega \cdot C} = 1000 \text{ rad/s} \rightarrow C = 0.2 \mu\text{F}$

$T_{G_a}(s) = -\frac{50k\Omega}{R + 100\Omega} \rightarrow$ Find R where the gain is -5

$$T_{V_a}(s) = T_{G_a}(s) \cdot T_{F_a}(s) = \left(-\frac{50k\Omega}{R + 100\Omega} \right) \left(\frac{1}{2 + 2 \cdot 10^{-3} s} \right)$$

\rightarrow DC Gain = $\lim_{s \rightarrow 0} T_{V_a}(s) = -\frac{1}{2} \cdot \frac{50k\Omega}{R + 100\Omega} = -5 \rightarrow 25k\Omega = 5R + 500\Omega$

$$R = 4900\Omega$$

Then, we have:

$$T_{V_a}(s) = (-10) \frac{500}{(s + 1000)} = \frac{-5000}{s + 1000}$$


\rightarrow DC Gain = -5
 $\omega_c = 1000 \text{ rad/s}$

✓ Correct now

12-47

$$T(s) = \frac{10^6 s^2}{(s+1000)^2}$$

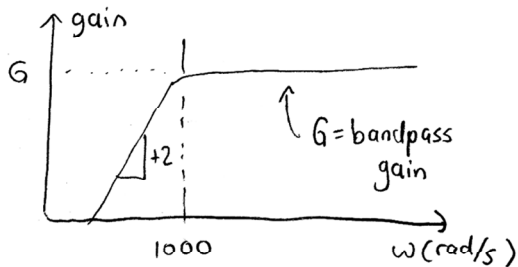a) Construct bode plot for the gain! Is this a low/high/band-pass/band-stop filter?
Estimate cutoff freq. and bandpass gain!



→ High Pass Filter

$$G = \lim_{s \rightarrow \infty} T(s) = \lim_{s \rightarrow \infty} \left(\frac{10^6}{1 + \frac{2000}{s} + \frac{10^6}{s^2}} \right) \rightarrow G = 10^6$$

$G = 10^6$

Cutoff freq: ω_c where $|T(j\omega_c)| = \frac{1}{\sqrt{2}} \cdot G$

$$|T(j\omega_c)| = \left| \frac{10^6 (-\omega_c^2)}{-\omega_c^2 + j2000\omega_c + 10^6} \right| = \left| \frac{-10^6 \omega_c^2 (10^6 - \omega_c^2 + j2000\omega_c)}{(10^6 - \omega_c^2)^2 + (2000\omega_c)^2} \right|$$

$$= \frac{10^6 \omega_c^2}{((10^6 - \omega_c^2)^2 + (2000\omega_c)^2)^{1/2}} = \frac{10^6}{\sqrt{2}}$$

$$\rightarrow \sqrt{2} \omega_c^2 = \sqrt{(10^6 - \omega_c^2)^2 + (2000\omega_c)^2} \rightarrow 2\omega_c^4 = \omega_c^4 - 2 \cdot 10^6 \omega_c^2 + 2000^2 \omega_c^2 + 10^{12}$$


$$\rightarrow \omega_c^4 - 2 \cdot 10^6 \omega_c^2 - 10^{12} = 0 \rightarrow \omega_c^2 = \{2.414 \cdot 10^6, -0.414 \cdot 10^6\}$$

Frequency is a positive real number $\rightarrow \omega_c^2 = 2.414 \cdot 10^6 \rightarrow \omega_c = 1554 \text{ rad/s}$

b) Use Matlab to plot the bodeplot! → (at the end)

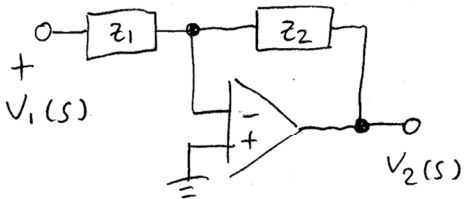c) Design a circuit with practical components with the same transfer function!

We have $T(s) = \left(\frac{10^3 s}{s+1000} \right)^2$, so try cascading 2 OP Amps with $TF = \frac{10^3 s}{s+1000}$



$$T_1(s) = \frac{V_2(s)}{V_1(s)} = \frac{-Z_2}{Z_1} = \frac{10^3 s}{s+1000}$$


$$= \frac{10^3}{1 + \frac{1000}{s}} \rightarrow R \text{ circuit} \rightarrow R, C \text{ in series}$$

$$\left. \begin{aligned} Z_1 &= R_1 + \frac{1}{Cs} \\ Z_2 &= R_2 \end{aligned} \right\} T_1(s) = \frac{-R_2}{R_1 + \frac{1}{Cs}} = \frac{-R_2/R_1}{1 + (\frac{1}{R_1 C}) \frac{1}{s}} \rightarrow \begin{cases} \frac{R_2}{R_1} = 10^3 \\ \frac{1}{R_1 C} = 10^3 \end{cases}$$

We can use

$$C = 1\mu\text{F}, R_1 = 1\text{k}\Omega, R_2 = 1\text{M}\Omega$$

→

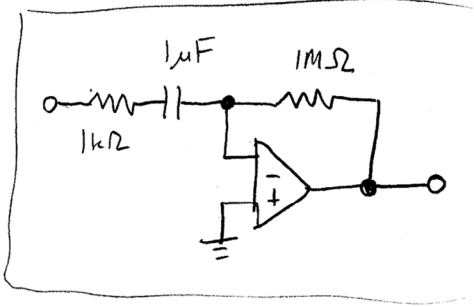

Cascade 2 of this circuit to form $T(s) = T_1(s)^2$


d) Use orCAD to compare this with the Mathob's plot! → (not needed)

12-51

$$T_V(s) = \frac{4s}{0.04s^2 + 0.2s + 1} = \frac{100s}{s^2 + 5s + 25}$$

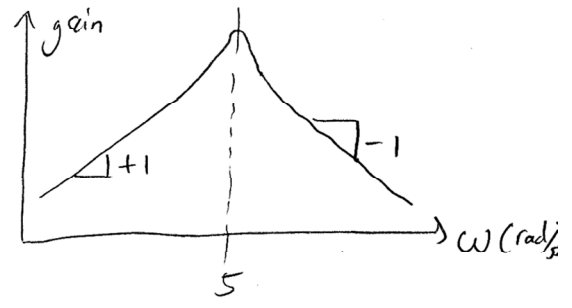a) Construct the body-plot of the gain! Is this low/high/band-pass/band-stop?

$$T_V(s) = \frac{100s}{s^2 + 5s + 25} \rightarrow \text{Complex poles, } \omega_c = \sqrt{25} = 5 \text{ rad/s}$$



Band-pass filter

b) Estimate the max gain!


Max gain is at the resonant frequency $\omega_c = 5 \text{ rad/s}$

$$\hookrightarrow |T_V(j\omega_c)| = |T_V(5j)| = \left| \frac{4(5j)}{(5j)^2 + 0.2(5j) + 1} \right| = \left| \frac{20j}{-1 + j + 1} \right|$$


$$|T_V(j\omega_c)| = 20$$

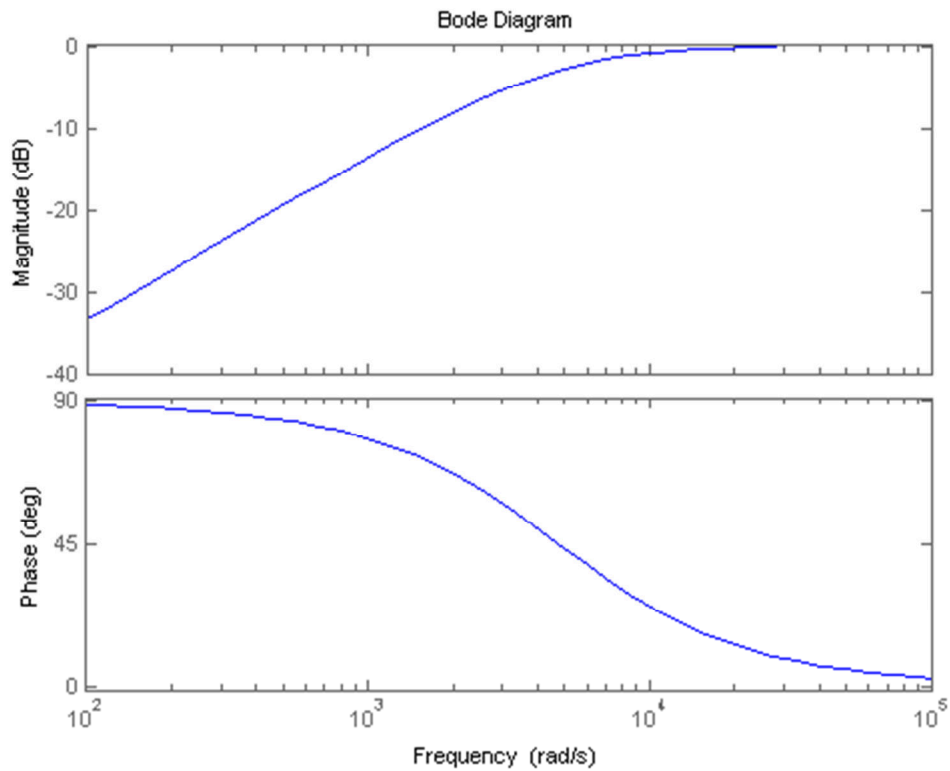c) Use Matlab to draw the bode plot! → (at the end)

Matlab's bode plot for Problem 12-5, for $T(s) = s/(s+4700)$



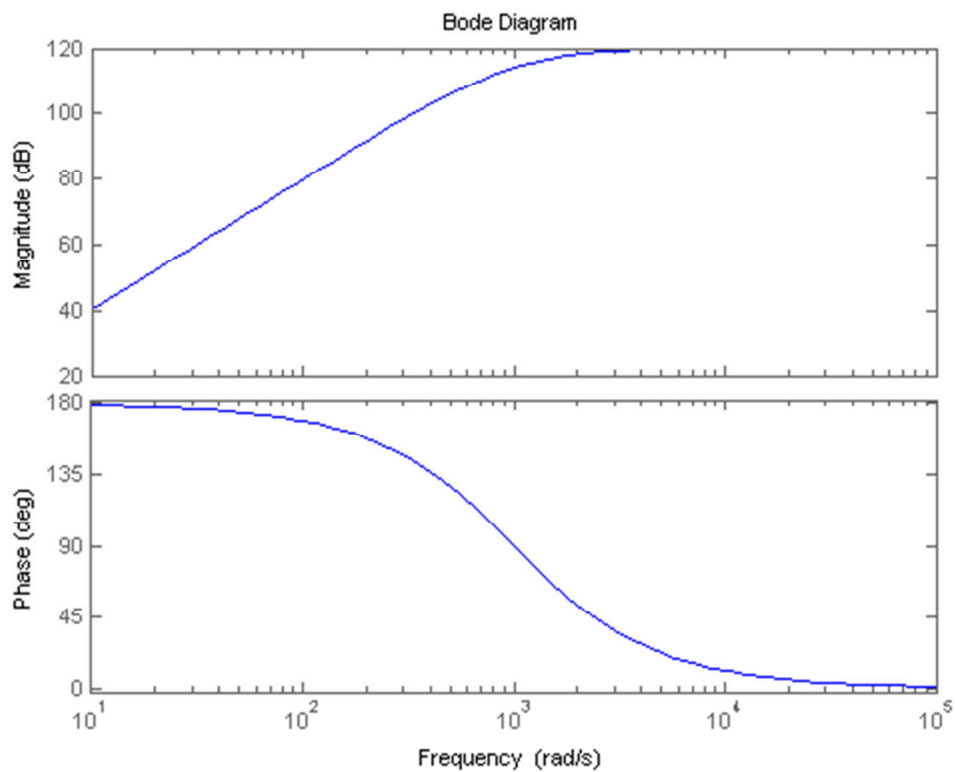Matlab's bode plot for Problem 12-47, for $T(s) = 10^6 s^2/(s+1000)^2$



Matlab's bode plot for Problem 12-51, for $T(s) = 4 s / (0.04 s^2 + 0.2 s + 1)$

