

## 1. Part I.

For node-voltage equations, we know the presence of the voltage source is a problem. However, based on the location of ground, we can use Method 2 to state

$$V_A = V_S \quad [+1.5 \text{ point}]$$

Therefore, we just need to write KCL equations for nodes  $\textcircled{B}$  and  $\textcircled{C}$ .

$$\text{KCL at } \textcircled{B} : G_3(V_B - V_C) + G_4 V_B + aV_x = 0 \quad [+1 \text{ point}]$$

$$\text{KCL at } \textcircled{C} : G_2 V_C + G_3 (V_C - V_B) = aV_x \quad [+1 \text{ point}]$$

(Here, we have used the notation  $G_i = \frac{1}{R_i}$  for convenience).

The presence of the dependent source means that we need one more equation. Looking at the circuit, we see that

$$V_x = V_A - V_B \quad [+1.5 \text{ point}]$$

Therefore, we have 4 equations in 4 unknowns,  $V_A, V_B, V_C, V_x$ . Alternatively, we can also express this as

$$G_3(V_B - V_C) + G_4 V_B + aV_X = 0$$

$$G_2 V_C + G_3(V_C - V_B) - aV_X = 0$$

$$V_X = V_S - V_B$$

that is, 3 equations in 3 unknowns,

$$V_B, V_C, V_X.$$

[+1 point]

## Part II.

By looking at the circuit, we have

$$i_X = G_3(V_B - V_C) \quad [+0.5 \text{ point}]$$

$$i_1 = G_1 V_A \quad [+0.5 \text{ point}]$$

$$i_2 = -aV_X = -a(V_A - V_B) \quad [+0.5 \text{ point}]$$

$$i_3 = G_4 V_B \quad [+0.5 \text{ point}]$$

## 3. - Part I.


We are asked to use two inverting op-amps  
and one inverting summer to realize

$$V_o = 2V_{in} - 27$$


with the devices in our toolbox. One possibility is to decompose this operation as

$$\begin{aligned}
 V_o &= -(27 - 2V_{in}) = \\
 &= -(-27 - 2V_{in}) \quad \text{inverting op-amp} \\
 &= -(-3 \cdot 9 - 2V_{in}) \quad \text{op-amp} \\
 &\quad \text{inverting opamp} \quad \text{inverting summer}
 \end{aligned}$$

This corresponds to the following design

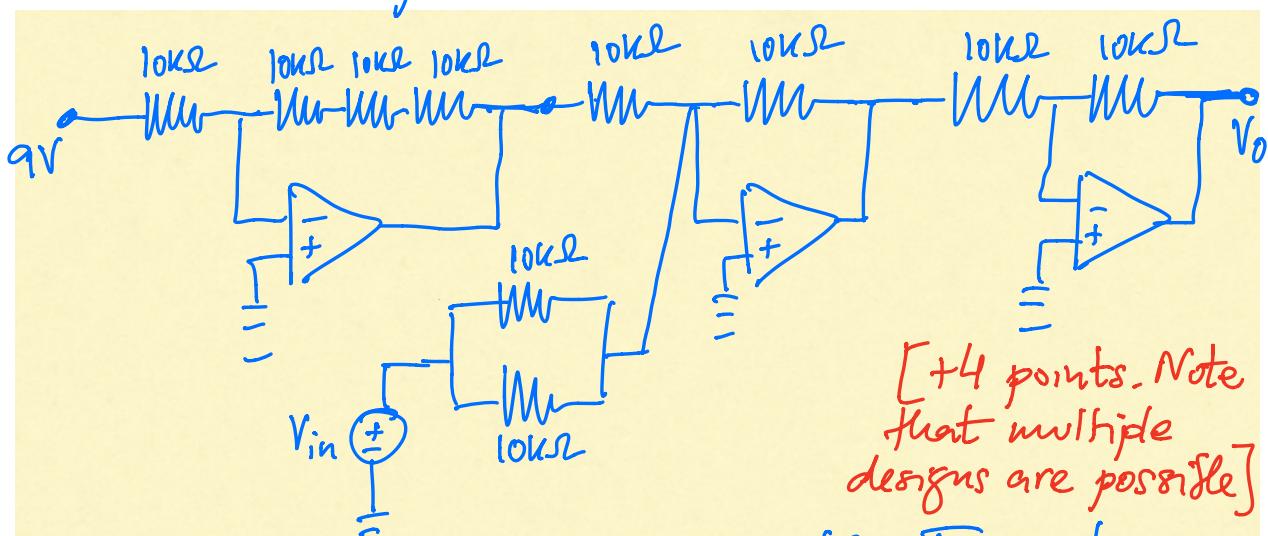

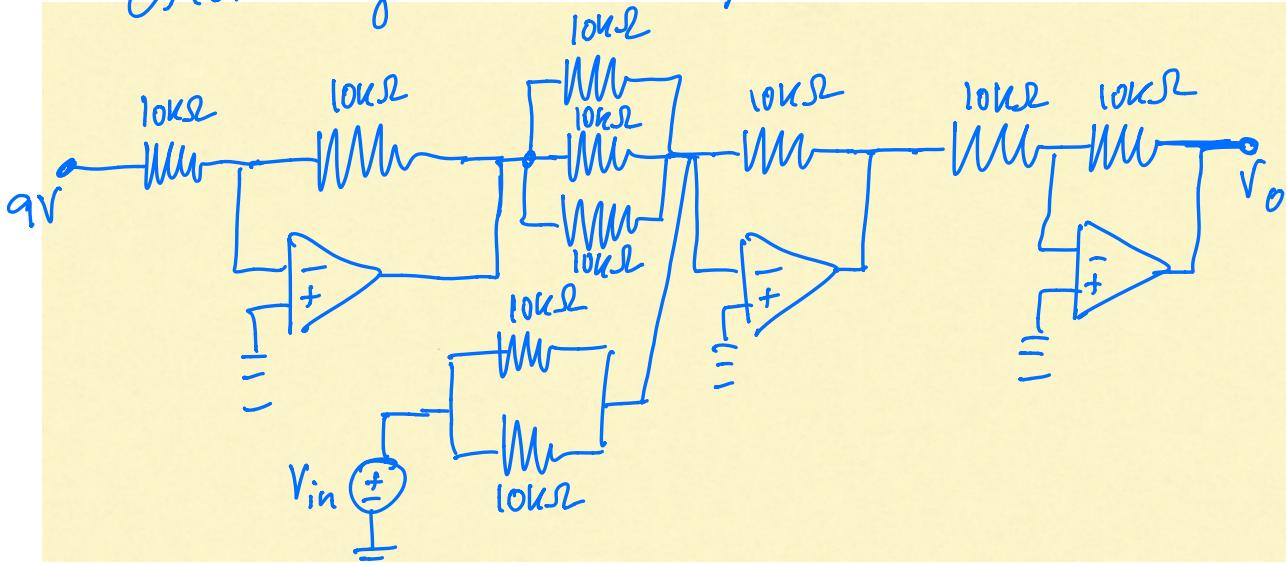Other designs are also possible. For instance,




which realizes the operation

$$V_o = -(-3 \cdot (-9) - 2V_{in}).$$

Part II.

Here we are asked to use only one op-amp.  
Given the operation we have to realize,  
the candidate to try is the differential  
amplifier.

[+1 point]

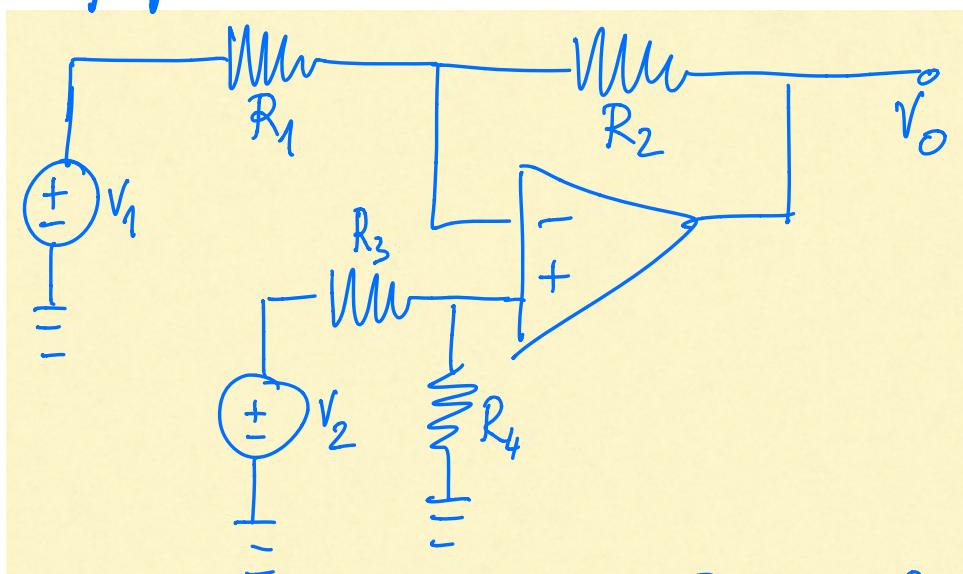

We know that  $V_o = -\frac{R_2}{R_1} V_1 + \frac{R_4}{R_3+R_4} \cdot \frac{R_1+R_2}{R_1} V_2$

If we set  $V_1 = 9V$  and  $V_2 = V_m$ , we need

$$\frac{R_2}{R_1} = 3 \quad \frac{R_4}{R_3+R_4} \cdot \frac{R_1+R_2}{R_1} = 2$$

Using the first equation in the second, this can also be expressed as

$$\frac{R_2}{R_1} = 3 \quad \frac{R_4}{R_3+R_4} = \frac{1}{2} \quad [+1\text{ point}]$$

So for instance, we can make this happen with


$$R_1 = 10k\Omega$$

$$R_2 = 10 + 10 + 10 = 30k\Omega$$


$$R_4 = R_3 = 10k\Omega$$

[+1 point]

So our design is as follows.

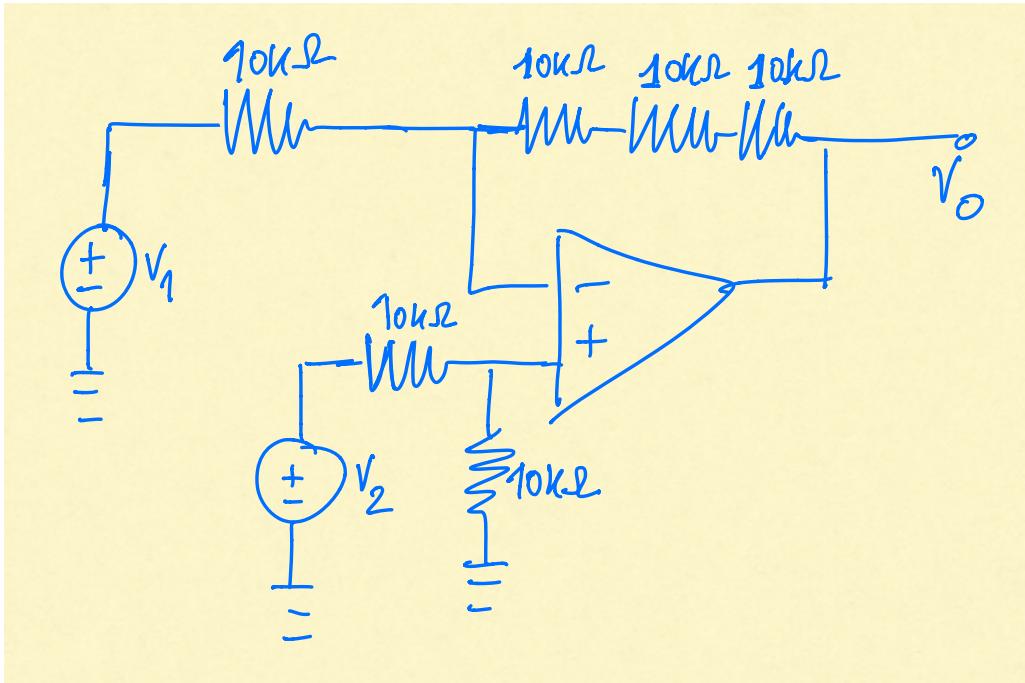

[+1 point]

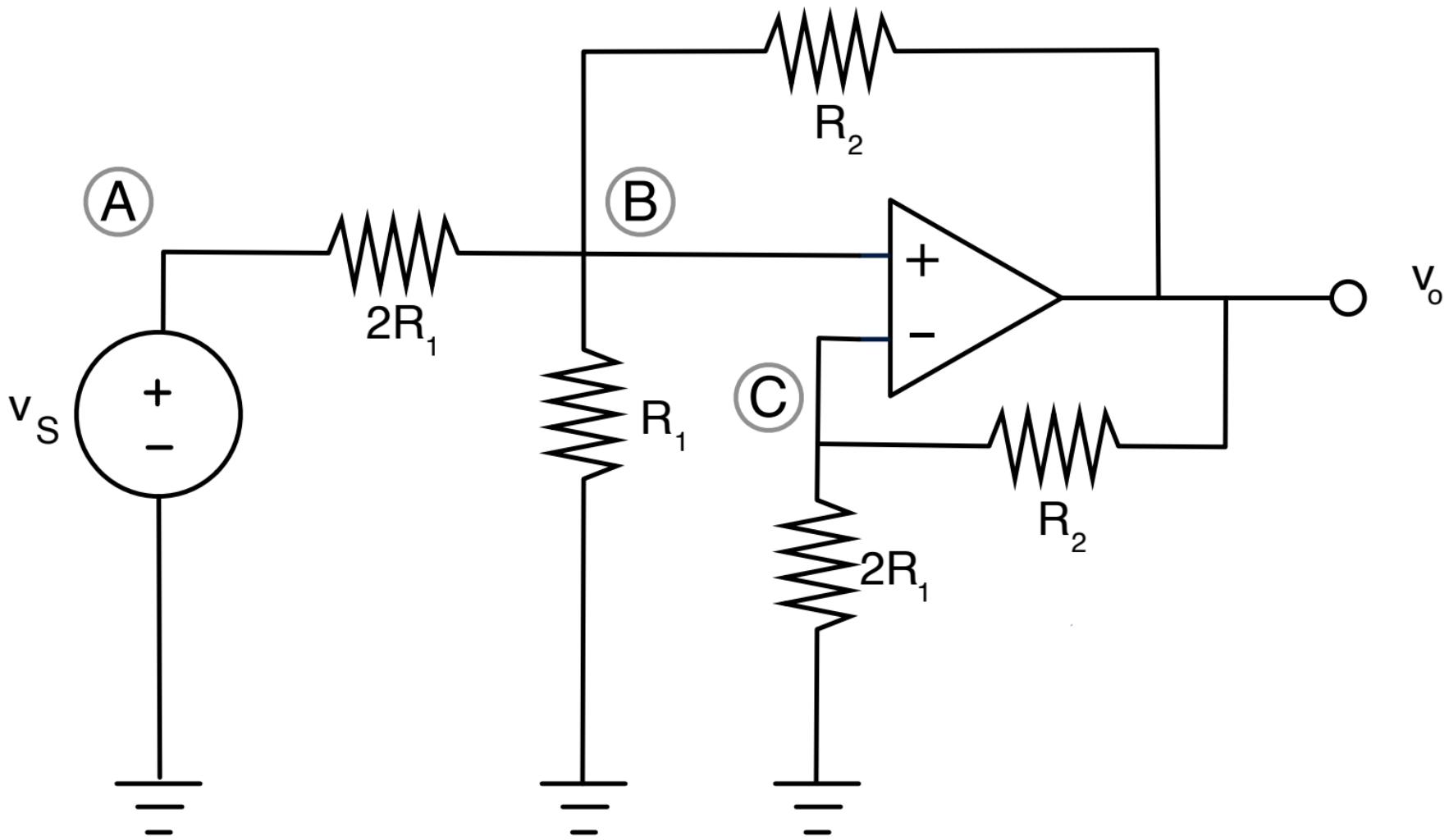

## 2.- Part I.

Labels are already in place for the nodes, so we use them to set up node-voltage eqs.

$$V_A = V_S$$

[+1 point]

$$\text{KCL at } \textcircled{B} \quad \frac{1}{2R_1}(V_B - V_A) + \frac{1}{R_1}V_B + \frac{1}{R_2}(V_B - V_O) = 0 \quad [\text{+1.5 point}]$$

$$\text{KCL at } \textcircled{C} \quad \frac{1}{2R_1}V_C + \frac{1}{R_2}(V_C - V_O) = 0 \quad [\text{+1.5 point}]$$

where we have used  $i_p = i_N = 0$  for the input currents to the op-amp. From ideal conditions, we also know

$$V_B = V_C$$

[+1 point]

Next, we solve for  $V_O$  to determine which engineer was correct. Substituting,

$$\left( \frac{1}{2R_1} + \frac{1}{R_1} + \frac{1}{R_2} \right) V_B = \frac{1}{2R_1}V_S + \frac{1}{R_2}V_O$$

$$\left( \frac{1}{2R_1} + \frac{1}{R_2} \right) V_B = \frac{1}{R_2}V_O$$

Therefore

$$\frac{1}{R_1} V_B = \frac{1}{2R_1} V_S$$

Hence  $V_B = \frac{V_S}{2}$

Finally

$$V_o = R_2 \cdot \frac{R_2 + 2R_1}{2R_1 R_2} \cdot \frac{V_S}{2} = \\ = \frac{R_2 + 2R_1}{4R_1} V_S \quad [+1 \text{ point}]$$

So the second engineer was correct.

## Part II.

With the known resistor values, we have

$$V_o = \frac{20+10}{40} V_S = \frac{3}{4} V_S$$

The op-amp does not saturate if

$$-V_{CC} \leq V_o \leq V_{CC} \quad [+1 \text{ point}]$$

Therefore

$$-6 \leq \frac{3}{4} v_S \leq 6$$

Hence

$$-8 \leq v_S \leq 8.$$

[+1 point]