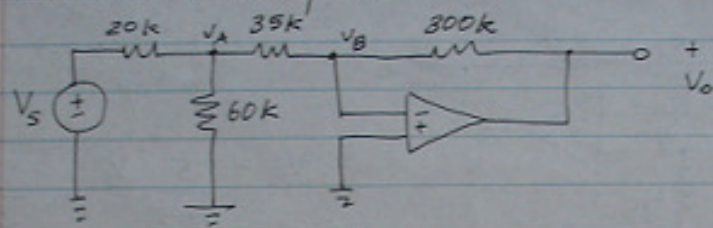


4.21, 4.24, 4.28, 4.29, 4.32, 4.33, 4.35, 4.38, 4.48, 4.54
 4.21) Find V_o in terms of V_s



$$V_p = V_n = 0 \\ i_p = i_n = 0$$

$$V_B = V_n = 0$$

KCL @ Node A:

$$\frac{V_A - V_s}{20k} + \frac{V_A - V_B}{35k} + \frac{V_A}{60k} = 0$$

$$\frac{V_A - V_s}{20k} + \frac{V_A}{35k} + \frac{V_A}{60k} = 0$$

$$V_A \left(\frac{1}{20k} + \frac{1}{35k} + \frac{1}{60k} \right) - \frac{V_s}{20k} = 0$$

$$V_A \left(\frac{21 + 12 + 7}{420k} \right) - \frac{V_s (21)}{420k} = 0$$

$$40 V_A - 21 V_s = 0 \quad \text{--- (1)}$$

KCL @ Node B:

$$\frac{V_B - V_A}{35k} + \frac{V_B - V_o}{300k} = 0$$

$$\frac{-V_A}{35k} - \frac{V_o}{300k} = 0 \implies V_A = -\frac{V_o (35)}{300} \quad \text{--- (2)}$$

Plugging (2) in (1)


$$40 \left(-\frac{35 V_o}{300} \right) - 21 V_s = 0$$

$$-\frac{14}{3} V_o = 21 V_s \implies$$

$$\boxed{V_o = -\frac{9}{2} V_s}$$

4.24) Find V_o in terms of V_s

b) Find i_o for $V_s = 2V$

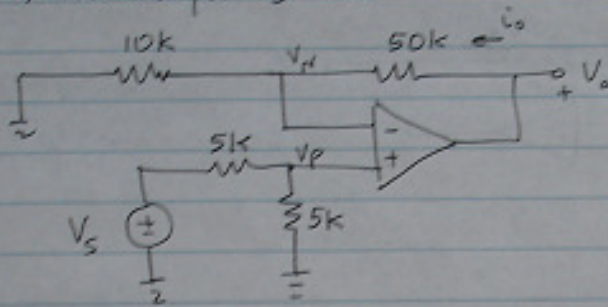

$$V_p = V_N$$
$$i_N = i_p = 0$$

$$V_p = \frac{5}{5+5} V_s = \frac{V_s}{2}$$

$$V_N = V_p = \frac{V_s}{2}$$

KCL @ V_N

$$\frac{V_N}{10k} + \frac{V_N - V_o}{50k} = 0$$

$$\frac{V_s}{20k} + \frac{V_s/2 - V_o}{50k} = 0$$

$$\frac{V_s}{20k} + \frac{V_s - 2V_o}{100k} = 0 \Rightarrow V_s \left(\frac{1}{20k} + \frac{1}{100k} \right) = \frac{2V_o}{100k}$$


$$V_s \left(\frac{6}{100k} \right) = \frac{2V_o}{100k}$$

$$\Rightarrow \boxed{V_o = 3V_s}$$

$$i_o = \frac{V_o - V_N}{50k} = \frac{3V_s - \frac{V_s}{2}}{50k} = \frac{5V_s}{100k} = \frac{5(2)}{100k} = 0.1mA$$

$$\boxed{i_o = 0.1mA}$$

18 1:55

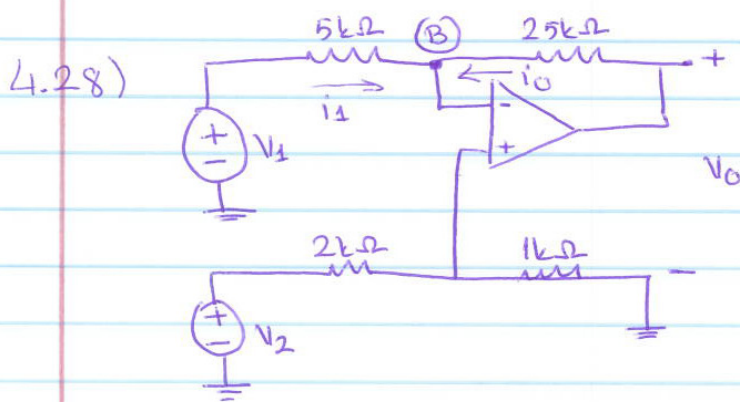

$$V_n = V_p \quad \text{and} \quad i_n = i_p = 0$$

$$V_p = \frac{1}{1+2} V_2 = \frac{V_2}{3} = V_n$$

KCL for node (B)


$$i_1 + i_0 = 0 \Rightarrow \frac{V_1 - V_n}{5} + \frac{V_0 - V_n}{25} = 0 \quad (V_n = V_p = \frac{V_2}{3})$$

$$\Rightarrow \frac{V_1}{5} - \frac{6V_n}{25} + \frac{V_0}{25} = 0$$

$$\Rightarrow \frac{V_0}{25} = \frac{6}{25} \frac{V_2}{3} - \frac{V_1}{5} \Rightarrow \frac{V_0}{25} = \frac{2V_2}{25} - \frac{V_1}{5}$$

$$\Rightarrow \boxed{V_0 = 2V_2 - 5V_1}$$

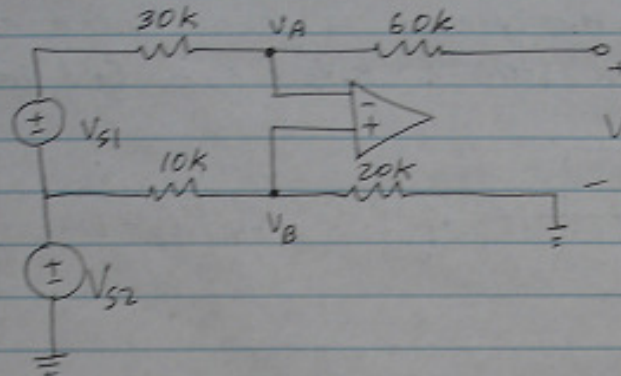4.29 Find V_o in terms of inputs V_{s1} and V_{s2}



$$\begin{aligned} V_N &= V_P \\ I_N &= I_P = 0 \\ V_A &= V_N \\ V_B &= V_P \end{aligned}$$

$$V_B = \frac{20k}{20k+10k} V_{s2} = \frac{2}{3} V_{s2} = V_N = V_P$$

KCL @ node A:

$$\frac{V_A - (V_{s1} + V_{s2})}{30k} + \frac{V_A - V_o}{60k} = 0$$

$$\frac{\frac{2}{3} V_{s2} - V_{s1} - V_{s2}}{30k} + \frac{\frac{2}{3} V_{s2} - V_o}{60k} = 0$$


$$\frac{2}{3} V_{s2} - V_{s1} - V_{s2} = \frac{1}{2} \left(V_o - \frac{2}{3} V_{s2} \right)$$

$$\frac{2}{3} V_{s2} - V_{s2} + \frac{1}{3} V_{s2} = V_{s1} = \frac{V_o}{2}$$

$$\boxed{V_o = -2V_{s1}}$$

18 1:55

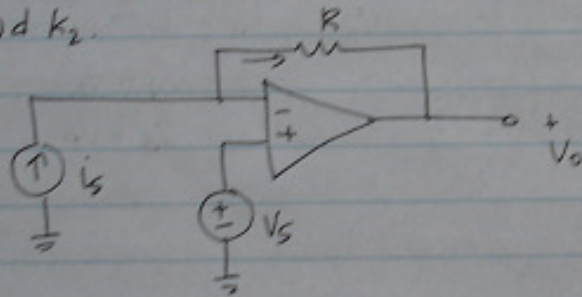4.32) The inputs to the circuit are a current source i_s and a voltage source V_s . When the op-amp is in its linear range, the output voltage has the form $V_o = k_1 V_s + k_2 i_s$. Find the constants k_1 and k_2 .




$$V_p = V_n = V_s$$

$$i_n = i_p = 0$$

$$\frac{V_n - V_o}{R} = i_s$$

$$V_o - V_s = -i_s R \quad \Rightarrow \quad V_o = V_s - R i_s$$
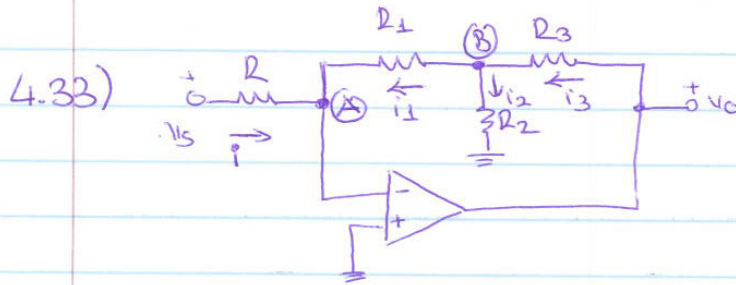
$$\therefore \begin{cases} k_1 = 1 \\ k_2 = -R \end{cases}$$



$$V_n = V_p = 0 \text{ and } i_n = i_p = 0$$

Apply KCL for Node A

$$i + i_1 = 0 \Rightarrow \frac{V_s - V_n}{R} + \frac{V_B - V_n}{R_1} = 0 \Rightarrow V_B = \frac{-R_1}{R} V_s$$

Apply KCL for Node B

$$-i_1 - i_2 + i_3 = 0 \Rightarrow \frac{-V_B}{R_1} - \frac{V_B}{R_2} + \frac{V_o - V_B}{R_3} = 0$$

$$\Rightarrow V_B \left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) + \frac{V_o}{R_3} = 0 \quad \left(V_B = \frac{-R_1}{R} V_s \right)$$


$$\Rightarrow \frac{-R_1}{R} V_s \left(-\frac{1}{R_1} - \frac{1}{R_2} - \frac{1}{R_3} \right) + \frac{V_o}{R_3} = 0$$

$$\Rightarrow V_s \left(\frac{1}{R} + \frac{R_1}{RR_2} + \frac{R_1}{RR_3} \right) = \frac{-V_o}{R_3}$$

$$\Rightarrow V_o = - \left(\frac{R_3}{R} + \frac{R_1 R_3}{RR_2} + \frac{R_1}{R} \right) V_s$$

$$\Rightarrow V_o = - \left(\frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R R_2} \right) V_s$$

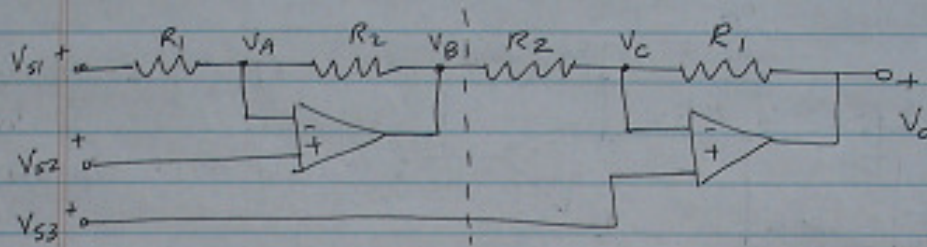4.35) Find V_o in terms of the inputs V_{s1} , V_{s2} , and V_{s3}



For op-amp 1 : $V_p = V_N = V_{s2}$, $i_p = i_N = 0$
 $V_A = V_{s2}$

KCL @ A:

$$\frac{V_A - V_{s1}}{R_1} + \frac{V_A - V_B}{R_2} = 0$$

$$\frac{V_{s2} - V_{s1}}{R_1} + \frac{V_{s2} - V_B}{R_2} = 0$$

$$\frac{-V_B}{R_2} = -\frac{V_{s2}}{R_1} + \frac{V_{s1}}{R_1} - \frac{V_{s2}}{R_2} \Rightarrow V_B = R_2 \left(\frac{V_{s2}}{R_1} - \frac{V_{s1}}{R_1} + \frac{V_{s2}}{R_2} \right)$$

For op-amp 2 : $V_p = V_N = V_{s3}$, $i_p = i_N = 0$

KCL @ C

$$\frac{V_C - V_B}{R_2} + \frac{V_C - V_o}{R_1} = 0$$

$$\frac{V_{s3} - V_B}{R_2} + \frac{V_{s3} - V_o}{R_1} = 0$$


$$\frac{V_{s3}}{R_2} - \frac{V_{s2} R_2}{R_2 R_1} + \frac{V_{s1} R_2}{R_2 R_1} + \frac{V_{s2}}{R_2} + \frac{V_{s3}}{R_1} = \frac{V_o}{R_1}$$

$$V_o = V_{s3} \frac{R_1}{R_2} - V_{s2} + V_{s1} + V_{s2} \frac{R_1}{R_2} + V_{s3}$$

$$V_o = V_{s1} - \left(1 + \frac{R_1}{R_2}\right) V_{s2} + \left(1 + \frac{R_1}{R_2}\right) V_{s3}$$

18 1:5

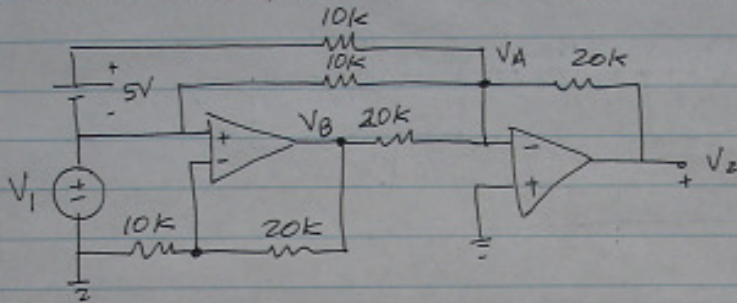4.38) Find the output V_2 in terms of the input V_1 .



Op-Amp 2: $V_p = V_n = 0$

$i_p = i_n = 0$

Op-Amp 1: $V_p = V_n = V_1$

KCL @ A:

$$\frac{V_A + 5 + V_1}{10k} + \frac{V_A - V_1}{10k} + \frac{V_A - V_B}{20k} + \frac{V_A - V_2}{20k} = 0$$

$$\frac{V_A}{20k} + \frac{5}{10k} - \frac{V_1}{10k} - \frac{V_B}{20k} - \frac{V_2}{20k} = 0$$

$$V_B - V_2 = 10 \quad \text{--- (1)}$$

KCL @ B:

$$\frac{V_B - V_1}{20k} + \frac{V_B - V_A}{20k} = 0$$

$$\frac{V_B - V_1}{20k} + \frac{V_B}{20k} = 0$$

$$\frac{V_B}{10k} = \frac{V_1}{20k} \Rightarrow V_B = \frac{V_1}{2} \quad \text{--- (2)}$$

plugging in (2) in (1)

$$\frac{V_1}{2} - V_2 = 10$$

$$V_2 = \frac{V_1}{2} - 10$$


$$\frac{V_1}{10} + \frac{V_1 - V_B}{20}$$

$$V_1 \left(\frac{1}{10} + \frac{1}{20} \right) - \frac{V_B}{20}$$


$$V_1 \left(\frac{3}{20} \right) - \frac{V_1}{20}$$

18 1:56

4.8)

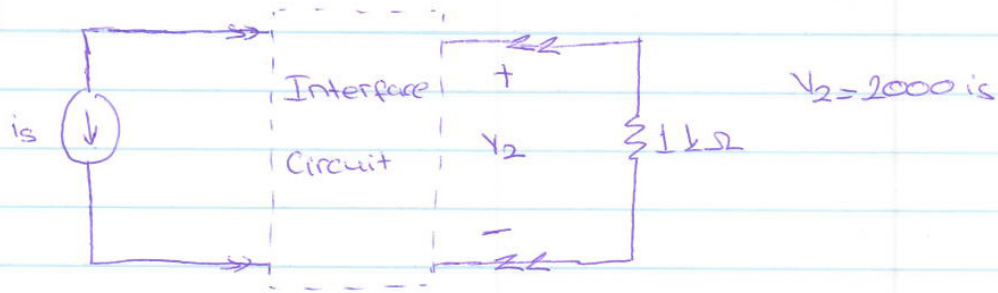

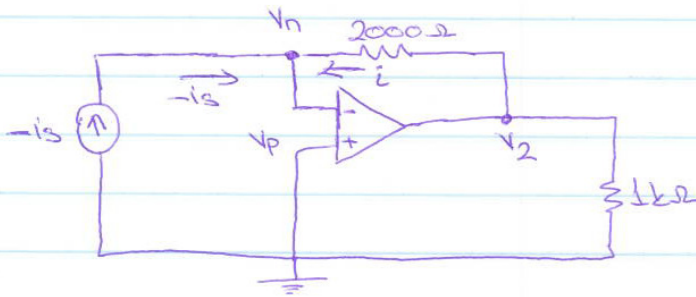You can find different solution. Here is the one by inspiring from 4.32.



Let's check if it works

$$v_n = v_p = 0 \text{ and } i_n = i_p = 0$$


$$-i_s + i = 0 \Rightarrow -i_s + \frac{v_2}{2000} = 0 \Rightarrow v_2 = 2000 i_s \checkmark$$

4.54) The output voltage of a semi-conductor temp. sensor is $V_s = (10T + 500) \text{ mV}$, where T - temp ($^{\circ}\text{C}$). The sensor is to be used to measure temperatures in the range -40°C to 110°C . Design an interface circuit that translates this temperature range to a 0V to 3V output voltage range. Use a standard 5V reference source to obtain any required bias voltage.

$$-40^{\circ}\text{C} \leq T \leq 110^{\circ}\text{C} \Rightarrow 0.1 \text{ V} \leq V_s \leq 1.6 \text{ V}$$

$$\text{Output voltage desired } 0 \leq V_o \leq 3 \text{ V}$$

Example : one possible design

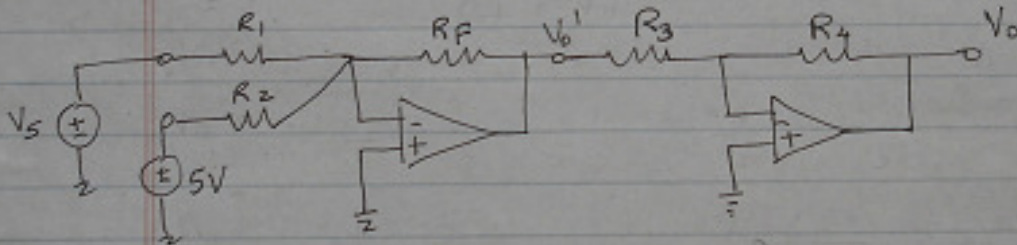

$$V_0' = -\frac{R_F}{R_1} V_s - \frac{R_F}{R_2} (5 \text{ V})$$

$$V_o = \frac{-R_4}{R_3} V_0'$$

$$R_F = 1 \text{ k}, R_1 = R_2 = R_4 = 1 \text{ k}, R_3 = 3 \text{ k}$$

$$V_0' = -V_s - 5$$

$$V_o = \frac{-1}{3} (-V_s - 5) = \frac{V_s + 5}{3}$$

$$\text{if } V_s = 0.1 \Rightarrow V_o = \frac{5.1}{3} = 1.7 \text{ V}$$

$$\text{if } V_s = 1.6 \Rightarrow V_o = \frac{6.6}{3} = 2.2 \text{ V}$$