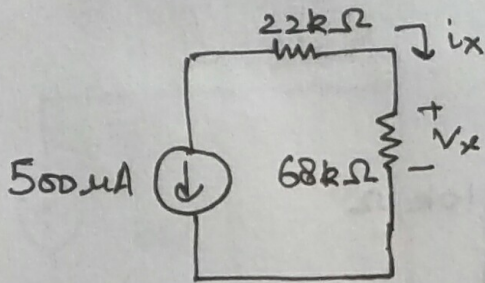



2.25)



$$i_x = -500 \mu\text{A}$$

$$\begin{aligned} V_x &= i_x \times 68 \text{ k}\Omega \\ &= -500 \times 10^{-6} \times 68 \times 10^3 \\ &= -34000 \times 10^{-3} \\ &= -34 \text{ V} \end{aligned}$$

2.29)

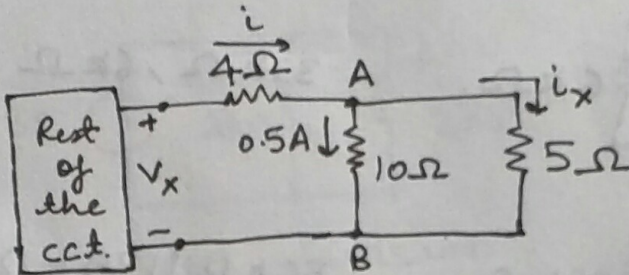

$$\begin{aligned} \text{KCL at A: } i - 0.5 - i_x &= 0 \\ \Rightarrow i &= 0.5 + i_x \end{aligned}$$

$$V_{10\Omega} = V_{5\Omega} \text{ (KVL)}$$

$$\Rightarrow 10 \times 0.5 = 5 \times i_x$$

$$\Rightarrow i_x = 1 \text{ A}$$


$$\therefore i = 1.5 \text{ A}$$

$$V_x = V_{4\Omega} + V_{10\Omega} = 4 \times 1.5 + 10 \times 0.5$$

$$\Rightarrow V_x = 11 \text{ V}$$

2.33)

$$i_x = -0.5 \text{ mA}$$

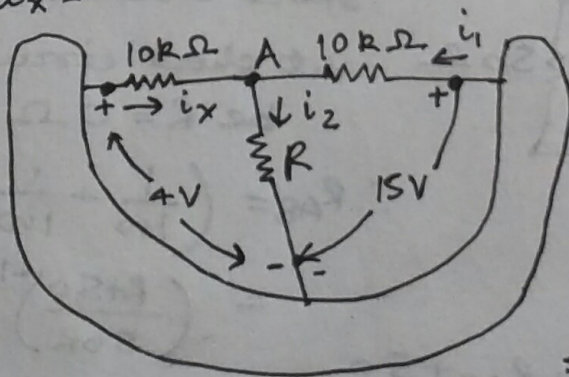

KCL at A:

$$i_x + i_1 - i_2 = 0$$

$$\begin{aligned} 4 &= 10 \times 10^3 \times (-0.5) \times 10^{-3} \\ &\quad + i_2 \times R \end{aligned}$$

$$\Rightarrow 4 = -5 + i_2 R \quad \text{--- (i)}$$

$$-10 \times 10^3 \times i_1 + 15 - i_2 R = 0$$

$$\Rightarrow 15 = 10 \times 10^3 i_1 + i_2 R$$


$$\therefore i_2 R = 9 \Rightarrow 15 = 10^4 i_1 + 9$$

$$\Rightarrow i_1 = 6 \times 10^{-4} = 0.6 \text{ mA}$$


$$i_2 = i_x + i_1 = -0.5 + 0.6 = 0.1 \text{ mA}$$

$$\therefore R = 9 / 0.1 \times 10^{-3} = 90 \text{ k}\Omega$$


2.37)

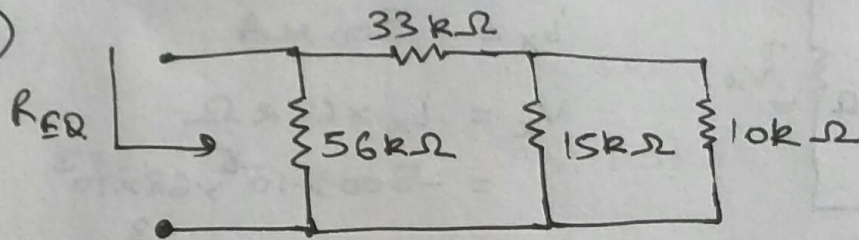
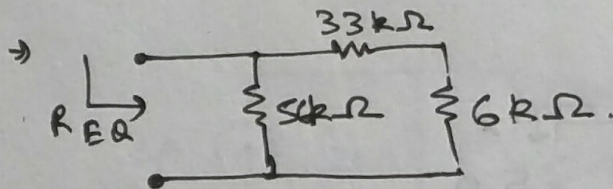
$$15k\Omega \parallel 10k\Omega = \frac{15 \times 10}{15 + 10} = \frac{150}{25} = 6k\Omega$$




33kΩ, 6kΩ series

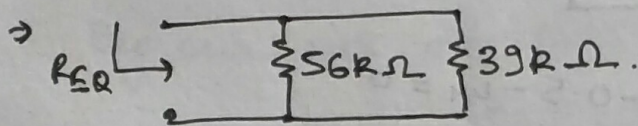

56kΩ || 39kΩ


$$\therefore R_{EQ} = \frac{56 \times 39}{56 + 39} = 22.99k\Omega$$

2.39) switch open.

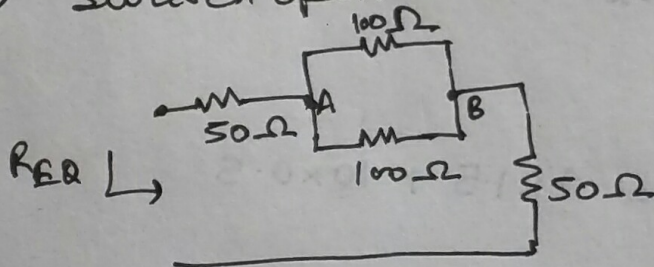

$$\begin{aligned} R_{EQ} &= 50 + (100 \parallel 100) + 50 \\ &= 50 + 50 + 50 = 150\Omega \end{aligned}$$

switch closed


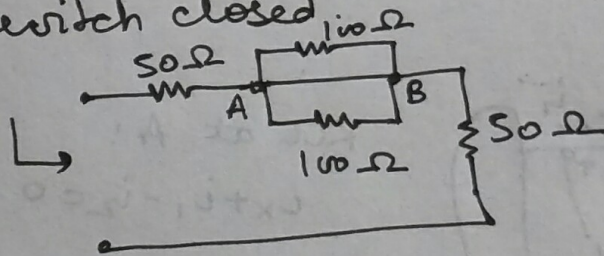


short circuit b/w A, B.
let short circuit resistance be $R = 0\Omega$.


$$\begin{aligned} \therefore R_{AB} &= \left(\frac{1}{100} + \frac{1}{100} + \frac{1}{R} \right)^{-1} \\ &= \left(\frac{R + 50}{50R} \right)^{-1} = \frac{50R}{50 + R} = 0 \end{aligned}$$

$$\begin{aligned} \therefore R_{EQ} &= 50 + R_{AB} + 50 \\ &= 50 + 0 + 50 = 100\Omega \end{aligned}$$


2.42)

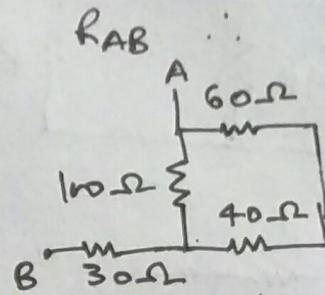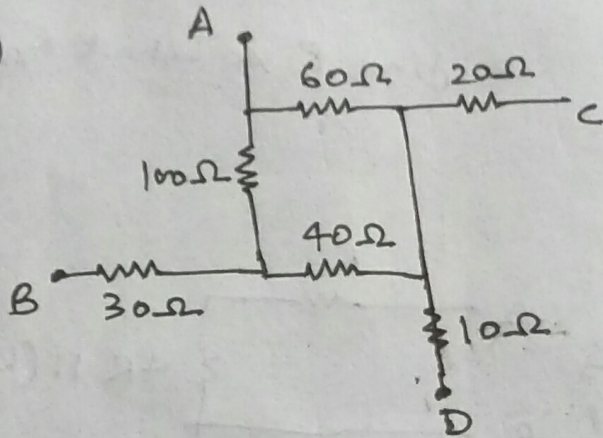

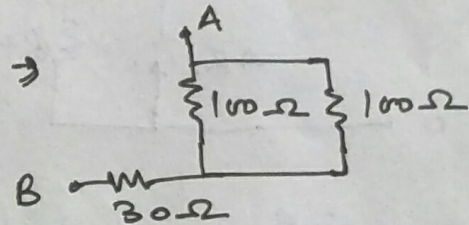60, 40 in series.
 $R = 60 + 40 = 100 \Omega$



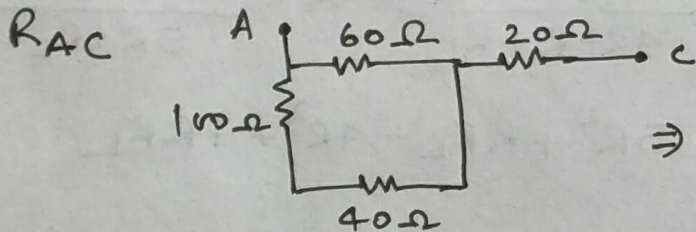
$$\therefore R_{AB} = 30 + (100 \parallel 100) = 30 + 50 = 80 \Omega$$



$\Rightarrow (100, 40 \text{ in series}) R = 100 + 40 = 140 \Omega$

$$60 \parallel 140$$
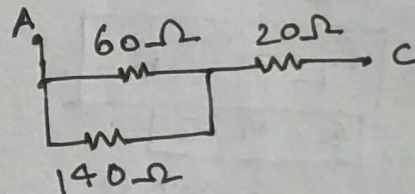
$$\Rightarrow R = \frac{60 \times 140}{60 + 140} = \frac{8400}{200} = 42 \Omega$$



$$\therefore R_{AC} = 42 \Omega + 20 \Omega = 62 \Omega$$

Similarly,

$$R_{AD} = (60 \parallel (100 + 40)) + 10 = (60 \parallel 140) + 10 = 42 + 10 = 52 \Omega$$


$$\begin{aligned} R_{BC} &= 30 + ((60 + 100) \parallel 40) + 20 \\ &= 30 + (160 \parallel 40) + 20 \\ &= 50 + \frac{160 \times 40}{160 + 40} = 50 + \frac{6400}{200} = 32 + 32 = 64 \Omega \end{aligned}$$

$$R_{BD} = 30 + ((60 + 100) \parallel 40) + 10 = 32 + 40 = 72 \Omega$$


$$R_{C-D} = 10 + ((60 + 100 + 40) \parallel 0) + 20 = 30 \Omega$$

(as short circuit)

6

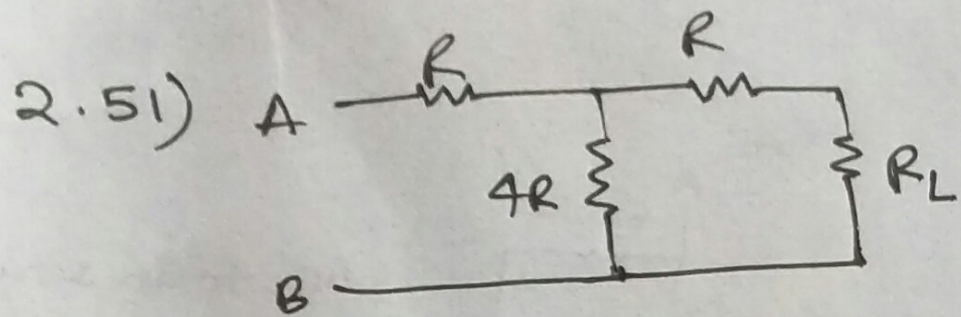

to find R so that $R_{AB} = R_L$.

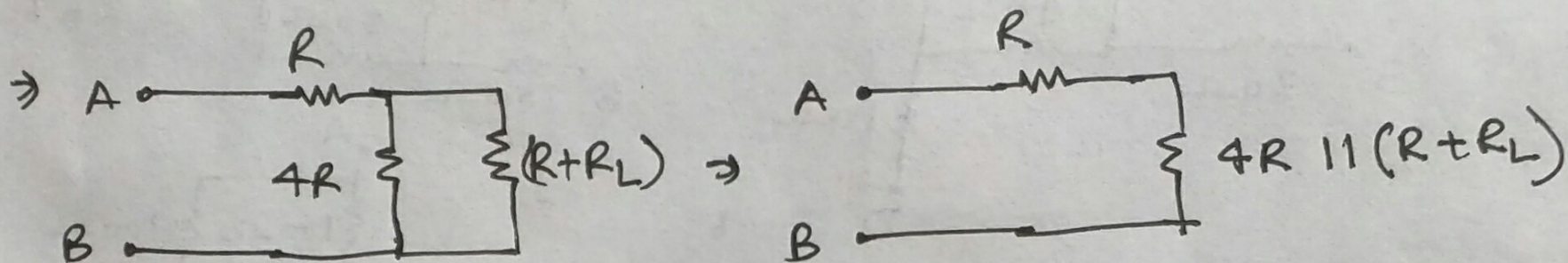

$$\therefore R_{AB} = R + (4R \parallel (R+R_L))$$

$$\Rightarrow R_L = R + \frac{4R \times (R+R_L)}{4R+R+R_L} = R + \frac{4R^2 + 4RR_L}{5R+R_L}$$

$$\Rightarrow 5RR_L + R_L^2 = 5R^2 + RR_L + 4R^2 + 4RR_L$$



$$\Rightarrow R_L^2 = 9R^2$$

$$\Rightarrow \boxed{R_L = 3R}$$

$$\Rightarrow \boxed{R = R_L/3}$$

verify: $R_{AB} = R + (4R \parallel (R+3R))$
 $= R + (4R \parallel 4R)$
 $= R + 2R = 3R = R_L$

2.56)

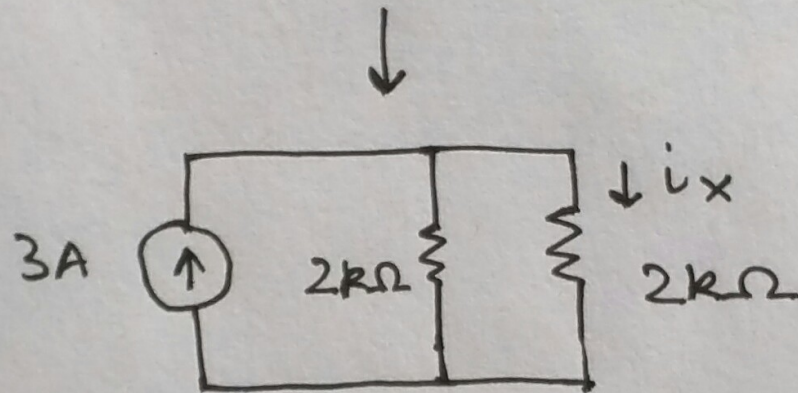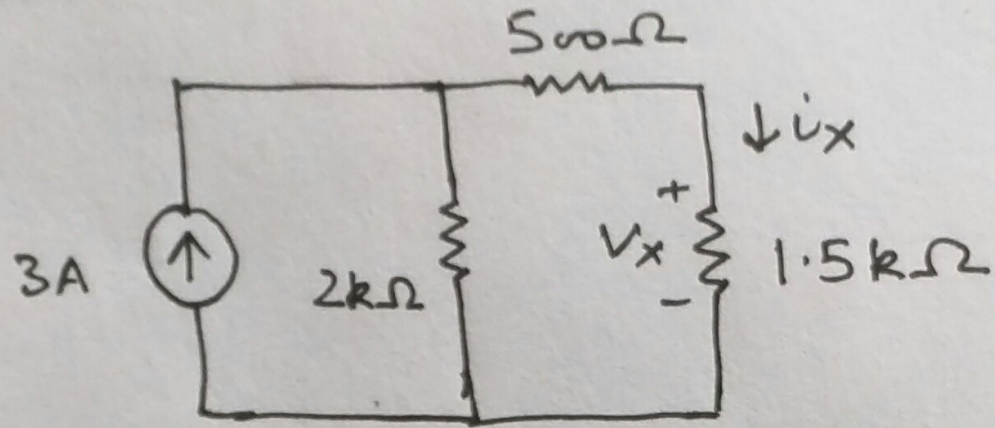


By current division,


$$i_x = \frac{2\text{k}\Omega}{2\text{k}\Omega + 2\text{k}\Omega} \times 3 = 1.5\text{A}$$

$$\therefore V_x = 1.5\text{A} \times 1.5\text{k}\Omega = 2.25\text{kV}$$

2.72)

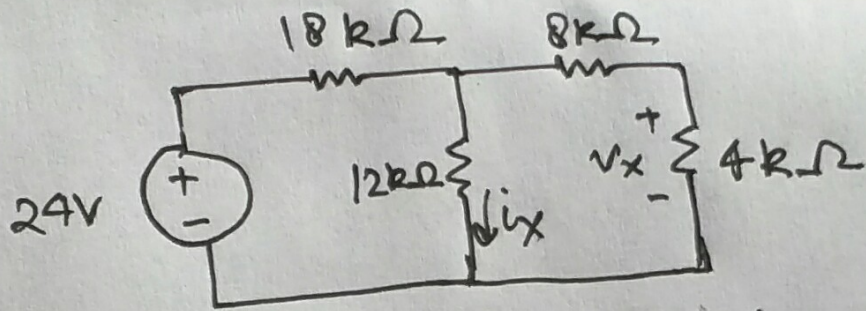

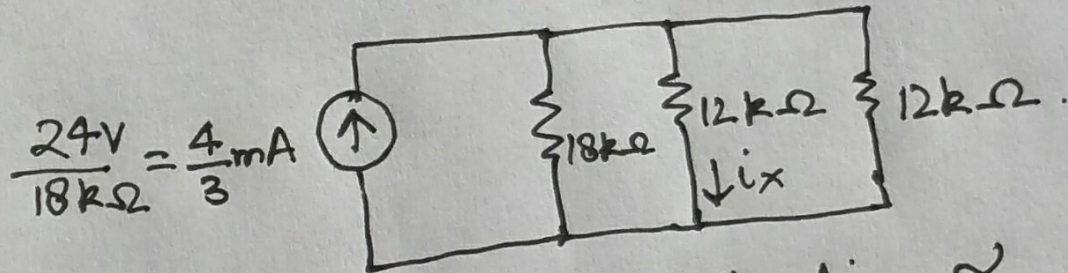↓ Source transformation & combining $8k\Omega$ & $4k\Omega$



$$\frac{24V}{18k\Omega} = \frac{4mA}{3}$$

Since current distribution $\propto \frac{1}{\text{Resistance}}$. (as $18k\Omega, 12k\Omega, 12k\Omega$ in parallel)

current distribution in $18k\Omega, 12k\Omega, 12k\Omega$ is in ratio


$$\frac{1}{18} : \frac{1}{12} : \frac{1}{12} = 2 : 3 : 3$$

$$\therefore i_x = \frac{3}{8} \times \frac{4}{3} \text{ mA} = 0.5 \text{ mA}$$


$$\text{Also current through } 4k\Omega \text{ resistor} = \frac{3}{8} \times \frac{4}{3} \text{ mA} = 0.5 \text{ mA}$$

$$\therefore V_x = 0.5 \times 10^{-3} \times 4 \times 10^3 = 2 \text{ V}$$

2.73)

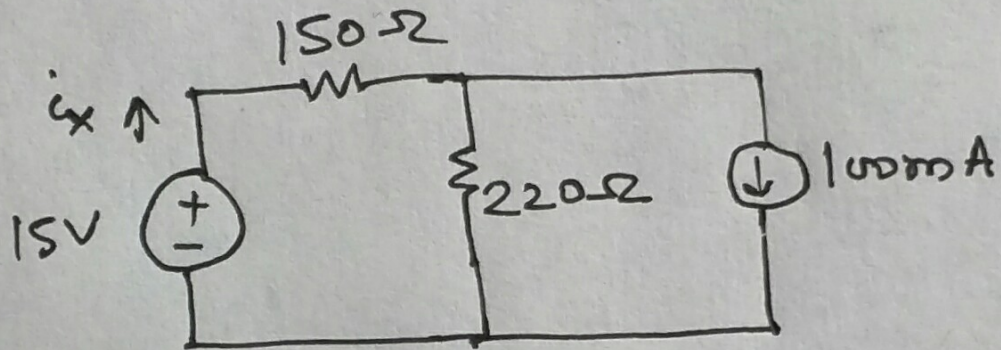

~~Solve~~!

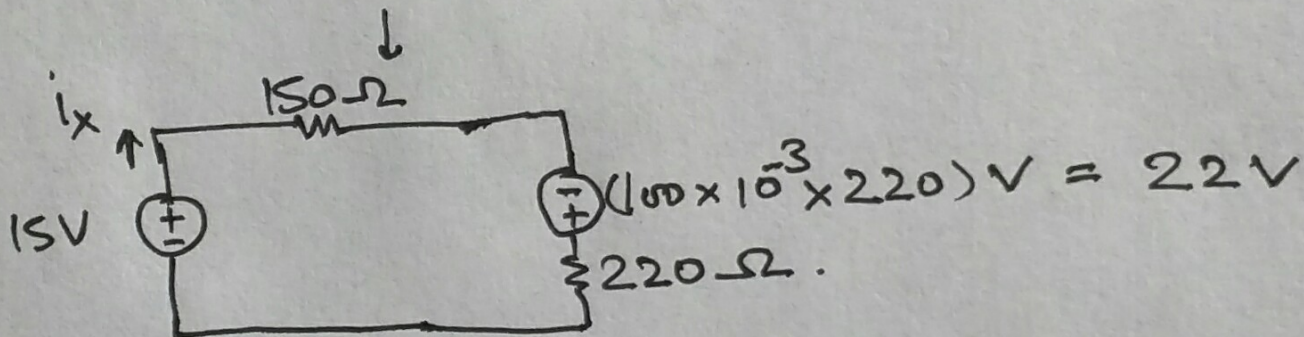

By KVL: $-15 + 150 \times i_x - (22) + 220 i_x = 0$

$\Rightarrow i_x = 100 \text{ mA}$