
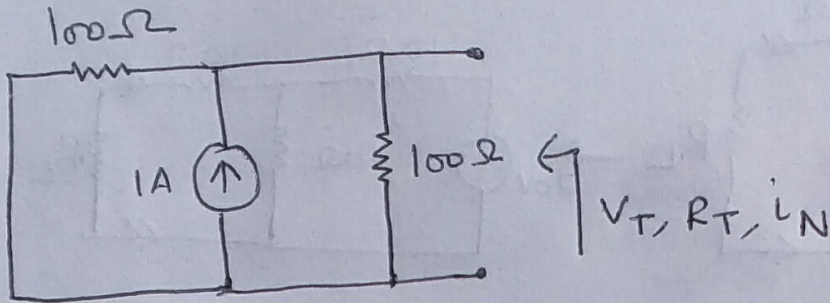


3.48)

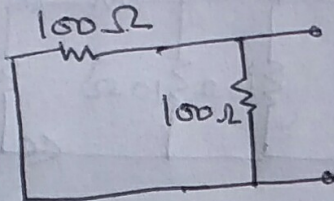


For R_T , switch off current source.



$$R_T = 100 \parallel 100 = 50 \Omega$$

For i_N , short circuit the load side.

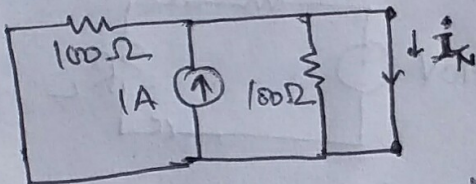


Since the resistors are short-circuited, no current will flow in resistors.

$$i_N = 1A$$

$$V_T = i_N \times R_T = 1 \times 50 = 50 \text{ V}$$

Verify!

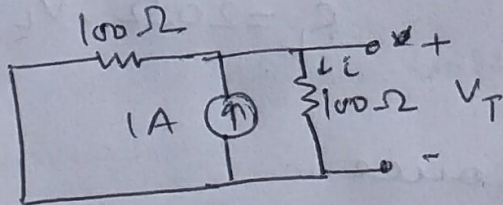


By current division, current i in 100Ω resistor


$$= \frac{1/100 \Omega}{1/100 \Omega + 1/100 \Omega} \times 1A = \frac{100}{100+100} \times 1 = 0.5A$$

$$\therefore V_T = 100 \times 0.5 = 50V$$

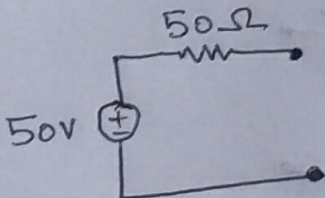Any two pairs can be found & the third can be calculated.




Thevenin equivalent

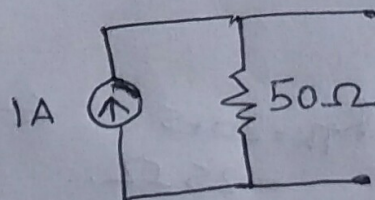


Norton equivalent


3.51)

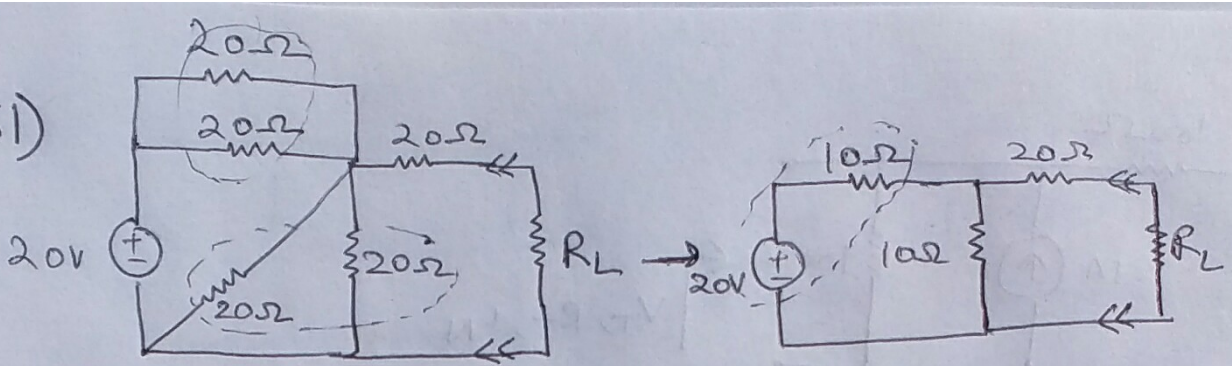

↓ source transformation.

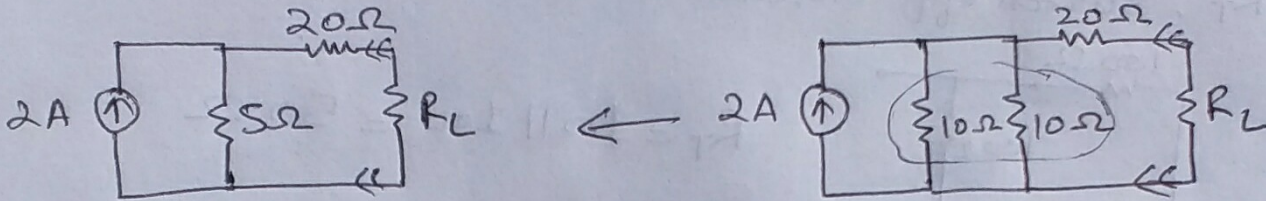

↓ source transformation

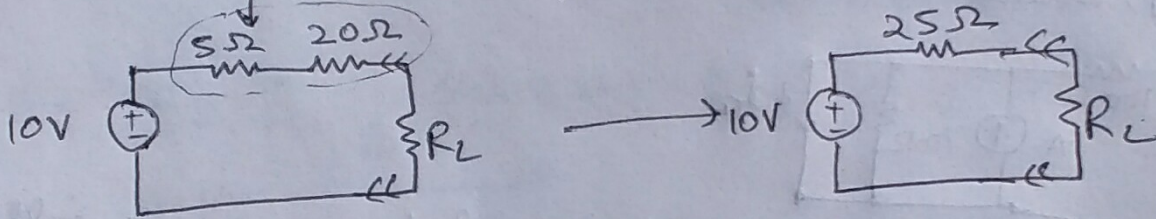

Thevenin equivalent circuit.

Using voltage division,

$$V_L = \frac{R_L}{R_L + 25} \times 10$$




$$R_L = 5\Omega, V_L = 1.67V$$

$$R_L = 10\Omega, V_L = 2.86V$$

$$R_L = 20\Omega, V_L = 4.44V$$


R_{Th} alternate!

switch off voltage source.

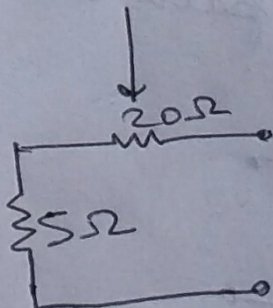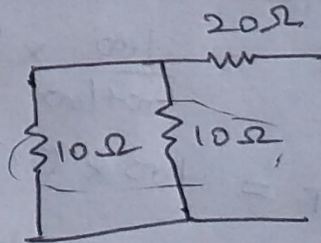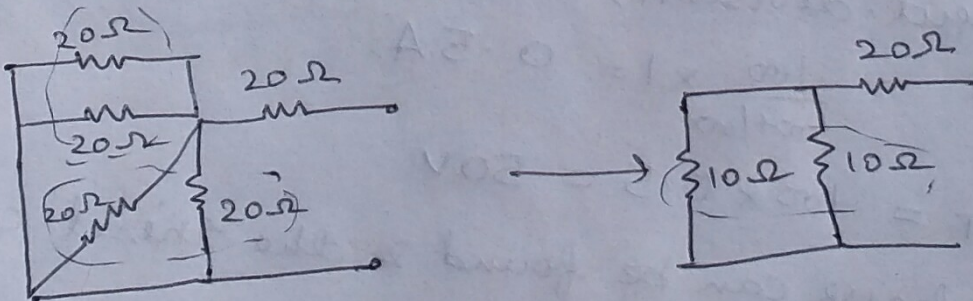


$$R_{Th} = 20 + 5 = 25\Omega$$



3.64)

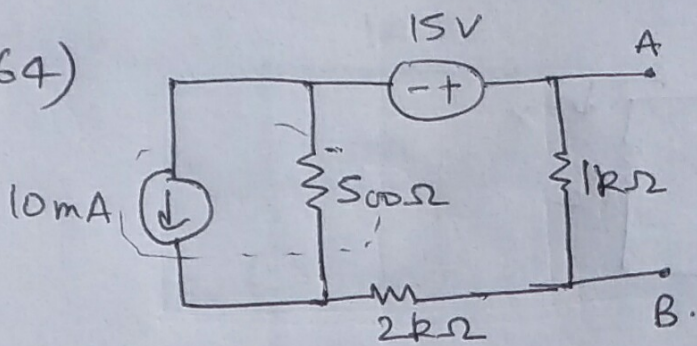


Source transformation

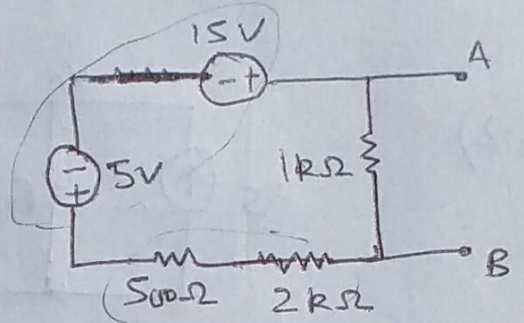


source addition

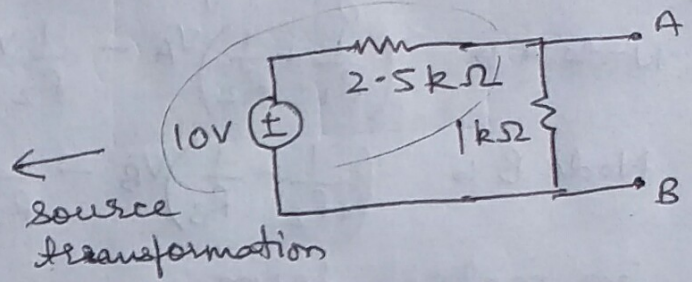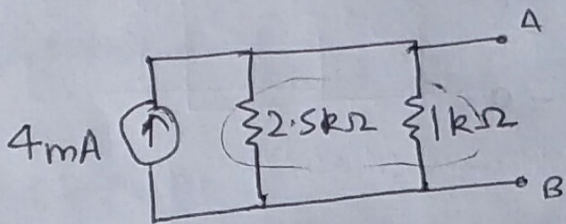
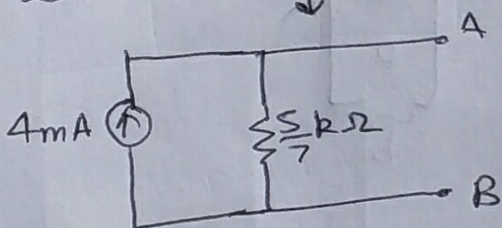
$$\frac{5}{7} k\Omega = \frac{2500\Omega \times 1000\Omega}{2500\Omega + 1000\Omega} \quad \downarrow \quad 2.5k\Omega \parallel 1k\Omega = \frac{2500 \times 1000}{2500 + 1000} = \frac{2500000}{3500} = 714.28\Omega$$




Source transformation

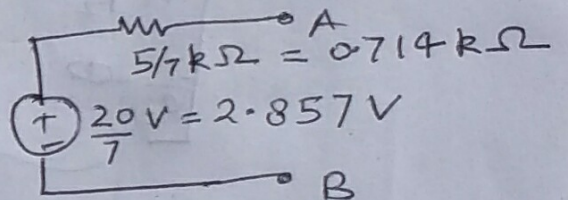

Thevenin eqt.


Alternate

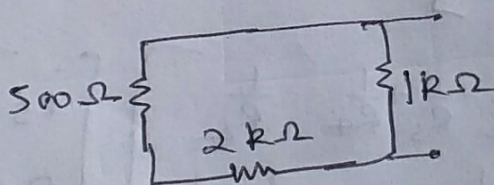For R_T , switch off the voltage & current sources.



$$\rightarrow 2.5k\Omega \parallel 1k\Omega \rightarrow R_{eq} = 2.5k\Omega \parallel 1k\Omega = 0.714k\Omega$$

3.2)

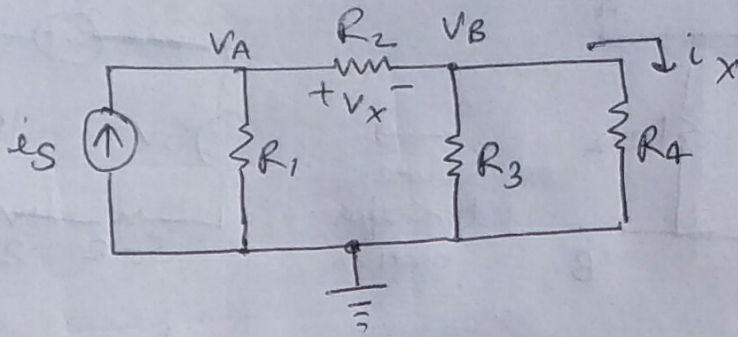

a) Node voltage equations

$$\text{Node A} \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V_A - \frac{1}{R_2} V_B - i_s = 0$$

$$\text{Node B} \Rightarrow \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) V_B - \frac{1}{R_2} V_A = 0$$

in matrix form.

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

$$\Rightarrow Ax = b$$

$$x = A^{-1} b$$

$$b) \Rightarrow \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix}^{-1} \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$

$$= \left(\frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{1}{R_2^2}} \right) \begin{bmatrix} \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & \frac{1}{R_2} \\ \frac{1}{R_2} & \frac{1}{R_1} + \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} i_s \\ 0 \end{bmatrix}$$


$$\Rightarrow V_A = \left(\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{1}{R_2^2} \right)^{-1} \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) i_s$$

$$V_B = \left(\left(\frac{1}{R_1} + \frac{1}{R_2} \right) \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) - \frac{1}{R_2^2} \right)^{-1} \frac{i_s}{R_2}$$

$$c) V_x = V_A - V_B$$

$$i_x = \frac{V_B}{R_4}$$

3.5)

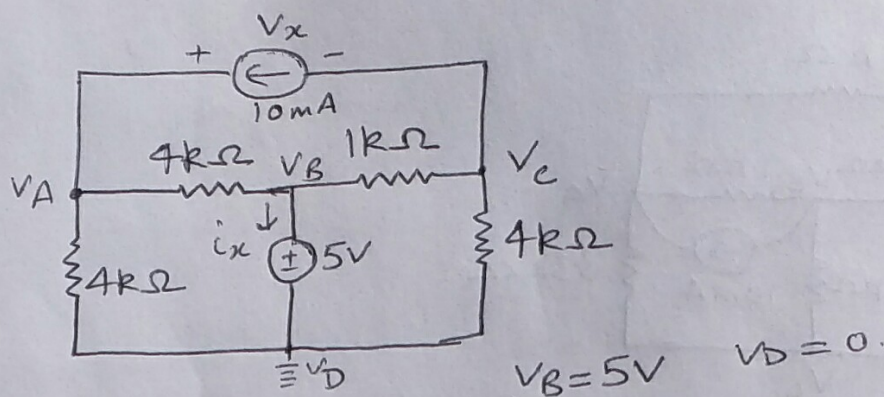

a)

$$\text{Node A: } \left(\frac{1}{4 \times 10^3} + \frac{1}{4 \times 10^3} \right) V_A - \frac{V_B}{4} - 10 \times 10^{-3} = 0$$

$$\text{Node C: } \left(\frac{1}{4 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_C + 10 \times 10^{-3} - \frac{V_B}{1 \times 10^3} = 0$$

$$\underbrace{\begin{bmatrix} \frac{1}{4 \times 10^3} + \frac{1}{4 \times 10^3} & 0 \\ 0 & \frac{1}{4 \times 10^3} + \frac{1}{1 \times 10^3} \end{bmatrix}}_A \underbrace{\begin{bmatrix} V_A \\ V_C \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 10 \times 10^{-3} + 5/4 \\ 5 \times 10^{-3} - 10 \times 10^{-3} \end{bmatrix}}_b$$

(substituting
value of B.)

b) Solving the above equation

$$Ax = b.$$

$$\text{as } x = A^{-1}b.$$

$$V_A = 22.5V$$


$$V_C = -4V$$

$$c) V_x = V_A - V_C = 22.5 - (-4) = 26.5V$$

$$\text{at Node B: } \frac{V_A - V_B}{4 \times 10^3} + \frac{V_C - V_B}{1 \times 10^3} = i_x$$

$$\Rightarrow i_x = -4.625 \text{ mA}$$

3.5) Using supernode.

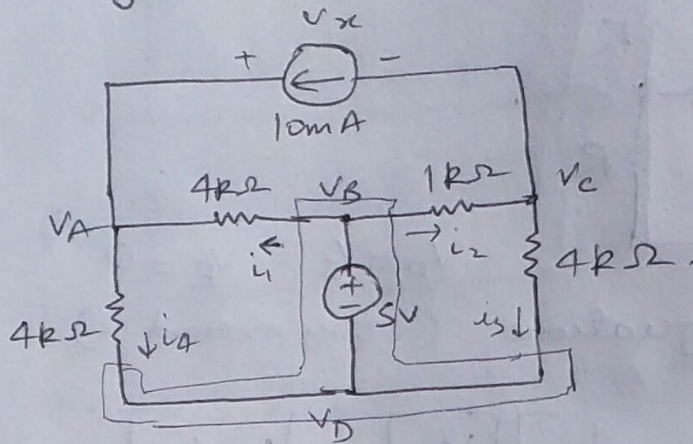

$$-i_1 - i_2 + i_3 + i_4 = 0$$

$$\Rightarrow -\frac{v_B - v_A}{4 \times 10^3} - \frac{v_B - v_C}{1 \times 10^3} + \frac{v_A - v_D}{4 \times 10^3} + \frac{v_C - v_D}{4 \times 10^3} = 0.$$

$$v_B - v_D = 5V.$$


$$\text{KCL at A: } \frac{v_B - v_A}{4 \times 10^3} + 10 \times 10^{-3} - \frac{v_A - v_D}{4 \times 10^3} = 0$$

$$\text{KCL at C: } \frac{v_B - v_C}{1 \times 10^3} - \frac{v_C - v_D}{4 \times 10^3} - 10 \times 10^{-3} = 0.$$

Solving this gives.

$$v_A = 22.5V \quad v_C = -4V.$$

3.8)

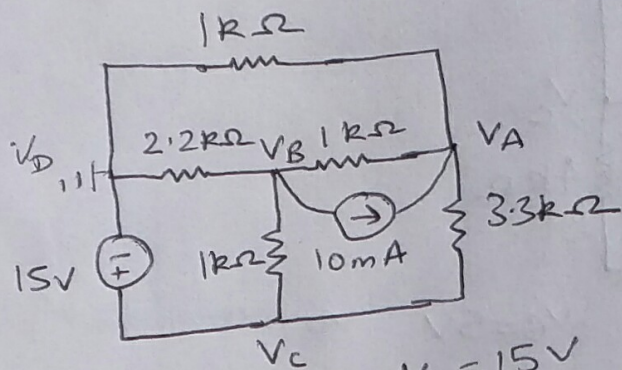

Using method 2.

$$a) \text{ Node A: } \left(\frac{1}{1 \times 10^3} + \frac{1}{3.3 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_A - \frac{1}{1 \times 10^3} V_B - \frac{1}{3.3 \times 10^3} V_C - 10 \times 10^{-3} = 0$$

$$\text{Node B: } \left(\frac{1}{1 \times 10^3} + \frac{1}{2.2 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_B - \frac{1}{1 \times 10^3} V_A - \frac{1}{1 \times 10^3} V_C + 10 \times 10^{-3} = 0$$

Multiplying both equations by 10^3 & substituting for V_C , we get.

$$\begin{bmatrix} 1 + \frac{1}{3.3} + 1 & -1 \\ -1 & 1 + \frac{1}{2.2} + 1 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} \frac{15}{3.3} + 10 \\ 15 - 10 \end{bmatrix} = \begin{bmatrix} 14.546 \\ 5 \end{bmatrix}$$


b) Solving the ~~at~~ above equation, we get.

$$V_A \approx 8.75 \text{ V} \quad V_B \approx 5.6 \text{ V}$$

$$V_x = V_A - 0 = 8.75 \text{ V}$$

$$i_x = \frac{0 - V_B}{2.2 \times 10^3} \approx -2.55 \text{ mA}$$

3.10)

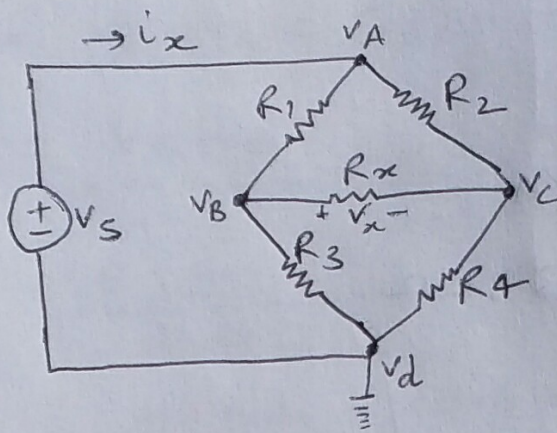

a) $V_D = 0V$
 $V_A = V_S$

~~node B: $\left(\frac{1}{R_3} + \frac{1}{R_x} + \frac{1}{R_1}\right)V_B - \frac{1}{R_1}V_A - \frac{1}{R_x}V_C = 0$~~

~~node C: $-\frac{1}{R_x}V_B + \left(\frac{1}{R_x} + \frac{1}{R_2} + \frac{1}{R_4}\right)V_C = 0$~~

node B: $\left(\frac{1}{R_3} + \frac{1}{R_x} + \frac{1}{R_1}\right)V_B - \frac{1}{R_1}V_A - \frac{1}{R_x}V_C = 0$

$\Rightarrow \left(\frac{1}{R_3} + \frac{1}{R_x} + \frac{1}{R_1}\right)V_B - \frac{V_S}{R_1} - \frac{V_C}{R_x} = 0$

node C: $\left(\frac{1}{R_x} + \frac{1}{R_4} + \frac{1}{R_2}\right)V_C - \frac{1}{R_x}V_B - \frac{1}{R_2}V_A - \frac{1}{R_4}V_D = 0$

$\Rightarrow \left(\frac{1}{R_x} + \frac{1}{R_4} + \frac{1}{R_2}\right)V_C - \frac{V_B}{R_x} - \frac{V_S}{R_2} = 0$

$$\begin{bmatrix} \frac{1}{R_3} + \frac{1}{R_x} + \frac{1}{R_1} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & \frac{1}{R_x} + \frac{1}{R_4} + \frac{1}{R_2} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{V_S}{R_1} \\ \frac{V_S}{R_2} \end{bmatrix}$$

for $R_1 = R_4 = 2k\Omega$, $R_2 = R_3 = 500\Omega$, $R_x = 750\Omega$, $V_S = 15V$.

b)

$$\Rightarrow \begin{bmatrix} \frac{1}{500} + \frac{1}{750} + \frac{1}{2000} & -\frac{1}{750} \\ -\frac{1}{750} & \frac{1}{750} + \frac{1}{2000} + \frac{1}{500} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 15/2000 \\ 15/500 \end{bmatrix}$$

$\Rightarrow V_B = 5.32V$

$V_C = 9.68V$

$$\Rightarrow V_x = V_B - V_C = 5.32 - 9.68 = -4.36 \text{ V}$$

$$\begin{aligned} i_x &= -\frac{V_B - V_A}{R_1} + -\frac{V_C - V_A}{R_2} \\ &= -\frac{5.32 - 15}{2000} + -\frac{9.68 - 15}{500} \\ &= 4.8 \text{ mA} + 10.6 \text{ mA} \\ &= 15.4 \text{ mA} \end{aligned}$$

c) R_4 is variable;

$$V_x = 0$$

$$\Rightarrow V_B = V_C$$

$$\begin{bmatrix} \frac{1}{500} + \frac{1}{750} + \frac{1}{2000} & -\frac{1}{750} \\ -\frac{1}{750} & \frac{1}{750} + \frac{1}{500} + \frac{1}{R_4} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 15/2000 \\ 15/500 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0.0038 & -0.0013 \\ -0.0013 & \frac{1}{R_4} + 0.0033 \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 0.0075 \\ 0.03 \end{bmatrix}$$


$$0.0038 V_B - 0.0013 V_C = 0.0075$$

$$\Rightarrow V_B = 3 \text{ V}$$

$$-0.0013 \times 3 + \left(\frac{1}{R_4} + 0.0033 \right) \times 3 = 0.03$$

$$\Rightarrow \frac{1}{R_4} + 0.0033 = 0.0113$$
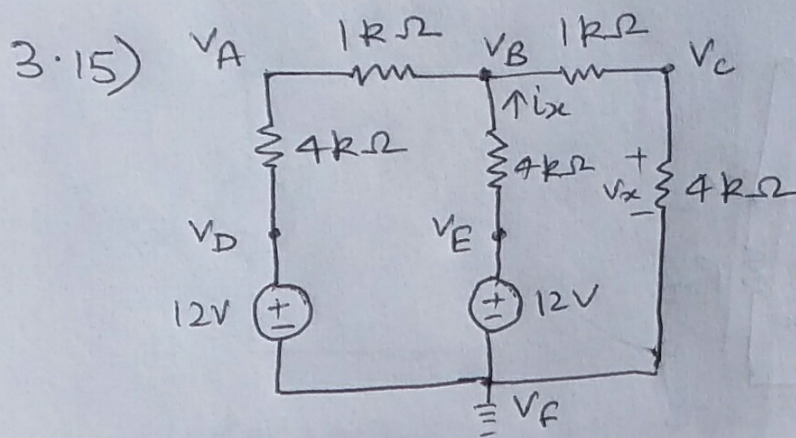
$$\Rightarrow R_4 = \frac{1}{0.0080} = 125 \Omega$$



$$V_D = 12V \quad V_E = 12V \quad V_F = 0$$

Using method 2.

$$a) \text{ Node A: } \left(\frac{1}{4 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_A - \frac{1}{1 \times 10^3} V_B - \frac{V_D}{4 \times 10^3} = 0$$

$$\text{Node B: } \left(\frac{1}{4 \times 10^3} + \frac{1}{1 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_B - \frac{1}{1 \times 10^3} V_A - \frac{1}{1 \times 10^3} V_C - \frac{V_E}{4 \times 10^3} = 0$$

$$\text{Node C: } \left(\frac{1}{4 \times 10^3} + \frac{1}{1 \times 10^3} \right) V_C - \frac{1}{1 \times 10^3} V_B - \frac{1}{4 \times 10^3} V_F = 0$$

Substituting for V_D, V_E & V_F & multiplying by 10^3 both sides

$$\begin{bmatrix} 1.25 & -1 & 0 \\ -1 & 2.25 & -1 \\ 0 & -1 & 1.25 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 3 \\ 3 \\ 0 \end{bmatrix}$$

$$\bullet \quad V_A = 9.05V \quad V_B = 8.31V \quad V_C = 6.65V$$

$$b) \quad i_A = \frac{V_D - V_A}{4 \times 10^3} = \frac{12 - 9.05}{4 \times 10^3} \approx 0.74 \text{ mA}$$


$$i_B = \frac{V_C - V_F}{4 \times 10^3} = \frac{6.65 - 0}{4 \times 10^3} \approx 1.67 \text{ mA}$$

$$c) \quad V_x = V_C - V_F = V_C - 0 = 6.65V$$

$$i_x = \frac{V_E - V_B}{4 \times 10^3} = \frac{12 - 8.31}{4 \times 10^3} \approx 0.93 \text{ mA}$$

another way: $i_x = i_B - i_A = 0.93 \text{ mA}$

3.17)

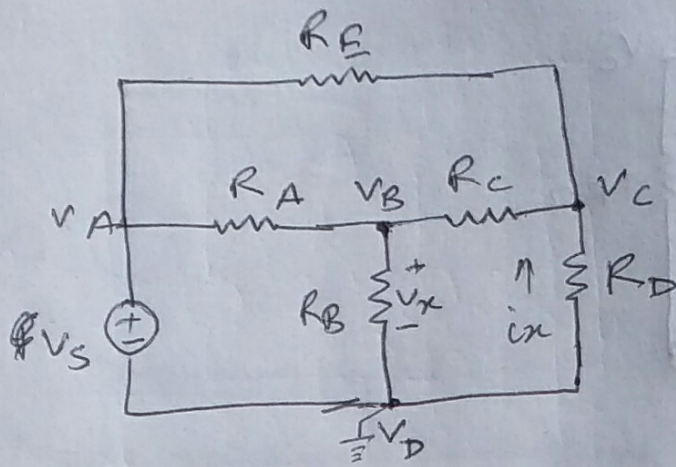

$V_D = 0$ $V_A = V_S$. Using method 2

b) at Node B: $\left(\frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}\right)V_B - \frac{1}{R_A}V_A - \frac{1}{R_B}V_D - \frac{1}{R_C}V_C = 0$

$$\rightarrow \left(\frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}\right)V_B - \frac{V_C}{R_C} = \frac{V_S}{R_A}$$

node C: $\left(\frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E}\right)V_C - \frac{1}{R_C}V_B = \frac{V_S}{R_E}$


$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} & -\frac{1}{R_C} \\ -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} V_S/R_A \\ V_S/R_E \end{bmatrix}$$

e) $\begin{bmatrix} V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \left(\left(\frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}\right)\left(\frac{1}{R_C} + \frac{1}{R_D} + \frac{1}{R_E}\right) - \frac{1}{R_C^2}\right) & \frac{1}{R_C} \\ \frac{1}{R_C} & \frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C} \end{bmatrix} \begin{bmatrix} V_S/R_A \\ V_S/R_E \end{bmatrix}$

$$V_x = V_B$$

$$i_x = \frac{-V_C}{R_D}$$

3.23)

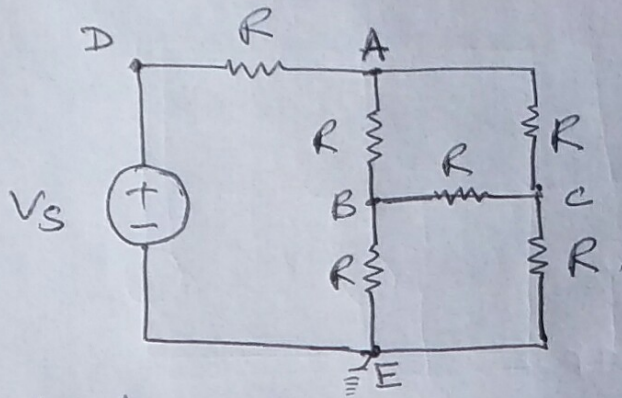

$$V_D = V_s \quad V_E = 0$$

Node voltage equations (Using method 2)

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{R} + \frac{1}{R} & -\frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{1}{R} + \frac{1}{R} + \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & -\frac{1}{R} & \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} V_s/R \\ 0 \\ 0 \end{bmatrix}$$

$$\Rightarrow 3V_A - V_B - V_C = V_s \quad \text{--- (i)}$$

$$-V_A + 3V_B - V_C = 0 \quad \text{--- (ii)}$$

$$-V_A - V_B + 3V_C = 0 \quad \text{--- (iii)}$$

Solving this,

$$V_A = 2V_B$$


$$V_B = V_C$$

As $V_B = V_C$, no current flows through resistor between B & C.

~~So it is an open circuit.~~

So it acts as an ~~open~~ short circuit.

putting in (i)

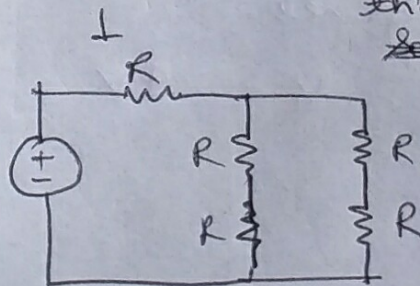

$$R_{Eq} = R_{IN} = R + (2R \parallel 2R) = 2R$$

Alternatively,

current through D to A = current from A to B +
current from A to C.

(KCL at node A).

$$\Rightarrow \frac{V_D - V_A}{R} = \frac{V_A - V_B}{R} + \frac{V_A - V_C}{R}$$

$$\Rightarrow V_S - V_A = 2V_A - (V_B + V_C) = V_A$$

$$\Rightarrow V_A = \frac{V_S}{2}, \quad V_B = \frac{V_S}{4}, \quad V_C = \frac{V_S}{4}$$

current through resistor between D & A is

$$i = \frac{V_S - \frac{V_S}{2}}{R} = \frac{V_S}{2R}$$

equivalent resistance = ?

$$\frac{i}{V_S} = \left(\frac{V_S}{2R} \right) / V_S = \frac{1}{2R}$$

$$\therefore \text{eqnt resistance} = \frac{V_S}{\frac{1}{2R}} = 2R$$