

HW 1 solution


1.7) given $i(t) = 3 \mu\text{A}$ for all t .

Find $q(t)$?

$$\begin{aligned} q(t) &= \int_{t_1}^{t_2} i(t) dt = \int_0^{500\text{ms}} 30 \mu\text{A} dt = (30 \mu\text{A}) (500\text{ms}) \\ &= 15000 \times 10^{-6} \times 10^{-3} \text{C} \\ &= 15 \mu\text{C} \end{aligned}$$

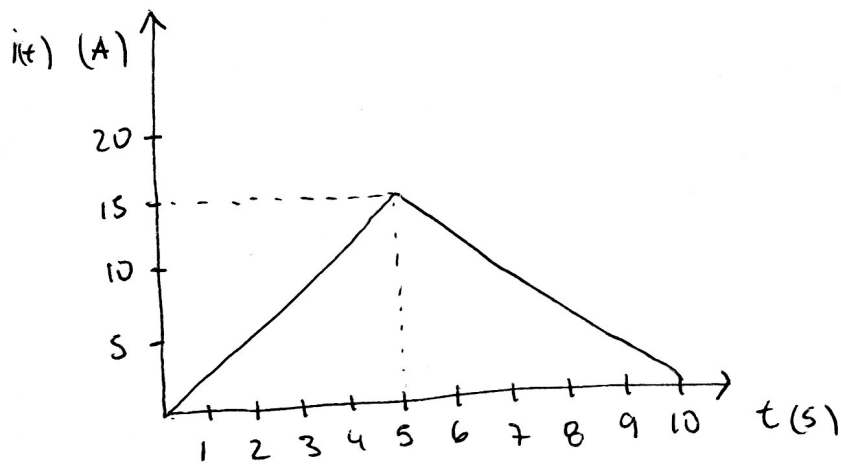1.12)

$$i(t) = \begin{cases} 3t \text{ A} & 0 \leq t \leq 5 \text{ s} \\ 30 - 3t \text{ A} & 5 < t \leq 10 \text{ s} \\ 0 \text{ A} & t > 10 \text{ s} \end{cases}$$



$$q_T = \int_0^5 3t dt + \int_5^{10} (30 - 3t) dt$$

$$= \frac{3}{2} t^2 \Big|_0^5 + \left(30t - \frac{3}{2} t^2 \right) \Big|_5^{10}$$

$$= \frac{3}{2} (5^2) + 30(10) - \frac{3}{2} (10)^2 - 30(5) + \frac{3}{2} (5)^2$$

$$= \frac{3}{2} (25) + 300 - 150 - 150 + \frac{3}{2} (25)$$

$$= 75 \text{ C}$$

1.15)

$$i(t) = \begin{cases} 0 \text{ A} & t < 0 \\ 5e^{-3t} & t \geq 0 \end{cases}$$

$$q(t) = \int_0^t 5e^{-3t_1} dt_1 = -\frac{5}{3} e^{-3t_1} \Big|_0^t = -\frac{5}{3} (e^{-3t} - e^{-3(0)}) \\ = \frac{5}{3} (1 - e^{-3t})$$

1.22) Recall that $P = V \cdot i$

Device	Power	Absorbing / delivering
1	$(15)(-1) = -15$	delivering
2	$(5)(1) = 5$	Absorbing
3	$(10)(2) = 20$	Absorbing
4	$(-10)(-1) = 10$	Absorbing
5	$(20)(-3) = -60$	Delivering
6	$(20)(2) = 40$	Absorbing

Power balance:

$$P_1 + P_2 + \dots + P_6 = -15 + 5 + 20 + 10 - 60 + 40 \\ = 0 \text{ W}$$

2.6) It is given $G = 0.05 \text{ mS}$, Then $R = \frac{1}{0.05 \times 10^{-3} \text{ S}}$

$$R = 20 \text{ k}\Omega$$

Recall that $i = \frac{V}{R}$, where $V = 1.5 \text{ V}$

$$\text{Then, } i = \frac{1.5 \text{ V}}{20 \text{ k}\Omega} = 0.075 \text{ mA}$$

2.9) By the color code, the resistor should be:

$$= 33 \times 10^3 \pm 5\% \Omega$$

$$\text{or } = 33 \times 10^3 \pm 1.65 \times 10^3 \Omega$$

$$= 33 \text{ k}\Omega \pm 1.65 \text{ k}\Omega$$

Therefore, the resistor is not properly coded.


2.15) It is given $i_2 = -6 \text{ A}$ and $i_3 = 2 \text{ A}$

Using KCL we have:

$$-i_1 - i_2 = 0 \Rightarrow i_1 = -i_2 = 6 \text{ A}$$

$$i_2 + i_3 = i_4 \Rightarrow i_4 = -4 \text{ A}$$

~~XXXXXXXX~~

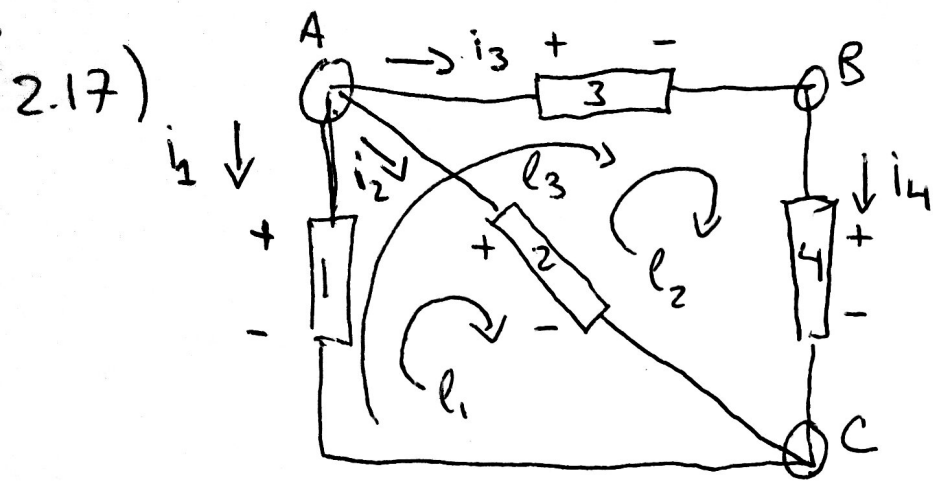

a) Nodes: A, B, C

loops: l_1, l_2, l_3

b) Elements in series: 3 with 4

Elements in parallel: 1 with 2

c) KCL:

$$i_1 + i_2 + i_3 = 0$$

$$i_3 = i_4$$

$$i_4 + i_2 + i_1 = 0$$

KVL:

$$-V_1 + V_2 = 0$$

$$-V_2 + V_3 + V_4 = 0$$

$$-V_1 + V_3 + V_4 = 0$$

2.23) There are not elements in series nor parallel

We are given: $V_2 = 10V$, $V_4 = 10V$, $V_5 = 5V$

Find V_1 , V_3 , V_6

KVL:

$$\begin{aligned} * -V_1 + V_2 + V_4 + V_5 &= 0 \Rightarrow V_1 = V_2 + V_4 + V_5 \\ V_1 &= 10V + 10V + 5V \\ V_1 &= 25V \end{aligned}$$

$$\begin{aligned} * -V_1 + V_2 + V_3 &= 0 \Rightarrow V_3 = V_1 - V_2 \\ V_3 &= 25V - 10V \\ V_3 &= 15V \end{aligned}$$

$$\begin{aligned} * V_6 - V_4 - V_2 &= 0 \Rightarrow V_6 = V_2 + V_4 \\ V_6 &= 10V + 10V \\ V_6 &= 20V \end{aligned}$$

2.27)

