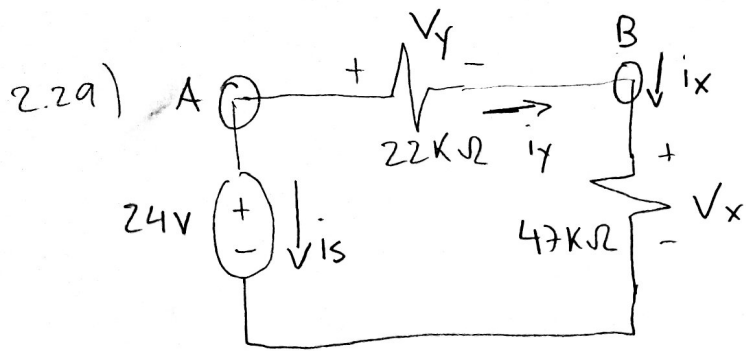


Homework 2



Connection Constraints:

$$\text{KVL: } -24\text{V} + V_y + V_x = 0 \quad (1)$$

$$\text{KCL: Node (A): } i_s + i_y = 0 \Rightarrow i_s = -i_y$$

$$\text{Node (B): } i_y - i_x = 0 \Rightarrow i_y = i_x$$

Element Constraints:

$$V_y = 22\text{k}\Omega i_y = 22\text{k}\Omega i_x$$

$$V_x = 47\text{k}\Omega i_x \quad (2)$$

Using (1) and Replacing V_y and V_x in terms of i_x :

$$-24\text{V} + 22\text{k}\Omega i_x + 47\text{k}\Omega i_x = 0$$


$$69\text{k}\Omega i_x = 24\text{V}$$

$$i_x = \frac{24\text{V}}{69\text{k}\Omega} = 0.347\text{mA}$$

Using (2):

$$V_x = 47\text{k}\Omega (0.347\text{mA}) = 16.34\text{V}$$

Z.34)

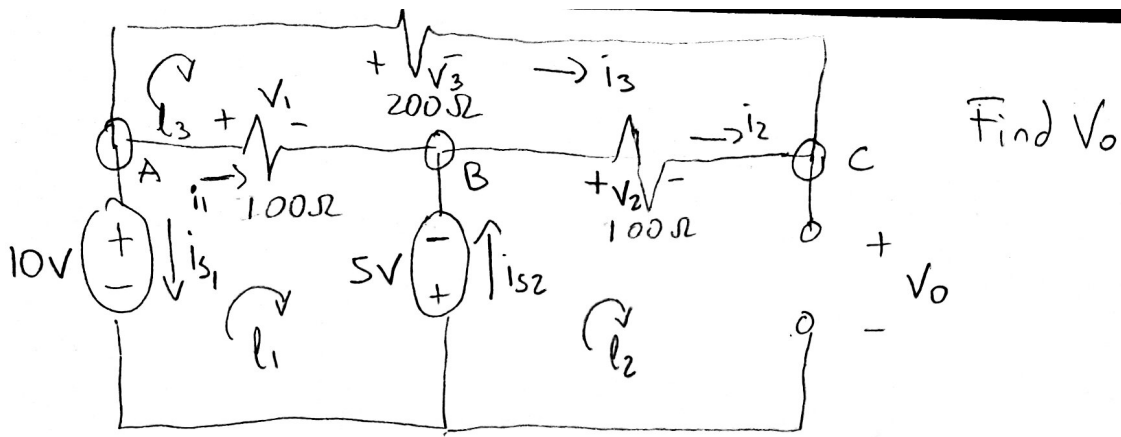

KVL: $l_1: -10V + V_1 - 5V = 0 \Rightarrow V_1 = 15V$

$l_2: 5V + V_2 + V_0 = 0$

$l_3: -V_1 + V_3 - V_2 = 0$

KCL: A: $i_1 + i_3 + i_{s1} = 0$

B: $i_1 + i_{s2} - i_2 = 0$

C: $i_2 + i_3 = 0 \Rightarrow i_2 = -i_3$

Element constraints: $V_1 = 100\Omega i_1 \Rightarrow i_1 = \frac{15V}{100\Omega} = \frac{3}{20}A$

$V_2 = 100\Omega i_2 = -100i_3$

$V_3 = 200\Omega i_3$

In (l_3) replace V_2 and V_3 in terms of i_3 :

$-V_1 + 200\Omega i_3 + 100\Omega i_3 = 0 \Rightarrow -15V + 300\Omega i_3 = 0$


$i_3 = \frac{15V}{300\Omega} = \frac{1}{20}A$

Find V_2 and V_3 :

$V_2 = -100\Omega \left(\frac{1}{20}A\right) = -5V$

$V_3 = 200\Omega \left(\frac{1}{20}A\right) = 10V$

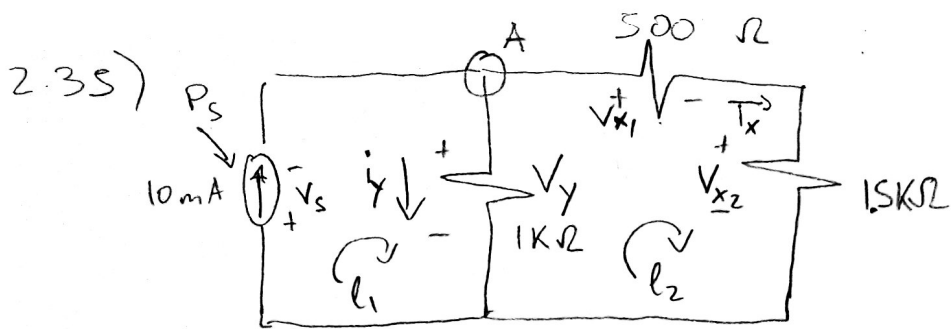From (l_2) : $5V + (-5V) + V_0 = 0 \Rightarrow \boxed{V_0 = 0}$



KCL: A: $10\text{mA} - i_y - i_x = 0 \Rightarrow i_x = 10\text{mA} - i_y$ (1)

KVL: l_1 : $V_s + V_y = 0 \Rightarrow V_s = -V_y$

l_2 : $-V_y + V_{x1} + V_{x2} = 0$

Element constraints:

$V_y = 1\text{k}\Omega i_y$

$V_{x1} = 500\Omega \times i_x = 500\Omega (10\text{mA} - i_y)$

$V_{x2} = 1.5\text{k}\Omega i_x = 1.5\text{k}\Omega (10\text{mA} - i_y)$

Replace in (l_2) V_y , V_{x1} , and V_{x2} in terms of i_y :

$-1\text{k}\Omega i_y + 500\Omega (10\text{mA} - i_y) + 1.5\text{k}\Omega (10\text{mA} - i_y) = 0$

$-1 \times 10^3 i_y + 5000 \times 10^{-3} - 500 i_y + 15 - 1.5 \times 10^3 i_y = 0$

$-3000 i_y = 20$

$i_y = \frac{20}{3000} \text{ A} = \frac{1}{150} \text{ A}$

$V_y = 1 \times 10^3 \left(\frac{1}{150}\right) = 6.66 \text{ V}$, $i_s = 10\text{mA}$



$V_s = -6.66 \text{ V}$

Power provided by the source: $P_s = V_s i_s = (-6.67\text{V})(10 \times 10^{-3}\text{A})$

$P_s = -66.7 \text{ mW}$


2.43)

When the switch is open:

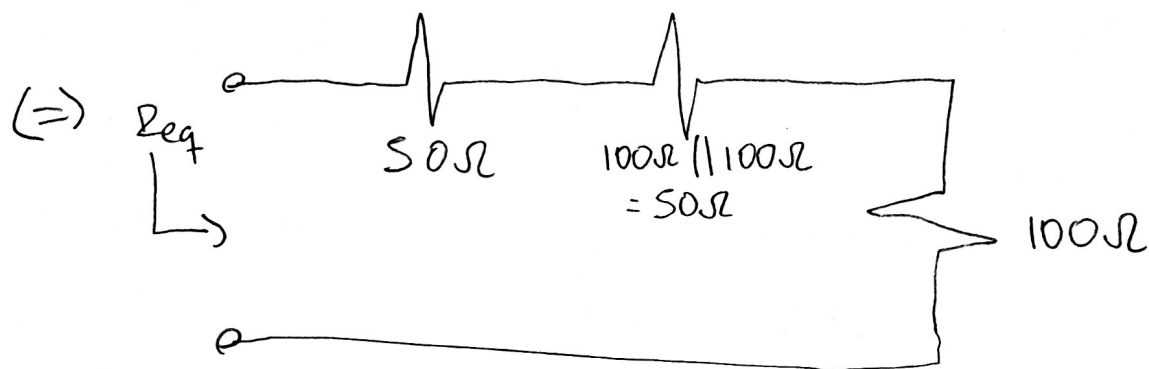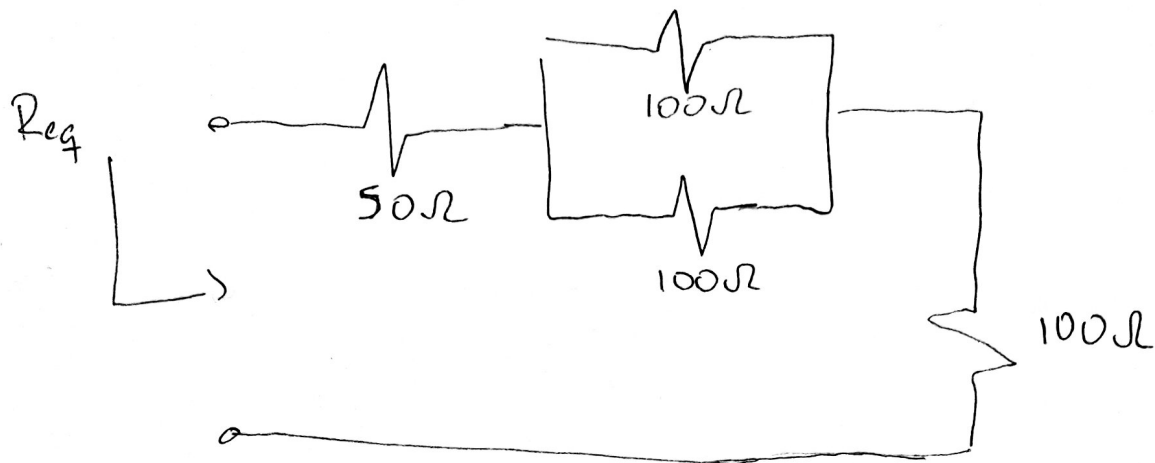


$$R_{eq} = 50\Omega + 50\Omega + 100\Omega = 200\Omega$$

When the switch is closed:

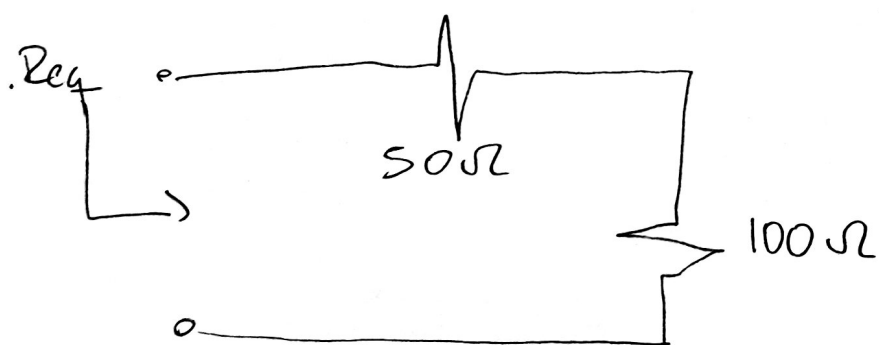

$$R_{eq} = 50\Omega + 100\Omega = 150\Omega$$

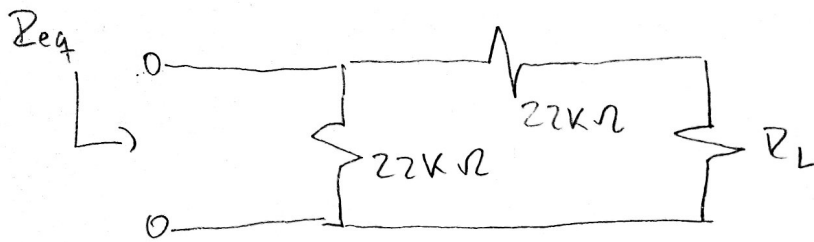2.48) a) When $R_{eq} = 15 \text{ k}\Omega$, Find R_L



$$\begin{aligned}
 R_{eq} &= (22 \text{ k}\Omega + R_L) \parallel 22 \text{ k}\Omega \\
 &= \frac{(22 \text{ k}\Omega + R_L) 22 \text{ k}\Omega}{22 \text{ k}\Omega + R_L + 22 \text{ k}\Omega} \\
 &= \frac{484 \times 10^6 + 22 \times 10^3 R_L}{44 \times 10^3 + R_L} \Omega
 \end{aligned}$$

Since it is given $R_{eq} = 15 \text{ k}\Omega$,

$$(15 \times 10^3)(44 \times 10^3 + R_L) = 484 \times 10^6 + 22 \times 10^3 R_L \quad (1)$$

$$660 \times 10^6 + 15 \times 10^3 R_L = 484 \times 10^6 + 22 \times 10^3 R_L$$

$$7 \times 10^3 R_L = 176 \times 10^6$$

$$R_L = \frac{176}{7} \times 10^3 \Omega$$

$$\boxed{R_L = 25.14 \text{ k}\Omega}$$

b) when $R_{eq} = 11 \text{ k}\Omega$

In (1) we replace 15×10^3 by 11×10^3 , i.e.,


$$(11 \times 10^3)(44 \times 10^3 + R_L) = 484 \times 10^6 + 22 \times 10^3 R_L$$

$$\cancel{484 \times 10^6} + 11 \times 10^3 R_L = \cancel{484 \times 10^6} + 22 \times 10^3 R_L$$


$$\boxed{R_L = 0}$$

2.50)


a)

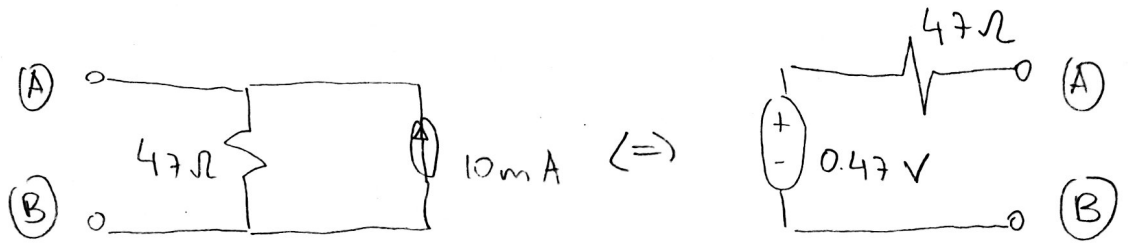

b)

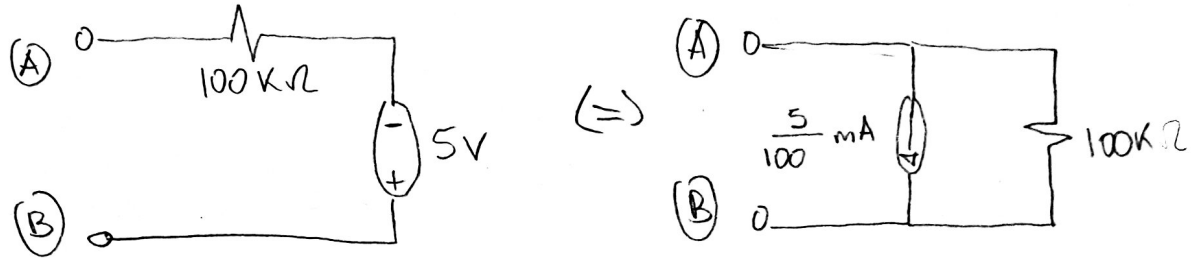

2.59)

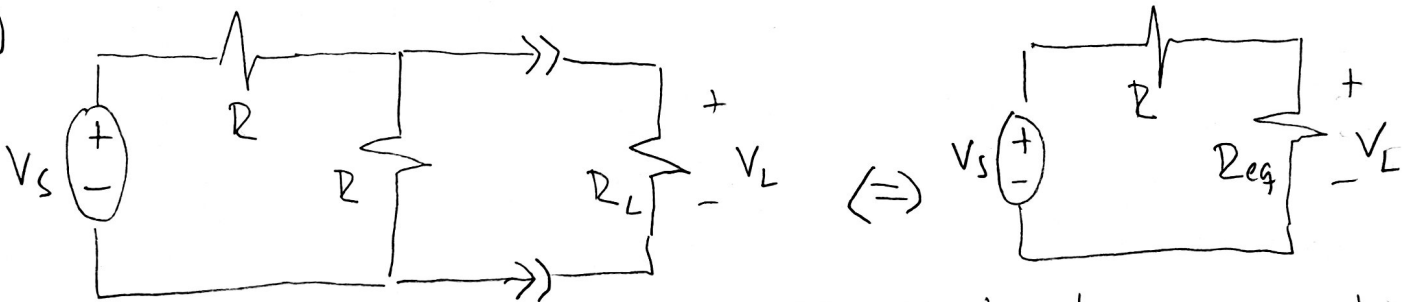


$$R_{eq} = R \parallel R_L = \frac{R R_L}{R + R_L}$$

Note that when we combine R and R_L in parallel, V_L remains unchanged in R_{eq} .

Using voltage division:

$$\begin{aligned} V_L &= \frac{R_{eq}}{R + R_{eq}} V_s \\ &= \frac{\frac{R R_L}{R + R_L}}{R + \frac{R R_L}{R + R_L}} V_s \\ &= \frac{R R_L}{R(R + R_L) + R R_L} V_s \\ &= \frac{R_L}{R + 2R_L} V_s \end{aligned}$$

2.60)

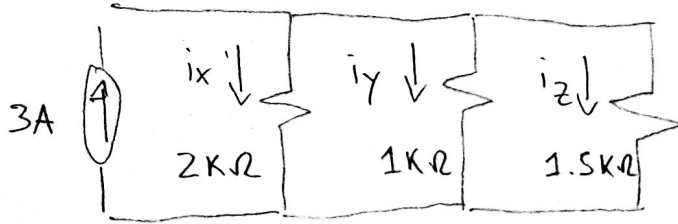


Using current division:

$$i_x = \frac{\frac{1}{2k\Omega}}{\left(\frac{1}{2k\Omega} + \frac{1}{1k\Omega} + \frac{1}{1.5k\Omega}\right)} (3A) = \frac{\frac{1}{2} \times 3A}{\frac{13}{6}} = \frac{3}{13} \times 3A = \frac{9}{13} A = 0.69 A$$

$$i_y = \frac{\frac{1}{1k\Omega}}{\frac{1}{2k\Omega} + \frac{1}{1k\Omega} + \frac{1}{1.5k\Omega}} (3A) = \frac{\frac{1}{13} \times 3A}{\frac{13}{6}} = \frac{18}{13} A = 1.38 A$$

$$i_z = \frac{\frac{1}{1.5k\Omega}}{\frac{1}{2k\Omega} + \frac{1}{1k\Omega} + \frac{1}{1.5k\Omega}} (3A) = \frac{\frac{1}{1.5} \times 3A}{\frac{13}{6}} = \frac{12}{13} A = 0.92 A$$

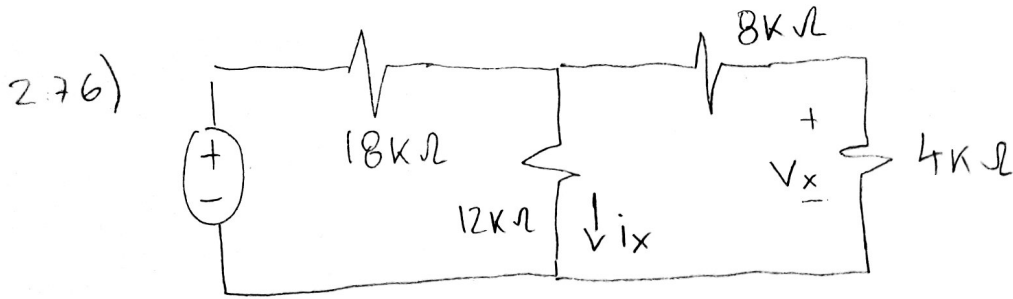Sum of the currents: $i_x + i_y + i_z = \frac{9}{13} A + \frac{18}{13} A + \frac{12}{13} A = 3A$



First we find i_x . For that we apply source transformation

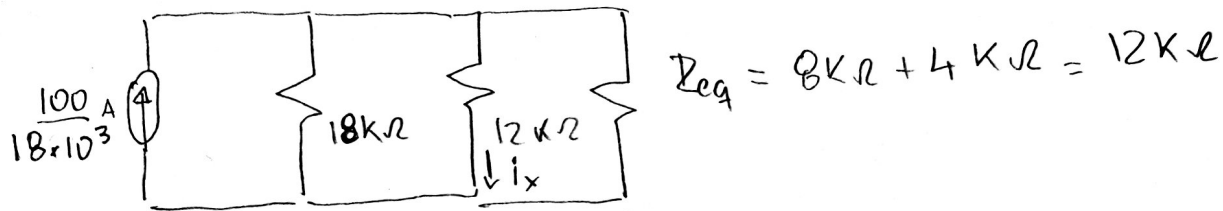



Fig 1

using current division:

$$i_x = \frac{\frac{1}{12}}{\frac{1}{18} + \frac{1}{12} + \frac{1}{12}} \cdot \frac{100}{18} \text{ mA} = \frac{\frac{1}{12}}{\frac{2+3+3}{36}} \cdot \frac{100}{18} \text{ mA}$$

$$= \frac{3}{8} \cdot \frac{100}{18} \text{ mA} = 2.08 \text{ mA}$$

Next, we find V_x . From Fig 1 we have:

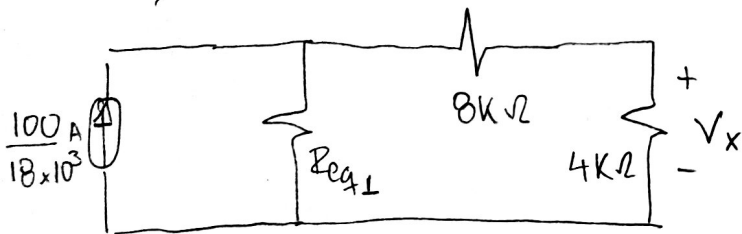


$$R_{eq1} = 18 \text{ k}\Omega \parallel 12 \text{ k}\Omega$$

$$= 7.2 \text{ k}\Omega$$

We apply source transformation:
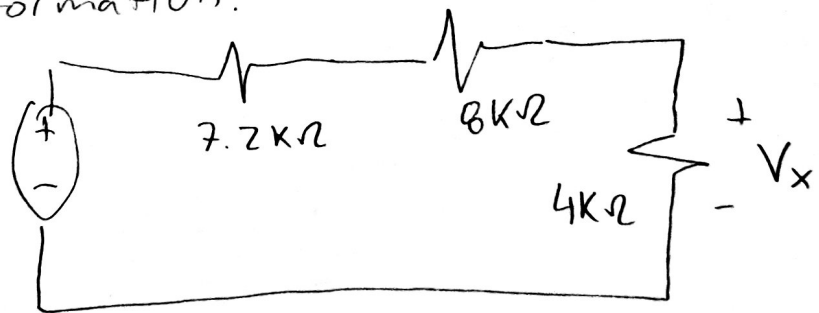
$$\frac{100}{18 \times 10^3} \cdot 7.2 \times 10^3 \text{ V} = 40 \text{ V}$$



Using voltage division: $V_x = \frac{4}{19.2} \times 40 \text{ V} = 8.33 \text{ V}$

2.7B)

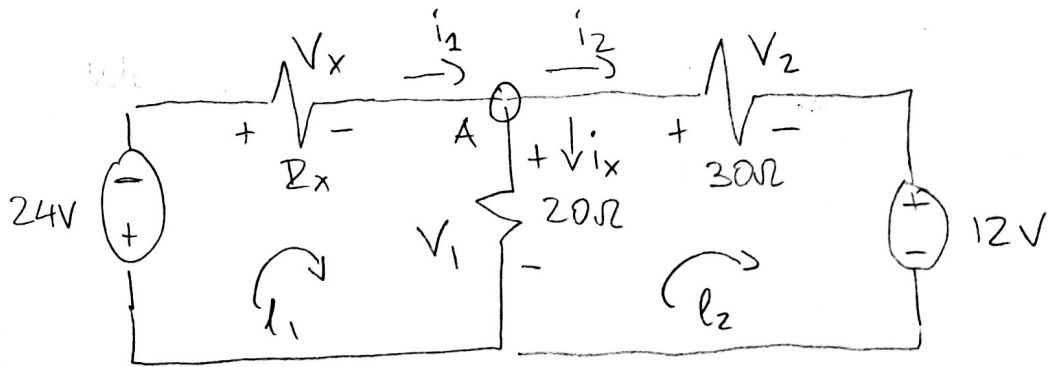


Fig 1

KVL: $l_1: 24 + V_x + V_1 = 0$

$l_2: -V_1 + V_2 + 12V = 0$

Element constraints: $V_1 = 20\Omega i_x = 0$

(Recall that the problem gives $i_x = 0$)

$V_2 = 30\Omega i_2$ (1)

KCL: Node A: $i_1 - i_2 - i_x = 0$

$i_1 = i_2$ (since $i_x = 0$)

Using (1), we have $V_x = -24V$ (2)

Using (2), we have $V_2 = V_1 - 12V = -12V$


From (1): $V_2 = 30\Omega i_2 = -12V \Rightarrow i_2 = \frac{-12V}{30} = -\frac{2}{5}A$

$V_x = R_x i_1 = R_x i_2 = R_x \left(-\frac{2}{5}A\right) \Rightarrow$ Using (2): $-24V = -\frac{2}{5}R_x$

$R_x = 60\Omega$

Another way to do it:

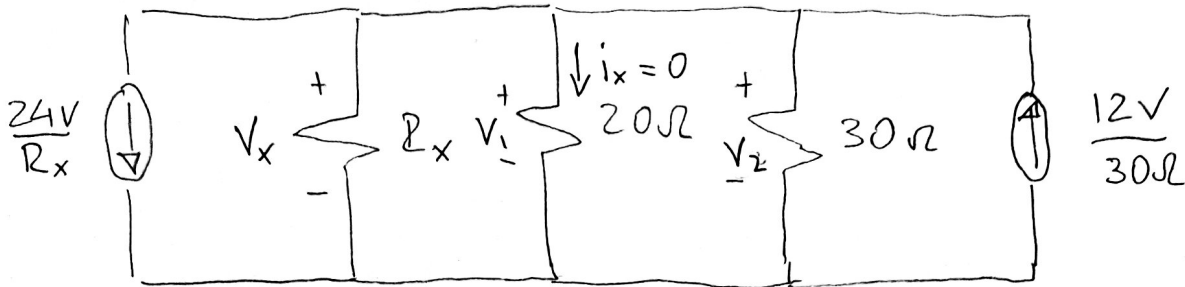We use source transformation to the circuit in P2-78



$$V_x = V_1 = V_2 \quad (\text{since all resistors are in parallel})$$

$$V_1 = 20\Omega i_x = (20)(0)V = 0V \Rightarrow V_x = 0, V_2 = 0$$

Since there is not voltage drop in any resistor, then there is not current flowing through the resistors.

It follows:

$$\underbrace{\frac{24V}{R_x}}_{\text{current source 1}} = \underbrace{\frac{12V}{30\Omega}}_{\text{current source 2}}$$

$$R_x = \frac{(24)(30)}{12} = 60\Omega$$