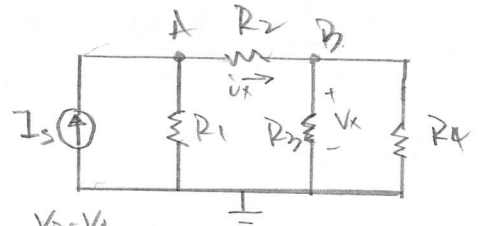


HW3 Solution


2.2

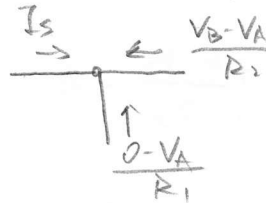a) Note: Assume all current flows into



$$A: I_s + \frac{0 - V_A}{R_1} + \frac{V_B - V_A}{R_2} = 0$$

$$B: \frac{V_A - V_B}{R_2} + \frac{0 - V_B}{R_3} + \frac{0 - V_B}{R_4} = 0$$



Rearrange into matrix form:

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} I_s \\ 0 \end{pmatrix}$$

* You could directly jump into matrix form and receive full credit.

$$b) V_A = \frac{I_s}{\frac{1}{R_1} + \frac{1}{R_2} - \frac{1}{R_2^2}} = \frac{R_1 R_2 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3}{R_3 R_4 + R_2 R_4 + R_2 R_3 + R_1 R_4 + R_1 R_3} I_s$$

$$\text{or} = \frac{I_s}{G_1 + G_2 - \frac{G_2^2}{G_3 + G_4}} = \frac{G_3 + G_4}{G_1 G_2 + G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4} I_s$$

$$V_B = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} - \frac{1}{R_2^2}} I_s = \frac{R_1 R_3 R_4}{R_3 R_4 + R_2 R_4 + R_2 R_3 + R_1 R_4 + R_1 R_3} I_s$$

$$\text{or} = \frac{\frac{G_2}{G_3 + G_4}}{G_1 + G_2 - \frac{G_2^2}{G_3 + G_4}} I_s = \frac{G_2}{G_1 G_2 + G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4} I_s$$

c) $V_x = V_B$ \nearrow

$$i_x = \frac{V_A - V_B}{R_2} = \frac{R_1 R_4 + R_1 R_3}{R_3 R_4 + R_2 R_4 + R_2 R_3 + R_1 R_4 + R_1 R_3} I_s \quad \text{or} \quad \frac{G_3 G_3 + G_2 G_4}{G_1 G_2 + G_1 G_3 + G_1 G_4 + G_2 G_3 + G_2 G_4} I_s$$


3.6 KCL:

assume current flows
into node $\rightarrow \sum_{k=1}^n i_k = 0$

$$a) A: i_s + \frac{V_B - V_A}{R_4} + \frac{V_C - V_A}{R_3} = 0$$

$$B: \frac{V_A - V_B}{R_4} + \frac{0 - V_B}{R_1} + \frac{V_C - V_B}{R_2} = 0$$
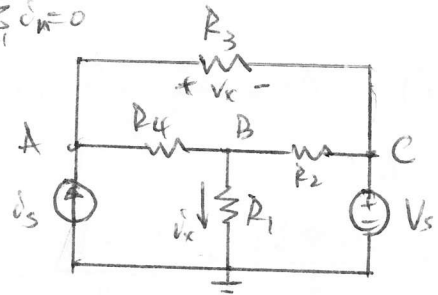
$$C: V_C = V_s \quad (\text{because of the way we choose ground} \rightarrow \text{Method 2 in Lecture slide})$$



rearrange:

$$\begin{bmatrix} \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} & -\frac{1}{R_3} \\ -\frac{1}{R_4} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} & -\frac{1}{R_2} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ V_C \end{pmatrix} = \begin{pmatrix} i_s \\ 0 \\ 0 \end{pmatrix} \quad w/ \quad V_C = V_s.$$

$$b) V_x = V_A - V_C, \quad i_x = \frac{V_B - 0}{R_1} = \frac{V_B}{R_1}$$

$$\text{plug in } R_1 = R_2 = R_3 = R_4 = 5 \text{ k}\Omega, \quad V_s = 12 \text{ V}, \quad i_s = 2 \text{ mA}$$

$$\begin{bmatrix} \frac{2}{5} & -\frac{1}{5} & -\frac{1}{5} \\ -\frac{1}{5} & \frac{3}{5} & -\frac{1}{5} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ 12 \end{pmatrix} = \begin{pmatrix} 2 \\ 0 \end{pmatrix} \Rightarrow \text{solve for: } V_A = 15.6 \text{ V} \quad V_B = 9.2 \text{ V}$$

$$\Rightarrow V_x = 3.6 \text{ V} \quad i_x = 1.84 \text{ mA}$$


3.7.

1st eqn: ~~node A~~ only V_s btw node A & ground.

2nd eqn: R_1 is btw A and B, R_2 is btw B & C, i_s flow into node B.

3rd eqn: R_3 is btw A & C, R_4 is btw C & ground.

4th eqn: D is grounded

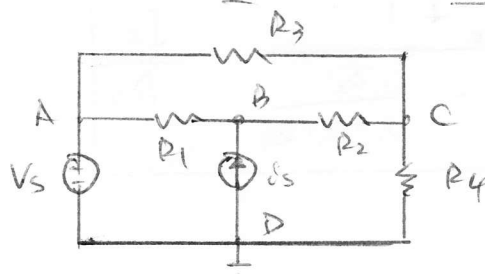


3.11.

$$a) A: \frac{V_D - V_A}{R_x} + \frac{V_B - V_A}{R_1} + \frac{0 - V_A}{R_2} = 0$$

$$B: V_B = V_S$$

$$D: \frac{V_A - V_D}{R_x} + \frac{V_B - V_D}{R_3} + \frac{0 - V_D}{R_4} = 0$$
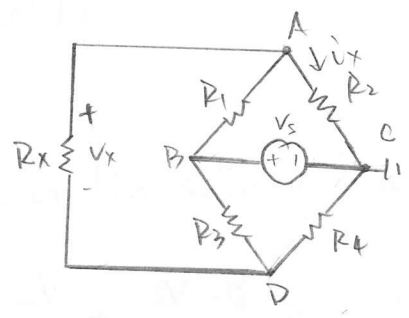
$$\Rightarrow \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x} & -\frac{1}{R_1} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & -\frac{1}{R_3} & \frac{1}{R_x} + \frac{1}{R_3} + \frac{1}{R_4} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ V_D \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \end{pmatrix}$$



b) plug in values and solve for V_A & V_D :

$$\begin{bmatrix} 11.6667 & -1 & -10 \\ -10 & -2 & 12.5 \end{bmatrix} \begin{pmatrix} V_A \\ V_B \\ V_D \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \end{pmatrix} \Rightarrow V_A = 10.6364 \text{ V} \quad V_D = 10.9091 \text{ V}$$

$$i_x = \frac{V_A}{R_2} = \boxed{7.0909 \text{ mA}} \quad V_x = V_A - V_D = \boxed{-0.2727 \text{ V}}$$

3.12

choosing bottom node as ground $\Rightarrow V_A = -15 \text{ V}$

form supernode between B and C, assume

all current flows into supernode.


$$i_1 + i_2 + i_3 + i_4 = 0 \Rightarrow \frac{V_A - V_B}{1 \text{ k}\Omega} + \frac{0 - V_B}{1.5 \text{ k}\Omega} + \frac{0 - V_C}{2 \text{ k}\Omega} + \frac{V_A - V_C}{1 \text{ k}\Omega} = 0 \quad (2)$$

2 equations, 2 unknowns, $V_B, V_C \Rightarrow$ solve for: $V_B = -7.1053 \text{ V} \quad V_C = -12.1053 \text{ V}$.

$$V_x = V_C = \boxed{-12.1053 \text{ V}} \quad i_x = \frac{V_C - V_A}{1 \text{ k}\Omega} = \boxed{-2.8947 \text{ mA}}$$

rearrange (1), (2):

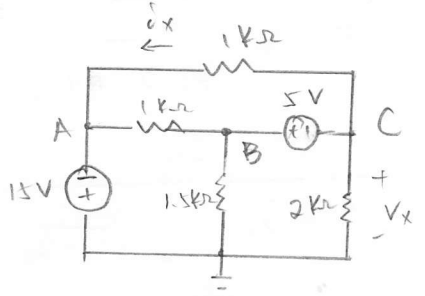
$$\begin{bmatrix} 1 & -1 \\ 1.6667 & 1.5 \end{bmatrix} \begin{pmatrix} V_B \\ V_C \end{pmatrix} = \begin{pmatrix} 5 \\ \frac{2V_A}{1 \text{ k}\Omega} \end{pmatrix}$$



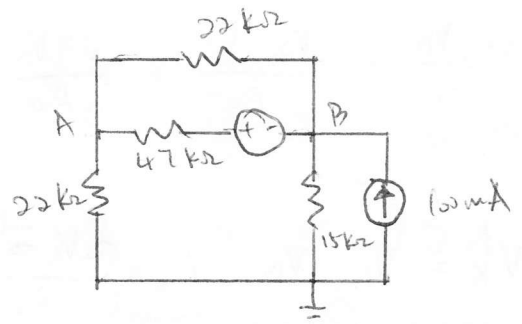3.26.

$$b) A: \frac{0 - V_A}{20k\Omega} + \frac{V_B - V_A}{20k\Omega} + \frac{V_B + 50V - V_A}{47k\Omega} = 0$$

$$B: \frac{0 - V_B}{15k\Omega} + 100\text{mA} + \frac{V_A - V_B}{20k\Omega} + \frac{V_A - 50V - V_B}{47k\Omega} = 0$$



$$\begin{bmatrix} \frac{1}{20k\Omega} + \frac{1}{47k\Omega} + \frac{1}{20k\Omega} & -\frac{1}{47k\Omega} - \frac{1}{20k\Omega} \\ -\frac{1}{47k\Omega} - \frac{1}{20k\Omega} & \frac{1}{20k\Omega} + \frac{1}{15k\Omega} + \frac{1}{47k\Omega} \end{bmatrix} \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} \frac{50V}{47k\Omega} \\ -\frac{50V}{47k\Omega} + 100\text{mA} \end{pmatrix} \Rightarrow \begin{pmatrix} V_A \\ V_B \end{pmatrix} = \begin{pmatrix} 641.5\text{ V} \\ 1062.6\text{ V} \end{pmatrix}$$


3.27 e

$$c) A: \boxed{V_A = 24\text{ V}}$$

$$B: V_B - V_A = 50\text{ V} \Rightarrow \boxed{V_B = 74\text{ V}}$$

$$C: \frac{V_B - V_C}{20k\Omega} + \frac{V_D - V_C}{33k\Omega} + \frac{0 - V_C}{81k\Omega} = 0$$

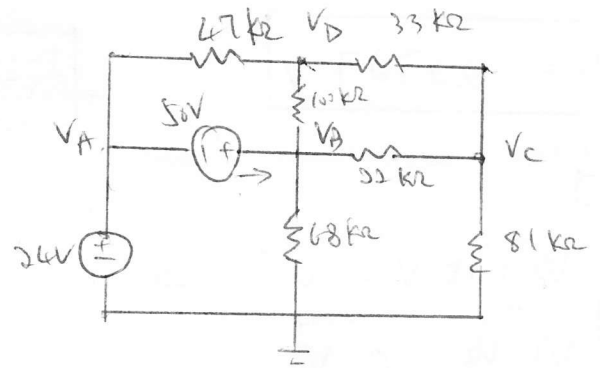
$$D: \frac{V_A - V_D}{47k\Omega} + \frac{V_B - V_D}{100k\Omega} + \frac{V_C - V_D}{33k\Omega} = 0$$




$$\Rightarrow \begin{bmatrix} \frac{1}{55k\Omega} + \frac{1}{33k\Omega} + \frac{1}{81k\Omega} & -\frac{1}{33k\Omega} \\ -\frac{1}{33k\Omega} & \frac{1}{47k\Omega} + \frac{1}{100k\Omega} + \frac{1}{33k\Omega} \end{bmatrix} \begin{pmatrix} V_C \\ V_D \end{pmatrix} = \begin{pmatrix} \frac{V_B}{20k\Omega} \\ \frac{V_B}{100k\Omega} + \frac{V_A}{47k\Omega} \end{pmatrix} \Rightarrow \begin{pmatrix} V_C = 54.3653\text{ V} \\ V_D = 47.0622\text{ V} \end{pmatrix}$$

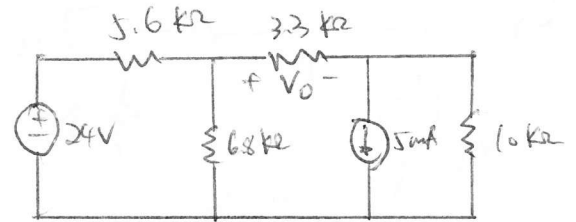3.42

Turn off current source $\rightarrow V_{01}$




and use source transformation:

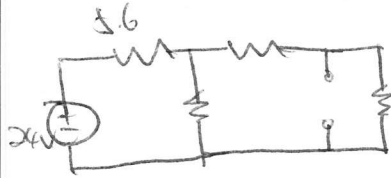


$$J_1 = \frac{\frac{1}{13.3k}}{\frac{1}{13.3k} + \frac{1}{5.6k} + \frac{1}{6.8k}} \cdot \frac{24}{5.6k} = 0.8039 \text{ mA}$$

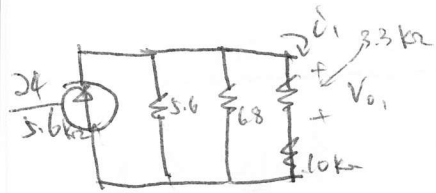
$$V_{01} = J_1 \cdot 3.3k = \boxed{2.653 \text{ V}}$$



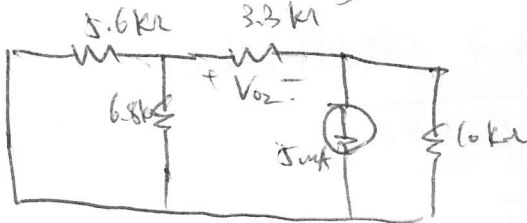Turn off voltage source & open current source $\rightarrow V_{02}$






Source transform

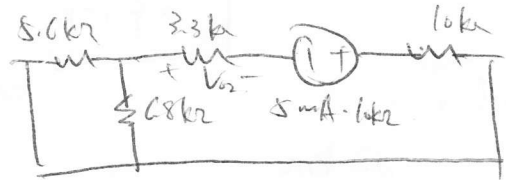


$$V_{02} = \frac{3.3k}{3.3k + 10k + 5.6k \parallel 6.8k} \cdot (50 \text{ V}) = \boxed{2.078 \text{ V}}$$

$$V_0 = V_{01} + V_{02} = \boxed{12.732 \text{ V}}$$

3.54

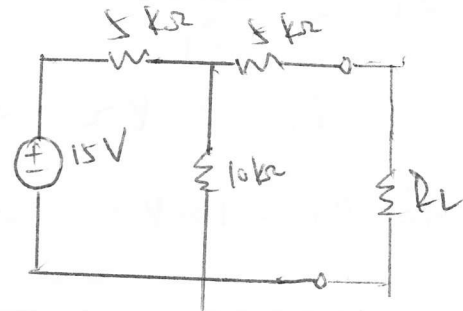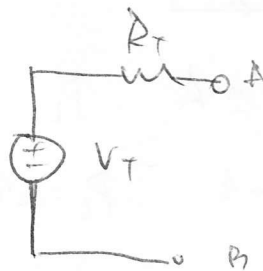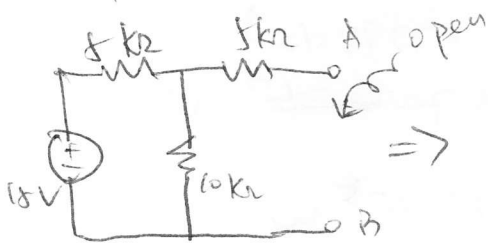

Zero out source \rightarrow

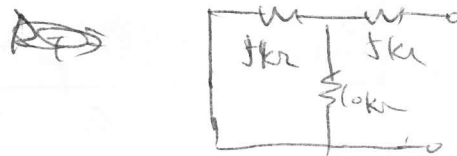


$$R_T = 5k + 5k \parallel 10k = \boxed{8.333 \text{ k}\Omega}$$

using voltage divider:




$$V_T = \frac{10k}{5k + 10k} \cdot 15 \text{ V} = \boxed{10 \text{ V}}$$

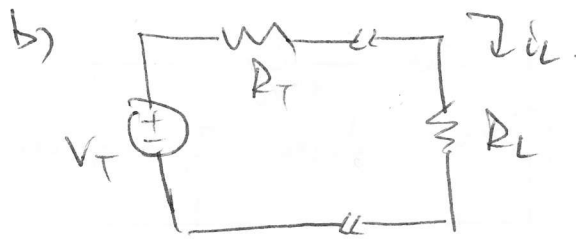* Note: 5k on the right sees no current because of open connection btw A, B.




$$I_L = \frac{V_T}{R_T + R_L} = \frac{10V}{8.333k\Omega + 1k\Omega}$$

$$= \boxed{0.4286 \text{ mA}}$$

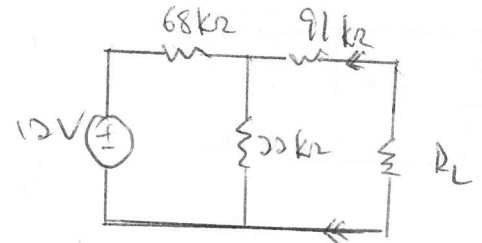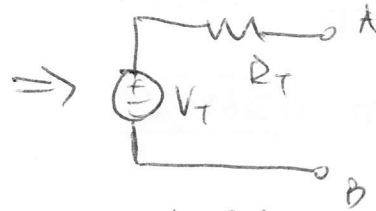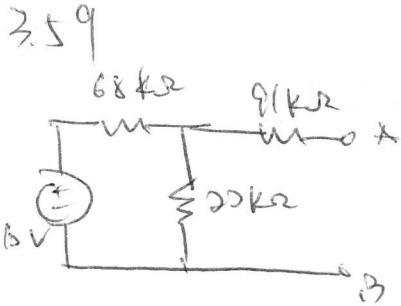

zero out source \rightarrow

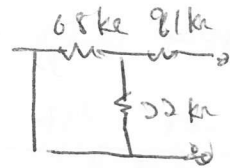

$$R_T = 91k\Omega + 68k\Omega \parallel 22k\Omega$$


$$= \boxed{107.622 \text{ k}\Omega}$$

voltage divider =

$$V_T = \frac{22k\Omega}{22k\Omega + 68k\Omega} (12V) = \boxed{2.9333 \text{ V}}$$

$$P_L = VI = I_L^2 R_L$$

$$I_L = \frac{V_T}{R_T + R_L}$$

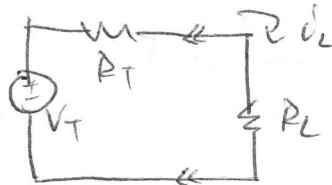

for $R_L = 50k\Omega \rightarrow I_L = 0.0186 \text{ mA} \cdot P_L = 1.7298 \times 10^{-8} \text{ W}$

for $R_L = 100k\Omega \rightarrow I_L = 0.0141 \text{ mA} \cdot P_L = 1.9961 \times 10^{-8} \text{ W}$

$$\boxed{P_{50k\Omega} = 17.298 \mu\text{W}}$$

$$\boxed{P_{100k\Omega} = 19.961 \mu\text{W}}$$

* Note: when computing V_T , $91k\Omega$ resistor sees not current because open connection btw A & B.