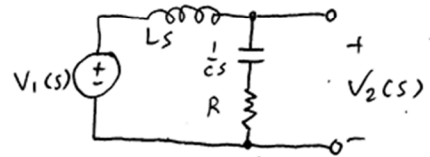


Homework 8 Solution

1/6

11-4 a) Find driving point impedance seen by the Volt. source, find $T_V(s) = V_2(s)/V_1(s)$


$$Z_{dp}(s) = Ls + \frac{1}{Cs} + R = \frac{1 + RCs + LCs^2}{Cs}$$



Voltage divider

$$\rightarrow V_2(s) = \frac{\frac{1}{Cs} + R}{Z_{dp}(s)} \cdot V_1(s) = \frac{1 + RCs}{1 + RCs + LCs^2} \cdot V_1(s)$$
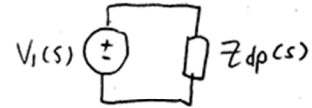
$$\rightarrow T_V(s) = \frac{1 + RCs}{1 + RCs + LCs^2}$$



b) Select R, C, L such that the poles are $s = -9998 \text{ rad/s}$, $s = -101 \text{ rad/s}$. What's the zero?

So, we want $\frac{1}{LC}(1 + RCs + LCs^2) = (s + 9998)(s + 101)$

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = s^2 + 9999s + 999698$$

Using $L = 1 \text{ H} \rightarrow R = 9999 \Omega$
 $C = 1.0003 \mu\text{F}$

with zeros of:

$$\frac{1}{LC}(1 + RCs) \Rightarrow s = -\frac{1}{RC}, s = \infty$$

zeros = $\{-99.98, \infty\}$


11-8 a) Find DP Impedance seen by $V_1(s)$, find $T_V(s) = V_1(s)/V_2(s)$!

This is an inverting OP Amp configuration.

Input impedance $\rightarrow Z_1(s) = \left(\frac{1}{R_1} + Cs\right)^{-1} = \frac{R_1}{1 + R_1Cs}$

Feedback impedance $\rightarrow Z_2(s) = \left(\frac{1}{R_2} + C_2s\right)^{-1} = \frac{R_2}{1 + R_2C_2s}$
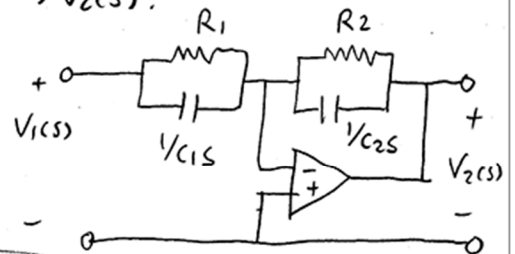
$$V_2(s) = -\frac{Z_2}{Z_1} V_1(s) \rightarrow T_V(s) = -\frac{R_2}{R_1} \frac{1 + R_1Cs}{1 + R_2C_2s}$$



b) Select R_1, R_2, C_1, C_2 s.t. there is a pole at $s = -10000 \text{ rad/s}$ and zero at $s = -5000 \text{ rad/s}$ and input impedance at DC is $2 \text{ k}\Omega$.


DC input impedance $\rightarrow Z_1(s) \Big|_{s=0} = \frac{R_1}{1} = 2 \text{ k}\Omega \rightarrow \boxed{R_1 = 2 \text{ k}\Omega}$

zero $\rightarrow 1 + R_1 C_1 s = 0 \rightarrow s = \frac{-1}{R_1 C_1} = -5000 \rightarrow \boxed{C_1 = 100 \text{ nF}}$

pole $\rightarrow 1 + R_2 C_2 s = 0 \rightarrow s = \frac{-1}{R_2 C_2} = -10000 \rightarrow \boxed{R_2 = 2 \text{ k}\Omega}$
 $\boxed{C_2 = 50 \text{ nF}}$

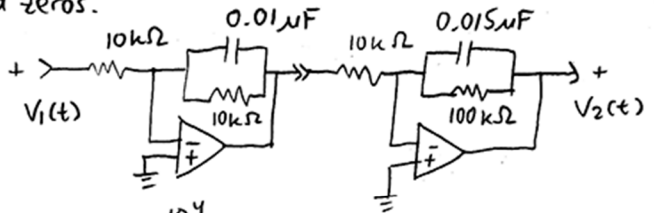11-14 Find $T_V(s) = V_2(s)/V_1(s)$. Locate poles and zeros.

Cascade of 2 inverting OP Amps (non-loading)



First OP Amp's gain

$$G_1(s) = \frac{-\left(\frac{1}{10 \text{ k}\Omega} + 0.01 \mu\text{F} \cdot s\right)^{-1}}{10 \text{ k}\Omega} = \frac{-1}{1 + 10^{-4} s} = \frac{-10^4}{s + 10^4}$$


$$G_2(s) = \frac{-\left(\frac{1}{100 \text{ k}\Omega} + 0.015 \mu\text{F} \cdot s\right)^{-1}}{10 \text{ k}\Omega} = \frac{-10}{1 + 0.0015 s} = \frac{-6666.7}{s + 666.67}$$

$$T_V(s) = G_1(s) \cdot G_2(s) = \frac{-6.67 \cdot 10^7}{(s + 1000)(s + 666.7)} \rightarrow \boxed{\begin{matrix} \text{poles} = \{-1000, -666.7\} \\ \text{zeros} = \{\infty, \infty\} \end{matrix}}$$

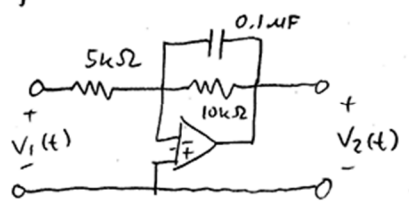11-36 Steady state $V_1(t) = 5 \cos(500t) \text{ V}$. Find $V_{2ss}(t)$. Repeat for $V_1(t) = 5 \cos(1 \text{ kt}) \text{ V}$ and $V_1(t) = 5 \cos(10 \text{ kt}) \text{ V}$. Where is the pole?

Inverting OP Amp.

$$T_V(s) = \frac{V_2(s)}{V_1(s)} = -\frac{\left(\frac{1}{10 \text{ k}\Omega} + 0.1 \mu\text{F} \cdot s\right)^{-1}}{5 \text{ k}\Omega} = \frac{-2}{1 + 0.001 s} = \frac{-2000}{s + 1000}$$



For sinusoidal input $V_1(t) = A \cos(\omega t)$, the steady state output $V_{2ss}(t)$ is:

$$V_{2ss}(t) = A \cdot |T_V(j\omega)| \cdot \cos(\omega t + \angle T_V(j\omega))$$

$T_V(j\omega)$ is a complex number,

$$V_1(t) = 5 \cdot \cos(500t) \rightarrow T_V(j500) = \frac{-2000}{500j + 1000} = \frac{-2000(1000 - 500j)}{1000^2 + 500^2} = \underline{\underline{-1.6 + j0.8}}$$

$$\hookrightarrow V_{2ss}(t) = 5 \cdot |-1.6 + j0.8| \cos(500t + \angle(-1.6 + j0.8)) = \underline{\underline{5 \cdot \sqrt{3.2} \cos(500t + 2.68)}}$$

$$V_1(t) = 5 \cdot \cos(1kt) \rightarrow T_V(1000j) = -1 + j \rightarrow |T_V(1000j)| = \sqrt{2}, \angle T_V(1000j) = \frac{3}{4}\pi$$

$$\hookrightarrow V_{2ss}(t) = \underline{\underline{5 \cdot \sqrt{2} \cos(1000t + \frac{3}{4}\pi)}}$$

$$V_1(t) = 5 \cdot \cos(10kt) \rightarrow T_V(10kj) = -0.0198 + j0.198 \rightarrow |T_V(10kj)| = 0.199$$

$$\angle T_V(10kj) = 1.67$$


$$\hookrightarrow V_{2ss}(t) = \underline{\underline{5 \cdot 0.199 \cos(10kt + 1.67)}}$$

The pole $\Rightarrow s = -1000 \text{ rad/s}$

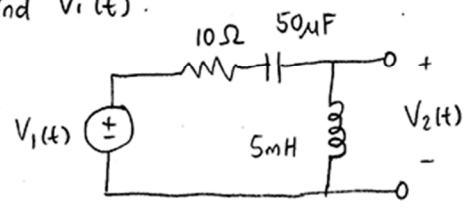11-38 If we have $V_{2ss}(t) = 25.5 \cos(10kt + 11.8^\circ)$, find $V_1(t)$.

Voltage divider: $\frac{V_2(s)}{V_1(s)} = \frac{0.005 \cdot s}{10\Omega + \frac{1}{50 \cdot 10^{-6} s} + 0.005 s}$

$$T_V(s) = \frac{s^2}{s^2 + 2000s + 4 \cdot 10^6}$$



Then we have

$$T_V(10kj) = \frac{(10000j)^2}{(10000j)^2 + 2000(1000j) + 4 \cdot 10^6} = 0.9983 + 0.208j$$


$$\hookrightarrow |T_V(10kj)| = 1.0198 \quad \angle T_V(10kj) = 11.8^\circ$$

So, $V_1(t) = \frac{25.5}{1.0198} \cos(10kt + 11.8^\circ - 11.8^\circ) \rightarrow \underline{\underline{V_1(t) = 25 \cos(10kt)}}$


12-4 Find $T_V(s) = V_2(s) / V_1(s)$.

$$T_V(s) = \frac{100}{0.1s + 100 + 100} = \underline{\underline{\frac{1000}{s + 2000}}}$$

using Voltage divider

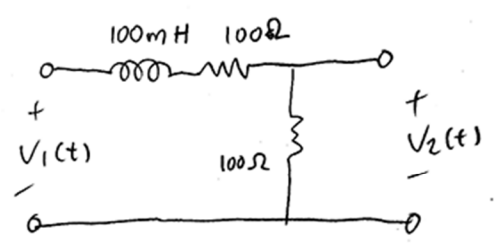

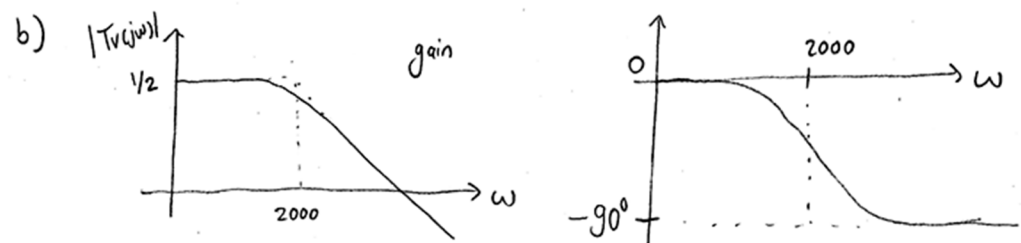a) DC gain = $\lim_{s \rightarrow 0} T_v(s) = \frac{1}{2}$
 ∞ freq. gain = $\lim_{s \rightarrow \infty} T_v(s) = 0$
 cutoff freq. = 2000 rad/s } This is a lowpass filter.




c) Gain at $w = 0.1 w_c$, $w = w_c$, $w = 10 w_c$. $w_c = 2000$ rad/s.

↳ $|T_v(200j)| = \left| \frac{1000}{200j + 2000} \right| = 0.4975$
 $|T_v(2000j)| = \left| \frac{1000}{2000j + 2000} \right| = 0.3536$
 $|T_v(20000j)| = \left| \frac{1000}{20000j + 2000} \right| = 0.0498$

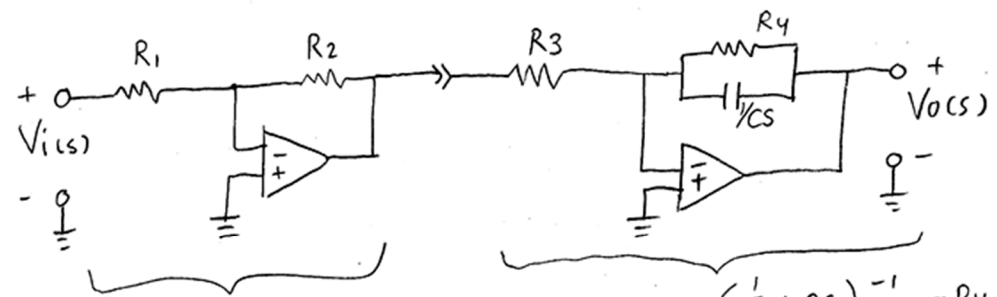12-10 Design a low pass filter with 20 krad/s cutoff freq. and passband gain of 200.

↳ want: $T_v(s) = \frac{200 \cdot 20000}{s + 20000}$

Simplest way is to use 2 inverting OP Amps. with gains of -200 and $\frac{-20000}{s + 20000}$



gain = $-\frac{R_2}{R_1} = -200$

gain = $-\frac{(\frac{1}{R_4} + Cs)^{-1}}{R_3} = -\frac{R_4}{R_3} \frac{1}{1 + R_4Cs}$
 $= -\frac{1}{R_3 C} \cdot \frac{1}{s + 1/R_4 C} = -\frac{20000}{s + 20000}$


We can use:
 $R_2 = 200 \text{ k}\Omega$
 $R_1 = 1 \text{ k}\Omega$

We can use:
 $C = 100 \text{ nF}$
 $R_4 = 500 \Omega$
 $R_3 = 500 \Omega$

12-14 Design a lowpass filter w/ $\omega_c = 100 \text{ Hz}$ and passband gain of 1.
 $\omega_c = 100 \text{ Hz} = 628.3 \text{ rad/s}$

Want: $T_V(s) = \frac{628.3}{s + 628.3}$

We can use this circuit below:

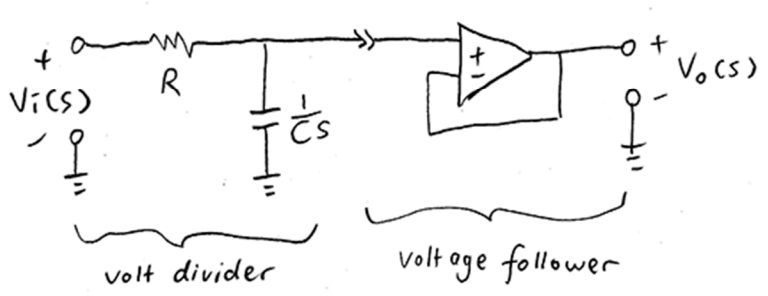



$$\text{gain} = \frac{1/Cs}{R + 1/Cs} = \frac{1}{RCs + 1}$$

$$= \frac{1/RC}{s + 1/RC}$$

Use $C = 1 \mu\text{F}$
 $R = 1592 \Omega$


12-23 $T_V(s) = \frac{50s}{s + 10000}$

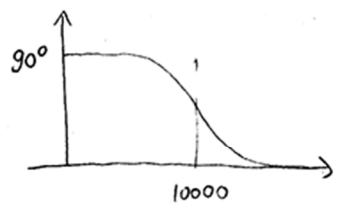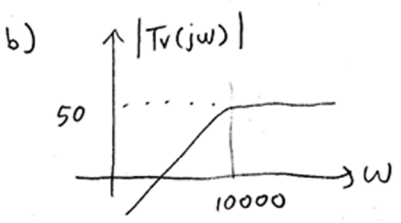a) This is a highpass filter, $\omega_c = 10000 \text{ rad/s}$, passband gain = $\lim_{s \rightarrow \infty} T_V(s) = 50$



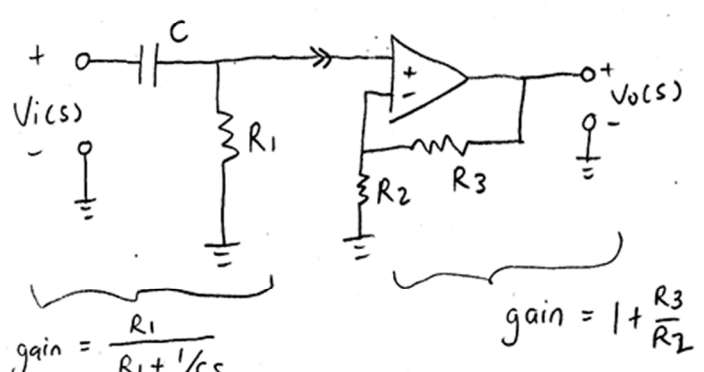c) Design the circuit.

$$T_V(s) = \frac{50s}{s + 10000} = 50 \left(\frac{s}{s + 10000} \right)$$



$$\text{gain} = \frac{R_1}{R_1 + 1/Cs}$$

$$= \frac{R_1 Cs}{1 + R_1 Cs} = \frac{s}{s + 1/R_1 C}$$

$$\text{gain} = 1 + \frac{R_3}{R_2}$$

$$\text{Total gain} = \left(1 + \frac{R_3}{R_2} \right) \left(\frac{s}{s + 1/R_1 C} \right)$$

we can use:

$$C = 1 \mu\text{F}$$

$$R_1 = 100 \Omega$$


$$R_2 = 1 \text{ k}\Omega$$

$$R_3 = 49 \text{ k}\Omega$$

12-32) Bandpass circuit.

Identify the elements that control the 2 cutoff frequencies

↳ C_1, R_2 and C_2, R_3

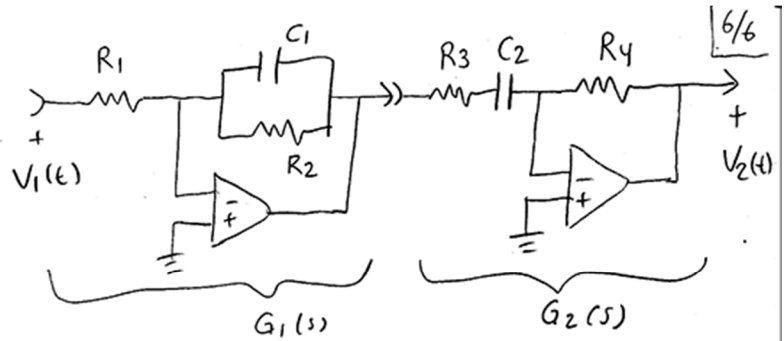

Want: passband gain 100, cutoff frequencies: 1000 rad/s, 40 krad/s

Cascade of 2 inverting OP Amps.

$$G_1(s) = - \frac{(\frac{1}{R_2} + C_1 s)^{-1}}{R_1} = - \frac{R_2}{R_1} \frac{1}{1 + R_2 C_1 s} = - \frac{1/R_1 C_1}{s + 1/R_2 C_1}$$

$$G_2(s) = - \frac{R_4}{R_3 + 1/C_2 s} = - \frac{R_4 C_2 s}{1 + R_3 C_2 s} = - \frac{(R_4/R_3) s}{s + 1/R_3 C_2}$$

Then we have: $T_V(s) = \frac{V_2(s)}{V_1(s)} = G_1(s) \cdot G_2(s) =$

$$T_V(s) = \frac{R_4}{R_1 R_3 C_1} \left(\frac{s}{(s + \frac{1}{R_2 C_1})(s + \frac{1}{R_3 C_2})} \right)$$

Bandpass gain of $\frac{s}{(s+1000)(s+40000)}$ → evaluate around $\sqrt{1000 \cdot 40000} \approx 6300$ rad/s

$$\left| \frac{6300j}{(6300j+1000)(6300j+40000)} \right| = 2.44 \cdot 10^{-5}$$

$$T_V(s) = 4.1 \cdot 10^6 \frac{s}{(s+1000)(s+40000)}$$

So, we want:

$$\frac{1}{R_2 C_1} = 1000 \text{ rad/s}$$

$$\frac{1}{R_3 C_2} = 40000 \text{ rad/s}$$

$$\frac{R_4}{R_1 R_3 C_1} = \frac{100}{2.44 \cdot 10^{-5}}$$

We can use:

$$C_1 = 1 \text{ nF}$$

$$C_2 = 1 \text{ nF}$$

$$R_1 = 10 \text{ k}\Omega$$

$$R_2 = 1 \text{ M}\Omega$$

$$R_3 = 25 \text{ k}\Omega$$

$$R_4 = 1.025 \text{ M}\Omega$$