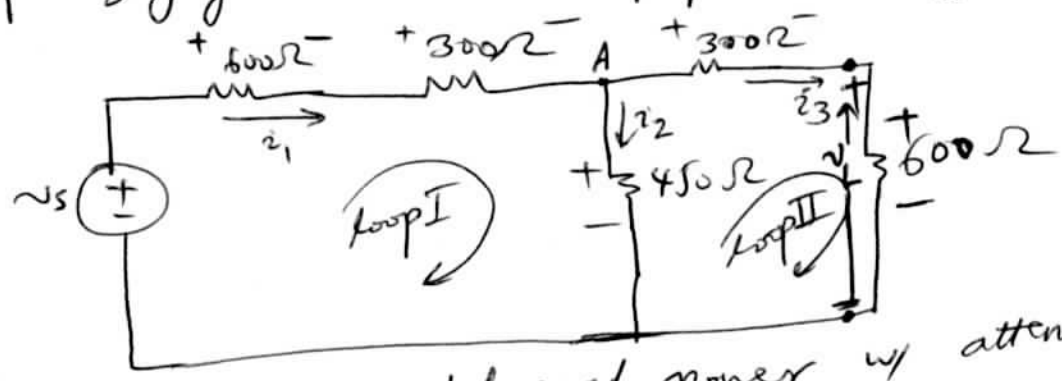


P 3-72:

Topology of the circuit w/ proper labeling:



1st) Compute the delivered power w/ attenuator:

- Kcl at node A:

$$i_1 = i_2 + i_3 \quad (1)$$

- Kvl loop II:

$$300 i_3 + 600 i_3 = 450 i_2 \quad (2.1) \Rightarrow 900 i_3 = 450 i_2 \Rightarrow 2 i_3 = i_2 \quad (2.2)$$

- Kvl loop I:

$$v_s = 600 i_1 + 300 i_1 + 450 i_2 \quad (3)$$

Equations (1) & (2.2) yield:

$$i_1 = i_2 + i_3 \xrightarrow{(2.2)} i_1 = i_3 + 2 i_3 \Rightarrow i_1 = 3 i_3 \quad (4)$$

Derive i_3 in terms of v_s based on the equations (2.2), (4) & (3):

$$v_s = 600 (3 i_3) + 300 (3 i_3) + 450 (2 i_3) \Rightarrow v_s = 3600 i_3$$

$$\Downarrow$$

$$i_3 = \frac{1}{3600} v_s \quad (5)$$


Then, derive v_L i.e., the voltage drop across the load based on equation (5):

$$v_L = 600 \cdot i_3 = 600 \cdot \frac{1}{3600} v_s \Rightarrow v_L = \frac{1}{6} v_s \quad (6)$$

Hence, the power delivered at the load side:

$$P_L = v_L i_L = \frac{1}{6} v_s \cdot \frac{1}{3600} v_s \Rightarrow P_L = \frac{1}{21600} v_s^2 \quad (7)$$

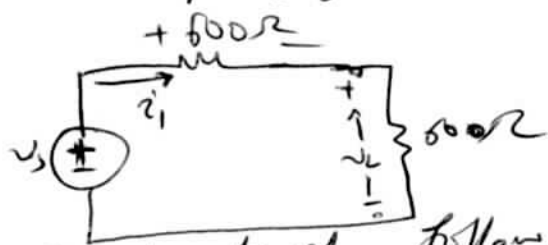2nd) Compute the delivered power w/o attenuator:
 The considered topology will be thus:



It is easy to check the following:

$$v_s = 600 i_1 + 600 i_1 \Rightarrow v_s = 1200 i_1 \Rightarrow \boxed{i_1 = \frac{1}{1200} v_s} \quad (8)$$

$$\therefore v_L = v_s - 600 i_1 = v_s - \frac{600}{1200} v_s \Rightarrow \boxed{v_L = \frac{v_s}{2}} \quad (9)$$

Denote P'_L = the power delivered at the load side w/o attenuator:

$$\text{Equations (8), (9)} \Rightarrow P'_L = \frac{1}{1200} v_s \cdot \frac{v_s}{2} \Rightarrow \boxed{P'_L = \frac{1}{2400} v_s^2} \quad (10)$$

3rd) Having developed equations (7) & (10), we compute the fraction of delivered power in these cases as follows:

(Let f_p be the ^{desired} fraction)

$$f_p = \frac{P_L}{P'_L} = \frac{\frac{1}{21600} v_s^2}{\frac{1}{2400} v_s^2} = 1.11 \times 10^{-2} = \frac{1}{9}$$

Therefore:

$$f_{p, dB} = 10 \log_{10} f_p = 10 \log_{10} (1.11 \times 10^{-2}) \Rightarrow \boxed{f_{p, dB} = -9.54 \text{ dB}}$$

Requirements: $\begin{cases} V_{oc} = 36V \\ R_T \leq 10\Omega \end{cases}$

1st type of cells: $\begin{cases} V_{oc1} = 9V \\ R_{T1} = 4\Omega \\ m_1 = 40g \end{cases}$

2nd type of cells: $\begin{cases} V_{oc2} = 4V \\ R_{T2} = 0.5\Omega \\ m_2 = 15g \end{cases}$


we are allowed to use EITHER 1st type OR 2nd type:

- using 1st type of cells:

Design I: to put 4 of these cells in series $\Rightarrow \begin{cases} V_{oc} = 4 \times 9 = 36V \checkmark \\ R_T = 4 \times R_{T1} = 16 \gg 10\Omega \end{cases}$

this design is NOT desirable, because $R_T = 16 \gg 10\Omega$

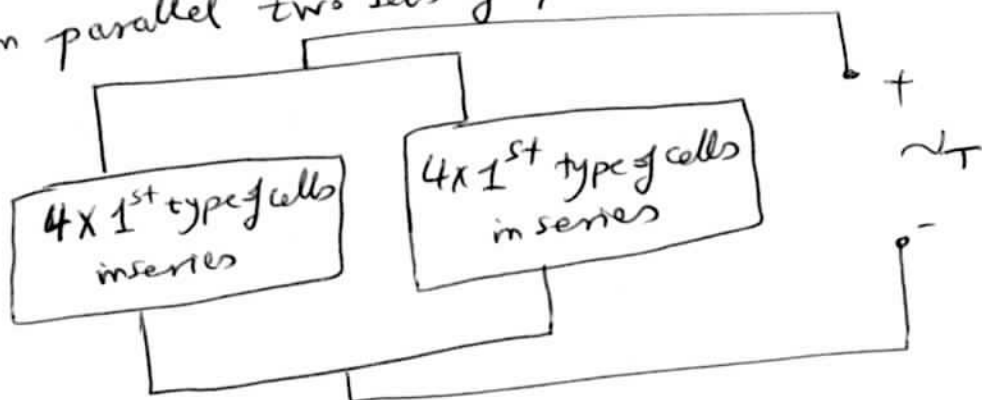Design II: to put in parallel two sets of 4 series cells of this type:



$$V_T = 4 \times 9 = 36V \checkmark$$

$$R_T = (4 \times R_{T1}) \parallel (4 \times R_{T1}) = \frac{16 \times 16}{16 + 16} \Rightarrow R_T = 8\Omega \leq 10\Omega \checkmark$$

this design is, so far, desirable, w/ $m_{tot} = 8 \times 40 = 320g$.

- using 2nd type of cells:

Design III: to put in series 9 of these cells in series $\Rightarrow \begin{cases} V_{oc} = 9 \times 4 = 36V \checkmark \\ R_T = 9 \times R_{T2} = 4.5 \leq 10\Omega \checkmark \end{cases}$

this design is, so far, desirable, w/ $m_{tot} = 9 \times 15 = 135g$.

- The best design:


Comparing Design II & Design III \Rightarrow as $m_{tot} |_{\text{Design II}} > m_{tot} |_{\text{Design III}}$,

So, the best design is Design III.

P3-75:

(P.4)

Circuit 1:

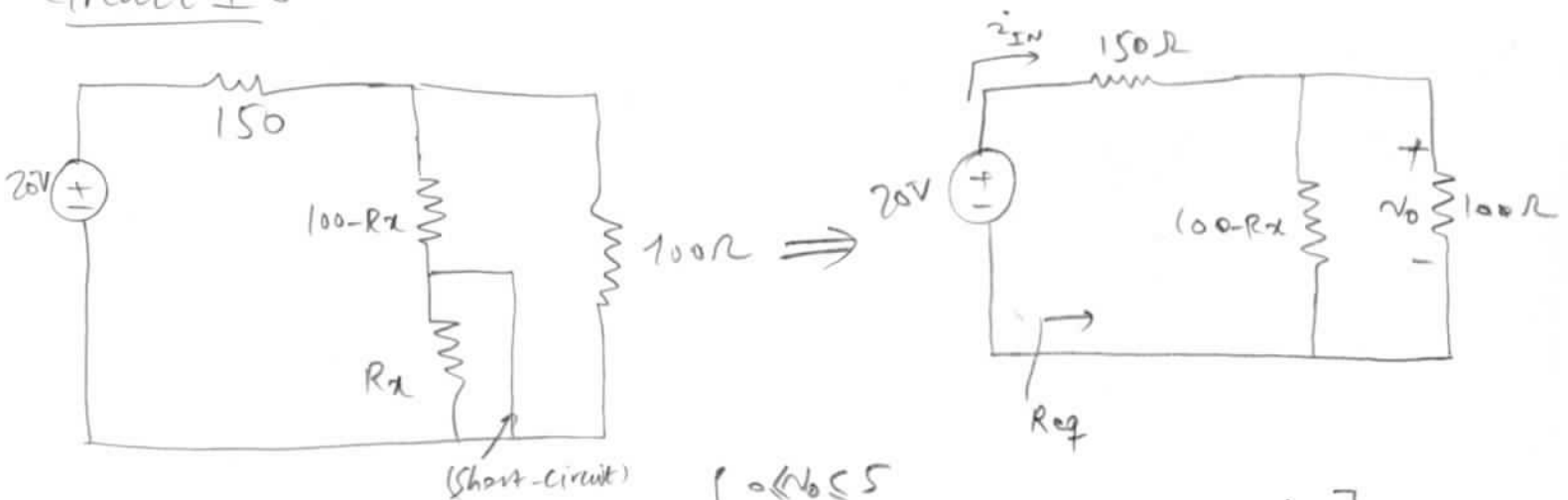

where $0 < R_x < 100$ Φ to maintain $\begin{cases} 0 < V_o \leq 5 \\ P_{IN} \leq 2.5W \quad [P_{IN} = 20 \cdot i_{IN}] \end{cases}$

$$R_{eq} = 150 + (100 - R_x) \parallel (100 \Omega) = 150 + \frac{(100 - R_x)(100)}{100 - R_x + 100} = 150 + \frac{10^4 - 10^2 R_x}{200 - R_x}$$

$$\Rightarrow V_o = 20 - 150 \times \frac{20}{R_{eq}} = 8 + \frac{480}{R_x - 160}$$

So, to check: $0 < V_o \leq 5 \Rightarrow 0 \leq 8 + \frac{480}{R_x - 160} \leq 5$
 \Downarrow some simplifications
 $0 < R_x \leq 100 \checkmark$

Then, to check: $P_{IN} \leq 2.5 \Rightarrow 20 \cdot i_{IN} \leq 2.5 \Rightarrow 20 \left(\frac{20}{R_{eq}} \right) \leq 2.5$

$$\Rightarrow R_{eq} \geq 160 \Rightarrow 150 + \frac{10^4 - 10^2 R_x}{200 - R_x} \geq 160$$


\Downarrow some simplifications

$$R_x \leq 88.89 \text{ X}$$

it means that for $88.89 < R_x < 100$, $P_{IN} \leq 2.5$ is NOT satisfied, so it is not acceptable.

Circuit 2:

P.5

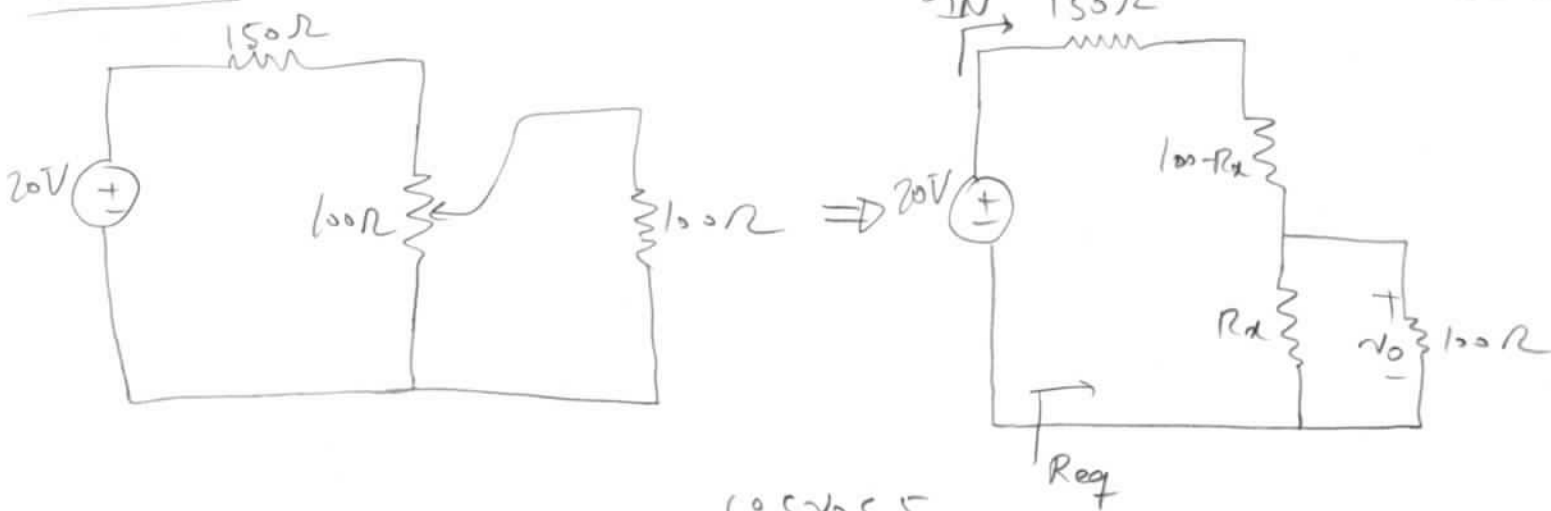

where $0 \leq R_x \leq 100 \Omega$ to maintain $\begin{cases} 0 \leq v_o \leq 5 \\ P_{IN} \leq 2.5W \quad [P_{IN} = 20 \cdot i_{IN}] \end{cases}$

$$R_{eq} = (150 + 100 - R_x) + R_x \parallel 100 = 250 - R_x + \frac{100 R_x}{100 + R_x}$$

$$v_o = 20 - (150 + (100 - R_x)) \frac{20}{R_{eq}} \xrightarrow[\text{simplification}]{\text{Some}} v_o = - \frac{2000 R_x}{R_x^2 - 250 R_x - 25000}$$

So, to check: $0 \leq v_o \leq 5 \Rightarrow 0 \leq - \frac{2000 R_x}{R_x^2 - 250 R_x - 25000} \leq 5$

↓ some simplifications

$$0 \leq R_x \leq 100 \quad \checkmark$$

Then, to check: $P_{IN} \leq 2.5 \Rightarrow 20 \cdot i_{IN} \leq 2.5 \Rightarrow 20 \left(\frac{20}{R_{eq}} \right) \leq 2.5$

$$\Rightarrow R_{eq} \geq 160 \Rightarrow 250 - R_x + \frac{100 R_x}{100 + R_x} \geq 160$$

↓ some simplifications


$$R_x \leq 100 \quad \checkmark$$

Hence, both requirements are met for $0 \leq R_x \leq 100$, so this design is desirable.

P3-1:

(P.6)

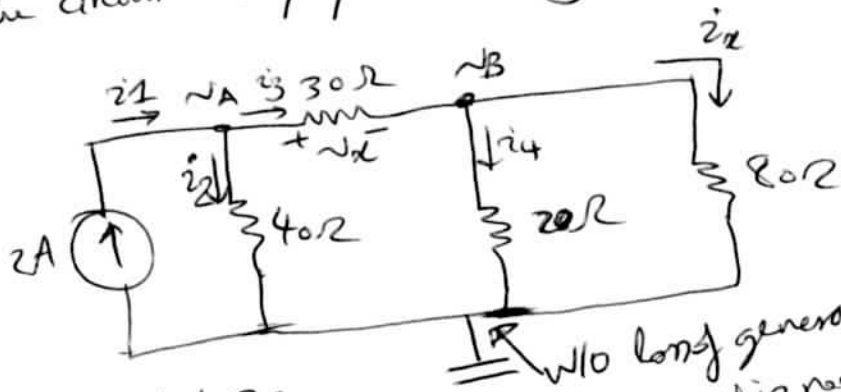The topology of the circuit w/ proper labeling is drawn as follows:



w/o loss of generality, we can assume this node to be the reference node.

(I) KCL at node A & B:

$$i_1 = i_2 + i_3$$

$$i_3 = i_4 + i_x$$

(II) Element eq'n's:

$$i_1 = 2A \quad (\text{current source})$$

$$i_2 = \frac{v_A}{40}$$

$$i_3 = \frac{v_A - v_B}{30} \quad \left[\text{where we also note that: } \underbrace{v_x = v_A - v_B}_{(*)} \right]$$

$$i_4 = \frac{v_B}{20}$$

$$i_x = \frac{v_B}{80} \quad (**)$$

(III) plugging back the obtained eq'n's in step (II), back into step (I):

$$2 = \frac{v_A}{40} + \frac{v_A - v_B}{30} \Rightarrow \begin{cases} 7v_A - 4v_B = 240 \\ -4v_A + 11.5v_B = 0 \end{cases}$$

$$\frac{v_A - v_B}{30} = \frac{v_B}{20} + \frac{v_B}{80} \Rightarrow$$


(IV) Solving for the set of linear eq'n's obtained in step (III):

$$\begin{bmatrix} 7 & -4 \\ -4 & 11.5 \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 240 \\ 0 \end{bmatrix} \Rightarrow \begin{cases} v_A = 42.79V \\ v_B = 14.88V \end{cases}$$

Therefore:

$$\text{from } (*): v_x = v_A - v_B \Rightarrow v_x = 27.91V$$
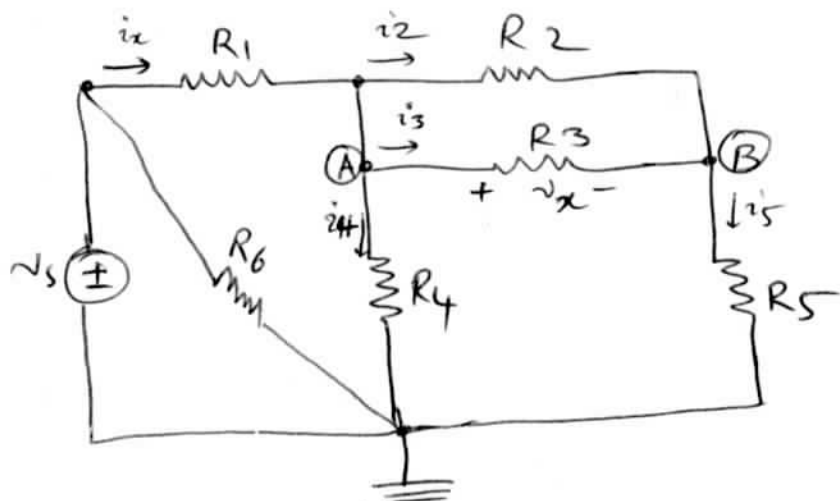
$$i_x = \frac{v_x}{80} \Rightarrow i_x = 0.3489A$$



(a) node-voltage eq'ns:

In analogous ^{way} to the sol'n of P 3-1, we obtain:

$$\text{node (A): } i_2 = i_3 + i_4 \Leftrightarrow \frac{v_s - v_A}{R_1} = \frac{v_A - v_B}{R_2} + \frac{v_A - v_B}{R_3} + \frac{v_A}{R_4}$$

$$\Leftrightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) v_A - \left(\frac{1}{R_2} + \frac{1}{R_3} \right) v_B = \left(\frac{1}{R_1} \right) v_s$$

$$\text{node (B): } i_2 + i_3 = i_5 \Leftrightarrow \frac{v_A - v_B}{R_2} + \frac{v_A - v_B}{R_3} = \frac{v_B}{R_5}$$

$$\Leftrightarrow -\left(\frac{1}{R_2} + \frac{1}{R_3} \right) v_A + \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) v_B = 0$$

and so, in matrix form:

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) & -\left(\frac{1}{R_2} + \frac{1}{R_3} \right) \\ -\left(\frac{1}{R_2} + \frac{1}{R_3} \right) & \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} \\ 0 \end{bmatrix} v_s$$

(b) Given: $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 10 \text{ k}\Omega$ & $v_s = 24 \text{ V}$:


$$\begin{bmatrix} 0.4 \times 10^{-3} & -0.2 \times 10^{-3} \\ -0.2 \times 10^{-3} & 0.3 \times 10^{-3} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 0.1 \times 10^{-3} \\ 0 \end{bmatrix} 24 \Rightarrow \begin{cases} v_A = 9 \text{ V} \\ v_B = 6 \text{ V} \end{cases}$$

where we have:

$$\begin{cases} v_x = v_A - v_B \Rightarrow \boxed{v_x = 3 \text{ V}} \\ i_x = \frac{v_s - v_A}{R_1} \Rightarrow \boxed{i_x = 15 \times 10^{-4} \text{ A}} \end{cases}$$

P3-7:

(P.8)

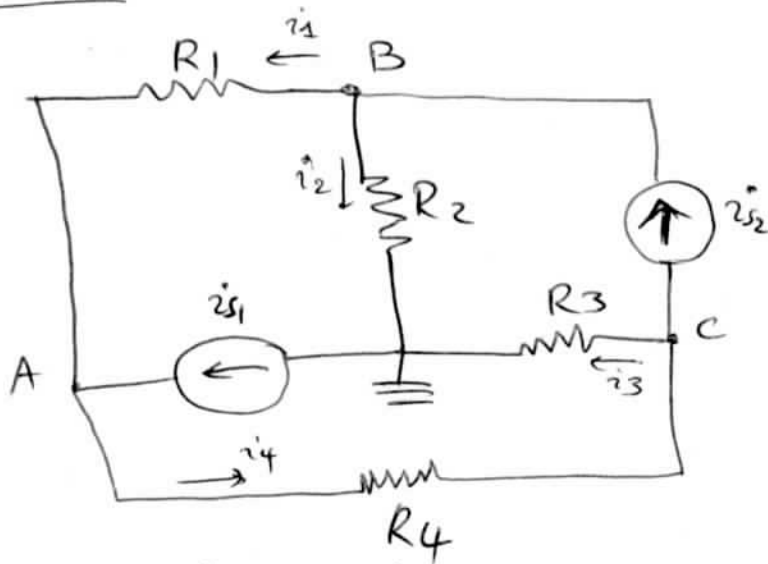

(a) node-voltage eq'ns:

In analogous way to P3-1:

node A: $i_{s1} + i_1 = i_4 \Leftrightarrow \frac{v_A - v_C}{R_4} - \frac{v_B - v_A}{R_1} = i_{s1} \Leftrightarrow \left(\frac{1}{R_1} + \frac{1}{R_4}\right)v_A - \frac{1}{R_4}v_C - \frac{1}{R_1}v_B = i_{s1}$

node B: $i_{s2} = i_1 + i_2 \Leftrightarrow \frac{v_B - v_A}{R_1} + \frac{v_B}{R_2} = i_{s2} \Leftrightarrow \left(-\frac{1}{R_1}\right)v_A + \left(\frac{1}{R_1} + \frac{1}{R_2}\right)v_B = i_{s2}$

node C: $i_{s2} + i_3 = i_4 \Leftrightarrow \frac{v_A - v_C}{R_4} - \frac{v_C}{R_3} = i_{s2} \Leftrightarrow -\left(\frac{1}{R_4}\right)v_A + \left(\frac{1}{R_4} + \frac{1}{R_3}\right)v_C = i_{s2}$

and so, in matrix form:

$$\begin{bmatrix} \left(\frac{1}{R_1} + \frac{1}{R_4}\right) & -\frac{1}{R_1} & -\frac{1}{R_4} \\ -\frac{1}{R_1} & \left(\frac{1}{R_1} + \frac{1}{R_2}\right) & 0 \\ -\frac{1}{R_4} & 0 & +\left(\frac{1}{R_4} + \frac{1}{R_3}\right) \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} i_{s1} \\ i_{s2} \\ -i_{s2} \end{bmatrix}$$


It is also possible to use "writing node equations by inspection" method, instead.

(b) Given $R_1 = 1.5 \text{ k}\Omega$, $R_2 = 2.2 \text{ k}\Omega$, $R_3 = 3.3 \text{ k}\Omega$, $R_4 = 4.7 \text{ k}\Omega$, $i_{s1} = i_{s2} = 2 \text{ mA}$:

$$\begin{bmatrix} 9 \times 10^{-4} & -4 & -2 \times 10^{-4} \\ -7 \times 10^{-4} & 1.1 \times 10^{-3} & 0 \\ -2 \times 10^{-4} & 0 & +5 \times 10^{-4} \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} 1 \\ 1 \\ -1 \end{bmatrix} \times 2 \times 10^{-3} \Rightarrow \begin{cases} v_A = 5.98 \text{ V} \\ v_B = 5.34 \text{ V} \\ v_C = -1.41 \text{ V} \end{cases}$$

P-3-8:

(E.9)

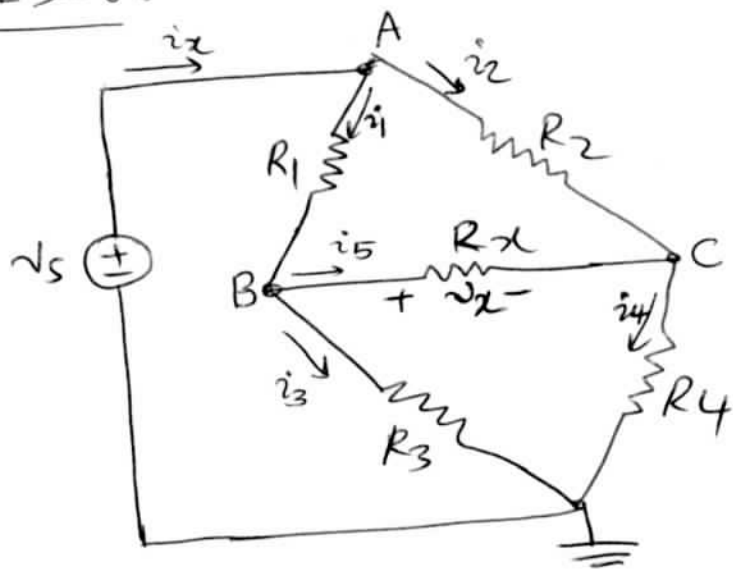

(a) node-voltage eq'ns

In analogy our way to P 3-1:

$$\text{node } \textcircled{B}: i_1 = i_5 + i_3 \Leftrightarrow \frac{v_s - v_B}{R_1} = \frac{v_B - v_C}{R_x} + \frac{v_B}{R_3} \Leftrightarrow \left(\frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_x}\right)v_B - \frac{1}{R_x}v_C = \frac{v_s}{R_1}$$

$$\text{node } \textcircled{C}: i_2 + i_5 = i_4 \Leftrightarrow \frac{v_s - v_C}{R_2} + \frac{v_B - v_C}{R_x} = \frac{v_C}{R_4} \Leftrightarrow \left(-\frac{1}{R_x}\right)v_B + \left(\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_x}\right)v_C = \frac{v_s}{R_2}$$

and so, in matrix form

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_3} + \frac{1}{R_x} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & \frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_x} \end{bmatrix} \begin{bmatrix} v_B \\ v_C \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} \\ \frac{1}{R_2} \end{bmatrix} v_s$$

(b) Given: $R_1 = R_4 = 1\text{ k}\Omega$, $R_2 = R_3 = 250\ \Omega$, $R_x = 500\ \Omega$, $v_s = 15\text{ V}$:

$$\begin{bmatrix} 7 \times 10^{-3} & -2 \times 10^{-3} \\ -2 \times 10^{-3} & 7 \times 10^{-3} \end{bmatrix} \begin{bmatrix} v_B \\ v_C \end{bmatrix} = \begin{bmatrix} 1.5 \times 10^{-2} \\ 6 \times 10^{-2} \end{bmatrix} \Rightarrow \begin{cases} v_B = 5\text{ V} \\ v_C = 10\text{ V} \end{cases}$$


Referring to circuit:

$$v_x = v_B - v_C \Rightarrow \boxed{v_x = -5\text{ V}}$$

$$\text{KCL at node } \textcircled{A}: i_x = i_1 + i_2 = \frac{v_s - v_B}{R_1} + \frac{v_s - v_C}{R_2} \Rightarrow \boxed{i_x = 0.03\text{ A}}$$

P 3-15:

(2-10)

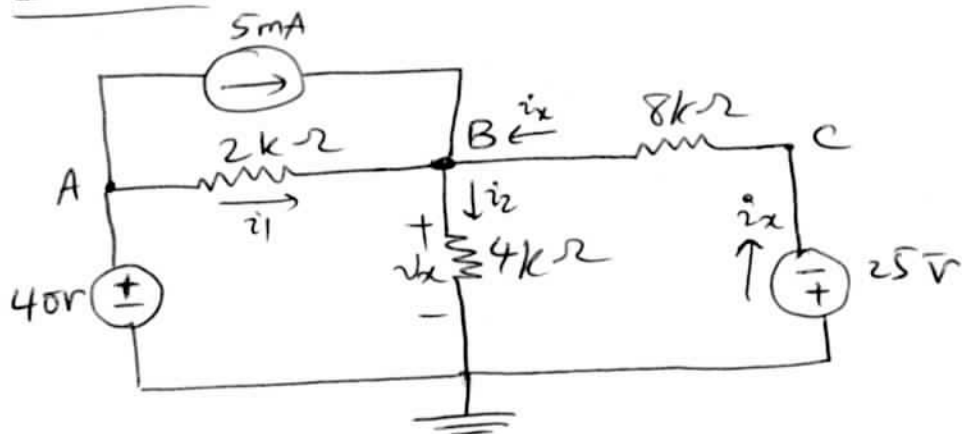

(b) node-voltage eqn:

$$\text{node (B)}: i_1 + 5 \times 10^{-3} = i_2 - i_x \Leftrightarrow \frac{40 - v_B}{2 \times 10^3} + 5 \times 10^{-3} = \frac{v_B}{4 \times 10^3} - \frac{-25 - v_B}{8 \times 10^3}$$


$$\Leftrightarrow v_B \left(\frac{1}{4} + \frac{1}{8} + \frac{1}{2} \right) = (5 - 3.125 + 20)$$

$$\Leftrightarrow \boxed{v_B = 25 \text{ V}}$$

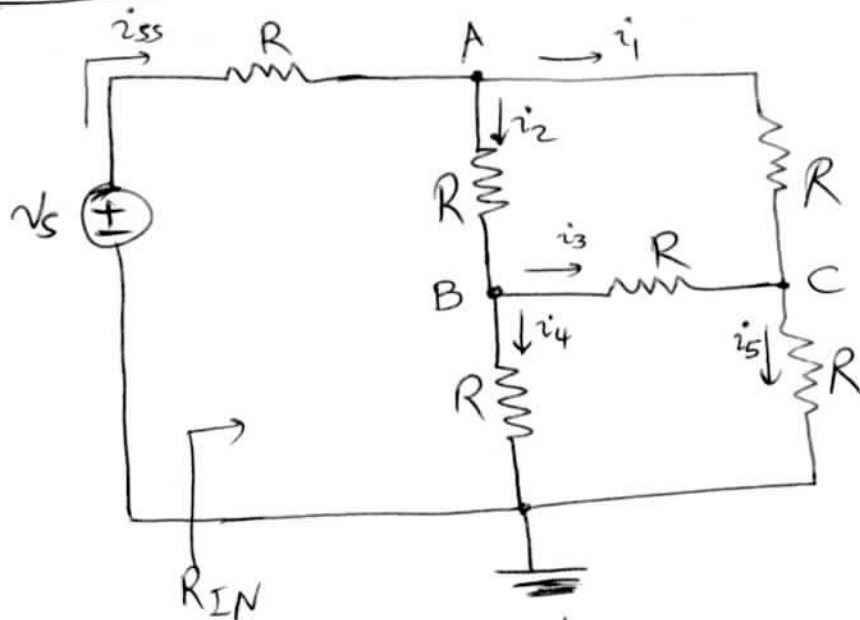(d) Referring to the circuit:

$$i_x = \frac{-25 - v_B}{8 \times 10^3} \Rightarrow i_x = \frac{-25 - 25}{8 \times 10^3} \Rightarrow \boxed{i_x = -6.25 \text{ mA}}$$

$$v_x = v_B - v_{\text{ground}} = v_B - 0 \Rightarrow \boxed{v_x = 25 \text{ V}}$$



GOAL: find $R_{IN} = \frac{v_s}{i_{ss}}$

node A: $i_{ss} = i_1 + i_2$

[note that: $v_s = Ri_{ss} + v_A \Leftrightarrow i_{ss} = \frac{v_s - v_A}{R}$]

$$\frac{v_s - v_A}{R} = \frac{v_A - v_C}{R} + \frac{v_A - v_B}{R} \Leftrightarrow \left(\frac{3}{R}\right)v_A - \frac{1}{R}v_B - \frac{1}{R}v_C = \frac{v_s}{R}$$

$$\Leftrightarrow 3v_A - v_B - v_C = v_s$$

node B: $i_2 = i_3 + i_4 \Leftrightarrow \frac{v_A - v_B}{R} = \frac{v_B - v_C}{R} + \frac{v_B}{R} \Leftrightarrow \left(\frac{3}{R}\right)v_B - \frac{1}{R}v_A - \frac{1}{R}v_C = 0$

$$\Leftrightarrow 3v_B - v_A - v_C = 0$$

node C: $i_3 + i_4 = i_5 \Leftrightarrow \frac{v_B - v_C}{R} + \frac{v_A - v_C}{R} = \frac{v_C}{R} \Leftrightarrow \left(\frac{3}{R}\right)v_C - \frac{1}{R}v_B - \frac{1}{R}v_A = 0$

$$\Leftrightarrow 3v_C - v_B - v_A = 0$$



and so, in matrix form:

$$\begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix} \begin{bmatrix} v_A \\ v_B \\ v_C \end{bmatrix} = \begin{bmatrix} v_s \\ 0 \\ 0 \end{bmatrix} \Rightarrow \begin{cases} v_A = v_s/2 \\ v_B = v_s/4 \\ v_C = v_s/4 \end{cases}$$

$$\Rightarrow i_{ss} = \frac{v_s - v_A}{R} = \frac{v_s}{2R} \Rightarrow R_{IN} = \frac{v_s}{i_{ss}} = \frac{v_s}{v_s/2R} \Rightarrow \boxed{R_{IN} = 2R}$$

P 3-19:

P.12

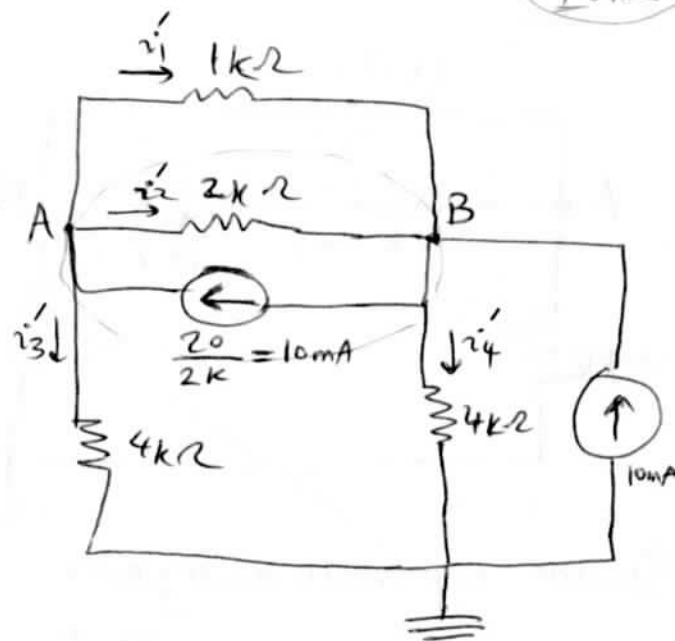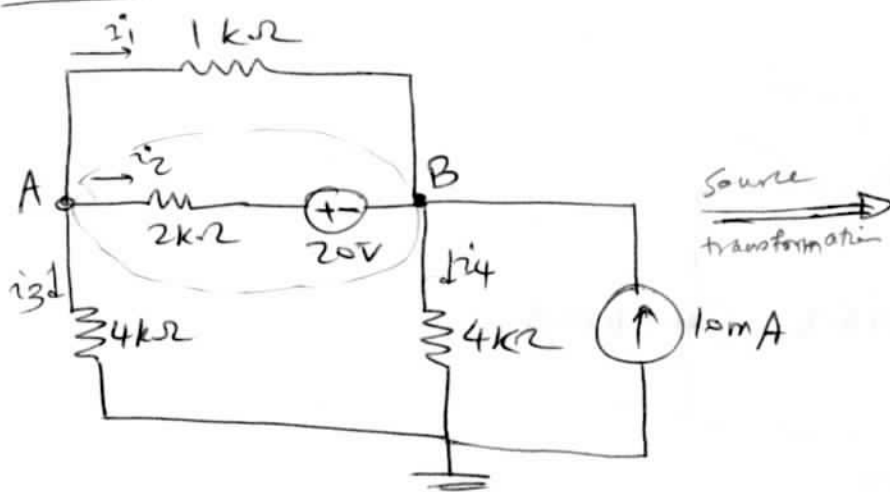

Node-voltage eq'n:

kcl at A: $i_1' + i_2' + i_3' = 10 \Rightarrow \frac{v_A - v_B}{1} + \frac{v_A - v_B}{2} + \frac{v_A}{4} = 10 \Rightarrow v_A(1 + 1/2 + 1/4) - v_B(1 + 1/2) = 10$

kcl at B: $i_1' + i_2' = i_4' \Rightarrow \frac{v_A - v_B}{1} + \frac{v_A - v_B}{2} = \frac{v_B}{4} \Rightarrow -v_A(1 + 1/2) + v_B(1 + 1/2 + 1/4) = 0$

So, in matrix form:

$$\begin{bmatrix} 1 + 1/2 + 1/4 & -(1 + 1/2) \\ -(1 + 1/2) & 1 + 1/2 + 1/4 \end{bmatrix} \begin{bmatrix} v_A \\ v_B \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \Rightarrow \begin{cases} v_A = 21.54V \\ v_B = 18.46V \end{cases}$$

Then, we can find the currents:

$$i_1 = \frac{v_A - v_B}{1k} \Rightarrow i_1 = 3.08mA$$

$$i_2 = \frac{v_A - 20}{2k} \Rightarrow i_2 = 0.77mA$$

$$i_3 = \frac{v_A}{4k} \Rightarrow i_3 = 5.385mA$$

$$i_4 = \frac{v_B}{4k} \Rightarrow i_4 = 4.615mA$$