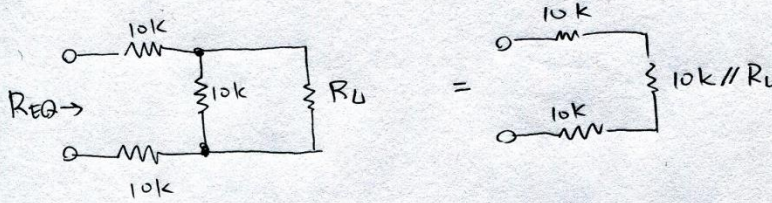


2.32




$$R_{eq} = 10 + 10 + 10 // R_L = 20 + \frac{10 \cdot R_L}{10 + R_L} \quad (k\Omega)$$

$$\text{For } R_{eq} = 25 \text{ k}\Omega \Rightarrow 20 + \frac{10 \cdot R_L}{10 + R_L} = 25 \quad R_L = 10 \text{ (k}\Omega)$$

$$\text{For } R_{eq} = 20 \text{ k}\Omega \Rightarrow 20 + \frac{10 \cdot R_L}{10 + R_L} = 20 \quad R_L = 0 \text{ (short wire)}$$


2.47

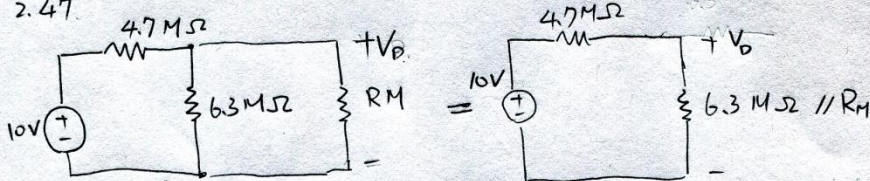

Applying formula for voltage divider:

$$V_0 = 10 \cdot \frac{6.3 // R_M}{4.7 + 6.3 // R_M} = \frac{63 R_M}{29.61 + 11 R_M} = 3.81 \Rightarrow R_M = 5.3492 \text{ (M}\Omega)$$

3.20

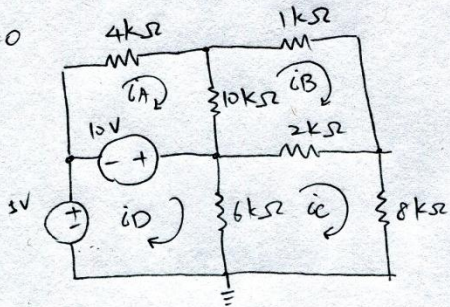

$$\text{KVL of Loop A: } \bar{i}_A \cdot 4k + (\bar{i}_A - \bar{i}_B) \cdot 10k = -10$$

$$\text{" " B: } \bar{i}_B \cdot 1k + (\bar{i}_B - \bar{i}_A) \cdot 10k + (\bar{i}_B - \bar{i}_C) \cdot 2k = 0$$

$$\text{C: } \bar{i}_C \cdot 8k + (\bar{i}_C - \bar{i}_B) \cdot 2k + (\bar{i}_C - \bar{i}_D) \cdot 8k = 0$$

$$\text{D: } (\bar{i}_D - \bar{i}_C) \cdot 6k = 15$$

$$1000 \times \begin{bmatrix} 14 & -10 & 0 & 0 \\ -10 & 13 & -2 & 0 \\ 0 & -2 & 16 & -6 \\ 0 & 0 & -6 & 6 \end{bmatrix} \begin{bmatrix} \bar{i}_A \\ \bar{i}_B \\ \bar{i}_C \\ \bar{i}_D \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \\ 0 \\ 15 \end{bmatrix} \Rightarrow$$


$$\bar{i}_A = -1.2565 \text{ mA}$$

$$\bar{i}_B = -0.7592 \text{ mA}$$

$$\bar{i}_C = 1.3482 \text{ mA}$$

$$\bar{i}_D = 3.8482 \text{ mA}$$

↓ use node-voltage:

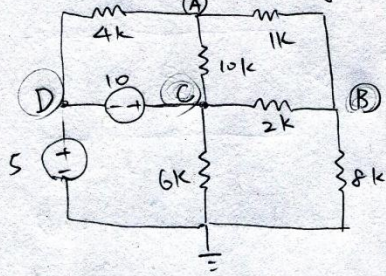

By observation, $V_D = 5$, $V_C = 15$

$$\text{KCL @ A: } \frac{1}{4}(V_A - V_D) + \frac{1}{10}(V_A - V_C) + \frac{1}{1}(V_A - V_B) = 0$$


$$\text{KCL @ B: } \frac{1}{1}(V_B - V_A) + \frac{1}{2}(V_B - V_C) + \frac{1}{8}(V_B) = 0$$

$$\begin{bmatrix} \frac{1}{4} + \frac{1}{10} + \frac{1}{1} & -\frac{1}{10} & -\frac{1}{1} & \frac{1}{4} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{2} + \frac{1}{8} & -\frac{1}{2} & 0 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix} \quad \& \quad V_C = 15, \quad V_D = 5$$

Solve the equation we get: $V_A = 10.062 \text{ (V)}$ $V_B = 10.7853 \text{ (V)}$


It's easier to solve this circuit using Node-Voltage because with grounded voltage source there will be only 2 unknowns left to be solved.

3.29

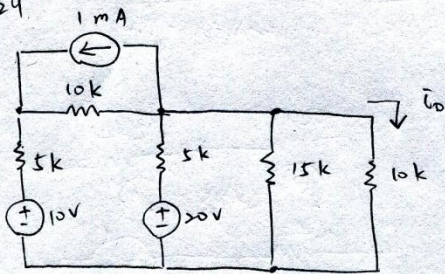

Use node voltage:


1mA source on:

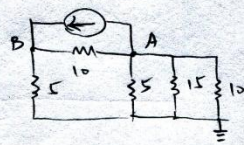

$$\begin{bmatrix} \frac{1}{10} + \frac{1}{5} + \frac{1}{15} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} -1 \text{ mA} \\ 1 \text{ mA} \end{bmatrix}$$

$$\Rightarrow V_A = -1.5385, \quad \bar{U}_0 = \frac{V_A}{10} = -0.15385$$

10V source on:

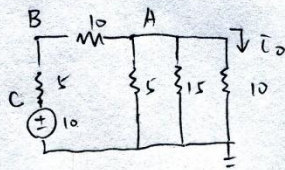



$$\begin{bmatrix} \frac{1}{10} + \frac{1}{5} + \frac{1}{15} + \frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} + \frac{1}{5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$V_C = 10$$

(cont.)

Solve equation we get : $V_A = 1.5385$ $i_o = \frac{V_A}{10} = 0.15385$


20V source on:

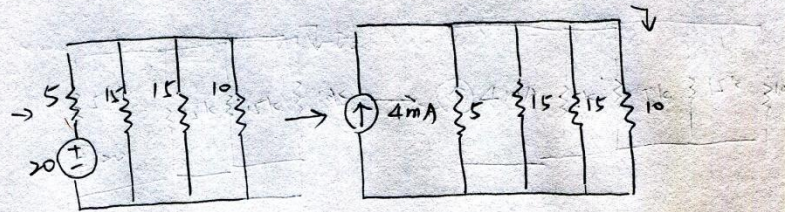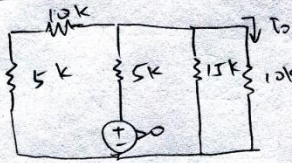


$$i_o = 4 \text{ mA} \cdot \frac{\frac{1}{10}}{\frac{1}{5} + \frac{1}{15} + \frac{1}{15} + \frac{1}{10}} = 0.9231$$

$$\sum i_o = -0.1538 + 0.1538 + 0.9231 = \underline{0.9231 \text{ (mA)}} \quad *$$

3-38:

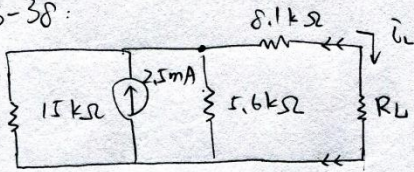

Short circuit:
to find I_N

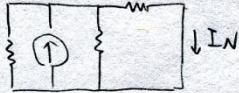

$$I_N = 2.5 \cdot \frac{1/8.1}{1/8.1 + 1/5.6 + 1/15} = 0.8371 \text{ (mA)}$$


Open circuit:
to find V_T



$$V_T = 2.5 \cdot \frac{15 \cdot 5.6}{15 + 5.6} = 10.194 \text{ (V)}$$

$$R = \frac{V_T}{I_N} = 12.178 \text{ (k}\Omega\text{)}$$

Norton equivalent seen by R_L :

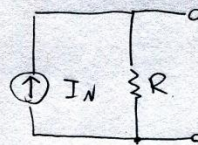

where $I_N = 0.8371 \text{ mA}$

$R = 12.178 \text{ k}\Omega$


For $R_L = 4.7 \text{ k}\Omega$. Apply formula for current divider:

$$i_L = I_N \cdot \frac{1/R_L}{1/R_L + 1/R} = 0.604 \text{ (mA)}$$


For $R_L = 15 \text{ k}\Omega$, $i_L = 0.3751 \text{ (mA)}$

$R_L = 68 \text{ k}\Omega$, $i_L = 0.1271 \text{ (mA)}$ **

3-39

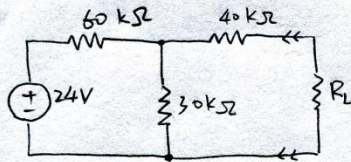

Short circuit to find I_N :

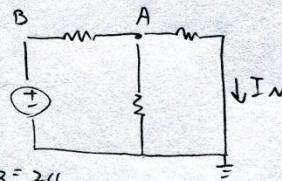


$$\left(\frac{1}{60} + \frac{1}{40} + \frac{1}{30}\right) V_A - \frac{1}{60} V_B = 0 \quad V_B = 24$$

$$\Rightarrow V_A = 5.3 \quad I_N = \frac{V_A}{40 \text{ k}} = 0.133 \text{ (mA)}$$

Open circuit to find V_T :

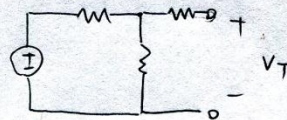
$$\Rightarrow V_T = 24 \cdot \frac{30}{30+60} = 8 \text{ (V)}$$



(cont.)

$$R = \frac{V_T}{I_N} = 60 \text{ (k}\Omega\text{)}$$

Thevenin equivalent of the circuit is:

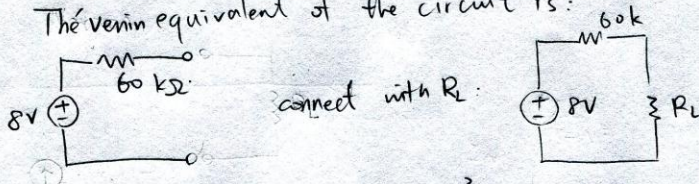

$$V_L = 8 \cdot \frac{R_L}{R_L + 60}$$


$$P = \frac{V_L^2}{R_L} = \frac{64 R_L}{(R_L + 60)^2}$$

For $R_L = 50 \text{ k}\Omega$,

$$P = 2.645 \cdot 10^{-4} \text{ (W)}$$

For $R_L = 200 \text{ k}\Omega$

$$P = 1.893 \cdot 10^{-4} \text{ (W)}$$

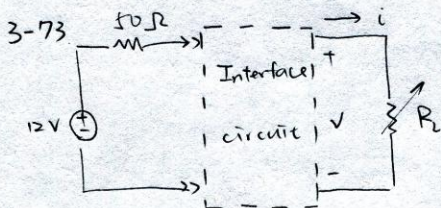

Design Interface circuit using 3 50 Ω

let: 1) $V \leq 4 \text{ V}$

2) $i \leq 100 \text{ mA}$


regardless of the value of R_L

i : reach its maximum when $R_L \rightarrow 0$

V : reach its maximum when $R_L \rightarrow \infty$


which implies that we need to design one circuit with $V_T \leq 4 \text{ V}$ & $I_N \leq 100 \text{ mA}$

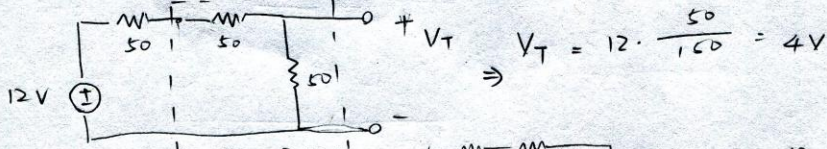In order to decrease $V_T \Rightarrow$ use voltage divider with 2 50 Ω resistors:




$$V_T = 12 \cdot \frac{50}{150} = 4 \text{ V}$$

check current:

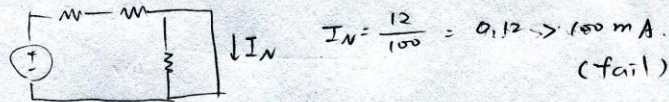

$$I_N = \frac{12}{100} = 0.12 > 100 \text{ mA. (fail)}$$

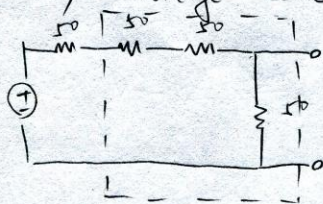Try voltage divider with 3 more 50 Ω resistors:





$$V_T = 12 \cdot \frac{50}{200} = 3 \text{ V, (✓)}$$

$$I_N = \frac{12}{150} = 0.08 < 100 \text{ mA (✓)}$$


This is a valid design!

(cont.)

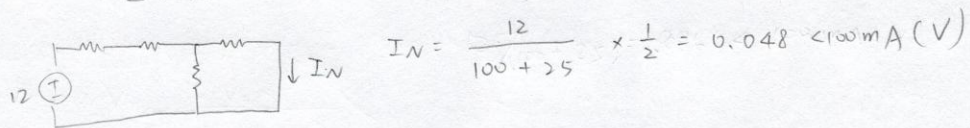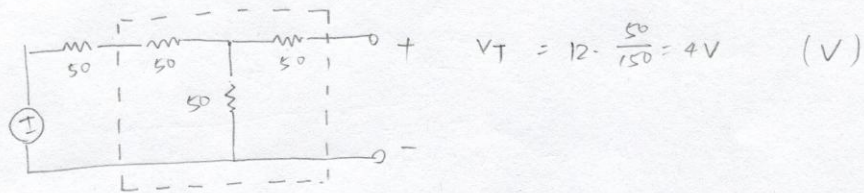Another possible design: start from voltage divider



This is also a possible design!

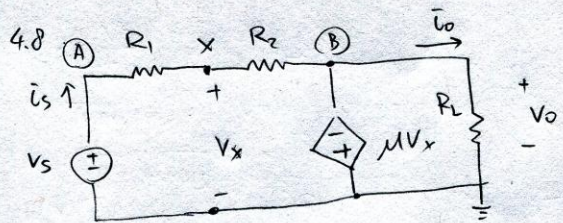

By setting up ground, $V_A = v_s$, $V_B = -\mu V_x$

$$\text{KCL @ } x : (V_x - V_A) \cdot \frac{1}{R_1} + (V_x - V_B) \cdot \frac{1}{R_2} = 0,$$

$$\Rightarrow V_x = \frac{v_s R_2}{R_1 + R_1 \mu + R_2}$$

$$i_o = \frac{V_B - 0}{R_L}, \quad i_s = \frac{V_x - V_B}{R_2} = \frac{V_x (1 + \mu)}{R_2} = \frac{-i_o v_s R_2}{v_s} = \frac{\mu}{(1 + \mu)} \cdot \frac{R_2}{R_L} *$$

$$V_o = V_B = -\mu V_x \quad \frac{V_o}{v_s} = \frac{-\mu R_2}{R_1 + R_1 \mu + R_2} *$$

Note: express $\frac{i_o}{v_s}$, $\frac{V_o}{v_s}$, in terms of R_1, R_2, μ ,