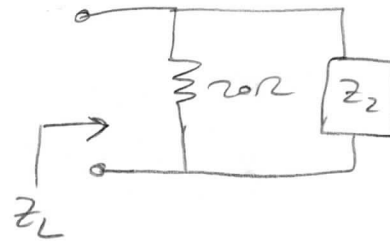


10-53:

(a) Goal: to achieve $Z_L(s) = \frac{s+5}{s+10}$ in the circuit:



by properly choosing Z_2 .

Analysis: Given the circuit, we find Z_L :

$$Z_L = 20 \parallel Z_2 = \frac{20 Z_2}{Z_2 + 20}$$

then we equate it w/ the given eq'n for Z_L :

$$Z_L = \frac{20 Z_2}{Z_2 + 20} = \frac{s+5}{s+10}$$

where solving this eq'n for Z_2 we get:

$$Z_2 = \frac{20s + 100}{19s + 195}$$

(b) To realize Z_2 , we first compute Y_L :

$$Y_L = \frac{1}{Z_L} = \frac{s+10}{s+5}$$

where we know from the circuit:

$$Y_L = \frac{s+10}{s+5} \equiv \frac{1}{20} + Y_2 = 0.05 + Y_2$$

↓

$$\frac{s+5+5}{s+5} = 1 + \frac{5}{s+5} = 0.05 + 0.95 + \frac{5}{s+5} \equiv 0.05 + Y_2$$

$$Y_2 = 0.95 + \frac{5}{s+5} \quad (*)$$


from eq'n (8), we can guess that the term $Y = 0.95$ represents a resistance in parallel w/ admittance $Y = \frac{5}{s+5}$, where the latter is also representing:

$$Y = \frac{5}{s+5} \Rightarrow Z = \frac{s+5}{5} = \frac{1}{5}s + \frac{1}{5}$$

↑ an inductor ↑ a resistance


(because of summation, they are in series)

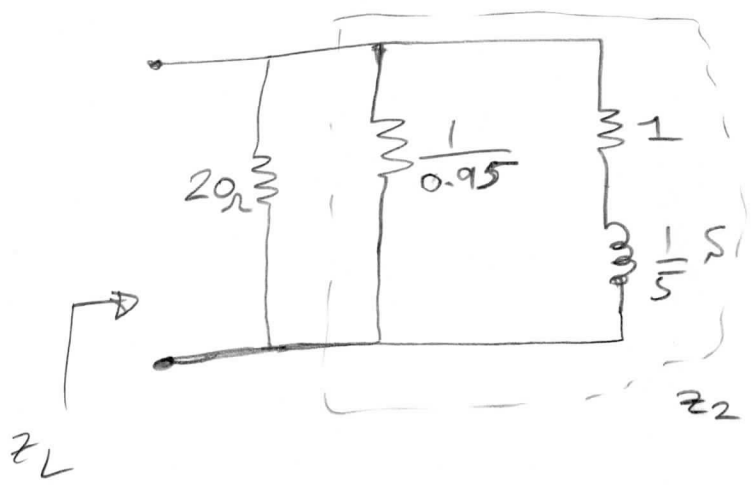Therefore, Z_2 can be realized in the following way:



12-4:

Given:

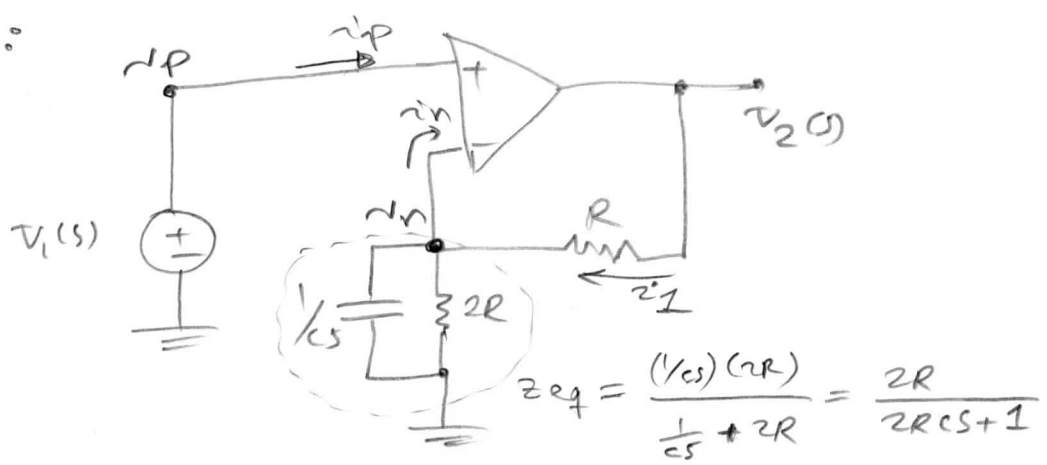

- from basic properties of op-amp: $Z_p = \infty \Rightarrow$ therefore, the driving-point impedance seen by $V_1(s)$ is ∞ .

- also, from basic properties of op-amp: $V_n = V_p = V_1(s)$, so we find Z_i :

$$Z_i = \frac{V_n - 0}{Z_{eq}} \Rightarrow Z_i = \frac{V_1(2RCs + 1)}{2R}$$


and so:

$$\frac{V_2 - V_1}{R} = i_1 \Rightarrow \frac{V_2 - V_1}{R} = \frac{V_1 (2RCs + 1)}{2R} \Rightarrow 2V_2 - 2V_1 = V_1 (2RCs + 1)$$

$$\Rightarrow T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{2RCs + 3}{2}$$

11-6:

Given:

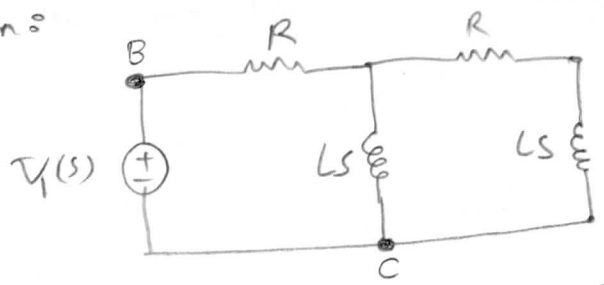


the driving-point impedance or the equivalent impedance seen from B-C ports

$$Z_{BC} = (R + LS) \parallel (LS) + R = \frac{(R + LS)(LS)}{(R + LS) + LS} + R = \frac{L^2 s^2 + RLS}{2LS + R} + R$$

$$\Rightarrow Z_{BC} = \frac{L^2 s^2 + 3RLS + R^2}{2LS + R}$$

Given:

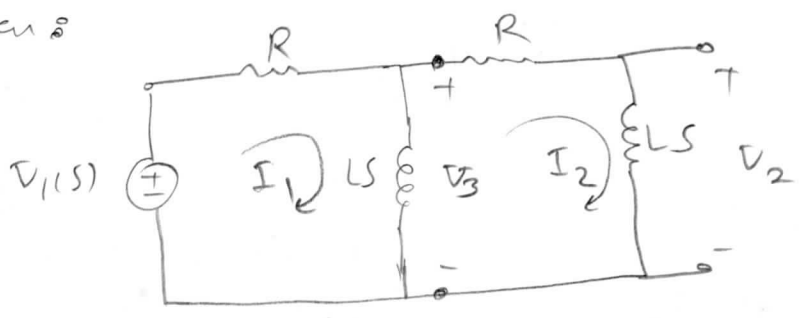

we can have:

$$\begin{cases} V_2(s) = LS I_2(s) \\ LS I_2(s) + LS(I_2 - I_1) + R I_2 = 0 \\ V_1(s) - R I_1 - LS(I_1 - I_2) = 0 \end{cases}$$

from these eq'ns we get:


$$\begin{cases} (2LS + R) \frac{V_2}{LS} = LS I_1 \Rightarrow I_1 = \frac{2LS + R}{(LS)^2} V_2 \\ V_1 = (R + LS) I_1 - LS I_2 \\ I_2 = \frac{V_2}{LS} \end{cases}$$

$$\Rightarrow V_1 = (R + LS) \left(\frac{2LS + R}{(LS)^2} \right) V_2 - LS \frac{V_2}{LS}$$

$$\Rightarrow V_1 = \frac{(R + LS)(2LS + R) - (LS)^2}{(LS)^2} V_2 \Rightarrow T_V(s) = \frac{V_2}{V_1} = \frac{(LS)^2}{(R + LS)(2LS + R) - (LS)^2}$$

some simplification $T_V(s) = \frac{L^2 s^2}{L^2 s^2 + 3RLS + R^2}$

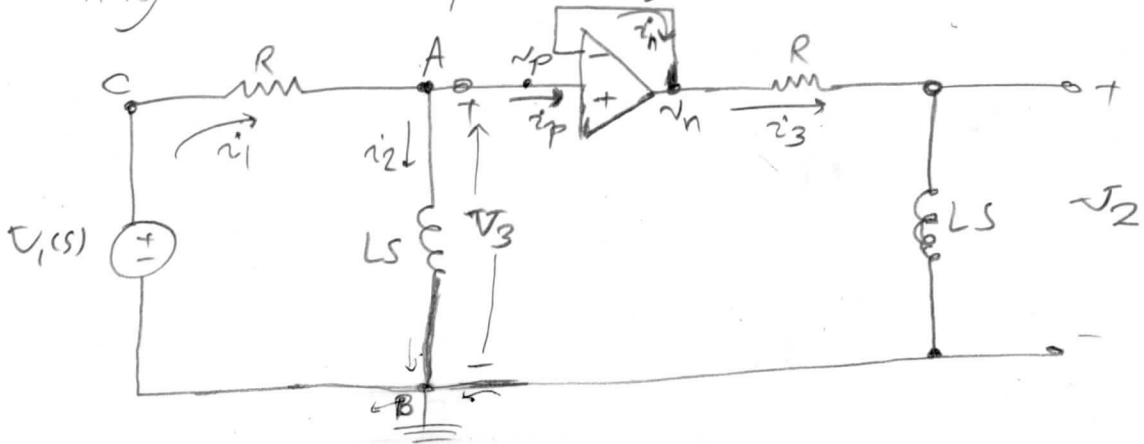By inserting a follower at point A, we get:



from basic properties of op-amp: $v_n = v_p$
 where $v_p = v_A$ } $\Rightarrow v_n = v_A$

moreover, $i_p = 0$ so there is no effect of loading & so we can apply the chain rule:

rule:
 $T_V = \frac{V_2}{V_1} = \frac{V_3}{V_1} \cdot \frac{V_2}{V_3}$

where from voltage division we have:

$\frac{V_3}{V_1} = \frac{LS}{R+LS}$ and $\frac{V_2}{V_3} = \frac{LS}{R+LS}$

therefore:


$T_V = \left(\frac{LS}{R+LS}\right) \left(\frac{LS}{R+LS}\right) \Rightarrow T_V(s) = \frac{L^2 S^2}{L^2 S^2 + 2RLS + R^2}$

Moreover, $V_2 = V_3$ means that there is an ∞ -impedance in parallel w/ LS ,

So driving-point impedance:

$Z_{BC} = R + (LS) \parallel \infty \Rightarrow Z_{BC} = R + LS$

11-10
 Given:

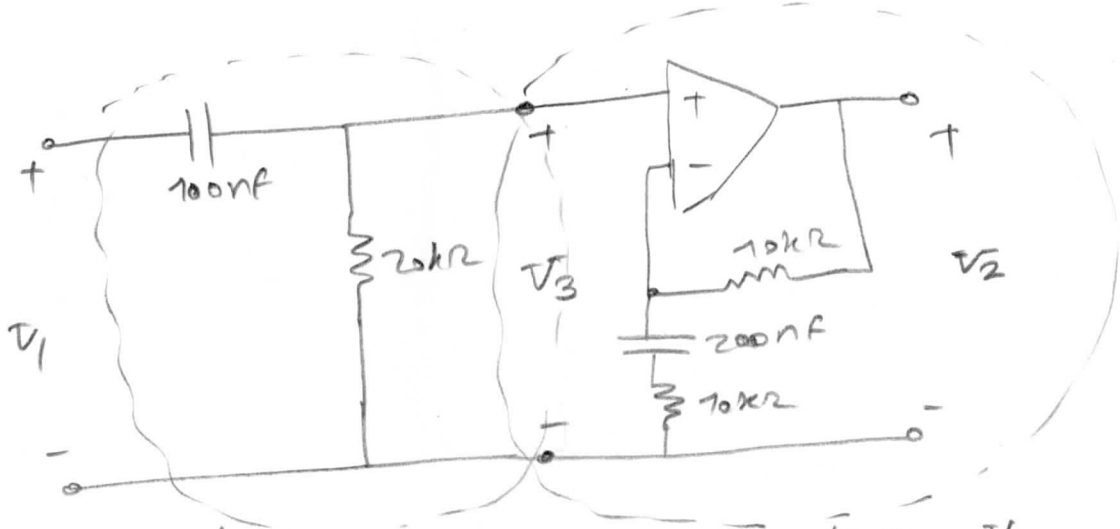

$T_{V1} = \frac{V_3}{V_1}$

$T_{V3} = \frac{V_2}{V_3}$

As demonstrated on the circuit, we solve this problem using chain rule:

(P5)

$$T_V = \frac{V_2}{V_1} = T_{V_1} \cdot T_{V_3}$$

where

$$T_{V_1} = \frac{20 \text{ k}\Omega}{20 \text{ k}\Omega + \frac{1}{100 \text{ nF}s}} \quad (\text{voltage-division})$$

$$T_{V_3} = \frac{z_1 + z_2}{z_1} \quad \text{w/ } z_1 = 10 \text{ k}\Omega + \frac{1}{200 \text{ nF}s} \quad \& \quad z_2 = 10 \text{ k}\Omega \quad (\text{non-inverting op-amp})$$

Simplifying these transfer f'ns:

$$\boxed{T_{V_1} = \frac{2 \times 10^{-3} s}{2 \times 10^{-3} s + 1}}$$

$$\& \quad T_{V_3} = \frac{10^4 + \frac{1}{2 \times 10^{-7} s} + 10^4}{10^4 + \frac{1}{2 \times 10^{-7} s}} \Rightarrow \boxed{T_{V_3} = \frac{4 \times 10^{-3} s + 1}{2 \times 10^{-3} s + 1}}$$

So, finally we get:

$$\Rightarrow T_V = T_{V_1} \cdot T_{V_3} = \left(\frac{2 \times 10^{-3} s}{2 \times 10^{-3} s + 1} \right) \left(\frac{4 \times 10^{-3} s + 1}{2 \times 10^{-3} s + 1} \right)$$


where by some simplification:

$$\boxed{T_V(s) = \frac{s(8 \times 10^{-6} s + 2 \times 10^{-3})}{(2 \times 10^{-3} s + 1)^2}}$$

$$\text{the poles: } (2 \times 10^{-3} s + 1)^2 = 0 \Rightarrow \boxed{\text{repetitive pole at } s_{p2} = -\frac{1}{2 \times 10^{-3}} = -500}$$

$$\text{the zeros: } s(8 \times 10^{-6} s + 2 \times 10^{-3}) = 0 \Rightarrow \boxed{z_1 = 0} \quad \& \quad \boxed{z_2 = -\frac{2 \times 10^{-3}}{8 \times 10^{-6}} = -0.25 \times 10^3}$$

Given:

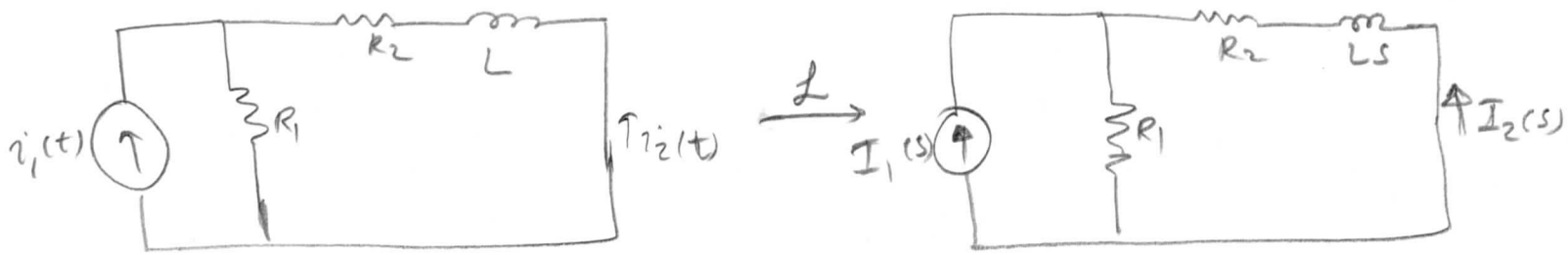

We note that in general w/ input: $i_1(t) = A \cos(\omega t)$, the steady-state output is of the form: $i_{ss,2}(t) = A |T(j\omega)| \cos(\omega t + \theta)$, where $\theta = \angle T(j\omega)$ and

$T(s)$ is mapping $I_1(s)$ to $I_2(s)$. Therefore, we compute $T(s)$:

$$\text{(from current-division eq'n): } T(s) = \frac{I_2(s)}{I_1(s)} = \frac{\frac{1}{R_2 + LS}}{\frac{1}{R_1} + \frac{1}{R_2 + LS}} \Rightarrow \boxed{T(s) = \frac{R_1}{LS + (R_1 + R_2)}}$$

Hence, given parameters: $R_1 = 1000 \Omega$, $R_2 = 4000 \Omega$, $L = 100 \text{ mH}$, we get:

$$T(s) = \frac{1000}{s + 5000} \Rightarrow \boxed{T(j\omega) = \frac{1000}{j\omega + 5000}} \quad (*)$$

- For the first part: $i_1 = 10 \cos(500t) \text{ mA}$, so we compute (*) at $\omega = 500$:

$$T(j\omega) = \frac{1000}{500j + 5000} \Rightarrow \begin{cases} |T(j\omega)| = \frac{1000}{\sqrt{500^2 + 5000^2}} = \frac{2}{\sqrt{101}} = 0.199 \\ \theta(j\omega) = \angle T(j\omega) = 0 - \tan^{-1}\left(\frac{500}{5000}\right) = -0.0997 \end{cases}$$

Therefore, for given: $i_1 = 10 \cos(500t) \text{ mA}$, the steady-state output is:

$$i_{ss,2} = 10 \times 0.199 \times \cos(500t - 0.0997)$$

↓

$$\boxed{i_{ss,2} = 1.99 \cos(500t - 0.0997) \text{ mA}}$$

- For the second part: $i_2 = 10 \cos(5000t) \text{ mA}$, so we compute (*) at $\omega = 5000$:

$$T(j\omega) = \frac{1000}{5000j + 5000} \Rightarrow \left\{ \begin{aligned} |T(j\omega)| &= \frac{1000}{\sqrt{5000^2 + 5000^2}} = \frac{1}{5\sqrt{2}} = 0.141 \\ \theta = \angle T(j\omega) &= -\tan^{-1}\left(\frac{5000}{5000}\right) = -0.7854 \end{aligned} \right.$$

Therefore, w/ $i_1 = 70 \cos(5000t) \text{ mA}$, we get:

$$i_{ss,2} = -10 \times 0.141 \times \cos(5000t - 0.7854)$$


$$\Downarrow$$

$$i_{ss,2} = -1.41 \cos(5000t - 0.7854) \text{ mA}$$

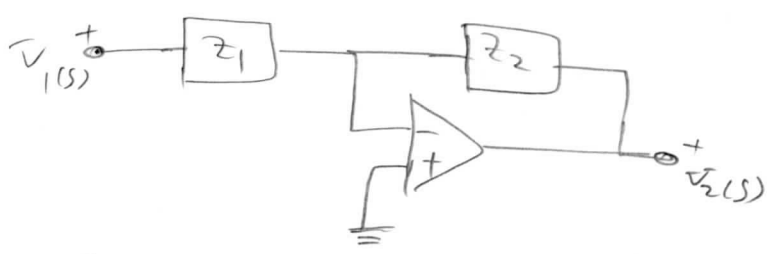11-53: [Difficult design, refer to page 10 for simpler design]

Goal: Design a circuit to realize: $T_V(s) = \pm \frac{1000s}{(s+500)(s+1000)}$

As an example, we can use inverting op-amp w/ the following setup:



where the transfer function:

$$T_V(s) = \frac{V_2}{V_1} = -\frac{Z_2}{Z_1}$$


So, if we choose: $Z_2 = \frac{1}{\frac{1}{R} + sC_2}$ & $Z_1 = R + \frac{1}{sC_1}$, we get:

$$T_V(s) = -\frac{Z_2}{Z_1} = -\frac{R}{RC_2s + 1} \cdot \frac{C_1s}{RC_1s + 1} = -\frac{1}{RC_2} \cdot \frac{1}{s + \frac{1}{RC_2}} \cdot \frac{s}{s + \frac{1}{RC_1}}$$

and so, by picking: $\begin{cases} R = 20k\Omega \\ C_1 = 100nF \\ C_2 = 50nF \end{cases}$ we have:



$$T_V(s) = -\frac{1000s}{(s+500)(s+1000)} \text{ which satisfies our goal!}$$

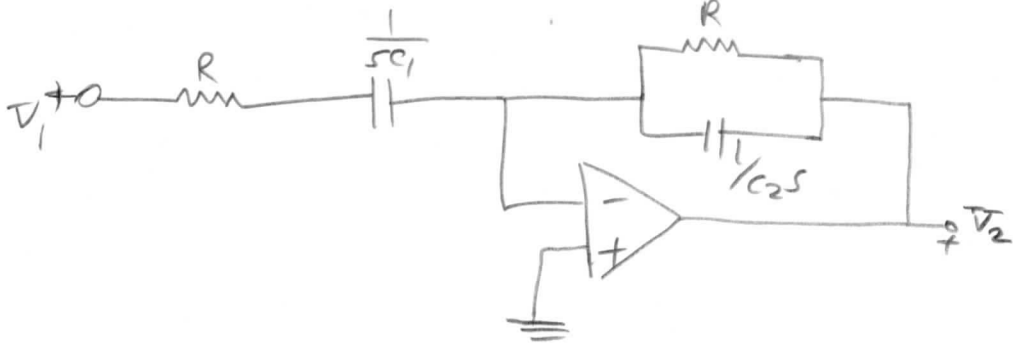where the final realization of Z_1 & Z_2 is drawn below:



11-58:

Given:

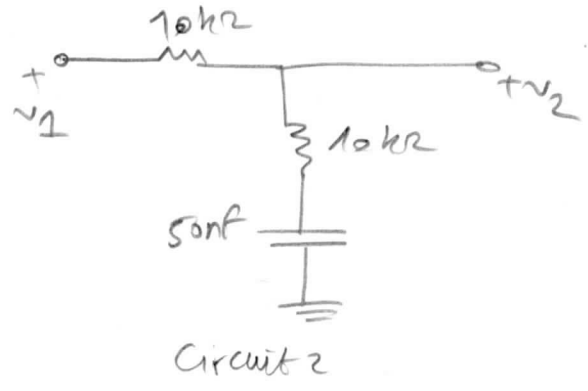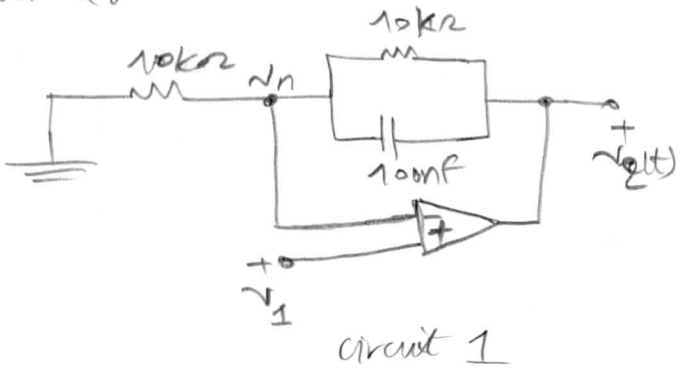

(a) For circuit 1:

$$v_n = v_p = v_1$$

where also we can find v_n from voltage-division:

$$v_1 = v_2 \left(\frac{10k}{10k + \frac{10k}{100nS}} \right) \Rightarrow \text{by some simplifications:}$$

$$v_1 = v_2 \left(\frac{10^5 + 10^4}{10^5 + 2 \times 10^4} \right) (*)$$

we want: $T_V(s) = \frac{v_2}{v_1} \xrightarrow{(*)} \boxed{T_V(s) = \frac{s + 2000}{s + 1000}}$

For circuit 2:

(P9)

It's simply a voltage-division:

$$V_2(s) = \frac{10k + \frac{1}{50nS}}{10k + 10k + \frac{1}{50nS}} V_1(s) \Rightarrow \text{by some simplification:}$$

$$V_2(s) = \frac{5 \times 10^{-4} s + 1}{10^{-3} s + 1} V_1(s) (**)$$

$$\text{we want: } T_V(s) = \frac{V_2(s)}{V_1(s)} \xrightarrow{(**)} T_V(s) = \frac{1}{2} \left(\frac{s + 2000}{s + 1000} \right)$$

(b) A $1k\Omega$ load connected to the output $V_2(t)$ in the 2nd circuit produces loading which will then change its value to a new $V_2'(t)$. Whereby, there is no change in the overall transfer T_{cm} when connecting a load to the output of an op-amp (recalling the basic properties of op-amps). Therefore, 1st circuit is preferred.

(c) Both circuits can be chosen if the load is of 50Ω . The reason is that $50\Omega \ll 10k\Omega$ which satisfies the rule $Z_{out} \ll Z_{in}$ to prevent loading in circuit 2. Whereby, circuit 1 is a non-inverting op-amp so any load can be connected to V_1 w/o changing the overall transfer T_{cm} , so circuit 1 is preferred.

(d) the claim is true, because the op-amp used is non-inverting op-amp.

11-53 [alternative & simpler design]:

Given: $T_V(s) = \frac{10kS}{(S+1k)(S+5k)}$, we will design a 3-stage cct:

$$T_V(s) = \underbrace{\left(\frac{k_1}{S+1k}\right)}_{1^{st} \text{ stage}} \underbrace{(k_2)}_{2^{nd} \text{ stage}} \underbrace{\left(\frac{k_3 S}{S+5k}\right)}_{3^{rd} \text{ stage}} \quad (*)$$

1st stage can be realized by using RC divider realization:

$$\frac{k_1}{S+1k} = \frac{k_1/S}{1+1k/S} \equiv \frac{z_2(s)}{z_1(s)+z_2(s)}$$

where we obtain: (equating numerator & denominator)

$$z_2(s) = k_1/S$$

$$z_1(s) = 1+1k/S - z_2(s) = 1+1k/S - k_1/S \Rightarrow z_1(s) = 1+(1000-k_1)/S$$

thus, for simplicity we pick: $k_1 = 1000 \Rightarrow \begin{cases} z_1 = 1 \Rightarrow R_1 = 1 \Omega \\ z_2 = \frac{1000}{S} \Rightarrow C_2 = \frac{1}{1000} F \end{cases}$

3rd stage can be realized by using RC divider realization as well:

$$\frac{k_3 S}{S+5k} = \frac{k_3}{1+5k/S} = \frac{z_4(s)}{z_3(s)+z_4(s)}$$

where we obtain:

$$z_4(s) = k_3$$

$$z_3(s) = 1+5k/S - z_4(s) = 1-k_3+5k/S$$

thus, for simplicity we pick: $k_3 = 1 \Rightarrow \begin{cases} z_4 = 1 \Omega \Rightarrow R_4 = 1 \Omega \\ z_3 = 5k/S \Rightarrow C_3 = \frac{1}{5000} F \end{cases}$

recalling (*) & our given transfer fn, we get the constraint:


(11)

$$\left. \begin{array}{l} k_1 k_2 k_3 = 10^6 \\ \text{where we have } k_1 = 1000 \\ \text{already chosen } k_3 = 1 \end{array} \right\} \Rightarrow \underline{k_2 = 10}$$

Hence, for the 2nd stage, we could use non-inverting opamp realization as follows:

$$\left. \begin{array}{l} k_2 = \frac{R_5 + R_6}{R_5} = 10 \\ \text{for simplicity, we pick: } R_5 = 1\Omega \end{array} \right\} \Rightarrow \underline{R_6 = 9\Omega}$$

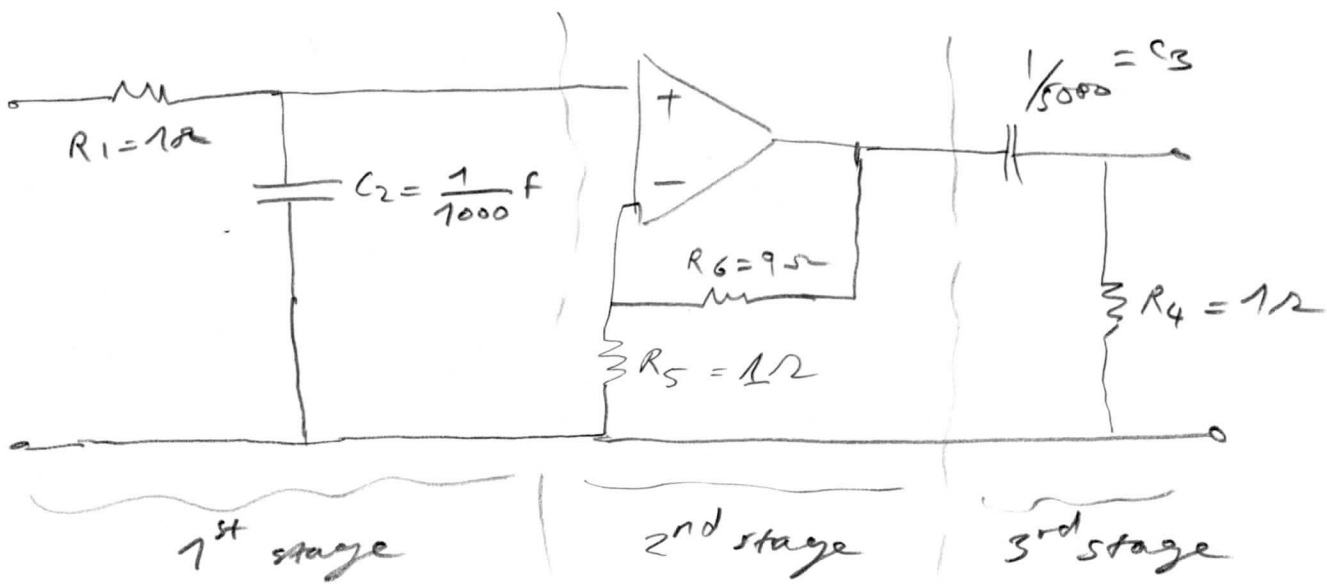Aggregating our analysis so far, the circuit looks like:



We note that this is a "prototype" i.e., the values for resistances & capacitors are not realistic, we use "magnitude scaling" concept to scale these values & get the realistic values:

Regarding 1st stage:

$$\left. \begin{array}{l} R_{\text{after}} = k_m R_{\text{before}} = k_m \times 1 \\ C_{\text{after}} = \frac{C_{\text{before}}}{k_m} = \frac{10^{-3}}{k_m} \end{array} \right\} \begin{array}{l} \text{pick} \\ k_m = 10^6 \end{array} \left\{ \begin{array}{l} R_{\text{after}} = 1\text{M}\Omega \checkmark \\ C_{\text{after}} = 1\text{pF} \checkmark \end{array} \right.$$


Regarding 2nd stage:

$$\left. \begin{aligned} R_{5\text{after}} &= k_m R_{5\text{before}} = k_m \times 1 \\ R_{6\text{after}} &= k_m R_{6\text{before}} = k_m \times 9 \end{aligned} \right\} \begin{array}{l} \text{pick} \\ k_m = 10^6 \end{array} \left\{ \begin{array}{l} R_{5\text{after}} = 1\text{M}\Omega \checkmark \\ R_{6\text{after}} = 9\text{M}\Omega \checkmark \end{array} \right.$$

Regarding 3rd stage:


$$\left. \begin{aligned} C_{3\text{after}} &= \frac{C_{3\text{before}}}{k_m} = \frac{2 \times 10^{-4}}{k_m} \\ R_{4\text{after}} &= k_m R_{4\text{before}} = k_m \times 1 \end{aligned} \right\} \begin{array}{l} \text{pick} \\ k_m = 10^4 \end{array} \left\{ \begin{array}{l} C_{3\text{after}} = 0.2\text{pF} \checkmark \\ R_{4\text{after}} = 10\text{k}\Omega \checkmark \end{array} \right.$$

So, the final realistic design will be:

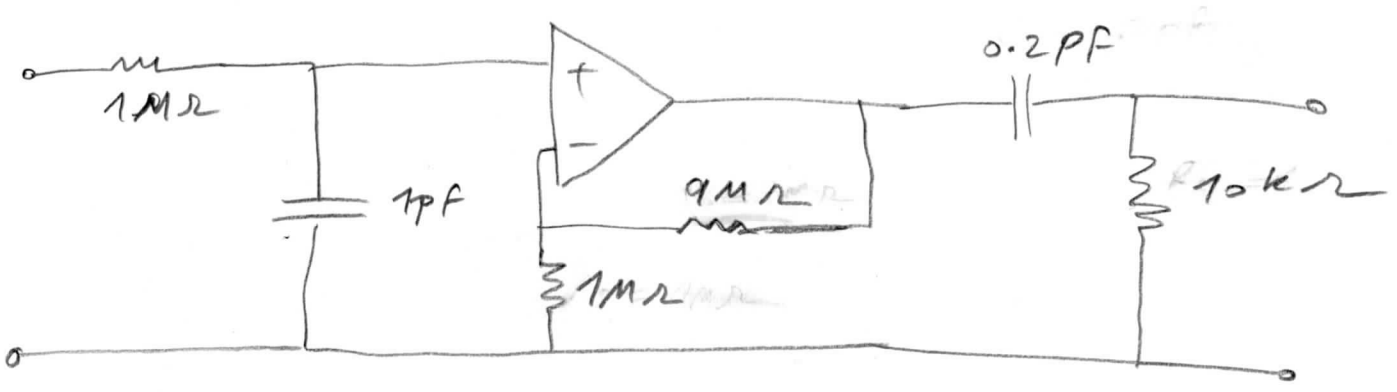

12-2

Given:

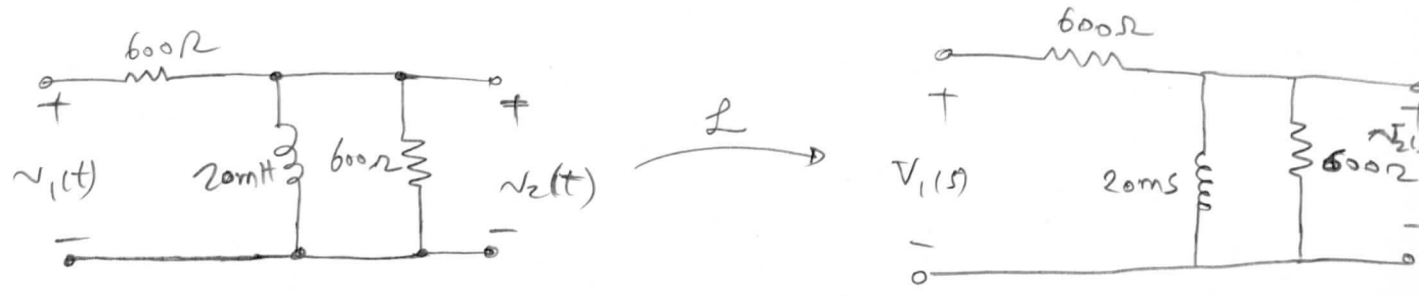

using voltage division we get:

$$V_2 = V_1 \left(\frac{2 \times 10^{-2} S \times 6 \times 10^2}{2 \times 10^{-2} S + 6 \times 10^2} \right)$$

$$\Rightarrow V_2 = V_1 \left(\frac{S}{2S + 30000} \right)$$

$$\Rightarrow T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{S}{2S + 3 \times 10^4}$$

(a)

DC-gain = $T_V(j0) = 0$


Infinite-freq gain = $\lim_{\omega \rightarrow \infty} T_V(j\omega) = \frac{1}{2}$

Cut-off frequency = $3 \times 10^4 / 2 = 1.5 \times 10^4$ rad/sec

It is a first order HIGH pass filter.

(b) Straight-line approximation of the gain:

$$|T(j\omega)| = |T(j \times 1.5 \times 10^4)| = \left| \frac{j \times 1.5 \times 10^4}{2j \times 1.5 \times 10^4 + 3 \times 10^4} \right| = \left| \frac{j}{2j + 2} \right| = 0.3536$$

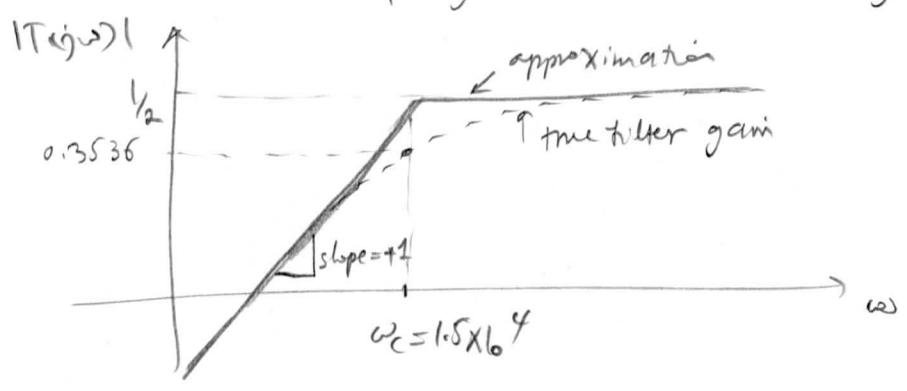

(c) Having computed $\omega_c = 1.5 \times 10^4$ rad/sec, we get:



$$|T(j0.5\omega_c)| = |T(j7500)| = \left| \frac{7500j}{2 \times 7500j + 3 \times 10^4} \right| = \left| \frac{j}{2j + 4} \right| = 0.2236$$

$$|T(j\omega_c)| = 0.3536 \text{ (Computed previously)}$$

$$|T(j2\omega_c)| = |T(j3 \times 10^4)| = \left| \frac{3 \times 10^4 j}{2 \times 3 \times 10^4 j + 3 \times 10^4} \right| = \left| \frac{j}{2j + 1} \right| = 0.4472$$

12-14

Given:

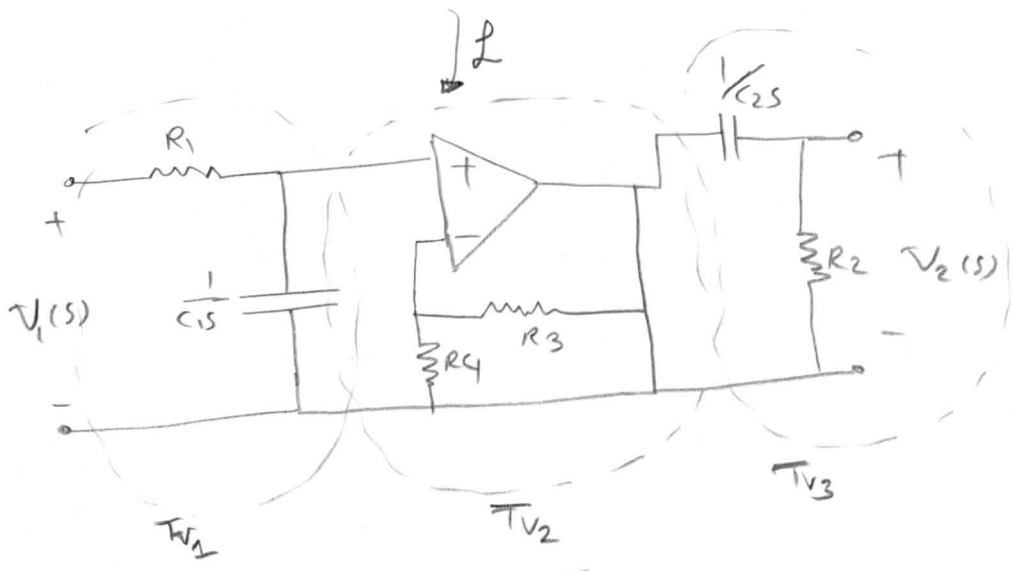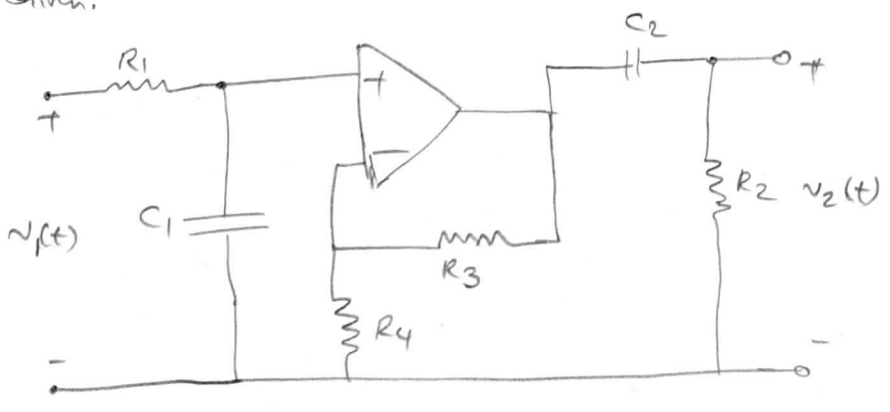

Chain rule: $T_V = \underbrace{T_{V1}}_{\text{voltage division}} \cdot \underbrace{T_{V2}}_{\text{non-inverting op-amp}} \cdot \underbrace{T_{V3}}_{\text{voltage-division}}$

So, we compute these 3 transfer fns:

$$T_{V1}(s) = \frac{1/Cs}{R1 + 1/Cs} = \frac{1}{R1Cs + 1}$$

$$T_{V_2}(s) = \frac{R_4 + R_3}{R_4}$$

$$T_{V_3}(s) = \frac{R_2}{R_2 + \frac{1}{C_2 s}} = \frac{R_2 C_2 s}{R_2 C_2 s + 1}$$

and so, we get:

$$T_V(s) = \left(\frac{1}{R_1 C_1 s + 1} \right) \left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{R_2 C_2 s}{R_2 C_2 s + 1} \right)$$

Therefore, the two cut-off frequencies are:

$$\left[\alpha_2 = \frac{1}{R_1 C_1} ; \alpha_1 = \frac{1}{R_2 C_2} \right] : \text{cut-off frequencies}$$

So, $R_1, C_1 ; R_2, C_2$ are controlling the cut-off frequencies.

Moreover, the gains are obtained as follows:

$$\left[K_1 = \frac{R_4 + R_3}{R_4} ; K_2 = \frac{1}{R_1 C_1} \right] : \text{high pass \& low pass gain}$$

which will match the pattern:

$$T_V(s) = \left(\frac{K_2}{s + \alpha_2} \right) \left(\frac{K_1 s}{s + \alpha_1} \right) = \left(\frac{\frac{1}{R_1 C_1}}{s + \frac{1}{R_1 C_1}} \right) \left(\frac{\left(\frac{R_4 + R_3}{R_4} \right) s}{s + \frac{1}{R_2 C_2}} \right)$$

and so, the pass band gain is:

$$\left[K_{PB} = \frac{|k_1 k_2|}{\alpha_2} = \frac{\left(\frac{R_4 + R_3}{R_4} \right) \left(\frac{1}{R_1 C_1} \right)}{\frac{1}{R_1 C_1}} = \frac{R_4 + R_3}{R_4} \right] : \text{passband gain}$$

We would like to have:

$$K_{PB} = 30 = \frac{R_4 + R_3}{R_4}$$

$$\alpha_1 = \frac{1}{R_2 C_2} = 100 \text{ rad/sec}$$

$$\alpha_2 = \frac{1}{R_1 C_1} = 2500 \text{ rad/sec}$$

subject to $R \geq 10 \text{ k}\Omega$, $C \leq 1 \mu\text{F}$

So, one set of parameters are:

- $R_1 = 10 \text{ k}\Omega$
- $R_2 = 10 \text{ k}\Omega$
- $R_3 = 100 \text{ k}$
- $R_4 = 11.11 \text{ k}$
- $C_1 = 0.04 \mu\text{F}$
- $C_2 = 1 \mu\text{F}$
- (they need not be unique).

12-56:


Design requirements:

- (1) low-pass filter
- (2) pass band gain: $9 \pm 10\%$
- (3) cut off freq: $90 \pm 10\%$ krad/sec
- (4) sensor driven the input w/ a $1 \text{ k}\Omega$ resistance & open-circuit voltage: $\pm 1.6 \text{ V}$

Evaluation criteria:

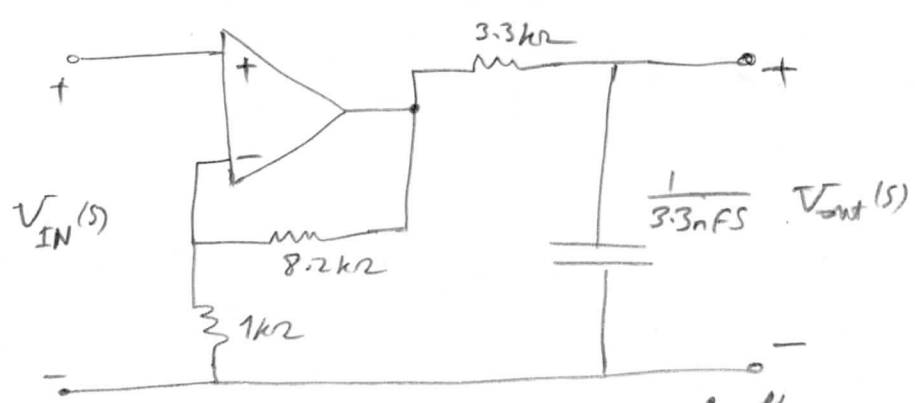- (5) Filter performance
- (6) parts count
- (7) use of standard parts
- (8) cost.

"First-order filter company" design: (already transformed into s-domain)



use chain rule to get the overall transfer fun:

non-inverting op amp:

$$T_{V_1} = \frac{z_1 + z_2}{z_1} \Rightarrow T_{V_1} = 9.2$$

$z_1 = 1 \text{ k}\Omega$
 $z_2 = 8.2 \text{ k}\Omega$

voltage divider:


$$T_{V_2} = \frac{1}{2.3 \times 10^3 + \frac{1}{3.3 \times 10^{-9} s}} = \frac{1}{(8.3)^2 \times 10^{-6} s + 1}$$

$$\Rightarrow T_V(s) = T_{V1} \times T_{V2} \Rightarrow T_V(s) = \frac{9.2 \times 10^6 / (3.3)^2}{s + \frac{10^6}{(3.3)^2}}$$

So, it is a low pass filter w/ $\left\{ \begin{array}{l} \text{cutoff freq} = 91.83 \text{ krad/sec} \\ \text{passband gain} = 9.2 \end{array} \right.$

So, it satisfies design requirements (1) - (3).

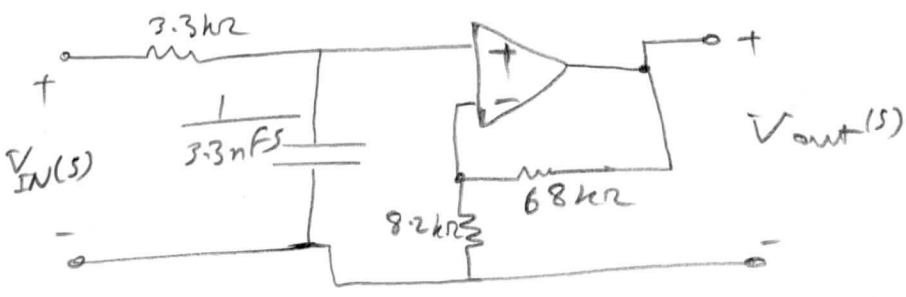"Simply Filters" design: (already transformed into s-domain)



In an analogous way to the previous circuit analysis:

$$T_{V1} = \frac{1}{3.3 \times 10^3 + \frac{1}{3.3 \times 10^{-9} s}} = \frac{1}{(3.3)^2 \times 10^{-6} s + 1} \Rightarrow T_V = \frac{9.29 \times 10^6 / (3.3)^2}{s + \frac{10^6}{(3.3)^2}}$$

$$T_{V2} = \frac{z_1 + z_2}{z_1} = \frac{68 + 8.2}{8.2} = 9.29$$

So, it is a low-pass filter w/ $\left\{ \begin{array}{l} \text{cutoff freq} = 91.83 \text{ krad/sec} \\ \text{passband gain} = 9.29 \end{array} \right.$

So, it satisfies design requirements (1) - (3)

Evaluation statement:

- they both have the same parts ~~but~~
- they both use standard elements
- The "Simply Filters, Ltd." design does not meet the specifications, the

Reason is that there is a source resistance of $1\text{ k}\Omega$, which is connected in series w/ $3.3\text{ k}\Omega$ resistance which will change the transfer fcn, where as it is not the case for "first-order filter compony", because source resistance of $1\text{ k}\Omega$ is in series w/ op-amp. (P18)

Moreover, in "first-order filter compony" the input voltage will not saturate as it is in $\pm 1.6\text{ V}$ range.
