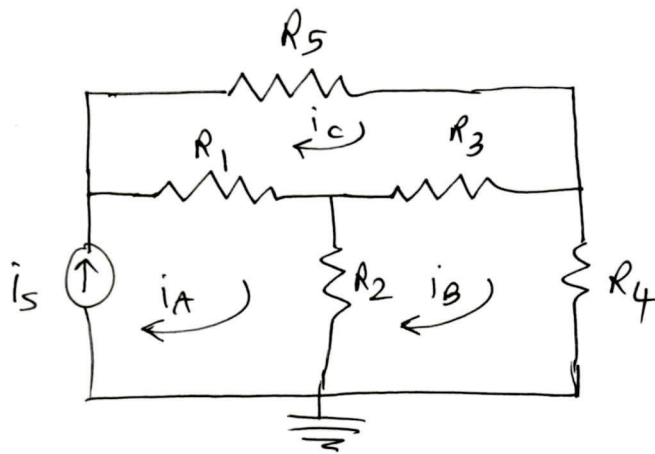


HW #4

MAE 140

Fall 2013

3-1



Using inspection:

$$\underbrace{\begin{bmatrix} 1 & 0 & 0 \\ -R_2 & R_2 + R_3 + R_4 & -R_3 \\ -R_1 & -R_3 & R_1 + R_3 + R_5 \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix}}_x = \underbrace{\begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}}_b$$


$$\Rightarrow Ax = b$$

Note that in loop A, we have  $i_A = i_s$   
so for that row of matrix we have;

$$\begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = i_s$$

3-5

(a)

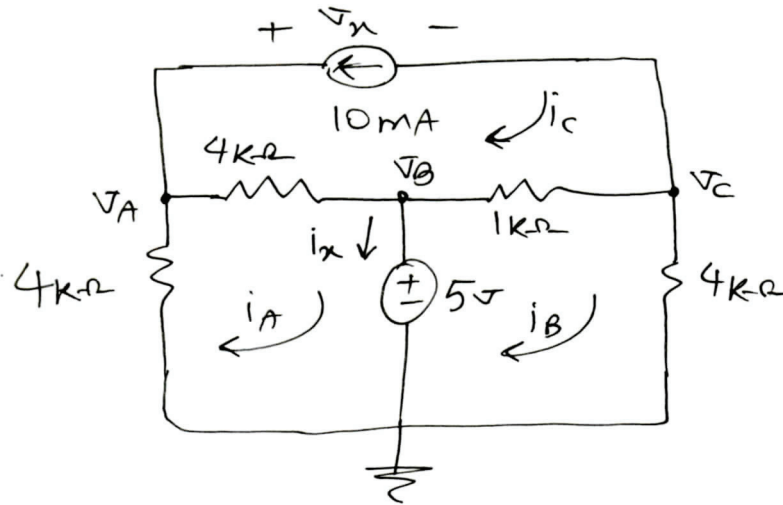

$$\begin{aligned} \text{Mesh A: } &\rightarrow \begin{bmatrix} (4+4) \times 10^3 & 0 & -4 \times 10^3 \\ 0 & (1+4) \times 10^3 & -1 \times 10^3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -5 \\ 5 \end{bmatrix} \\ \text{Mesh B: } &\rightarrow \end{bmatrix}$$

$$i_C = -10 \text{ mA}$$

$$\Rightarrow i_A = -5.62 \text{ mA}, i_B = -1 \text{ mA}$$

(b)

$$V_A = -4i_A = 22.5 \text{ V}$$

$$V_C = 4i_B = -4 \text{ V}$$


(c)

$$V_x = V_A - V_C = 22.5 + 4 = 26.5 \text{ V}$$

$$i_x = i_A - i_B = -4.62 \text{ mA}$$

3-6

a)

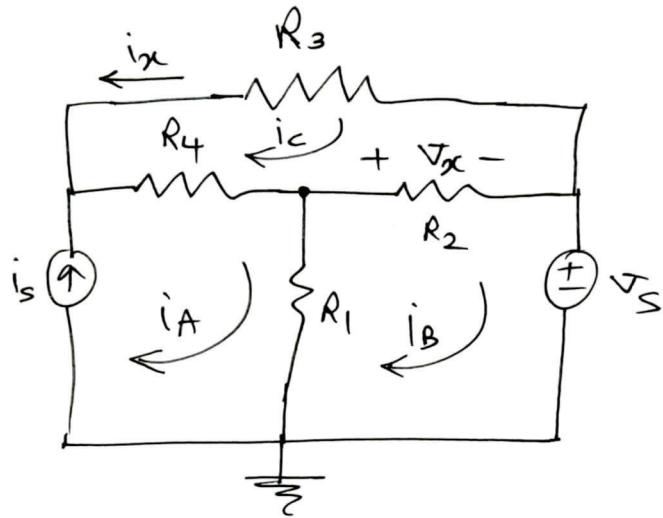


$$\begin{aligned} \text{Mesh B: } & \rightarrow \begin{bmatrix} -R_1 & R_1+R_2 & -R_2 \\ -R_4 & -R_2 & R_2+R_3+R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -V_s \\ 0 \end{bmatrix} \\ \text{Mesh C: } & \rightarrow \\ i_A & = i_s \end{aligned}$$


$$\begin{aligned} \text{(b)} \quad & i_A = i_s = 1 \text{ mA} \\ & R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega \\ & V_s = 25 \text{ V} \end{aligned} \quad \left. \vphantom{\begin{aligned} \text{(b)} \quad} \right\} \Rightarrow \begin{aligned} & i_C = 0.1 \text{ mA} \\ & i_B = -0.7 \text{ mA} \end{aligned}$$

$$\begin{aligned} \Rightarrow \quad & i_x = -i_C = -0.1 \text{ mA} \\ & V_x = 10(i_B - i_C) \\ & = 10(-0.7 - 0.1) = -8 \text{ V} \end{aligned}$$

a)

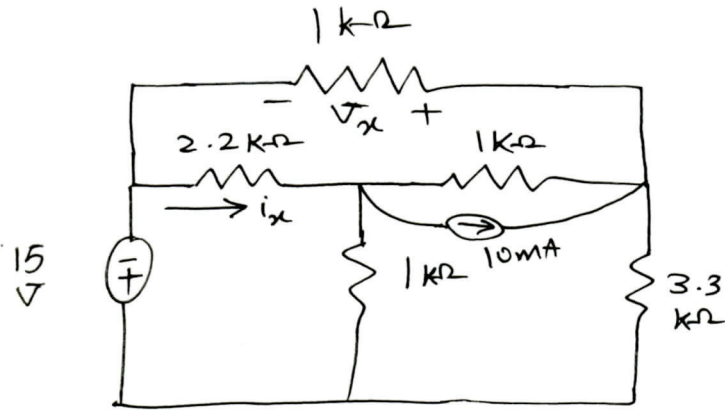

Source transformation

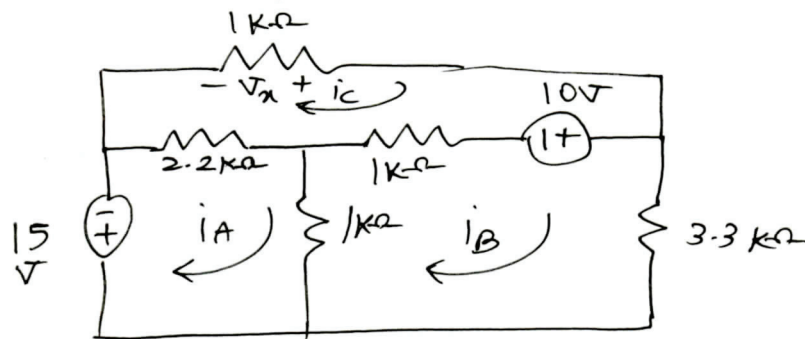


$$\begin{bmatrix} (2.2+1) \times 10^3 & -1 \times 10^3 & -2.2 \times 10^3 \\ -1 \times 10^3 & (1+1+3.3) \times 10^3 & -1 \times 10^3 \\ -2.2 \times 10^3 & -1 \times 10^3 & (1+1+2.2) \times 10^3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -15 \\ 10 \\ -10 \end{bmatrix}$$

b)

$$\left. \begin{aligned} i_A &= -11.29 \text{ mA} \\ i_B &= -1.89 \text{ mA} \\ i_C &= -8.74 \text{ mA} \end{aligned} \right\} \Rightarrow \begin{aligned} i_x &= i_A - i_C = -2.55 \text{ mA} \\ V_x &= -1 \times i_C = 8.74 \text{ V} \end{aligned}$$

3-12

a

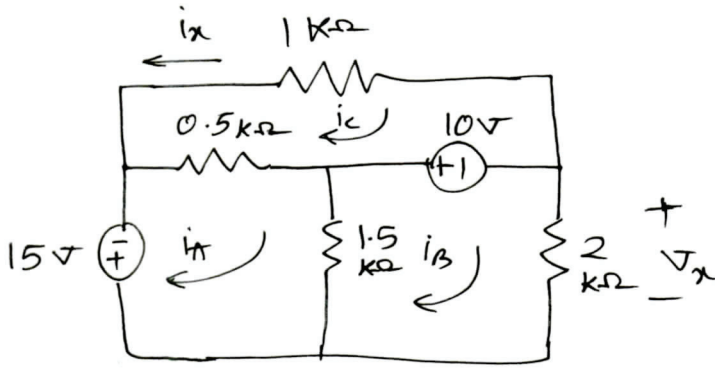


$$\begin{bmatrix} (0.5+1.5) \times 10^3 & -1.5 \times 10^3 & -0.5 \times 10^3 \\ -1.5 \times 10^3 & (1.5+2) \times 10^3 & 0 \\ -0.5 \times 10^3 & 0 & (1+0.5) \times 10^3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -15 \\ -10 \\ +10 \end{bmatrix}$$

b

$$i_A = -13.4 \text{ mA}$$

$$i_B = -8.6 \text{ mA}$$


$$i_C = +2.2 \text{ mA}$$

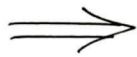

$$i_x = -i_c = -2.2 \text{ mA}$$

$$v_x = 2 i_B = -17.2 \text{ V}$$

3-16

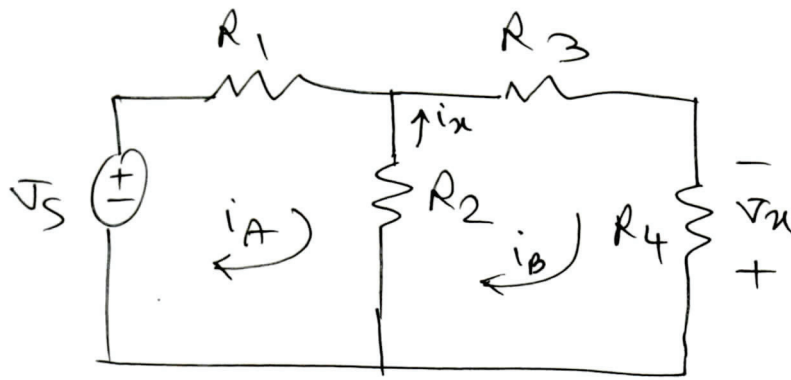

$$\textcircled{a} \quad \begin{cases} R_1 i_A + R_2 i_A - R_2 i_B - V_S = 0 \\ -R_1 i_A + R_2 i_B + R_3 i_B + R_4 i_B = 0 \end{cases}$$

$$\underbrace{\begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_1 & R_2 + R_3 + R_4 \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_A \\ i_B \end{bmatrix}}_x = \underbrace{\begin{bmatrix} +V_S \\ 0 \end{bmatrix}}_b$$


⑥

$$Ax = b \implies x = A^{-1}b$$

$$\textcircled{c} \quad i_x = i_B - i_A$$

$$v_x = -R_4 i_B$$

3-21

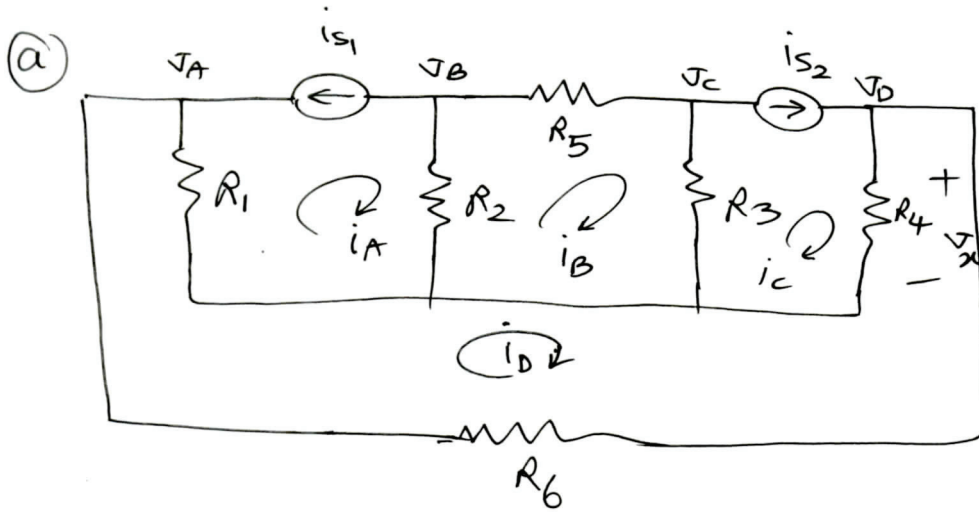

(b)


$$\begin{cases} i_A = -i_{s1} \\ -R_2 i_A + (R_2 + R_3 + R_5) i_B - R_3 i_C = 0 \\ i_C = i_{s2} \\ -R_1 i_A - R_4 i_C + (R_1 + R_4 + R_6) i_D = 0 \end{cases}$$

(c)

$$\left. \begin{aligned} R_1 = R_2 = R_3 = R_4 = 4 \text{ k}\Omega \\ R_5 = R_6 = 2 \text{ k}\Omega \\ i_{s1} = 80 \text{ mA} \\ i_{s2} = 40 \text{ mA} \end{aligned} \right\} \Rightarrow \begin{aligned} i_A &= -80 \text{ mA} \\ i_B &= -16 \text{ mA} \\ i_C &= 40 \text{ mA} \\ i_D &= -16 \text{ mA} \end{aligned}$$

$$v_x = 4(i_C - i_D) = 4(40 + 16) = 224 \text{ V}$$

3-26

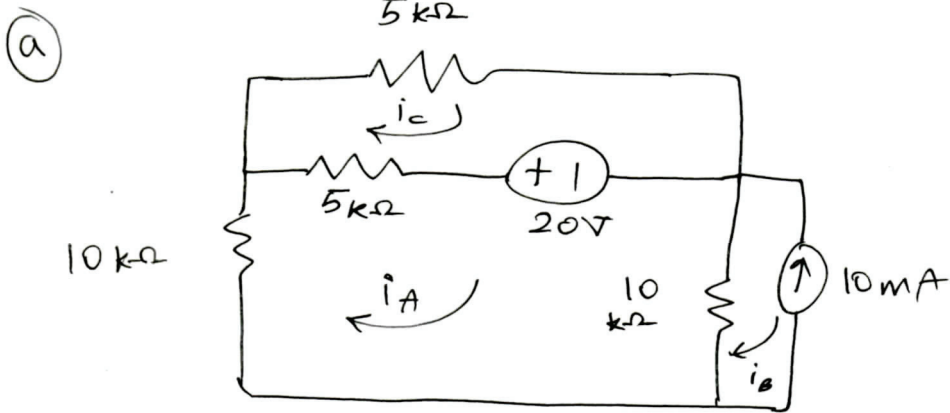

$$\begin{array}{l} \text{Mesh A:} \rightarrow \\ \text{Mesh C:} \rightarrow \end{array} \begin{bmatrix} (10+5+10) \times 10^3 & -10 \times 10^3 & -5 \times 10^3 \\ -5 \times 10^3 & 0 & 10 \times 10^3 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} -20 \\ 20 \end{bmatrix}$$



$$i_B = -10 \text{ mA}$$

(d)  $i_A = -4.88 \text{ mA}$


$$i_C = -0.44 \text{ mA}$$



3-36

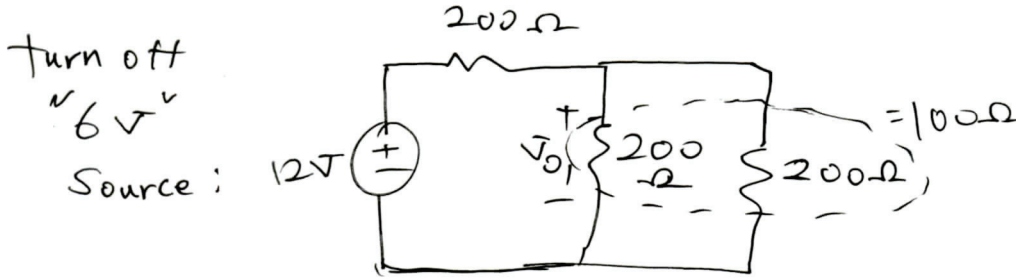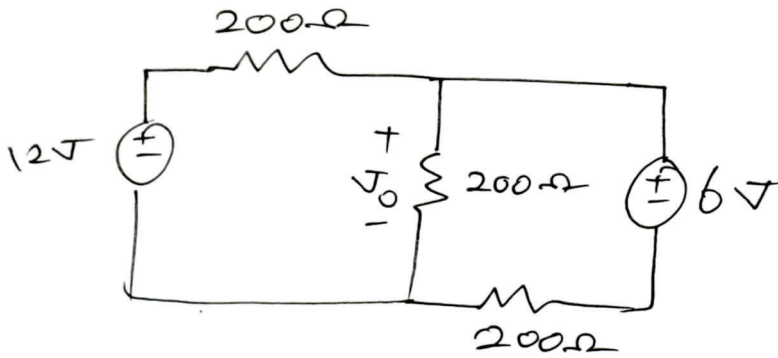

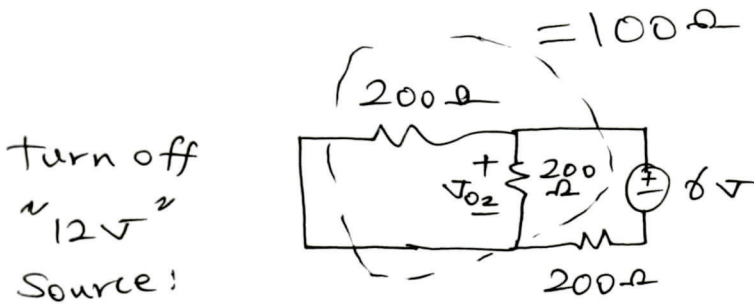
$$\Rightarrow V_{01} = \frac{100 \times 12}{200 + 100} = 4V$$




$$\Rightarrow V_{02} = \frac{100 \times 6}{200 + 100} = 2V$$

$$V_0 = V_{01} + V_{02} = 4 + 2 = 6V$$

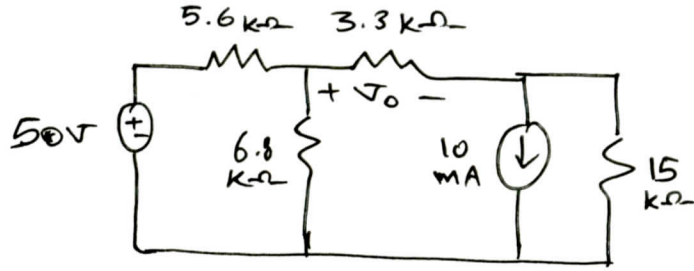

turn off  
current  
source:


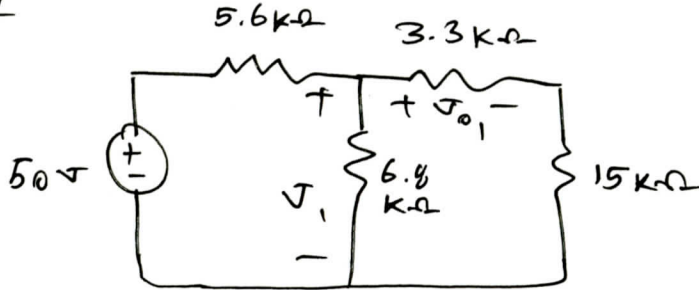


$$(3.3 \times 10^3 + 15 \times 10^3) \parallel (6.8 \times 10^3) = 4.95 \text{ k}\Omega$$

$$V_1 = \frac{4.95 \times 10^3 \times 50}{5.6 \times 10^3 + 4.95 \times 10^3} = 23.45 \text{ V}$$

$$V_{01} = \frac{3.3 \times 10^3 \times 23.45}{3.3 \times 10^3 + 15 \times 10^3} = 4.22 \text{ V}$$

turn off  
voltage  
source:

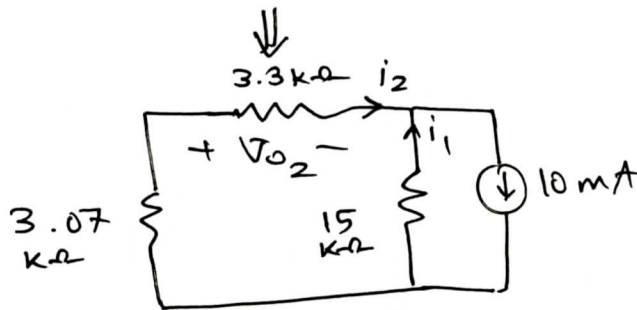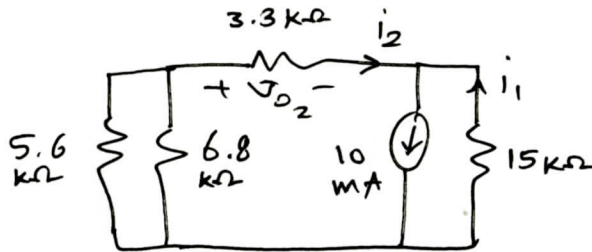

current division: 
$$i_2 = \frac{15 \times 10^3 \times 10 \text{ mA}}{15 \times 10^3 + 3.3 \times 10^3 + 3.07 \times 10^3} = 7.01 \text{ mA}$$

$$V_{02} = 3.3 \times 10^3 \times i_2 = 23.16 \text{ V}$$

$$V_0 = V_{01} + V_{02} = 4.22 + 23.16 = 27.38 \text{ V}$$