

MAE 140 HW 2 Solution

2-26



To find i_x and v_x , use the KVL to get the equation

$$\begin{aligned} -18V + v_1 + v_x &= 0 \\ -18V + i_x(22k\Omega) + i_x(68k\Omega) &= 0 \\ (22k\Omega + 68k\Omega) i_x &= 18V \end{aligned}$$

Can also use the voltage divider equation to get v_x

$$\hookrightarrow v_x = \left(\frac{68k\Omega}{22k\Omega + 68k\Omega} \right) 18V = 13.6V$$


$$i_x = \frac{18V}{90k\Omega} = 20mA$$

$$v_x = 20mA \cdot 68k\Omega = 13.6V$$

Can also use resistor in series equation to get i_x

$$\hookrightarrow i_x = \frac{18V}{R_{\text{equivalent}}} = \frac{18V}{22k\Omega + 68k\Omega} = 20mA$$

2-29

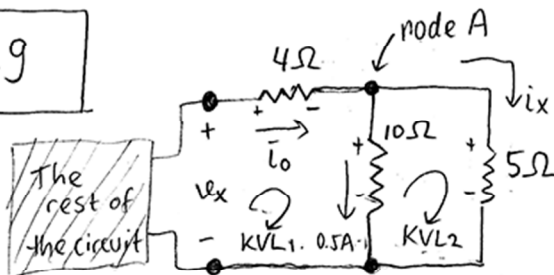

To find the v_x and i_x , use 2 KVL loops and one KCL at node A to get 3 equations:

$$\begin{aligned} \text{KVL}_1 &\rightarrow -v_x + i_0(4\Omega) + (0.5A)(10\Omega) = 0 \\ \text{KVL}_2 &\rightarrow (-0.5A)(10\Omega) + i_x(5\Omega) = 0 \\ \text{KCL}_A &\rightarrow i_0 - 0.5A - i_x = 0 \end{aligned}$$

$$\text{From KVL}_2 \rightarrow i_x = \frac{(0.5A)(10\Omega)}{5\Omega} = 1A$$


$$\text{From KVL}_1 \& \text{KCL}_2 \rightarrow -v_x + (0.5A + i_x)(4\Omega) + 5V = 0$$

$$v_x = 5V + (1.5A)(4\Omega) = 11V$$

3 Equations,

3 unknowns: i_0, i_x, v_x

2-31

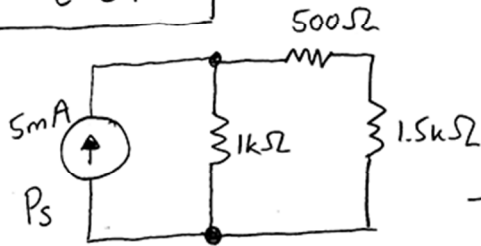

Find the power provided by the source (P_s)!
Use the series and parallel equivalent resistance to find the total resistance of the circuit.

→ 500Ω and $1.5k\Omega$ are in series

$$\hookrightarrow R_1 = 500\Omega + 1.5k\Omega = \underline{2k\Omega}$$

→ $1k\Omega$ and R_1 are in parallel

$$\begin{aligned} \hookrightarrow R_{total} &= 1k\Omega \parallel R_1 = \left(\frac{1}{1k\Omega} + \frac{1}{2k\Omega} \right)^{-1} \\ &= \left(\frac{3k\Omega}{2k\Omega^2} \right)^{-1} = \underline{\underline{\frac{2}{3}k\Omega}} \end{aligned}$$


Then the total power is =

$$P_s = (5mA)^2 (R_{total}) = (5mA)^2 \left(\frac{2}{3}k\Omega \right) \rightarrow \boxed{P_s = -0.01667 W}$$

(providing power)

2-35


Find R_{eq} for the circuit below!

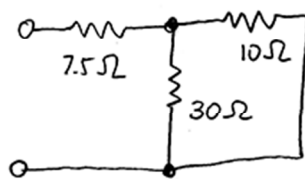

→ 30Ω and 10Ω are in parallel

$$\hookrightarrow R_1 = \left(\frac{1}{10\Omega} + \frac{1}{30\Omega} \right)^{-1} = \left(\frac{40\Omega}{300\Omega^2} \right)^{-1}$$
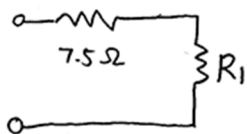
$$\underline{\underline{R_1 = 7.5\Omega}}$$




→ R_1 and 7.5Ω are in series

$$\hookrightarrow R_{eq} = R_1 + 7.5\Omega = 7.5\Omega + 7.5\Omega$$

$$\boxed{R_{eq} = 15\Omega}$$

2-37

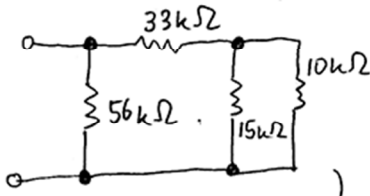Find the equivalent resistance R_{eq} !

→ 10 kΩ and 15 kΩ are in parallel

$$\hookrightarrow R_1 = \left(\frac{1}{10 \text{ k}\Omega} + \frac{1}{15 \text{ k}\Omega} \right)^{-1} = \left(\frac{25 \text{ k}\Omega}{150 \text{ k}\Omega^2} \right)^{-1} = \underline{6 \text{ k}\Omega}$$



→ 33 kΩ and R_1 are in series

$$\hookrightarrow R_2 = 33 \text{ k}\Omega + 6 \text{ k}\Omega = 39 \text{ k}\Omega$$


→ 56 kΩ and R_2 are in parallel

$$\hookrightarrow R_{eq} = \left(\frac{1}{56 \text{ k}\Omega} + \frac{1}{39 \text{ k}\Omega} \right)^{-1} = \left(\frac{95 \text{ k}\Omega}{2184 \text{ k}\Omega^2} \right)^{-1}$$


$$R_{eq} = 22.99 \text{ k}\Omega$$

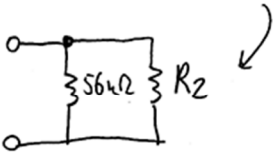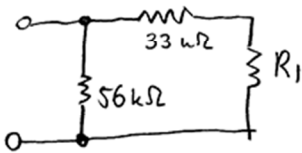

2-39

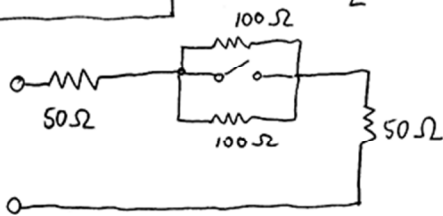Find R_{eq} when the switch is open and repeat for when switch is closed!

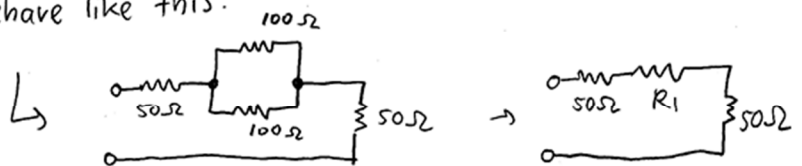If the switch is open, then the circuit will behave like this:




→ Both 100 Ω are in parallel

$$R_1 = \left(\frac{1}{100 \Omega} + \frac{1}{100 \Omega} \right)^{-1} = \left(\frac{200 \Omega}{10000 \Omega^2} \right)^{-1} = \underline{50 \Omega}$$


→ R_1 and both 50 Ω are in series

$$R_{eq} = 50 \Omega + 50 \Omega + 50 \Omega = \underline{150 \Omega}$$

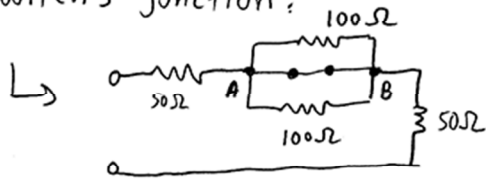If the switch is closed, then you will have a short circuit at the switch's junction.



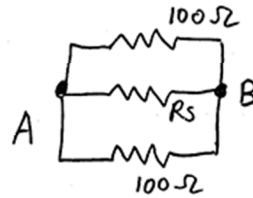So, we have a parallel junction from A to B



Where $R_s = 0\Omega$

Then we have the equivalent resistance across A-B


$$\hookrightarrow R_1 = \left(\frac{1}{100\Omega} + \frac{1}{100\Omega} + \frac{1}{R_s} \right)^{-1} = \left(\frac{200\Omega + R_s}{10000\Omega R_s} \right)^{-1} = \frac{10000\Omega R_s}{200\Omega + R_s}$$

with $R_s = 0$, we have $R_1 = \frac{0}{200\Omega} = 0\Omega$.

Then the equivalent resistance is $R_{eq} = 50\Omega + 0\Omega + 50\Omega \rightarrow R_{eq} = 100\Omega$

2-54

Use Voltage division to find V_x !

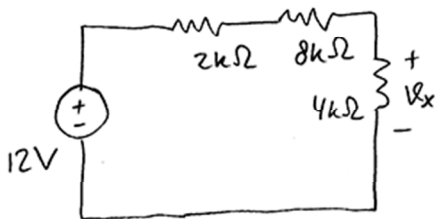


$$V_x = \left(\frac{4k\Omega}{2k\Omega + 8k\Omega + 4k\Omega} \right) 12V = \frac{4}{14} \cdot 12V$$

$$V_x = 3.43V$$

2-61


Find the range of values of V_o !

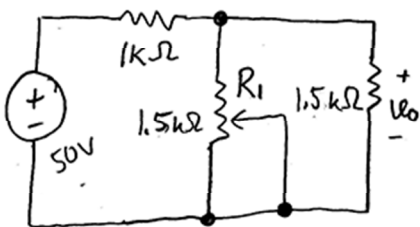


The resistor in the middle is called a potentiometer.

It has a variable resistance with a range from
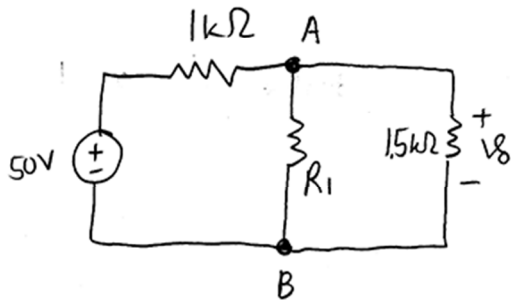
$$0\Omega \text{ to } 1.5k\Omega \rightarrow R_i \in [0, 1.5k\Omega]$$



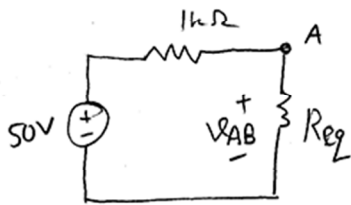V_0 is the voltage across node AB, so we can find V_0 by using the equivalent resistance across AB.



→ R_1 and $15k\Omega$ are parallel

$$\rightarrow R_2 = \left(\frac{1}{R_1} + \frac{1}{15k\Omega} \right)^{-1} = \left(\frac{R_1 + 15k\Omega}{R_1 \cdot 15k\Omega} \right)^{-1}$$

$$R_2 = \frac{R_1 \cdot 15k\Omega}{R_1 + 15k\Omega}$$

So, using voltage dividing equation, we can find $V_{AB} = V_0$

$$V_0 = \left(\frac{R_{eq}}{R_{eq} + 1k\Omega} \right) 50V = \left(\frac{\frac{R_1 \cdot 15k\Omega}{R_1 + 15k\Omega}}{\frac{R_1 \cdot 15k\Omega}{R_1 + 15k\Omega} + 1k\Omega} \right) 50V = \left(\frac{R_1 \cdot 15k\Omega}{R_1 \cdot 15k\Omega + (R_1 + 15k\Omega)(1k\Omega)} \right) 50V$$

$$V_0 = \left(\frac{R_1 \cdot 1.5k\Omega}{R_1 \cdot 2.5k\Omega + 1.5k\Omega^2} \right) 50V$$


At $R_1 = 0 \rightarrow V_0 = 0$

At $R_1 = 15k\Omega \rightarrow V_0 = \left(\frac{15k\Omega \cdot 1.5k\Omega}{15k\Omega \cdot 2.5k\Omega + 1.5k\Omega^2} \right) 50V$

→ $V_0 = 21.43V$

You can also use KCL and KVL, but it will be more complicated.

2-71

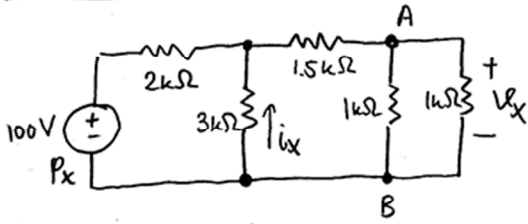
Use circuit reduction to find v_x , i_x , P_x !

v_x is the voltage difference across AB, so we should reduce the connection between AB.

→ Both $1k\Omega$ are parallel

$$\rightarrow R_1 = \left(\frac{1}{1k\Omega} + \frac{1}{1k\Omega} \right)^{-1} = \left(\frac{2k\Omega}{1k\Omega^2} \right)^{-1}$$

$$R_1 = 0.5k\Omega$$

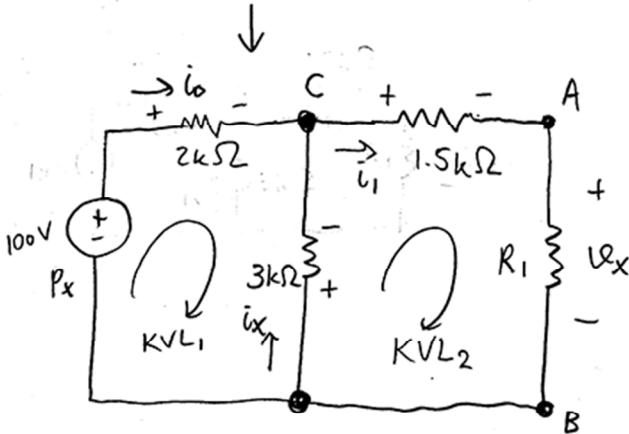

$$KVL_1 \rightarrow -100V + i_0(2k\Omega) + (-i_x)(3k\Omega) = 0$$

$$KVL_2 \rightarrow -i_x(3k\Omega) + i_1(1.5k\Omega) + i_1 R_1 = 0$$

$$KCL_C \rightarrow i_0 + i_x - i_1 = 0$$

$$i_0 = i_1 - i_x$$

So, we have:

$$KVL_2 \rightarrow i_1 = -i_x \left(\frac{3k\Omega}{1.5k\Omega + 0.5k\Omega} \right) = -\frac{3}{2} i_x$$

$$KVL_1 \text{ \& } KCL_C \rightarrow -100V + (i_1 - i_x)(2k\Omega) + (-i_x)(3k\Omega) = 0$$

$$i_1(2k\Omega) - i_x(5k\Omega) = 100V$$

$$-\frac{3}{2} i_x(2k\Omega) - i_x(5k\Omega) = 100V$$

$$\rightarrow i_x = \frac{-100V}{\left(\frac{3}{2} \cdot 2k\Omega + 5k\Omega \right)} = -12.5mA$$



$$\text{Find } i_1 \rightarrow i_1 = -\frac{3}{2} i_x = -\frac{3}{2} (-12.5mA) = +18.75mA$$

$$\text{Find } v_x \rightarrow v_x = i_1 R_1 = (18.75mA)(0.5k\Omega) \rightarrow v_x = 9.375V$$


$$\text{Find } i_0 \rightarrow i_0 = i_1 - i_x = 18.75mA - (-12.5mA) = 31.25mA$$

$$\rightarrow P_x = i_0(-100V) = (31.25mA)(100V) \rightarrow P_x = -3.125W \leftarrow \text{providing power}$$


2-75

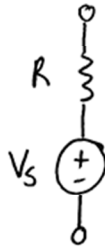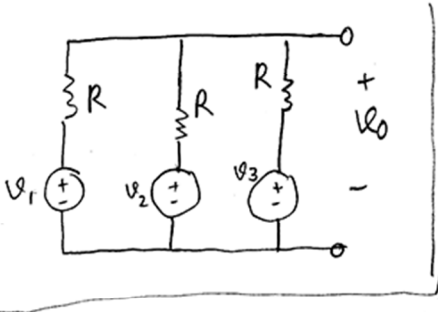Use source transformation to relate V_0 to v_1, v_2, v_3 !

is equivalent to:

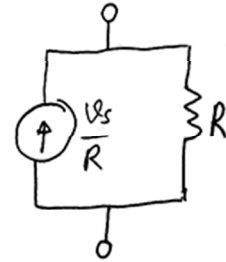


So, we have:

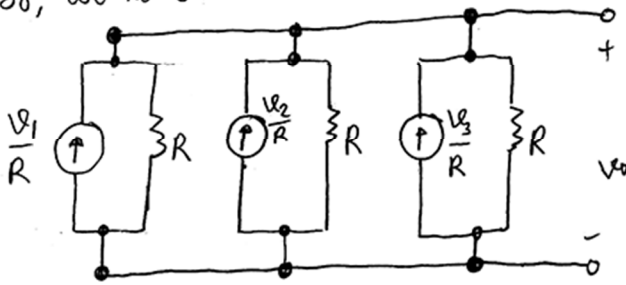All R are parallel, so we can reduce the circuit further.

$$R_1 = \left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R}\right)^{-1} = \left(\frac{3}{R}\right)^{-1} = \frac{R}{3}$$

Reduced further into

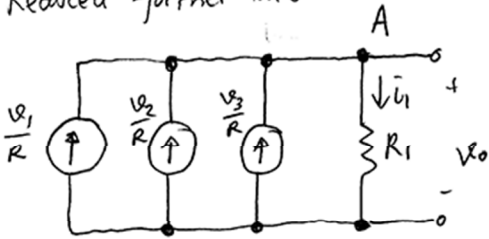

Using KCL at node A, we have

$$\hookrightarrow \frac{v_1}{R} + \frac{v_2}{R} + \frac{v_3}{R} - \bar{i}_1 = 0$$

$$\bar{i}_1 = \frac{1}{R}(v_1 + v_2 + v_3)$$

$$\text{Then, } V_{AB} = V_0 = \bar{i}_1 R_1 = \frac{1}{R}(v_1 + v_2 + v_3) \frac{R}{3}$$

 \hookrightarrow

$$V_0 = \frac{1}{3}(v_1 + v_2 + v_3)$$