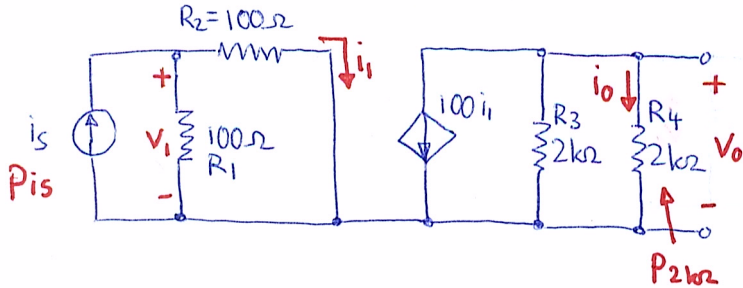


4.2 4.7 4.23 4.27 4.30 4.31 4.35 4.36 4.37 4.43

4.2 Find $\frac{V_0}{V_1}$ and $\frac{i_0}{i_s}$. For $i_s = 5 \text{ mA}$, find the power P_{i_s} and $P_{2k\Omega}$.



Using current division we find

$$i_0 = \frac{\frac{1}{R_4}}{\frac{1}{R_3} + \frac{1}{R_4}} (-100 i_1) = -50 i_1 \quad (1)$$

for the circuit on the RHS and

$$i_1 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} * i_s = \frac{1}{2} i_s \quad (2)$$

for the circuit on the LHS.

Substituting (2) in (1) we obtain $i_0 = -25 i_s \rightarrow \boxed{\frac{i_0}{i_s} = -25}$

Using Ohm's law we know that $V_0 = i_0 R_4 = -25 i_s \cdot 2k\Omega \quad (3)$

Since R_1 and R_2 are in parallel, the voltages across R_1 and R_2 are equal and thus

$$V_1 = V_2 = i_1 R_2 \quad (4)$$

Substituting (2) in (4)

$$V_1 = \frac{1}{2} R_2 i_s \rightarrow i_s = \frac{2V_1}{R_2} \quad (5)$$

Substituting (5) in (3)

$$V_0 = -25 \cdot 2k\Omega \cdot \frac{2V_1}{100\Omega} = -1000 V_1$$

$$\rightarrow \boxed{\frac{V_0}{V_1} = -1000}$$

The power supplied by i_s is

$$P_{i_s} = V \cdot i_s = i_s^2 R_{EQ} = i_s^2 \cdot \frac{100 \cdot 100}{100 + 100}$$

$$P_{i_s} = i_s^2 \cdot 50\Omega = \boxed{1.3 \text{ mW}}$$


The power delivered to the $2k\Omega$ resistor is

$$P_{2k\Omega} = i_0^2 R_4 = (-25 i_s)^2 2k\Omega$$


$$P_{2k\Omega} = \boxed{31.25 \text{ W}}$$

4.7

2/9

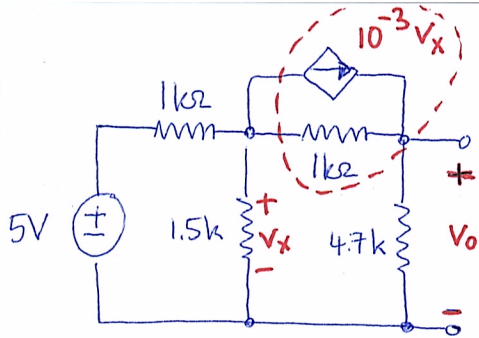

Using source transformation we obtain

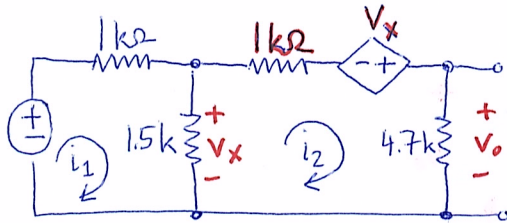

Mesh-current analysis yields

$$\begin{bmatrix} (1+1.5)k\Omega & -1.5k\Omega \\ -1.5k\Omega & (1.5+1+4.7)k\Omega \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5V \\ V_x \end{bmatrix}$$

$$V_x = Ri = 1.5k\Omega (i_1 - i_2)$$

Rearranging

$$\begin{bmatrix} (1+1.5)k\Omega & -1.5k\Omega \\ -(1.5+1.5)k\Omega & (1.5+1+4.7+1.5)k\Omega \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5V \\ 0 \end{bmatrix}$$


$$i_1 = 2.5217 \text{ mA}$$

$$i_2 = 0.8696 \text{ mA}$$

V_o can be computed using Ohm's law

$$V_o = i_2 4.7k\Omega = \boxed{4.087 \text{ V}}$$

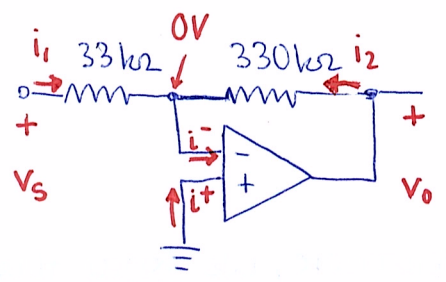4.23 Find the voltage gain for both circuits



From the properties of operational amplifiers learned in class we know that

$$i^- = 0 \text{ and } i^+ = 0$$

Thus, and since the '+' terminal is connected to ground, we know that the voltage potential at the '-' terminal is also 0V.

Consequently, we have

$$i_1 = -i_2 \quad \text{with } i_1 = \frac{V_s}{33k\Omega}$$

$$i_2 = \frac{V_o}{330k\Omega}$$

Substituting yields

$$\frac{V_s}{33k\Omega} = -\frac{V_o}{330k\Omega}$$

$$\frac{V_o}{V_s} = -\frac{330k\Omega}{33k\Omega} = \boxed{-10}$$

This is an inverting op-amp!
 $\rightarrow \frac{V_o}{V_s} = -\frac{R_f}{R_{in}} = -\frac{330k\Omega}{33k\Omega}$

With i^- and i^+ being equal to zero, the voltage at node A is equal to V_s .

Thus, we can write

$$i_1 = i_2 \quad \text{with } i_1 = \frac{V_s}{33k\Omega}$$

$$i_2 = \frac{V_o - V_s}{330k\Omega}$$


Substituting yields

$$\frac{V_s}{33k\Omega} = \frac{V_o - V_s}{330k\Omega}$$


$$10 = \frac{V_o}{V_s} - 1 \quad \text{so } \boxed{\frac{V_o}{V_s} = 11}$$

This is a non-inverting op-amp
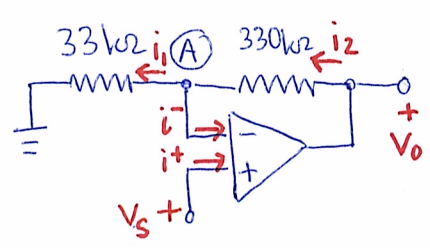
$$\rightarrow \frac{V_o}{V_s} = 1 + \frac{R_f}{R_{in}} = 1 + \frac{330k\Omega}{33k\Omega}$$



4.27

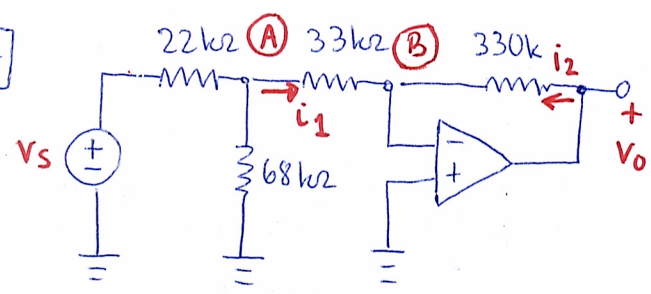

since $i^- = i^+ = 0$, $V_B = 0V$. Using KCL at node B we obtain

$$i_1 = -i_2 \quad \text{with} \quad i_1 = \frac{V_A - V_B}{33k\Omega} = \frac{V_A}{33k\Omega} \quad (1)$$

$$i_2 = \frac{V_0 - V_B}{330k\Omega} = \frac{V_0}{330k\Omega}$$

To find V_A we use voltage division. Note that the 33k and 68k resistors are in parallel, so the equivalent resistance is

$$R_{EQ} = \frac{33k\Omega \cdot 68k\Omega}{33k\Omega + 68k\Omega} = 22.2178k\Omega$$

Using voltage division we obtain

$$V_A = \frac{R_{EQ}}{R_{EQ} + 22k\Omega} V_s = 0.5025 V_s \quad (2)$$

Substituting (2) in (1) yields

$$\frac{V_A}{33k\Omega} = -\frac{V_0}{330k\Omega}$$

$$\frac{0.5025 V_s}{33k\Omega} = -\frac{V_0}{330k\Omega} \quad \rightarrow \quad \boxed{\frac{V_0}{V_s} = -5.025}$$


! Alternative way of solving this problem:

- Find Thevenin equivalent circuit (of everything to the left of (B))

→ open circuit yields Thevenin voltage

$$V_T = V_B = V_A = \frac{68k\Omega}{22k\Omega + 68k\Omega} V_s = 0.7556 V_s$$
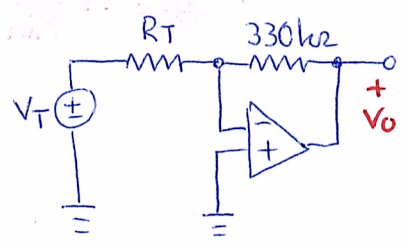
$$R_T = 33k\Omega + 22k\Omega \parallel 68k\Omega = 49.62k\Omega$$




This is an inverting op-amp!

$$V_0 = -\frac{330k\Omega}{R_T} V_T = -\frac{330k\Omega}{49.62k\Omega} \cdot 0.7556 V_s$$

$$\boxed{\frac{V_0}{V_s} = -5.025}$$

4.30

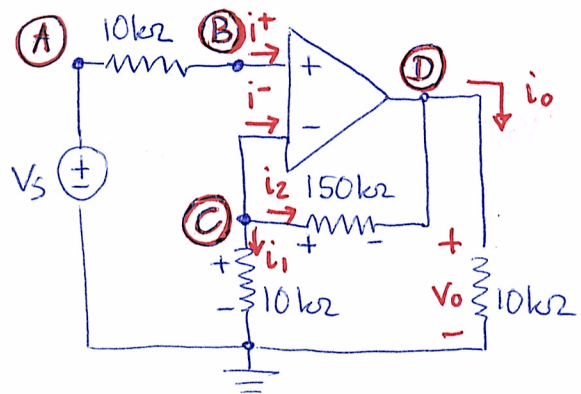

$V_{CC} = \pm 24V$

5/9

(a) Find V_o in terms of V_s

Remember that $i^+ = i^- = 0$ and thus, $V_B = V_C$.
 Also, since $i^+ = 0$ we have $V_B = V_A = V_s$.
 Using KCL we can write for node C

$$i_1 = -i_2$$

$$\frac{V_C}{10k\Omega} = -\frac{(V_C - V_D)}{150k\Omega} = \frac{V_D - V_C}{150k\Omega}$$

$$15 = \frac{V_D}{V_C} - 1 \quad \rightarrow \quad V_D = 16 V_C \quad \text{where } V_D = V_o, V_C = V_s$$

$V_o = 16 V_s$

(b) Find i_o for $V_s = 1V$ and $V_s = 3V$


$$i_o = \frac{V_o}{10k\Omega}$$

$$V_o(V_s = 1V) = 16V \quad \rightarrow \quad \boxed{i_o = 1.6mA}$$

$$V_o(V_s = 3V) = 48V > V_{CC} \quad \text{op-amp becomes saturated}$$

$$\text{and thus } V_o = 24V \quad \rightarrow \quad \boxed{i_o(V_s = 3V) = 2.4mA}$$

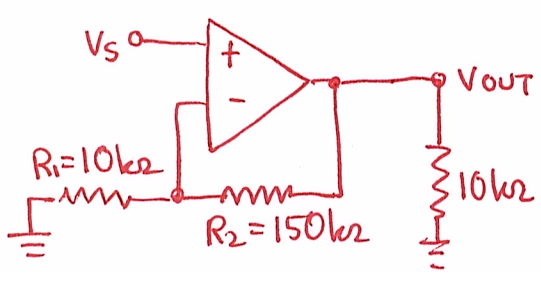
Note: This is a non-inverting op-amp! We know from class that



$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_s = 16 V_s$$

4.31

6/9

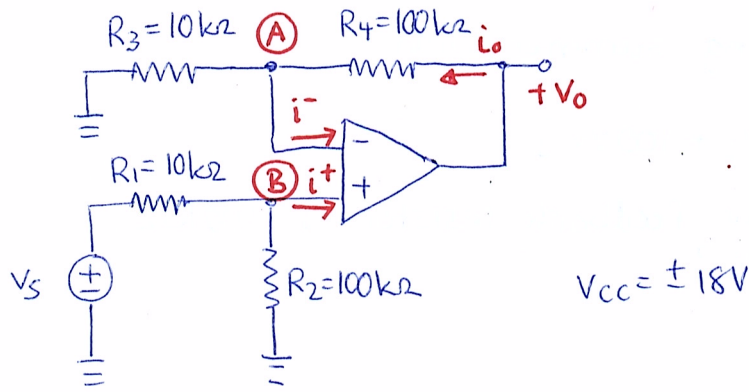

a) Find v_o in terms of v_s

For an ideal op-amp we have $i^- = i^+ = 0$ and $v_A = v_B$.
Using voltage division we can write

$$v_B = \frac{R_2}{R_1 + R_2} v_s = \frac{10}{11} v_s \quad (1)$$

$$v_A = \frac{R_3}{R_3 + R_4} v_o = \frac{1}{11} v_o \quad (2)$$

Substituting (1) in (2) using $v_A = v_B$ yields

$$v_o = 10 v_s$$

b) Find i_o for $v_s = 0.5V$ and $v_s = 2V$

$$i_o = \frac{v_o - v_B}{100k\Omega} = \frac{v_o - \frac{10}{11} v_s}{100k\Omega}$$

$$\bullet v_o(v_s = 0.5V) = 10 \cdot 0.5V = 5V$$

$$\rightarrow i_o(v_s = 0.5V) = 45.45 \mu A$$

$$\bullet v_o(v_s = 2V) = 20V$$

↑
 $20V > V_{cc}$ so the op-amp becomes saturated so
 $v_o(v_s = 2V) = 18V$

$$\rightarrow i_o(v_s = 2V) = \frac{(18 - \frac{20}{11})V}{100000 \frac{V}{A}} = 161.8 \mu A$$

Note that this is a voltage divider connected to a non-inverting op-amp. Thus we know that

$$v_o = \left(1 + \frac{R_4}{R_3}\right) v_B \quad \text{where} \quad v_B = \frac{R_2}{R_1 + R_2} v_s = \frac{10}{11} v_s$$


$$\rightarrow v_o = 11 \cdot \frac{10}{11} v_s = 10 v_s$$

4.35 Three-input inverting summer with

7/9

$$v_o = - [v_1 + 10v_2 + 100v_3]$$

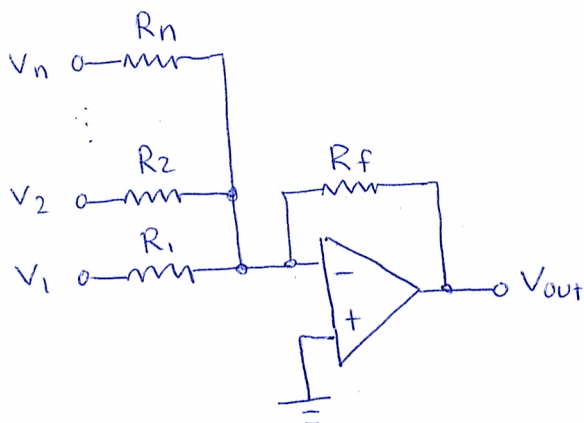The resistance of the feedback resistor is $100\text{ k}\Omega$.
What is R_1, R_2, R_3 ?




$$V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n} \right)$$

so

$$\begin{aligned} R_1 &= 100\text{ k}\Omega \\ R_2 &= 10\text{ k}\Omega \\ R_3 &= 1\text{ k}\Omega \end{aligned}$$

4.36

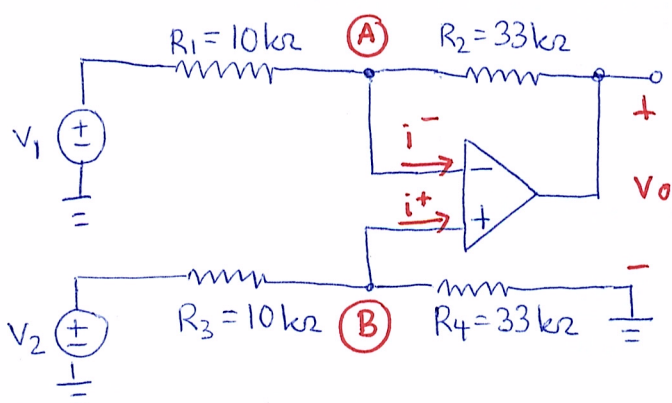

For an ideal op-amp
we have $i^- = i^+ = 0$
 $V_A = V_B$

To find v_o in terms of v_1 and v_2
we use the superposition principle.

(1) Turn off v_2 : Since both R_3 and R_4 are connected to ground we have $V_A = V_B = 0$ and the circuit acts like an inverting amplifier. Thus

$$v_{o,1} = -\frac{R_f}{R_{in}} v_1 = -\frac{R_2}{R_1} v_1 = -3.3 v_1$$

(2) Turn off v_1 : The circuit acts like a non-inverting amplifier with gain

$$v_{o,2} = \left(1 + \frac{R_2}{R_1} \right) V_B = 4.3 V_B$$

V_B can be obtained using voltage division


$$V_B = \frac{R_4}{R_3 + R_4} v_2 = \frac{33}{43} v_2$$

$$\Rightarrow v_o = v_{o,1} + v_{o,2} = -3.3 v_1 + 4.3 \frac{3.3}{4.3} v_2 = \boxed{3.3(v_2 - v_1) = v_o}$$

← This is a differential amplifier

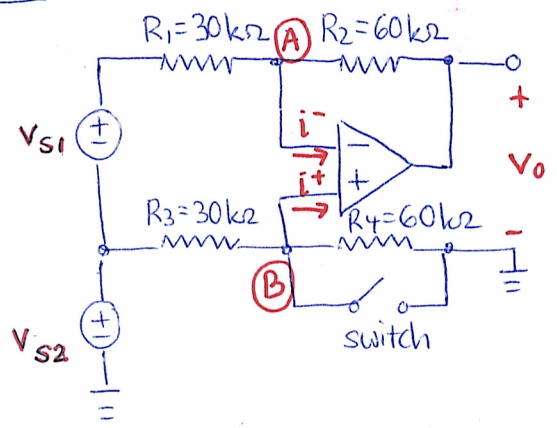4.37

Find v_o in terms of v_{s1} and v_{s2} for case 1: switch open
 case 2: switch closed



For an ideal op-amp we have


$$i^- = i^+ = 0$$

$$V_A = V_B$$

We use the superposition principle to find v_o in terms of v_{s1} and v_{s2} .

Case 1 (switch open)


1) Turn off v_2

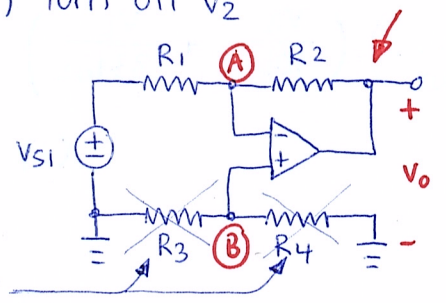

$v_B = 0$ so the circuit behaves like an inverting amplifier:

$$V_{o,1} = -\frac{R_2}{R_1} v_{s1} = -2 v_{s1}$$

2) Turn off v_1

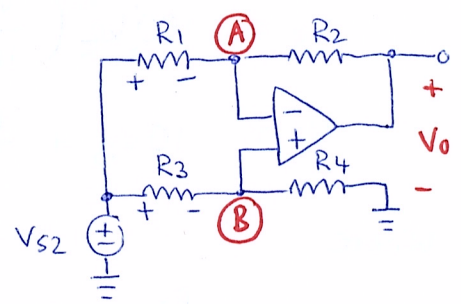


Since $V_A = V_B$ we have $V_{o,2} = 0$

$$\Rightarrow V_o = V_{o,1} + V_{o,2} = -2 v_{s1} \quad (\text{switch open})$$

Case 2 (switch closed) circuit behaves like an inverting amplifier!


1) Turn off v_2

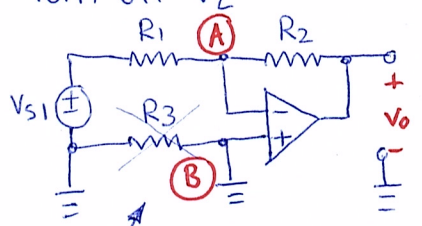

This circuit behaves like an inverting amplifier.

$$V_{o,1} = -\frac{R_2}{R_1} v_{s1} = -2 v_{s1}$$

2) Turn off v_1

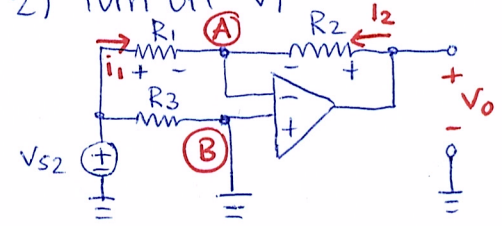


$V_A = V_B = 0V$ and using KCL we can write for node A

$$i_1 = -i_2$$

$$\frac{v_{s2}}{R_1} = -\frac{v_o}{R_2} \Rightarrow V_{o,2} = -\left(\frac{R_2}{R_1}\right)^2 v_{s2} = -2 v_{s2}$$

$$\Rightarrow V_o = V_{o,1} + V_{o,2} = -2(v_{s1} + v_{s2}) \quad (\text{switch closed})$$

4.43

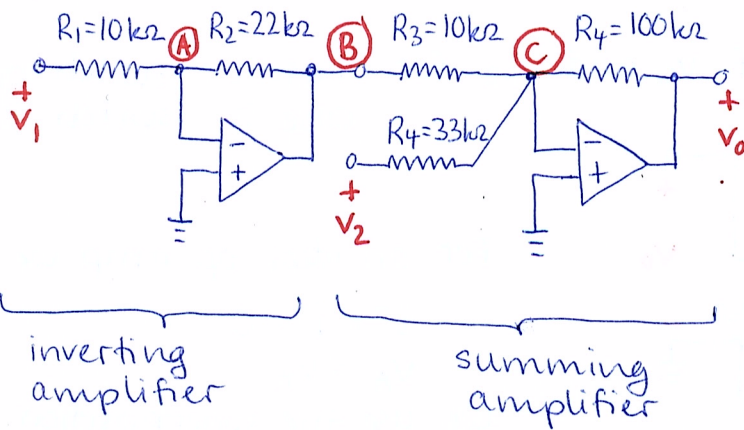

9/9

This is essentially an inverting amplifier connected to a summing amplifier.

Starting on the far right we can write

$$V_0 = -R_4 \left(\frac{V_B}{R_3} + \frac{V_2}{R_4} \right) = -100\text{k}\Omega \left(\frac{V_B}{10\text{k}\Omega} + \frac{V_2}{33\text{k}\Omega} \right)$$

$$V_0 = -10V_B - \frac{100}{33}V_2 \quad (1)$$

where

$$V_B = -\frac{R_2}{R_1}V_1 = -\frac{22}{10}V_1 \quad (2)$$

Substituting (2) in (1) yields

$$V_0 = 22V_1 - \frac{100}{33}V_2$$