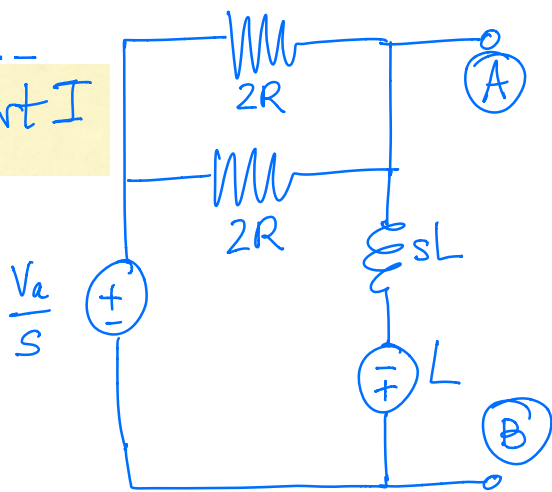


1. -
Part I




(Here, we have used
 $\mathcal{L}(v_a u(t)) = \frac{v_a}{s}$ and
the information that
 $i_L(0) = 1A$)

[+1 point for correct
initial condition;
+1 point for correct
overall circuit]

Part II

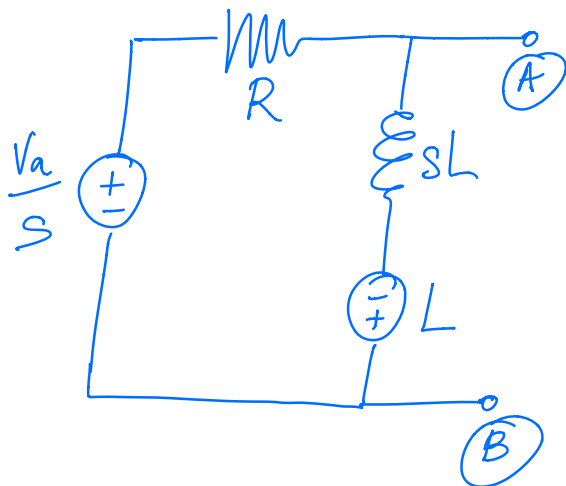To find the open circuit voltage, we
combine the two $2R$ impedances in parallel to
obtain



[+0.5 point]

The voltage drop across the sL -impedance is, by
voltage division,

$$V_{sL}(s) = \frac{sL}{R+sL} \left(\frac{V_a}{s} + L \right)$$


[+0.5 point]

Therefore,

$$\begin{aligned}
 V_{AB}(s) &= V_{sL}(s) - L = \frac{sL}{R+sL} \frac{V_a}{s} + L \left(\frac{sL}{R+sL} - 1 \right) \\
 &= \frac{V_a L}{R+sL} + L \frac{\cancel{sL} - R - \cancel{sL}}{R+sL} = \frac{L(V_a - R)}{R+sL} \quad [+1 \text{ point}]
 \end{aligned}$$

Part III

We have

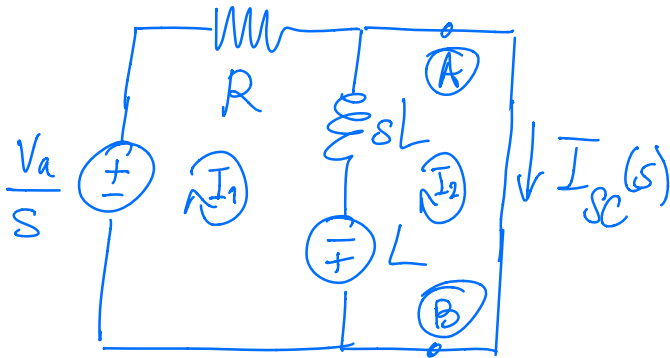

We set up mesh current analysis equations to obtain the short-circuit current

$$\text{Mesh 1: } R I_1(s) + sL (I_1(s) - I_2(s)) = \frac{V_a}{s} + L$$

$$\text{Mesh 2: } sL (I_2(s) - I_1(s)) = -L \quad [+1 \text{ point}]$$

$$\text{Therefore, } R I_1(s) = \frac{V_a}{s} \Rightarrow I_1(s) = \frac{V_a}{sR}$$

$$\text{And hence } sL I_2(s) = -L + \cancel{sL} \cdot \frac{V_a}{\cancel{sR}} \Rightarrow$$

$$\Rightarrow I_2(s) = \frac{-R + V_a}{R_s} = I_{sc}(s) \quad [+1 \text{ point}]$$


Part IV

Given that we know $V_{oc}(s)$ (from Part II) and $I_{sc}(s)$ (from Part III), we conclude

$$Z_{AB}(s) = \frac{V_{oc}(s)}{I_{sc}(s)} = \frac{L(V_a - R)}{R + sL} \cdot \frac{R_s}{V_a - R} = \frac{RLs}{R + sL}$$

[+1 point]

Therefore,

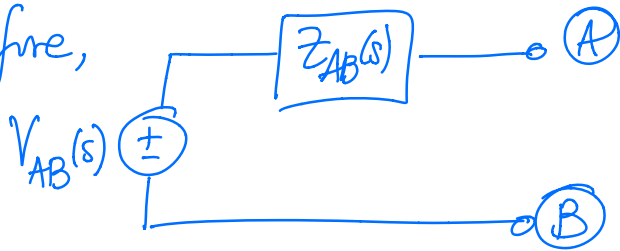

[+1 point]

Part V

We have

$$V_{AB}(s) = \frac{L(V_a - R)}{R + sL}$$

Zero-input corresponds to zeroing the input (i.e., $V_a = 0$), so

$$V_{zi}(s) = \frac{-RL}{R + sL}$$

[+0.5 point]

Therefore,

$$V_{zs}(s) = \frac{LV_a}{R + sL}$$

[+0.5 point]

So the break-down is

$$V_{AB}(s) = \underbrace{\frac{LV_a}{R + sL}}_{zs} + \underbrace{\frac{-RL}{R + sL}}_{zi}$$

The forced response corresponds to the terms with the same poles as the input $\frac{V_a}{s}$.
Looking at our expression for $V_{AB}(s)$, we deduce


$$V_{fr}(s) = 0 \quad \text{and} \quad V_{nr}(s) = V_{AB}(s).$$

[+0.5 point]


[+0.5 point]

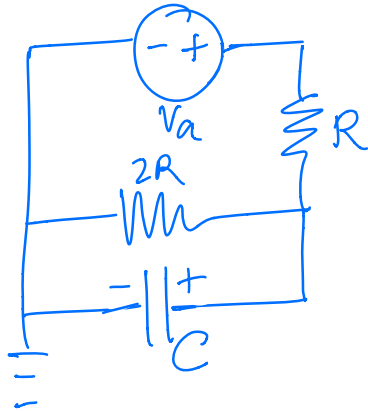2.- Part I

Since the circuit is kept in position A for a very long time, we need to consider



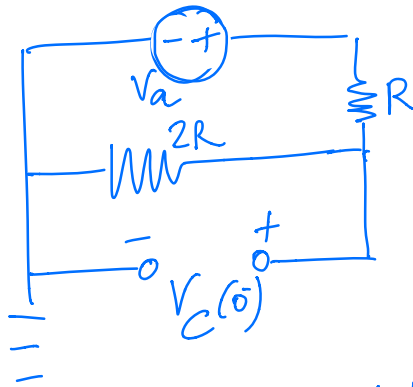V_a is constant. Under DC excitation, we know the capacitor behaves like an open circuit.
Therefore, we are looking at [+1 point]




By looking at the plot, we see that $V_c(0^-)$ is equal to the voltage drop across the $2R$ resistor.
Using voltage division, [+1 point]

$$V_c(0^-) = \frac{2R}{2R+R} V_a = \frac{2}{3} V_a$$

Part II

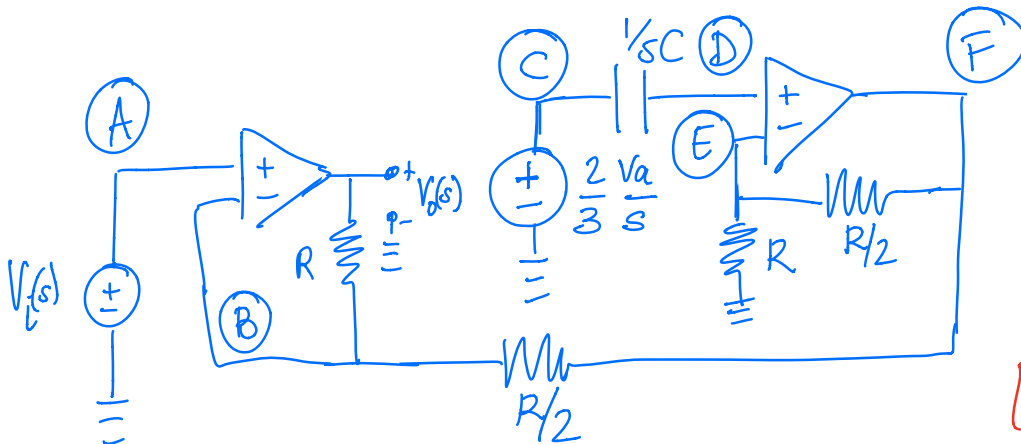We use the initial condition to transform the circuit into the s-domain.



[+1 point]

We use nodal analysis to express the output response transform $V_o(s)$ as a function of $V_i(s)$ and V_a .

Looking at the plot, we know

[+0.5 point]

$$V_A(s) = V_i(s)$$

$$V_C(s) = \frac{2}{3} \frac{V_a}{s} = V_D(s) \quad (\text{b/c of } I_P = 0) \quad \text{[+0.5 point]}$$

- ideal op-amp - point

Because of ideal op-amp conditions,

[+0.5 point]

$$V_A(s) = V_B(s)$$

$$V_D(s) = V_E(s)$$

[+0.5 point]

We only need to write KCL for nodes \textcircled{B} and \textcircled{E} .

KCL @ (B)

$$\frac{1}{R}(V_B(s) - V_O(s)) + \frac{2}{R}(V_B(s) - V_F(s)) = 0 \quad [+0.5 \text{ point}]$$

KCL @ (E)

$$\frac{1}{R}(V_E(s)) + \frac{2}{R}(V_E(s) - V_F(s)) = 0 \quad [+0.5 \text{ point}]$$

Solving the last equation,

$$V_F(s) = \frac{3}{2} V_E(s) = \frac{3}{2} V_D(s) = \frac{\cancel{3}}{\cancel{2}} \cdot \frac{\cancel{2}}{\cancel{3}} \frac{V_a}{s} = \frac{V_a}{s}$$

Solving KCL @ (B),

$$\begin{aligned} V_O(s) &= 3V_B(s) - 2V_F(s) = \\ &= 3V_i(s) - 2 \frac{V_a}{s} \end{aligned} \quad [+1 \text{ point}]$$

Part III

$$\text{With } V_i(s) = \frac{1}{(s+2)^2} \text{ and } V_a = 2, \quad [+1 \text{ point}]$$

we have

$$V_O(s) = \frac{3}{(s+2)^2} - \frac{4}{s} \quad [+1 \text{ point}]$$

Therefore,

$$v_o(t) = (3te^{-2t} - 4)u(t) \quad [+1 \text{ point}]$$

Part IV

$$(V_o)_{fr}(t) = (3te^{-2t})u(t)$$

[+0.5 extra
point]

$$(V_o)_{nr}(t) = -4u(t)$$

[+0.5 extra
point]

$$(V_o)_{zs}(t) = (3te^{-2t})u(t)$$

[+0.5 extra
point]

$$(V_o)_{zi}(t) = -4u(t)$$

[+0.5 extra
point]

3. Part I

$$T(j\omega) = \frac{500j\omega}{-\omega^2 + 520j\omega + 10000}$$

$$|500j\omega| = 500\omega$$

$$\angle 500j\omega = \frac{\pi}{2}$$

} [+0.5 point]

$$|10^4 - \omega^2 + 520j\omega| = \sqrt{(10^4 - \omega^2)^2 + 520^2\omega^2} =$$

$$= \sqrt{10^8 + \omega^4 - 2 \cdot 10^4\omega^2 + 270400\omega^2}$$

$$= \sqrt{10^8 + \omega^4 + 250400\omega^2}$$

$$= \sqrt{(25 \cdot 10^4 + \omega^2)(4 \cdot 10^2 + \omega^2)}$$

} [+0.5 point]

$$\angle(10^4 - \omega^2 + 520j\omega) = \arctan \frac{520\omega}{10^4 - \omega^2}$$

Therefore,

$$|T(j\omega)| = \frac{500\omega}{\sqrt{(25 \cdot 10^4 + \omega^2)(4 \cdot 10^2 + \omega^2)}}$$

[+1 point]

$$\angle T(j\omega) = \frac{\pi}{2} - \arctan \frac{520\omega}{10^4 - \omega^2}$$

[+1 point]

Part II

DC gain corresponds to $\omega = 0$

$$|T(j0)| = \frac{0}{10^4} = 0$$

[+0.5 point]

∞ -freq gain corresponds to $\omega = \infty$

$$|T(j\infty)| = \lim_{\omega \rightarrow \infty} |T(j\omega)| = 0$$

[+0.5 point]

The corresponding values of the phase function

$$\angle T(j0) = \frac{\pi}{2} - 0 = \frac{\pi}{2}$$

[+0.5 point]

$$\angle T(j\infty) = \frac{\pi}{2} - \pi = -\frac{\pi}{2}$$

[+0.5 point]

Based on the fact that $|T(j0)| = 0 = |T(j\infty)|$, one might suspect we are dealing with a bandpass filter. In fact,

$$T(s) = \underbrace{\frac{s}{s+20}}_{\text{high-pass}} \cdot \underbrace{\frac{500}{s+500}}_{\text{low-pass}}$$

Cut-off frequency of high-pass is $\omega_1 = 20 \text{ rad/s}$

Cut-off frequency of low-pass is $\omega_2 = 500 \text{ rad/s}$

[This would also be ok: derive $|T(j\omega)|$ to find

$T_{\max} = \frac{25}{26}$ at $\omega_{\max} = 100$, and then setting



$|T(j\omega_c)| = \frac{25}{26} \cdot \frac{1}{\sqrt{2}}$, which gives solutions

$$\omega_{c1} \approx 18.57$$


$$\omega_{c2} \approx 538.57$$

[+1 point]

Part III Sketch of plots

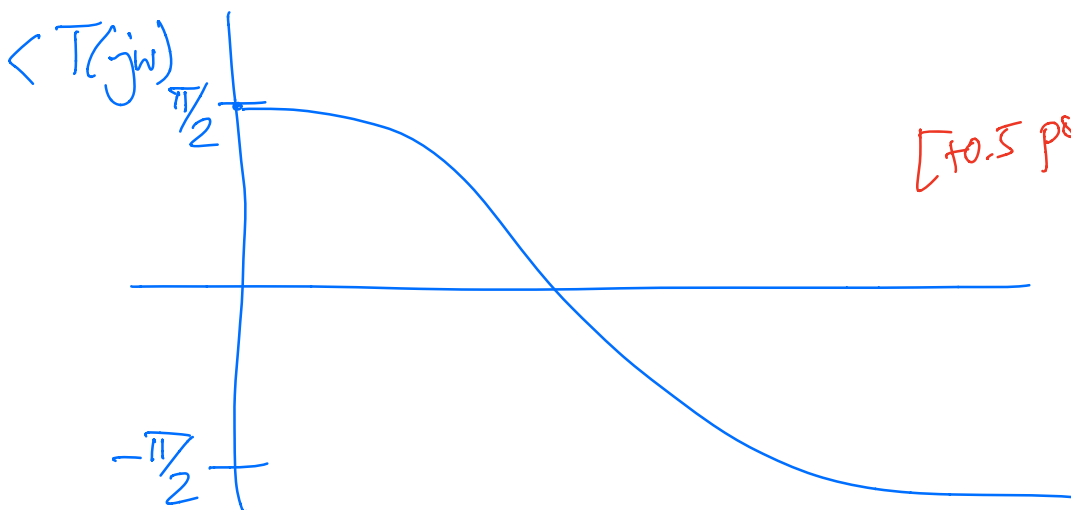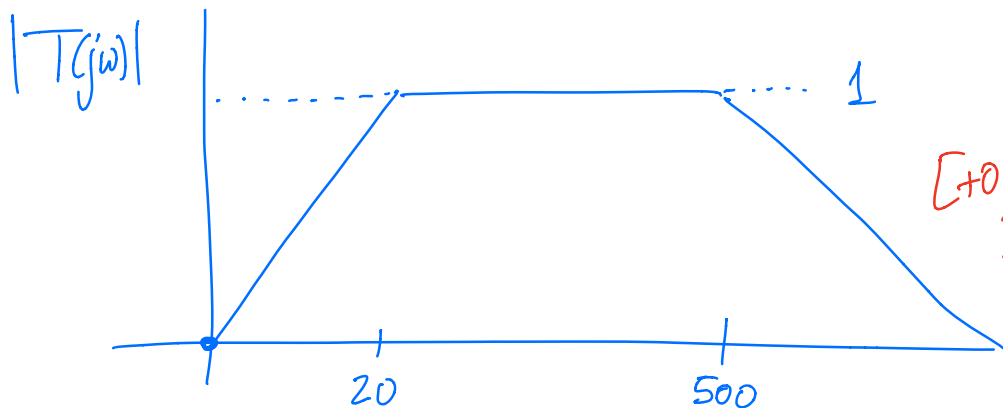

Bode plot from matlab

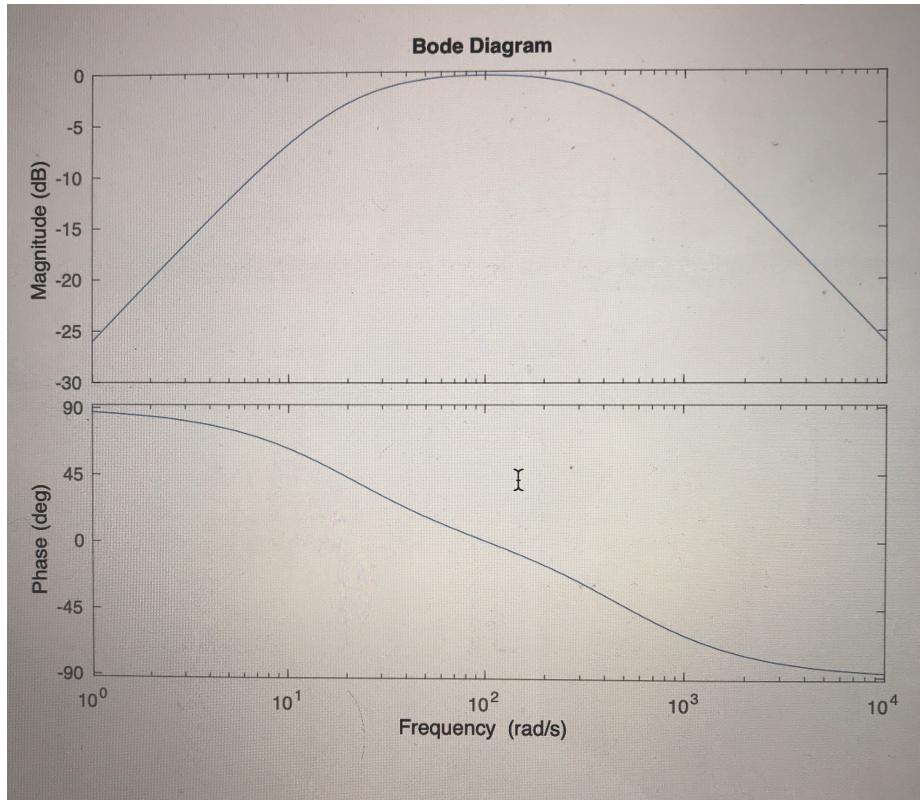

This is a bandpass filter.

[+1 point]

Part IV

$$v_i(t) = \cos\left(300t + \frac{\pi}{4}\right)$$

We know that

$$v_o^{ss}(t) = |T(j300)| \cos\left(300t + \frac{\pi}{4} + \angle T(j300)\right)$$

[+1 point]

Now,

$$\begin{aligned} |T(j300)| &\approx 0.8556 \\ \angle T(j300) &\approx -0.474 \end{aligned}$$


Therefore,

$$v_o^{ss}(t) = 0.8556 \cdot \cos\left(300t + 0.3115\right)$$

[+1 point]

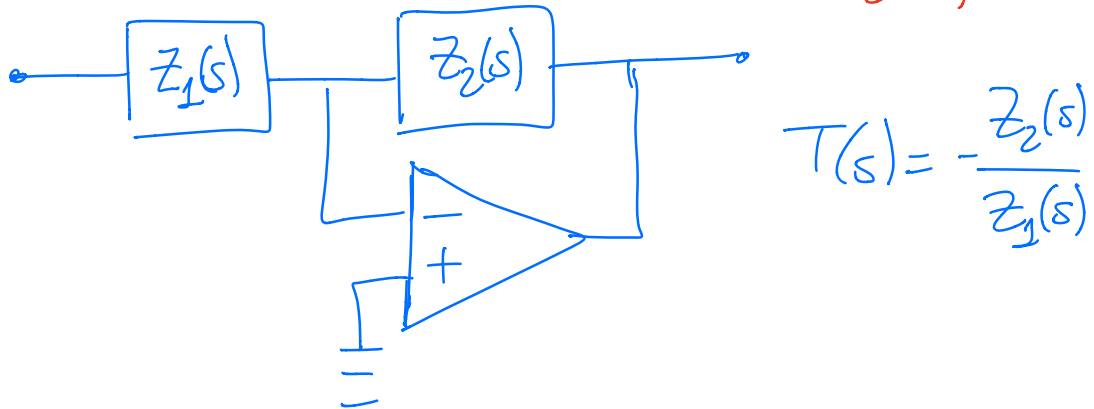4. - Part I

Based on the given decomposition, we try a design with inverting op-amps, since [+1 point]




$$T(s) = -\frac{Z_2(s)}{Z_1(s)}$$

Since we cannot use inductors, we rewrite

$$\begin{aligned} T_1(s) &= \frac{-20}{s+20} = \frac{-20/s}{1+20/s} = \frac{-20000}{1000 + \frac{20000}{s}} \\ &= \frac{-\frac{1}{5 \cdot 10^{-5} s}}{1000 + \frac{1}{5 \cdot 10^{-5} s}} \end{aligned}$$

Therefore, we design

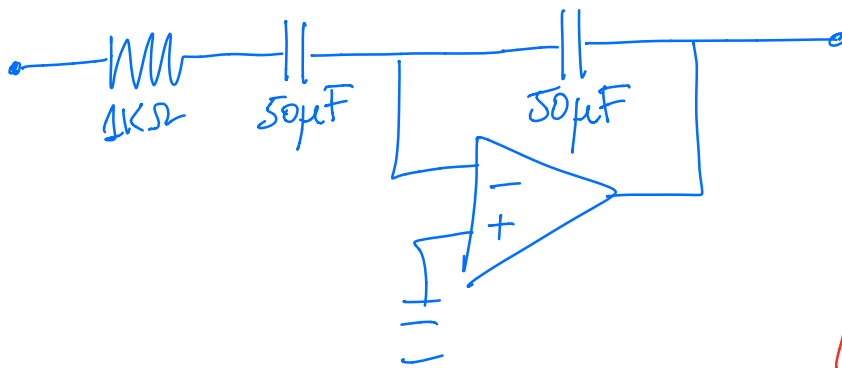


[+1 point]

Regarding $T_2(s)$, we write


$$T_2(s) = -\frac{25s}{s+500} = -\frac{2500}{100 + \frac{50000}{s}} = -\frac{2500}{100 + \frac{1}{8 \cdot 10^{-5}}}$$

Therefore, we design

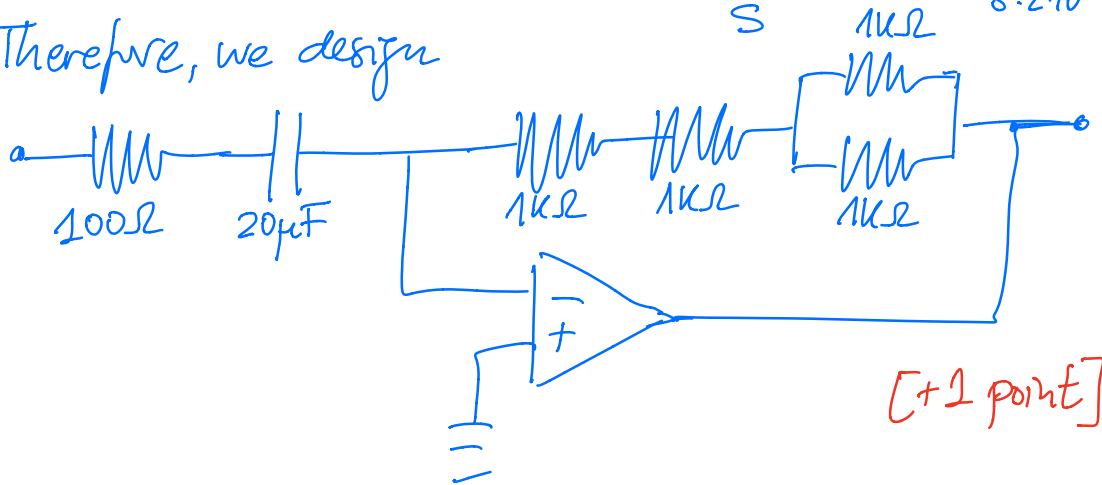

[+1 point]

Our design is then

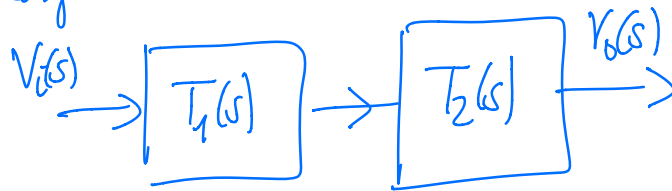

The chain rule applies: zero-output impedance of stage 1 means stage 2 does not load it.


[+1 point]

Part II

Given the decomposition, we attempt a design with voltage dividers and a voltage follower. Since we cannot use inductors, we rewrite

$$T_1(s) = \frac{s}{s+20} = \frac{1}{1 + \frac{20}{s}} = \frac{1000}{1000 + \frac{1}{5 \cdot 10^{-5}}}$$

Therefore we design

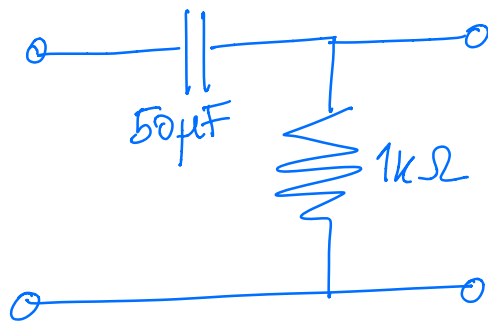


[+1 point]

On the other hand,

$$T_2(s) = \frac{500}{s+500} = \frac{500/s}{1+500/s} = \frac{50000/s}{100+50000/s} =$$

$$= \frac{\frac{1}{s \cdot 2 \cdot 10^{-5}}}{100 + \frac{1}{s \cdot 2 \cdot 10^{-5}}}$$


Therefore, we design

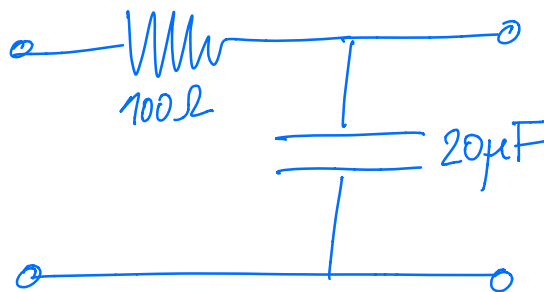

[+1 point]

Simply connecting the two voltage dividers in series would not work [since the second stage would load the first, disrupting the chain rule]. This is why we use a voltage follower

in the middle (leveraging the fact that it has ∞ -input impedance and 0-output impedance). Our final design is [+1 point]

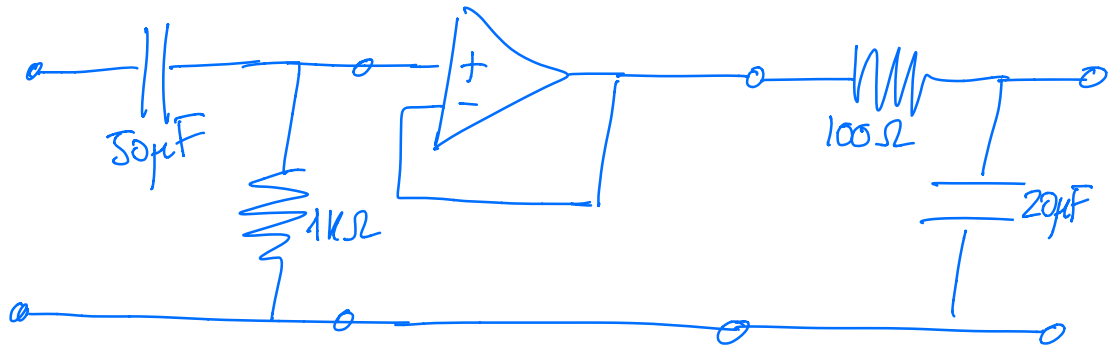

Part III


Given the decomposition, we also employ voltage division in this design, but this time paired with a non-inverting op-amp.

Note that

$$T_1(s) = \frac{20}{20+s} = \frac{\frac{1}{s \cdot 5 \cdot 10^{-5}}}{10^3 + \frac{1}{s \cdot 5 \cdot 10^{-5}}} \quad [+0.5 \text{ point}]$$

$$T_2(s) = \frac{s}{s+500} = \frac{100}{100 + \frac{1}{s \cdot 2 \cdot 10^{-5}}} \quad [+0.5 \text{ point}]$$

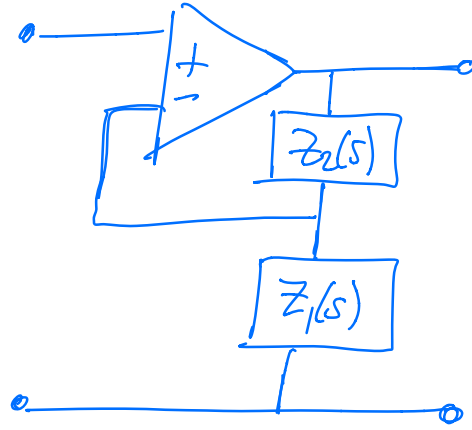Finally, we can realize $T_3(s) = 25$ with a non-inverting opamp





by setting

$$\frac{Z_1(s) + Z_2(s)}{Z_1(s)} = 25 \quad \Leftrightarrow \quad Z_2(s) = 24 Z_1(s)$$

We can make this happen with values


$$Z_1(s) = 50 \quad \& \quad Z_2(s) = 1200$$

So we choose

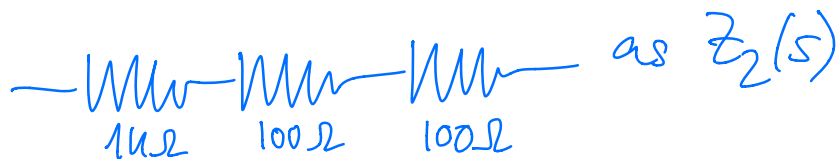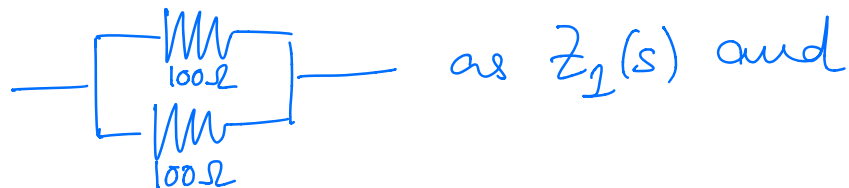

[+1 point]

Consequently, our design is

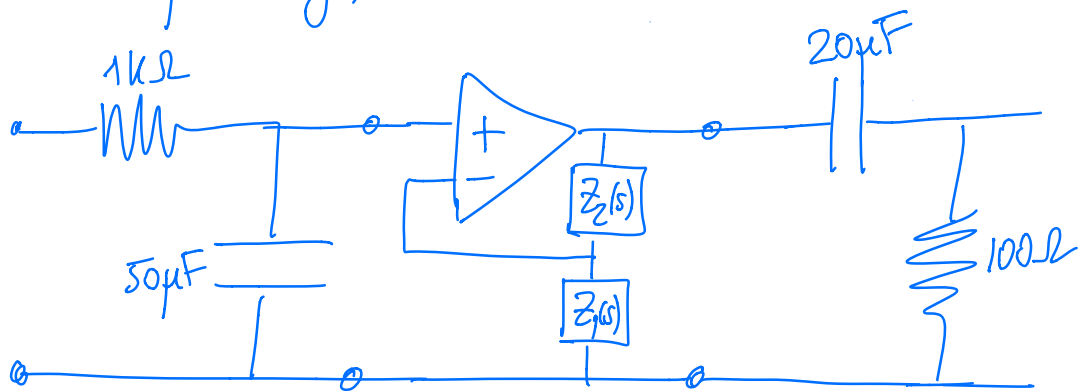

Again, the ∞ -input impedance and 0 -output impedance of the op-amp ensures that the chain rule applies.

[+1 point]