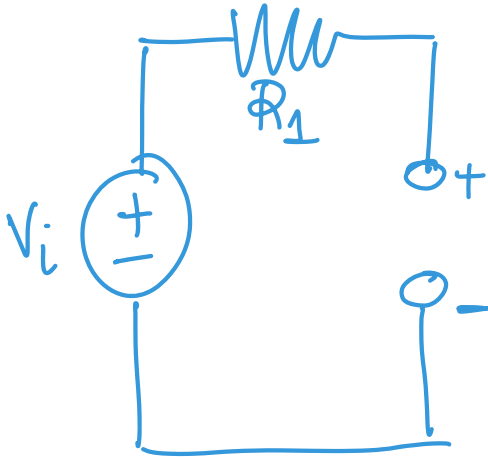


1. Part I

Under DC excitations, we know the capacitor behaves as an open circuit. Therefore, we have

[+1 point]




From the picture, we deduce that

$$V_C(0) = V_i$$

[+1 point]

Part II

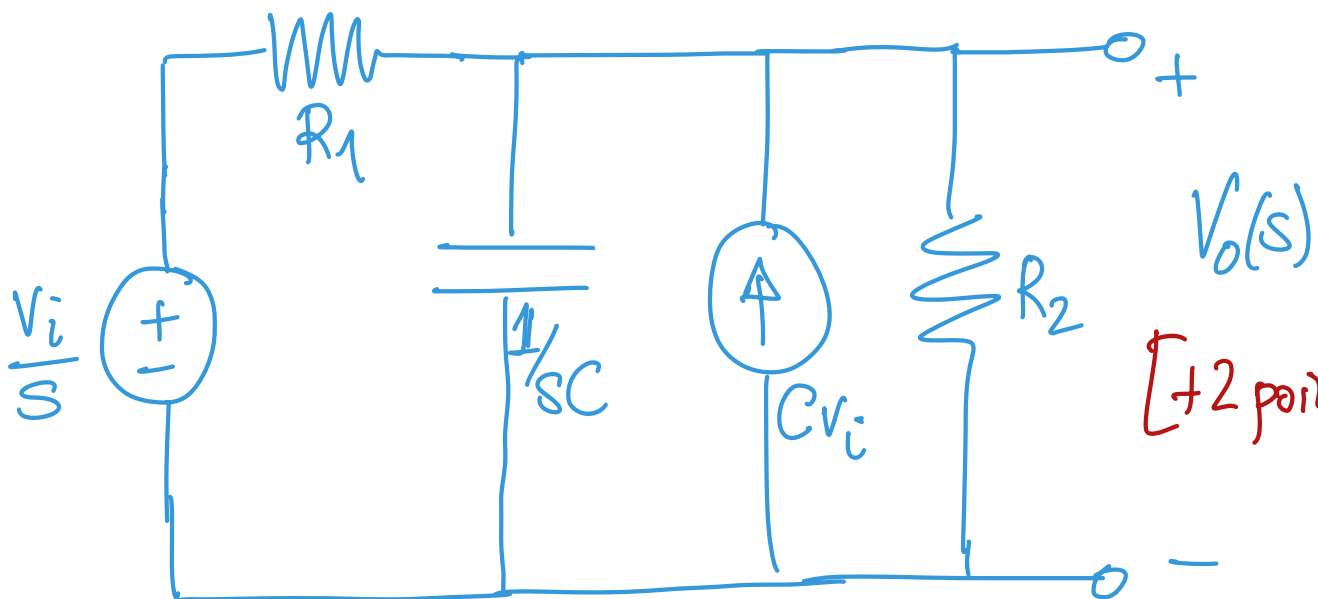
Next, we transform the circuit into the s-domain, using a current source to account for the initial condition.



[+2 points]

Part III

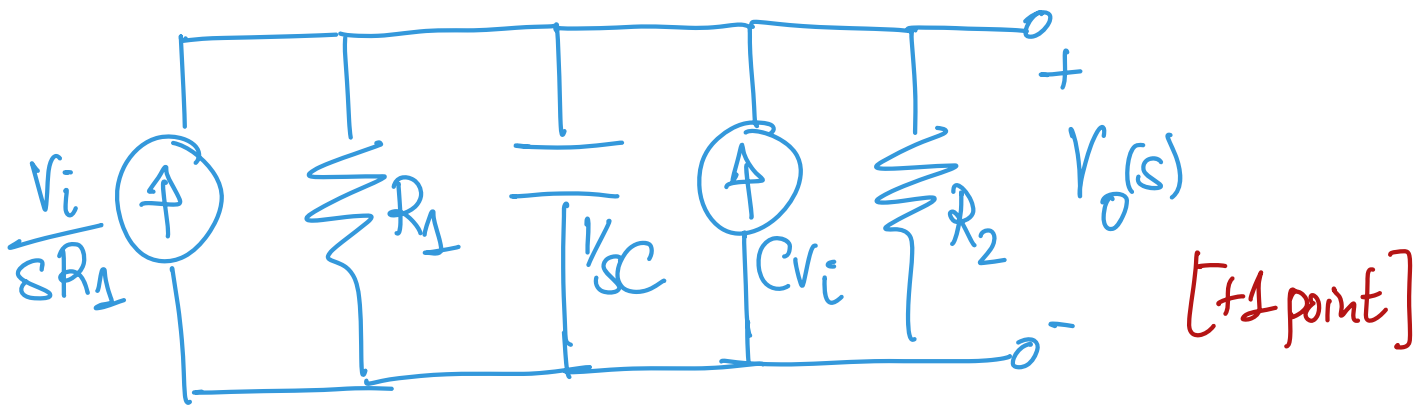We use source transformation to redraw the circuit as



We can now use current division to find the current through the R_2 -impedance as

$$i_{R_2} = \frac{\frac{1}{R_2}}{\frac{1}{R_2} + \frac{1}{R_1} + sC} \left(\frac{V_i}{sR_1} + Cv_i \right)$$

Finally,

$$\begin{aligned} V_o(s) &= R_2 \cdot i_{R_2} = \frac{R_2 R_1}{R_1 + R_2 + R_1 R_2 C s} \cdot \frac{V_i + C R_1 V_i s}{s R_1} \\ &= \frac{R_2 (1 + C R_1 s) V_i}{(R_1 + R_2 + R_1 R_2 C s) s} \end{aligned} \quad [+1 \text{ point}]$$

Part IV

Zero-state component corresponds to when the initial conditions are set to zero.

Therefore,

$$(V_o)_{zs}(s) = \frac{R_2 V_i}{(R_1 + R_2 + R_1 R_2 C s) s} \quad [+1 \text{ point}]$$

Zero-input component corresponds to when the input is set to zero. Therefore,

$$(V_o)_{zi}(s) = \frac{R_1 R_2 C V_i}{R_1 + R_2 + R_1 R_2 C s} \quad [+1 \text{ point}]$$

Part V

Forced component corresponds to the poles of the input. In this case, the input has a pole at 0. To answer the question, we use partial fractions to decompose $V_o(s)$ as

$$V_o(s) = \frac{A}{s} + \frac{B}{s + \frac{R_1 + R_2}{R_1 R_2 C}}$$

We use the residue method to find A & B.

$$\begin{aligned} A &= \lim_{s \rightarrow 0} s V_0(s) = \lim_{s \rightarrow 0} \frac{R_2 (1 + CR_1 s) v_i}{R_1 + R_2 + R_1 R_2 C s} = \\ &= \frac{R_2 v_i}{R_1 + R_2} \end{aligned}$$

$$B = \lim_{s \rightarrow -\frac{R_1 + R_2}{R_1 R_2 C}} \left(s + \frac{R_1 + R_2}{R_1 R_2 C} \right) V_0(s) =$$

$$= \lim_{s \rightarrow -\frac{R_1 + R_2}{R_1 R_2 C}} \frac{R_2 (1 + CR_1 s) v_i}{s \cdot CR_1 R_2} =$$

$$= \frac{R_2 v_i \left(1 - \frac{CR_1 (R_1 + R_2)}{CR_1 R_2} \right)}{\frac{-(R_1 + R_2) R_1 R_2 C}{R_1 R_2 C}} = \frac{\cancel{R_2} v_i \left(+ \frac{R_1}{R_2} \right)}{+(R_1 + R_2)}$$

$$= \frac{R_1 v_i}{R_1 + R_2}$$


Therefore, we conclude that

$$(V_o)_{fr}(s) = \frac{R_2 v_i}{(R_1 + R_2)s} \quad [+1 \text{ point}]$$

$$(V_o)_{nr}(s) = \frac{R_1 v_i}{R_1 + R_2} \cdot \frac{1}{s + \frac{R_1 + R_2}{R_1 R_2 C}} \quad [+1 \text{ point}]$$

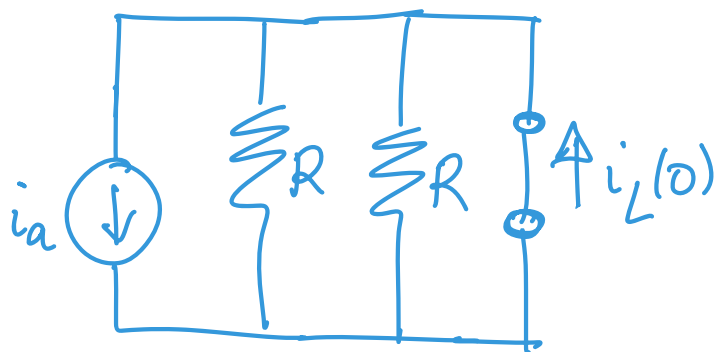2. - Part I

Under DC excitation, we know the inductor behaves as a short circuit. Therefore, we have




From the picture we deduce that

$$i_L(0) = i_a$$

[+1 point]

Part II

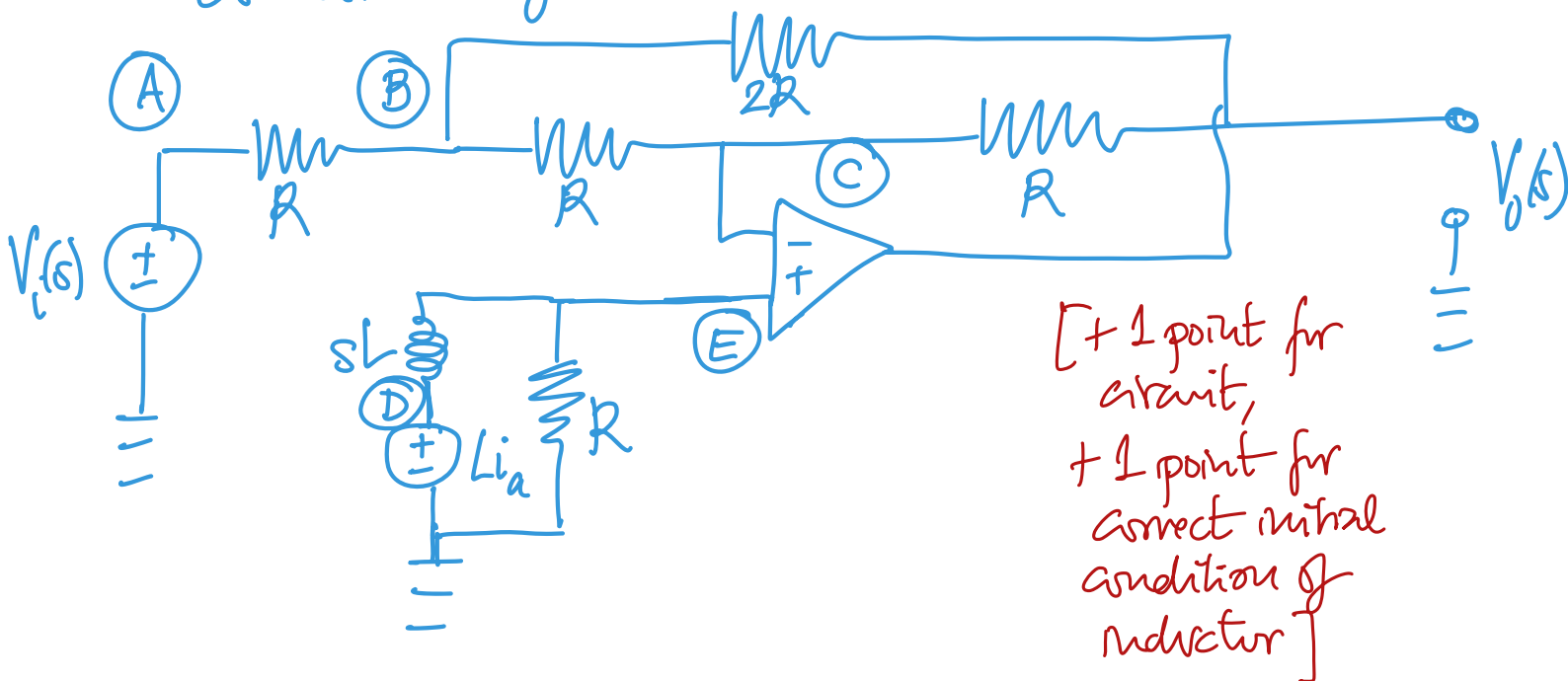We transform the circuit into the S-domain, using a voltage source to represent the initial condition of the inductor.



[+1 point for circuit,
+1 point for correct initial condition of inductor]

Part III

We use the node labels provided in the plot above. Right away, we have that

$$V_A = V_i(s) \quad ; \quad V_D = L i_a \quad [+1 \text{ point}]$$

Because of ideal op amp conditions, we know that the op-amp has infinite input impedance, and hence R and sL are in series with the voltage source $L i_a$. Therefore,

$$V_E = \frac{R}{R+sL} L i_a \quad [+1 \text{ point}]$$

KCL @ node (B)

$$\frac{1}{R} (V_B - V_A) + \frac{1}{2R} (V_B - V_D) + \frac{1}{R} (V_B - V_C) = 0 \quad [+1 \text{ point}]$$

KCL @ node (C)

$$\frac{1}{R} (V_C - V_B) + \frac{1}{R} (V_C - V_D) = 0 \quad [+1 \text{ point}]$$

Finally, we do not write KCL for the output node of the op-amp, relying instead on ideal op-amp conditions.

$$V_C = V_E$$

[+1 point]

Therefore, we have

$$V_O = 2V_C - V_B = \frac{2RLi_a}{R+sL} - V_B$$

Substituting into KCL for \textcircled{B} ,

$$\frac{1}{R}(V_B - V_i) + \frac{1}{2R}\left(V_B + V_B - \frac{2RLi_a}{R+sL}\right) + \frac{1}{R}\left(V_B - \frac{RLi_a}{R+sL}\right) = 0$$

$$V_B - V_i + V_B - \frac{RLi_a}{R+sL} + V_B - \frac{RLi_a}{R+sL} = 0$$

Hence

$$V_B = \frac{1}{3}\left(V_i + \frac{2RLi_a}{R+sL}\right)$$

And therefore

$$V_O(s) = \frac{2RLi_a}{R+sL} - \frac{1}{3}V_i(s) - \frac{2}{3}\frac{RLi_a}{R+sL} =$$

$$= -\frac{1}{3}V_i(s) + \frac{4}{3}\frac{RLi_a}{R+sL}$$

Part IV

Substituting the values provided, we get

$$V_0(s) = -\frac{1}{3} V_i(s) + \frac{4}{3} \cdot \frac{10^2 \cdot 10^{-3} \cdot 10^{-2}}{10^2 + s10^{-3}} =$$

$$= -\frac{1}{3} \left(\frac{1}{s} - \frac{1}{s+1} \right) + \frac{4}{3} \frac{1}{10^5 + s} =$$

$$= -\frac{1}{3} \frac{1}{s} + \frac{1}{3} \frac{1}{s+1} + \frac{4}{3} \frac{1}{s+10^5} \quad [+1 \text{ point}]$$

Taking inverse Laplace transforms, we get

$$v_0(t) = \left(-\frac{1}{3} + \frac{1}{3} e^{-t} + \frac{4}{3} e^{-10^5 t} \right) u(t)$$

$$= -\frac{1}{3} \left(1 - e^{-t} - 4e^{-10^5 t} \right) u(t)$$

[+1 point]

3. - Part I

To compute the gain and phase functions, we evaluate the transfer function at $s = j\omega$,

$$T(j\omega) = \frac{10j\omega}{-\omega^2 + 11j\omega + 10}$$

Therefore

$$|T(j\omega)| = \frac{10\omega}{\sqrt{(10 - \omega^2)^2 + 121\omega^2}} = \frac{10\omega}{\sqrt{100 + \omega^4 + 101\omega^2}} \quad [+1 \text{ point}]$$

$$\angle T(j\omega) = \frac{\pi}{2} - \arctan \frac{11\omega}{10 - \omega^2} \quad [+1 \text{ point}]$$

Part II

$$|T(j0)| = \frac{0}{\sqrt{100}} = 0 \quad [+0.5 \text{ point}]$$

$$|T(j\infty)| = \lim_{\omega \rightarrow \infty} |T(j\omega)| = 0 \quad [+0.5 \text{ point}]$$

$$\angle T(j\omega) = \frac{\pi}{2} - 0 = \frac{\pi}{2} \text{ rad} \quad [+0.5 \text{ point}]$$

$$\angle T(j\infty) = \frac{\pi}{2} - \pi = -\frac{\pi}{2} \text{ rad} \quad [+0.5 \text{ point}]$$

To compute the cutoff frequencies, we have to compute the maximum value of the gain function.

Note that $|T(j\omega)|$ and $|T(j\omega)|^2$ achieve the maximum at the same point, so we use the latter (which is easier to derive),

$$\frac{100\omega^2}{100 + \omega^4 + 101\omega^2}$$

We derive it

$$\frac{200\omega(100 + \omega^4 + 101\omega^2) - 100\omega^2(4\omega^3 + 202\omega)}{(100 + \omega^4 + 101\omega^2)^2}$$

This vanishes when the numerator vanishes, i.e.,

$$0 = -200\omega^5 + 20000\omega = 200\omega(-\omega^4 + 100)$$

i.e., $w=0$ or $w^4=100$
 $w^2=\pm 10$
 $w=\sqrt{10}$

So the maximum is

$$T_{\max} = \frac{10 \cdot \sqrt{10}}{\sqrt{100 + 100 + 101 \cdot 10}} = \frac{10\sqrt{10}}{11\sqrt{10}} = \frac{10}{11}$$

[+1 point]

Therefore, the cutoff frequencies are found by solving:

$$\frac{10w_c}{\sqrt{100 + w_c^4 + 101w_c^2}} = |T(jw_c)| = \frac{T_{\max}}{\sqrt{2}} = \frac{10}{11\sqrt{2}}$$

$$\frac{\cancel{100}w_c^2}{100 + w_c^4 + 101w_c^2} = \frac{\cancel{100}}{121 \cdot 2}$$

$$242w_c^2 = 100 + w_c^4 + 101w_c^2$$

$$100 + w_c^4 - 141w_c^2 = 0 \quad w_c^2 = z$$

$$z^2 - 141z + 100 = 0$$

$$z = \frac{141 \pm \sqrt{141^2 - 4 \cdot 100}}{2} = \begin{cases} 0.7128 \\ 140.287 \end{cases}$$

Therefore

$$\omega_c = \sqrt{z} = \begin{cases} 0.8442 \\ 11.843 \end{cases} \quad [+1 \text{ point}]$$


Part III

$$|T(j\omega)| = \frac{10\omega}{\sqrt{100 + \omega^4 + 101\omega^2}}$$



$$\text{For } \omega \ll 1, \quad |T(j\omega)| \approx \frac{10\omega}{10} = \omega$$

$$\text{For } \omega \gg 1, \quad |T(j\omega)| \approx \frac{10\omega}{\omega^2} = \frac{10}{\omega}$$

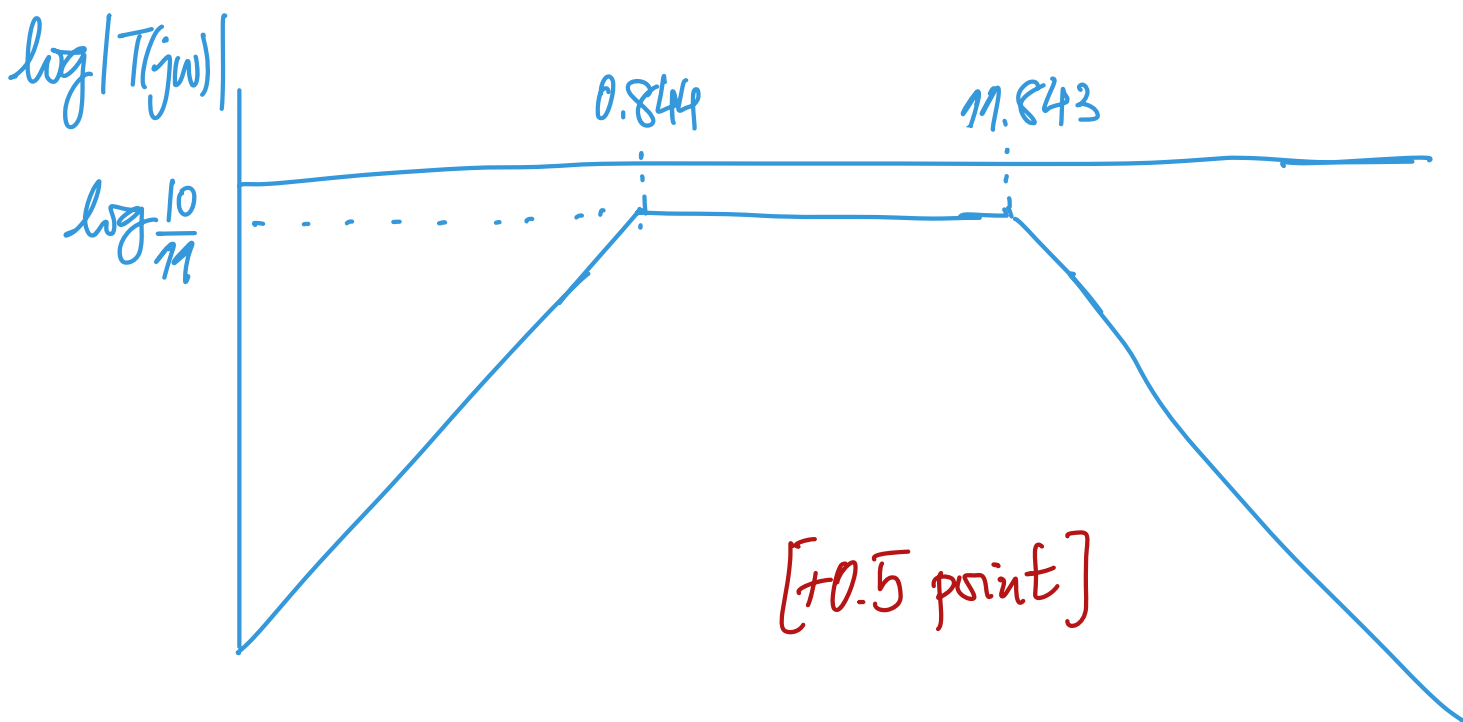Sketches can be done in linear or logarithmic scale.



[+0.5 point]

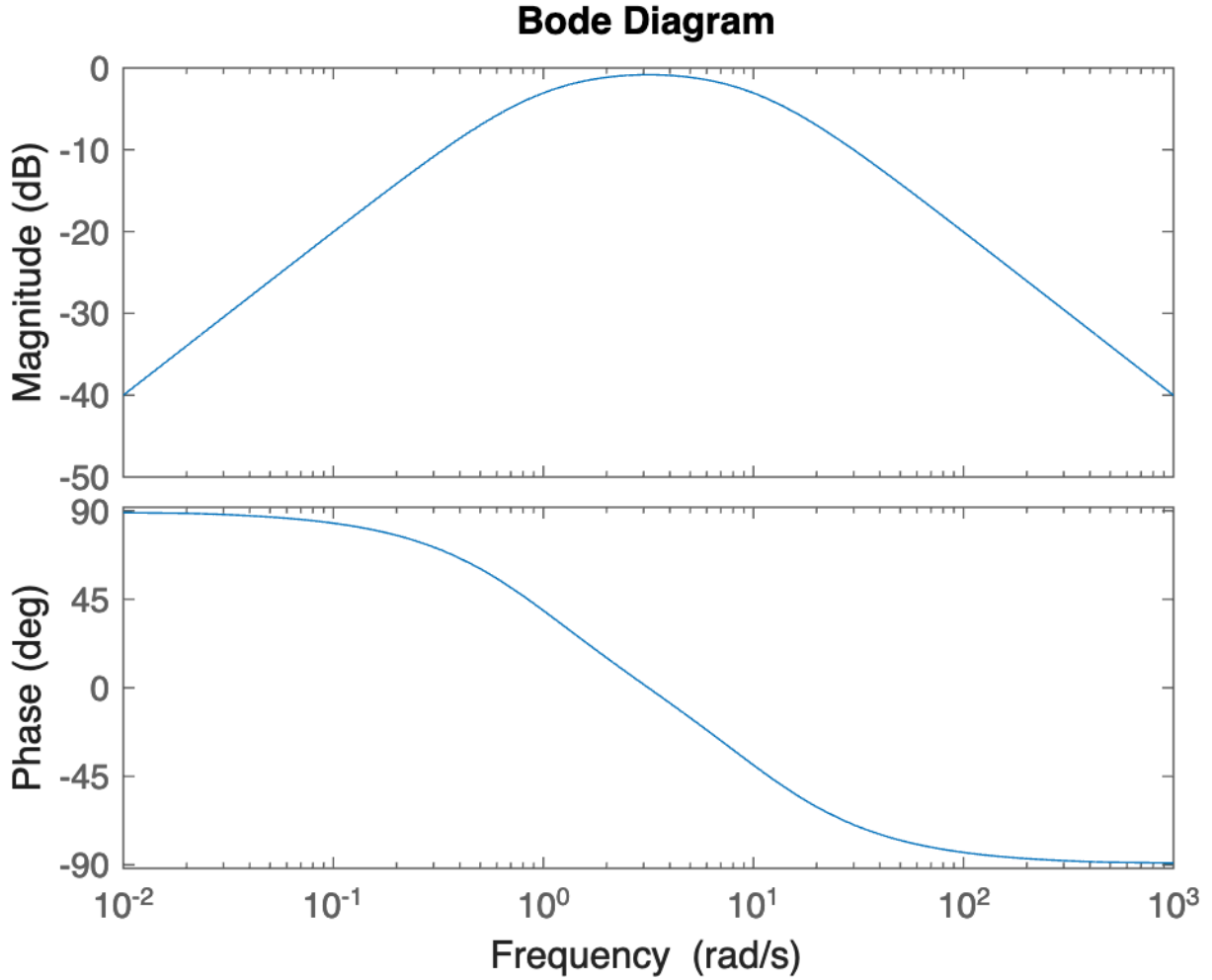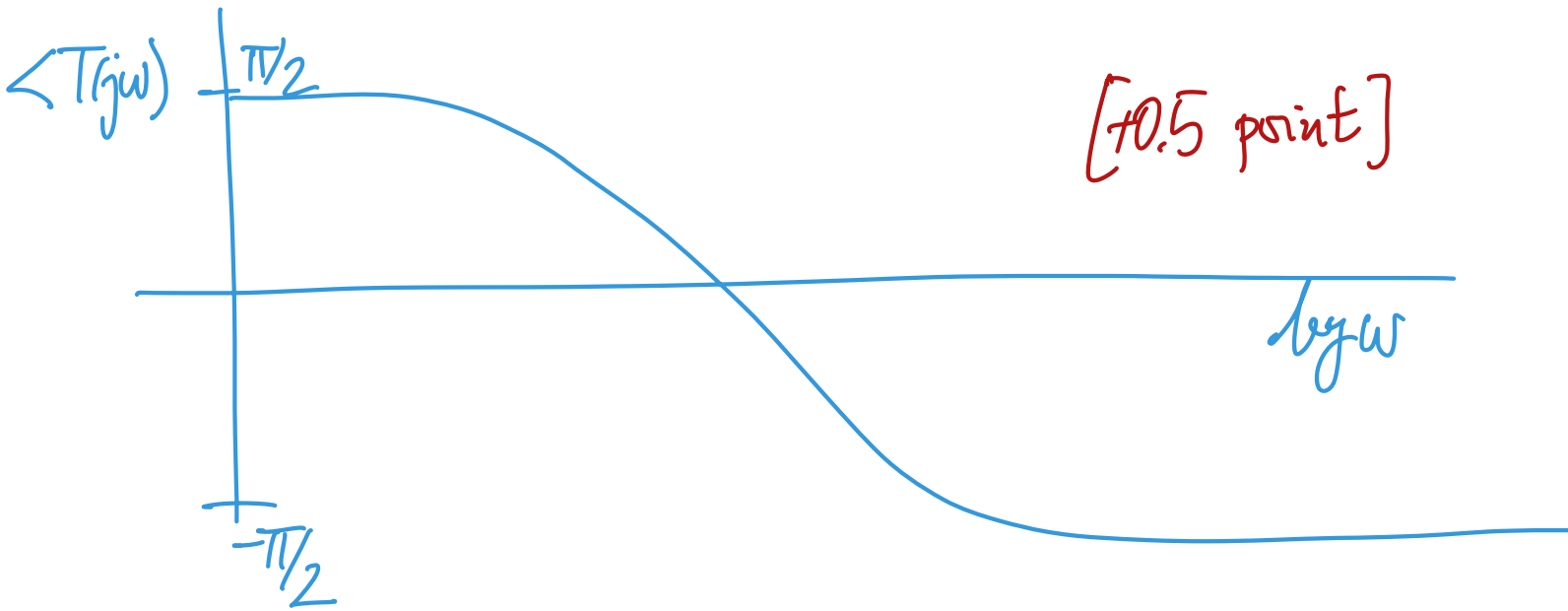

This is a bandpass filter. [+1 point]

Part IV

The input is

$$V_m(t) = 0.33 \cos\left(\frac{t}{6} - \pi\right) + \cos(2t) + 0.25 \cos\left(30t + \frac{\pi}{3}\right)$$

We therefore compute

$$|T(j\frac{1}{6})| \approx 0.164 \quad \angle T(j\frac{1}{6}) \approx 1.389 \text{ rad}$$

$$|T(j2)| \approx 0.877 \quad \angle T(j2) = 0.266 \text{ rad}$$

$$|T(j30)| \approx 0.31 \quad \angle T(j30) = -1.21 \text{ rad}$$

Therefore

$$V_o^{SS}(t) = 0.055 \cos\left(\frac{t}{6} - 1.75\right) + 0.877 \cos(2t + 0.266)$$


$$+ 0.079 \cos(30t - 0.168)$$

[+1 point]


Yes, the transfer function reasonably accomplished the engineer's goals. The time-varying bias almost disappeared in the filtered signal, and the noise was significantly reduced. Meanwhile, the signal with frequency

2 rad/s remained strong.

[+1 point]

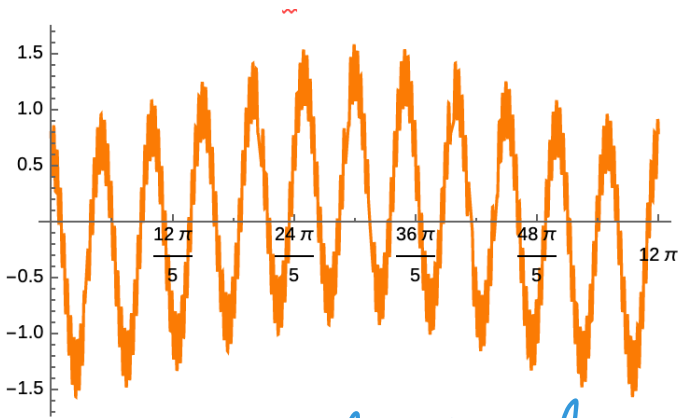

original signal
 $v_m(t)$

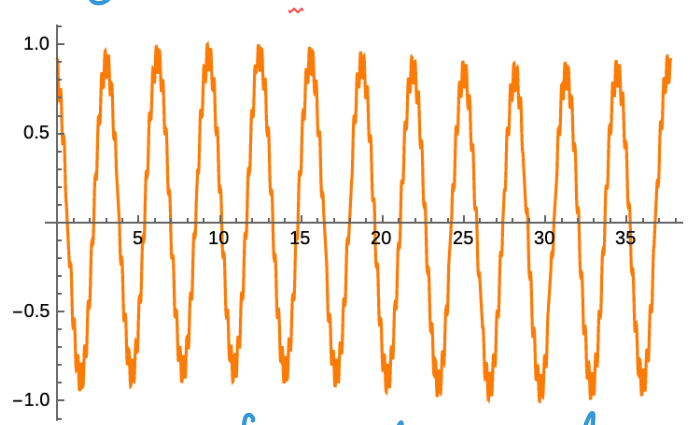

filtered signal
 $v_o^{SS}(t)$

4. Part I

We find the poles of the transfer function.

$$s^2 + 11s + 10 = 0$$

$$s = \frac{-11 \pm \sqrt{121 - 4 \cdot 10}}{2} = \frac{-11 \pm 9}{2} = \begin{cases} -1 \\ -10 \end{cases}$$

Therefore

[+1 point]

$$T(s) = \frac{10s}{s^2 + 11s + 10} = \frac{10s}{(s+1)(s+10)} = \frac{s}{s+1} \cdot \frac{10}{s+10}$$

$$\alpha_1 = 1 \text{ [+1 point]}$$


$$\alpha_2 = 10$$

Part II


$$T_1(s) = \frac{s}{s+1} = \frac{1}{1 + \frac{1}{s}} = \frac{10^4}{10^4 + \frac{1}{s10^{-4}}} \text{ [+1 point]}$$

$$T_2(s) = \frac{10}{s+10} = \frac{10/s}{1 + 10/s} = \frac{\frac{1}{s10^{-5}}}{10^4 + \frac{1}{s10^{-5}}} \text{ [+1 point]}$$

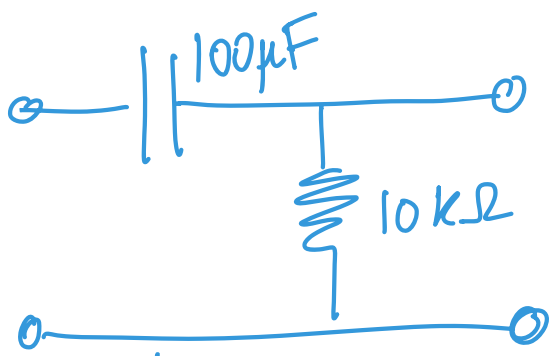We have manipulated the numerator/denominator of these transfer functions to make sure we can design circuits that do not employ inductors. We design them next as voltage dividers.




$T_1(s)$ [+1 point]

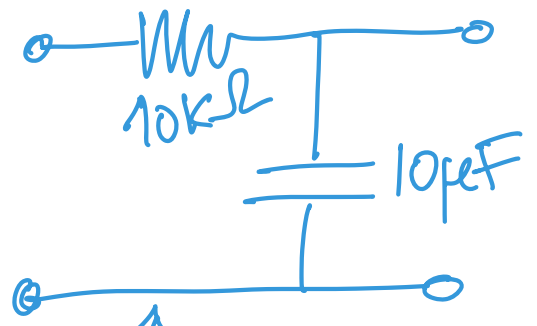

$T_2(s)$ [+1 point]

Part III

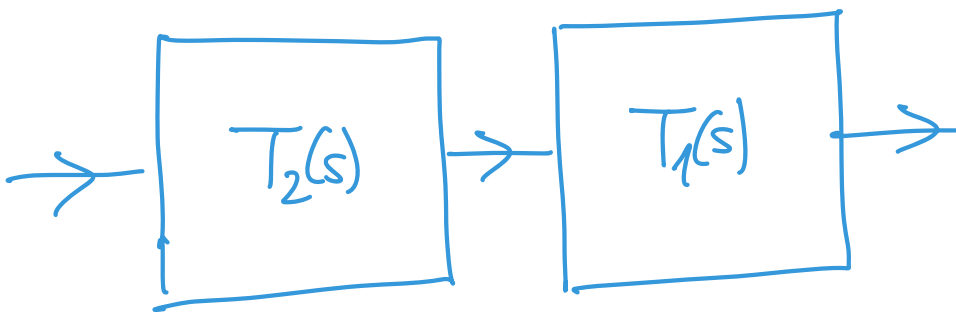No matter how we connect the circuits in part II, there is loading. [+1 point]




This means that the actual transfer function for the interconnection is not $T_1(s) \cdot T_2(s)$. This explains why, after filtering $v_{in}(t)$ the output is not exactly the same as the one we computed in Q3. Part IV. [+1 point]

Part IV

To avoid loading, we could use a voltage follower. The gain of a VF is 1.

[+1 point]

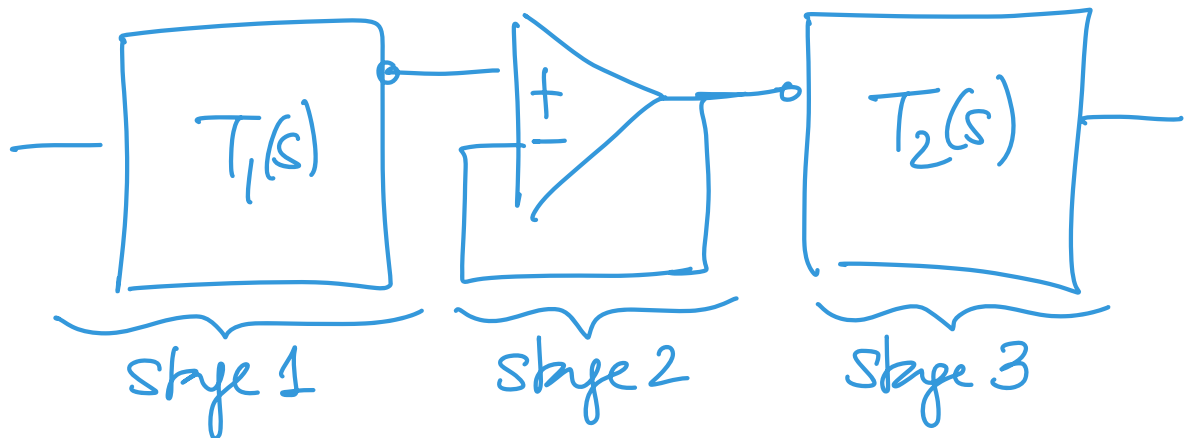





With this design, stage 2 does not load stage 1, because of the ∞ -input impedance of the op-amp. Also, stage 3 does not load stage 2 because of the zero-output impedance of the op-amp. Therefore, the transfer function of the interconnection is

$$T(s) = T_1(s) \cdot 1 \cdot T_2(s) = T_1(s) \cdot T_2(s)$$

as the engineer had originally intended. This will make the output of the filtered signal equal to our answer in Q3. Part IV.

[+1 point]

5. Part I

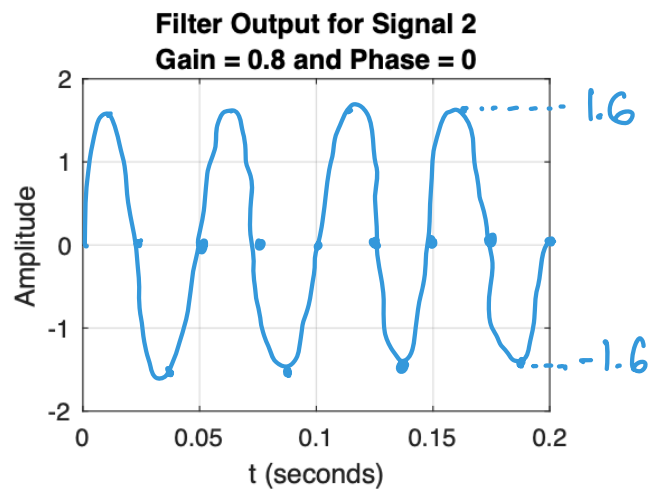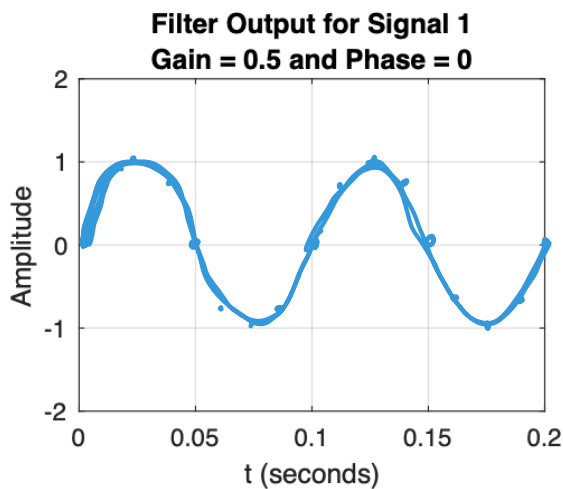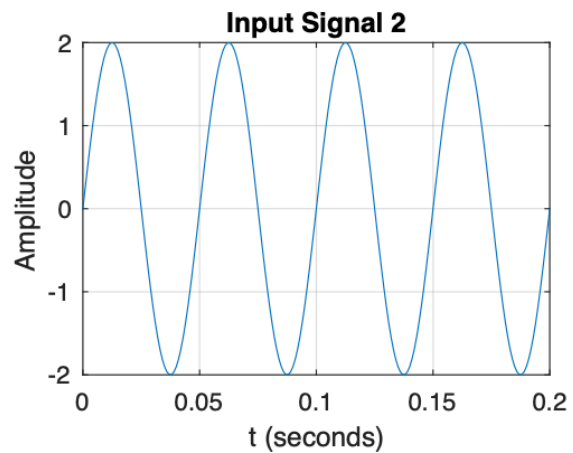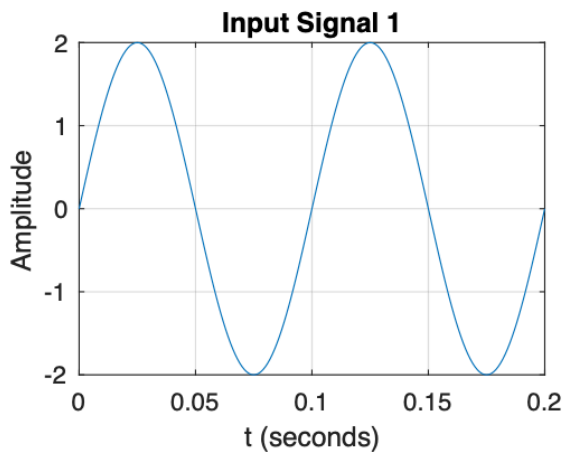

[+ 1 extra point]

Part II

It is not a low-pass filter, because the signal with smaller frequency has a significantly smaller gain than the signal with higher frequency.

[+0.5 extra point]

It could be a high-pass filter. It could also be a bandpass or a bandstop filter.

[+0.5 extra point]

6. - Part I

This is a voltage follower. We therefore know that

$$V_o(t) = V_i(t) \quad (\text{the gain is } 1)$$

[+1 extra point]

Part II

The question asks why using



instead of using simply



The answer is to avoid loading. If stage 1 does not have 0 output impedance and stage 2 does not have ∞ input impedance then simply connecting the stages creates loading.

Instead, using a voltage follower in-between makes sure loading is avoided. In this way, the output voltage of stage 1 is actually delivered to stage 2. We have used this in Q4. Part IV. [+1 extra point]