

**MAE40 - Linear Circuits - Fall 23 - Section A00**  
**Midterm #2, November 14**

**Instructions**

- (i) The exam is open book. You may use your class notes and textbook.
- (ii) The exam has 3 questions for a total of 23 points and 4 bonus points.
- (iii) You have from 11:00am to 12:20pm to do the exam – but should require less time!
- (iv) You can use a calculator with no communication capabilities.
- (v) In your responses, clearly articulate your reasoning, and properly justify the steps.
- (vi) **Important:** start each part below on a separate page, use only one side, and write your name & PID at the top of each page.

Good luck!

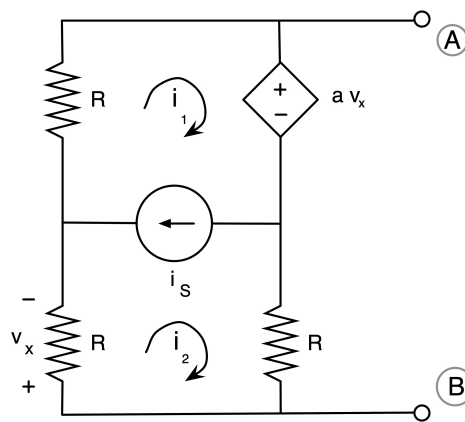


Figure 1: Circuit for Question 1.

**1. Mesh-current analysis with dependent sources**

For the circuit in Figure 1,

**Part I:** [4 points] Use mesh-current analysis to find the open-circuit voltage as seen from terminals (A) and (B) (use the labels provided and notice the presence of the dependent source).

**Part II:** [5 points] Connect the terminals (A) and (B) and find the short-circuit current, using again mesh current analysis.

**Part III:** [1 point] Given your answers to Parts I and II, can you tell what the Thevenin equivalent of this circuit is?

**Part IV** [+ Extra 1 point] If, instead of short-circuiting the circuit as in Part II, you turn off the current source in the circuit of Figure 1, what is the equivalent resistance? Is this the same as  $R_T$  in Part III? Why?

**2. OpAmp circuit analysis and design**

**Part I:** [5 points] Use node-voltage analysis to determine which one of the following expressions of the output voltage in the circuit in Figure 2 is correct;

$$v_o = -\frac{2}{3}v_S \quad v_o = -\frac{v_S}{3} \quad v_o = -\frac{v_S}{2}$$

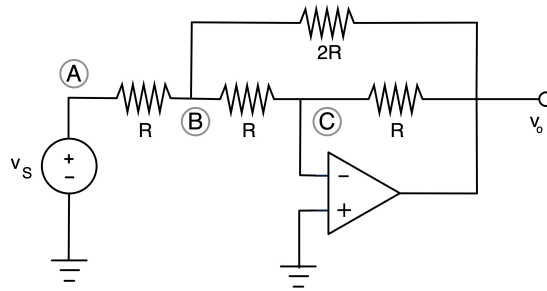


Figure 2: Circuit for Question 2.

- Part II:** [2 points] Under ideal OpAmp conditions, if you connect a load resistor  $R_L$  between the output node and ground, will the output voltage change? Why?
- Part III:** [2 points] Let  $R_L = 10\ \Omega$ . An engineer used a voltage source with  $v_S = 9V$  and measured the power consumed by the load as  $P_L = 0.9W$ , as expected. However, when the engineer connected a voltage source with  $v_S = 15V$ , the power consumed by the load was  $P_L = 1.6W$ . How do you explain this? Can you deduce what the external power supply  $-v_{CC}$  of the Op-Amp is?
- Part IV:** [+ Extra 1 point] Design your own circuit, using only basic OpAmp building blocks, two resistors with value  $R$  and 1 resistor with value  $2R$ , that generates the same output voltage as the circuit in Figure 2.

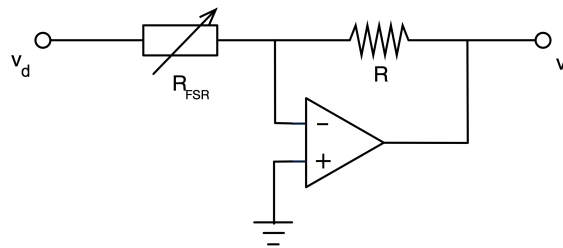


Figure 3: Circuit for Question 3.

### 3. Force sensing resistor

A Force Sensing Resistor (FSR) is a low cost and compact force sensor. The FSR behaves as a variable resistor whose value is a function of the applied force:  $R_{FSR}$  drops as force is applied. Figure 3 shows an OpAmp circuit with an FSR and a drive voltage  $v_d$ .

- Part I:** [2 points] Calculate the output voltage as a function of  $R_{FSR}$  and  $R$  when  $v_d = -5V$ .
- Part II:** [2 points] What would happen to  $v_o$  if  $v_d = 0$ ? Would this be a good way to measure the force applied on the FSR? Why?
- Part III:** [+ Extra 2 points] The characteristic of FSR is that the resistance does not vary linearly with applied load. Rather  $R_{FSR} = \frac{a}{b^F}$ , where  $a > 0$ ,  $b > 1$ , and  $F$  is the magnitude of the applied force. Do the following to explain the benefit of using the OpAmp circuit shown in Figure 3:
- Freehand sketch  $R_{FSR}$  vs  $F$  and show the slope for a high value of  $R_{FSR}$  that characterizes the change in  $R_{FSR}$  for a small change in  $F$ ;
  - For  $v_d = -5V$ , freehand sketch  $v_o$  vs  $R_{FSR}$  and show the slope for a high value of  $R_{FSR}$  that characterizes the change in  $v_o$  for a small change in  $R_{FSR}$ ;
  - Describe the effect of using the OpAmp circuit to generate the voltage  $v_o$  to represent the applied force (rather than using  $R_{FSR}$  directly).