

MAE40 - Linear Circuits - Fall 25  
Final Exam, December 11, 2025

**Instructions**

- (i) You can use 3 two-sided 1-page handwritten cheatsheets.
  - (ii) The exam has 4 questions, for a total of 40 points and 5 bonus points.
  - (iii) You have from 3:00pm to 6:00pm to do the exam – but should require less time!
  - (iv) You can use a calculator with no communication capabilities.
  - (v) In your responses, clearly *articulate your reasoning* and *properly justify the steps*.
  - (vi) **Important:** start each part below on a separate page, and write your name & PID at the top of each page.
- Good luck!

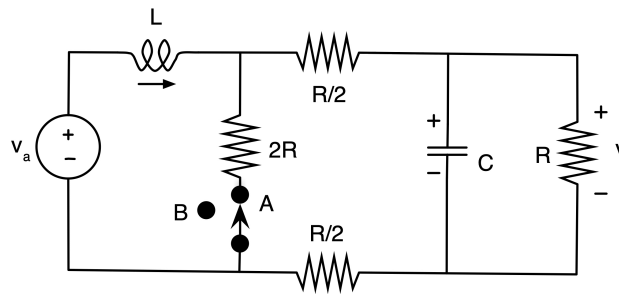


Figure 1: Circuit for Question 1.

**1.  $s$ -Domain Analysis**

Consider the circuit depicted in Figure 1. The value  $v_a$  of the voltage source is constant. The switch is kept in position **A** for a very long time. At time  $t = 0$ , it is moved to position **B**.

**Part I:** [3 points] Find the initial condition  $v_C(0)$  for the capacitor and  $i_L(0)$  for the inductor.

**Part II** [4 points] Transform the circuit in Figure 1 to the  $s$ -domain, using voltage sources to account for the initial conditions.

**Part III** [3 points] Set up mesh-current equations for the transformed circuit obtained in Part II (write them in matrix form). No need to solve any equations!

**Part IV** [1 bonus point] Express the transform  $V(s)$  of the  $R$ -resistor voltage in terms of the mesh currents. What element in the transformed circuit obtained in Part II has voltage drop  $V(s) - v_C(0)/s$ ?

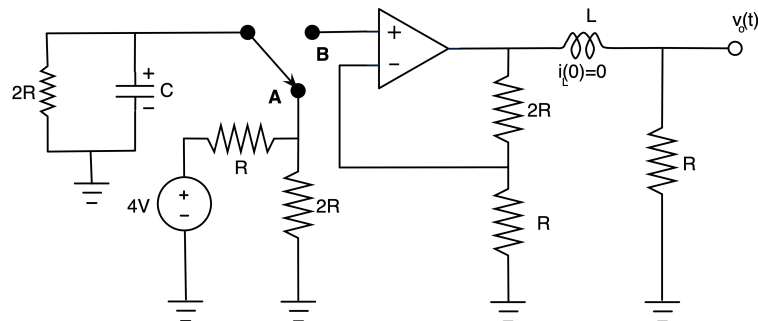


Figure 2: Circuit for Question 2.

## 2. Laplace Domain Circuit Analysis

**Part I:** [2 points] Consider the circuit depicted in Figure 2. The voltage source is constant. The switch is kept in position **A** for a very long time. At  $t = 0$  it is moved to position **B**. Show that the initial capacitor voltage is given by

$$v_C(0^-) = 2V.$$

[Show your work]

**Part II:** [3 points] Use this initial condition to transform the circuit into the  $s$ -domain for  $t \geq 0$ . Use an equivalent model for the capacitor in which the initial condition appears as a voltage source. Show that the transfer function of the circuit is

$$T(s) = \frac{6R^2Cs}{(Ls + R)(2RCs + 1)}.$$

[Show your work]

**Part III:** [5 points] Use domain circuit analysis and inverse Laplace transforms to show that the output voltage  $v_o(t)$  when  $C = \frac{1}{6}F$ ,  $L = 1H$ , and  $R = 3\Omega$  is

$$v_o(t) = 9(e^{-t} - e^{-3t})u(t).$$

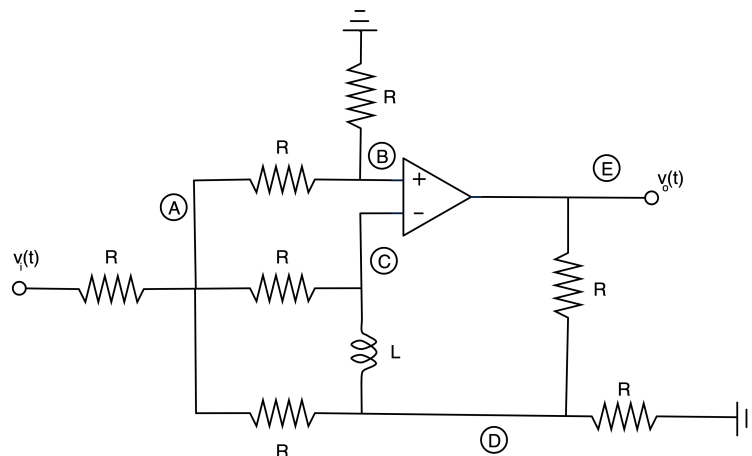


Figure 3: Circuit for Question 3.

## 3. Frequency Response Analysis

**Part I:** [1 point] Assuming zero initial conditions, transform the circuit in Figure 3 into the  $s$ -domain.

**Part II:** [3 points] Show that the transfer function from  $V_i(s)$  to  $V_o(s)$  is given by

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{-3Ls}{5R + Ls}.$$

[Show your work]

**Part III** [4 points] Let  $R = 100 \text{ m}\Omega$ ,  $L = 10 \text{ mH}$ . Compute the gain and phase functions of  $T(s)$ . What are the DC gain and the  $\infty$ -freq gain? What is the cut-off frequency  $\omega_c$ ? Use these values to sketch the magnitude of the frequency response. Is the circuit a low-pass, high-pass, or band-pass filter?

[Explain your answer]

**Part IV** [2 points] Using what you know about frequency response, compute the steady state response  $v_o^{SS}(t)$  of this circuit when  $v_i(t) = -2\cos(50t - \frac{\pi}{4})$  using the same values of  $R$  and  $L$  as in Part III.

**Part V:** [2 bonus points] Design an inverting OpAmp circuit that has transfer function  $T(s)$ . What design would you recommend, your design or the one in Figure 3? Why?

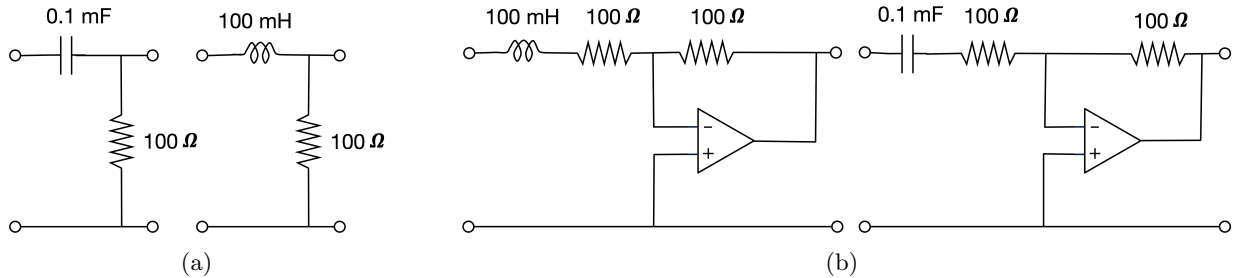


Figure 4: Circuits for Question 4.

#### 4. Loading and the Chain Rule

A former instructor of MAE140 was given the task of designing a circuit with the following transfer function

$$T(s) = \frac{1000s}{s^2 + 1100s + 10^5}$$

**Part I:** [2 points] The instructor first decomposed the transfer function as follows

$$T(s) = \left( \frac{s}{s + 100} \right) \left( \frac{1000}{s + 1000} \right)$$

and came up with a design that combines in series two voltage dividers, see Figure 4(a). Compute the transfer function of each voltage divider and show that their product is equal to  $T(s)$ .

**Part II:** [3 points] When the instructor connected the two stages in series and used the input  $v_i(t) = \cos(500t)$ , they were surprised to observe that the steady-state output was not  $v_o^{SS}(t) = \sqrt{\frac{10}{13}} \cos(500t - 0.2662)$ , which is what the instructor was expecting. Can you explain why the instructor was expecting that response and why they did not get it? Justify your answer.

**Part III:** [1 point] Could you fix the design provided by the instructor, still employing the two voltage dividers and possibly using one op-amp, so that the instructor gets the steady-state output they were aiming for? Explain how.

**Part IV:** [3 points] The instructor could not figure out why the design with voltage dividers was not working, so they abandoned it. The instructor decomposed again the transfer function, this time as

$$T(s) = \left( \frac{-1000}{s + 1000} \right) \left( \frac{-s}{s + 100} \right)$$

and came up with a design that combines in series the two stages in Figure 4(b). Compute the transfer function of each stage and show that their product is equal to  $T(s)$ .

**Part V:** [1 point] If the instructor connects in series the two stages in Figure 4(b) and uses the input  $v_i(t) = \cos(500t)$ , would the steady-state output be what they were expecting in Part II? Why? Justify your answer.

**Part VI:** [2 bonus points] If the instructor were to connect a source circuit whose Thévenin equivalent is  $v_T(t) = v_i(t)$  and  $R_T = 100\Omega$  to the design with op-amps in Part IV, should the instructor expect to get the steady-state output they were looking for too?