

**MAE40 - Linear Circuits - Fall 25**  
**Midterm #1, October 21**

**Instructions**

- (i) You can use a two-sided 1-page handwritten cheatsheet.
- (ii) The exam has 2 questions for a total of 20 points and 2 bonus points.
- (iii) You have from 2:00pm to 3:20pm to do the exam, but it should require less time for you to complete it.
- (iv) You can use a calculator with no communication capabilities.
- (v) In your responses, clearly articulate your reasoning, and properly justify the steps.
- (vi) **Important:** start each part below on a separate page and write your name & PID at the top of each page.

Good luck!

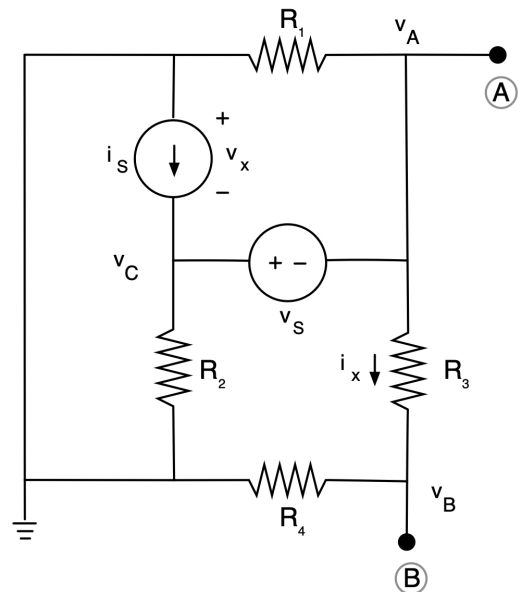


Figure 1: Circuit for all questions.

**1. Circuit analysis**

**Part I:** [6 points] Formulate node-voltage equations for the circuit in Figure 1. Use the node labels provided. Clearly indicate the final equations and circuit variable unknowns. Write the final equations **in matrix form** in the unknown node-voltages. **Do not modify the circuit or the labels.** No need to solve any equations!

**Part II:** [2 points] Provide expressions for the voltage  $v_x$  and the current  $i_x$  in terms of node voltages.

**Part III:** [2 points] Among the choices for ground other than the one in Figure 1, are there any that are better? Why?

**2. Equivalent circuits**

For this question, in the circuit in Figure 1, assume  $v_s = 10V$ ,  $i_s = 2A$ ,  $R_1 = R_2 = 20\Omega$ ,  $R_3 = 10\Omega$ , and  $R_4 = 5\Omega$ . Do the following:

**Part I:** [5 points] Turn off the sources and find the equivalent resistance as seen from terminals (A) and (B).

**Part II:** [3 points] Given your knowledge of Norton/Thévenin equivalence and your answer to Part I, if the short-circuit current when connecting terminals (A) and (B) is  $i_{sc} = 1A$  (going downwards), what is the open-circuit voltage  $v_{oc}$  as seen from terminals (A) and (B) for the circuit in Figure 1?

**Part III:** [2 points] Use your answers to Part I and Part II to find out the power delivered to a  $R = 2\Omega$  resistor connected to terminals (A) and (B).

**Part IV:** [Extra 2 points] What would happen if the resistor connected in Part III has a power rating of  $1W$ ? Could you have prevented this from happening by using a fuse? What is the maximum current rating that the fuse could have?