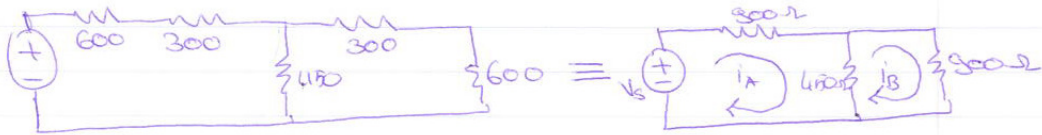


3.72) With Attenuator, calculate the power delivered to the load.

To do that calculate the current on the load



$$\text{Mesh A: } -V_s + 900 i_A + 450 i_A - 450 i_B = 0$$

$$\text{Mesh B: } -450 i_A + 450 i_B + 900 i_B = 0$$

from mesh B

$$1350 i_B = 450 i_A \Rightarrow 3 i_B = i_A$$

substitute into mesh A

$$\Rightarrow i_B = V_s / 3600$$

Current flow over the  $600 \Omega$  load is equal to  $i_B$  then we can calculate Power from equation

$$P_1 = i^2 \cdot R = \frac{V_s^2}{(3600)^2} \cdot 600 = \frac{V_s^2}{3600 \cdot 6}$$

Now remove the Attenuator



from voltage division

$$V = \frac{600}{(600+600)} V_s = \frac{V_s}{2}$$

$$P_2 = \frac{V^2}{R} = \frac{V_s^2}{600 \cdot 4}$$

then Power ratios in dB

$$10 \log\left(\frac{P_2}{P_1}\right) = 10 \log(S)$$


3.73



Design I/c such that  
 $V \leq 4V$  &  $i \leq 100mA$  regardless of  $R_L$

$\Rightarrow$  At least 1 of the  $50\Omega$  resistors must be arranged in parallel with  $R_L$  in order to meet the design criteria.

Use 1 in parallel and 2 in series:

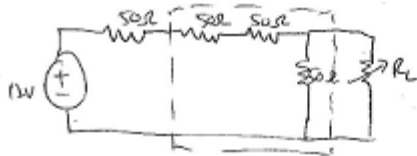



$$\therefore V = \frac{\left(\frac{50R_L}{50+R_L}\right)}{150 + \left(\frac{50R_L}{50+R_L}\right)} \times 12 \leq 4 \text{ for any } R_L$$

$$i_{\max} = \frac{12}{150} = 0.08 A \leq 100mA \quad \checkmark$$



3.95)

Required to deliver 0 to 5V to a  $100\Omega$  load from a 20V source rated at 2.5W.

Which circuit would you choose?

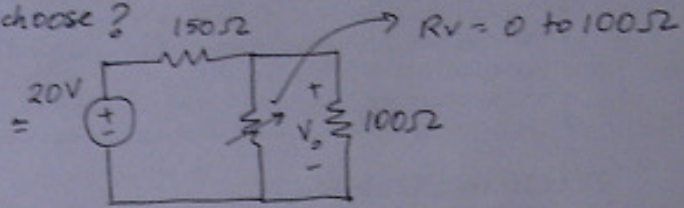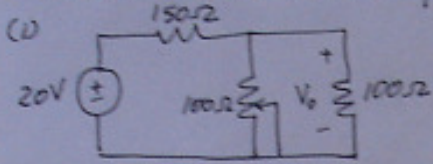
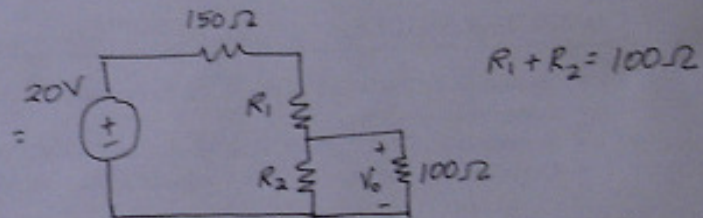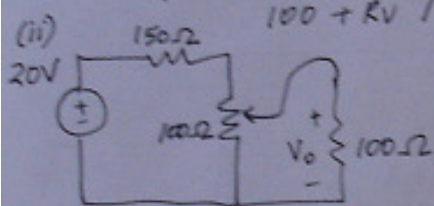
$$V_o = \left( \frac{\frac{100R_v}{100 + R_v}}{150 + \frac{100R_v}{100 + R_v}} \right) 20V = 20 \left( \frac{100R_v}{15000 + 250R_v} \right)$$




$$V_o = 20 \left( \frac{\frac{100R_2}{100 + R_2}}{150 + R_1 + \frac{100R_2}{100 + R_2}} \right) = 20 \left( \frac{100R_2}{(150 + R_1)(100 + R_2) + 100R_2} \right)$$

Since  $R_1 + R_2 = 100$   
 $\Rightarrow R_1 = 100 - R_2$

$$V_o = 20 \left( \frac{100R_2}{25000 + 250R_2 - R_2^2} \right)$$

We are required to find a circuit where the output voltage is close to 0. By looking at the equations for  $V_o$  for each of the circuit, it can be seen that  $V_o$  in the I circuit is more sensitive to changes in  $R_v$ . Therefore, it would be difficult to obtain  $V_o$  close to 0. On the other hand,  $V_o$  in the second circuit is less sensitive to changes in  $R_2$ . Therefore, circuit 2 should be chosen.

3.2)

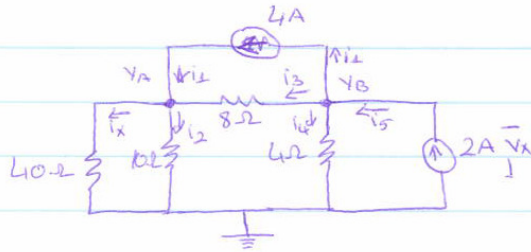

a) step 1: The reference node, node voltage and element currents are shown in the figure.

step 2:

$$\text{Node A: } i_1 + i_3 - i_x - i_2 = 0$$

$$\text{Node B: } i_5 - i_4 - i_4 - i_3 = 0$$

step 3:

$$i_1 = 4A$$

$$i_4 = \frac{V_B}{4}$$

$$i_2 = \frac{V_A}{10}$$

$$i_5 = 2A$$

$$i_3 = \frac{(V_B - V_A)}{8}$$

$$i_x = \frac{V_A}{40\Omega}$$

step 4: Substituting the element equation into KCL constraints

$$\text{Node A: } V_A \frac{1}{4} - V_B \frac{1}{8} = 4 \Rightarrow 2V_A - V_B = 32$$

$$\text{Node B: } V_A \frac{1}{8} - 3V_B \frac{1}{8} = 2 \Rightarrow V_A - 3V_B = 16$$


$$\begin{bmatrix} 2 & -1 \\ 1 & -3 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 32 \\ 16 \end{bmatrix}$$

b) By solving the linear equation, we can find

$$V_A = 16 \quad \text{and} \quad V_B = 0$$

$$i_x = \frac{V_A}{40} \Rightarrow i_x = \frac{4}{10} A \quad \text{and} \quad V_x = V_B = 0$$

3.5

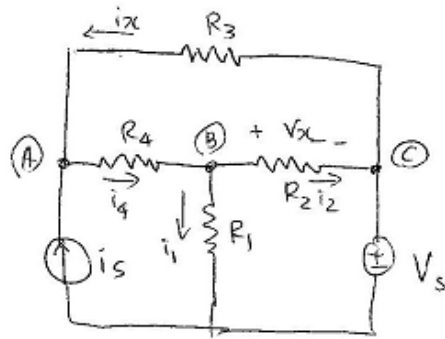

a) Formulate node-voltage equations

KCL @ A

$$i_s + i_x - i_4 = 0 \quad \dots \textcircled{1}$$

KCL @ B

$$i_4 - i_1 - i_2 = 0 \quad \dots \textcircled{2}$$

$$i_1 = \frac{V_B}{R_1}, \quad i_2 = \frac{V_B - V_C}{R_2}, \quad i_4 = \frac{V_A - V_B}{R_4}, \quad i_x = \frac{V_C - V_A}{R_3}, \quad V_C = V_s$$

Egn ① becomes

$$\frac{V_s - V_A}{R_3} - \frac{V_A - V_B}{R_4} = -i_s \quad \dots \textcircled{3}$$

Egn ② becomes

$$\frac{V_A - V_B}{R_4} - \frac{V_B}{R_1} - \frac{V_B - V_s}{R_2} = 0 \quad \dots \textcircled{4}$$

$$b) R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

$$V_S = 20 \text{ V}$$

$$i_S = 2 \text{ mA}$$

Solve for  $V_x$  and  $i_x$

$$\text{Egn } \textcircled{3}: \frac{V_S}{R_3} - \frac{V_A}{R_3} - \frac{V_A}{R_4} + \frac{V_B}{R_4} = -i_S$$

$$-\left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_A + \frac{V_B}{R_4} = -i_S - \frac{V_S}{R_3} \quad \dots \textcircled{5}$$

$$\text{Egn } \textcircled{4}: \frac{V_A}{R_4} - \frac{V_B}{R_4} - \frac{V_B}{R_1} - \frac{V_B}{R_2} + \frac{V_S}{R_2} = 0$$

$$\frac{V_A}{R_4} - \left(\frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2}\right) V_B = -\frac{V_S}{R_2} \quad \dots \textcircled{6}$$

From Egn  $\textcircled{6}$ ,

$$V_A = \left( \left( \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right) V_B - \frac{V_S}{R_2} \right) R_4$$

Plug into Egn  $\textcircled{5}$ .

$$-\left(\frac{1}{R_3} + \frac{1}{R_4}\right) \left( \left( \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right) V_B - \frac{V_S}{R_2} \right) R_4 + \frac{V_B}{R_4} = -i_S - \frac{V_S}{R_3}$$

$$V_B \left[ -\left(\frac{1}{R_3} + \frac{1}{R_4}\right) \left( \frac{1}{R_4} + \frac{1}{R_1} + \frac{1}{R_2} \right) R_4 + \frac{1}{R_4} \right] + R_4 \left( \frac{1}{R_3} + \frac{1}{R_4} \right) \frac{1}{R_2} V_S = -i_S - \frac{V_S}{R_3}$$

$$-\frac{1}{2000} V_B + \frac{1}{500} (20) = -2 \times 10^{-3} - \frac{20}{10000}$$

$$-\frac{1}{2000} V_B = -\frac{1}{125}$$

$$V_B = 16 \text{ V}$$


$$V_A = 28 \text{ V}$$

$$\therefore V_x = V_B - V_C = 16 - 20 = -4 \text{ V}$$

$$\therefore i_x = \frac{V_C - V_A}{R_3} = \frac{20 - 28}{10000} = -0.0008 \text{ A} = -0.8 \text{ mA}$$

3.6) a) Formulate node voltage eqns for the circuit.

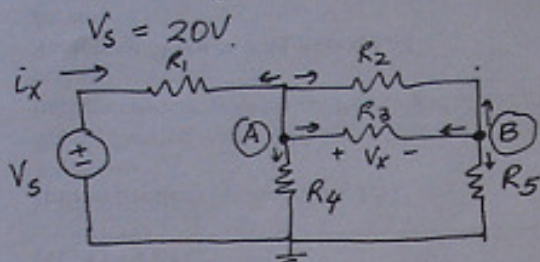b) Solve for  $V_x$  and  $i_x$  when  $R_1 = R_2 = R_3 = R_4 = R_5 = 10k\Omega$ , and



$$V_x = V_A - V_B$$

$$i_x = \frac{V_s - V_A}{R_1} = \frac{20 - V_A}{10k}$$

a) Node-voltage eqn

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_2} - \frac{1}{R_3} \\ -\frac{1}{R_2} - \frac{1}{R_3} & \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} \frac{V_s}{R_1} \\ 0 \end{bmatrix}$$

KCL @ Node A:

$$\frac{V_A}{R_4} + \frac{V_A - V_B}{R_3} + \frac{V_A - V_B}{R_2} + \frac{V_A - V_s}{R_1} = 0$$

$$V_A \left( \frac{1}{R_4} + \frac{1}{R_3} + \frac{1}{R_2} + \frac{1}{R_1} \right) + V_B \left( -\frac{1}{R_3} - \frac{1}{R_2} \right) = \frac{V_s}{R_1}$$

KCL @ Node B:

$$\frac{V_B}{R_5} + \frac{V_B - V_A}{R_3} + \frac{V_B - V_A}{R_2} = 0$$

$$V_B \left( \frac{1}{R_5} + \frac{1}{R_3} + \frac{1}{R_2} \right) + V_A \left( -\frac{1}{R_3} - \frac{1}{R_2} \right) = 0 \quad \text{--- (*)}$$

b)  $V_A \left( \frac{1}{10k} + \frac{1}{10k} + \frac{1}{10k} + \frac{1}{10k} \right) + V_B \left( -\frac{1}{10k} - \frac{1}{10k} \right) = \frac{20V}{10k}$

$$V_A \left( \frac{4}{10k} \right) - V_B \left( \frac{2}{10k} \right) = 2mA$$

$$4V_A - 2V_B = 20 \quad \text{--- (1)}$$

from (\*)  $3V_B - 2V_A = 0 \Rightarrow V_B = \frac{2V_A}{3}$

from (1)  $4V_A - 2 \left( \frac{2V_A}{3} \right) = 20$

$$12V_A - 4V_A = 60$$

$$\Rightarrow 8V_A = 60 \Rightarrow V_A = 7.5V$$


$$\therefore V_B = 5V$$

$$\therefore V_x = 7.5 - 5 = 2.5V$$

$$i_x = 1.25mA$$

20

3.7)

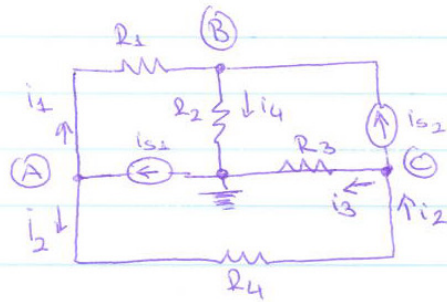

a) Step 1: The reference node, node voltage and element currents are shown in the figure

Step 2:

$$\text{Node A: } i_{s1} - i_1 - i_2 = 0$$

$$\text{Node B: } i_{s2} + i_1 - i_4 = 0$$

$$\text{Node C: } i_2 - i_3 - i_{s2} = 0$$

Step 3:

$$i_1 = \frac{(V_A - V_B)}{R_1}$$

$$i_2 = \frac{(V_A - V_C)}{R_4}$$

$$i_4 = \frac{V_B}{R_2}$$

$$i_3 = \frac{V_C}{R_3}$$

Step 4: Substituting the element eqn. into KCL constraints

$$\text{Node A: } \left( \frac{1}{R_1} + \frac{1}{R_4} \right) V_A - \frac{V_B}{R_1} - \frac{V_C}{R_4} = i_{s1}$$

$$\text{Node B: } \left( \frac{1}{R_1} + \frac{1}{R_2} \right) V_B - \frac{V_A}{R_1} = i_{s2}$$

$$\text{Node C: } \frac{V_A}{R_4} - \left( \frac{1}{R_3} + \frac{1}{R_4} \right) V_C = i_{s2}$$



3.7) cont.)

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_4} & -\frac{1}{R_1} & -\frac{1}{R_4} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} & 0 \\ \frac{1}{R_4} & 0 & -\frac{1}{R_4} - \frac{1}{R_3} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_{s1} \\ i_{s2} \\ i_{s2} \end{bmatrix}$$

b)  $R_1 = 1\text{k}\Omega$ ,  $R_2 = 2\text{k}\Omega$ ,  $R_3 = 4\text{k}\Omega$ ,  $R_4 = 2\text{k}\Omega$  and  $i_{s1} = i_{s2} = 2\text{mA}$

Then

$$\text{Node A: } \frac{3}{2}V_A - V_B - \frac{V_C}{2} = 2 \quad (\text{I})$$

$$\text{Node B: } \frac{3}{2}V_B - V_A = 2 \Rightarrow V_B = \frac{2}{3}V_A + \frac{4}{3} \quad (\text{II})$$

$$\text{Node C: } \frac{V_A}{2} - \frac{3}{4}V_C = 2 \Rightarrow V_C = \frac{2}{3}V_A - \frac{8}{3} \quad (\text{III})$$

Substitute eqn (II) and (III) into eqn (I)

and find  $V_A = 4\text{V}$  (units  $\text{k}\Omega \sim \text{mA}$  gives  $\text{V}$ )




By using eqn (II) and  $V_A = 4\text{V}$

$$V_B = \frac{2}{3} \cdot 4 + \frac{4}{3} = \frac{12}{3} = 4\text{V} = V_B$$

and finally eqn (III)

$$V_C = \frac{2}{3} \cdot 4 - \frac{8}{3} = 0 = V_C$$

3.9

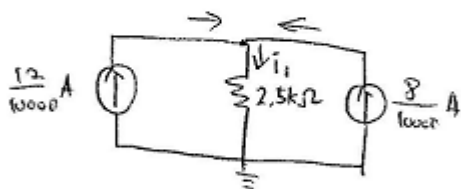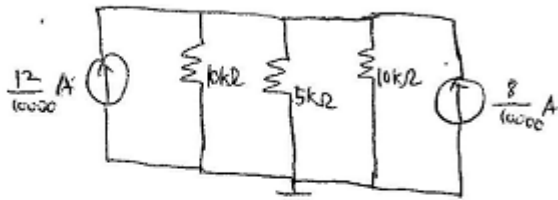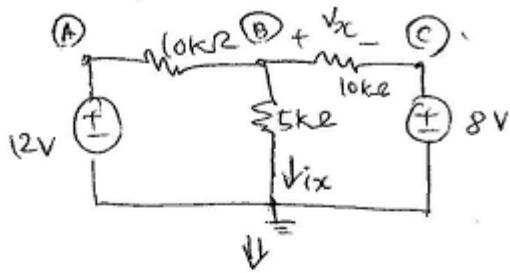

Nodal Analysis:

$$\frac{12}{10000} + \frac{8}{10000} = i_1$$

$$i_1 = 2 \times 10^{-3} \text{ A}$$


$$V_B = i_1 (2.5 \text{ k}\Omega) = 5 \text{ V}$$

$$V_B = 8 \text{ V} + V_x = 5 \text{ V}$$

$$\therefore V_x = 5 - 8 = \underline{\underline{-3 \text{ V}}}$$

$$\therefore \bar{i}_x = \frac{V_B}{5 \text{ k}\Omega} = \frac{5}{5000} = \underline{\underline{1 \text{ mA}}}$$

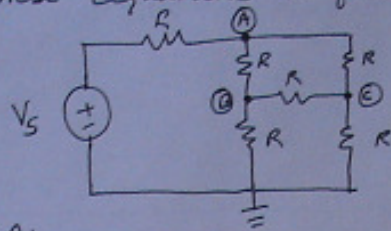- 3.16 a) Formulate node-voltage eqns for the circuit  
 b) Use these equations to find the input resistance.



a) KCL @ node A:

$$\frac{V_A - V_S}{R} + \frac{V_A - V_B}{R} + \frac{V_A - V_C}{R} = 0$$

$$V_A \left( \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right) - V_B \left( \frac{1}{R} \right) - V_C \left( \frac{1}{R} \right) = \frac{V_S}{R} \Rightarrow 3V_A - V_B - V_C = V_S \quad (1)$$

KCL @ node B:

$$\frac{V_B - V_A}{R} + \frac{V_B - V_C}{R} + \frac{V_B}{R} = 0$$

$$V_B \left( \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right) - V_A \left( \frac{1}{R} \right) - V_C \left( \frac{1}{R} \right) = 0 \Rightarrow -V_A + 3V_B - V_C = 0 \quad (2)$$

KCL @ node C:

$$\frac{V_C - V_A}{R} + \frac{V_C - V_B}{R} + \frac{V_C}{R} = 0$$

$$V_C \left( \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right) - V_A \left( \frac{1}{R} \right) - V_B \left( \frac{1}{R} \right) = 0 \Rightarrow -V_A - V_B + 3V_C = 0 \quad (3)$$

Node-voltage equations:

$$\begin{bmatrix} \frac{1}{R} + \frac{1}{R} + \frac{1}{R} & -\frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{1}{R} + \frac{1}{R} + \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & -\frac{1}{R} & \frac{1}{R} + \frac{1}{R} + \frac{1}{R} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} V_S/R \\ 0 \\ 0 \end{bmatrix}$$

b) From eqn (2):  $V_C = -V_A + 3V_B \quad (4)$

substituting (4) in (3):  $-V_A - V_B - 3V_A + 9V_B = 0$


$$-4V_A + 8V_B = 0$$

$$V_A = 2V_B \quad (5)$$

substituting (5) in (4):  $V_C = -2V_B + 3V_B$


$$V_C = V_B$$
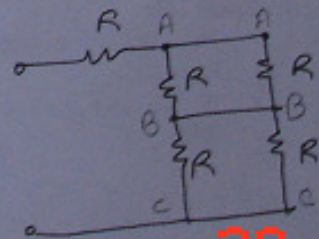
$$R_{IN} = R + \frac{R \cdot R}{R+R} + \frac{R \cdot R}{R+R} = 2R$$



20 2

### 3.17) Nodal Analysis:

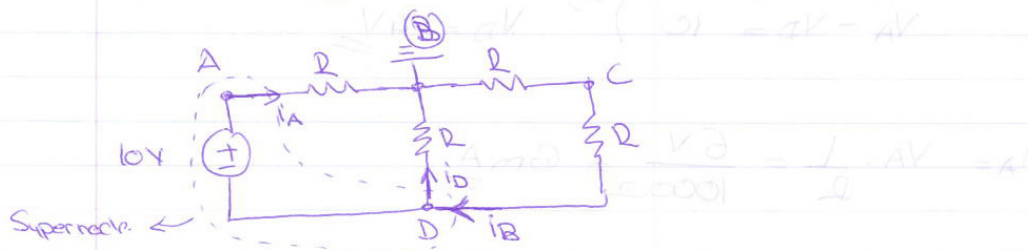

Here, we need to use Supernode approach. The voltage source is ungrounded.

Write the eqn for supernode

$$i_A + i_D - i_B = 0$$

We can write  $i_A$ ,  $i_D$  and  $i_B$  as (Remember  $V_B = 0$  (ground))

$$i_A = V_A \cdot G$$

$$i_B = (V_C - V_D)G \quad \text{The } V_C \text{ is given } V_C = -2$$

$$i_D = V_D \cdot G$$

Then first eqn

$$V_A G + V_D G - (-2 - V_D)G = 0$$

$$\Rightarrow V_A + 2V_D = -2 \quad (1^{\text{st}} \text{ Eqn})$$

We have two unknowns, we need 2<sup>nd</sup> equation


Applying the fundamental property of the node voltage inside the supernode we can write

$$V_A - V_D = 10V \quad (2^{\text{nd}} \text{ Eqn})$$

$$\left. \begin{array}{l} V_A + 2V_D = -2 \\ V_A - V_D = 10 \end{array} \right\} \Rightarrow \begin{array}{l} V_A = \underline{\underline{6V}} \\ V_D = \underline{\underline{-4V}} \end{array}$$

$$i_A = \frac{V_A}{R} = \frac{6V}{1000\Omega} = \underline{\underline{6mA}}$$
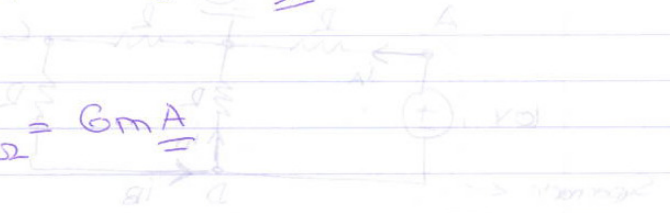
$$i_B = \frac{(V_C - V_D)}{R} = \frac{-2 + 4}{1000} = \underline{\underline{2mA}}$$



(with the sign for current)