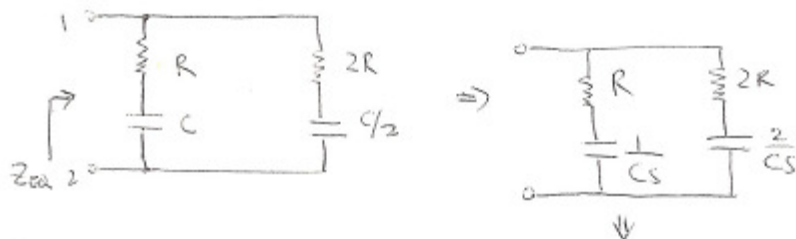


10.2 ✓

Find  $Z_{EQ}(s)$ . Express  $Z_{EQ}(s)$  as a rational fraction & locate its poles & zeros



$$\Rightarrow Z_1 = R + \frac{1}{Cs} = \frac{RCs + 1}{Cs}$$

$$Z_2 = 2R + \frac{2}{Cs} = \frac{2(RCs + 1)}{Cs}$$


$$Z_{EQ} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{\frac{RCs + 1}{Cs} \cdot \frac{2(RCs + 1)}{Cs}}{\frac{RCs + 1}{Cs} + \frac{2(RCs + 1)}{Cs}}$$

$$= \frac{2(RCs + 1)(RCs + 1)}{3(RCs + 1)Cs}$$

$$= \boxed{\frac{2}{3} \frac{RCs + 1}{Cs}}$$

$\therefore$  poles = 0, zeros =  $-\frac{1}{RC}$

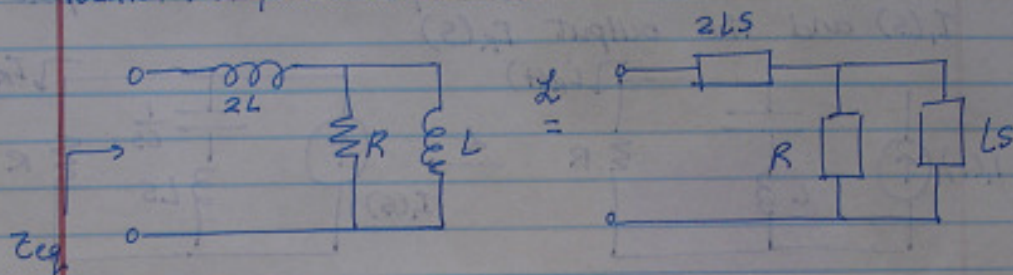10.5) Find  $Z_{eq}(s)$ . Express  $Z_{eq}(s)$  as a rational function and locate its poles and zeros.





$$Z_{eq} = 2Ls + \frac{1}{\frac{1}{R} + \frac{1}{Ls}} = 2Ls + \frac{1}{\frac{Ls+R}{RLs}} = 2Ls + \frac{RLs}{Ls+R}$$

$$\begin{aligned} Z_{eq}(s) &= \frac{2Ls(Ls+R) + RLs}{Ls+R} \\ &= \frac{s^2(2L^2) + 2RLs + RLs}{L(s+\frac{R}{L})} \\ &= \frac{s^2(2L^2) + 3RLs}{L(s+\frac{R}{L})} = \frac{s(2Ls + 3R)}{(s+\frac{R}{L})} \end{aligned}$$

poles:  $-\frac{R}{L}$

zeros:  $0, -\frac{3R}{2L}$

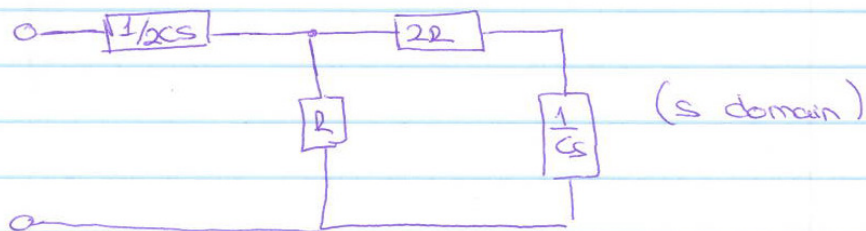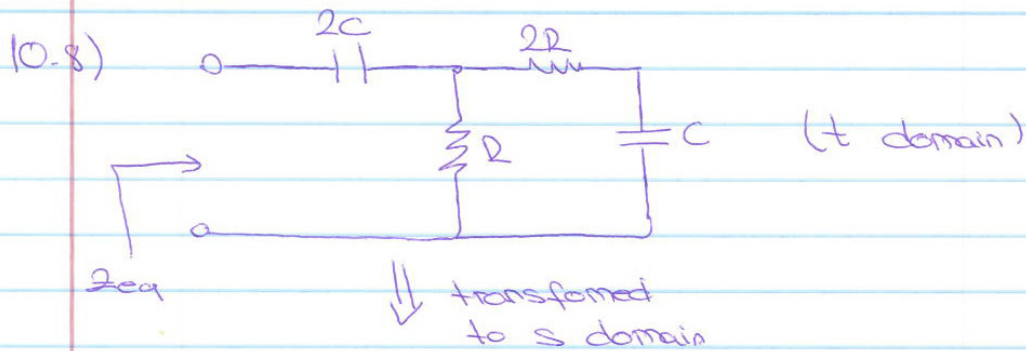

$$Z_{eq}(s) = \left( (2R + \frac{1}{Cs}) \parallel R \right) + \frac{1}{2Cs}$$

$$Z_{eq}(s) = \frac{R(2R + \frac{1}{Cs})}{3R + \frac{1}{Cs}} + \frac{1}{2Cs}$$

$$= \frac{2R^2Cs + R}{3RCs + 1} + \frac{1}{2Cs} = \frac{4R^2C^2s^2 + 5RCs + 1}{6R^2C^2s^2 + 2Cs}$$


$$\text{zeros: } \frac{-5RC \pm \sqrt{25R^2C^2 - 16R^2C^2}}{8R^2C^2} \Rightarrow s = \frac{-1}{4RC} \text{ and } \frac{1}{RC}$$

$$\text{poles: } s(6R^2C^2s + 2C) \Rightarrow s = 0 \text{ and } = \frac{-1}{3R^2C}$$

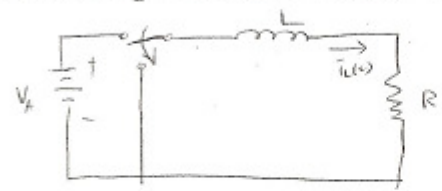
10.1 ✓

Switch moved to position B at  $t=0$

Transform the circuit into s domain & solve for  $I_L(s)$  and  $I_L(t)$



⇒ For  $t > 0$ ,  $I$  yields

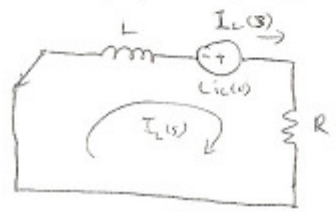

$$i_L(0) = \frac{V_A}{R}$$

$$LsI_L(s) - Li_L(0) + RI_L(s) = 0$$



$$I_L(s)(Ls + R) = L \frac{V_A}{R}$$

$$I_L(s) = \frac{L V_A}{R(Ls + R)}$$

$$= \frac{V_A}{R} \frac{1}{s + R/L}$$

$$\therefore I_L(t) = \mathcal{L}^{-1}\{I_L(s)\} = \frac{V_A}{R} e^{-R/L t} u(t)$$

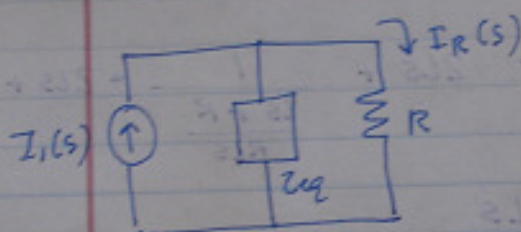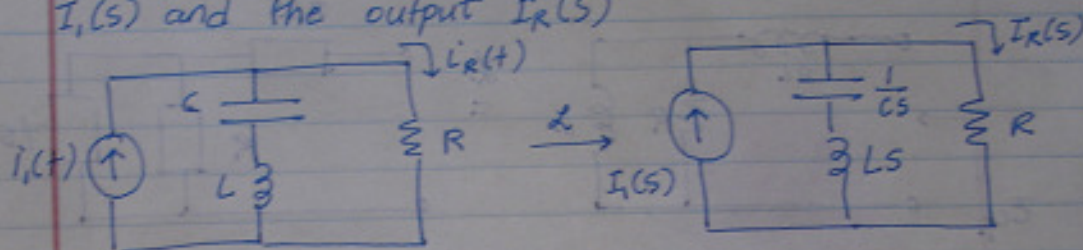10.19) The circuit in the figure below is in the zero state. Find the s-domain relationship between the input  $I_1(s)$  and the output  $I_R(s)$



$$Z_{eq} = \frac{1}{Cs} + LS$$


$$= \frac{1 + LCS^2}{Cs}$$

To find  $I_R(s)$ , use current division.


$$I_R(s) = \frac{Z_{eq}}{Z_{eq} + R} I_1(s) = \frac{\frac{1 + LCS^2}{Cs}}{R + \frac{1 + LCS^2}{Cs}} I_1(s)$$
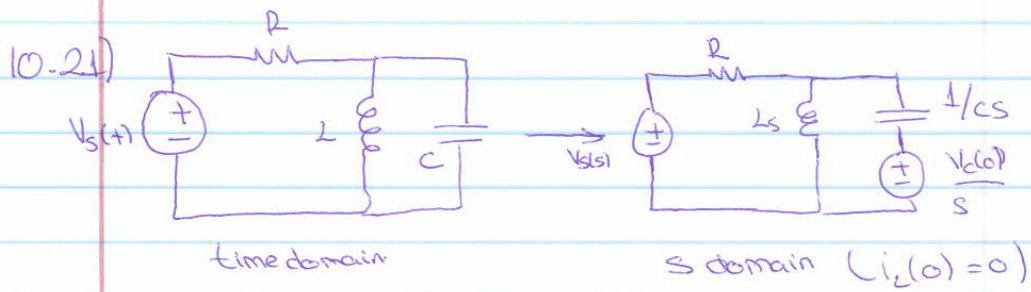
$$I_R(s) = \frac{1 + LCS^2}{RCs + 1 + LCS^2} I_1(s)$$






For zero state

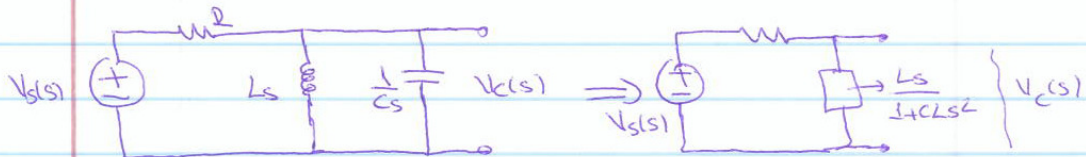

By voltage division

$$V_c(s) = \frac{Ls}{RCLs^2 + Ls + R} V_s(s)$$

For zero input



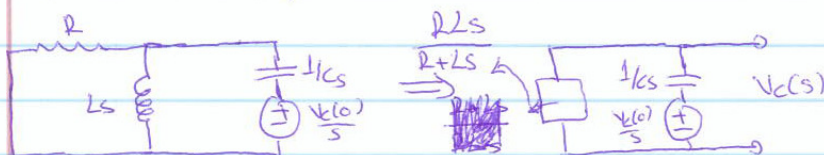


By using voltage division


$$V_c(s) = \frac{\left( \frac{R L s}{R + L s} \right) \frac{V_c(0)}{s}}{\left( \frac{1}{C s} + \frac{R L s}{R + L s} \right) s} = \frac{V_c R C L s}{(C R L s^2 + L s + R)}$$

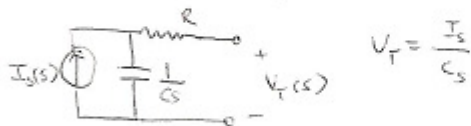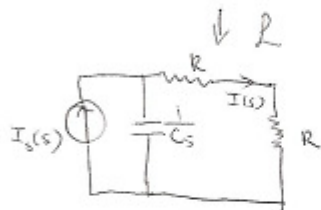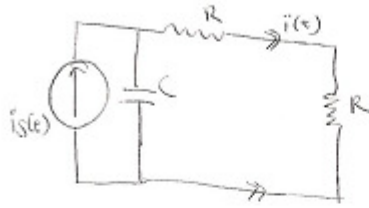10.25 V

Find the zero-state Thevenin Equivalent & use it to find the relationship between  $I_0(s)$  &  $I(s)$ .




$$V_T = \frac{I_0}{Cs}$$

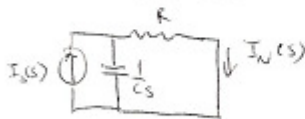

$$I_T(s) = \frac{1/R}{1/R + Cs} I_0(s) = \frac{I_0(s)}{RCs + 1}$$

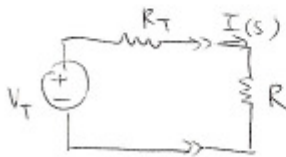
$$R_T = \frac{V_T}{I_T} = \frac{I_0/Cs}{I_0/Cs} \cdot \frac{RCs + 1}{1} = \frac{RCs + 1}{Cs}$$




$$I(s) = \frac{V_T}{R_T + R} = \frac{I_0(s)}{Cs} \frac{1}{\frac{RCs + 1}{Cs} + R}$$

$$\therefore I(s) = \frac{I_0(s)}{2RCs + 1}$$

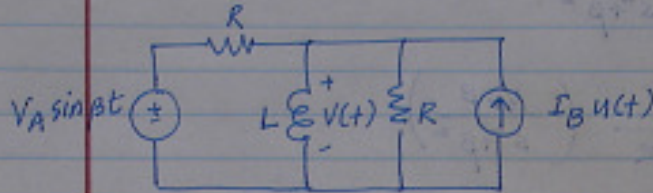
10.28) There is no initial energy stored in the circuit below. Transform the circuit into the s-domain and use superposition to find  $V(s)$ . Identify the forced and natural poles in  $V(s)$



Transforming into s-domain:

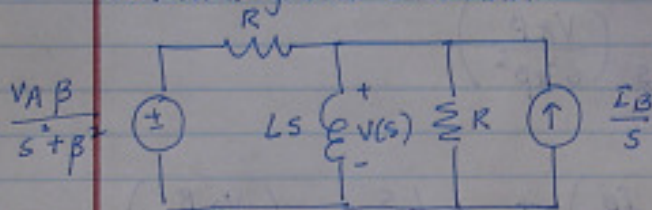


Superposition

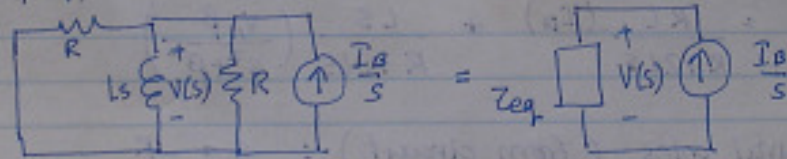

$$\frac{1}{Z_{eq}} = \frac{1}{R} + \frac{1}{R} + \frac{1}{Ls} = \frac{2Ls + R}{RLS}$$

$$Z_{eq} = \frac{RLS}{2Ls + R}$$
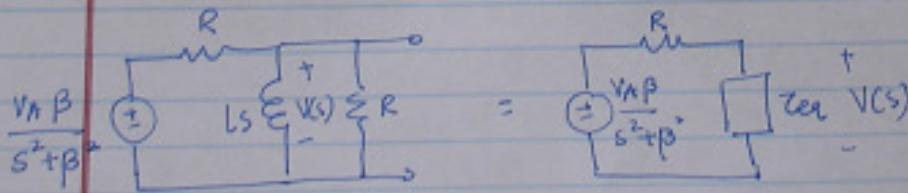
$$V(s) = Z_{eq} \frac{I_B}{s} = \frac{RLS}{1 + 2Ls} \left( \frac{I_B}{s} \right)$$



$$Z_{eq} = \frac{RLS}{R + Ls}$$



Using voltage division

$$V(s) = \frac{Z_{eq}}{Z_{eq} + R} \frac{VA\beta}{s^2 + \beta^2}$$

$$= \frac{RLS}{R + LS} \left( \frac{VA\beta}{s^2 + \beta^2} \right)$$

$$= \frac{RLS}{RLS + R^2 + RLS} \left( \frac{VA\beta}{s^2 + \beta^2} \right)$$

Total


$$V(s) = \frac{RLS}{R + 2LS} \left( \frac{I\beta}{s} \right) + \frac{LS}{LS + R + LS} \left( \frac{VA\beta}{s^2 + \beta^2} \right)$$

$$= \frac{RL}{R + 2LS} (I\beta) + \frac{LS}{R + 2LS} \left( \frac{VA\beta}{s^2 + \beta^2} \right)$$

Natural poles (from circuit) :  $s = \frac{-R}{2L}$

Forced poles (from input) :  $s = \pm j\beta$

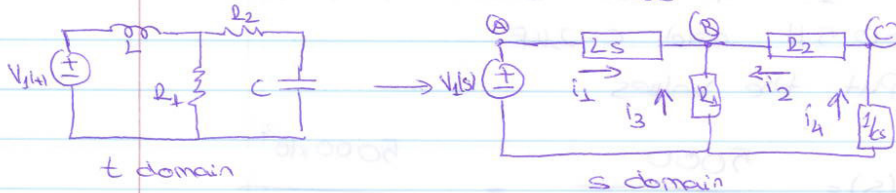10.32) There is no initial energy stored!



a) Node Voltage analysis

(A)  $V_A = V_1(s)$  and (B)  $i_1 + i_3 + i_2 = 0$  (C)  $i_4 - i_2 = 0 \Rightarrow i_4 = i_2$

Node B:  $\sum I = \frac{V_A - V_B}{Ls} + \frac{-V_B}{R_1} + \frac{V_C - V_B}{R_2}$

$$0 = \frac{V_A}{Ls} - V_B \left( \frac{1}{Ls} + \frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{V_C}{R_2} \quad (V_A = V_1(s))$$

$$\Rightarrow V_B \left( \frac{1}{Ls} + \frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{1}{R_2} V_C = \frac{V_1(s)}{Ls} \quad 1^{st} \text{ Eqn}$$

Node C:  $-\frac{V_C}{1/s} - \frac{V_C - V_B}{R_2} = 0 \Rightarrow -V_C \left( Cs + \frac{1}{R_2} \right) + V_B \frac{1}{R_2} = 0 \quad 2^{nd} \text{ eqn}$

b)  $V_2(s) = V_C(s)$  solve for  $V_C(s)$

$V_B = V_C (R_2(Cs + 1))$  from 2<sup>nd</sup> eqn substitute to 1<sup>st</sup> eqn.

$$V_C \left( \frac{(R_1 R_2 + R_2 Ls + R_1 Ls)(R_2(Cs + 1)) - 1}{R_1 R_2 Ls} - \frac{1}{R_2} \right) = \frac{V_1(s)}{Ls}$$

$$V_C = \frac{R_1 R_2 V_1(s)}{(R_1 R_2 + R_2 Ls + R_1 Ls)(R_2(Cs + 1)) - R_1 Ls} = \frac{V_1(s) R_1}{((R_1 + R_2)LC)^2 + (R_1 R_2 C + L)S + R_1}$$

c) Find  $v_2(t)$  for  $v_1(t) = 10u(t)$  V,  $R_1 = R_2 = 500 \Omega$   
 $L = 0.5$  H and  $C = 2 \mu$ F

Put the values

$$V_2(s) = \frac{5000}{s(10^{-3}s^2 + s + 500)} = \frac{5000 \times 10^3}{s(s^2 + 1000s + 500 \times 10^3)}$$

poles are  $s_1 = 0$ ,  $s_2 = -500 + j500$ ,  $s_3 = -500 - j500$

This has complex poles then we can write

$$V_2(s) = \frac{k_1}{s} + \frac{k_2}{s + 500 - j500} + \frac{k_2^*}{s + 500 + j500}$$

$$k_1 = \lim_{s \rightarrow 0} \frac{5000 \times 10^3}{s^2 + 1000s + 500 \times 10^3} = 10$$

$$k_2 = \lim_{s \rightarrow -500 + j500} \frac{5000 \times 10^3}{s(s + 500 + j500)} = -\frac{10}{1 + j} = -5 + j5$$




$$V_2(s) = \frac{10}{s} + \frac{(-5 + j5)}{s + 500 - j500} + \frac{(-5 - j5)}{s + 500 + j500}$$

$$v_2(t) = \left[ 10 + (-5 + j5)e^{(-500 + j500)t} + (-5 - j5)e^{(-500 - j500)t} \right] u(t)$$

$$v_2(t) = \left[ 10 + 10\sqrt{2} e^{-500t} \cos(500t + 35/4) \right] u(t)$$

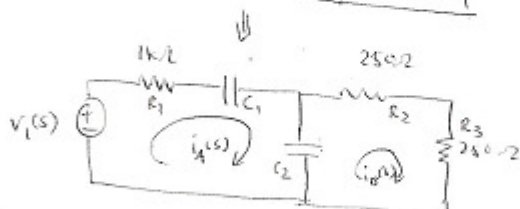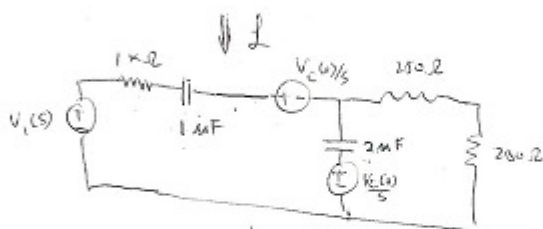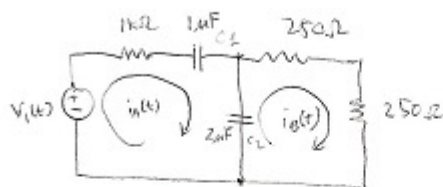10.37 ✓

There is no internal energy stored. Find zero-state mesh currents  $i_A(t)$  &  $i_B(t)$  when  $v_1(t) = 1000e^{-t}$  V.



Mesh A

$$-V_1(s) + \left( R_1 + \frac{1}{C_1 s} \right) i_A(s) + \frac{1}{C_2 s} (i_A(s) - i_B(s)) = 0$$

Mesh B

$$(i_B(s) - i_A(s)) \frac{1}{C_2 s} + (R_2 + R_3) i_B(s) = 0$$

10.37 cont'd

Rearranging these eqns:

$$\text{Mesh A: } \left( R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s} \right) i_A(s) - \frac{1}{C_2 s} i_B(s) = \frac{100}{s} \quad \text{--- (1)}$$

$$\text{Mesh B: } -\frac{1}{C_2 s} i_A(s) + \left( \frac{1}{C_2 s} + R_2 + R_3 \right) i_B(s) = 0 \quad \text{--- (2)}$$

$$\begin{bmatrix} R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s} & -\frac{1}{C_2 s} \\ -\frac{1}{C_2 s} & \frac{1}{C_2 s} + R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_A(s) \\ i_B(s) \end{bmatrix} = \begin{bmatrix} \frac{100}{s} \\ 0 \end{bmatrix}$$

From (2),

$$i_A(s) = (1 + C_2 R_2 s + C_2 R_3 s) i_B(s) \quad \text{--- (3)}$$

plug (3) into (1).

$$\left( R_1 + \frac{1}{C_1 s} + \frac{1}{C_2 s} \right) (1 + C_2 R_2 s + C_2 R_3 s) i_B(s) - \frac{1}{C_2 s} i_B(s) = \frac{100}{s}$$

$$\left[ R_1 + C_2 R_1 R_2 s + C_2 R_1 R_3 s + \frac{1}{C_1 s} + \frac{C_2 R_2}{C_1} + \frac{C_2 R_3}{C_1} + \frac{1}{C_2 s} + R_2 + R_3 - \frac{1}{C_2 s} \right] i_B(s) = \frac{100}{s}$$

$$\left[ 1000 + 2400(1000)(250)s + 2400(1000)(250)s + \frac{1}{10^{-6}s} + 2(250) + 2(250) + 500 \right] i_B(s) = \frac{100}{s}$$

$$\left[ 1000 + \frac{1}{2}s + \frac{1}{2}s + \frac{10^6}{s} + 1500 \right] i_B(s) = \frac{100}{s}$$

$$i_B(s) = \frac{100}{2500s + s^2 + 10^6} = \frac{100}{s^2 + 2500s + 10^6}$$

}



$$\begin{aligned}
 i_A(s) &= (1 + (2R_2s + 2R_3s)) i_B(s) \\
 &= (1 + 2 \times 10^6 (250)s + 2 \times 10^6 (250)s) i_B(s) \\
 &= \left(1 + \frac{s}{2500} + \frac{s}{2500}\right) i_B(s) \\
 &= \left(1 + \frac{s}{1250}\right) i_B(s) \\
 &= \left(1 + \frac{s}{1250}\right) \left(\frac{100}{s^2 + 2500s + 10^6}\right) \\
 &= \frac{1000 + s}{10(s^2 + 2500s + 10^6)}
 \end{aligned}$$

∥

$$i_A(s) = \frac{100}{3} \left[ \frac{1}{s+500} + \frac{2}{s+2500} \right]$$

$$\mathcal{L}^{-1} \int i_A(t) = \frac{100}{3} \left[ e^{-500t} + 2e^{-2500t} \right]$$

$$i_B(s) = \frac{100}{s^2 + 2500s + 10^6} \Rightarrow 2 \times \frac{100}{3} \left[ \frac{1}{s+500} - \frac{1}{s+2500} \right]$$

$$\mathcal{L}^{-1} \int i_B(t) = \frac{200}{3} \left[ e^{-500t} - e^{-2500t} \right]$$