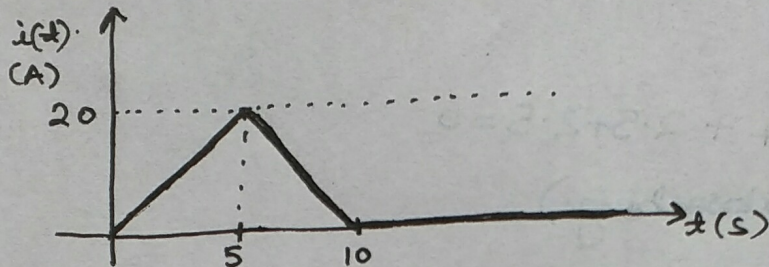


$$1.11) \quad i(t) = \begin{cases} 4t \text{ A} & 0 \leq t \leq 5 \text{ s} \\ 40 - 4t \text{ A} & 5 < t \leq 10 \text{ s} \\ 0 \text{ A} & t > 10 \text{ s} \end{cases}$$



We know that $i = \frac{dq}{dt} \Rightarrow q = \int i dt$.

which is infact area under the $i(t)$ vs. t curve.

$$q = \text{Area} = \frac{1}{2} \times (10 - 0) \times (20 - 0) = \frac{1}{2} \times 10 \times 20 = 100 \text{ A-s} = 100 \text{ C.}$$

When calculated using integral,

$$q = \int_0^5 4t dt + \int_5^{10} (40 - 4t) dt + \int_{10}^{\infty} 0 dt$$

$$= 4 \times \left[\frac{t^2}{2} \right]_0^5 + \left(40t - \frac{4t^2}{2} \right) \Big|_5^{10} + 0$$

$$= 50 + 200 - 150 = 100 \text{ A-s} = 100 \text{ C.}$$

1.19) Maximum power dissipated by device $P = 0.25 \text{ W}$

Voltage $V = 9 \text{ V}$.

$$P_{\text{max}} = V \times i_{\text{max}}$$

$$\Rightarrow i_{\text{max}} = \frac{P_{\text{max}}}{V} = \frac{0.25}{9} = 0.0278 \text{ A}$$

1.23) $P_1 = V_1 i_1 = 20 \times (-2) = -40W$

$P_2 = 20W$ $P_3 = 10W$ $P_4 = ?$ $P_5 = P_6 = 2.5W$

Since sum of device powers = 0


$$\Rightarrow \sum_{i=1}^6 P_i = 0$$

$$\Rightarrow -40 + 20 + 10 + P_4 + 2.5 + 2.5 = 0$$


$$\Rightarrow P_4 = 5W \text{ (absorbing)}$$

$$i_4 = 1A$$
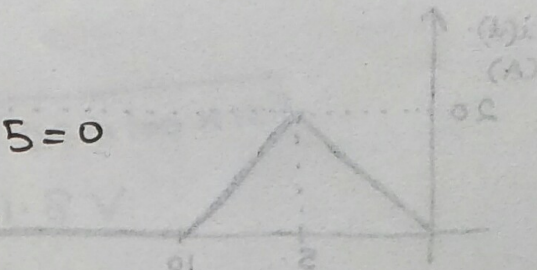
$$\therefore V_4 = \frac{P_4}{i_4} = \frac{5}{1} = 5V$$



2.6)

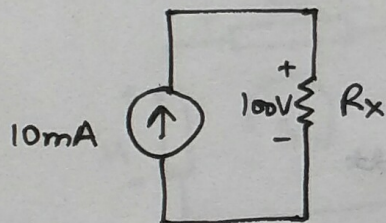

$$R_x = \frac{100}{10 \times 10^{-3}} = 100 \times 10^2 = 10k\Omega$$

Power delivered to resistor = $V_i = 100 \times 10 \times 10^{-3} = 1W$

2.7) Resistor has 3 orange stripes followed by a gold stripe.

$$R = 33k\Omega \pm 5\%$$

given resistance = $34.9k\Omega$

tolerance margin here = $\frac{34.9 - 33}{33} \times 100 = 5.76\%$

This does not lie in tolerance limit.

Hence, the resistor is not properly coded.

correct coding: orange, yellow, orange, gold. or 3 stripes of orange & followed by silver.


2.9) $R = 100 \text{ k}\Omega$
Power rating $P = 0.125 \text{ W}$

$\therefore V_{\text{max}} = ?$

$$\therefore P = \frac{V_{\text{max}}^2}{R}$$

$$\Rightarrow V_{\text{max}} = \sqrt{P \times R} = \sqrt{0.125 \times 100 \times 10^3}$$
$$= \sqrt{125 \times 100} = 111.8 \text{ V}$$

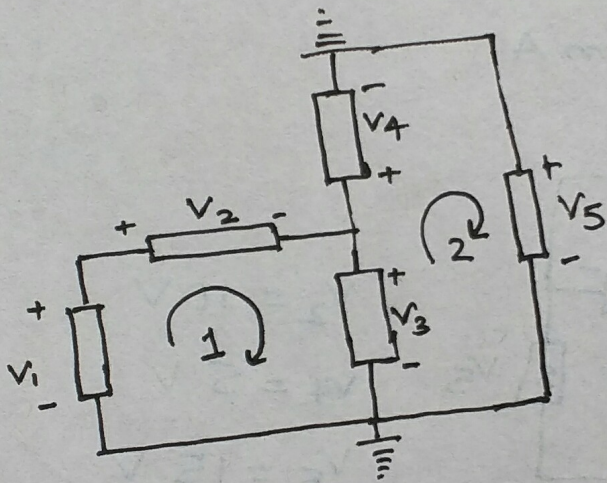2.14) $V_1 = 3 \text{ V}$ $V_3 = 5 \text{ V}$.




$$\text{KVL in 1} \Rightarrow -V_1 + V_2 + V_3 = 0$$
$$\Rightarrow -3 + V_2 + 5 = 0$$
$$\Rightarrow V_2 = -2 \text{ V}$$

For V_5 , both terminals are connected to ground.
 \therefore voltage drop $V_5 = 0 \text{ V}$.

$$\text{KVL in 2} \Rightarrow -V_3 + V_4 + V_5 = 0$$
$$\Rightarrow -5 + V_4 + 0 = 0$$
$$\Rightarrow V_4 = 5 \text{ V}$$

2.16)

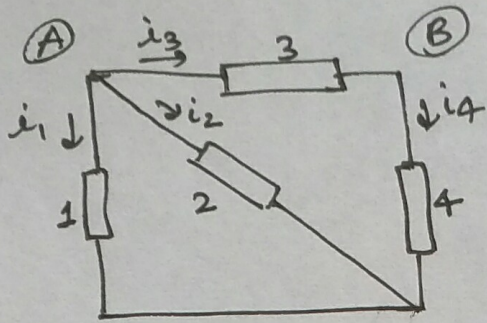

$$i_2 = -20 \text{ mA}$$


$$i_4 = 10 \text{ mA}$$

$$i_1, i_3 = ?$$

KCL at B $\Rightarrow i_3 - i_4 = 0$
 $\Rightarrow i_3 = i_4 = 10 \text{ mA}$

KCL at A $\Rightarrow -i_1 - i_2 - i_3 = 0$
 $\Rightarrow -i_1 + 20 \text{ mA} - 10 \text{ mA} = 0$
 $\Rightarrow i_1 = 10 \text{ mA}$

2.21)

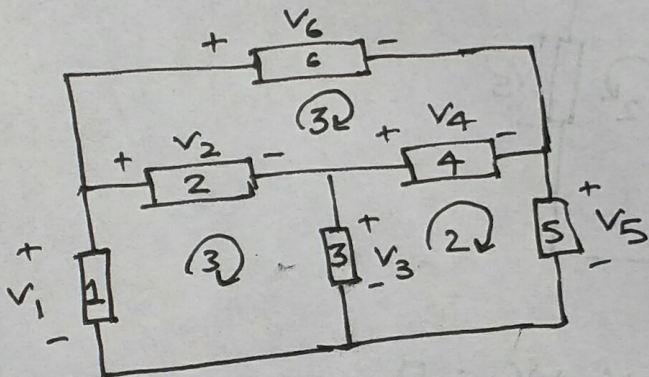

$$v_2 = 10 \text{ V}$$

$$v_4 = 5 \text{ V}$$

$$v_5 = 15 \text{ V}$$

KVL in 3: $-v_2 + v_6 - v_4 = 0$
 $\Rightarrow -10 \text{ V} + v_6 - 5 \text{ V} = 0$
 $\Rightarrow v_6 = 15 \text{ V}$

KVL in 2: $-v_3 + v_4 + v_5 = 0$
 $\Rightarrow v_3 = v_4 + v_5 = 5 + 15 = 20 \text{ V}$

KVL in 1: $-v_1 + v_2 + v_3 = 0$
 $\Rightarrow v_1 = v_2 + v_3 = 10 + 20 = 30 \text{ V}$

2.22) KCL at A: $i_1 - i_2 - i_4 + i_3 = 0 \Rightarrow i_4 = i_1 - i_2 + i_3$
 $\Rightarrow i_4 = 25 \text{ mA} - 10 \text{ mA} - 15 \text{ mA} = 0 \text{ mA}$

KCL at B: $-i_1 + i_2 - i_5 = 0 \Rightarrow i_5 = -i_1 + i_2$
 $= -25 \text{ mA} + 10 \text{ mA}$
 $= -15 \text{ mA}$