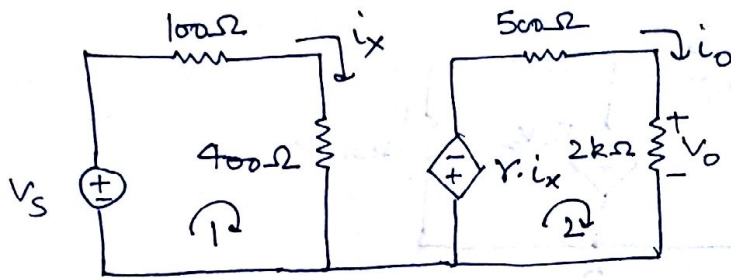


4.1)



$$\gamma = 5 \text{ k}\Omega$$

$$\text{KVL in 1: } i_x = \frac{V_s}{100 + 400} = 2 V_s \text{ mA}$$

$$\text{KVL in 2: } i_o = \frac{-\gamma \cdot i_x}{500 + 2000} = \frac{-5 \times 10^3 i_x}{2500} = -2 i_x$$


Using voltage division:

$$V_o = i_o \times 2000 = -2 i_x \times 2000 = -4 i_x \text{ kV}$$

$$\therefore \frac{V_o}{V_s} = \frac{-4 i_x \times 10^3}{V_s} = \frac{-4 \times 10^3 \times 2 V_s \times 10^{-3}}{V_s} = -8$$

$$\frac{i_o}{i_x} = \frac{-2 i_x}{i_x} = -2$$

4.5)

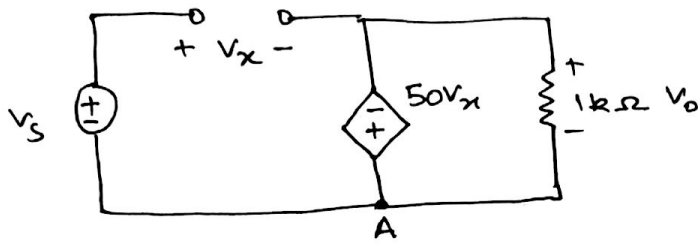

Assume A is grounded

$$\text{then } v_x = v_s - (-50v_x)$$


$$\Rightarrow v_x = \frac{-v_s}{49}$$

$$\text{Also, } v_o = -50v_x = -50 \times \left(\frac{-v_s}{49} \right)$$

$$= \frac{50}{49} v_s.$$

$$\therefore \frac{v_o}{v_s} = \frac{50}{49}$$

4.8)

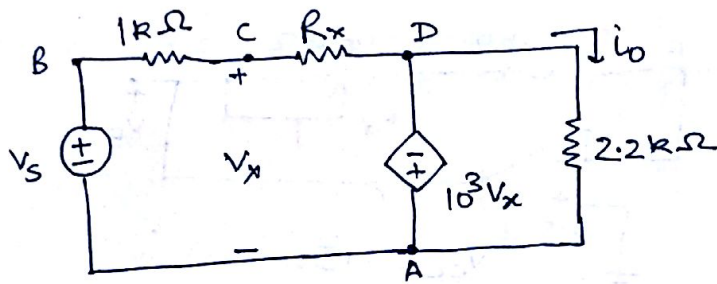

let A be grounded.

(a)

$$\text{Then } V_B = V_s$$

$$V_C = V_x$$

$$V_D = -10^3 V_x$$

$$\text{Also, } 2.2 \times 10^3 \times i_o = -10^3 V_x.$$

$$i_o = -\frac{1}{2.2} V_x$$

Node voltage equation at C.

$$\frac{V_C - V_B}{1 \times 10^3} = \frac{V_C - V_D}{R_x} = 0$$

$$\Rightarrow \frac{V_x - V_s}{10^3} = -\frac{V_x - (-10^3 V_x)}{R_x}$$

$$\Rightarrow V_x R_x - V_s R_x = -10^3 (1 + 10^3) V_x$$

$$\Rightarrow V_x \left(1 + \frac{10^3 (1 + 10^3)}{R_x} \right) = V_s$$


$$\therefore V_x = \frac{V_s}{\left(1 + \frac{10^3 (1 + 10^3)}{R_x} \right)}$$

$$\therefore \frac{i_o}{V_s} = -\frac{1}{2.2} \times \frac{1}{\left(1 + \frac{10^3 (1 + 10^3)}{R_x} \right)}$$

$$\text{b) } \frac{i_o}{V_s} = -0.227 \Rightarrow -\frac{1}{2.2} \times \frac{1}{\left(1 + \frac{10^3 (1 + 10^3)}{R_x} \right)}$$

$$\Rightarrow 0.227 \times 2.2 \approx \frac{1}{1 + \frac{10^6}{R_x}} \Rightarrow R_x \approx 10^6 \Omega.$$

4.28)

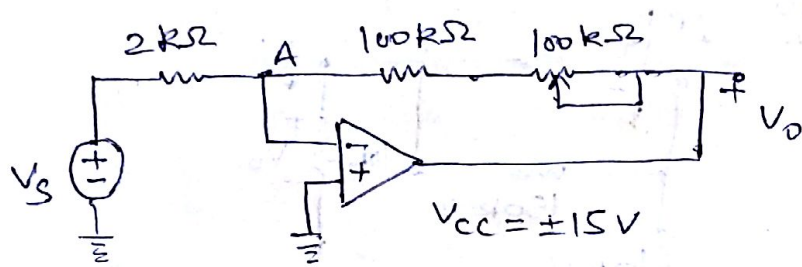

let variable resistor be R_v .

such that $0 \leq R_v \leq 100k\Omega$.

$$V_A = 0V.$$

This is an inverting amplifier with


$$V_o = - \left(\frac{100k\Omega + R_v}{2k\Omega} \right) V_s.$$

$$\therefore K = \frac{V_o}{V_s} = - \frac{100 \times 10^3 + R_v}{2 \times 10^3}$$

as $0 \leq R_v \leq 100k\Omega$.

$$\boxed{-100 \leq K = \frac{V_o}{V_s} \leq -50}$$


4.30)

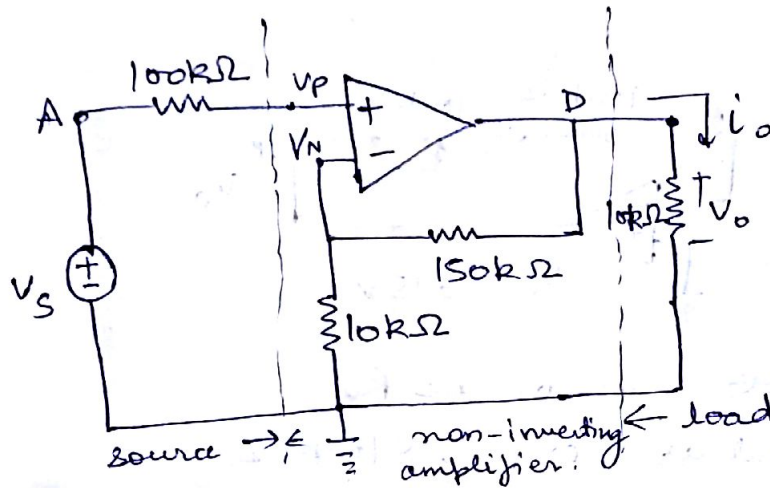

a) This is a non-inverting op amp with a load. Also, the load won't change the output voltage of the op amp.

$$V_P = V_N = V_S$$

eqvt. circuit :

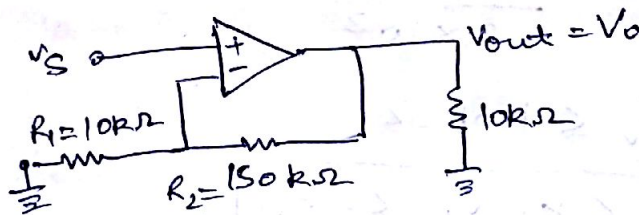

$$V_o = \left(1 + \frac{R_2}{R_1}\right) V_S = 16 V_S \quad (\text{as from class})$$

b) $V_S = 1V, 3V$.

$$i_o = \frac{V_o}{10 \times 10^3}$$

$$V_o (V_S = 1V) = 16V < V_{CC}$$

$$V_o (V_S = 3V) = 48V > V_{CC}$$


$$\therefore V_o = 24V$$

$$\rightarrow \boxed{i_o = 1.6 \text{ mA}}$$

op-amp gets saturated

$$\rightarrow \boxed{i_o = 2.4 \text{ mA}}$$

4.31)

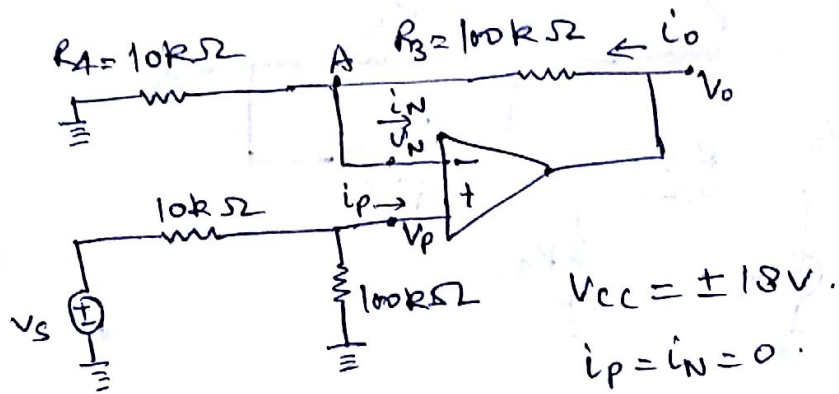

a) Using voltage division & observing that it is a non-inverting op-amp, we get.

$$V_p = \frac{100 \times 10^3}{100 \times 10^3 + 10 \times 10^3} \times V_s = \frac{10}{11} V_s$$

$$V_n = V_p$$

$$\text{Also, } K_s = \frac{V_p}{V_s} = \frac{10}{11}$$

$$K_{AMP} = \frac{V_o}{V_p} = \frac{R_3 + R_A}{R_A} = \frac{100 \times 10^3 + 10 \times 10^3}{10 \times 10^3} = 11$$

$$\therefore K_{circuit} = \frac{V_o}{V_s} = \frac{V_p}{V_s} \times \frac{V_o}{V_p} = K_s \times K_{AMP}$$

$$= \frac{10}{11} \times 11 = 10$$

$$\therefore \boxed{V_o = 10V_s}$$

b) $V_s = 0.5V, 2V$

$$i_0 = \frac{V_o - V_A}{100 \times 10^3} = \frac{10V_s - \frac{10}{11}V_s}{100 \times 10^3}$$

$$V_o (V_s = 0.5V) = 10 \times 0.5V = 5V$$

$$\therefore \boxed{i_0 = 45.45 \mu A}$$


$V_o (V_s = 2V) = 10 \times 2V = 20V > V_{cc}$ so op-amp gets saturated $\therefore V_o = 18V$

$$\boxed{i_0 = \frac{18 - \frac{10}{11} \times 2}{100 \times 10^3} = 161.8 \mu A}$$

Alternatively, since $i_n = 0$.

$$\therefore i_0 = \frac{V_o \times}{(R_3 + R_A)}$$

4.33) a)

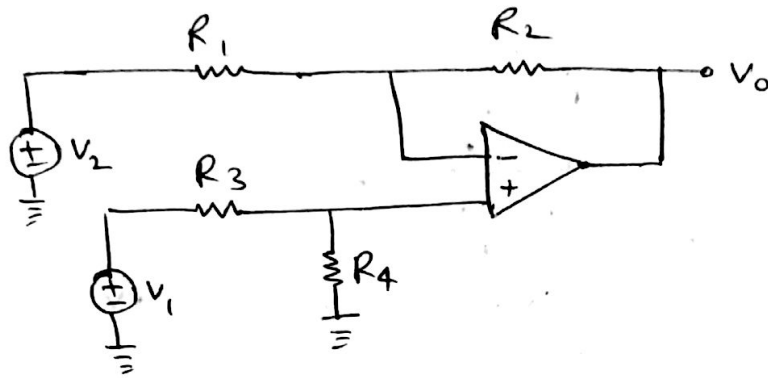

a) This is a differential amplifier, as derived in class. when v_1 is turned off.

$$V_{01} = -\frac{R_2}{R_1} V_2$$

when V_2 is turned off, it is a voltage divider at input with a noninverting amplifier.

$$V_{02} = \frac{R_4}{R_3 + R_4} \times \frac{R_1 + R_2}{R_1} \times V_1$$


$$\therefore V_0 = V_{01} + V_{02}$$

$$= -\left(\frac{R_2}{R_1}\right) V_2 + \left(\frac{R_4}{R_3 + R_4}\right) \left(\frac{R_1 + R_2}{R_1}\right) V_1$$

for $R_1 = 10 \text{ k}\Omega$, $R_2 = 30 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_4 = 20 \text{ k}\Omega$.

$$\Rightarrow \boxed{V_0 = 2V_1 - 3V_2}$$

4.36)

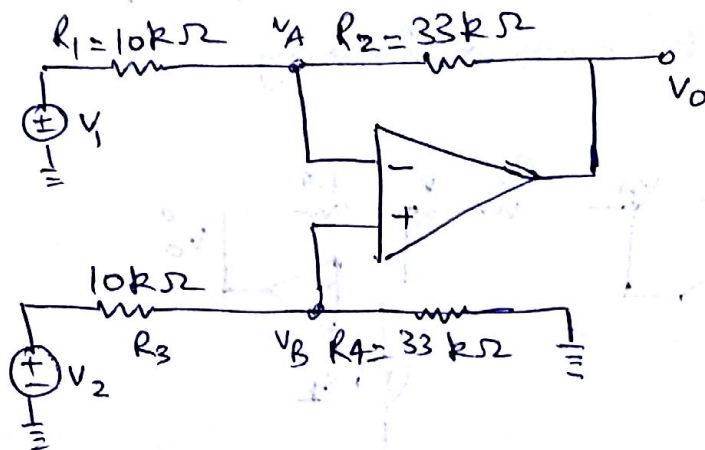

This is a differential amplifier.

We can also use superposition principle for V_0 in terms of V_1 & V_2

(1) Turn V_2 off: inverting amplifier.

$$V_{01} = -\frac{R_2}{R_1} V_1 = -3.3 V_1$$

(2) Turn V_1 off: noninverting amplifier.

$$\begin{aligned} V_{02} &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_2 \\ &= \frac{33}{10} \times 4.3 \times V_2 \end{aligned}$$


$$\therefore V_0 = V_{01} + V_{02} = -3.3 V_1 + 4.3 \times \frac{33}{10} V_2$$

$$= 3.3(V_2 - V_1)$$

differential amplifier.

can be calculated directly.

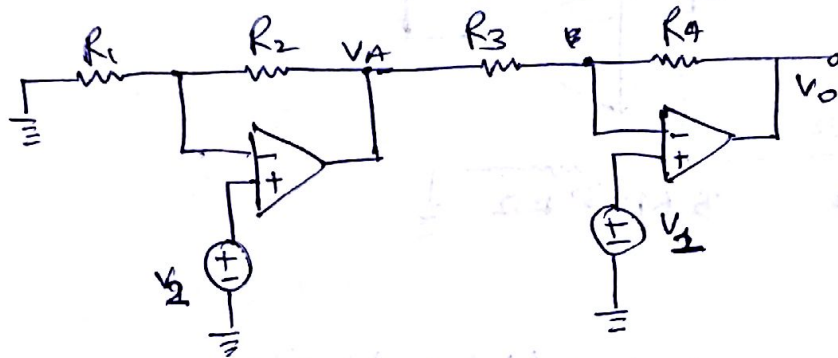- b) Both inputs must be into high input resistance amplifiers to avoid loading.



It is interconnection of noninverting & inverting amplifier, with v_2 applied at noninverting input.

V_A is output of the non-inverting amplifier.

$$V_A = \left(\frac{R_1 + R_2}{R_1} \right) v_1$$

as derived in class.


$$V_0 = V_{01} + V_{02}$$

$$= \left[\frac{R_3 + R_4}{R_3} \right] v_1 - \left(\frac{R_4}{R_3} \right) \left(\frac{R_1 + R_2}{R_1} \right) v_2$$

$$R_1 = 10k\Omega, R_2 = R_3 = R_4 = 20k\Omega$$

$$\Rightarrow \boxed{V_0 = 2v_1 - 3v_2}$$

4.38)

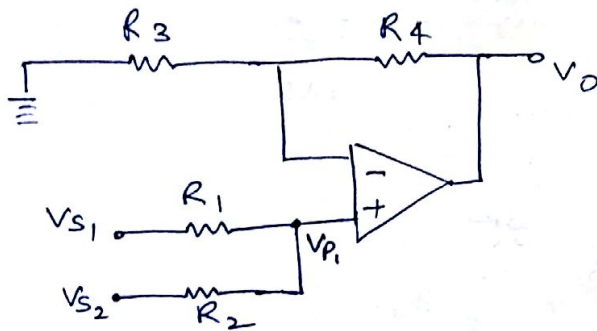

Using superposition,

(i) first set $V_{S2} = 0$.

it is a non-inverting amplifier with voltage divider at input. ($V_{S2} = 0$).

$$\therefore V_{P1} = \frac{R_2}{R_1 + R_2} V_{S1}$$

$$V_{O1} = \frac{R_3 + R_4}{R_3} V_{P1} = \frac{R_3 + R_4}{R_3} \times \frac{R_2}{R_1 + R_2} \times V_{S1}$$


(ii) similarly set $V_{S1} = 0$.

By symmetry of problem.

$$V_{O2} = \frac{R_3 + R_4}{R_3} \times \frac{R_1}{R_1 + R_2} V_{S2}$$


$$\therefore V_0 = V_{O1} + V_{O2} = \frac{R_3 + R_4}{R_3} \times \frac{1}{R_1 + R_2} (R_2 V_{S1} + R_1 V_{S2})$$

4.39)

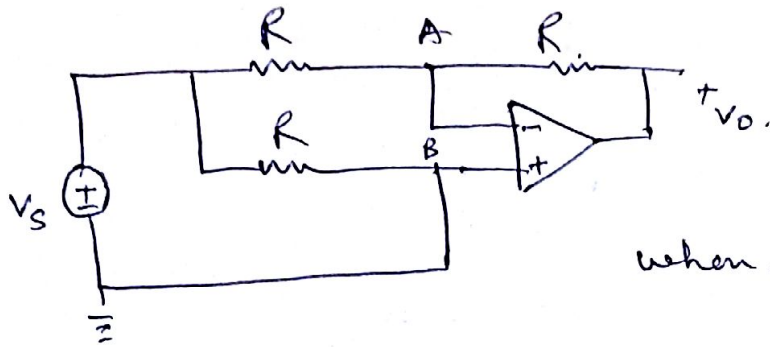

when switch is closed.

This is an inverting op-amp,

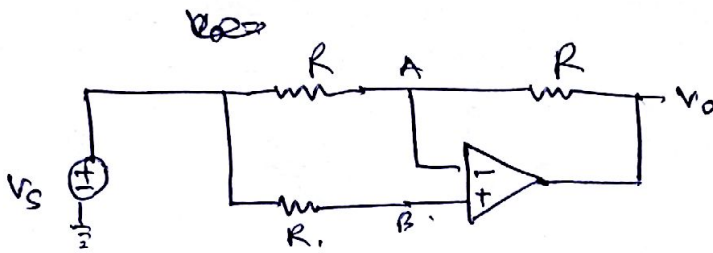

differential op-amp

This is a ~~non-inverting~~ (with infinite resistance to ground at input).

Hence, claim is false.

Alternate!

when switch is closed.

$$V_B = 0 \Rightarrow V_A = V_B = 0.$$

$$V_o = -V_s.$$

when switch is open.

$$V_B = V_s \Rightarrow V_A = V_s.$$

$$\Rightarrow V_o = V_s.$$