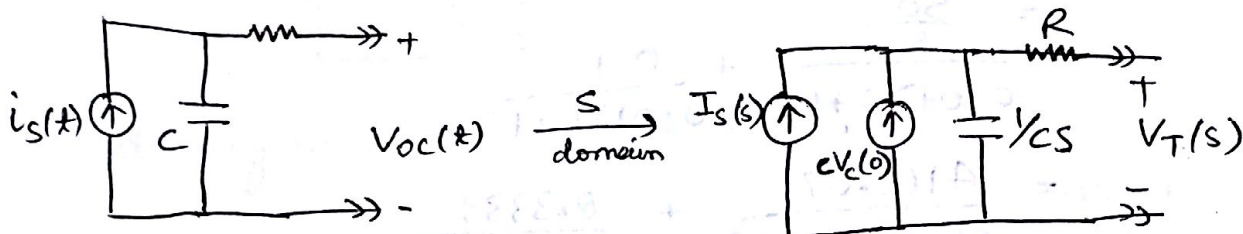


10.35) a) for open-circuit voltage:




$$\therefore V_T(s) = (I_S(s) + CV_c(0)) \cdot \frac{1}{Cs}$$

$$= \frac{I_S(s) + CV_0}{Cs}$$

(as  $V_c(0) = V_0$  Volts)
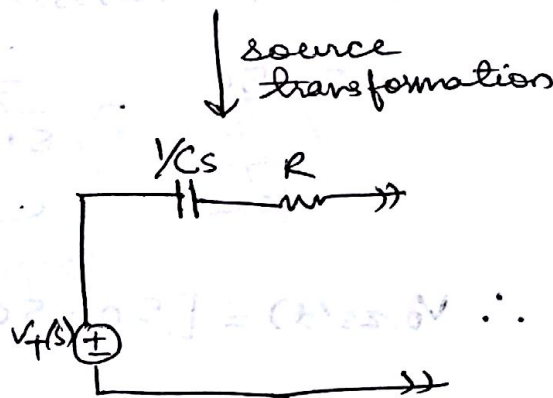
$$Z_T(s) = \frac{1}{Cs} + R = \frac{RCs + 1}{Cs}$$



b) Voltage delivered to load (by voltage division)

$$V_0(s) = \frac{5R}{5R + Z_T(s)} V_T(s) = \frac{5R(I_S(s) + cV_0)}{6RCs + 1}$$

$$V_c(0) = 10V \Rightarrow V_0 = 10$$

$$i_s(t) = 10u(t) \text{ mA} \Rightarrow I_S(s) = \frac{10 \times 10^{-3}}{s} = \frac{10^{-2}}{s}$$

$$R = 1 \text{ k}\Omega, C = 2 \mu\text{F}$$

$$\therefore V_0(s) = \frac{5 \times 10^3 \left( \frac{10^{-2}}{s} + 2 \times 10^{-6} \times 10 \right)}{6 \times 10^3 \times 2 \times 10^{-6} s + 1}$$

$$= \frac{\frac{50}{s} + 0.1}{0.012s + 1} = \frac{50}{s} + \frac{8.3333 - 50}{s + 83.3333}$$

$$\therefore V_0(s) = [50 - 41.667e^{-83.3333t}] u(t)$$

c)

$$V_o(s) = \frac{5RI_s(s)}{6RCs+1} + \frac{5RCV_o}{6RCs+1}$$

$\xrightarrow{\text{zero-state}}$ 
 $\xrightarrow{\text{zero-input}}$

$$= \frac{50}{0.012s+1} + \frac{0.1}{0.012s+1}$$

$$= \frac{4166.67}{s(s+83.3333)} + \frac{8.3333}{s+83.3333}$$


$$= \underbrace{\frac{50}{s}}_{\text{forced}} - \underbrace{\frac{50}{s+83.3333} + \frac{8.3333}{s+83.3333}}_{\text{natural}}$$

$$\therefore V_{o,zs}(t) = [50 - 50e^{-83.3333t}]u(t) \text{ V}$$

$$V_{o,zi}(t) = 8.3333e^{-83.3333t}u(t) \text{ V}$$

$$V_{o,\text{forced}}(t) = 50u(t) \text{ V} \quad V_{o,\text{natural}}(t) = -41.667e^{-83.3333t}u(t) \text{ V}$$

11.1)

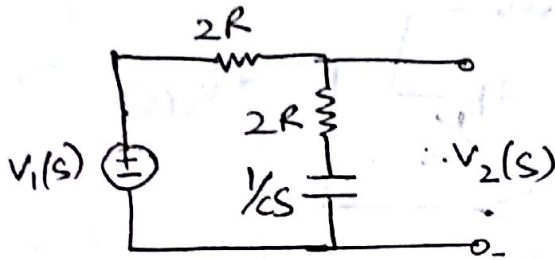

$$\begin{aligned} \text{driving point impedance} &= 2R + 2R + \frac{1}{Cs} \\ &= 4R + \frac{1}{Cs} = \frac{4RCs + 1}{Cs} \end{aligned}$$

For voltage transfer function.


$$V_2(s) = \text{voltage across } \left( 2R + \frac{1}{Cs} \right)$$

$$\therefore V_2(s) = \frac{\left( 2R + \frac{1}{Cs} \right)}{\left( \frac{4RCs + 1}{Cs} \right)} \times V_1(s)$$

$$= \frac{2RCs + 1}{4RCs + 1} \times V_1(s)$$

$$\therefore T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{2RCs + 1}{4RCs + 1}$$

11.11)

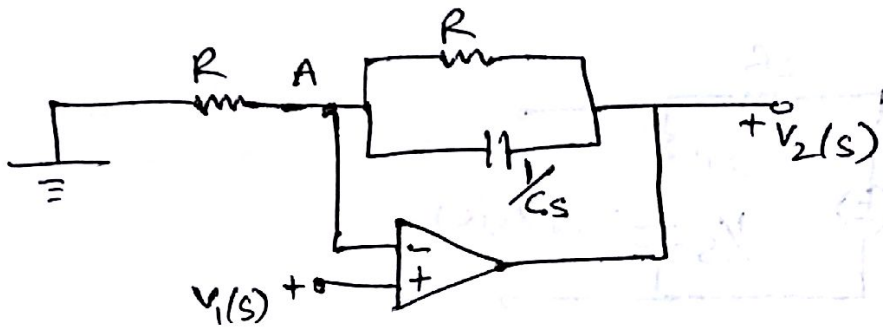

Using nodal analysis at A:  $(V_A(s) = V_1(s))$ .

$$\frac{V_A(s) - 0}{R} = (V_2(s) - V_A(s)) \left( \frac{1}{R} + Cs \right)$$

$$\Rightarrow \frac{V_A(s)}{R} = (V_2(s) - V_A(s)) \frac{(1 + RCs)}{R}$$

$$\Rightarrow V_1(s) + V_1(s) \frac{(1 + RCs)}{R} = V_2(s) (1 + RCs)$$

$$\Rightarrow \frac{V_2(s)}{V_1(s)} = T_V(s) = \frac{2 + RCs}{1 + RCs}$$


alternately it is a non-inverting op-amp.

$$\therefore \frac{V_2(s)}{V_1(s)} = \frac{R + R \parallel \frac{1}{Cs}}{R} = \frac{2 + RCs}{1 + RCs}$$

Pole at  $s = -\frac{1}{RC}$  we want  $\frac{1}{RC} = 100 \text{ krad/s} = 10^5 \text{ rad/s}$

$$\therefore \boxed{R = 1 \text{ k}\Omega \text{ \& } C = 10 \text{ pF}}$$

11.15)

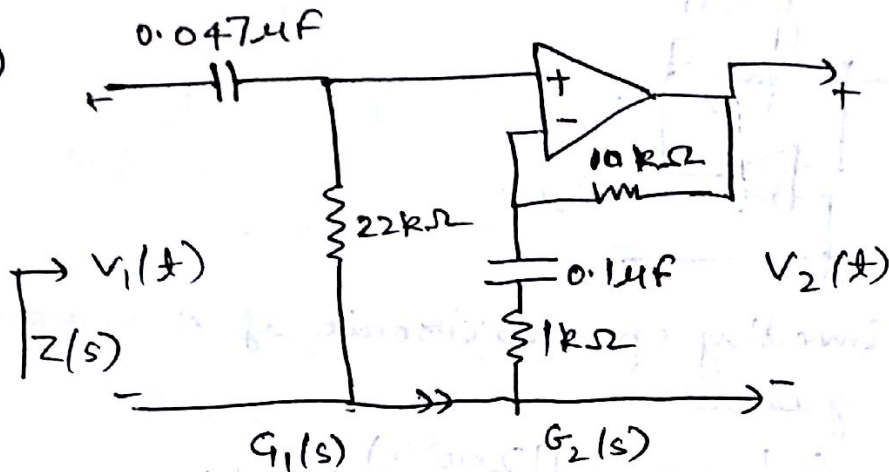

This is a cascade of voltage divider & non-inverting op-amp.

It is non-loading, hence  $T_V(s) = G_1(s) \cdot G_2(s)$   
(because of infinite input impedance of ideal op-amp)

$$G_1(s) = \frac{22k\Omega}{22k\Omega + \frac{1}{47 \times 10^{-9} \text{ F} \cdot s}} = \frac{22 \times 10^3 \times 47 \times 10^{-9} s}{22 \times 10^3 \times 47 \times 10^{-9} s + 1}$$

$$= \frac{1.034 \times 10^{-3} s}{1 + 1.034 \times 10^{-3} s} = \frac{s}{s + 967.12}$$

$$G_2(s) = 1 + \frac{10k\Omega}{1k\Omega + \frac{1}{0.1 \times 10^{-6} \text{ F} \cdot s}} = 1 + \frac{10^{-3} s}{1 + 10^{-4} s}$$


$$= 1 + \frac{10s}{10000 + s} = 11 \left( \frac{s + 909.1}{s + 10000} \right)$$

$$\therefore T_V(s) = G_1(s) \cdot G_2(s) = \frac{11 \cdot s (s + 909.1)}{(s + 967.12)(s + 10000)}$$

$$\text{Zeros} = \{-909.1, 0\}$$

$$\text{poles} = \{-967.12, -10000\}$$

11.35)

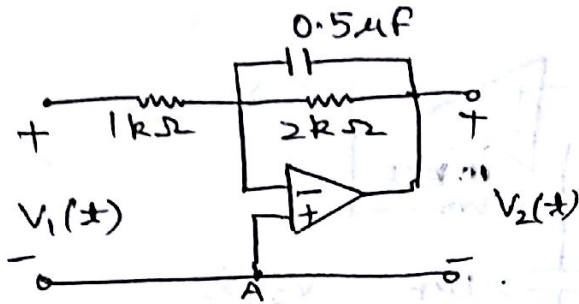

This is inverting op amp circuit if A is assumed to be grounded.

$$\therefore \frac{V_2(s)}{V_1(s)} = - \frac{\left( \frac{1}{0.5 \times 10^{-6} \text{ F} \cdot s} \parallel 2 \times 10^3 \Omega \right)}{1 \times 10^3 \Omega} = - \frac{\left( \frac{1}{2 \times 10^3 + 0.5 \times 10^{-6} s} \right)^{-1}}{1 \times 10^3}$$

$$\Rightarrow T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{-2}{1 + 10^{-3}s} = \frac{-2000}{s + 1000} \quad \therefore \text{pole} = -1000 \text{ rad/s}$$

For  $v(t) = 10 \cos \omega t$ , use  $T_V(j\omega)$  to find  $V_{2SS}(t)$

$$T_V(j\omega) = \frac{-2000}{j\omega + 1000} = \frac{-2000(-j\omega + 1000)}{\omega^2 + 10^6} = \frac{-2 \times 10^6 + 2000j\omega}{\omega^2 + 10^6}$$

$$\Rightarrow V_{2SS}(t) = 10 |T_V(j\omega)| \cdot \cos(\omega t + \angle T_V(j\omega))$$

$$(\omega = 500 \text{ rad/s})$$

$$\therefore |T_V(j\omega)| = 1.789, \quad \angle T_V(j\omega) = 2.678 \text{ rad}$$

$$V_{2SS}(t) = 17.89 \cos(500t + 2.678) \text{ V}$$

$$= \cancel{16 \cos 500t} (-16 \cos 500t - 8 \sin 500t) \text{ V}$$

$$(\omega = 1 \text{ k rad/s})$$

$$|T_V(j\omega)| = 1.414, \quad \angle T_V(j\omega) = 2.356 \text{ rad}$$


$$V_{2SS}(t) = 14.14 \cos(1000t + 2.356) \text{ V} = -10(\cos 1000t + \sin 1000t) \text{ V}$$

$$(\omega = 10 \text{ k rad/s})$$

$$|T_V(j\omega)| = 0.1990, \quad \angle T_V(j\omega) = 1.670 \text{ rad}$$

$$V_{2SS}(t) = 1.99 \cos(10000t + 1.670) \text{ V} \\ = (-0.198 \cos 10000t - 1.98 \sin 10000t) \text{ V}$$

110.36)

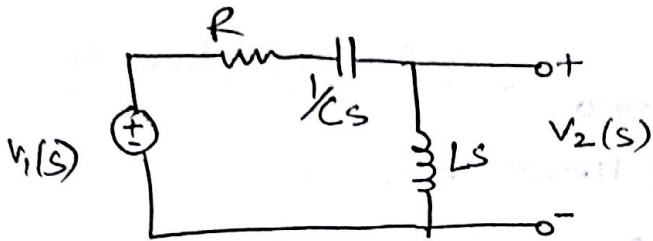

$$\begin{aligned} R &= 10 \Omega \\ C &= 50 \mu\text{F} \\ L &= 5 \text{mH} \end{aligned}$$

$$T(s) = \frac{v_2(s)}{v_1(s)} = \frac{Ls}{R + \frac{1}{Cs} + Ls} = \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{s^2}{s^2 + 2 \times 10^3 s + 4 \times 10^6}$$

$\therefore$  poles at  $\{-1000 \pm 1732j\}$ , zeros at  $\{0, 0\}$

when  $v_1(t) = 25 \cos(2000t)$ ,  $\omega = 2000$ ,  $T(j\omega) = j$

$$|T(j\omega)| = 1, \angle T(j\omega) = 1.57$$

$$\therefore v_{2SS}(t) = 25 \cos(2000t + 1.57) \text{ V}$$

For  $v_1(t) = 25 \cos(10^4 t)$ ,  $\omega = 10^4$

$$|T(j\omega)| = 1.02, \angle T(j\omega) = 0.205$$


$$\Rightarrow v_{2SS}(t) = 25.5 \cos(10^4 t + 0.205) \text{ V}$$

$$11.63) \quad T_V(s) = \frac{20000}{s+1000}$$


$$T_V(s) = (-1) \cdot \left( \frac{-20000}{s+1000} \right)$$

↓                      ↓  
inverting          inverting.

For an inverting op amp.

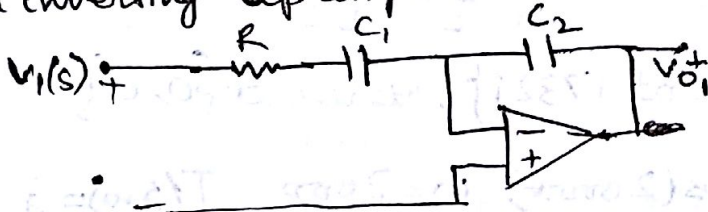

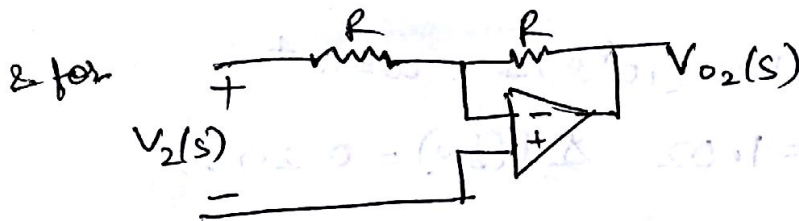
$$\frac{V_{01}(s)}{V_1(s)} = - \frac{1/sC_2}{R + \frac{1}{sC_1}} = - \frac{C_1/C_2}{1 + RC_1s}$$



$$\frac{V_{02}(s)}{V_2(s)} = - \frac{R}{R} = -1$$

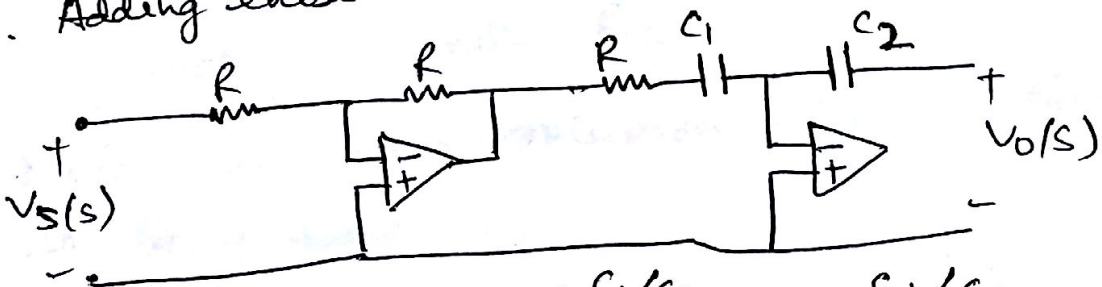∴ Adding these circuits to multiply gains.



$$\therefore \text{gain } K_V = -1 \times - \frac{C_1/C_2}{1+RC_1s} = \frac{C_1/C_2}{1+RC_1s}$$

choose  $R_1 = 1 \text{ k}\Omega$ ,  $C_1 = 1 \mu\text{F}$ .

$C_2 = 0.05 \mu\text{F}$




11.63) Alternate solution

$$T_V(s) = \frac{20000}{s+1000} = (20) * \left( \frac{1000}{s+1000} \right)$$

↑ voltage divider.

↑ non-inverting amplifier.

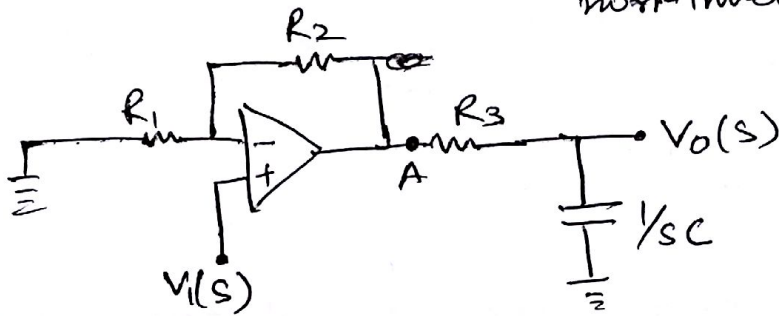

$$\therefore \frac{V_A(s)}{V_I(s)} = \frac{R_1 + R_2}{R_1} \quad \text{choose } R_1 \text{ \& } R_2 \text{ such that}$$

$$\frac{R_1 + R_2}{R_1} = 20.$$

Now, using voltage division...

$$\frac{V_O(s)}{V_A(s)} = \frac{1/sC}{1/sC + R_3} = \frac{1}{R_3Cs + 1} = \frac{1/R_3C}{s + 1/R_3C}$$

choose  $R_3C$  such that


$$1/R_3C = 1000$$

$$\text{let } R_3 = 1k\Omega \quad C = 1\mu F$$

$$\text{let } R_1 = 100\Omega \quad R_2 = 1.9k\Omega.$$

Note: in this solution only one op-amp is being used.

12.4)

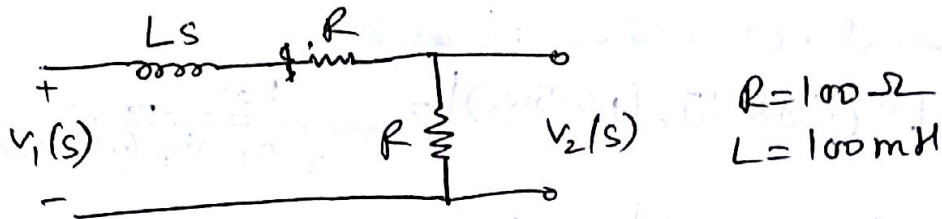

$$T_V = \frac{V_2(s)}{V_1(s)} = \frac{R}{R + Ls + R} = \frac{100}{100 + 100 + 100 \times 10^{-3}s}$$

$$= \frac{100}{200 + 0.1s} = \frac{1000}{s + 2000}$$

DC gain =  $\lim_{s \rightarrow 0} T_V(s) = \frac{1000}{2000} = 0.5 = \frac{1}{2}$

Infinite frequency gain  $\Rightarrow \lim_{s \rightarrow \infty} T_V(s) = 0$

cutoff frequency  $\omega_c$  where  $|T_V(j\omega_c)| = \frac{1}{\sqrt{2}} T_{V \text{ max.}}$

$$\Rightarrow \frac{1000}{\sqrt{(2000)^2 + \omega^2}} = \frac{1}{\sqrt{2}} \times \frac{1}{2}$$

$$\Rightarrow (1000)^2 \times (2\sqrt{2})^2 = (2000)^2 + \omega^2$$


$$\Rightarrow \omega^2 = 4 \times 10^6$$

$$\Rightarrow \boxed{\omega_c = 2000 \text{ rad/s}} \text{ low-pass filter}$$

b)  $|T(j\omega)|_{dB} = 20 \log_{10} |T(j\omega)|$

gain at  $\omega_c = 0 = 20 \log_{10}(0.5) = -6.02 \text{ dB}$

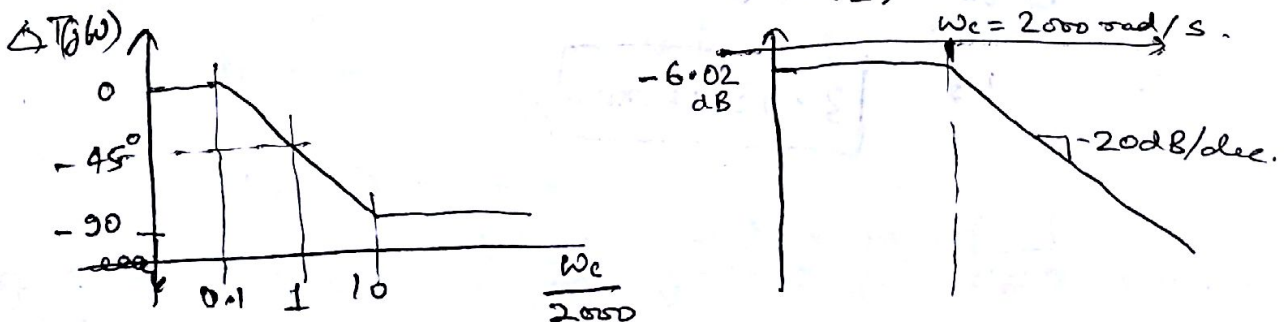gain at  $\omega_c = 20 \log_{10}\left(\frac{1}{2\sqrt{2}}\right) = -9.03 \text{ dB}$



c) gain at  $\omega = 0.5\omega_c, \omega_c$  &  $2\omega_c$ .

$$|T_v(j\omega)| = |T_v(j0.5\omega_c)| = \frac{1000}{\sqrt{(2000)^2 + (0.5 \times 2000)^2}} = 0.4472.$$

$$|T_v(j\omega_c)| = \frac{1}{\sqrt{2}} \times \frac{1}{2} = 0.3536.$$

$$|T_v(2\omega_cj)| = \frac{1000}{\sqrt{(2000)^2 + (2 \times 2000)^2}} = 0.2236.$$

d) from matlab plot.

$$|T_v(j0.5\omega_c)|_{dB} = -7$$

$$\Rightarrow |T_v(j0.5\omega_c)| = 0.4467.$$

$$|T_v(j\omega_c)|_{dB} = \cancel{0.3536} - 9.03$$

$$\Rightarrow |T_v(j\omega_c)| = 0.3536.$$

$$|T_v(j2\omega_c)|_{dB} = -13$$

$$\Rightarrow |T_v(j2\omega_c)| = 0.2239.$$

Hence we see that the values calculated in c) are almost the same as from the bode plot in matlab.

e) one octave past the cut-off

$$\omega = 2\omega_c \quad \text{Gain } |T_v(2j\omega_c)|_{dB} = 0.2236$$

$$\text{Gain } |T_v(j\omega_c)|_{dB} = \cancel{9.03} \text{ dB}$$

$$\text{Gain } |T_v(2j\omega_c)|_{dB} = \cancel{13.01} \text{ dB}$$


magnitude

the filter, down the  
the passband gain  
at one octave past  
the cut-off is


$$= 20 \log \left( \frac{0.2236}{0.5} \right)$$

$$= -6.99 \text{ dB lower.}$$
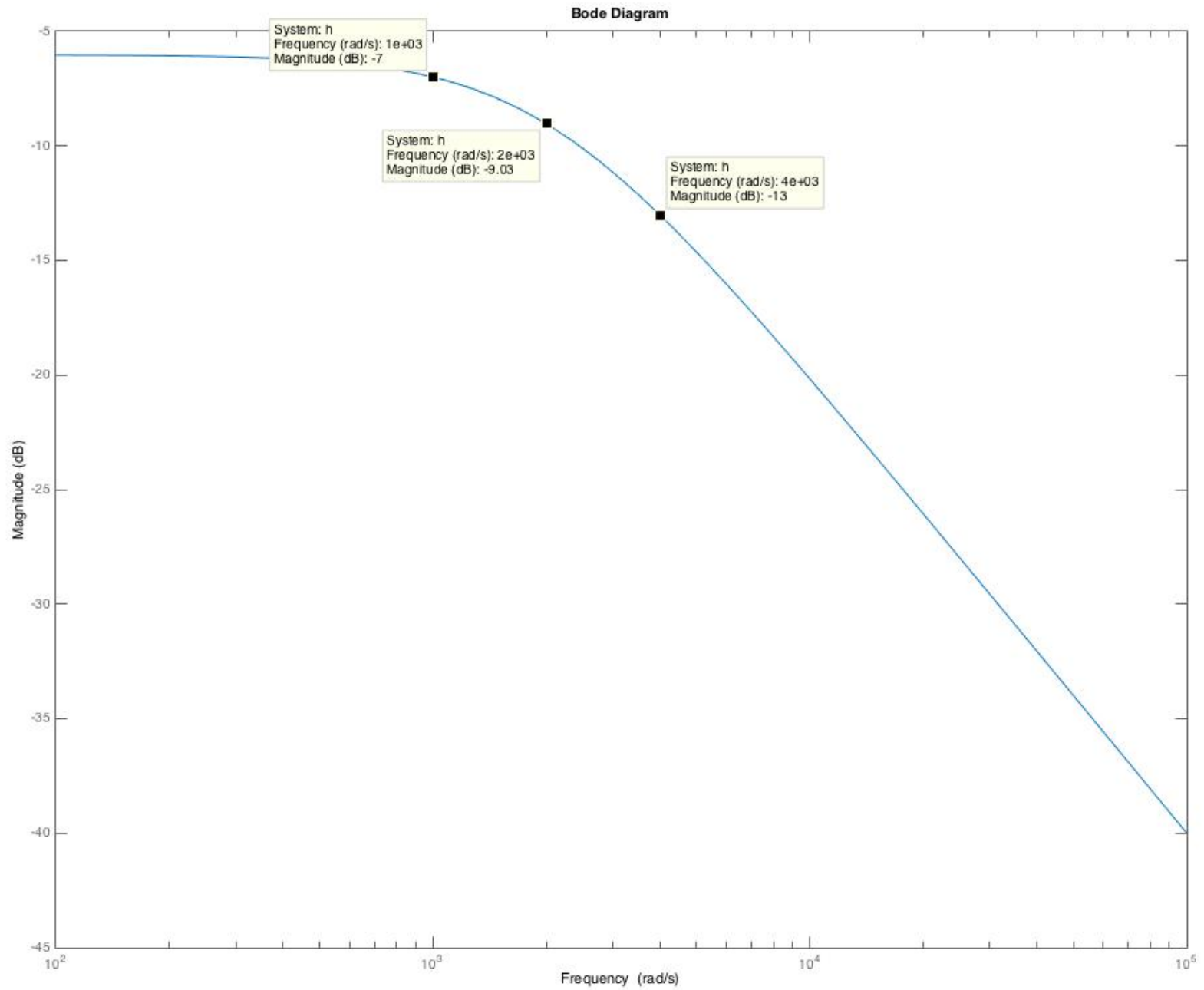
$$\text{Gain in passband} = \text{DC gain} = \frac{1}{2}$$



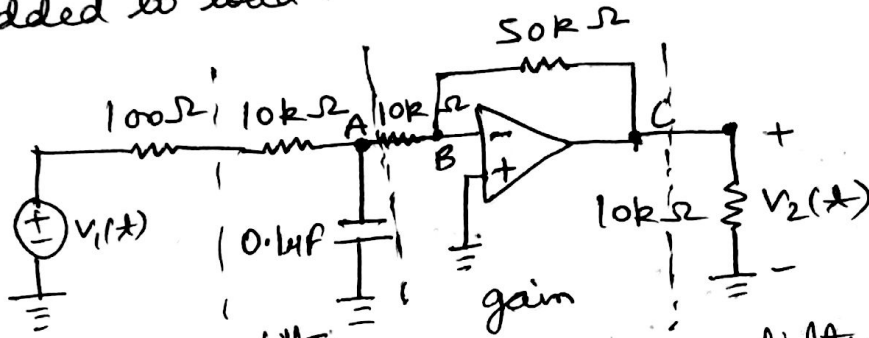12.9) Let us look first at configuration when filter stage is added between source & gain stage. & gain stage is added to load:



Here the gain stage loads the filter stage.  
in s transform domain,  
at node A.

$$\frac{V_1(s) - V_A(s)}{10k\Omega + 100\Omega} = \frac{V_A(s) - 0}{(0.1\mu F \cdot s)^{-1}} + \frac{V_A(s) - 0}{10k\Omega}$$

$$\Rightarrow \frac{V_1(s)}{10.1k\Omega} = \left( \frac{1}{10k\Omega} + \frac{1}{10.1k\Omega} + 0.1\mu F \cdot s \right) V_A(s)$$

$$\Rightarrow \frac{V_A(s)}{V_1(s)} = \frac{1/10.1k\Omega}{\left( \frac{1}{10k\Omega} + \frac{1}{10.1k\Omega} + 0.1\mu F \cdot s \right)}$$

$$\therefore T_F(s) = \frac{V_A(s)}{V_1(s)} = \frac{1}{\left( \frac{10.1 \times 10^3}{10 \times 10^3} + \frac{10.1 \times 10^3}{10.1 \times 10^3} + \frac{0.1 \times 10^{-6} \times 10^6}{10^3} \right) s}$$

$$= \frac{1}{2.01 + 0.00101s}$$

for gain stage.

$$V_2(s) = \frac{-50k\Omega}{10k\Omega} V_A(s) = -5 V_A(s)$$

$$\Rightarrow T_g(s) = -5$$

$$\therefore T_V(s) = \frac{V_2(s)}{V_1(s)} = \frac{V_A(s)}{V_1(s)} \times \frac{V_2(s)}{V_A(s)} = \left( \frac{1}{2.01 + 0.00101s} \right) \times (-5)$$


hence (-5)

For this  $\omega_c = 1990 \text{ rad/s}$ .

& DC gain =  $-2.488$ .

hence we do not get the desired cutoff frequency of  $1 \text{krad/s}$  & gain of  $-5$ .

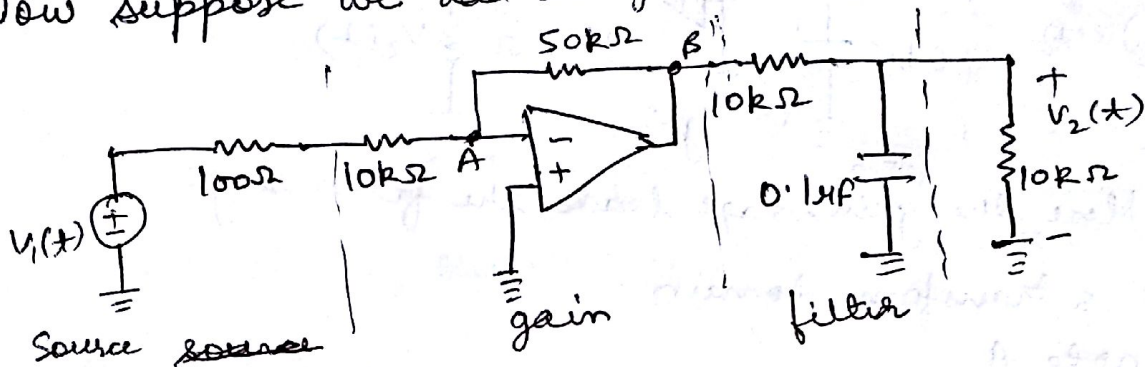Now suppose we add the filter stage after gain stage



here, the gain stage loads the source.

in s-domain

at Node A:

$$\frac{V_1(s) - V_A(s)}{100\Omega + 10\text{k}\Omega} = \frac{V_A(s) - V_B(s)}{50\text{k}\Omega}$$

$$V_A(s) = 0$$

can use

$$\left( \frac{V_B(s)}{V_1(s)} = -\frac{R_2}{R_1} \right)$$

$R_2 = 50\text{k}\Omega$   
 $R_1 = 10\text{k}\Omega + 100\Omega$

$$\Rightarrow \frac{V_1(s)}{10100} = -\frac{V_B(s)}{50000}$$

$$\Rightarrow \frac{V_B(s)}{V_1(s)} = -\frac{50000}{10100} = -4.95$$

$$V_2(s) = \frac{Z_2}{Z_1 + Z_2} V_B(s)$$

$$\Rightarrow \frac{V_2(s)}{V_B(s)} = \frac{\left( \frac{1}{10\text{k}\Omega} + 0.1\mu\text{F} \cdot s \right)^{-1}}{10\text{k}\Omega + \left( 0.1\mu\text{F} \cdot s + \frac{1}{10\text{k}\Omega} \right)^{-1}} = \frac{1000}{s + 2000}$$

we can multiply the gains


$$\therefore V_2(s) = \frac{1000}{s + 2000} \times V_B(s) = \frac{1000}{s + 2000} \times (-4.95)$$

$$\omega_c = 2000, \text{ DC gain} = -4.95 \times \frac{1000}{2000} = -2.475$$

hence we do not get the desired output.

Now, to fix this, we have the source connected to gain stage, which is then connected to the filter. Now we add a buffer between filter & the load.

So the circuit diagram looks like.

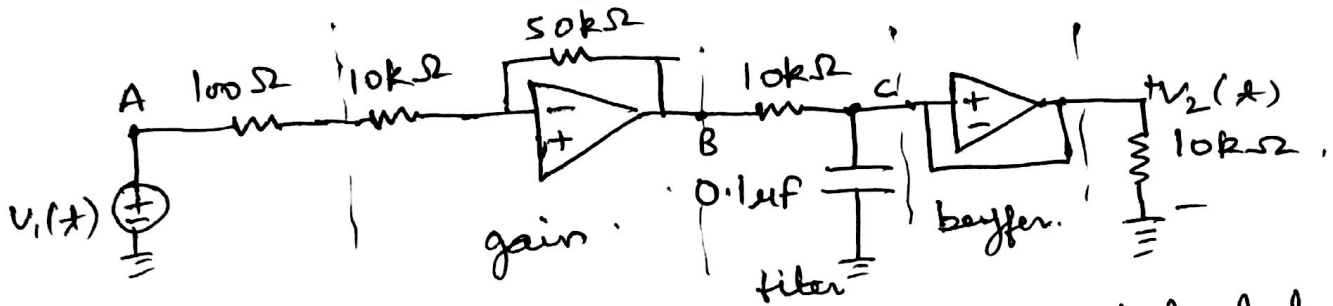

Using the buffer, the voltage divider is not loaded with load.

$$\therefore \frac{V_B(s)}{V_A(s)} = -\frac{50 \times 10^3 \Omega}{10 \times 10^3 \Omega + 100 \Omega} = -4.95$$

$$\begin{aligned} \frac{V_C(s)}{V_B(s)} &= \frac{\frac{1}{0.1 \times 10^{-6} \times s}}{\frac{1}{0.1 \times 10^{-6} \text{ s}} + 10 \times 10^3} = \frac{10^7/s}{10^7/s + 10^4} \\ &= \frac{10^3/s}{10^3/s + 1} = \frac{10^3}{s + 10^3} = \frac{1000}{s + 1000} \end{aligned}$$


$$\therefore V_2(s) = V_C(s)$$

$$\therefore T_V(s) = \frac{V_2(s)}{V_C(s)} \times \frac{V_C(s)}{V_B(s)} \times \frac{V_B(s)}{V_A(s)} = \frac{-4.95 \times 1000}{s + 1000}$$

$$\begin{aligned} \therefore \text{DC gain} &= -4.95 \approx -5 && \text{(desired)} \\ \text{cutoff freq} &= 1000 \text{ rad/s} && \text{(desired)} \end{aligned}$$

12.43) We need a low-pass filter with  $\omega_c = 10 \text{ rad/s}$  & gain of -5. The filter must fit.

12.43)

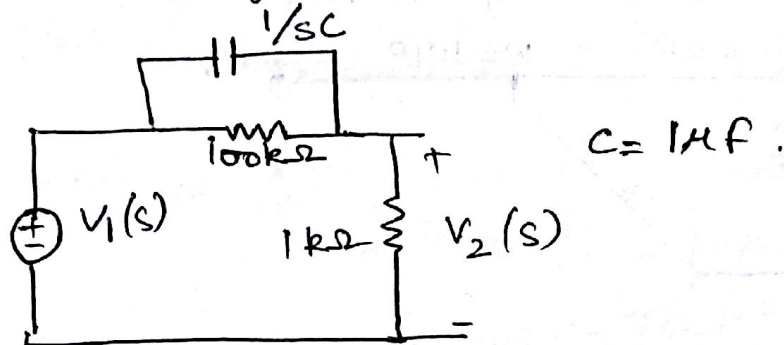

$$\begin{aligned} \therefore \frac{V_2(s)}{V_1(s)} = T_V(s) &= \frac{1 \times 10^3}{1 \times 10^3 + (100 \times 10^3 \parallel \frac{1}{s \times 1 \times 10^{-6}})} \\ &= \frac{10^3}{10^3 + \frac{10^5 \times \frac{1}{s \times 10^{-6}}}{10^5 + \frac{1}{s \times 10^{-6}}}} \\ &= \frac{10^3}{10^3 + \frac{10^5}{10^5 \cdot 10^{-1} s + 1}} = \frac{10^3}{10^3 + \frac{10^6}{s + 10}} \\ &= \frac{1}{1 + \frac{10^3}{s + 10}} = \frac{s + 10}{s + 1010} \end{aligned}$$

a) DC gain:  $\lim_{s \rightarrow 0} T_V(s) = \frac{10}{1010} = 0.0099 \text{ in dB} = -40.41 \text{ dB}$


$\infty$  gain:  $\lim_{s \rightarrow \infty} T_V(s) = 1$ , in dB = 0

corner frequency = 10 (zero), 1010 (pole)


no critical point at  $\omega = 0$ , the slope of gain asymptote entering plot from left is 0 till it reaches, corner frequency 10, from where slope



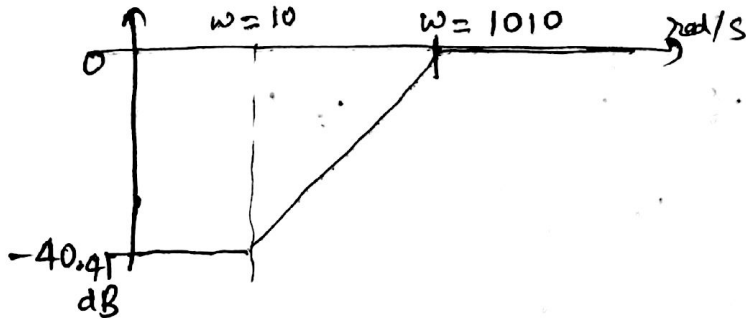becomes +1. This happens till another corner frequency 1010 & slope change to 0 ( $+1 - 1 = 0$ )  
 & becomes straight (horizontal)



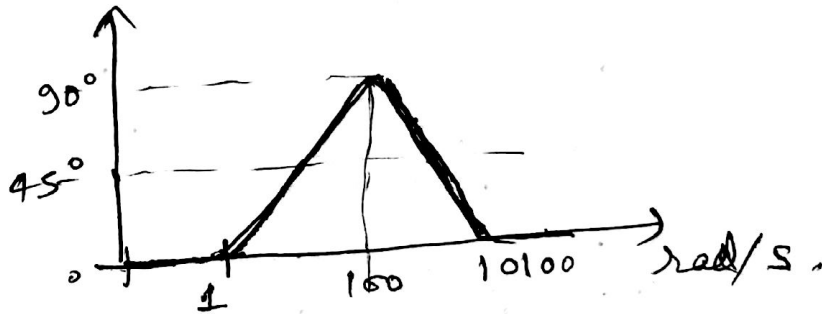similar observation is done for phase where  
 phase starts increasing from  $0.1 \times 10$  to  $10 \times 10$  (rad/s)  
 due to ~~pole~~ zero 10  
 & starts decreasing from  $0.1 \times 1010$  to  $10 \times 1010$  (rad/s)  
 combining these we get



For  $V_1(t) = 10 \sin(100t) \text{ V} = 10 \cos(100t - \frac{\pi}{2})$

$\omega = 100 \text{ rad/s}$  gain  $\Rightarrow -20 \text{ dB} = 0.1$   
 phase  $\Rightarrow 90^\circ = \frac{\pi}{2}$

$\therefore V_2(t) \Rightarrow 10 \times 0.1 \sin(100t + \frac{\pi}{2})$   
 $\Rightarrow \sin(100t + \frac{\pi}{2})$

or  $V_2(t) = 10 \times 0.1 \cos(100t - \frac{\pi}{2} + \frac{\pi}{2})$   
 $= \cos(100t)$

b) For actual output amplitude & phase for input,  $\omega = 100 \text{ rad/s}$ .

$$|T_v(j100)| = \frac{\sqrt{10^2 + (100)^2}}{\sqrt{1010^2 + 100^2}} \approx 0.1$$

$$\angle T_v(j100) = \angle \frac{10 + j100}{j100 + 1010} = 1.3724 \text{ rad} = 78.635^\circ$$

$$\therefore v_2(t) = 10 \times 0.1 \sin(100t + 1.3724)$$

$$\text{or } v_2(t) = 10 \times 0.1 \cos(100t - \frac{\pi}{2} + 1.3724) = \cos(100t - 0.1984)$$

c) Using matlab plot

$$|T_v(j0)|_{dB} = -40 \quad \angle T_v(j0) = 5.69$$

$$|T_v(j100)|_{dB} = -20.1 \text{ dB}, \quad \angle T_v(j100) = 78.6$$

$$|T_v(j1010)|_{dB} = -3.02 \text{ dB}, \quad \angle T_v(j1010) = 42.3$$

$$|T_v(j10100)|_{dB} = -0.0373 \text{ dB}, \quad \angle T_v(j10100) \approx 0$$

Hence, we see that the computations conform to computations done in b & c.

Bode Diagram

