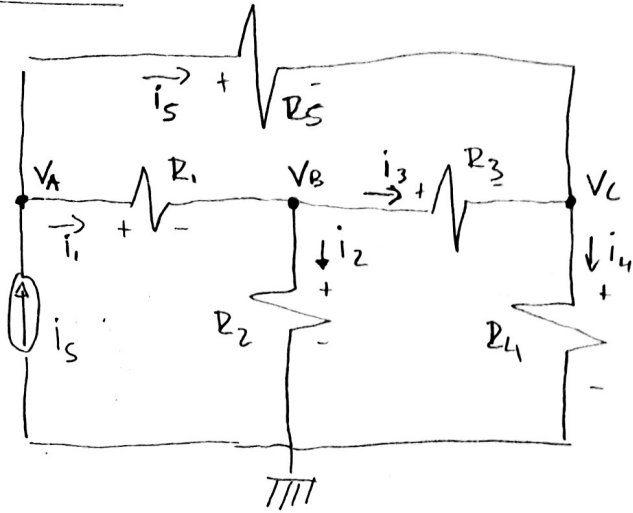


Homework 3

3.1)



1) KCL:

$$A: i_s - i_1 - i_5 = 0$$

$$B: i_1 - i_2 - i_3 = 0$$

$$C: i_5 + i_3 - i_4 = 0$$

2) Relate element currents to node voltages:

$$i_1 = \frac{1}{R_1} (V_A - V_B), \quad i_2 = \frac{V_B}{R_2}, \quad i_3 = \frac{1}{R_3} (V_B - V_C), \quad i_4 = \frac{V_C}{R_4}$$

$$i_5 = \frac{1}{R_5} (V_A - V_C)$$

3) Node voltage equations:

$$A: i_s - \frac{1}{R_1} (V_A - V_B) - \frac{1}{R_5} (V_A - V_C) = 0$$


$$B: \frac{1}{R_1} (V_A - V_B) - \frac{V_B}{R_2} - \frac{1}{R_3} (V_B - V_C) = 0$$

$$C: \frac{1}{R_5} (V_A - V_C) + \frac{1}{R_3} (V_B - V_C) - \frac{V_C}{R_4} = 0$$

4) Node voltage equations in the form $Ax = b$

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_5} & -\frac{1}{R_1} & -\frac{1}{R_5} \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_5} & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} i_s \\ 0 \\ 0 \end{bmatrix}$$

3.3)

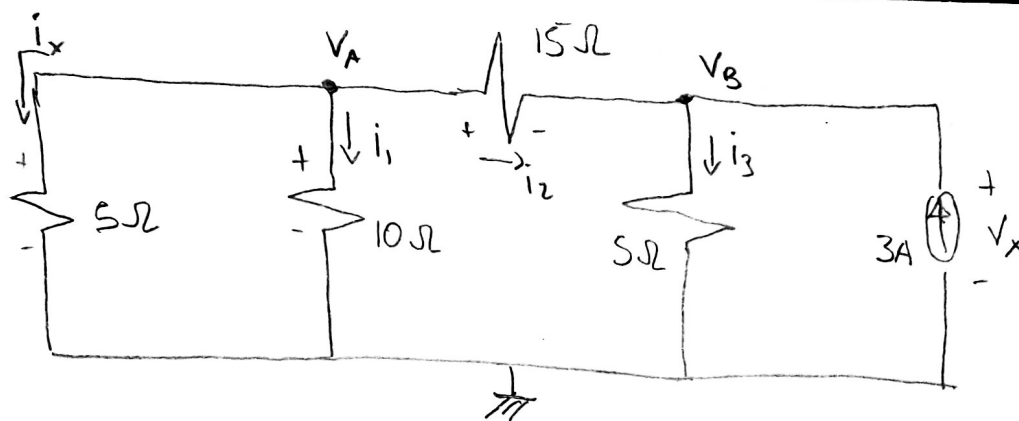1) KCL

$$A: i_x + i_1 + i_2 = 0$$

$$B: i_3 - i_2 - 3A = 0$$

2) Relate element currents to node voltages:

$$i_1 = \frac{V_A}{10\Omega}, \quad i_2 = \frac{1}{15\Omega} (V_A - V_B), \quad i_3 = \frac{V_B}{5\Omega}, \quad i_x = \frac{V_A}{5\Omega}$$

3) Node-Voltage equations:

$$A: \frac{1}{5} V_A + \frac{V_A}{10} + \frac{1}{15} (V_A - V_B) = 0$$

$$B: \frac{V_B}{5} - \frac{1}{15} (V_A - V_B) - 3A = 0$$

a) Node-Voltage equations in the form $Ax = b$

$$\begin{bmatrix} \frac{1}{5} + \frac{1}{10} + \frac{1}{15} & -\frac{1}{15} \\ -\frac{1}{15} & \frac{1}{5} + \frac{1}{15} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} 0 \\ 3A \end{bmatrix}$$


$$b) A^{-1} = \frac{1}{\left(\frac{1}{5} + \frac{1}{10} + \frac{1}{15}\right)\left(\frac{1}{5} + \frac{1}{15}\right) - \left(\frac{1}{15}\right)^2} \begin{bmatrix} \frac{1}{5} + \frac{1}{5} & \frac{1}{15} \\ \frac{1}{15} & \frac{1}{5} + \frac{1}{10} + \frac{1}{15} \end{bmatrix} = \begin{bmatrix} 2.0571 & 0.7143 \\ 0.7143 & 3.9286 \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = A^{-1} \begin{bmatrix} 0 \\ 3 \end{bmatrix} = \begin{bmatrix} 2.14V \\ 11.78V \end{bmatrix}$$

$$c) V_x = V_B = 11.78V$$

$$i_x = \frac{V_A}{5\Omega} = \frac{2.14}{5\Omega} = 0.428A$$

3.5)

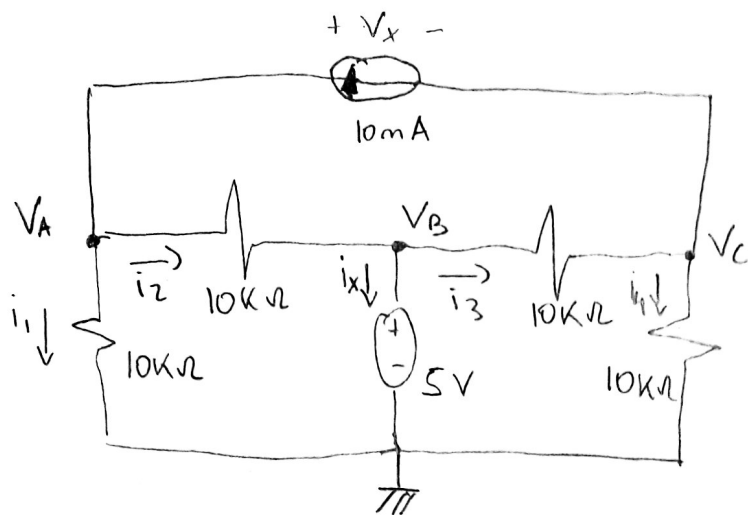

KCL:

$$A: i_1 + i_2 - 10\text{mA} = 0$$

$$B: i_x + i_3 - i_2 = 0$$

$$C: i_4 - i_3 + 10\text{mA} = 0$$

Relate element currents to node voltages:

$$i_1 = \frac{V_A}{10\text{k}\Omega}, \quad i_2 = \frac{1}{10\text{k}\Omega} (V_A - V_B), \quad i_3 = \frac{1}{10\text{k}\Omega} (V_B - V_C)$$

$$i_4 = \frac{V_C}{10\text{k}\Omega}, \quad V_B = 5\text{V} \text{ (By inspection)}$$

Node-voltage equations:

$$A: \frac{V_A}{10\text{k}\Omega} + \frac{1}{10\text{k}\Omega} (V_A - 5\text{V}) - 10\text{mA} = 0$$

$$C: \frac{V_C}{10\text{k}\Omega} - \frac{1}{10\text{k}\Omega} (5\text{V} - V_C) + 10\text{mA} = 0$$


a) In matrix form $Ax = b$:

$$\begin{bmatrix} \frac{1}{10\text{k}} + \frac{1}{10\text{k}} & 0 \\ 0 & \frac{1}{10\text{k}} + \frac{1}{10\text{k}} \end{bmatrix} \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 10 \times 10^3 + \frac{5}{10\text{k}} \\ -10 \times 10^3 + \frac{5}{10\text{k}} \end{bmatrix}$$

$$b) \begin{bmatrix} V_A \\ V_C \end{bmatrix} = \begin{bmatrix} 52.5\text{V} \\ -47.5\text{V} \end{bmatrix}$$

$$c) V_x = V_A - V_C = 52.5\text{V} - (-47.5) = 100\text{V}, \quad i_x = i_2 - i_3 = -0.5\text{mA}$$

3.8)

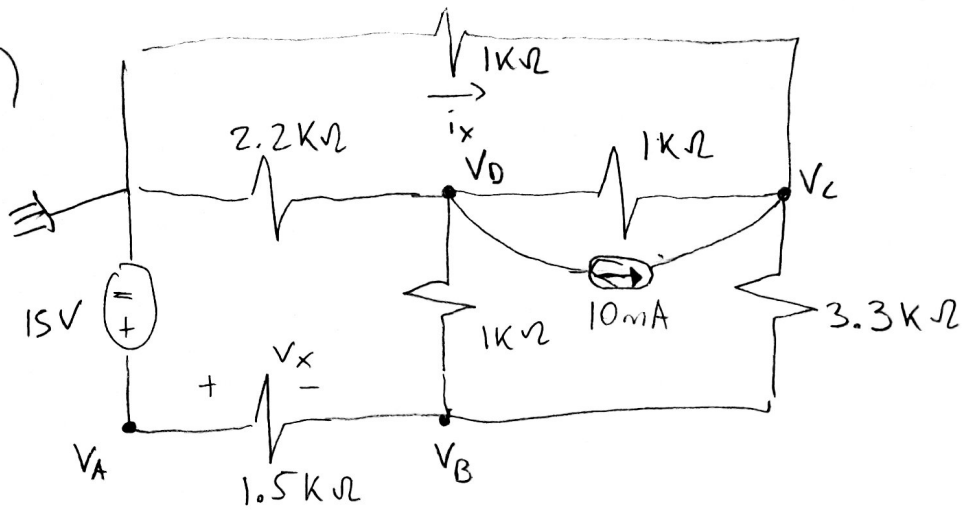

By inspection $V_A = 15V$

Nodal-voltage equations in matrix form $Ax = b$


$$\begin{bmatrix} \frac{1}{1.5K} + \frac{1}{1K} + \frac{1}{3.3K} & -\frac{1}{3.3K} & -\frac{1}{1K} \\ -\frac{1}{3.3K} & \frac{1}{3.3K} + \frac{1}{1K} + \frac{1}{1K} & -\frac{1}{1K} \\ -\frac{1}{1K} & -\frac{1}{1K} & \frac{1}{2.2K} + \frac{1}{1K} + \frac{1}{1K} \end{bmatrix} \begin{bmatrix} V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} \frac{15}{1.5K} \\ 10 \times 10^{-3} \\ -10 \times 10^{-3} \end{bmatrix}$$

$$\begin{bmatrix} V_B \\ V_C \\ V_D \end{bmatrix} = A^{-1} x = \begin{bmatrix} 6.286V \\ 5.482V \\ 0.7203V \end{bmatrix}$$

$$V_x = V_A - V_B = 15V - 6.286V = 8.714V$$

$$i_x = -\frac{V_C}{1K} = -\frac{5.482}{1K} = -5.482 \text{ mA}$$

3.11)

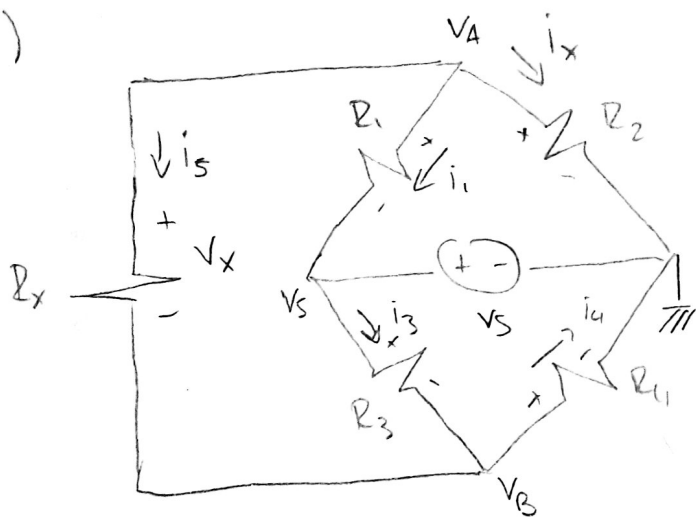

Node A: $i_1 + i_x + i_5 = 0$

$$\frac{1}{R_1}(V_A - V_S) + \frac{1}{R_2}(V_A) + \frac{1}{R_x}(V_A - V_B) = 0$$

$$\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x}\right)V_A - \frac{1}{R_x}V_B = \frac{1}{R_1}V_S$$

Node B:

$$\left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_x}\right)V_B - \frac{1}{R_x}V_A = \frac{1}{R_3}V_S$$

b) We solve using the matrix form $Ax = b$


$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_x} & -\frac{1}{R_x} \\ -\frac{1}{R_x} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_x} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \end{bmatrix} = \begin{bmatrix} \frac{1}{R_1} V_S \\ \frac{1}{R_3} V_S \end{bmatrix}$$

When $R_1 = 1\text{ k}\Omega$, $R_2 = 1.5\text{ k}\Omega$, $R_3 = 500\ \Omega$, $R_4 = 2\text{ k}\Omega$, $R_x = 100\ \Omega$, $V_S = 15\text{ V}$

$$\begin{bmatrix} V_A \\ V_B \end{bmatrix} = A^{-1} \begin{bmatrix} \frac{1}{1.5\text{ k}} 15 \\ \frac{1}{500} 15 \end{bmatrix} = \begin{bmatrix} 10.63\text{ V} \\ 10.90\text{ V} \end{bmatrix}$$

$$V_x = V_A - V_B = 10.63 - 10.90 = -0.27\text{ V}$$
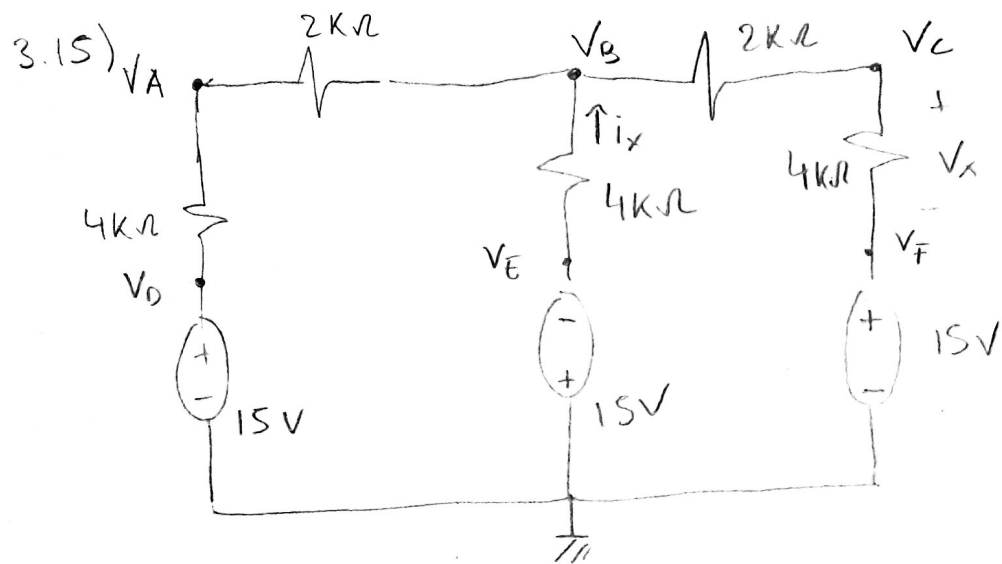
$$i_x = \frac{V_A}{R_2} = \frac{10.63\text{ V}}{1.5\text{ k}\Omega} = 7.1\text{ mA}$$



By inspection:

$$V_D = 15V, V_E = -15, V_F = 15V$$


$$a) \begin{bmatrix} \frac{1}{2k} + \frac{1}{4k} & -\frac{1}{2k} & 0 \\ -\frac{1}{2k} & \frac{1}{2k} + \frac{1}{4k} + \frac{1}{2k} & -\frac{1}{2k} \\ 0 & -\frac{1}{2k} & \frac{1}{2k} + \frac{1}{4k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} \frac{1}{4k} (15) \\ \frac{1}{4k} (-15) \\ \frac{1}{4k} (15) \end{bmatrix}$$

$$\begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = A^{-1} \begin{bmatrix} \frac{15}{4k} \\ -\frac{15}{4k} \\ \frac{15}{4k} \end{bmatrix} = \begin{bmatrix} 6.4286V \\ 2.1429V \\ 6.4286V \end{bmatrix}$$

$$c) V_x = V_C - V_F = 6.4286V - 15V = -8.5714V$$

$$i_x = \frac{V_E - V_B}{4k} = \frac{-15V - 2.1429V}{4k} = -4.3mA$$

318)

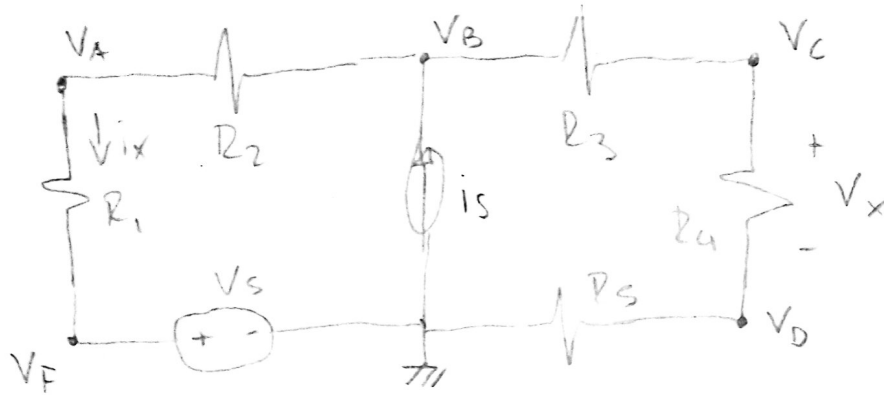By inspection: $V_F = V_S$

$$a) \begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} & -\frac{1}{R_2} & 0 & 0 \\ -\frac{1}{R_2} & \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} & 0 \\ 0 & -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} & -\frac{1}{R_4} \\ 0 & 0 & -\frac{1}{R_4} & \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = \begin{bmatrix} \frac{V_S}{R_1} \\ i_S \\ 0 \\ 0 \end{bmatrix}$$

$$b) R_1 = 2.7 \text{ k}\Omega, R_2 = 1.5 \text{ k}\Omega, R_3 = 680 \Omega, R_4 = 2.2 \text{ k}\Omega, R_5 = 3.3 \text{ k}\Omega$$

$$i_S = 10 \text{ mA}, V_S = 12 \text{ V}$$


we solve using

$$\begin{bmatrix} V_A \\ V_B \\ V_C \\ V_D \end{bmatrix} = A^{-1} \begin{bmatrix} \frac{12}{2.7 \text{ k}} \\ 10 \text{ mA} \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 24.9538 \text{ V} \\ 32.1503 \text{ V} \\ 28.6127 \text{ V} \\ 17.1676 \text{ V} \end{bmatrix}$$


$$V_x = V_C - V_D = 28.6127 \text{ V} - 17.1676 \text{ V} = 11.4451 \text{ V}$$

$$i_x = \frac{V_A - V_F}{R_1} = \frac{24.9538 \text{ V} - 12 \text{ V}}{2.7 \text{ k}\Omega} = \frac{12.9538 \text{ V}}{2.7 \text{ k}\Omega} = 4.8 \text{ mA}$$

3.52)

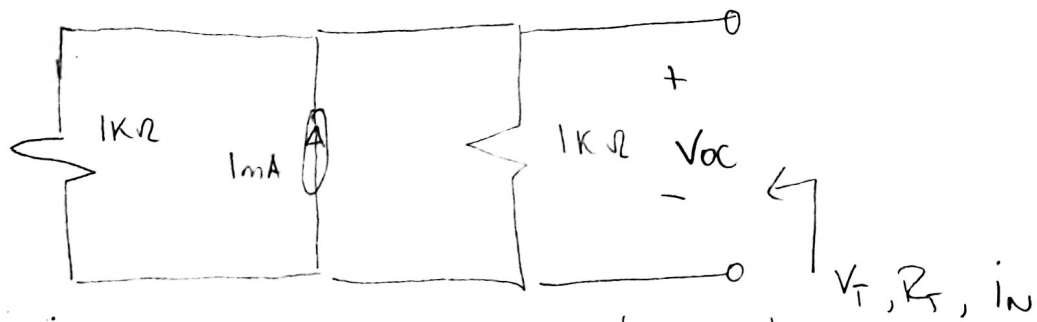

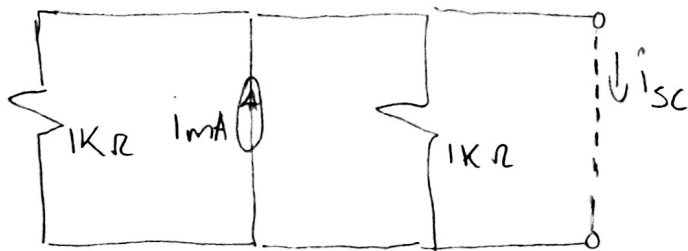
First we find the current in short circuit i_{sc} :



$$i_{sc} = 1\text{mA}$$

Note that i_{sc} is the Norton current i_N .

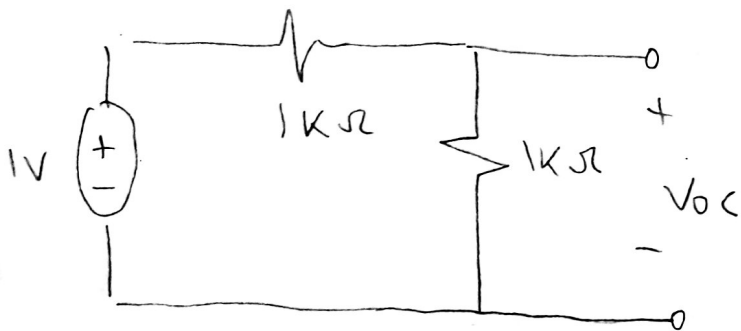
Now we find V_{oc} (Voltage when the circuit is open) using source transformation and voltage division:




$$V_{oc} = \frac{1}{2}(1\text{V}) = \frac{1}{2}\text{V}$$

$$R_T = \frac{V_{oc}}{i_{sc}} = \frac{1/2}{1 \times 10^{-3}} = 500\Omega$$


Then, the Thévenin equivalent is:

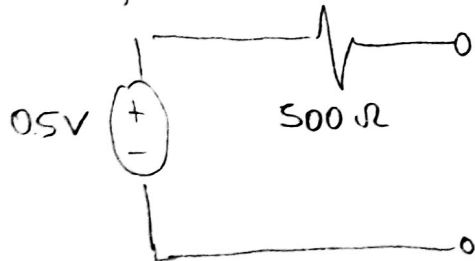


The Norton equivalent:

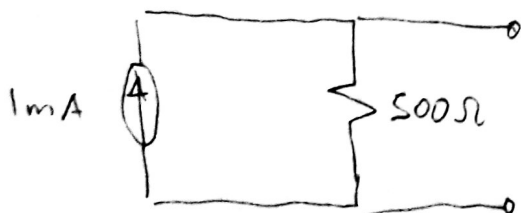


3.57)

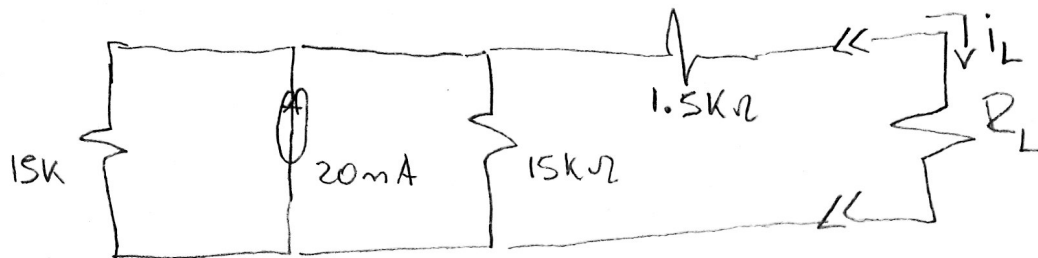

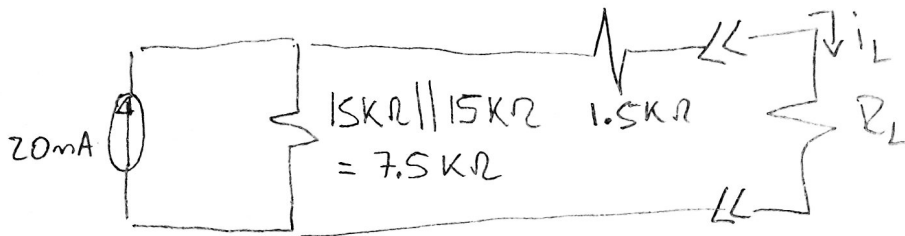
Note that the circuit above is equivalent to:



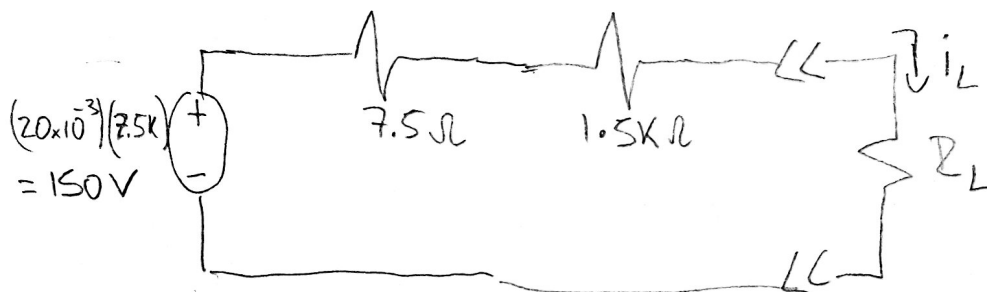which is equivalent to: (using source transformation)



We use a source transformation again:

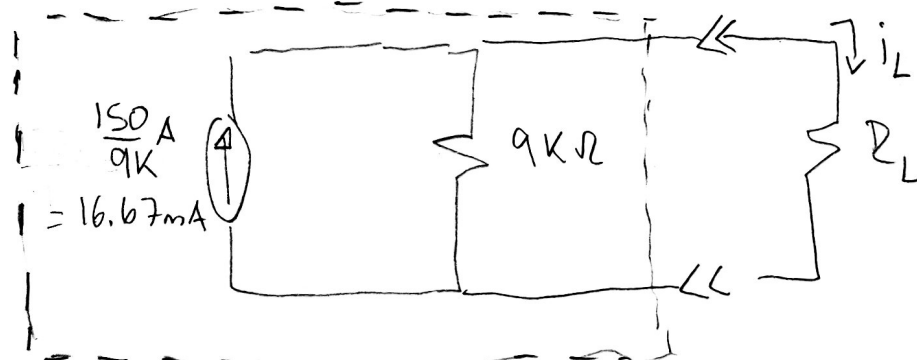

Norton equivalent


$$i_N = 16.67 \text{ mA} \text{ and } R_N = 9 \text{ k}\Omega$$

• When $R_L = 4.7 \text{ k}\Omega$, $i_L = \frac{\frac{1}{4.7}}{\frac{1}{9} + \frac{1}{4.7}} (16.67 \text{ mA}) = 10.95 \text{ mA}$

• When $R_L = 15 \text{ k}\Omega$, $i_L = \frac{\frac{1}{15}}{\frac{1}{9} + \frac{1}{15}} (16.67 \text{ mA}) = 6.25 \text{ mA}$

• When $R_L = 68 \text{ k}\Omega$, $i_L = \frac{\frac{1}{68}}{\frac{1}{9} + \frac{1}{68}} (16.67 \text{ mA}) = 1.95 \text{ mA}$

3.62)

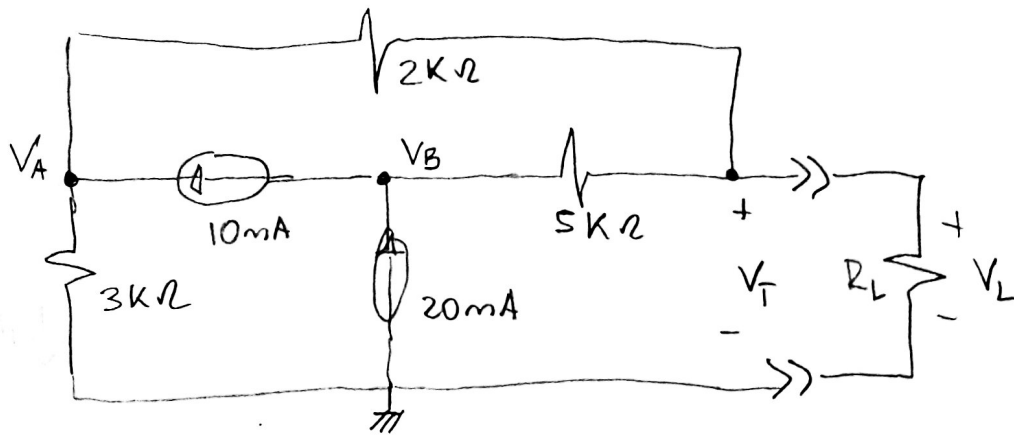

We find V_T when the circuit is open. For that we use Nodal equations in the matrix form $Ax = b$


$$\begin{bmatrix} \frac{1}{3k} + \frac{1}{2k} & 0 & -\frac{1}{2k} \\ 0 & \frac{1}{5k} & -\frac{1}{5k} \\ -\frac{1}{2k} & -\frac{1}{5k} & \frac{1}{2k} + \frac{1}{5k} \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_T \end{bmatrix} = \begin{bmatrix} 10 \times 10^{-3} \\ 20 \times 10^{-3} - 10 \times 10^{-3} \\ 0 \end{bmatrix}$$

Solving $x = A^{-1}b$ we have


$$\begin{bmatrix} V_A \\ V_B \\ V_T \end{bmatrix} = \begin{bmatrix} 60 \text{ V} \\ 130 \text{ V} \\ 80 \text{ V} \end{bmatrix}$$

Therefore $V_T = 80 \text{ V}$.

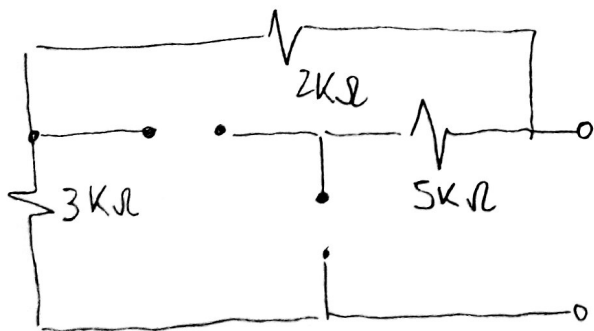We find next R_T : (By turning off all sources)



$$R_T = 5k\Omega$$

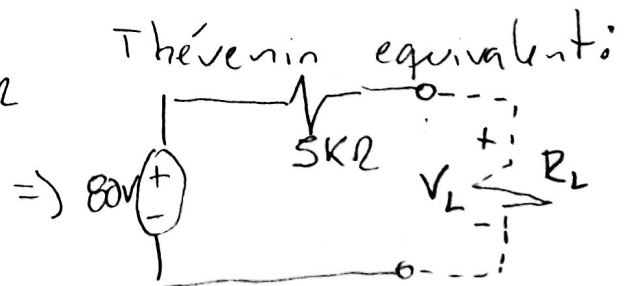

$$\text{When } R_L = 2.5k\Omega, V_L = \frac{R_L}{R_T + R_L} V_T = \frac{2.5}{5 + 2.5} \cdot (80 \text{ V}) = 26.66 \text{ V}$$