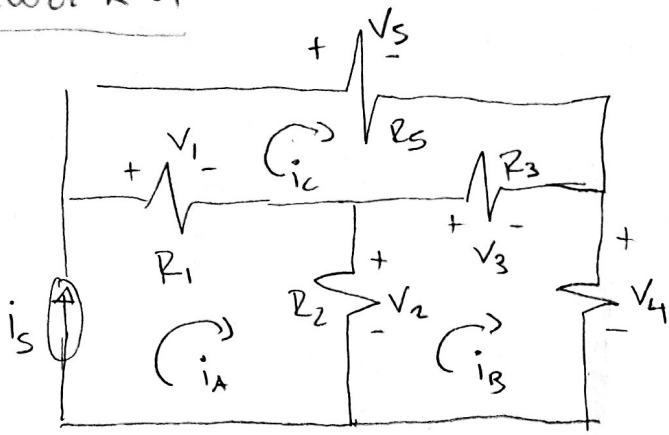


Homework 4

3.1)



KVL: By inspection $i_A = i_s$

$$\text{Mesh B: } -V_2 + V_3 + V_4 = 0$$

$$\text{Mesh C: } -V_1 + V_5 - V_3 = 0$$

Element voltages

$$V_1 = R_1 (i_s - i_c), \quad V_2 = R_2 (i_s - i_B), \quad V_3 = R_3 (i_B - i_c)$$

$$V_4 = R_4 i_B, \quad V_5 = R_5 i_c$$

Mesh-analysis:


$$\text{Mesh B: } -R_2 (i_s - i_B) + R_3 (i_B - i_c) + R_4 i_B = 0$$

$$(R_2 + R_3 + R_4) i_B - R_3 i_c = R_2 i_s$$

$$\text{Mesh C: } +(R_1 + R_2 + R_5) i_c - R_3 i_B = R_1 i_s$$

In matrix form
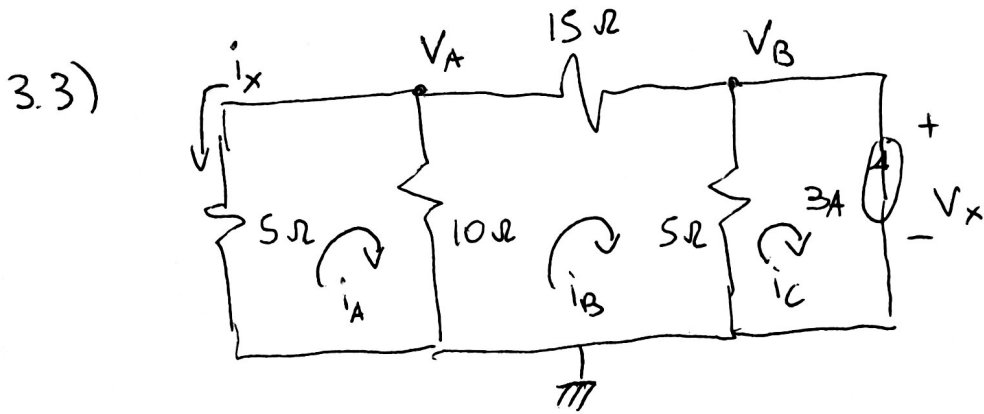
$$\begin{bmatrix} R_2 + R_3 + R_4 & -R_3 \\ -R_3 & R_1 + R_3 + R_5 \end{bmatrix} \begin{bmatrix} i_B \\ i_c \end{bmatrix} = \begin{bmatrix} R_2 i_s \\ R_1 i_s \end{bmatrix}$$



By inspection $i_C = -3A$

a)

$$\begin{bmatrix} 5+10 & -10 \\ -10 & 10+15+5 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 0 \\ -5(3) \end{bmatrix}$$

$$\begin{bmatrix} 15 & -10 \\ -10 & 30 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 0 \\ -15 \end{bmatrix}$$

b)

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -0.4286 A \\ -0.6429 A \end{bmatrix}$$

$$V_A = -5\Omega i_A = -5(-0.4286) = 2.14 V$$


$$V_B = 5(i_B - i_C) = 5(-0.6429 + 3) = 11.78 V$$

c)

$$i_x = -i_A = 0.4286 A$$

$$V_x = V_B = 11.78 V$$

3.5)

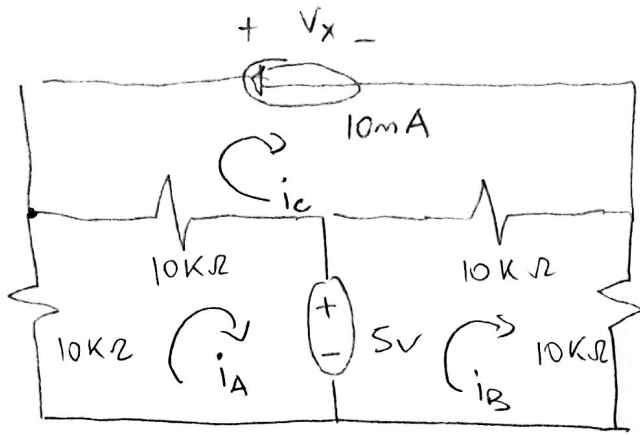

By inspection $i_c = -10\text{mA}$

$$a) \begin{bmatrix} 10\text{K} + 10\text{K} & 0 \\ 0 & 10\text{K} + 10\text{K} \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 10\text{K}(-10\text{mA}) - 5 \\ 10\text{K}(-10\text{mA}) + 5 \end{bmatrix}$$

$$\begin{bmatrix} 20\text{K} & 0 \\ 0 & 20\text{K} \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -105 \\ -95 \end{bmatrix}$$

$$b) \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -5.25\text{mA} \\ -4.75\text{mA} \end{bmatrix}$$


$$V_A = -10\text{K}(-5.25\text{mA}) = 52.5\text{V}$$

$$V_C = 10\text{K} i_B = 10\text{K}(-4.75\text{mA}) = -47.5\text{V}$$

$$c) V_x = V_A - V_C = 52.5\text{V} + 47.5\text{V} = 100\text{V}$$

$$i_x = i_A - i_B = -5.25\text{mA} + 4.75\text{mA} = -0.5\text{mA}$$

3.15)

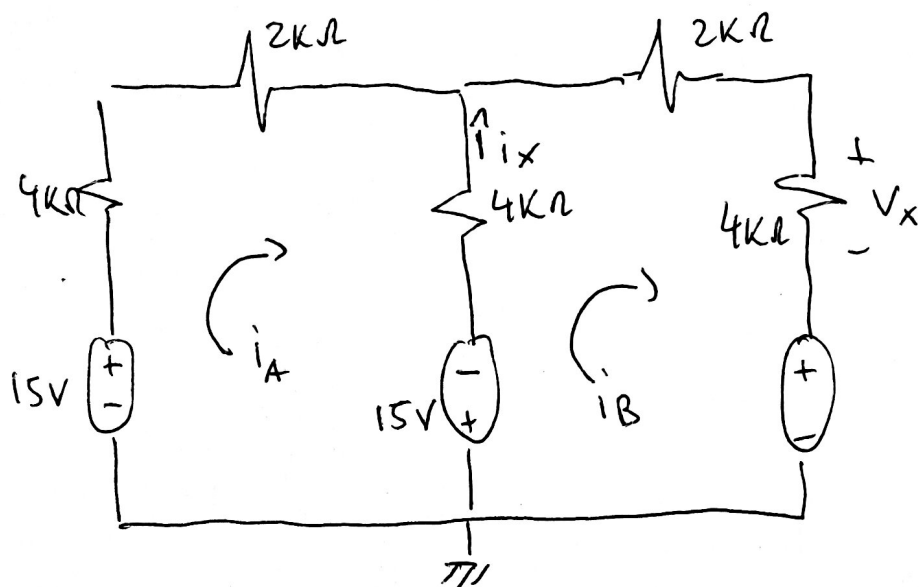

a)

$$\begin{bmatrix} 4k + 2k + 4k & -4k \\ -4k & 4k + 2k + 4k \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 15 + 15 \\ -15 - 15 \end{bmatrix}$$

$$\begin{bmatrix} 10k & -4k \\ -4k & 10k \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 30 \\ -30 \end{bmatrix}$$

b)


$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 2.1429 \text{ mA} \\ -2.1429 \text{ mA} \end{bmatrix}$$

c)

$$i_x = i_B - i_A = -2.1429 \text{ mA} - 2.1429 \text{ mA} = -4.2858 \text{ mA}$$

$$V_x = 4k(i_B) = 4k(-2.1429 \text{ mA}) = -8.5716 \text{ V}$$

3.18)

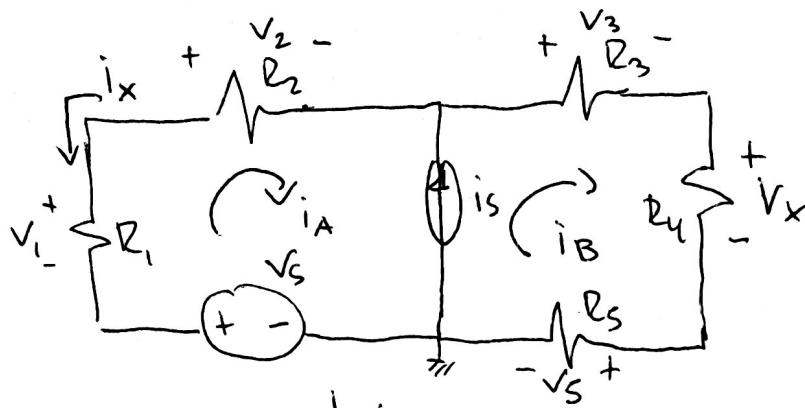

We use supermesh:

$$i_s = i_B - i_A$$

$$-V_1 + V_2 + V_3 + V_x + V_5 - V_s = 0$$

$$+R_1 i_A + R_2 i_A + R_3 i_B + R_4 i_B + R_5 i_B - V_s = 0$$

in matrix form

$$a) \begin{bmatrix} R_1 + R_2 & R_3 + R_4 + R_5 \\ -1 & 1 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} V_s \\ i_s \end{bmatrix}$$


$$b) \begin{bmatrix} 2.7k + 1.5k & 680k + 2.2k + 3.3k \\ -1 & 1 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} 12V \\ 10mA \end{bmatrix}$$

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -4.7977 \text{ mA} \\ 5.2023 \text{ mA} \end{bmatrix}$$

$$V_x = R_4 (i_B) = 2.2k (5.2023 \text{ mA}) = 11.44 \text{ V}$$

$$i_x = -i_A = 4.7977 \text{ mA}$$

19)

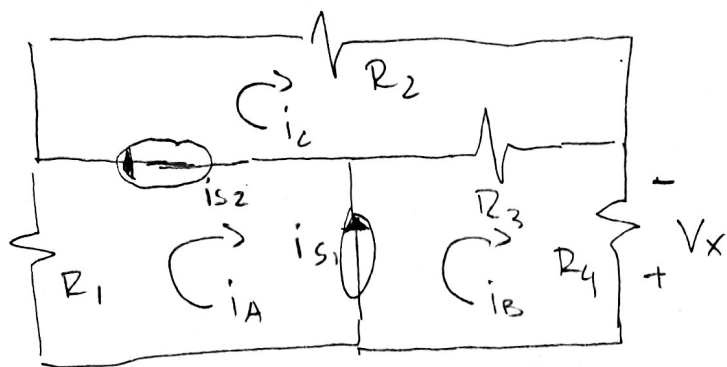

a)

$$i_{S1} = i_B - i_A \quad (1)$$

$$i_{S2} = i_C - i_A \quad (2)$$

Supermesh:

$$R_1 i_A + R_2 i_C + R_4 i_B = 0 \quad (3)$$

$$(1) - (2) \Rightarrow i_{S1} - i_{S2} - i_B + i_C = 0$$

$$\Rightarrow i_B = i_{S1} - i_{S2} + i_C \quad (4)$$

Replace $i_A = i_B - i_{S1}$ in (3):

$$R_1 (i_B - i_{S1}) + R_2 i_C + R_4 i_B = 0 \quad (5)$$

Use (4) in (5):

$$R_1 (-i_{S1} - i_{S2} + i_C - i_{S1}) + R_2 i_C + R_4 (i_{S1} - i_{S2} + i_C) = 0$$

$$-R_1 i_{S2} + (R_1 + R_2 + R_4) i_C + R_4 (i_{S1} - i_{S2}) = 0$$

$$\Rightarrow i_C = \frac{R_1 i_{S2} - R_4 (i_{S1} - i_{S2})}{R_1 + R_2 + R_4} = \frac{(R_1 + R_4) i_{S2} - R_4 i_{S1}}{R_1 + R_2 + R_4}$$


$$i_B = i_{S1} - i_{S2} + \frac{(R_1 + R_4) i_{S2} - R_4 i_{S1}}{R_1 + R_2 + R_4} = \frac{(R_1 + R_2) i_{S1} - R_2 i_{S2}}{R_1 + R_2 + R_4}$$

$$i_A = i_B - i_{S1} = \frac{(R_1 + R_2) i_{S1} - R_2 i_{S2}}{R_1 + R_2 + R_4} - i_{S1}$$


$$= \frac{-R_4 i_{S1} - R_2 i_{S2}}{R_1 + R_2 + R_4}$$

$$b) V_x = -R_4 i_B = -R_4 \left(\frac{(R_1 + R_2) i_{S1} - R_2 i_{S2}}{R_1 + R_2 + R_4} \right)$$

3.40)

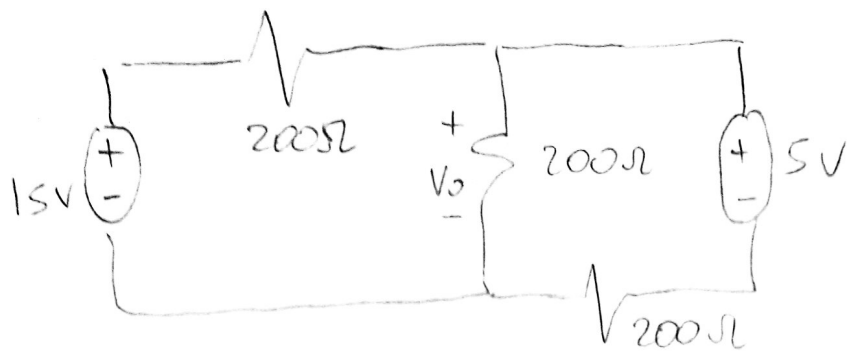


Turn off one voltage source:

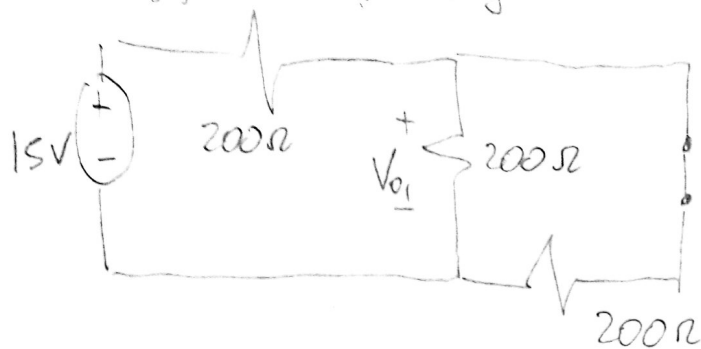

$$V_{o1} = \frac{100}{200+100} (15V) = 5V$$

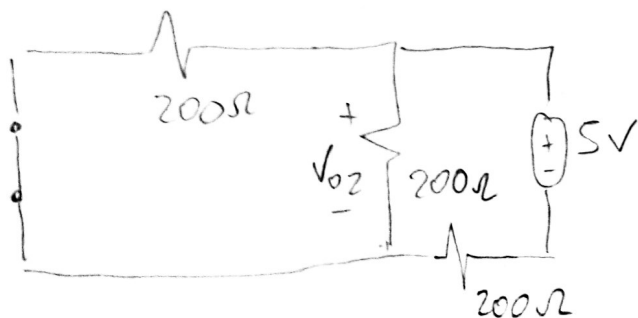
Next, we turn off the other voltage source:




$$V_{o2} = \frac{100}{300} (5V) = 1.66V$$

It follows that $V_o = V_{o1} + V_{o2} = 5 + 1.66 = 6.66V$


3.42)

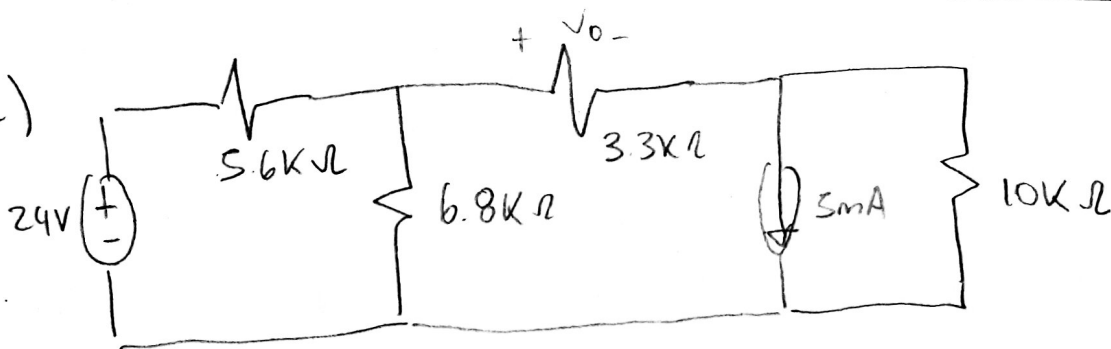

We turn off the current source:

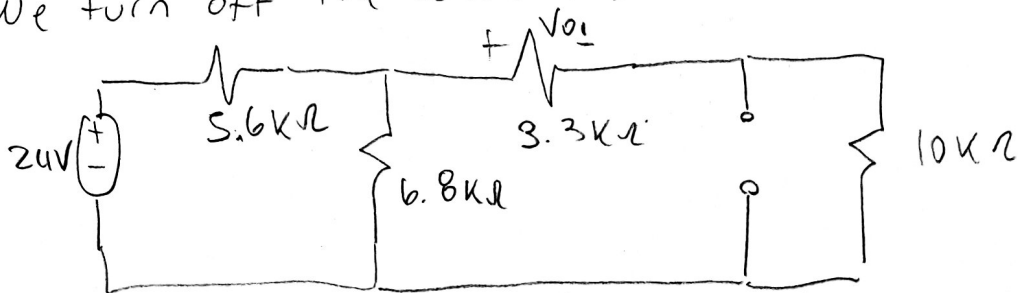



We use source transformation:

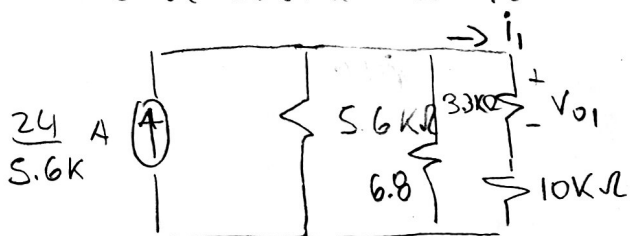

$$i_1 = \frac{\frac{1}{13.3}}{\frac{1}{13.3} + \frac{1}{5.6} + \frac{1}{6.8}} \cdot \frac{24}{5.6k} = 0.8039$$

$$V_{01} = i_1 \cdot 3.3k\Omega = 2.653V$$


Next, we turn off the voltage source:

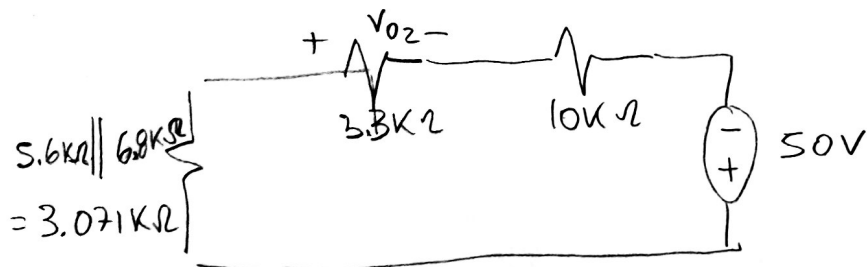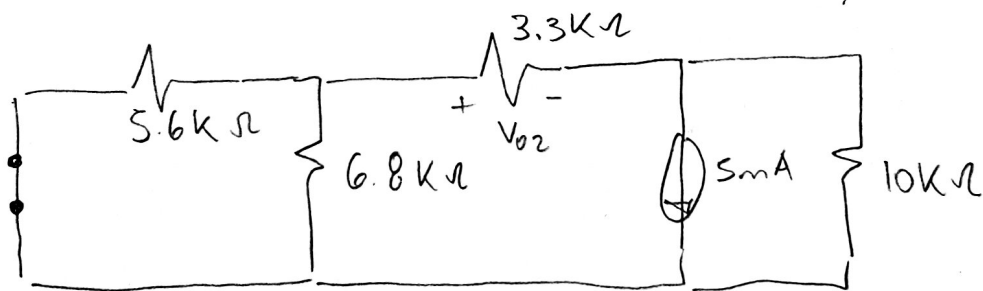


$$V_{02} = \frac{3.3}{3.3 + 10 + 3.071} \cdot (50V) = 10.078V$$

$$V_0 = V_{01} + V_{02} = 2.653V + 10.078V = 12.7318V$$


3-100)

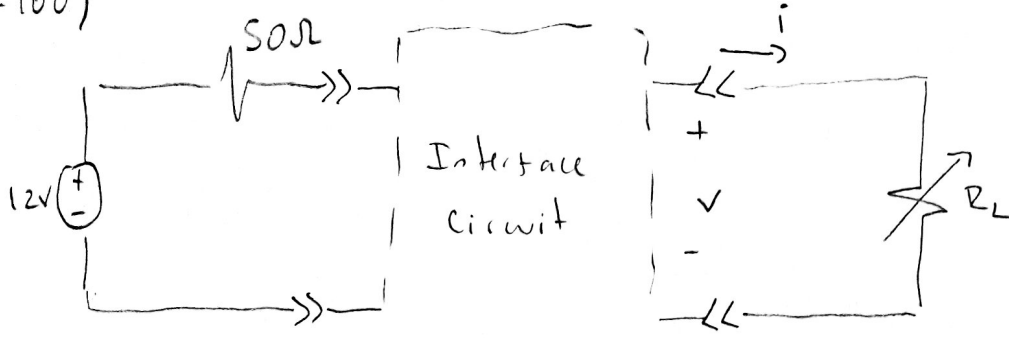

$V \leq 4V, i \leq 50mA$

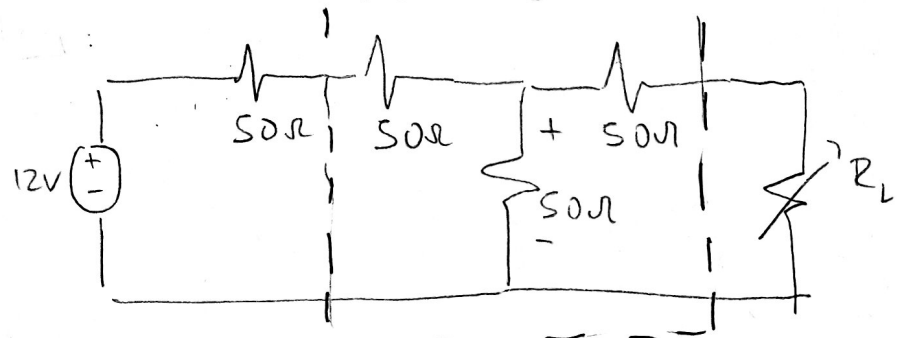


When $R_L = 0$ (short circuit)

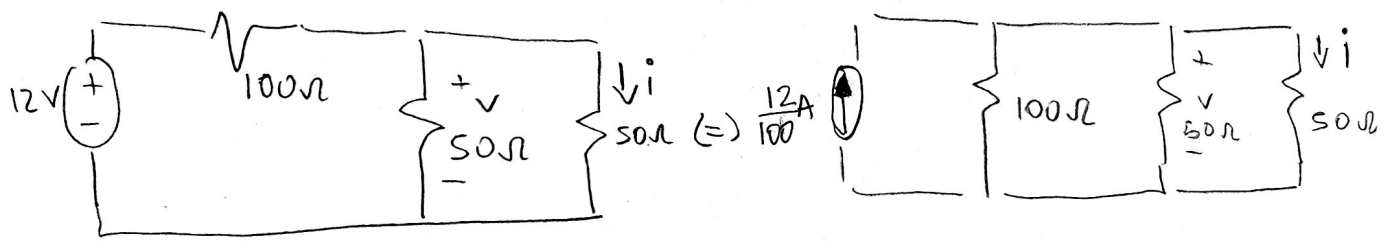

$$i = \frac{\frac{1}{50}}{\frac{1}{100} + \frac{1}{50} + \frac{1}{50}} \left(\frac{12V}{100} \right) = 48mA, \quad V = i \times 50\Omega = 48mA \times 50\Omega = 2.4V$$

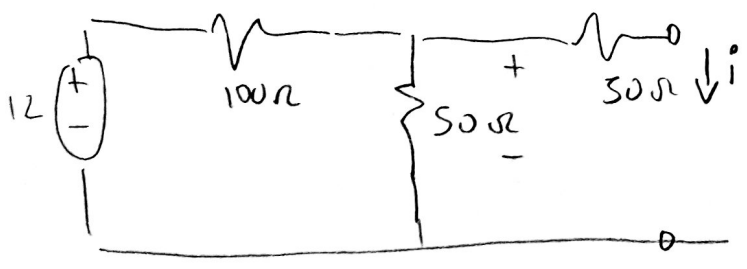When $R_L \rightarrow +\infty$ (open circuit)



we use voltage division:


$$V = \frac{50}{100+50} \cdot 12 = 4V$$

$$i = 0$$

Therefore, the interface circuit meets the required specification.

3.102)


Circuit 1:

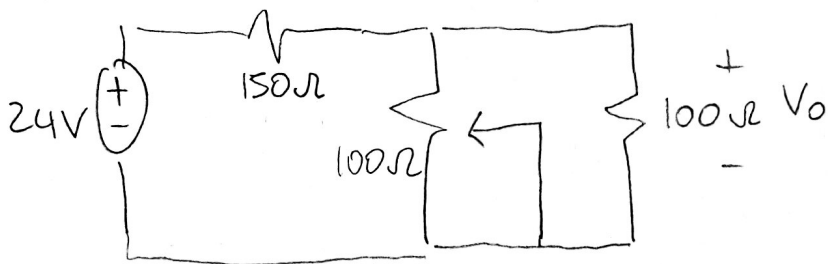

Required Specifications:

- 1-Deliver 0-6V
- 2-Power Source 3W

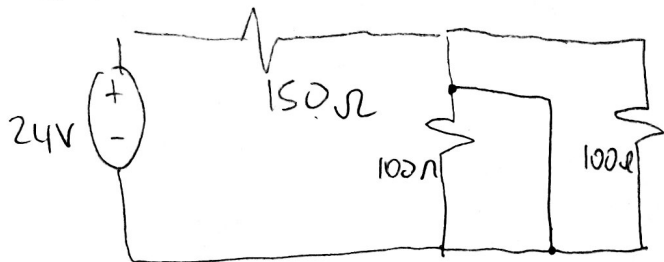
when the circuit is connected at the top:



$$V_0 = 0V$$

$$P_1 = \text{By the voltage source} = \left(\frac{24V}{150\Omega}\right) 24V = 3.84W$$

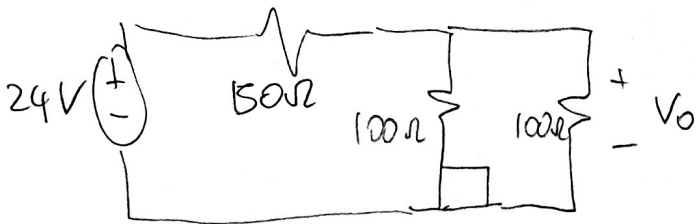when the circuit is connected at the bottom:




$$V_0 = \frac{50}{150+50} (24V) = 6V$$


$$P_2 = \text{By the voltage source} = \left(\frac{24V}{200\Omega}\right) 24V = 2.88W$$

- Notice that $P_1 > 3W$, then circuit 1 doesn't satisfy the required specifications.

Circuit 2:

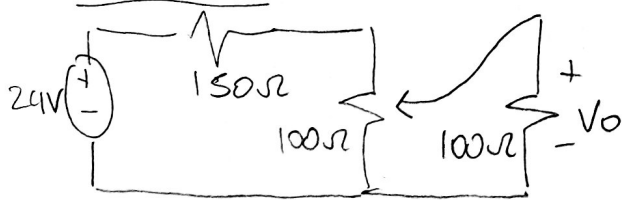

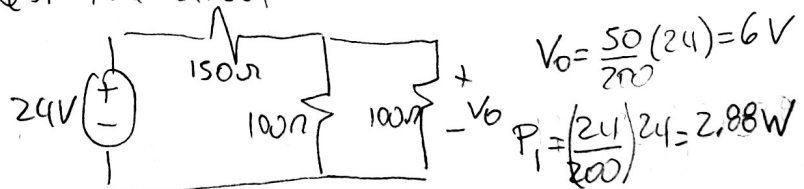
when the circuit is connected at the top:



$$V_0 = \frac{50}{200} (24) = 6V$$

$$P_1 = \left(\frac{24}{200}\right) 24 = 2.88W$$

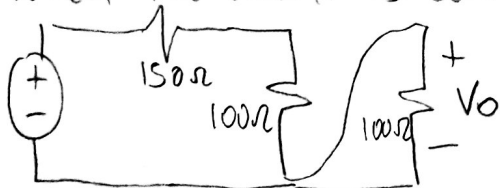when the circuit is connected at the bottom:



$$V_0 = 0$$

$$P_2 = \left(\frac{24}{250}\right) (24) = 2.304W$$

Circuit 2 meets the required specifications!