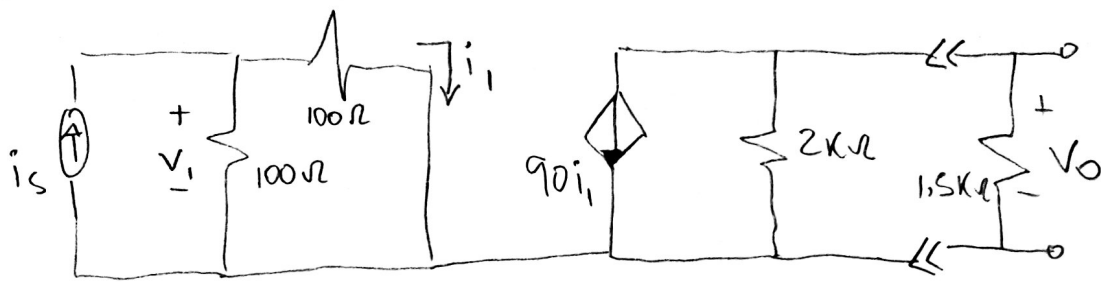


Homework 5

4.2)



Using current division, one has

$$i_1 = \frac{\frac{1}{100}}{\frac{1}{100} + \frac{1}{100}} i_s = \frac{1}{2} i_s$$

By noticing that the voltage in both 100Ω resistors is the same, we have

$$V_1 = 100 i_1 = 100 \left(\frac{1}{2} i_s\right) = 50 i_s \quad (*)$$

For the second part of the circuit, one has (using current div.)

$$i_0 = \frac{\frac{1}{1.5}}{\frac{1}{1.5} + \frac{1}{2}} (-90 i_1) = -51.42 i_1 = -51.42 \left(\frac{1}{2} i_s\right) = -25.71 i_s$$

$$\Rightarrow \frac{i_0}{i_s} = -25.71$$

$$V_0 = 1.5K\Omega i_0 = 1.5K\Omega (-25.71 i_s) = 1.5K\Omega (-25.71) \left(\frac{1}{50} V_1\right) = -771.42 V_1$$

where we have used (*) in the last expression. It follows?

$$\frac{V_0}{V_1} = -771.42$$


• When $i_s = 10 \text{ mA}$:

- $V_1 = 50 (10 \times 10^{-3}) = 500 \text{ mV}$. Then the power supplied by the current source is $P_S = V_1 i_s = (500 \times 10^{-3})(10 \times 10^{-3}) = 5 \text{ mW}$

- The power delivered to the $1.5K\Omega$ resistor is

$$P_L = i_0^2 1.5K\Omega = (25.71 \times 10^{-3})^2 (1.5 \times 10^3) = 99.15 \text{ W}$$

4.7)

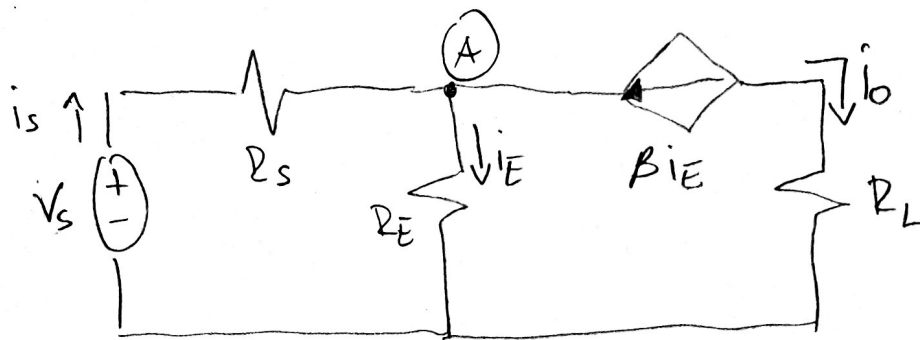

KCL:

$$\text{Node A: } i_s - i_o - i_E = 0 \quad (*)$$

we know that $i_o = -\beta i_E \Rightarrow i_E = -\frac{1}{\beta} i_o$


Replacing i_E in $(*)$, one has

$$i_s - i_o + \frac{1}{\beta} i_o = 0$$

$$i_s = \left(1 - \frac{1}{\beta}\right) i_o = \left(\frac{\beta - 1}{\beta}\right) i_o$$

$$\Rightarrow \frac{i_o}{i_s} = \frac{\beta}{\beta - 1}$$

4.13)

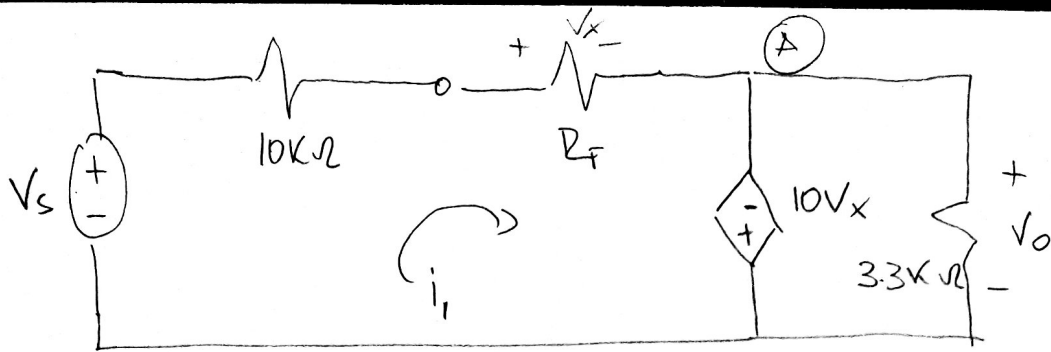

$$V_o = -10V_x$$

$$\text{KVL for } i_1: -V_s + 10K i_1 + R_F i_1 + V_o = 0$$

$$-V_s + (10K + R_F) i_1 + V_o = 0 \quad (*)$$

$$V_x = R_F i_1 \Rightarrow -\frac{1}{10} V_o = R_F i_1 \Rightarrow i_1 = -\frac{1}{10R_F} V_o$$

Replacing i_1 in $(*)$:

$$-V_s + (10K + R_F) \left(-\frac{1}{10R_F} V_o\right) + V_o = 0$$

$$\left(1 - \frac{10K + R_F}{10R_F}\right) V_o = V_s$$

$$(10R_F - 10K - R_F) V_o = 10R_F V_s \Rightarrow \boxed{\frac{V_o}{V_s} = \frac{10R_F}{9R_F - 10K}}$$

• For $K = \frac{V_o}{V_s}$ to go to infinity, the denominator should go to zero


$$9R_F - 10K = 0 \Rightarrow R_F = \frac{10 \times 10^3}{9} = 1.11 K\Omega$$

• To have $K=2$, We need:

$$K = \frac{V_o}{V_s} = \frac{10R_F}{9R_F - 10 \times 10^3} = 2$$

$$\Rightarrow 18R_F - 20 \times 10^3 = 10R_F$$
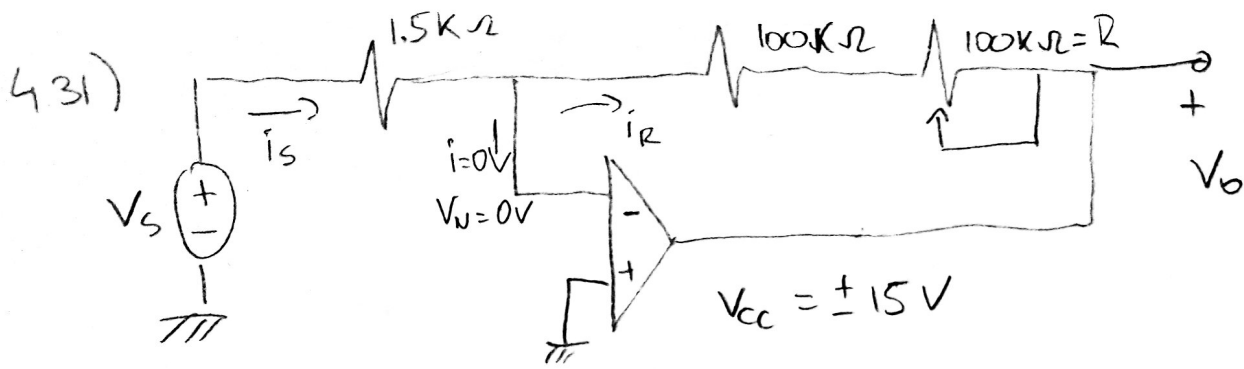
$$8R_F = 20 \times 10^3 \Rightarrow \boxed{R_F = 2.5 K\Omega}$$



$$i_s = i_R$$

$$\frac{V_s}{1.5\text{ k}} = \frac{0 - V_o}{100\text{ k} + R}$$

$$-\left(\frac{100\text{ k} + R}{1.5\text{ k}}\right) = \frac{V_o}{V_s}$$

$$\text{When } R = 0 \Rightarrow \frac{V_o}{V_s} = -\frac{100\text{ k}}{1.5\text{ k}} = -66.66$$

$$\text{When } R = 100\text{ k}\Omega \Rightarrow \frac{V_o}{V_s} = -\frac{200\text{ k}}{1.5\text{ k}} = -133.33$$


So, the range of $\frac{V_o}{V_s}$ is from -133.33 to -66.66 .

Another way to do it:

Notice that the circuit is an inverting amplifier with $R_1 = 1.5\text{ k}\Omega$ and R_2 takes values from $100\text{ k}\Omega$ to $200\text{ k}\Omega$. Recall that the gain is $K = \frac{V_o}{V_s} = -\frac{R_2}{R_1}$.

It follows that $\frac{V_o}{V_s}$ ranges from -133.33 to -66.66 .

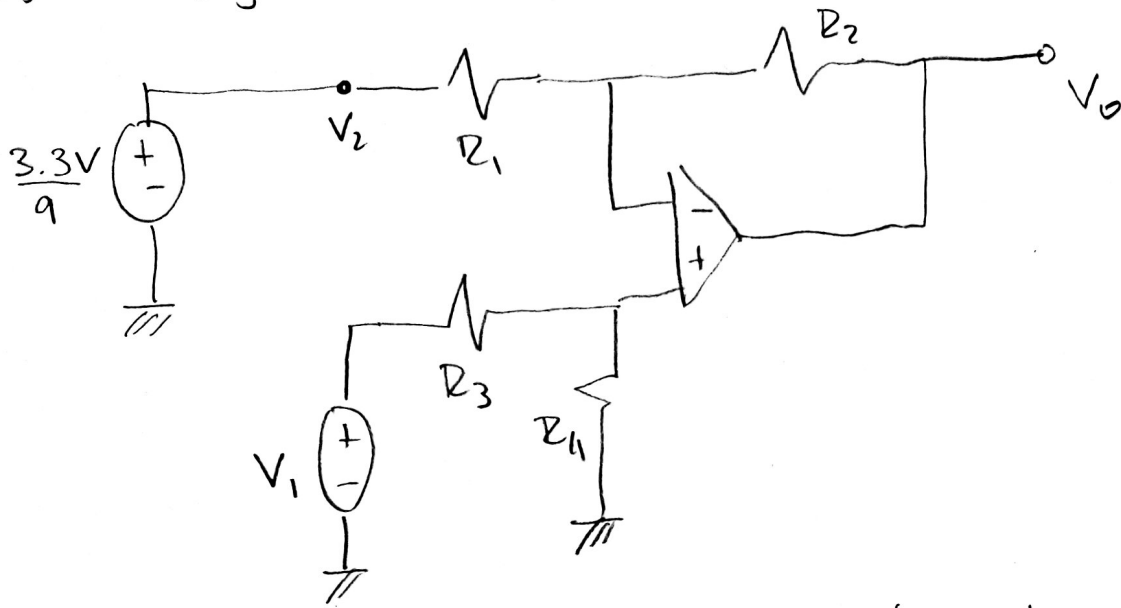4.33) Design $V_o = 5V_1 - 3.3V$. We design a subtractor




where

$$K_1 = -\frac{R_2}{R_1}$$

$$K_2 = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right)$$

Block diagram:

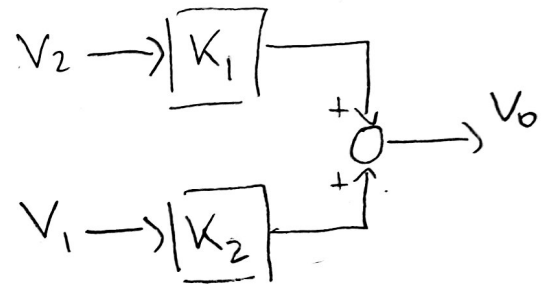

$$V_o = K_1 V_2 + K_2 V_1$$


We pick $R_3 = R_4 = 10k\Omega$ and $R_1 = 10k\Omega$, $R_2 = 90k\Omega$

$$\text{Then, } K_2 = \left(\frac{10k + 90k}{10k} \right) \left(\frac{10k}{10k + 10k} \right) = \frac{100}{20} = 5$$

$$\text{and } K_1 = -\frac{90k}{10k} = -9$$

$$\text{Therefore, } V_o = K_1 V_2 + K_2 V_1 = -9 \left(\frac{3.3V}{9} \right) + 5V_1 \\ = -3.3V + 5V_1$$

4.37)

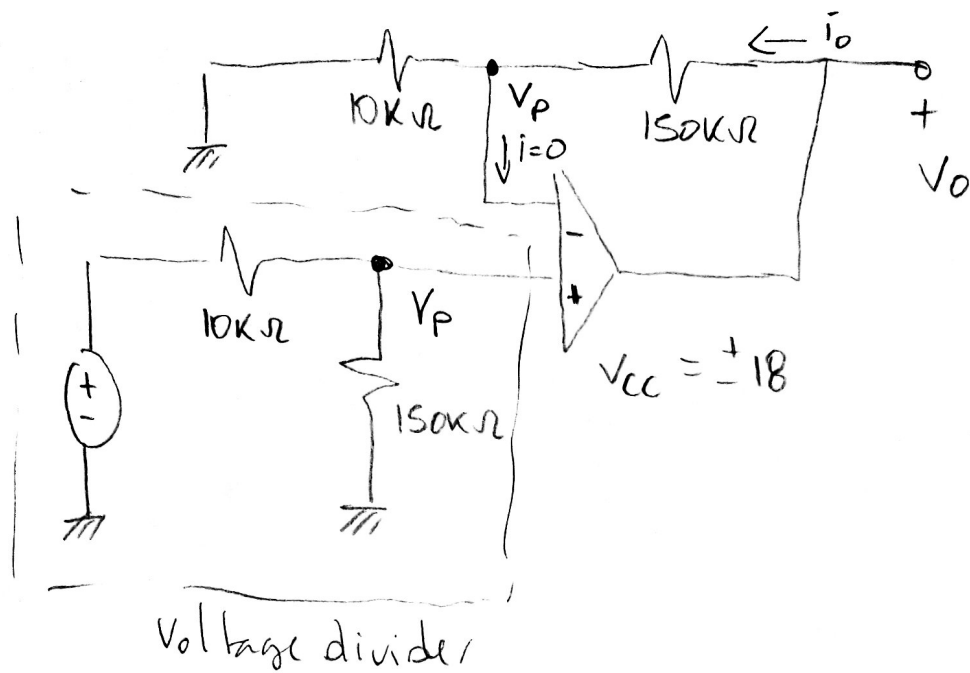

Notice that the circuit is a voltage divider connected to a noninverting amplifier with gain $K = \left(\frac{150k + 10k}{10k} \right) = 16$

$$V_p = \frac{150}{150+10} V_s = \frac{15}{16} V_s \quad (\text{voltage div.})$$

a) The output voltage is $V_o = K V_p = 16 \left(\frac{15}{16} V_s \right) = 15 V_s$

b) Find i_o when $V_s = 1V$:

$$V_o = 15(1V) = 15V$$

$$i_o = \frac{V_o - V_p}{150k} = \frac{15V_s - \frac{15}{16} V_s}{150k} = \frac{(16-1)V_s}{160k} = \frac{3}{32k} V_s$$


$$i_o = \frac{3}{32k} (1V) = 93.75 \mu A$$

When $V_s = 2V$:

$V_o = 15(2V) = 30$. Therefore, V_o is saturated to 18V.

$$\text{Then, } i_o = \frac{V_o}{150k + 10k} = \frac{18V}{160k} = 112 \mu A$$

4.44)

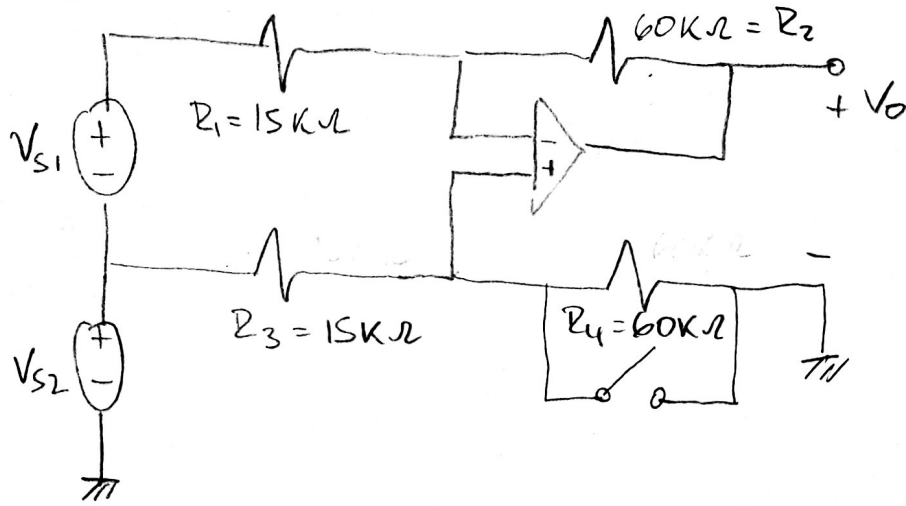

open switch:

The circuit is connected to a subtractor with inputs $V_{s1} + V_{s2}$ and V_{s2} . It follows that

$$\begin{aligned} V_o &= -\frac{R_2}{R_1} (V_{s1} + V_{s2}) + \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) V_{s2} \\ &= -\frac{60K}{15K} (V_{s1} + V_{s2}) + \left(\frac{75}{15}\right) \left(\frac{60}{75}\right) V_{s2} \\ &= -4V_{s1} - 4V_{s2} + 4V_{s2} \end{aligned}$$


$$\boxed{V_o = -4V_{s1}}$$

closed switch:

R_4 is shorted out. The positive input of the OPAMP is connected to ground directly. Then, the circuit is an inverting amplifier with gain $K = -\left(\frac{60K}{15K}\right) = -4$ and input voltage of $V_{s1} + V_{s2}$. Therefore,

$$\boxed{V_o = -4(V_{s1} + V_{s2})}$$

4.51)

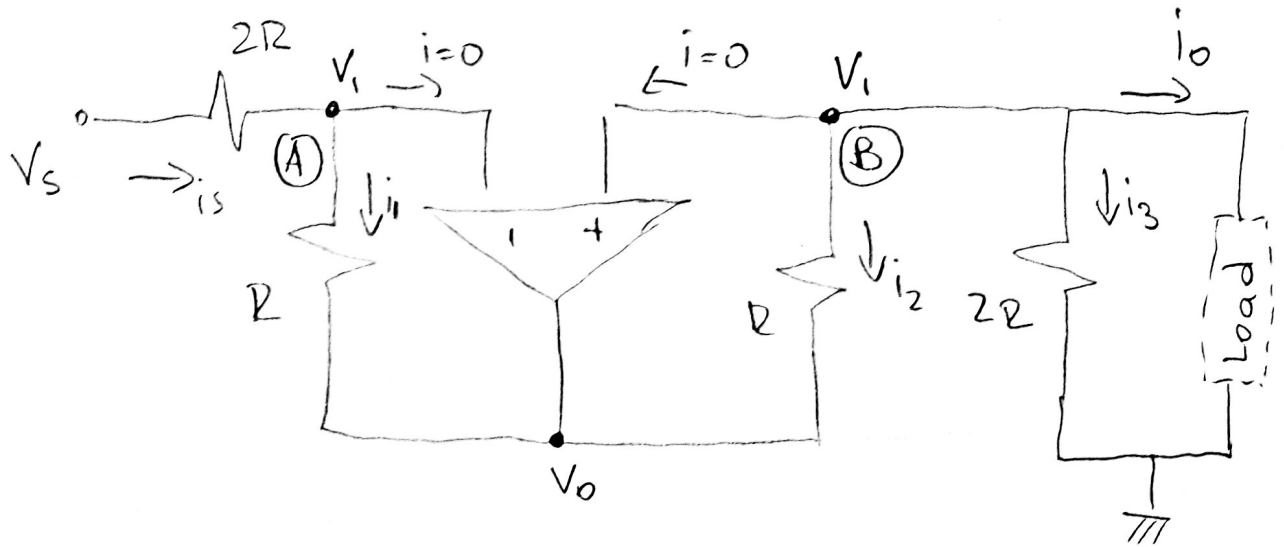

Node A: $i_s = i_1$

$$\frac{V_s - V_1}{2R} = \frac{V_1 - V_0}{R} \Rightarrow V_s - V_1 = 2(V_1 - V_0)$$

$$V_1 = \frac{1}{3}(V_s + 2V_0)$$

Node B:

$$i_2 + i_3 + i_o = 0$$

$$i_o = -i_2 - i_3$$


$$= -\left(\frac{V_1 - V_0}{R}\right) - \left(\frac{V_1}{2R}\right)$$

$$= -\left(\frac{\frac{1}{3}(V_s + 2V_0) - V_0}{R}\right) - \left(\frac{\frac{1}{3}(V_s + 2V_0)}{2R}\right)$$

$$= -\frac{1}{3R}(V_s + \frac{1}{2}V_s) - \left(\frac{2}{3R} - \frac{1}{R} + \frac{1}{3R}\right)V_0$$

$$= -\frac{1}{2R}\left(\frac{3}{2}V_s\right) - \left(\frac{1}{R} - \frac{1}{R}\right)V_0$$

$$\boxed{i_o = -\frac{1}{2R}V_s}$$

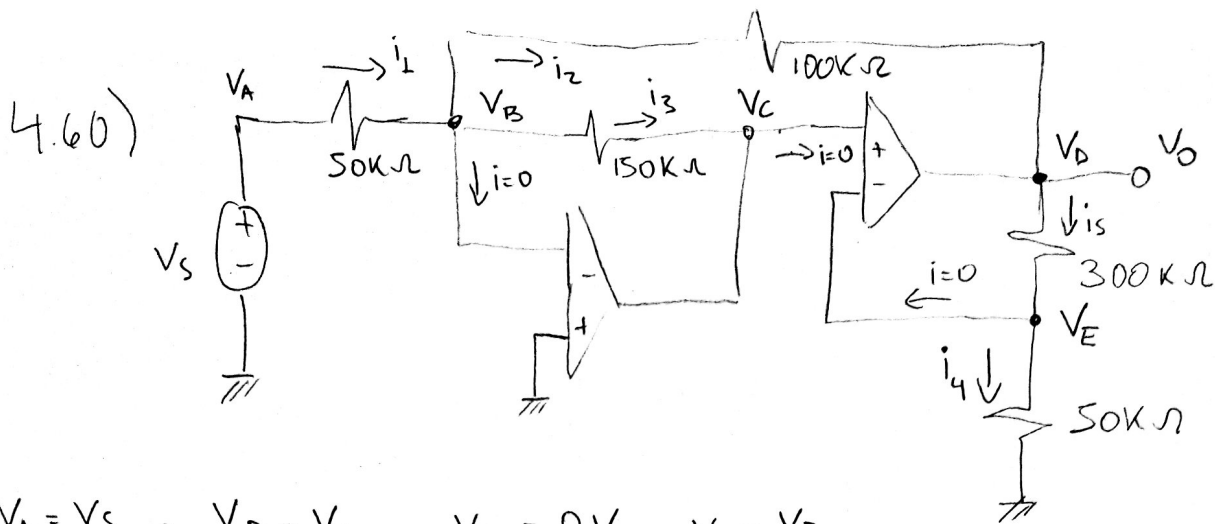

$$V_A = V_s, \quad V_D = V_o, \quad V_B = 0V, \quad V_C = V_E$$

KCL:

Node B: $i_1 - i_2 - i_3 = 0$

$$\frac{V_s - 0}{50k\Omega} - \frac{0 - V_o}{100k\Omega} - \frac{0 - V_E}{150k\Omega} = 0$$

$$V_E = -150 \left(\frac{V_s}{50} + \frac{V_o}{100} \right)$$

$$= -3V_s - \frac{3}{2}V_o \quad (1)$$

Node E: $i_4 - i_5 = 0$

$$\frac{V_E}{50k\Omega} - \frac{V_o - V_E}{300k\Omega} = 0 \Rightarrow 6V_E - V_o + V_E = 0$$

$$V_o = 7V_E \quad (2)$$


Replace (1) in (2):

$$V_o = 7 \left(-3V_s - \frac{3}{2}V_o \right)$$

$$V_o \left(1 + \frac{21}{2} \right) = -21V_s$$


$$\boxed{V_o = -\frac{42}{23} V_s}$$

b)

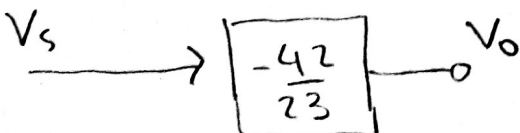

4.86) Given: Pressure (P) in mm Hg
 $V_{TR} = (0.06P - 0.75) \text{ mV}$

diagram:

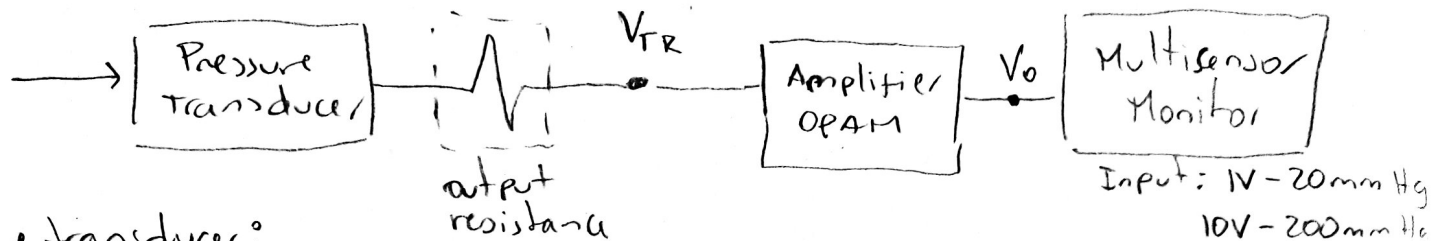

Pressure transducer:

i) When $P = 20 \text{ mmHg}$, then $V_{TR} = (0.06(20) - 0.75) \text{ mV} = 0.45 \text{ mV}$.

The designed circuit should produce $V_o = 1 \text{ V}$

ii) When $P = 200 \text{ mmHg}$, $V_{TR} = 11.25 \text{ mV}$. The designed circuit should produce $V_o = 10 \text{ V}$.

We have to fit a line of the form $V_o = K V_{TR} + b$, where

$$K = \frac{10 \text{ V} - 1 \text{ V}}{11.25 \text{ mV} - 0.45 \text{ mV}} = \frac{9 \text{ V}}{10.8 \text{ mV}} = 833$$

Now, we proceed to find b . For that, we pick a

Point $(\underbrace{0.45 \text{ mV}}_{V_{TR}}, \underbrace{1 \text{ V}}_{V_o})$



$$V_o = K (0.45 \text{ mV}) + b = 1 \text{ V}$$

$$833(0.45 \text{ mV}) + b = 1 \text{ V}$$

$$\boxed{b = 0.625 \text{ V}}$$


The equation we have to satisfy is: $\boxed{V_o = 833 V_{TR} + 0.625 \text{ V}}$

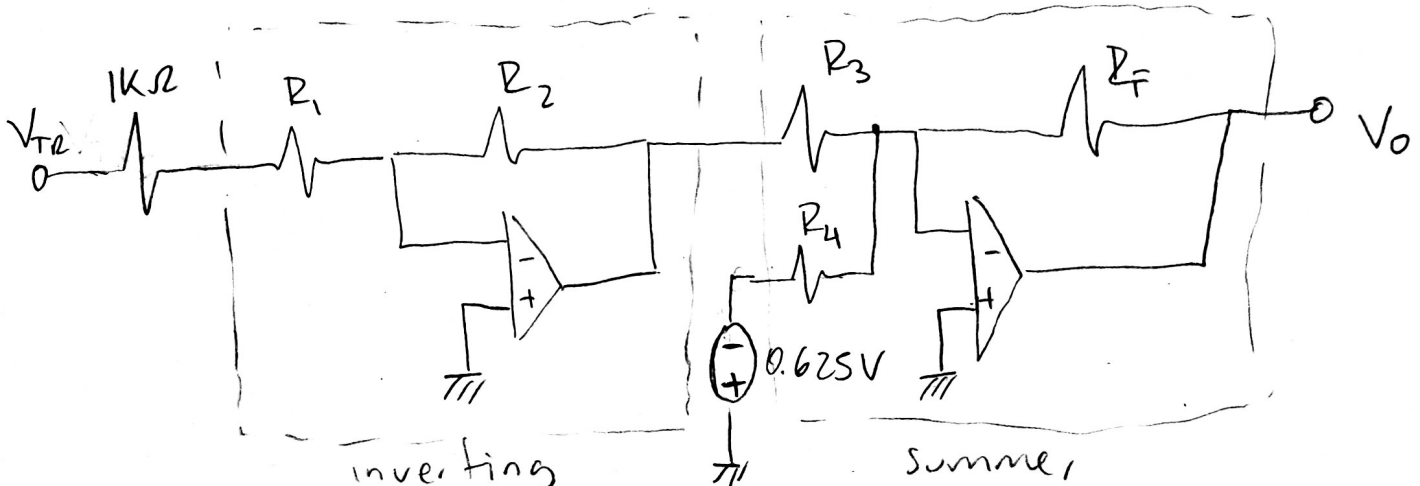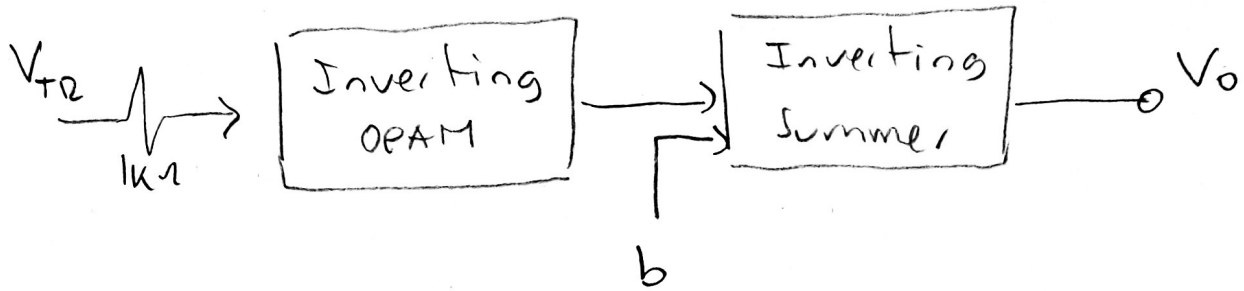For the circuit, we use the following idea



inverting
 $K_1 = -\frac{R_2}{R_1}$

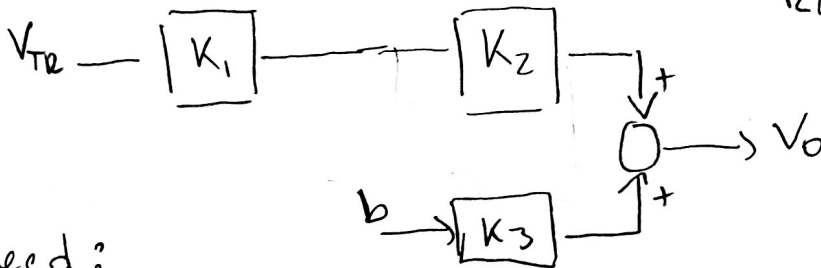summer
 $K_2 = -\frac{R_F}{R_3}$
 $K_3 = -\frac{R_F}{R_4}$



What we need:

$K_1, K_2 = 833$ and $K_3 = -1$

$R_F = 100k\Omega$
 $R_4 = 100k\Omega$ } $\Rightarrow K_3 = -1$
 $R_3 = 1k\Omega$ } $\Rightarrow K_2 = -100$
 $R_2 = 500k\Omega$
 $R_1 = 60k\Omega$ } $\Rightarrow K_1 = -833$

$\Rightarrow V_{T2} = 833 V_{T2} + 0.625V$
 Notice that R_1 much bigger than $1k\Omega$. Other option is to include a buffer as the input of our designed circuit