

# HW #1 Solution

1.7  $Q = I t = (30 \mu\text{A})(500 \text{ms}) = 15 \mu\text{C}$

$15 \mu\text{C}$  flow past in 500 ms.

1.13  $q(t) = 1 - e^{-1000t} \mu\text{C}$

$i = \frac{dq}{dt} = -1000 e^{-1000t} \mu\text{A}$ .  $t = 1.6094 \text{ms} \Rightarrow i = -4.9998 \text{mA}$

1.15  $q(t) = \int_0^t i(\tau) d\tau = \int_0^t 5e^{-3\tau} d\tau = -\frac{1}{3} e^{-3\tau} \Big|_0^t$

$q(t) = \frac{1}{3} (1 - e^{-3t}) \text{C}$

1.25

$i = \frac{P}{V} = \frac{40e^{-2t} \times 10^{-3} \text{W}}{2e^{-t}} \frac{\text{W}}{\text{V}} = 20e^{-t} \times 10^{-3} \text{A}$

$Q = \int_0^{\infty} i(\tau) d\tau = \int_0^{\infty} 20e^{-\tau} \times 10^{-3} d\tau = 20 \times 10^{-3} (-e^{-\tau} \Big|_0^{\infty})$

$= 20e \text{ } \boxed{20 \text{ mC}}$

2.1

$V = IR = (2.2 \text{mA})(33 \text{k}\Omega) = \boxed{72.6 \text{V}}$

2.4


$P = VI = I^2 R \Rightarrow I = \sqrt{\frac{P}{R}} = \sqrt{\frac{0.25 \text{W}}{10^5 \Omega}} = \boxed{1.91 \text{mA}}$

2.17

a) nodes: A, B, C.

Loops:  $A \rightarrow B \rightarrow C \rightarrow A$

$A \rightarrow C \rightarrow A$

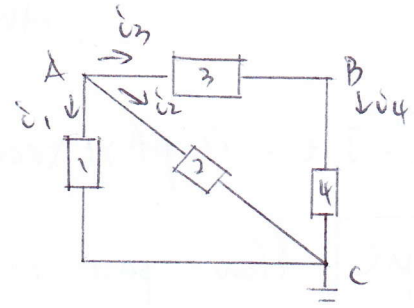

b) Series: 1 & 2

Parallel: 3 & 4

c) KCL

$$i_1 + i_2 + i_3 = 0$$

$$i_3 = i_4$$

$$i_1 + i_2 + i_4 = 0$$

KVL

$$-V_1 + V_2 = 0$$

$$-V_2 + V_3 + V_4 = 0$$

$$-V_1 + V_3 + V_4 = 0$$


2.19.

a) nodes: A, B, C, D

Loops:  $1 \rightarrow 3 \rightarrow 2 \rightarrow 1$

$3 \rightarrow 6 \rightarrow 4 \rightarrow 3$ ,  $4 \rightarrow 5 \rightarrow 2 \rightarrow 4$

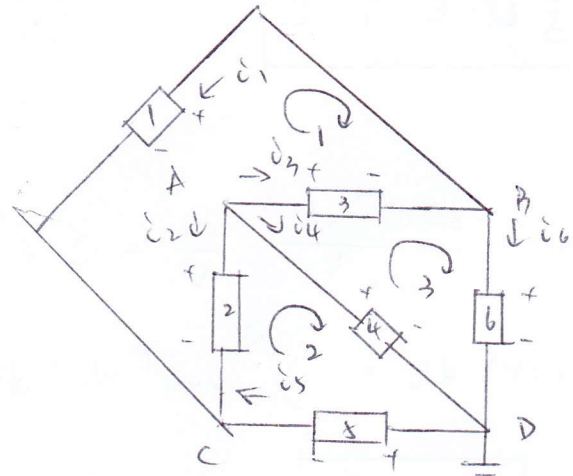$2 \rightarrow 3 \rightarrow 6 \rightarrow 5 \rightarrow 2$ ,  $1 \rightarrow 6 \rightarrow 5 \rightarrow 1$



b) none in series nor parallel

$$c) \text{ KCL } -i_2 - i_3 - i_4 = 0, \quad i_5 + i_2 + i_1 = 0$$

$$-i_1 + i_3 - i_6 = 0, \quad i_4 + i_6 - i_5 = 0$$

KVL

$$V_2 - V_1 - V_3 = 0 \quad \text{Loop 1}$$

$$-V_2 + V_5 + V_4 = 0 \quad \text{Loop 2}$$

$$V_6 - V_4 + V_3 = 0 \quad \text{Loop 3}$$

2.24.


3 & 4, 1 & 2 are in parallel.  
no series connection.

$$A = i_1 + i_3 - i_2 - i_4 = 0$$

$$i_4 = -30 \text{ mA}$$

$$B = i_2 - i_1 - i_5 = 0$$

$$i_5 = 15 \text{ mA}$$

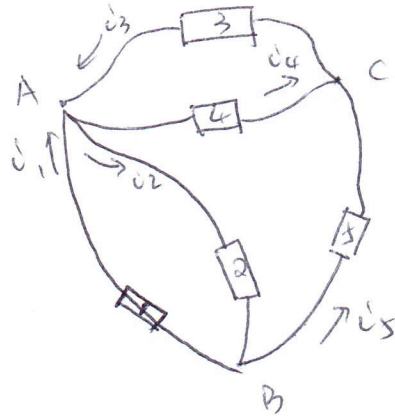

2.27.

