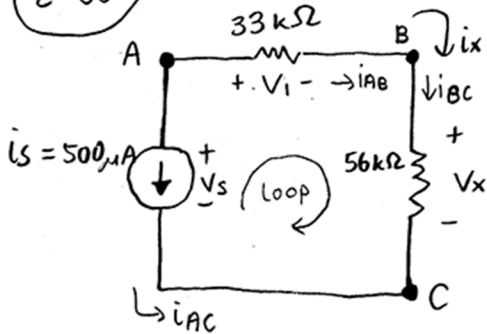


Homework 2 Solution

1/6

2-28



Set of connections: 1 loop and 3 nodes

Constraints =

$$\text{KVL on loop 1 : } -V_s + V_1 + V_x = 0$$

$$\text{KCL on node A : } i_{AB} + i_{AC} = 0$$

$$\text{node B : } i_{BC} - i_{AB} = 0$$

$$\text{node C : } -i_{AC} - i_{BC} = 0$$

$$\text{Also } i_s = i_{AC}, \quad i_x = i_{AB}$$


We only have 1 loop so all elements have the same current.

$$\hookrightarrow \boxed{i_x = -i_s = -500 \mu\text{A}}$$

$$\text{Find } V_x \text{ using Ohm's Law } \rightarrow V_x = 56 \text{ k}\Omega \cdot i_x = 56 \text{ k}\Omega (-500 \mu\text{A})$$

$$\hookrightarrow \boxed{V_x = -28 \text{ V}}$$

2-32

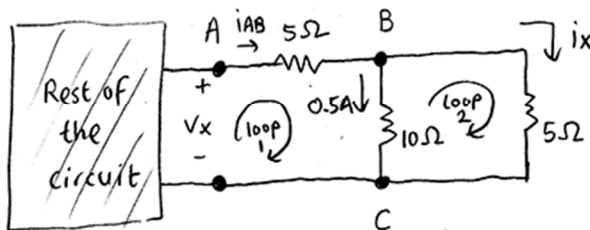

We have 2 loops and 3 nodes.

Find V_x and i_x !

KVL

$$\text{loop 1 } \rightarrow -V_x + 5 \Omega \cdot i_{AB} + 10 \Omega (0.5 \text{ A}) = 0 \quad \text{--- (1)}$$

$$\text{loop 2 } \rightarrow 10 \Omega (-0.5 \text{ A}) + 5 \Omega \cdot i_x = 0 \quad \text{--- (2)}$$

KCL

$$\text{node B } \rightarrow i_{AB} - 0.5 \text{ A} - i_x = 0 \quad \text{--- (3)}$$

3 equations,


3 unknowns:

V_x, i_x, i_{AB}

$$\text{(2)} \rightarrow 10 \Omega (-0.5 \text{ A}) + 5 \Omega i_x = 0 \rightarrow i_x = \frac{10 \Omega}{5 \Omega} \cdot (0.5 \text{ A}) \rightarrow \boxed{i_x = 1 \text{ A}} \quad \text{--- (4)}$$

$$\text{(4)} + \text{(3)} \rightarrow i_{AB} = 0.5 \text{ A} + i_x = 1.5 \text{ A} \quad \text{--- (5)}$$
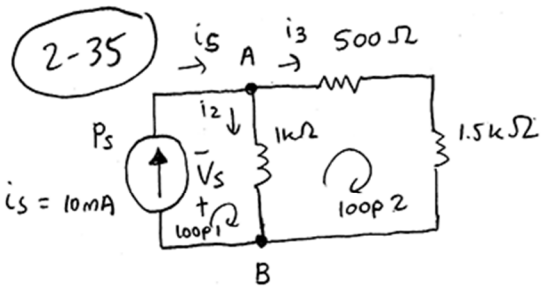
$$\text{(1)} + \text{(5)} \rightarrow V_x = 5 \Omega (1.5 \text{ A}) + 10 \Omega (0.5 \text{ A}) \rightarrow \boxed{V_x = 12.5 \text{ V}}$$



Find the power P_s !

KVL

loop 1 $\rightarrow V_s + 1k\Omega \cdot i_2 = 0$ ———— ①

loop 2 $\rightarrow 1k\Omega(-i_2) + 500\Omega \cdot i_3 + 1.5k\Omega \cdot i_3 = 0$ ———— ②

KCL

node A $\rightarrow i_s - i_2 - i_3 = 0$ ———— ③

3 equations, 3 unknowns: V_s, i_2, i_3


② $\rightarrow (500\Omega + 1.5k\Omega) i_3 = 1k\Omega i_2 \rightarrow i_3 = \frac{1}{2} i_2$ ———— ④

③ + ④ $\rightarrow 10mA - i_2 - \frac{1}{2} i_2 = 0 \rightarrow i_2 = \frac{20}{3} mA$ ———— ⑤


① + ⑤ $\rightarrow V_s = -1k\Omega \left(\frac{20}{3} mA \right) \rightarrow V_s = -\frac{20}{3} V$

Then, $P_s = V_s \cdot i_s = \left(-\frac{20}{3} V \right) (10mA) \rightarrow P_s = -\frac{200}{3} mW$

negative power \rightarrow power source.

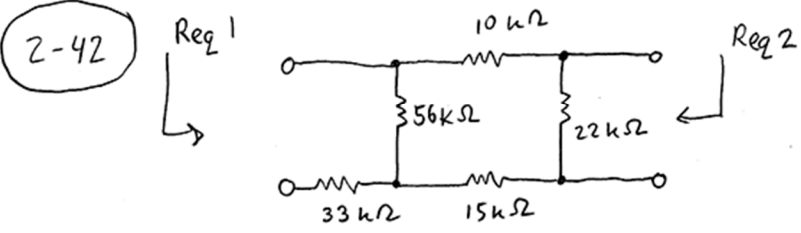

Find Req_1 and Req_2

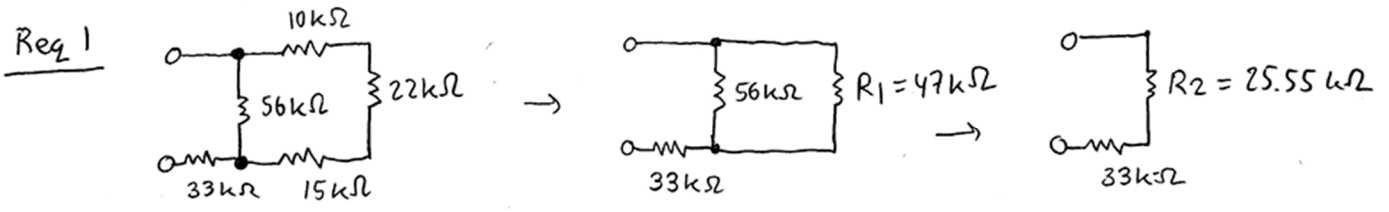



$R_1 \rightarrow$ serial circuit $\rightarrow R_1 = 10k\Omega + 22k\Omega + 15k\Omega = 47k\Omega$

$R_2 \rightarrow$ parallel circuit $\rightarrow R_2 = \left(\frac{1}{56k\Omega} + \frac{1}{47k\Omega} \right)^{-1} = \left(\frac{56 \cdot 47}{56 + 47} \right) k\Omega = 25.55 k\Omega$

$Req_1 \rightarrow$ serial circuit $\rightarrow Req_1 = 33k\Omega + 25.55 k\Omega$

$\rightarrow Req_1 = 58.55 k\Omega$

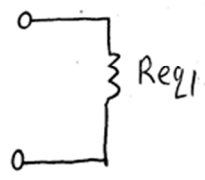


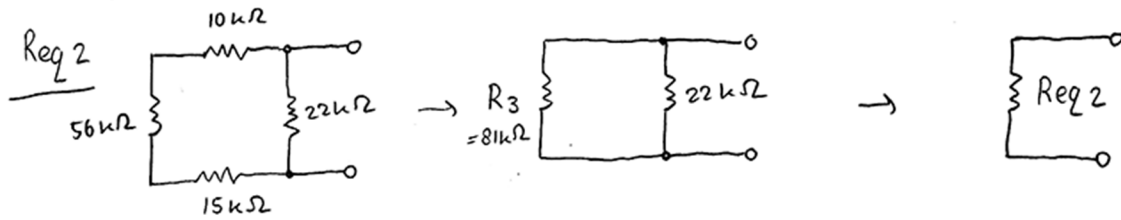


$R_3 \rightarrow$ serial circuit $\rightarrow R_3 = 10k\Omega + 56k\Omega + 15k\Omega \rightarrow R_3 = 81k\Omega$

$Req_2 \rightarrow$ parallel circuit $\rightarrow Req_2 = \left(\frac{1}{81k\Omega} + \frac{1}{22k\Omega} \right)^{-1} = \left(\frac{81 \cdot 22}{81 + 22} \right) k\Omega$

$\hookrightarrow Req_2 = 17.30 k\Omega$

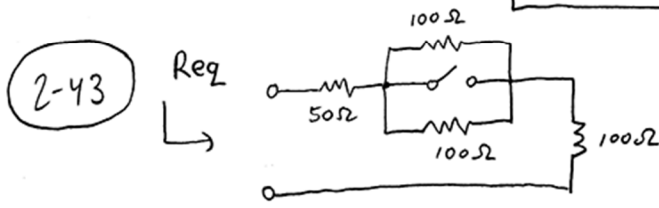

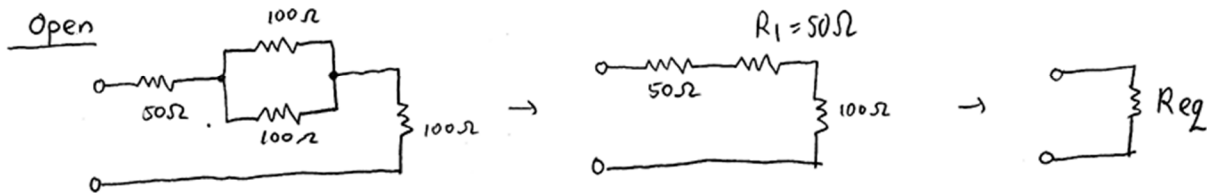
Find Req when the switch is open and closed!



$R_1 \rightarrow$ parallel $\rightarrow R_1 = \left(\frac{1}{100\Omega} + \frac{1}{100\Omega} \right)^{-1} = \left(\frac{100 \cdot 100}{100 + 100} \right) \Omega \rightarrow R_1 = 50\Omega$


$Req \rightarrow$ serial $\rightarrow Req = 50\Omega + 50\Omega + 100\Omega \rightarrow Req = 200\Omega$

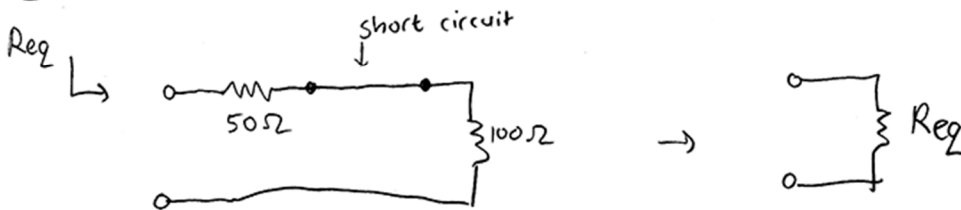Closed \rightarrow we will have a short circuit



$Req \rightarrow$ serial $\rightarrow Req = 50\Omega + 100\Omega \rightarrow Req = 150\Omega$

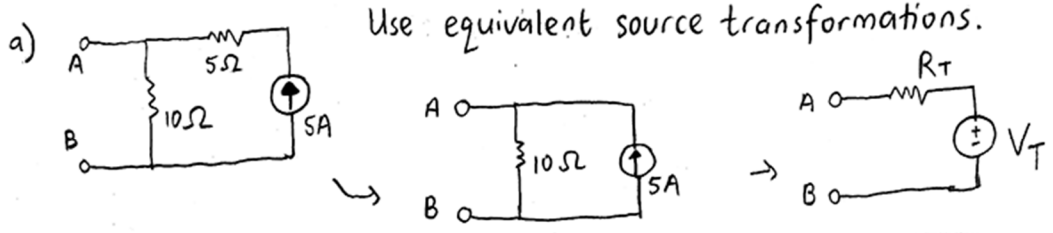
2-51 Find equivalent practical voltage source at terminals A and B!



$$R_T = 10\Omega$$


$$V_T = (5A)(10\Omega) = 50V$$

Practical voltage is 50V

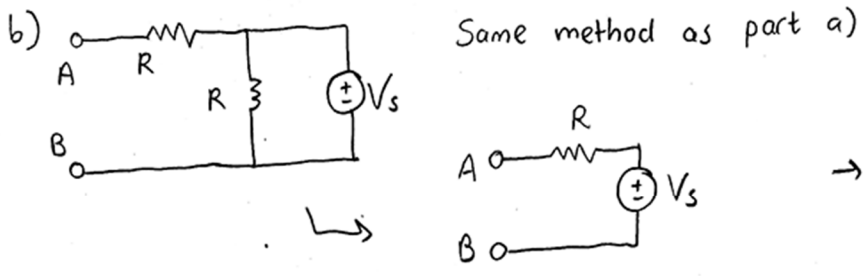

Practical voltage is V_s

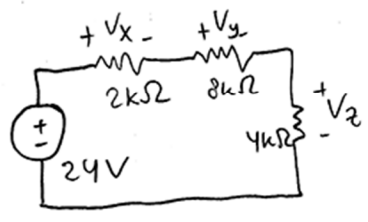2-58 Use voltage division to find V_x, V_y, V_z . Show that the sum is equal to the source voltage!



Voltage division

$$V_x = \frac{2k\Omega}{2k\Omega + 8k\Omega + 4k\Omega} \cdot 24V$$

$$V_y = \frac{8k\Omega}{2k\Omega + 8k\Omega + 4k\Omega} \cdot 24V$$

$$V_z = \frac{4k\Omega}{2k\Omega + 8k\Omega + 4k\Omega} \cdot 24V$$

$$V_x = \frac{48}{14} V$$


$$V_y = \frac{192}{14} V$$

$$V_z = \frac{96}{14} V$$

Sum of all voltage

$$\hookrightarrow V_x + V_y + V_z = \frac{48 + 192 + 96}{14} V = \frac{336}{14} V = \underline{\underline{24V}} \rightarrow \underline{\underline{\text{shown}}}$$

2-61 Use current division to find V_L !

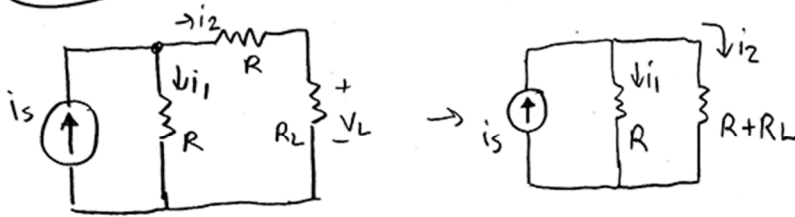

Current division


$$i_2 = \frac{1/(R+R_L)}{1/R + 1/(R+R_L)} \cdot i_s$$

$$i_2 = \frac{R}{2R+R_L} \cdot i_s$$

Then we have

$$V_L = R_L \cdot i_2 = \frac{R R_L}{2R+R_L} i_s$$

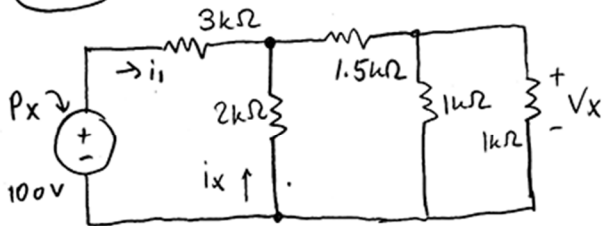2-75 Use circuit reduction to find V_x , i_x , P_x




$$P_x = -100V \cdot i_1$$

↑ negative because it provides power


→ Source transformation the 100V,
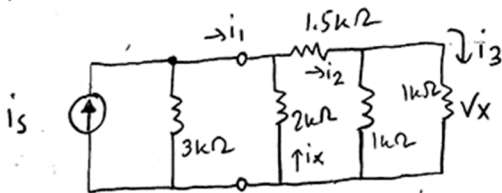
$$i_s = \frac{100V}{3k\Omega} = \frac{1}{30} A$$



Solve for i_1 , i_2 , i_3

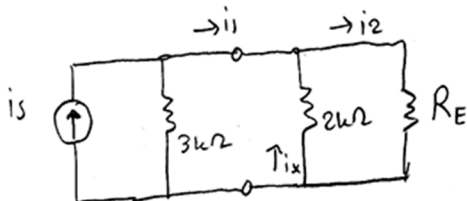→ Circuit reduction → $1.5k\Omega$ in series with parallel $1k\Omega$ and $1k\Omega$



$$R_E = 1.5k\Omega + \left(\frac{1}{1k\Omega} + \frac{1}{1k\Omega} \right)^{-1} = 1.5k\Omega + 0.5k\Omega$$

$$R_E = 2k\Omega$$

Use current division to find i_x and i_1 and i_2


$$i_x = \frac{-1/2k\Omega}{1/3k\Omega + 1/2k\Omega + 1/2k\Omega} \cdot \frac{1}{30} A = -12.5 mA$$

$$i_2 = \frac{1/2k\Omega}{1/3k\Omega + 1/2k\Omega + 1/2k\Omega} \cdot \frac{1}{30} A = 12.5 mA$$

$$i_1 = -i_x + i_2$$

$$i_1 = 25 mA$$

Then from the 2nd circuit, we have:

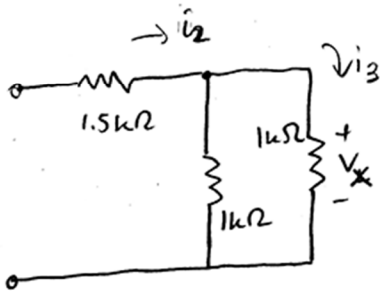

Solve i_3 using current division.

$$i_3 = \frac{1/1k\Omega}{1/1k\Omega + 1/1k\Omega} \cdot i_2 = \frac{1}{2} \cdot (12.5 \text{ mA})$$


$$= 6.25 \text{ mA}$$

Then $V_x = i_3 \cdot 1k\Omega = \boxed{6.25 \text{ V}}$

$P_x = -i_3(100 \text{ V}) = -(25 \text{ mA})(100 \text{ V}) = \boxed{-2.5 \text{ W}}$

→
$$\begin{aligned} i_x &= -12.5 \text{ mA} \\ V_x &= 6.25 \text{ V} \\ P_x &= -2.5 \text{ W} \end{aligned}$$

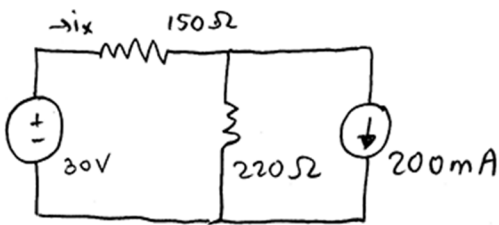
2-77 Use source transformation to find i_x



$$R_T = 220\Omega$$

$$V_T = 200 \text{ mA} \cdot 220\Omega = 44 \text{ V}$$

↓

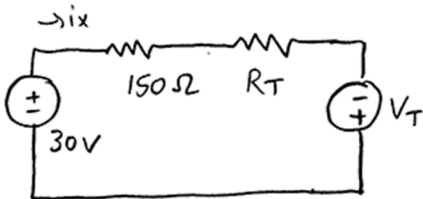

Then solve for i_x

$$i_x = \frac{30 \text{ V} + 44 \text{ V}}{150\Omega + 220\Omega} = \frac{74}{370} \text{ A}$$

$$i_x = \boxed{200 \text{ mA}}$$