


# Homework 4 Solution

3-13 Formulate mesh current, form  $A\vec{x} = \vec{b}$

mesh A  $\rightarrow -V_s + (R_1 + R_2) i_A - R_2 i_B = 0$

mesh B  $\rightarrow -R_2 i_A + (R_2 + R_3 + R_4) i_B = 0$
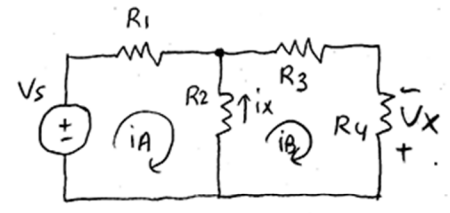
$$\rightarrow \begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 + R_4 \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} V_s \\ 0 \end{pmatrix}$$



a) Solve for  $i_A, i_B$ . We can solve this using Matlab too.

$-R_2 i_A + (R_2 + R_3 + R_4) i_B = 0$

$i_B = \frac{R_2}{R_2 + R_3 + R_4} i_A$

$(R_1 + R_2) i_A - R_2 i_B = V_s$

$\left[ R_1 + R_2 - \frac{R_2^2}{R_2 + R_3 + R_4} \right] i_A = V_s$

$$\rightarrow i_A = \frac{R_2 + R_3 + R_4}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V_s$$

$$i_B = \frac{R_2}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V_s$$


b) Solve  $V_x, i_x$

$$\rightarrow V_x = -R_4 i_B = \frac{-R_2 R_4}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V_s$$

$$i_x = i_B - i_A = \frac{-(R_3 + R_4)}{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)} V_s$$

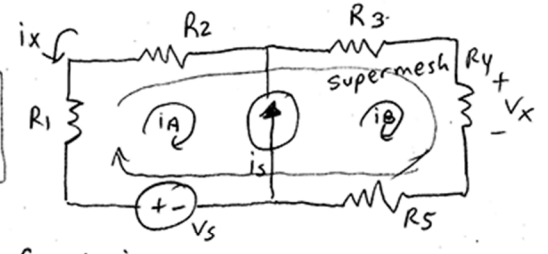3-18 a) Formulate mesh current

Supermesh  $\rightarrow -V_s + (R_1 + R_2) i_A + (R_3 + R_4 + R_5) i_B = 0$   
 $i_s \rightarrow i_B - i_A = i_s$



b) Using  $V_s = 12V, i_s = 10mA, R_1 = 2.7k\Omega, R_2 = 1.5k\Omega, R_3 = 680\Omega, R_4 = 2.2k\Omega, R_5 = 3.3k\Omega$ , solve for  $V_x, i_x$ .

$$\rightarrow \begin{bmatrix} 4200\Omega & 6180\Omega \\ -1 & 1 \end{bmatrix} \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} 12V \\ 0.01A \end{pmatrix} \rightarrow \begin{pmatrix} i_A \\ i_B \end{pmatrix} = \begin{pmatrix} -4.80mA \\ 5.20mA \end{pmatrix}$$


$$V_x = R_4 \cdot i_B = 11.44V$$

$$i_x = -i_A = 4.80mA$$

c) Find total power dissipated in the circuit.  $\rightarrow$  Sum of all positive power.  
 Resistors always dissipate power. Also note that current is entering the  $V_s$  positive terminal.  
 $\rightarrow V_s$  is absorbing power.

$$P_{diss} = (R_1 + R_2) i_A^2 + (R_3 + R_4 + R_5) i_B^2 - i_A V_s \rightarrow P_{diss} = 0.32W$$

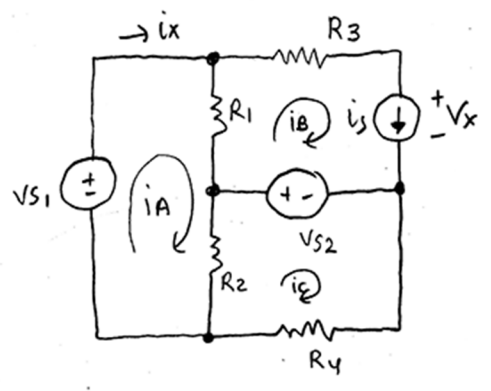- 3-20 a) Formulate mesh current, b) solve  $v_x, i_x$  symbolically, c) Solve  $v_x, i_x$   
 d) Find power supplied by  $V_{S1}$ .



a) mesh A  $\rightarrow -V_{S1} + (R_1 + R_2) i_A - i_B R_1 - i_C R_2 = 0$   
 mesh B  $\rightarrow i_B = i_S$   
 mesh C  $\rightarrow V_{S2} + (R_2 + R_4) i_C - R_2 i_A = 0$

$$\hookrightarrow \begin{bmatrix} R_1 + R_2 & -R_1 & -R_2 \\ 0 & 1 & 0 \\ -R_2 & 0 & R_2 + R_4 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} V_{S1} \\ i_S \\ -V_{S2} \end{bmatrix}$$

b) Solve with Matlab

$$\hookrightarrow \begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} \frac{V_{S1}(R_2 + R_4) - V_{S2}R_2 + (R_2 + R_4)R_1 i_S}{R_1R_2 + R_1R_4 + R_2R_4} \\ i_S \\ \frac{R_2V_{S1} + (R_1 + R_2)V_{S2} + R_1R_2 i_S}{R_1R_2 + R_1R_4 + R_2R_4} \end{bmatrix}$$

KVL on mesh B  $\rightarrow -V_{S2} + (i_B - i_A)R_1 + i_B R_3 + V_x = 0$

$$\begin{aligned} V_x &= V_{S2} - (R_1 + R_3) i_B + R_1 i_A \\ i_x &= i_A \end{aligned}$$

c) Solve using Matlab with  $V_{S1} = 15V, V_{S2} = 5V, i_S = 2.5mA, R_1 = R_2 = 8.2k\Omega$   
 $R_3 = 2.2k\Omega, R_4 = 3.3k\Omega$


$$\begin{bmatrix} i_A \\ i_B \\ i_C \end{bmatrix} = \begin{bmatrix} 3.026 \text{ mA} \\ 2.500 \text{ mA} \\ 1.723 \text{ mA} \end{bmatrix}$$

$$\begin{aligned} v_x &= 3.814 \text{ V} \\ i_x &= 3.026 \text{ mA} \end{aligned}$$

d)  $P_{V_{S1}} = -V_{S1} \cdot i_A$   
 $= -15V \cdot (3.026mA)$

$$P_{V_{S1}} = -45.4 \text{ mW}$$

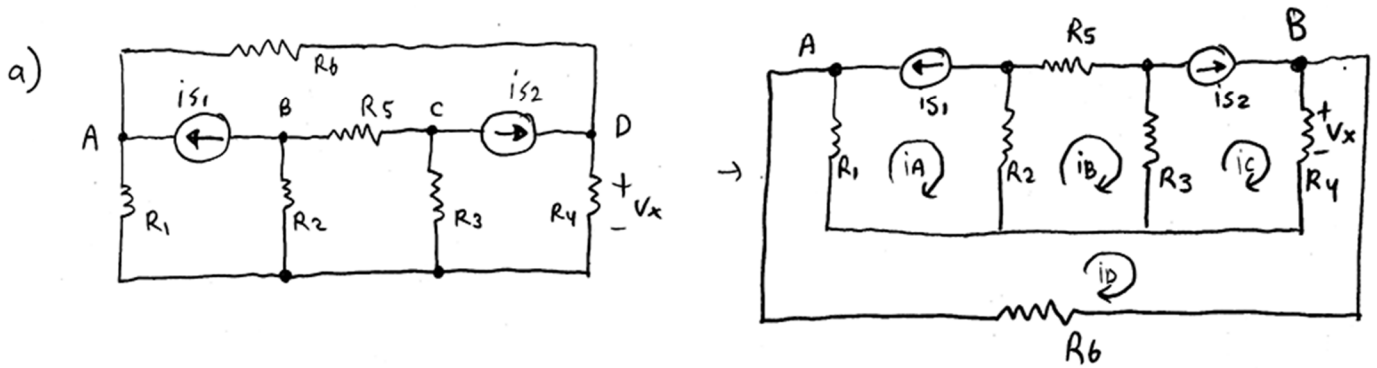- 3-21 a) Avoid supermesh, b) formulate mesh current, c) Solve  $V_x$   
 using  $R_1 = R_2 = R_3 = R_4 = 1k\Omega$ ,  $R_5 = R_6 = 10k\Omega$ ,  $i_{s1} = 100\text{ mA}$ ,  $i_{s2} = 50\text{ mA}$ .



- b) mesh A  $\rightarrow i_A = -i_{s1}$   
 mesh B  $\rightarrow (R_2 + R_3 + R_5) i_B - R_2 i_A - R_3 i_C = 0$   
 mesh C  $\rightarrow i_C = i_{s2}$   
 mesh D  $\rightarrow (R_1 + R_4 + R_6) i_D - R_1 i_A - R_4 i_C = 0$

$$\hookrightarrow \begin{bmatrix} 1 & 0 & 0 & 0 \\ -R_2 & R_2 + R_3 + R_5 & -R_3 & 0 \\ 0 & 0 & 1 & 0 \\ -R_1 & 0 & -R_4 & R_1 + R_4 + R_6 \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -i_{s1} \\ 0 \\ i_{s2} \\ 0 \end{bmatrix}$$


We have:

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ -1k\Omega & 12k\Omega & -1k\Omega & 0 \\ 0 & 0 & 1 & 0 \\ -1k\Omega & 0 & -1k\Omega & 12k\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -100\text{ mA} \\ 0 \\ 50\text{ mA} \\ 0 \end{bmatrix}$$

$$\hookrightarrow \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -100\text{ mA} \\ -4.1667\text{ mA} \\ 50\text{ mA} \\ -4.1667\text{ mA} \end{bmatrix}$$

c)  $V_x = R_4(i_C - i_D) = 1k\Omega(50\text{ mA} + 4.1667\text{ mA}) \rightarrow V_x = 54.1667\text{ V}$

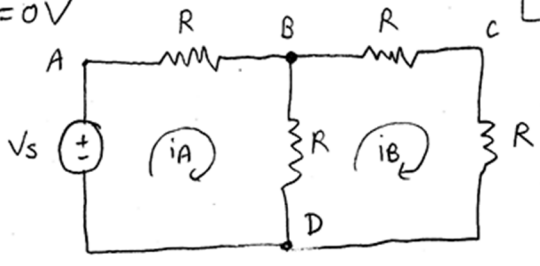3-24 All  $R = 1k\Omega$ ,  $V_S = 12V$ ,  $V_C = -2.4V$ ,  $V_B = 0V$   
 Find  $V_A, V_D$ , mesh current  $i_A, i_B$



Node voltages

$$\text{node B} \rightarrow \left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R}\right)V_B - \frac{V_A}{R} - \frac{V_C}{R} - \frac{V_D}{R} = 0$$

$$V_A + V_D = -V_C = 2.4V$$

$$V_A - V_D = V_S = 12V$$

$$\begin{aligned} V_A &= 7.2V \\ V_D &= -4.8V \end{aligned}$$

Mesh current

$$\begin{aligned} \text{mesh A} &\rightarrow -V_S + 2Ri_A - Ri_B = 0 \\ \text{mesh B} &\rightarrow -Ri_A + 3Ri_B = 0 \\ &\quad i_A = 3i_B \end{aligned}$$


$$-V_S + 5Ri_B = 0 \rightarrow i_B = \frac{V_S}{5R} = \frac{12V}{5k\Omega}$$

$$\begin{aligned} i_B &= 2.4mA \\ i_A &= 7.2mA \end{aligned}$$

3-25 a) Mesh current to solve  $i_A$ , b) Compute  $V_S/i_A$ , c) Find equivalent resistance  
 Solve symbolically.

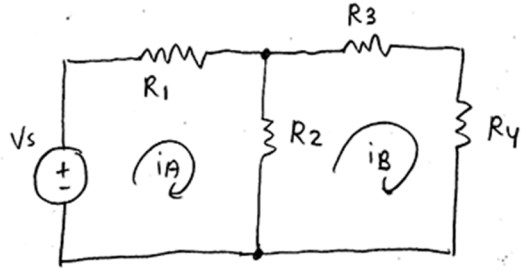
a) Same problem as 3-24.

$$\begin{aligned} \text{mesh A} &\rightarrow -V_S + (R_1 + R_2)i_A - R_2i_B = 0 \\ \text{mesh B} &\rightarrow (R_2 + R_3 + R_4)i_B - R_2i_A = 0 \end{aligned}$$



$$\hookrightarrow i_B = \frac{1}{R_2} ((R_1 + R_2)i_A - V_S)$$

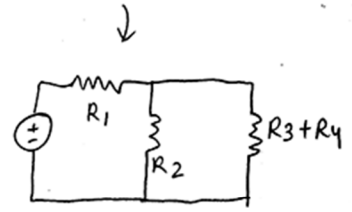
$$\begin{aligned} (R_2 + R_3 + R_4) \cdot \frac{1}{R_2} ((R_1 + R_2)i_A - V_S) - R_2i_A &= 0 \\ [(R_1 + R_2)(R_2 + R_3 + R_4) - R_2^2] i_A &= (R_2 + R_3 + R_4) V_S \end{aligned}$$



$$b) \frac{V_S}{i_A} = \frac{R_1(R_2 + R_3 + R_4) + R_2(R_3 + R_4)}{(R_2 + R_3 + R_4)}$$

$$\frac{V_S}{i_A} = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}$$


Same!

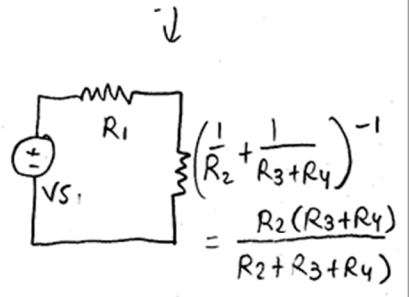

c) Shown on the right  $\rightarrow$  
$$R_{eq} = R_1 + \frac{R_2(R_3 + R_4)}{R_2 + R_3 + R_4}$$

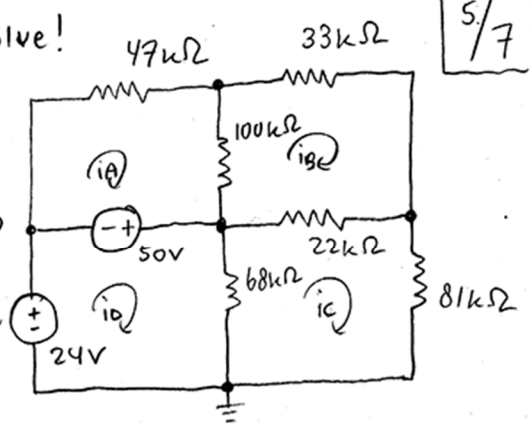3-27 a) Formulate mesh current into  $A\vec{x} = \vec{b}$  and solve!

mesh A  $\rightarrow (47k\Omega + 100k\Omega)i_A - (100k\Omega)i_B + 50V = 0$   
 mesh B  $\rightarrow (100k\Omega + 33k\Omega + 22k\Omega)i_B - (100k\Omega)i_A - (22k\Omega)i_D = 0$   
 mesh C  $\rightarrow (68k\Omega + 22k\Omega + 81k\Omega)i_C - (22k\Omega)i_B - (68k\Omega)i_D = 0$   
 mesh D  $\rightarrow -24V - 50V + 68k\Omega(i_D - i_C) = 0$




$$\begin{bmatrix} 147k\Omega & -100k\Omega & 0 & 0 \\ -100k\Omega & 155k\Omega & -22k\Omega & 0 \\ 0 & -22k\Omega & 171k\Omega & -68k\Omega \\ 0 & 0 & -68k\Omega & 68k\Omega \end{bmatrix} \begin{bmatrix} i_A \\ i_B \\ i_C \\ i_D \end{bmatrix} = \begin{bmatrix} -50V \\ 0 \\ 0 \\ 74V \end{bmatrix}$$

using Matlab  $\rightarrow \vec{x} = A^{-1}\vec{b}$

$$\begin{pmatrix} i_A \\ i_B \\ i_C \\ i_D \end{pmatrix} = \begin{pmatrix} -0.4907 \text{ mA} \\ -0.2213 \text{ mA} \\ 0.6712 \text{ mA} \\ 1.7594 \text{ mA} \end{pmatrix}$$

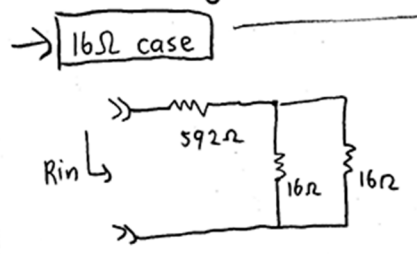3-97 Check if  $R_{in} = 600\Omega \pm 2\%$  and  $R_{out} = 16\Omega, 8\Omega, 4\Omega \pm 2\%$


Essentially, we have the following circuits  $\rightarrow$



$$R_{in} = 592\Omega + \left(\frac{1}{16\Omega} + \frac{1}{16\Omega}\right)^{-1}$$




$R_{in} = 600\Omega$

Thevenin Resistance =  $R_{out}$

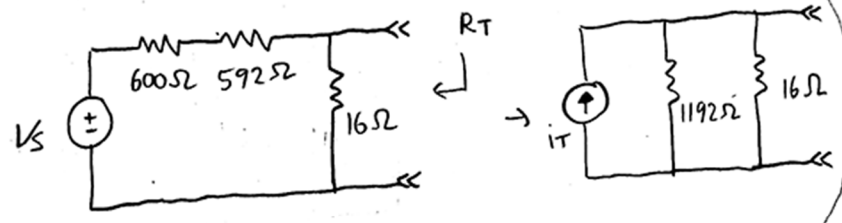


$$R_T = \left(\frac{1}{1192\Omega} + \frac{1}{16\Omega}\right)^{-1}$$

$R_T = 15.788\Omega \leftarrow R_{out}$

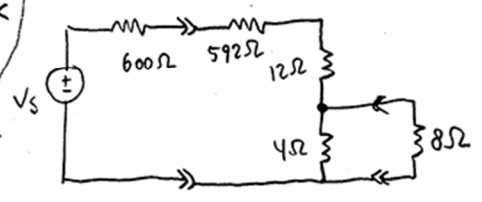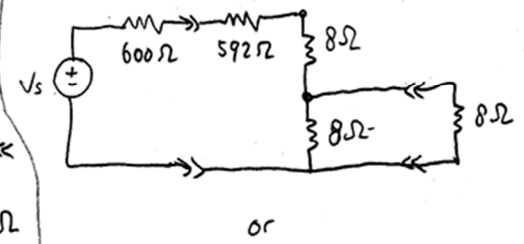
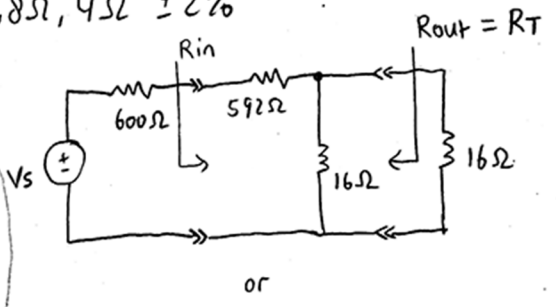


→ 8Ω case

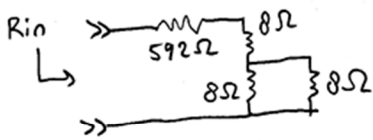

$$R_{in} = 592\Omega + 8\Omega + \left(\frac{1}{8\Omega} + \frac{1}{8\Omega}\right)^{-1}$$


$$R_{in} = 604\Omega$$

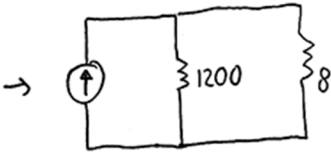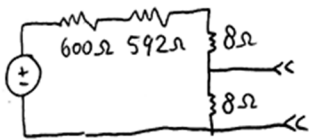

$$R_{out} = \left(\frac{1}{1200\Omega} + \frac{1}{8\Omega}\right)^{-1}$$



$$R_{out} = 7.947\Omega$$

→ 4Ω case

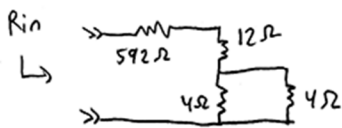

$$R_{in} = 592\Omega + 12\Omega + \left(\frac{1}{4\Omega} + \frac{1}{4\Omega}\right)^{-1}$$

$$R_{in} = 606\Omega$$

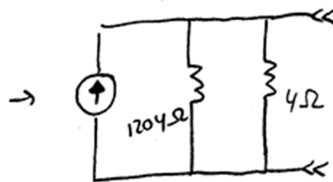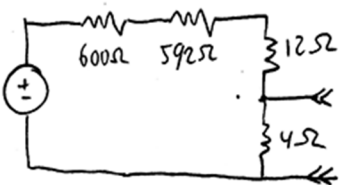

$$R_{out} = \left(\frac{1}{1204\Omega} + \frac{1}{4\Omega}\right)^{-1}$$

$$R_{out} = 3.987\Omega$$

So, we have :

case	R <sub>in</sub>	R <sub>out</sub>
16Ω	600Ω	15.788Ω
8Ω	604Ω	7.947Ω
4Ω	606Ω	3.987Ω

Target range :

$$R_{in} = 600\Omega \pm 2\% \in [588\Omega, 612\Omega]$$

$$R_{out} = 16\Omega \pm 2\% \in [15.68\Omega, 16.32\Omega]$$


$$8\Omega \pm 2\% \in [7.84\Omega, 8.16\Omega]$$

$$4\Omega \pm 2\% \in [3.92\Omega, 4.08\Omega]$$

Their claim is proven correct!

3-98

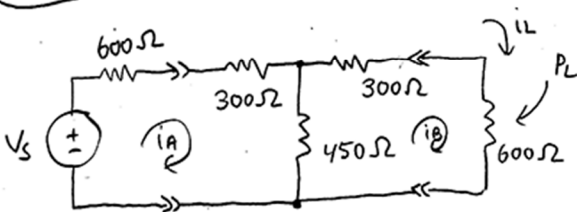Find the power with or without the attenuator! Express the fraction in dB!



Find  $i_L$  (load current)

$$\text{mesh A} \rightarrow -V_s + (600\Omega + 300\Omega + 450\Omega)i_A - (450\Omega)i_B = 0$$

$$\text{mesh B} \rightarrow (450\Omega + 300\Omega + 600\Omega)i_B - (450\Omega)i_A = 0$$

$$i_L = i_B$$

$$\begin{aligned} (1350\Omega) i_A - (450\Omega) i_B &= V_S \\ -(450\Omega) i_A + (1350\Omega) i_B &= 0 \rightarrow i_A = 3i_B \end{aligned}$$

$$(1350\Omega) 3i_B - (450\Omega) i_B = V_S$$

$$i_B = \frac{V_S}{3600\Omega}$$

$$\hookrightarrow i_L = \frac{V_S}{3600\Omega} \rightarrow P_L = R_L i_L^2 = (600\Omega) \left(\frac{V_S}{3600\Omega}\right)^2$$

$$P_{L1} = \frac{1}{21600\Omega} V_S^2$$

→ without the attenuator



$$i_L = \frac{V_S}{1200\Omega} \rightarrow P_L = R_L i_L^2 = (600\Omega) \left(\frac{V_S}{1200\Omega}\right)^2$$


$$P_{L2} = \frac{1}{2400\Omega} V_S^2$$

The attenuator reduction  $\rightarrow G = \frac{P_{L1}}{P_{L2}} = \frac{2400}{21600} = \frac{1}{9}$

$$\hookrightarrow 10 \cdot \log_{10}(G) = \underline{\underline{-9.54 \text{ dB}}}$$

3-100 Typo in the problem. We want to solve  $v \leq 4V$  and  $i \leq 50mA$

The following circuit should work:

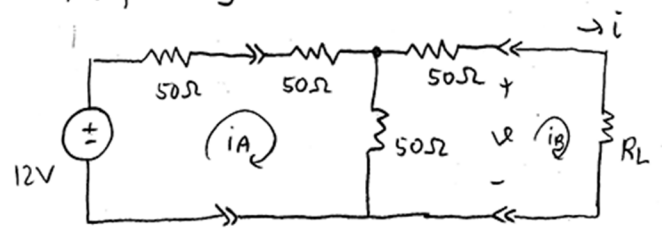

$$\begin{aligned} \text{mesh A} &\rightarrow -12V + (150\Omega) i_A - (50\Omega) i_B = 0 \\ \text{mesh B} &\rightarrow (-50\Omega) i_A + (100\Omega + R_L) i_B = 0 \end{aligned}$$

$$i_A = \frac{100\Omega + R_L}{50\Omega} i_B$$

$$\hookrightarrow (150\Omega) \frac{100\Omega + R_L}{50\Omega} i_B - (50\Omega) i_B = 12V$$

$$(250\Omega + 3R_L) i_B = 12V$$

$i = i_B$

Then,  $v = R_L i = \frac{R_L}{250\Omega + 3R_L} 12V$

$$i_B = \frac{12V}{250\Omega + 3R_L} = i$$

So, we have the following  $v$  and  $i$  range.

$\lim_{R_L \rightarrow 0} v = 0V$	$\lim_{R_L \rightarrow \infty} v = 4V$
$\lim_{R_L \rightarrow 0} i = 48mA$	$\lim_{R_L \rightarrow \infty} i = 0mA$

Shown that for any  $R_L$ ,  
 $v \leq 4V$  and  $i \leq 50mA$