

Homework 6 Solution

1/7

9-4 Find Laplace transform of $f(t) = 10(e^{-2000t} - 2e^{-1000t})u(t)$. Locate poles & zeros!

$$\begin{aligned} \mathcal{L}\{f(t)\} &= 10 \mathcal{L}\{e^{-2000t} u(t)\} - 20 \mathcal{L}\{e^{-1000t} u(t)\} \\ &= 10 \frac{1}{s+2000} - 20 \frac{1}{s+1000} = \frac{10(s+1000) - 20(s+2000)}{(s+2000)(s+1000)} \end{aligned}$$

$$\mathcal{L}\{f(t)\} = -10 \frac{(s+3000)}{(s+1000)(s+2000)}$$

$$\text{poles} = \{-1000, -2000\}, \text{zeros} = \{-3000, \infty\}$$

9-9 Find Laplace t. of $f(t) = \delta'(t) + \delta(t) - e^{-t}u(t)$. Locate poles & zeros!

$$\mathcal{L}\{f(t)\} = \mathcal{L}\{\delta'(t)\} + \mathcal{L}\{\delta(t)\} - \mathcal{L}\{e^{-t}u(t)\} = s\mathcal{L}\{\delta(t)\} - \delta(0^-) + 1 - \frac{1}{s+1}$$


$\delta(0^-) \rightarrow$ the 0^- is just before 0, so $\delta(0^-) = 0$

$$\hookrightarrow \mathcal{L}\{f(t)\} = s + 1 - \frac{1}{s+1} = \frac{s^2 + 2s + 1 - 1}{s+1} = \frac{s(s+2)}{s+1}$$

$$\begin{aligned} \text{zeros} &= 0, -2 \\ \text{pole} &= -1, \infty \end{aligned}$$

9-18
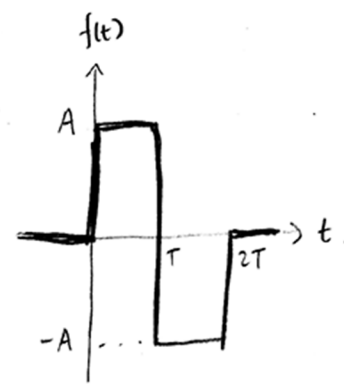
$$a) f(t) = Au(t) - 2Au(t-T) + Au(t-2T)$$



b) Find $\mathcal{L}\{f(t)\}$!

$$\hookrightarrow \mathcal{L}\{f(t)\} = A\left(\frac{1}{s}\right) - 2A\left(\frac{e^{-Ts}}{s}\right) + A\left(\frac{e^{-2Ts}}{s}\right)$$

$$\mathcal{L}\{f(t)\} = \frac{A}{s} (1 - 2e^{-Ts} + e^{-2Ts})$$

c) Solve for $\mathcal{L}\{f(t)\}$ using the Laplace transform definition!

$$\begin{aligned} F\{f(t)\} &= \int_0^\infty f(t) e^{-st} dt = \int_0^\infty Au(t) e^{-st} dt - \int_0^\infty 2Au(t-T) e^{-st} dt + \int_0^\infty Au(t-2T) e^{-st} dt \\ &= A \int_0^\infty e^{-st} dt - 2A \int_T^\infty e^{-st} dt + A \int_{2T}^\infty e^{-st} dt \\ &= A \left(\frac{1}{-s} e^{-st} \Big|_{t=0}^\infty \right) - 2A \left(\frac{1}{-s} e^{-st} \Big|_{t=T}^\infty \right) + A \left(\frac{1}{-s} e^{-st} \Big|_{t=2T}^\infty \right) \\ &= \left[A \frac{1}{s} - 2A \frac{e^{-Ts}}{s} + A \frac{e^{-2Ts}}{s} \right] \rightarrow \text{the same as b).} \end{aligned}$$

9-21 Find inverse Laplace Transform!

$$a) F_1(s) = \frac{10}{s(s+50)} = \frac{A}{s} + \frac{B}{s+50} = \frac{A(s+50) + Bs}{s(s+50)} = \frac{(A+B)s + 50A}{s(s+50)}$$

$$\hookrightarrow \begin{matrix} A = 1/5 \\ B = -1/5 \end{matrix} \rightarrow \mathcal{L}^{-1}\{F_1(s)\} = \mathcal{L}^{-1}\left\{\frac{1/5}{s} - \frac{1/5}{s+50}\right\} = \frac{1}{5}u(t) - \frac{1}{5}e^{-50t}u(t)$$

$$b) F_2(s) = \frac{s+2}{(s+3)(s+4)} = \frac{A}{s+3} + \frac{B}{s+4} = \frac{A(s+4) + B(s+3)}{(s+3)(s+4)} = \frac{(A+B)s + (4A+3B)}{(s+3)(s+4)}$$

$$\hookrightarrow \begin{matrix} A+B=1 \\ 4A+3B=2 \end{matrix} \rightarrow \begin{matrix} A = -1 \\ B = 2 \end{matrix} \rightarrow \mathcal{L}^{-1}\{F_2(s)\} = \mathcal{L}^{-1}\left\{-\frac{1}{s+3} + \frac{2}{s+4}\right\} = (-e^{-3t} + 2e^{-4t})u(t)$$

9-23 Find inverse Laplace!

$$a) F_1(s) = \frac{50(s+1000)(s+2000)}{(s+500)(s+5000)} = \left(\frac{A}{s+500} + \frac{B}{s+5000} + C\right) \cdot 50$$

$$50 \left(\frac{s^2 + 3000s + 2 \cdot 10^6}{(s+500)(s+5000)}\right) = 50 \left(\frac{A(s+5000) + B(s+500) + C(s+500)(s+5000)}{(s+500)(s+5000)}\right)$$

$$= 50 \left(\frac{Cs^2 + (A+B+5500C)s + (5000A+500B+25 \cdot 10^5C)}{(s+500)(s+5000)}\right)$$

Solving this =

$$\begin{matrix} C = 1 \\ A+B+5500C = 3000 \\ 5000A+500B+25 \cdot 10^5C = 2 \cdot 10^6 \end{matrix} \rightarrow \begin{matrix} A+B = -2500 \\ 5000A+500B = -5 \cdot 10^5 \end{matrix} \rightarrow \begin{matrix} A = 500/3 \\ B = -8000/3 \\ C = 1 \end{matrix}$$

$$\mathcal{L}\{F_1(s)\} = 50 \mathcal{L}^{-1}\left\{\frac{500/3}{s+500} - \frac{8000/3}{s+5000} + 1\right\} = \frac{50}{3} \left(500 e^{-500t}u(t) - 8000 e^{-5000t}u(t)\right) + 50\delta(t)$$

3/7

$$\begin{aligned}
 \text{b) } F_2(s) &= \frac{50s^2}{(s+100)(s+500)} = 50 \left(\frac{A}{s+100} + \frac{B}{s+500} + C \right) \\
 &= 50 \left(\frac{A(s+500) + B(s+100) + C(s+100)(s+500)}{(s+100)(s+500)} \right) \\
 &= 50 \left(\frac{Cs^2 + (A+B+600C)s + (500A+100B+50000C)}{(s+100)(s+500)} \right)
 \end{aligned}$$

$$\left. \begin{aligned} C &= 1 \\ A+B+600C &= 0 \\ 500A+100B+50000C &= 0 \end{aligned} \right\} \begin{aligned} A+B &= -600 \\ 500A+100B &= -50000 \end{aligned} \rightarrow \begin{cases} A = 25 \\ B = -625 \\ C = 1 \end{cases}$$


$$\begin{aligned}
 \mathcal{L}^{-1}\{F_2(s)\} &= 50 \mathcal{L}^{-1}\left\{ \frac{25}{s+100} - \frac{625}{s+500} + 1 \right\} \\
 &= \underline{\underline{50(25e^{-100t}u(t) - 625e^{-500t}u(t) + \delta(t))}}
 \end{aligned}$$

9-26 Find inverse Laplace and sketch w/ $\beta > 0$

$$\begin{aligned}
 \text{a) } F_1(s) &= A \frac{\beta(s+\beta)}{s(s^2+\beta^2)} = A\beta \left(\frac{K_1}{s} + \frac{K_2s}{s^2+\beta^2} + \frac{K_3\beta}{s^2+\beta^2} \right) \\
 &= A\beta \left(\frac{K_1(s^2+\beta^2) + K_2s^2 + K_3s\beta}{s(s^2+\beta^2)} \right)
 \end{aligned}$$

$$\begin{aligned}
 \hookrightarrow \begin{cases} (K_1+K_2) &= 0 \\ (K_3\beta) &= 1 \\ (K_1\beta^2) &= \beta \end{cases} \rightarrow \begin{cases} K_1 = 1/\beta \\ K_2 = -1/\beta \\ K_3 = 1/\beta \end{cases} \rightarrow F_1(s) = A \left(\frac{1}{s} - \frac{s}{s^2+\beta^2} + \frac{\beta}{s^2+\beta^2} \right)
 \end{aligned}$$

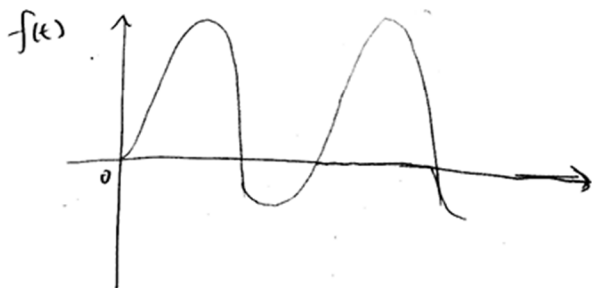
$$\mathcal{L}^{-1}\{F_1(s)\} = A \mathcal{L}^{-1}\left\{ \frac{1}{s} - \frac{s}{s^2+\beta^2} + \frac{\beta}{s^2+\beta^2} \right\} = \underline{\underline{A(1 - \cos(\beta t) + \sin(\beta t))u(t)}}$$



$$b) F_2(s) = \frac{As(s+\beta)}{s^2+\beta^2} = A \left(\frac{s^2+\beta s}{s^2+\beta^2} \right) = A \left(\frac{s^2+\beta^2 + (\beta s - \beta^2)}{s^2+\beta^2} \right)$$


$$= A \left(1 + \frac{\beta s}{s^2+\beta^2} - \frac{\beta \cdot \beta}{s^2+\beta^2} \right)$$
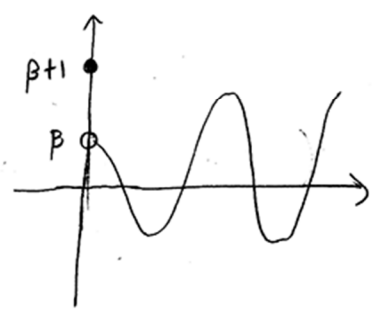
$$\begin{aligned} \hookrightarrow \mathcal{L}^{-1}\{F_2(s)\} &= A \mathcal{L}^{-1}\left\{1 + \frac{\beta s}{s^2+\beta^2} - \frac{\beta^2}{s^2+\beta^2}\right\} \\ &= A \left(\delta(t) + \beta \cos(\beta t) u(t) - \beta \sin(\beta t) u(t) \right) \end{aligned}$$



9-46 Switch is open for a long time and then closed at $t=0$. $R=10k\Omega, L=100mH, V_A=24V$

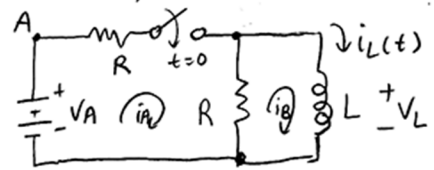a) We have $V_L(t) = L \frac{di_L(t)}{dt}$



Using mesh current

$$\begin{aligned} \hookrightarrow -V_A + i_A R + (i_A - i_B) R &= 0 \quad (1) \\ (i_B - i_A) R + L \frac{di_L(t)}{dt} &= 0 \quad (2) \end{aligned} \quad \left. \vphantom{\begin{aligned} \hookrightarrow -V_A + i_A R + (i_A - i_B) R \\ (i_B - i_A) R + L \frac{di_L(t)}{dt} \end{aligned}} \right\} \text{Solve for } i_B$$

$i_B = i_L(t)$

$$\begin{aligned} (1) \rightarrow 2R i_A &= R i_B + V_A & (2) \rightarrow \left(i_B - \frac{i_B}{2} - \frac{V_A}{2R} \right) R + L \frac{di_L(t)}{dt} &= 0 \\ i_A &= \frac{i_B}{2} + \frac{V_A}{2R} & \frac{i_B}{2} R + L \frac{di_L(t)}{dt} &= \frac{V_A}{2} \end{aligned}$$

Initial condition for $i_L(0) = 0$
because the switch is open \rightarrow no power.

$$\hookrightarrow \frac{1}{2} R i_L(t) + L \frac{di_L(t)}{dt} = \frac{V_A}{2}$$

b) s-domain $\rightarrow \frac{1}{2} R I_L(s) + L s I_L(s) = \frac{1}{2} V_A(s)$

c) $V_A(s) = \mathcal{L}\{V_A \cdot u(t)\} = \frac{24V}{s}$

$$\left(\frac{1}{2} \cdot 10k\Omega + 100mH s \right) I_L(s) = \frac{24V}{2s} \rightarrow I_L(s) = \frac{12V}{s(100mH s + 5k\Omega)}$$

Rearrange into $I_L(s) = \frac{120}{s(s+50000)} = \frac{0.0024}{s} - \frac{0.0024}{s+50000}$


$$d) \mathcal{L}^{-1}\{I_L(s)\} = \mathcal{L}^{-1}\left\{\frac{0.0024}{s} - \frac{0.0024}{s+50000}\right\}$$

$$= \underline{\underline{2.4 \text{ mA} (u(t) - e^{-50000t} u(t))}}$$


5/7

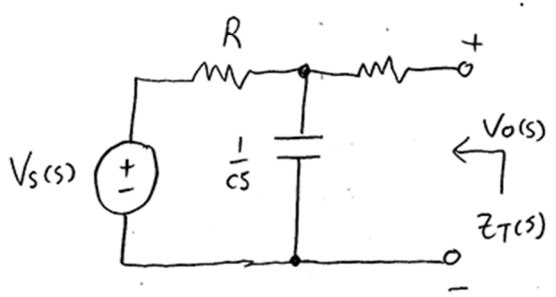10-17 a) Use voltage division to find $V_O(s)$

$$\hookrightarrow V_O(s) = \frac{1/cs}{R + 1/cs} V_S(s) = \frac{1}{1+Rcs} V_S(s)$$



b) Use the lookback method to find Z_T !

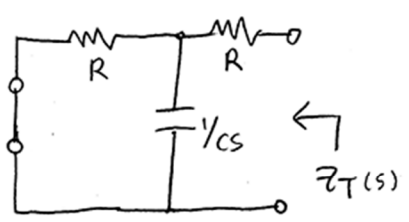

$$Z_T(s) = R + \left(\frac{1}{R} + cs\right)^{-1} = R + \left(\frac{R}{1+Rcs}\right)$$

$$= \frac{R(1+Rcs) + R}{1+Rcs} = \underline{\underline{\frac{Rcs + 2R}{Rcs + 1}}}$$

10-26 Switch at B for a long time, then moved to A at $t=0$.

The image indicates that it moved from A to B instead. Might be a typo, but I will solve for both.

Solve for $I_L(s)$ and $i_L(t)$



B to A

Not connected to power $\rightarrow i_L(0) = 0$
 KVL $\rightarrow -V_A(s) + I_L(s) Ls + I_L(s) 2R = 0$

$$V_A(s) = \mathcal{L}\{V_A u(t)\} = \frac{V_A}{s}$$

$$\hookrightarrow I_L(s) = \frac{V_A/s}{Ls + 2R} = \frac{V_A/L}{(s + 2R/L)s} = \frac{V_A/2R}{s} - \frac{V_A/2R}{s + \frac{2R}{L}}$$
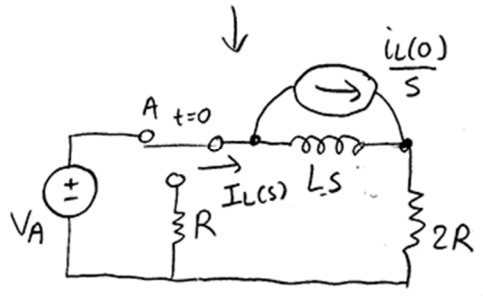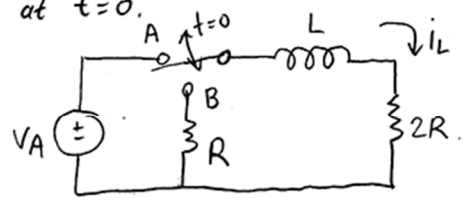
$$i_L(t) = \mathcal{L}^{-1}\{I_L(s)\} = \underline{\underline{\frac{V_A}{2R} (u(t) - e^{-\frac{2R}{L}t} u(t))}}$$




A to B

When connected for a long time, inductance becomes like a short circuit.


$i_L(0) = V_A / 2R$

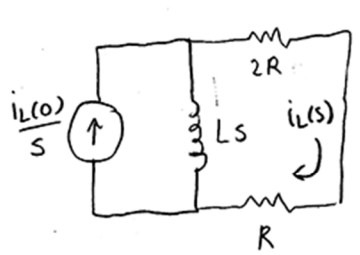Do circuit reduction and current division



$$I_L(s) = \left(\frac{1/3R}{1/s + 1/3R} \right) \frac{i_L(0)}{s}$$
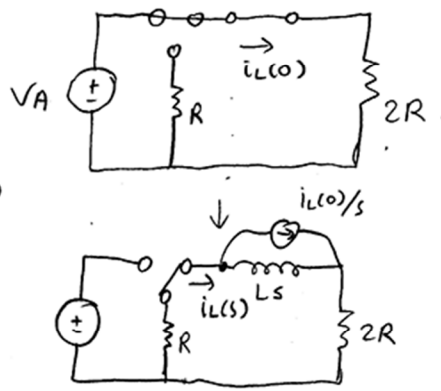
$$= \left(\frac{s}{3R/L + s} \right) \frac{V_A}{2Rs}$$




$I_L(s) = \frac{V_A}{2R} \left(\frac{1}{s + 3R/L} \right)$

Solve for $i_L(t)$


$i_L(t) = \mathcal{L}^{-1} \{ I_L(s) \} = \frac{V_A}{2R} \left(e^{-3R/Lt} u(t) \right)$

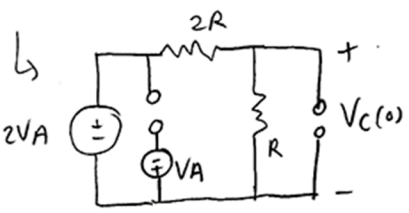10-27 Pos A to pos B. Solve for $I_C(s)$, $i_C(t)$, $V_C(s)$, $V_C(t)$.


Held for a long time, capacitor becomes like an open circuit.



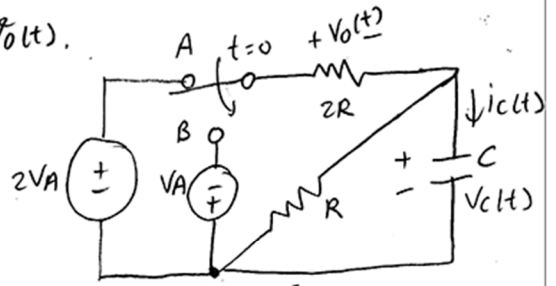Voltage division
 $V_C(0) = \frac{R}{2R+R} \cdot 2VA = \frac{2}{3} VA$



Circuit B

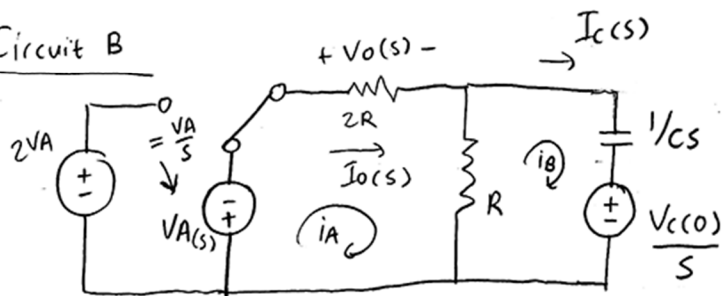

Solve for i_A , i_B using mesh current.

$I_C(s) = i_A$
 $I_C(s) = i_B$

mesh current

7/7

$$i_A \rightarrow V_A(s) + (2R+R)i_A - R i_B = 0$$
$$\frac{V_A}{s} + 3R i_A - R i_B = 0$$

$$i_B \rightarrow (R + \frac{1}{Cs}) i_B - R i_A + \frac{V_C(0)}{s} = 0$$
$$-R i_A + (R + \frac{1}{Cs}) i_B + \frac{2V_A}{3s} = 0$$

$$\begin{bmatrix} 3R & -R \\ -R & R + \frac{1}{Cs} \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} -\frac{V_A}{s} \\ -\frac{2V_A}{3s} \end{bmatrix}$$

Solve in Matlab \rightarrow

$$\begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} I_0(s) \\ I_C(s) \end{bmatrix} = \begin{bmatrix} -\frac{V_A}{3Rs} \left(\frac{3+5CRs}{3+2CRs} \right) \\ -\frac{3V_A C}{2CRs+3} \end{bmatrix}$$

Then $i_C(t) = \mathcal{L}^{-1}\{I_C(s)\} = \mathcal{L}^{-1}\left\{-\frac{3V_A C}{2RC} \left(\frac{1}{s+3/2RC}\right)\right\}$

$$= -\frac{3V_A}{2R} e^{-\frac{3}{2RC}t} u(t)$$

$$V_O(s) = 2R \cdot I_0(s) = -\frac{2V_A}{3s} \left(\frac{3+5CRs}{3+2CRs}\right) = -\frac{2V_A}{3} \left(\frac{K_1}{s} + \frac{K_2}{3+2CRs}\right)$$
$$= -\frac{2V_A}{3} \left(\frac{3K_1 + 2CRs K_1 + K_2 s}{s(3+2CRs)}\right) \rightarrow K_1 = 1$$
$$K_2 = 3CR$$

$$\hookrightarrow V_O(s) = -\frac{2V_A}{3} \left(\frac{1}{s} + \frac{3CR}{3+2CRs}\right)$$

$$V_O(t) = \mathcal{L}^{-1}\{V_O(s)\} = -\frac{2V_A}{3} \left(u(t) + \frac{3}{2} e^{-\frac{3}{2CR}t} u(t)\right)$$