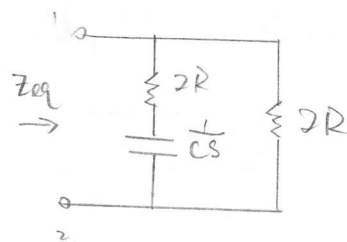


HW 7 Solution

10.3 a) S-domain circuits w/ zero IC

$$Z_{eq}(s) = (2R + \frac{1}{Cs}) \parallel 2R$$



$$= \frac{1}{\frac{1}{2R} + \frac{1}{2R + \frac{1}{Cs}}} = \frac{2R + \frac{1}{Cs}}{(2R + \frac{1}{Cs})\frac{1}{2R} + 1}$$

$$= \frac{2R + \frac{1}{Cs}}{2 + \frac{1}{2RCs}} = \boxed{\frac{Rs + \frac{1}{2C}}{s + \frac{1}{4RC}}} = R \frac{s + \frac{1}{2RC}}{s + \frac{1}{4RC}}$$

$$\boxed{\text{pole: } s = -\frac{1}{4RC}}$$

$$\boxed{\text{zero: } s = -\frac{1}{2RC}}$$

b) $-\frac{1}{4RC} = -22 \times 10^3 \text{ rad/s} \Rightarrow RC = 1.1364 \times 10^{-5}$


Let $R = 10 \Omega$, $C = 1.1364 \times 10^{-6} \text{ F} = 1.1364 \mu\text{F}$

Resulting zero:

$$s = -\frac{1}{2RC} = 2 \cdot s_{\text{pole}} = \boxed{-44 \text{ krad/s}}$$

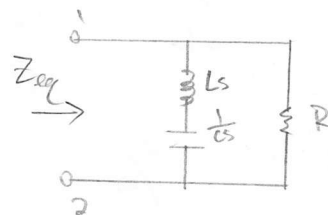10.7 a) S-domain circuits w/ zero initial condition

$$Z_{eq} = (Ls + \frac{1}{Cs}) \parallel R$$



$$= \frac{1}{\frac{1}{R} + \frac{1}{Ls + \frac{1}{Cs}}} = \frac{Ls + \frac{1}{Cs}}{\frac{1}{R}s + \frac{1}{RCs} + 1}$$

$$= \frac{Ls^2 + \frac{1}{C}}{\frac{1}{R}s^2 + s + \frac{1}{RC}} = \boxed{R \frac{s^2 + \frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}}$$

$$\boxed{\begin{aligned} \text{zeros: } s &= \pm \frac{1}{\sqrt{LC}} j \\ \text{poles: } s &= \frac{-RC \pm \sqrt{R^2C^2 - 4LC}}{2LC} \end{aligned}}$$

b) zeros: $s = \pm \frac{1}{\sqrt{LC}}j$ w/ $C = 0.1 \mu F = 10^{-7} F$

$10j \text{ krad/s} = \frac{1}{\sqrt{L(0.1 \mu F)}} \Rightarrow \boxed{L = 0.1 \text{ H}}$


c) pole: $s = \frac{-RC \pm \sqrt{R^2 C^2 - 4LC}}{2LC}$ w/ $R = 10^3 \Omega, C = 10^{-7} F, L = 0.1 \text{ H}$

$$s = \frac{-(10^3 \Omega)(10^{-7} F) \pm \sqrt{(10^3 \Omega)^2 (10^{-7} F)^2 - 4(0.1 \text{ H})(10^{-7} F)}}{2(0.1 \text{ H})(10^{-7} F)}$$

$$= -5000 \pm 8660j \text{ rad/s} = \boxed{-5 \pm 8.66j \text{ krad/s}}$$

10.9

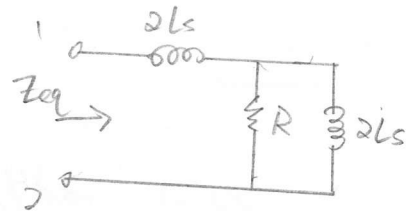a) S-domain circuits w/ zero initial condition:



$$Z_{eq}(s) = 2Ls + (R \parallel 2Ls)$$

$$= 2Ls + \frac{1}{\frac{1}{R} + \frac{1}{2Ls}} = 2Ls + \frac{2LRs}{2Ls + R} = \frac{2Ls(2Ls + R) + 2LRs}{2Ls + R}$$

$$= \frac{4L^2 s^2 + 4LRS}{2Ls + R} = \boxed{2L \frac{s^2 + \frac{R}{L}s}{s + \frac{R}{2L}}}$$

poles: $s = -\frac{R}{2L}$, zeros: $s = 0, -\frac{R}{L}$

b) pole: $s = -\frac{R}{2L} = -15 \text{ krad/s} = -15000 \text{ rad/s}$


$$\frac{R}{L} = 3 \times 10^4 \text{ rad/s}$$

Let $\boxed{L = 0.1 \text{ H}}$, then $\boxed{R = 3 \text{ k}\Omega}$

zeros: $\boxed{s_1 = 0}$, $\boxed{s_2 = -\frac{R}{L} = -30 \text{ krad/s}}$


10.36.

S-domain circuits:

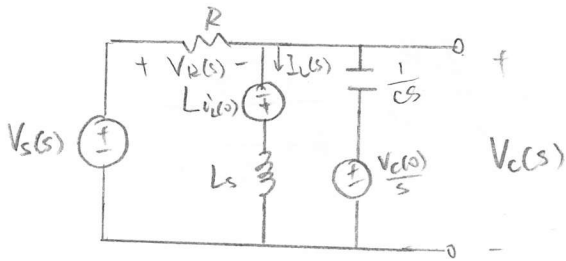


$$V_c(0) = 0, \quad i_L(0) = I_0$$

Zero state (no initial condition):

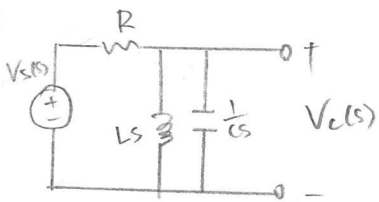

$$\begin{aligned} V_c^{zs}(s) &= V_s(s) \frac{L_s \parallel \frac{1}{cS}}{R + L_s \parallel \frac{1}{cS}} = V_s(s) \frac{\frac{1}{\frac{1}{cS} + cS}}{R + \frac{1}{\frac{1}{cS} + cS}} \\ &= \frac{V_s(s)}{\frac{R}{L} \frac{1}{c} + cRS + 1} = \frac{S V_s(s)}{RCs^2 + S + \frac{R}{L}} = \boxed{\frac{1}{RC} \frac{S}{S^2 + \frac{1}{RC}S + \frac{1}{LC}} V_s(s)} \end{aligned}$$


Zero input (no input $V_s(s)$):

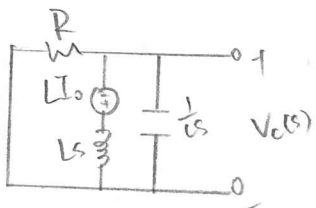

$$\begin{aligned} V_c^{zi}(s) &= (-LI_0) \frac{R \parallel \frac{1}{cS}}{Ls + R \parallel \frac{1}{cS}} = (-LI_0) \frac{\frac{1}{\frac{1}{R} + cS}}{Ls + \frac{1}{\frac{1}{R} + cS}} \\ &= -LI_0 \frac{1}{\frac{L}{R}S + LCs^2 + 1} = \boxed{-\frac{I_0}{C} \frac{1}{S^2 + \frac{1}{RC}S + \frac{1}{LC}}} \end{aligned}$$

10.47.

S-domain circuit (no initial energy)

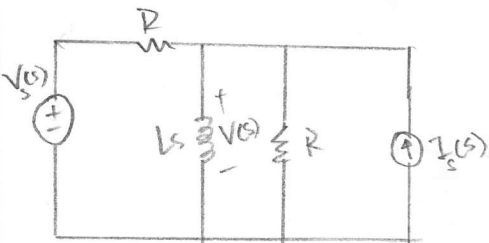


$$V_c(s) = \mathcal{L}\{V_A \sin \beta t\} = \frac{V_A \beta}{s^2 + \beta^2}$$

$$I_c(s) = \mathcal{L}\{I_B \cos t\} = \frac{I_B}{s}$$

Superposition :

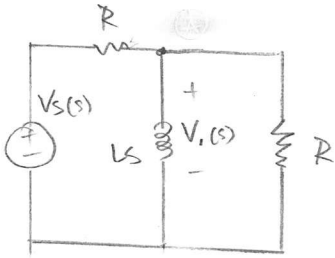① Zero out $I_s(s)$, analyze effect from $V_s(s)$ on $V_1(s)$




Voltage division

$$V_1(s) = V_s(s) \cdot \frac{L_s \parallel R}{R + L_s \parallel R} = \frac{V_A \beta}{s^2 + \beta^2} \cdot \frac{1}{R + \frac{1}{L_s + \frac{1}{R}}}$$

$$= \frac{V_A \beta}{s^2 + \beta^2} \cdot \frac{\frac{1}{s}}{\frac{R}{sL} + s}$$

② Zero out $V_s(s)$ analyze effect from $I_s(s)$ on $V_2(s)$

Current division

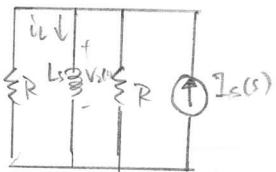

$$i_L(s) = \frac{\frac{1}{L_s}}{\frac{1}{R} + \frac{1}{L_s} + \frac{1}{R}} \cdot I_s(s) = \frac{R}{2Ls + R} \cdot \frac{I_s}{s}$$

$$V_2(s) = L_s \cdot i_L(s) = \frac{L_s R I_s}{2Ls + R} = \frac{\frac{R I_s}{s}}{s + \frac{R}{2L}}$$

$$V_s(s) = V_1(s) + V_2(s) = \frac{V_A \beta}{s^2 + \beta^2} \cdot \frac{\frac{1}{s}}{\frac{R}{sL} + s} + \frac{\frac{R I_s}{s}}{s + \frac{R}{2L}} = \frac{1}{s + \frac{R}{2L}} \left(V_A \beta \frac{s/2}{s^2 + \beta^2} + \frac{R I_s}{s} \right)$$

$$= \frac{\frac{R I_s s}{2s} + \frac{V_A \beta s}{2} + \frac{R I_s \beta^2}{2}}{(s + \frac{R}{2L})(s^2 + \beta^2)}$$


natural pole: $-\frac{R}{2L}$, forced pole: $\pm \beta j$

10.5 |

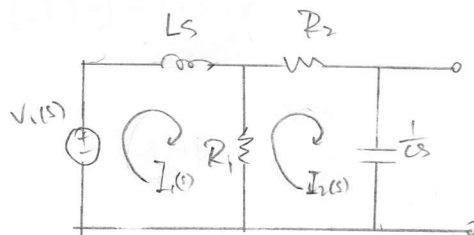a) S-domain w/ no initial condition

KVL at $\mathcal{P}_{i_1(s)}$

$$-V_1(s) + i_1 \cdot L_s + R_1(i_1 - i_2) = 0 \quad \text{①}$$



KVL at $\mathcal{P}_{i_2(s)}$

$$R_2 i_2 + \frac{1}{cs} i_2 + R_1(i_2 - i_1) = 0 \quad \text{②}$$

b) from ① $\rightarrow i_1(s) = \frac{V_1(s) + R_1 i_2(s)}{L_s + R_1}$ plug into ②

$$(R_2 + \frac{1}{cs} + R_1) i_2 = \frac{R_1}{L_s + R_1} V_1(s) + \frac{R_1^2}{L_s + R_1} i_2(s)$$

$$I_2(s) = \frac{R_1}{(Ls+R_1)(R_2+R_1+\frac{1}{Cs})-R_1^2} V_1(s)$$

$$= \frac{R_1}{LR_2s+LA_1s+\frac{L}{C}+R_1R_2+\frac{R_1}{Cs}} = \frac{R_1 Cs V_1(s)}{LC(A+B)s^2+(R_1R_2+L)s+R_1}$$

c) pole: $s = \frac{-(R_1R_2+L) \pm \sqrt{(R_1R_2+L)^2 - 4LCR_1(A+B)}}{2LC(A+B)}$

Zero: $s = 0$


d) $V_1(s) = \mathcal{L}\{v_1(t)\} = \frac{20}{s}$

$$I_2(s) = \frac{10^{-3}s}{1.5 \times 10^{-3}s^2 + 2s + 2 \times 10^3} \cdot \frac{20}{s} = \frac{13.33}{s^2 + 1.33 \times 10^3s + 1.33 \times 10^6} = \frac{13.33}{(s^2 + 666.66)^2 + 941.03^2}$$

$$I_2(t) = \mathcal{L}^{-1}\{I_2(s)\} = \boxed{0.014 e^{-666.66t} \sin(941.03t) \text{ u(t)}}$$

10.56

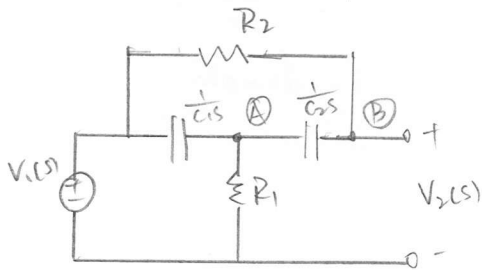a) s domain circuits w/ no initial energy



KCL at A:

$$\boxed{\frac{V_A - V_1}{\frac{1}{Cs}} + \frac{V_A - V_B}{\frac{1}{Cs}} + \frac{V_A}{R_1} = 0} \quad (1)$$

KCL at B:

$$\boxed{\frac{V_B - V_1}{R_2} + \frac{V_B - V_A}{\frac{1}{Cs}} = 0} \quad (2) \quad V_2(s) = V_B(s)$$

b) from ②. $V_A(s) = \frac{1}{C_2 s} \left(\frac{V_B - V_1}{R_2} + \frac{V_B}{C_2 s} \right)$ and plug into ①


$$\frac{1}{C_2 s} \left(\left(\frac{1}{R_2} + C_2 s \right) V_2 - \frac{1}{R_2} V_1 \right) \left(C_1 s + C_2 s + \frac{1}{R_1} \right) = C_1 s V_1 + C_2 s V_2$$

$$\left[\frac{\left(\frac{1}{R_2} + C_2 s \right) \left(C_1 s + C_2 s + \frac{1}{R_1} \right)}{C_2 s} - C_2 s \right] V_2 = \left[C_1 s + \frac{C_1 s + C_2 s + \frac{1}{R_1}}{R_1 C_2 s} \right] V_1$$

$$\boxed{\frac{V_2(s)}{V_1(s)} = \frac{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_1 C_2) s + 1}{R_1 C_1 R_2 C_2 s^2 + (R_1 C_1 + R_1 R_2 + R_2 C_2) s + 1}}$$

10.70


Initial condition as $t \rightarrow 0^-$

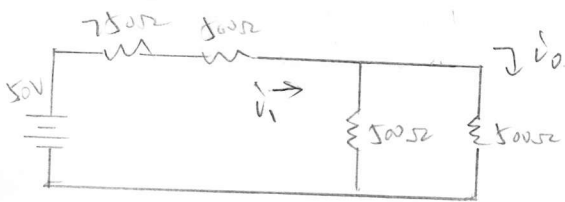

$$i_1(0^-) = \frac{50 \text{ V}}{750\Omega + 500\Omega + (500\Omega \parallel 500\Omega)} = \frac{50 \text{ V}}{1500\Omega} = \frac{1}{30} \text{ A} = 0.0333 \text{ A}$$

$$i_0(0^-) = \frac{1}{2} i_1 = 0.0167 \text{ A} = \frac{1}{60} \text{ A}$$

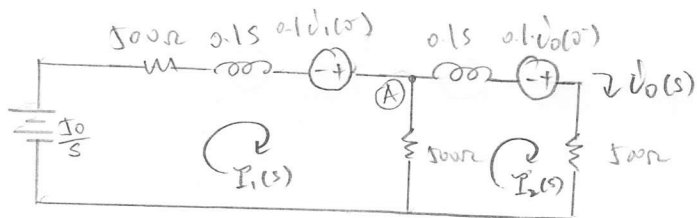Then, close the switch and transform into s-domain



Mesh Current:

$$\text{KVL } i_1: -\frac{50}{s} + (500 + 0.1s) I_1(s) - 0.1 i_0(0^-) + 500 (I_1 - I_2) = 0$$

$$\text{KVL } i_2: (0.1s + 500) I_2 - 0.1 i_0(0^-) + 500 (I_2 - I_1) = 0 \quad \sim (I_2(s) = i_0(s))$$

Solve for I_2 :


$$i_0(s) = I_2(s) = \frac{\frac{1}{60s} + \frac{\frac{50}{300} + \frac{25000}{s}}{(0.1s + 1000)^2}}{1 - \frac{500^2}{(0.1s + 1000)^2}} = \frac{s^2 + 20000s + 25000 \times 6000}{6000s \left(\frac{1}{100} s^2 + 200s + 10^6 - 500^2 \right)}$$

$$V_0(s) = \frac{-\frac{1}{40}}{s+5000} + \frac{1}{30} + \frac{1/120}{s+15000}$$

$$v_0(t) = \mathcal{L}^{-1}\{V_0(s)\} = \left(-\frac{1}{40}e^{-5000t} + \frac{1}{30} + \frac{1}{120}e^{-15000t}\right) u(t)$$

10.79

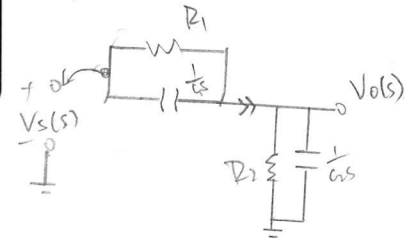a) Assume zero initial condition, s-domain circuits



Voltage division

$$V_0(s) = \frac{R_2 \parallel \frac{1}{C_2}}{(R_1 \parallel \frac{1}{C_1}) + (R_2 \parallel \frac{1}{C_2})} V_s(s)$$

$$V_0(s) = \frac{R_1 R_2 C_1 s + R_2}{R_1 R_2 (C_1 + C_2) s + R_1 + R_2} V_s(s)$$

b) let $\frac{V_0}{V_s} = \frac{1}{s}$, then, w/ $R_2 = 10 \text{ M}\Omega$, $C_2 = 5 \text{ pF}$

$$\partial R_1 R_2 C_1 s + \partial R_2 = R_1 R_2 (C_1 + C_2) s + (R_1 + R_2)$$

$$\Rightarrow \left. \begin{array}{l} \partial R_1 R_2 C_1 = R_1 R_2 (C_1 + C_2) \\ R_1 + R_2 = \partial R_2 \end{array} \right\} \Rightarrow \left. \begin{array}{l} R_1 = 10 \text{ M}\Omega \\ C_1 = 5 \text{ pF} \end{array} \right\}$$

10.83

The first op-Amp is a buffer to protect the source and the second op-Amp act as inverting, thus, ① when $\alpha \in \mathbb{R}$

$$\frac{V_0(s)}{V_s(s)} = -\frac{R_2}{R_1 \parallel \frac{1}{C_1}} = -\frac{R_2}{\frac{1}{\frac{1}{R_1} + C_1 s}} = -C_1 R_2 \left(\frac{1}{R_1} + s\right) \Rightarrow V_0(s) = -\left(s + \frac{1}{R_1 C_1}\right) \cdot C_1 R_2 \frac{K}{(s + \alpha)}$$

the pole $s = -\frac{1}{R_1 C_1}$ got cancelled and then, $V_0(s) = -C_1 R_2 K = -\frac{1}{\alpha R_1} R_2 K = -\frac{K}{\alpha} \frac{R_2}{R_1}$

$\frac{R_2}{R_1}$ could be used to adjust gain \therefore claim is correct when α is real

② when $x \in \mathbb{C}$.

There are no combination of $P, C \in \mathbb{R}$ such that $\frac{1}{P \cdot C} \in \mathbb{C}$

\therefore claim is not correct $\forall x \in \mathbb{C}$

③ $x = 0$.

$\frac{1}{P \cdot C} = 0$ either $P \rightarrow \infty$, or $C \rightarrow \infty$ would do.