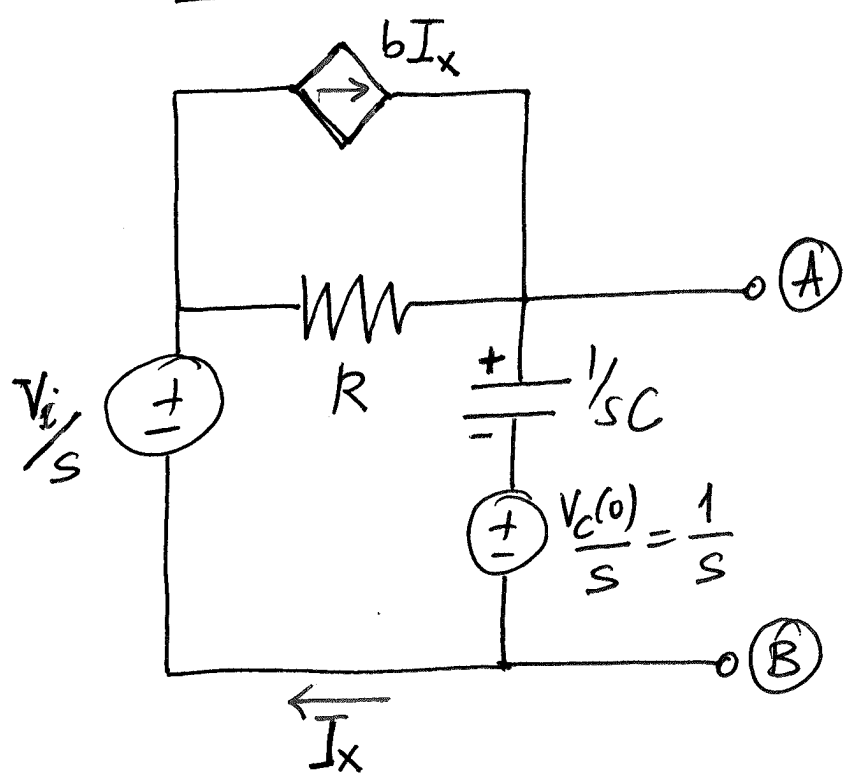



### 1. Part I



[+1 point for correct initial condition]  
 [+1 point for correct overall circuit]
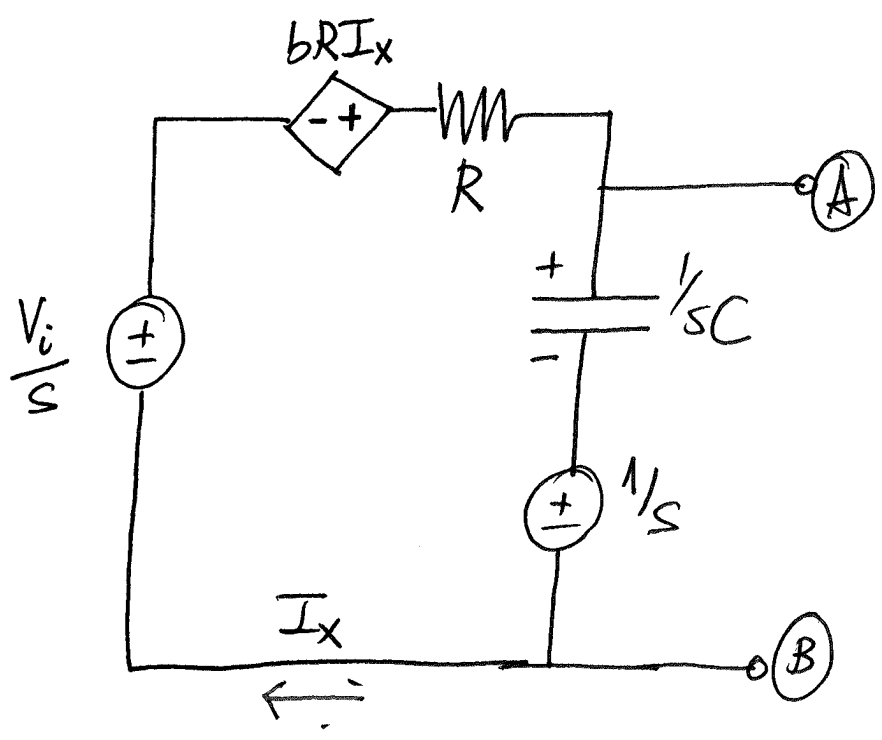
### Part II

We transform the current source in parallel w/ the resistor to obtain



We use voltage division to get the voltage drop across the impedance  $\frac{1}{sC}$

$$V_{\frac{1}{sC}} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R} \cdot \left( \frac{V_i}{s} + bRI_x - \frac{1}{s} \right)$$

Additionally,

$$I_x = \frac{1}{\frac{1}{sC} + R} \cdot \left( \frac{V_i}{s} + bRI_x - \frac{1}{s} \right) =$$

$$\text{Therefore,} \quad = \frac{Cs}{1+RCs} (V_i - 1 + bRI_x s) \quad [+1 \text{ point}]$$

$$I_x \left( 1 - \frac{C}{1+RCs} bRs \right) = \frac{C}{1+RCs} (V_i - 1)$$

$$\frac{1+RCs - bRCs}{1+RCs} = \frac{1+(1-b)RCs}{1+RCs}$$

$$I_x = \frac{C}{1+(1-b)RCs} (V_i - 1) \quad [+1 \text{ point}]$$

Therefore,

$$V_{1/CS} = \frac{1}{1+RCs} \left( \frac{1}{s}(V_i-1) + \frac{bRC}{1+(1-b)RCs} (V_i-1) \right)$$

$$= \frac{1}{1+RCs} \frac{(V_i-1)}{s} \left( 1 + \frac{bRC}{\frac{1+(1-b)RC}{s}} \right)$$

$$= \frac{1}{1+RCs} \frac{V_i-1}{s} \left( \frac{1}{s} + (1-b)RC + bRC \right) \frac{1}{1+(1-b)RCs}$$

$$= \frac{1}{1+RCs} (V_i-1) \frac{1}{1+(1-b)RCs} \left( \frac{1}{s} + RCs \right)$$

$$= \frac{1}{1+(1-b)RCs} \frac{1}{s} (V_i-1) \quad [+1 \text{ point}]$$

Finally,


$$V_{AB} = V_{1/SC} + \frac{1}{s} = \frac{V_i + (1-b)RCs}{s(1+(1-b)RCs)}$$

[+1 point]

Part III

Because we have dependent sources, we cannot turn off sources // use the hollback method. [+1 point]

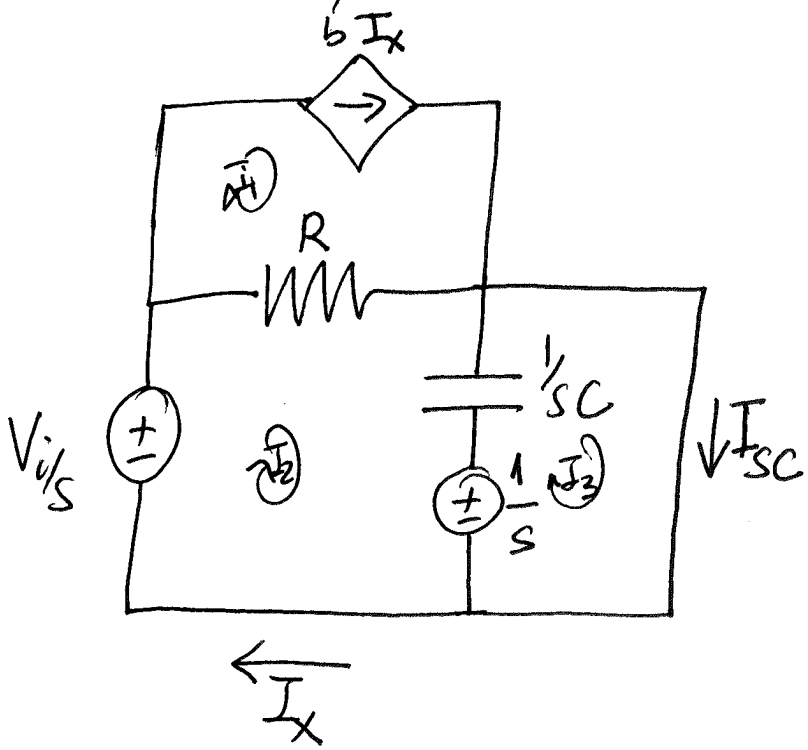Instead, we short-circuit the circuit and find  $i_{sc}$ .



[+1 point]

We use mesh current analysis;

method 2:  $I_1(s) = bI_x(s)$

$$\begin{aligned}
 \text{KVL @ mesh 2: } & R(I_2(s) - I_1(s)) + \frac{1}{sC} (I_2(s) - I_3(s)) \\
 & + \frac{1}{s} - \frac{V_i}{s} = 0
 \end{aligned}$$

$$\text{KVL @ mesh 3: } \frac{1}{sC} (I_3(s) - I_2(s)) - \frac{1}{s} = 0$$

Additionally,  $I_2(s) = I_x(s)$  &  $I_{sc}(s) = I_3(s)$

Solving for  $I_1(s)$ ,  $I_2(s)$ ,  $I_3(s)$ ,  $I_X(s)$ , we obtain

$$I_{sc}(s) = I_3(s) = \frac{CRs(1-b) + V_i}{(1-b)Rs} \quad [+1 \text{ point}]$$

Therefore


$$Z_T = \frac{V_{OT}(s)}{I_{sc}(s)} = \frac{\cancel{V_i + (1-b)RCs}}{s(1+(1-b)RCs)} \cdot \frac{(1-b)Rs}{\cancel{(1-b)RCs + V_i}}$$

$$= \frac{(1-b)Rs}{s(1+(1-b)RCs)} \quad [+1 \text{ point}]$$

We also know


$$V_T = V_{AB} \text{ from Part II}$$

Hence

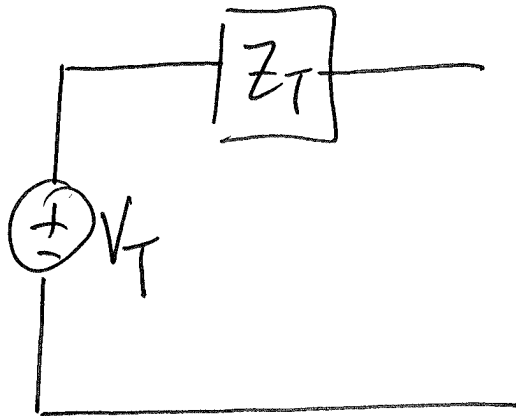
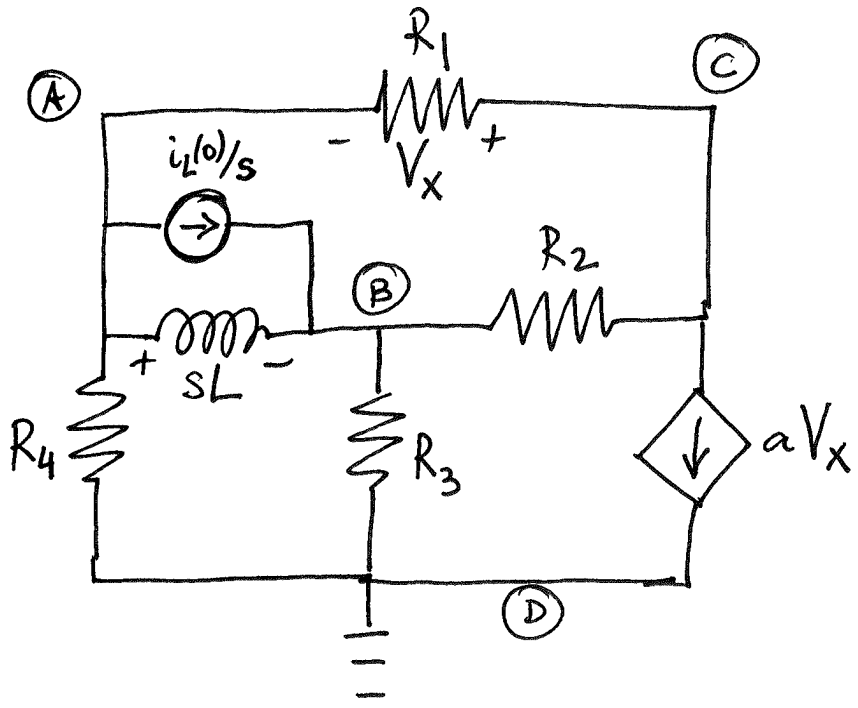
## 2. Part I

Since we cannot assume zero initial conditions, we need to worry about the initial condition of the inductor. Since we are gonna use nodal analysis, we employ a current source to take care of it. The circuit in the s-domain looks like



[+1 point]  
 (1/2 correct drawing,  
 1/2 correct initial condition)

Node (D) is ground, so we don't write KCL for it.

KCL @ (A)

$$G_1(V_A - V_C) + G_4(V_A) + \frac{1}{sL}(V_A - V_B) = -\frac{i_L(0)}{s} \quad [+1 \text{ point}]$$

KCL @ (B)

$$\frac{1}{sL}(V_B - V_A) + G_3 V_B + G_2(V_B - V_C) = \frac{i_L(0)}{s} \quad [+1 \text{ point}]$$

KCL @ (C)

$$G_1(V_C - V_A) + G_2(V_C - V_B) = -a V_X \quad \left(G_i = \frac{1}{R_i}\right) \quad [+1 \text{ point}]$$

We need to properly account for the dependent source.

Therefore


$$V_x = V_C - V_A \quad [+1 \text{ point}]$$

So we have 4 eqs in 4 unknowns ( $V_A(s), V_B(s), V_C(s), V_x(s)$ ).

### Part II

As in Part I, we need to worry about the initial condition of the inductor, and we use now a voltage source for it (since we are gonna employ mesh current analysis).

The circuit in the s-domain looks like

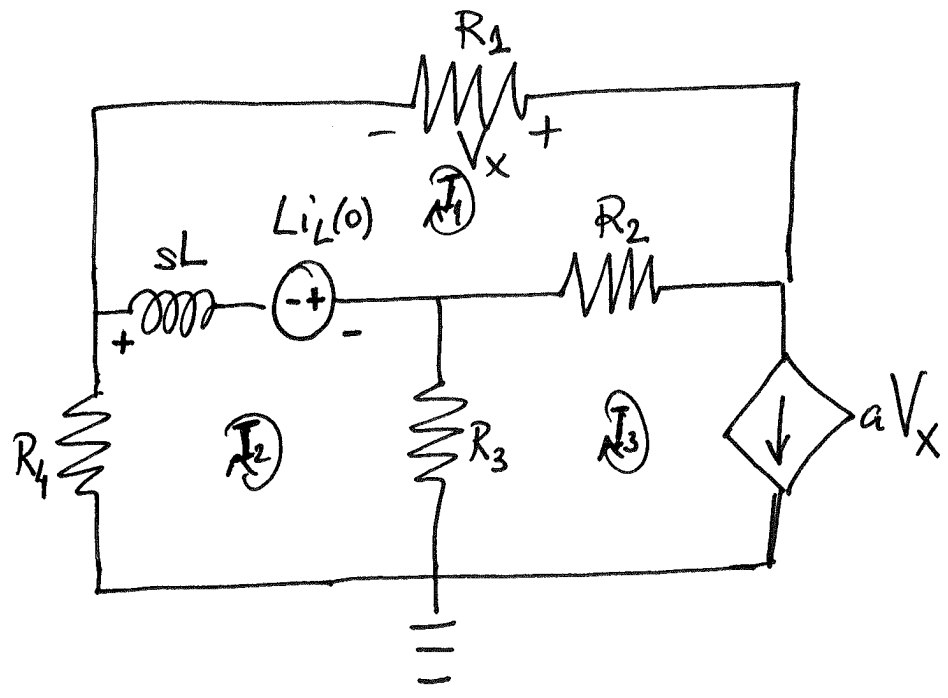

[+1 point]  
(1/2 correct drawing,  
1/2 correct initial condition)

We have a current source, which is a problem for mesh analysis. Fortunately, it just belongs to 1 mesh, so we employ method 2 to state

$$I_3(s) = aV_x(s) \quad [+1 \text{ point}]$$

Next, we write KVL eqs for meshes 1 & 2.

KVL @ mesh 1,

$$R_1 I_1 + R_2 (I_1 - I_3) + sL (I_1 - I_2) = -L i_L(0) \quad [+1 \text{ point}]$$

KVL @ mesh 2,

$$sL (I_2 - I_1) + R_3 (I_2 - I_3) + R_4 I_2 = L i_L(0) \quad [+1 \text{ point}]$$

Finally, we need to account for the dependent source,

$$V_x(s) = -R_1 I_1(s) \quad [+1 \text{ point}]$$

This gives us a total of 4 eqs in 4 unknowns  $(I_1(s), I_2(s), I_3(s), V_x(s))$ .

### Part III

With unknowns of Part I, we have

$$V_L(s) = V_A(s) - V_B(s) \quad [+1 \text{ bonus point}]$$


With unknowns of Part II, we have

$$V_L(s) = sL (I_2(s) - I_1(s)) - L i_L(0) \quad [+1 \text{ bonus point}]$$



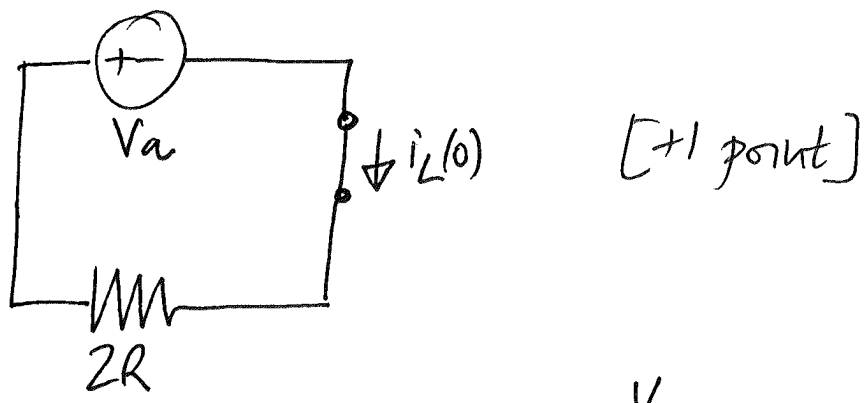3. Part I

Under DC excitation, the inductor behaves as a short circuit, hence




[+1 point]

By Ohm's law,  $i_L(0) = -\frac{V_a}{2R}$ . [+1 point]

Part II

Switch is at (B), hence

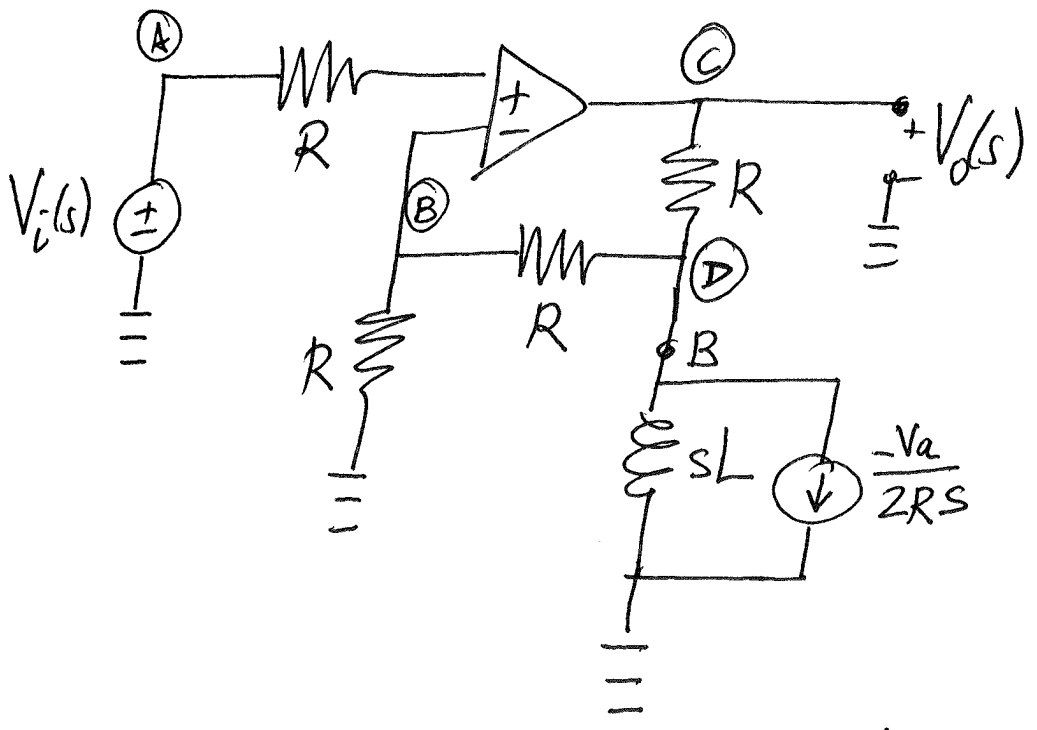

[+1 point]

As instructed, we use nodal analysis.

Method 2 tells us that  $V_A = V_i(s)$ . [+0.5 point]

Also, (C) is the output node for an op-amp, so we don't write KCL for it.

KCL @ (B)

$$G V_B + G (V_B - V_D) = 0$$

[+0.5 point]

KCL @ (D)

$$G (V_D - V_C) + G (V_D - V_B) + \frac{1}{sL} (V_D - 0) = \frac{V_a}{2R_s}$$

[+0.5 point]

Because of ideal op-amp,

$$V_A(s) = V_B(s)$$

[+0.5 point]

Solving for  $V_A, V_B, V_C, V_D$ , we obtain

$$V_o(s) = V_C(s) = + \frac{-L V_a + 4R V_i(s) + 6Ls V_i(s)}{2Ls}$$

$$= \frac{2R + 3Ls}{Ls} V_i(s) - \frac{V_a}{2s}$$

[+1 point]

Part III

With the values given, we have  $V_i(s) = \frac{1}{s+10}$

and then

$$V_o(s) = \frac{20 + 0.3s}{0.1s} - \frac{1}{s+10} - \frac{1}{2s} =$$

$$= \frac{200 + 3s}{s(s+10)} - \frac{1}{2s}$$

Using partial fractions

$$V_o(s) = \frac{A}{s} + \frac{B}{s+10} \quad [+1 \text{ point}]$$

After some computations,

$$A = 19.5$$

$$B = -17$$

[+1 point]

Using the inverse Laplace transform,

$$V_o(t) = (19.5 - 17e^{-10t})u(t)$$

Part IV

(i) forced pole is at  $s = -10$ . Hence

$$v_o(t) = \underbrace{19.5 u(t)}_{\text{natural}} - \underbrace{17 e^{-10t} u(t)}_{\text{forced}} \quad [+1 \text{ point}]$$

(ii) zero-state,

$$V_{zs}(s) = \frac{200 + 3s}{s(s+10)} \quad ; \quad v_{zs}(t) = 20 u(t) - 17 e^{-10t} u(t) \quad [+0.5 \text{ point}]$$


zero-input

$$V_{zi}(s) = -\frac{1}{2s}$$

$$; \quad v_{zi}(t) = -0.5 u(t) \quad [+0.5 \text{ point}]$$

#### 4. - Part I

(13)

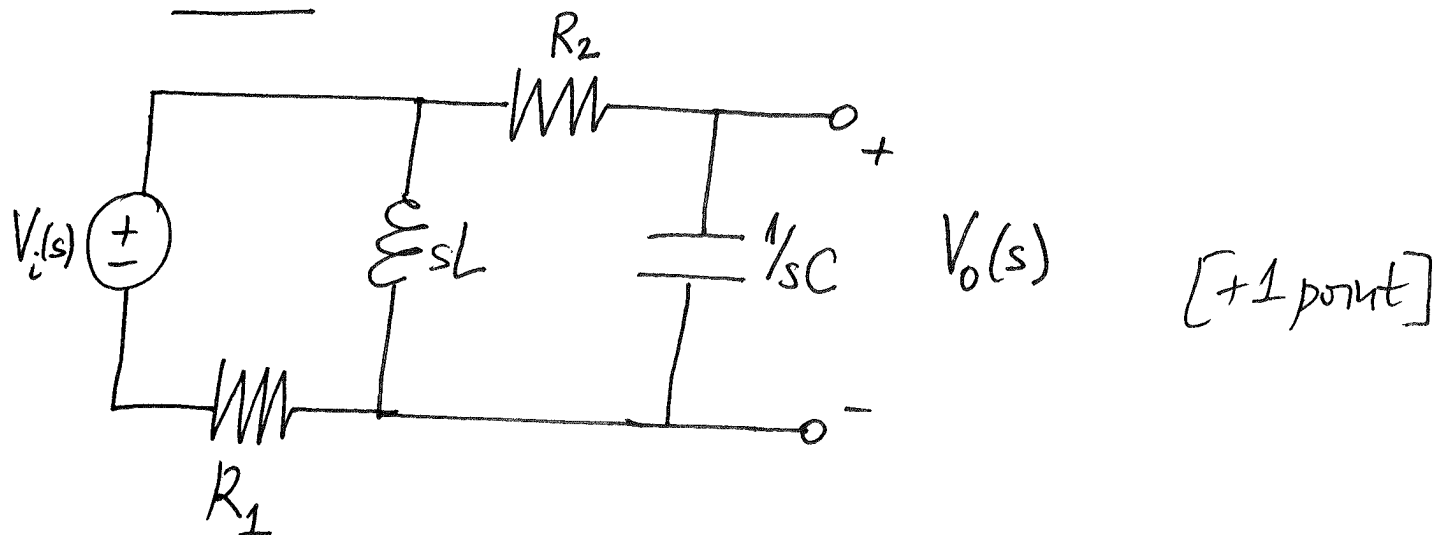

(zero initial conditions means we do not need to add sources for the capacitor or the inductor)

#### Part II

To show this, we can use a number of techniques (source transformation, nodal analysis, ...). We settle for mesh analysis, labelling meshes as 1 & 2 from left to right.

$$sL(I_1(s) - I_2(s)) + R_1 I_1(s) = V_i(s) \quad [+1 \text{ point}]$$

$$\frac{1}{sC} I_2(s) + R_2 I_2(s) + sL(I_2(s) - I_1(s)) = 0 \quad [+1 \text{ point}]$$

We solve for  $I_1(s)$  in the second equation,

$$(sL) I_1(s) = \left( R_2 + sL + \frac{1}{sC} \right) I_2(s)$$

$$I_1(s) = \frac{R_2 + sL + \frac{1}{sC}}{sL} I_2(s)$$

Substituting into the first equation,

$$-sL I_2(s) + (R_1 + sL) \frac{R_2 + sL + \frac{1}{sC}}{sL} I_2(s) = V_i(s)$$

$$I_2(s) = \frac{sL}{-s^2L^2 + (R_1 + sL) \left( R_2 + sL + \frac{1}{sC} \right)} V_i(s)$$

Therefore,

$$V_o(s) = \frac{1}{sC} I_2(s) = \frac{L/C}{-s^2L^2 + (R_1 + sL) \left( R_2 + sL + \frac{1}{sC} \right)} V_i(s) =$$

[+1 point]

$$= \frac{L \cdot sC}{R_1 R_2 C s + R_1 L C s^2 + R_1 + R_2 L C s^2 + L s} V_i(s) =$$

$$= \frac{sL}{(R_1 + R_2) L C s^2 + (R_1 R_2 C + L) s + R_1} V_i(s) \neq$$

Part III

With the values given, the transfer function takes the form

$$T(s) = \frac{0.1s}{123.85 + 0.866941s + 0.0012385s^2} \approx$$

$$\approx \frac{80.75s}{s^2 + 700s + 10^5} = \frac{80.75s}{(s+200)(s+500)}$$

Then,

$$T(j\omega) = \frac{80.75j\omega}{-\omega^2 + 700j\omega + 10^5} = \frac{80.75\omega \cdot j}{(10^5 - \omega^2) + 700\omega j}$$

The gain function is

$$|T(j\omega)| = \frac{80.75\omega}{\sqrt{(10^5 - \omega^2)^2 + 700^2\omega^2}} \quad [+0.5 \text{ point}]$$

The phase function is

$$\angle T(j\omega) = \frac{\pi}{2} - \arctan \frac{700\omega}{10^5 - \omega^2} \quad [+0.5 \text{ point}]$$

The DC gain is

$$|T(j0)| = 0 \quad [+0.5 \text{ point}]$$


The  $\infty$ -freq gain is

$$|T(j\infty)| = 0 \quad [+0.5 \text{ point}]$$

The corresponding values of the phase function are

$$\angle T(j0) = \frac{\pi}{2} \text{ rad} \quad [+0.5 \text{ point}]$$
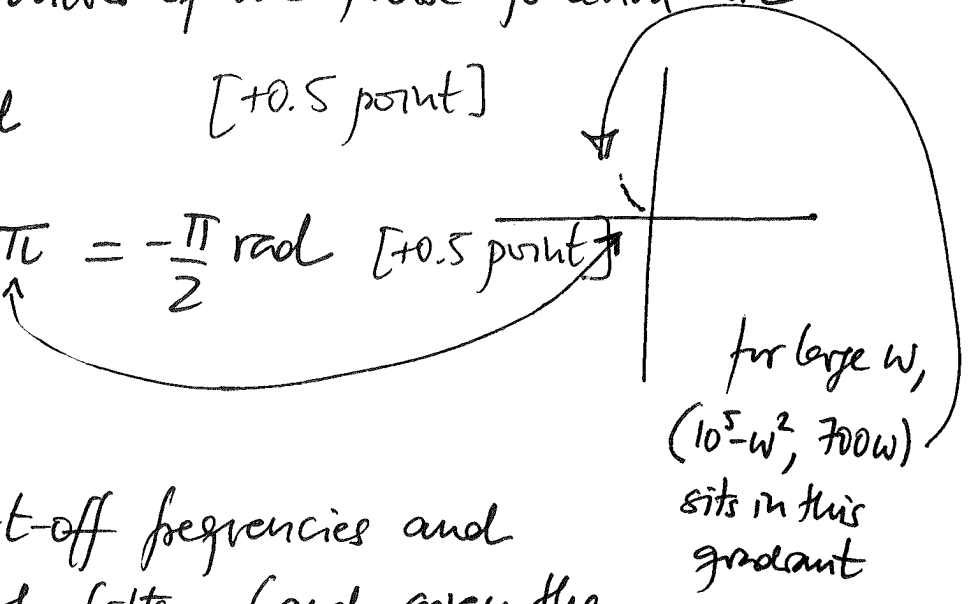
$$\angle T(j\infty) = \frac{\pi}{2} - \pi = -\frac{\pi}{2} \text{ rad} \quad [+0.5 \text{ point}]$$



To figure out the cut-off frequencies and determine the type of filter (and given the DC and  $\infty$ -freq gains found above, which makes us think about a bandpass filter), we observe that

$$T(s) = \frac{80.75s}{s+200} \cdot \frac{1}{s+500}$$



high-pass filter
low-pass filter

Cutoff freqs. are  $\omega_1 = 200 \text{ rad/s}$  and  $\omega_2 = 500 \text{ rad/s}$

$$(k_1 = 80.75 ; k_2 = 1) \quad [+1 \text{ point}]$$



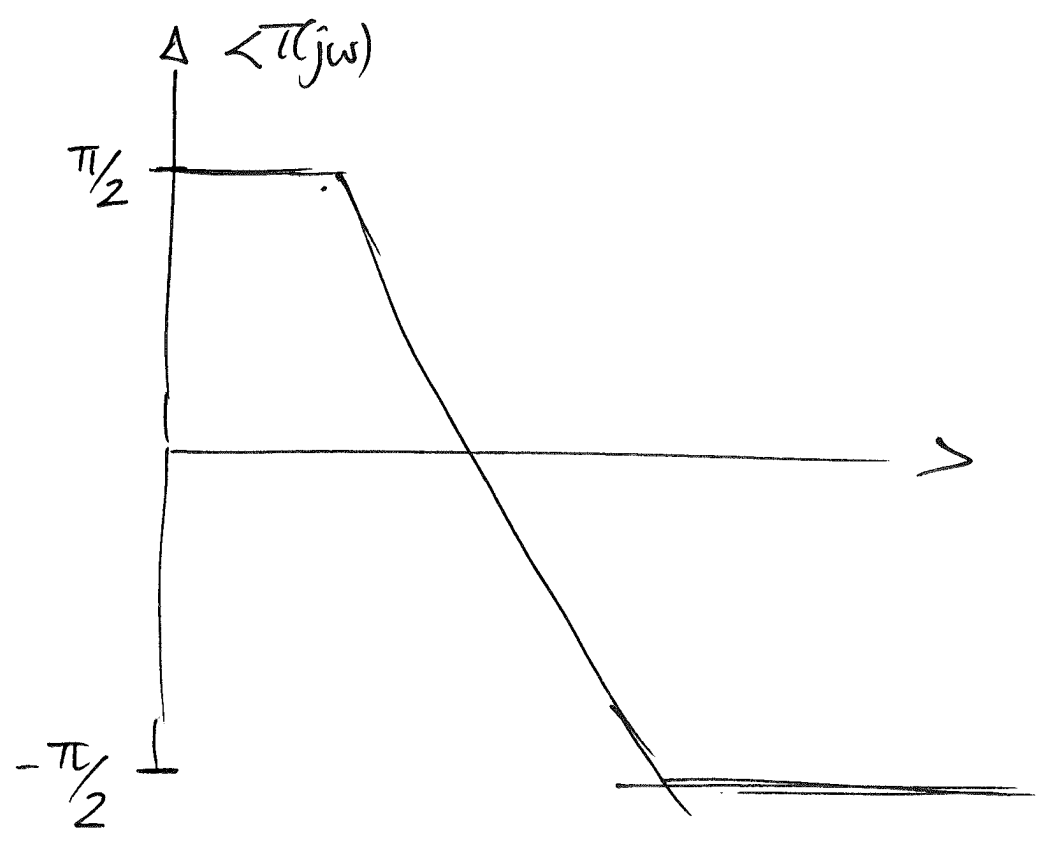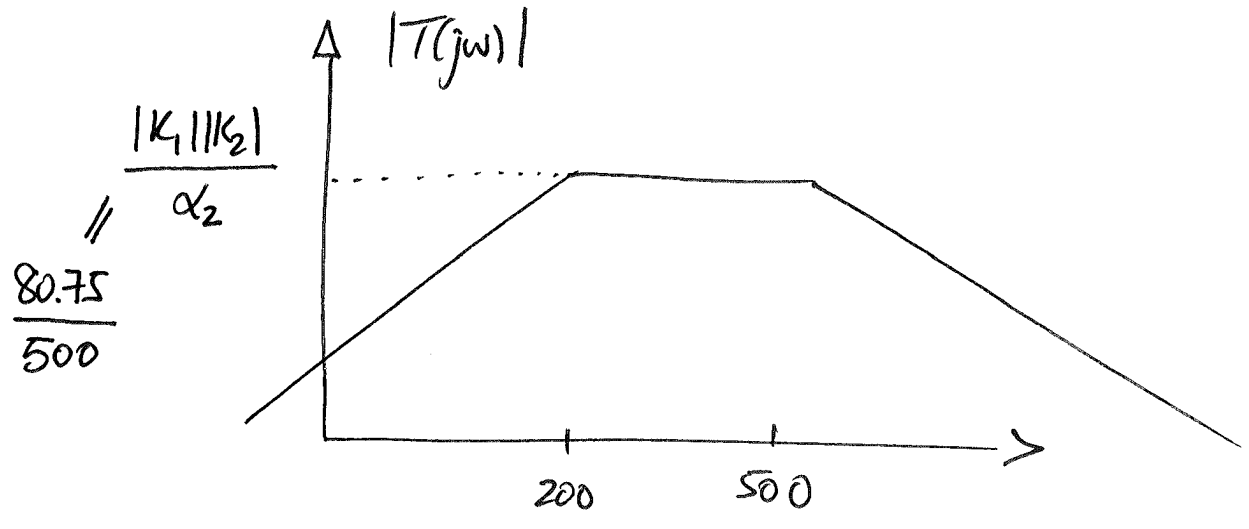
Here is a sketch, based on what we've learned in class



[+1 point]

This is a bandpass filter.

Bode Diagram

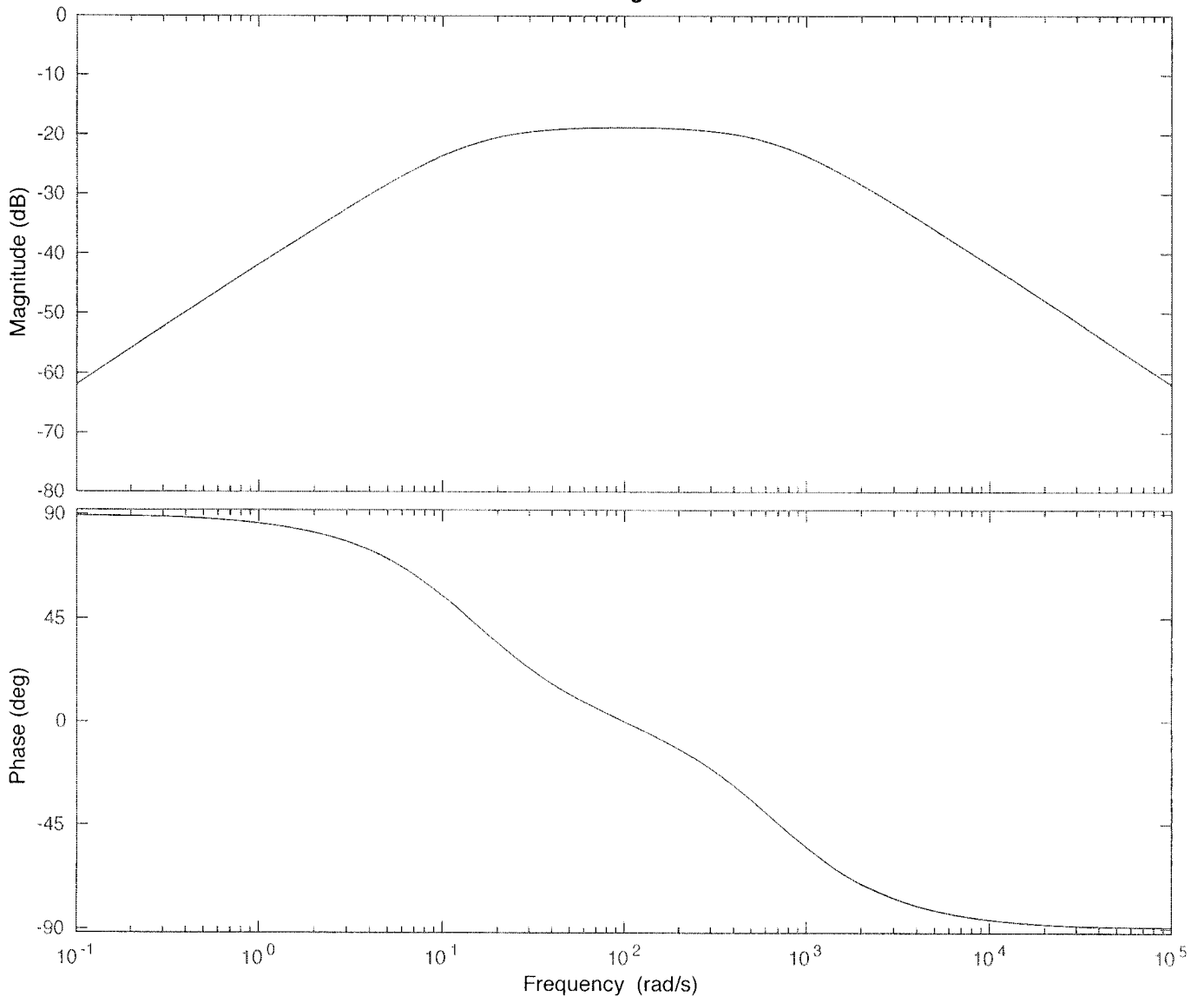

## Part IV

We know that

$$V_o^{ss}(t) = |T(j300)| \cdot \cos\left(300t + \frac{\pi}{4} + \angle T(j300)\right) \quad [+0.5 \text{ point}]$$

Since

$$|T(j300)| = 0.115277$$

$$\angle T(j300) = 0.04758 \text{ rad} \quad [+0.5 \text{ point}]$$

Therefore,

$$V_o^{ss}(t) = 0.115277 \cos\left(300t + \frac{\pi}{4} + 0.04758\right).$$

## 5.- Part I

(20)

We set

$$\frac{s^2 + 201s + 500}{s^2 + 700s + 10^5} = \frac{k_1 s}{s + \alpha} + \frac{k_2}{s + \beta}$$

Note that  $s^2 + 700s + 10^5 = (s + 200)(s + 500)$  [ +1 point ]

Therefore we set  $\alpha = 500$ ,  $\beta = 200$ , and we have [ +1 point ]

$$\frac{k_1 s}{s + 500} + \frac{k_2}{s + 200} = \frac{k_1 s^2 + 200k_1 s + k_2 s + 500k_2}{(s + 500)(s + 200)}$$

Therefore,


$$\left. \begin{array}{l} k_1 = 1 \\ 201 = 200k_1 + k_2 \\ 500 = 500k_2 \end{array} \right\} \Rightarrow \begin{array}{l} k_1 = 1 \\ k_2 = 1 \end{array} \quad [ +1 \text{ point} ]$$

## Part II

There are many possible designs based on the decomposition of Part I.

One could do for instance an inverting summer followed by a gain of  $-1$ .

[ +1 point ]

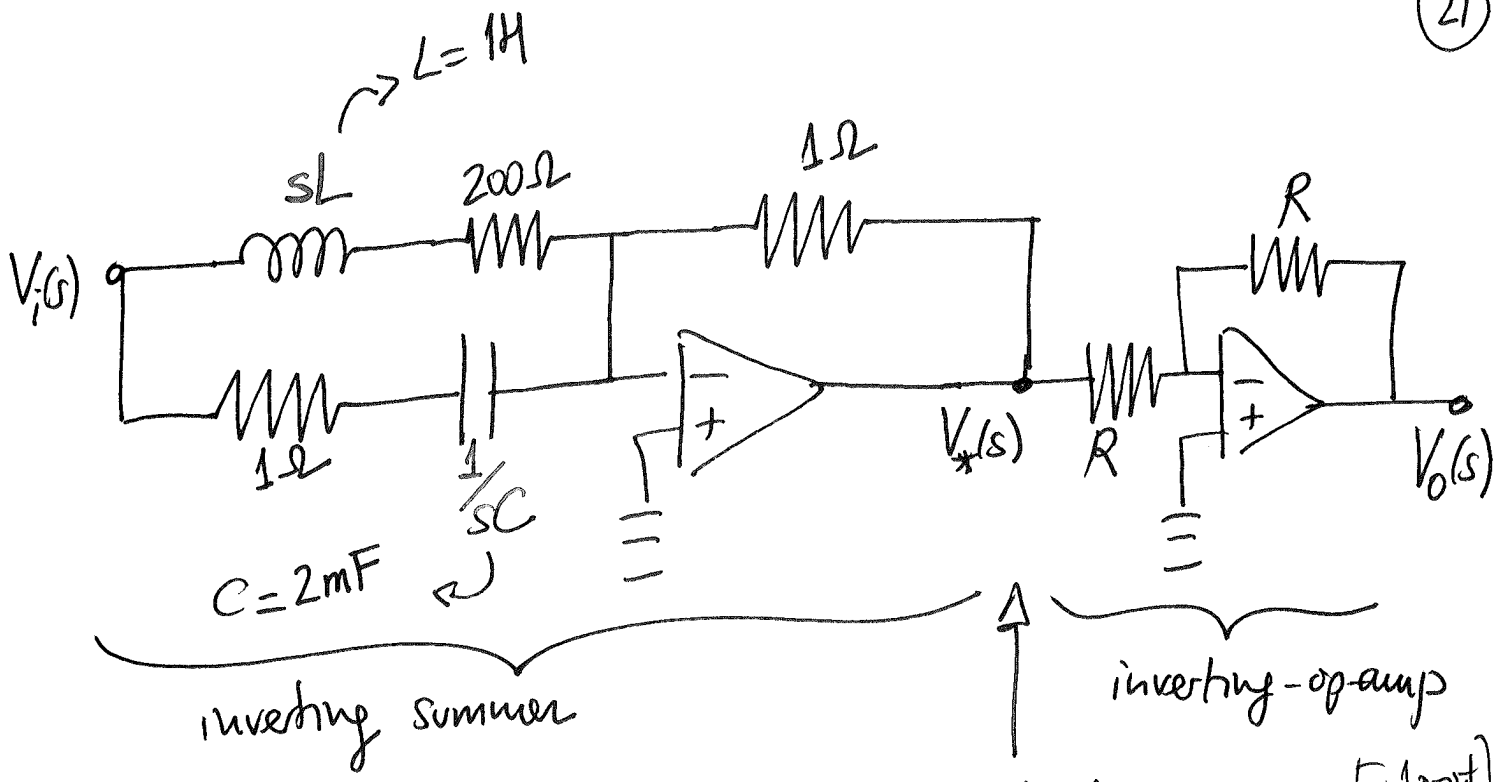

no loading because of 0 output impedance [ +1 point ]

$$\frac{V_*(s)}{V_i(s)} = - \frac{1}{s+200} - \frac{1}{1 + \frac{1}{s \cdot 2 \cdot 10^{-3}}} = - \left( \frac{1}{s+200} + \frac{s}{s + \frac{1}{2 \cdot 10^{-3}}} \right)$$

[ +1 point ]

$$\frac{V_o(s)}{V_*(s)} = -1$$

[ +1 point ]

$$\frac{V_o(s)}{V_i(s)} = - \left( \frac{1}{s+200} + \frac{s}{s+500} \right) \cdot (-1) = \frac{1}{s+200} + \frac{s}{s+500}$$

[ +1 point ]

Part III


From what we have seen in class, we know this is a bandstop filter

$$\frac{s}{s+500} + \frac{1}{s+200}$$

high pass
low-pass

[+2 points]

$200 < 500$

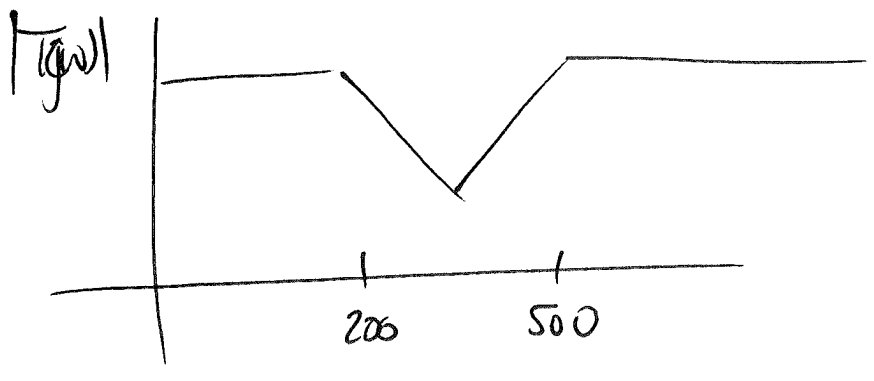

6. - Part I

Both are voltage dividers, so

$$T_1(s) = \frac{sL}{R_1 + sL} \quad [+1 \text{ point}]$$

$$T_2(s) = \frac{1/sC}{1/sC + R_2} = \frac{1}{1 + R_2Cs} \quad [+1 \text{ point}]$$

Part II

$$\tilde{T}(s) = T_1(s) T_2(s) = \frac{sL}{R_1 + sL} \cdot \frac{1}{1 + R_2Cs} = \frac{sL}{R_2CLs^2 + (R_1R_2C + L)s + R_1} \quad [+1 \text{ point}]$$

Part III

In fact,  $T(s)$  &  $\tilde{T}(s)$  are different (the coefficient of the  $s^2$  term in the denominator differs).

The answer in Q4, Part II is the correct one. [+1 point]

The reason is loading. The instructor incorrectly assumed that, when connecting the 2 stages in [+1 point]

Figure 5, the transfer function was the product.


This is only the case if the second stage does

not load the first one. When you put 2 voltage dividers in series, the second one loads the first one, invalidating the instructor's thinking.

[+2 points]

Part IV

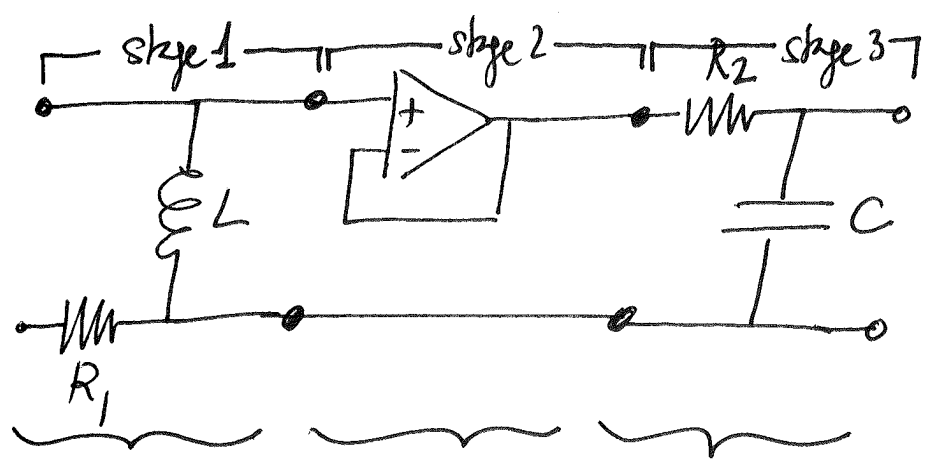We could do it with a voltage follower, like this



[+1 point]

$$T_1(s) \cdot 1 \cdot T_2(s) = \tilde{T}(s)$$

In this circuit, there is no loading, since the voltage follower does not load the voltage divider (because of  $\infty$  input impedance of op-amp) and the second voltage divider does not load the voltage follower (because of 0 output impedance of op-amp).

[+1 point]

The order matters, ~~the~~ meaning that stage 1 & stage 3 can be interchanged stage 2 must be in the middle.

[+1 point]