

MAE40 - Linear Circuits - Winter 20
Final Exam

Instructions

- (i) Prior to the exam, you must have completed the Academic Integrity Pledge at <https://academicintegrity.ucsd.edu/forms/form-pledge.html>
- (ii) The exam is open book. You may use your class notes and textbook.
- (iii) Collaboration is not permitted. The answers you provide should be the result only of your own work
- (iv) On the questions for which the answers are given, please provide detailed derivations
- (v) The exam has 5 questions for a total of 50 points and 5 bonus points

Good luck!

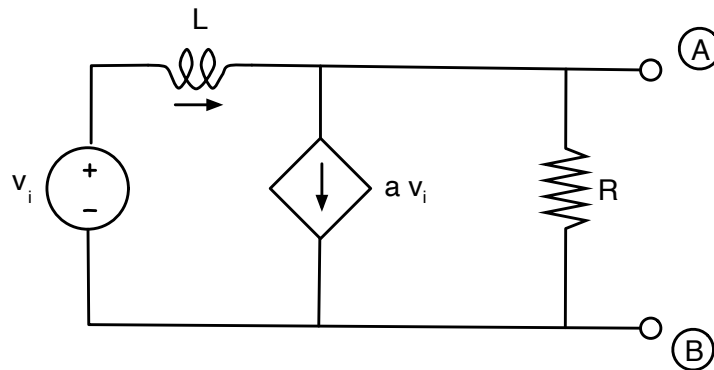


Figure 1: Circuit for Question 1.

1. Equivalent Circuits

Here, v_i is a constant voltage source and a is a positive constant.

Part I: [2 points] Assuming $i_L(0) = 2A$, transform the circuit in Figure 1 into the s -domain, using a voltage source to account for the initial condition of the inductor.

Part II: [3 points] For the circuit you obtained in Part I, find the open-circuit voltage transform as seen from terminals \textcircled{A} - \textcircled{B} . The answer should be given as a ratio of two polynomials.

Part III: [3 points] For the circuit you obtained in Part I, find the short-circuit current transform as seen from terminals \textcircled{A} - \textcircled{B} . The answer should be given as a ratio of two polynomials.

Part IV: [2 points] For the circuit you obtained in Part I, find the Thévenin equivalent in the s -domain as seen from terminals \textcircled{A} - \textcircled{B} (the impedance should be given as a ratio of two polynomials).

Part V: [Extra 2 points] Break down the open-circuit voltage transform you obtained in Part II as the sum of the zero-state and zero-input response transforms. Do the same as the sum of the forced and natural response transforms.

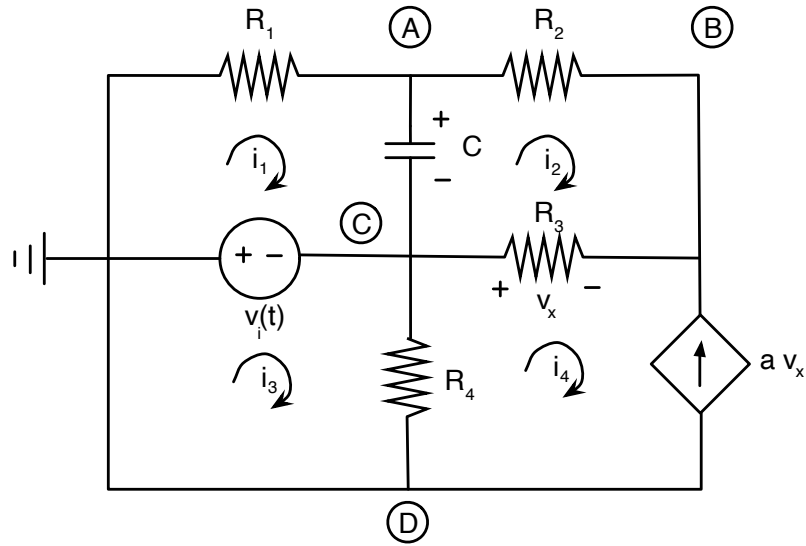


Figure 2: Nodal and Mesh Analysis Circuit for Question 2. a is a positive constant.

2. Nodal and Mesh Analysis on the s -domain

- Part I:** [5 points] Convert the circuit in Figure 2 to the s -domain and formulate its node-voltage equations. Use the reference node and other labels as shown in the figure. *Do not assume zero initial conditions.* Make sure your final answer has the *same* number of independent equations as unknown variables (notice the presence of the dependent source). No need to solve any equations!
- Part II:** [5 points] Convert the circuit in Figure 2 to the s -domain and formulate its mesh-current equations. Use the mesh currents shown in the figure. *Do not assume zero initial conditions.* Make sure your final answer has the *same* number of independent equations as unknown variables (notice the presence of the dependent source). No need to solve any equations!
- Part III:** [Extra 2 points] Express the capacitor's voltage transform $V_C(s)$ in terms of the node voltages. Do the same in terms of the mesh currents.

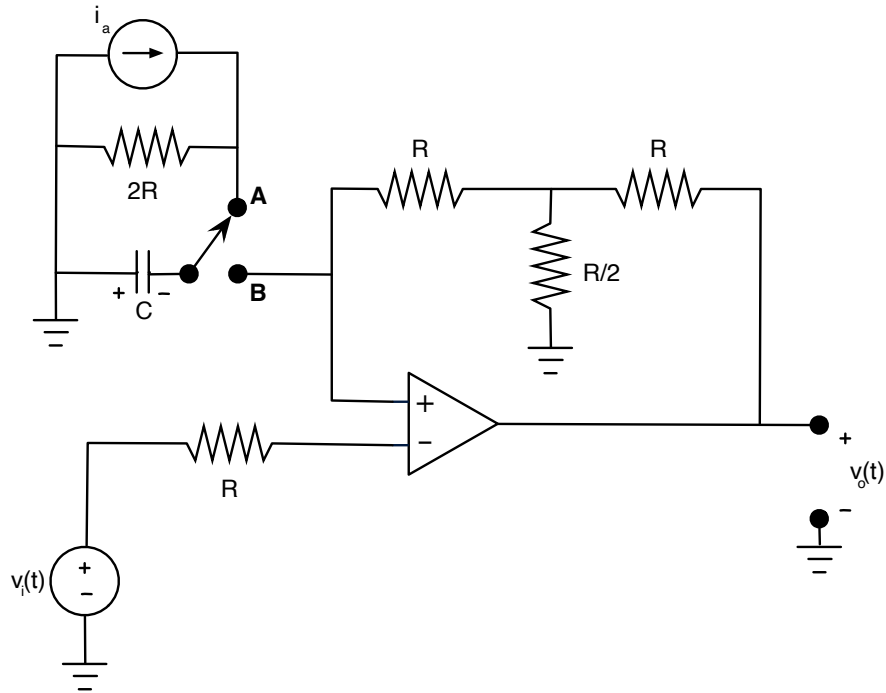


Figure 3: RCL circuit for Laplace Analysis for Question 3.

3. Laplace Domain Circuit Analysis

Part I: [2 points] Consider the circuit depicted in Figure 3. The value i_a of the current source is constant. The switch is kept in position **A** for a very long time. At $t = 0$, it is moved to position **B**. Show that the initial condition for the capacitor is given by

$$v_C(0^-) = -2Ri_a.$$

[Show your work]

Part II: [5 points] Use this initial condition to transform the circuit into the s -domain for $t \geq 0$. Use an equivalent model for the capacitor in which the initial condition appears as a voltage source. Use nodal analysis to express the output response transform $V_o(s)$ as a function of $V_i(s)$ and i_a .

Part III: [3 points] Use partial fractions and inverse Laplace transforms to show that the output voltage $v_o(t)$ when $i_a = 1 \text{ A}$, $v_i(t) = te^{-t}u(t) \text{ V}$, $C = 1 \text{ mF}$, and $R = 1 \text{ K}\Omega$ is

$$v_o(t) = \left(4e^{-t} - te^{-t} - 8000 \delta(t)\right)u(t).$$

Part IV: [Extra 1 point] In Part II we have used nodal analysis, yet the statement asks us to use a voltage source to represent the initial condition. Generally, is this what we would do? Why? Can you explain why the statement asked us to do it?

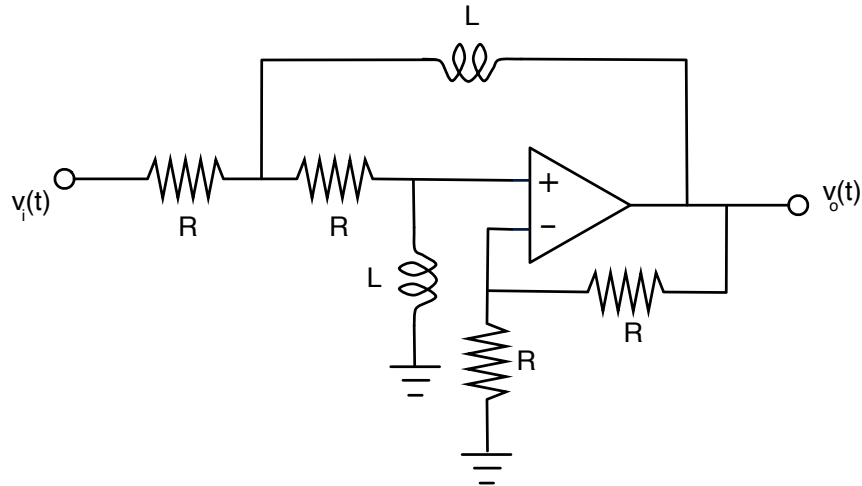


Figure 4: Frequency Response Analysis for Question 4.

4. Frequency Response Analysis

Part I: [1 point] Assuming zero initial conditions, transform the circuit in Figure 4 into the s -domain.

Part II: [3 points] Show that the transfer function from $V_i(s)$ to $V_o(s)$ is given by

$$T(s) = \frac{V_o(s)}{V_i(s)} = \frac{2L^2s^2}{L^2s^2 + LRs + R^2}.$$

[Show your work]

Part III [5 points] Let $R = 1\ \Omega$ and $L = 100\ \text{mH}$. Show that with these values, the transfer function takes the form

$$T(s) = \frac{2s^2}{s^2 + 10s + 100}$$

Compute the gain and phase functions of $T(s)$. What are the DC gain and the ∞ -freq gain? What are the corresponding values of the phase function? What is the cut-off frequency? Sketch plots for the gain and phase functions. What type of filter is this one?

[Explain your answer]

Part IV [1 point] Using what you know about frequency response, compute the steady-state response $v_o^{SS}(t)$ of this circuit when $v_i(t) = \cos(5t + \frac{\pi}{2})$ using the same values of R and L as in Part III.

5. OpAmp Design

Consider the following transfer function

$$T(s) = \frac{1 + 10s}{1000s^2 + 10s}$$

Part I: [4 points] Design a circuit as the series connection of two stages, each with 1 OpAmp, that implements $T(s)$. You can also use 10Ω and 100Ω -resistors, and $1F$ -capacitors, but not inductors. Be sure to properly justify why the overall transfer function of your design is the product of the individual transfer function of each stage.

Part II: [4 points] Design a circuit as the series connection of two stages, one with 1 OpAmp and the other without, that implements $T(s)$. You can also use 10Ω and 100Ω -resistors, and $1F$ -capacitors, but not inductors. Be sure to properly justify why the overall transfer function of your design is the product of the individual transfer function of each stage.

Part III: [2 points] Would the order in which you interconnect the two stages in Part I affect the resulting transfer function? How about in Part II?