

MAE40 - Linear Circuits - Winter 21  
Final Exam, March 18, 2021

**Instructions**

- (i) Prior to the exam, you must have completed the Academic Integrity Pledge at <https://academicintegrity.ucsd.edu/forms/form-pledge.html>
- (ii) The exam is open book. You may use your class notes and textbook
- (iii) Collaboration is not permitted. The answers you provide should be the result only of your own work
- (iv) On the questions for which the answers are given, please provide detailed derivations
- (v) The exam has 4 questions for a total of 40 points and 4 bonus points
- (vi) You have from 11:30am to 2:30pm to complete the exam. Allow sufficient time to post your answers in Canvas (submission closes at 2:40pm).
- (vii) If there is any clarification needed, post your question in the “Discussions” tab of the class Canvas webpage (“Clarifications on question statements of final”)

Good luck!

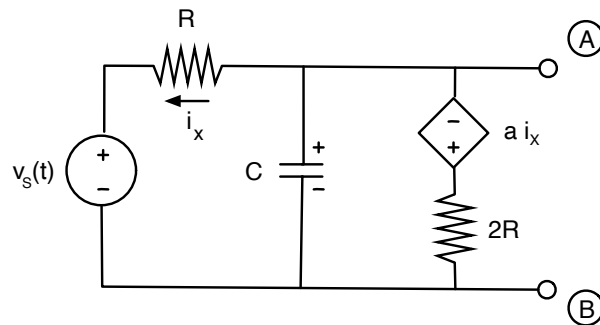


Figure 1: Circuit for Question 1.

**1. Equivalent Circuits**

Here,  $v_S(t) = e^{-t}u(t)$  and  $a$  is a known constant.

**Part I:** [2 points] Assuming  $v_C(0) = 1V$ , transform the circuit in Figure 1 into the  $s$ -domain, using a voltage source to account for the initial condition of the capacitor.

**Part II:** [3 points] For the circuit you obtained in Part I, find the open-circuit voltage transform as seen from terminals  $\textcircled{A}$ - $\textcircled{B}$ . The answer should be given as a ratio of two polynomials.

**Part III:** [3 points] For the circuit you obtained in Part I, find the short-circuit current transform as seen from terminals  $\textcircled{A}$ - $\textcircled{B}$ . The answer should be given as a ratio of two polynomials.

**Part IV:** [2 points] For the circuit you obtained in Part I, find the Norton equivalent in the  $s$ -domain as seen from terminals  $\textcircled{A}$ - $\textcircled{B}$  (the impedance should be given as a ratio of two polynomials).

**Part V:** [Extra 2 points] What is the capacitor voltage transform?

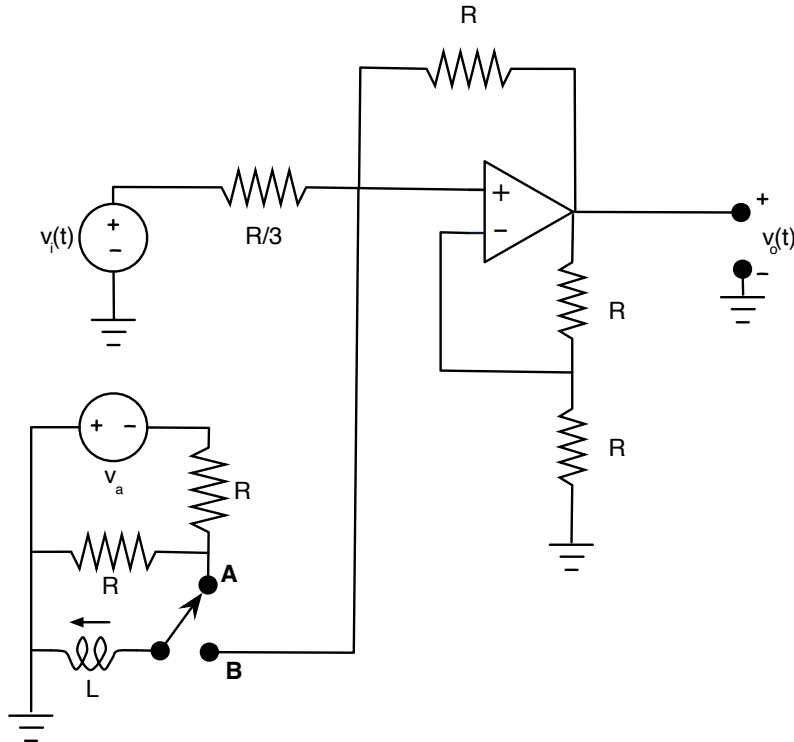


Figure 2: RL circuit for Laplace Analysis for Question 2.

## 2. Laplace Domain Circuit Analysis

**Part I:** [2 points] Consider the circuit depicted in Figure 2. The value  $v_a$  of the current source is constant. The switch is kept in position **A** for a very long time. At  $t = 0$ , it is moved to position **B**. Show that the initial condition for the inductor is given by

$$i_L(0^-) = -\frac{v_a}{R}.$$

[Show your work]

**Part II:** [5 points] Use this initial condition to transform the circuit into the  $s$ -domain for  $t \geq 0$ . Use an equivalent model for the inductor in which the initial condition appears as a voltage source. Use nodal analysis to express the output response transform  $V_o(s)$  as a function of  $V_i(s)$  and  $v_a$ .

**Part III:** [3 points] Use partial fractions and inverse Laplace transforms to show that the output voltage  $v_o(t)$  when  $v_a = 1 \text{ V}$ ,  $v_i(t) = e^{-t}u(t) \text{ V}$ ,  $L = 1 \text{ H}$ , and  $R = 1 \Omega$  is

$$v_o(t) = (6e^{-t} - 2e^{-t/2})u(t).$$

**Part IV:** [Extra 2 points] Decompose the output voltage of Part III as (i) the sum of the natural and forced response, and (ii) the sum of the zero-state and zero-input response.

### 3. Frequency Response Analysis

Consider the transfer function

$$T(s) = \frac{10}{s^2 + s + 1}$$

**Part I** [2 points] Compute the gain  $|T(j\omega)|$  and phase  $\angle T(j\omega)$  functions

**Part II** [4 points] What are the DC gain and the  $\infty$ -freq gain? What are the corresponding values of the phase function? What is the cut-off frequency?

**Part III** [2 points] Sketch plots for the gain and phase functions. What type of filter is this one?  
[Explain your answer]

**Part IV** [2 points] Using what you know about frequency response, compute the steady-state response  $v_o^{SS}(t)$  to the input  $v_i(t) = \sqrt{13} \cos(2t - \frac{\pi}{2})$ .

#### 4. OpAmp Design and Chain Rule

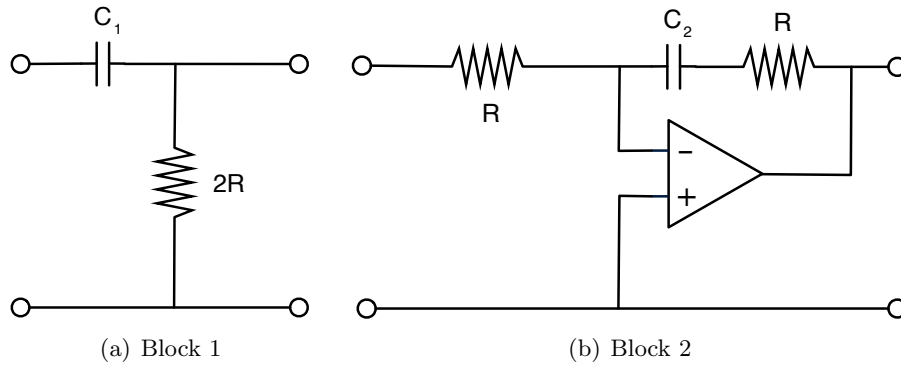


Figure 3: Circuits for Question 4.

**Part I:** [2 points] Find the transfer functions  $T_1(s)$  and  $T_2(s)$  for each block in Figure 3.

**Part II:** [2 points] If you were to connect the blocks in series in the following two configurations: (a) (block 1, block 2) and (b) (block 2, block 1), will you obtain the same transfer function? Why?

**Part III:** [3 points] An engineer used a configuration from Part II whose transfer function is

$$T(s) = T_1(s) \cdot T_2(s) = -\frac{s + \frac{1}{RC_2}}{s + \frac{1}{2RC_1}}$$

However, he was surprised to observe that when he hooked up a source circuit with Thévenin equivalent  $V_T(s)$  and  $Z_T(s)$ , the output transform was different from

$$V_o(s) = T(s)V_T(s)$$

which is what he had expected. Can you explain why? If you could use one additional op-amp, how will you fix his design so that he obtains the intended output? Justify your answer.

**Part IV:** [3 points] Eventually, the engineer gave up on the blocks above and came up with a different design for realizing  $T(s)$ . He did so by employing the same type of components (resistors with values  $R$  and  $2R$ , and capacitors with values  $C_1$  and  $C_2$ ) and using a non-inverting op-amp circuit and an inverting op-amp circuit based on the factorization

$$T(s) = 2 \cdot \left( -\frac{R + \frac{1}{C_2 s}}{2R + \frac{1}{C_1 s}} \right)$$

Verify that this factorization is correct. When he hooked up the source circuit with Thévenin equivalent  $V_T(s)$  and  $Z_T(s)$ , he finally got the desired output transform. Can you reproduce his design?