

---

## Linear Circuit Experiment (MAE171a)

---

**Prof:** Raymond de Callafon  
**email:** callafon@ucsd.edu

**TA:** Younghee Han  
tel. (858) 8221763/8223457, **email:** y3han@ucsd.edu

class information and lab handouts will be available on  
<http://maecourses.ucsd.edu/labcourse/>

## Main Objectives of Laboratory Experiment:

modeling, building and debugging of op-amp based linear circuits for standard signal conditioning

### Ingredients:

- modeling of standard op-amp circuits
- signal conditioning with application to audio (condensor microphone as input, speaker as output)
- implementation & verification of op-amp circuits
- sensitivity and error analysis

### Background Theory:

- Operational Amplifiers (op-amps)
- Linear circuit theory (resistor, capacitors)
- Ordinary Differential Equations (dynamic analysis)
- Amplification, differential & summing amplifier and filtering

## Outline of this lecture

- Linear circuits & purpose of lab experiment
- Background theory
  - op-amp
  - linear amplification
  - single power source
  - differential amplifier
  - summing circuit
  - filtering
- Laboratory work
  - week 1: microphone and amplification
  - week 2: mixing via difference and adding
  - week 3: filtering and power boost
- Summary

## Linear Circuits & Signal Conditioning

Signal conditioning crucial for proper signal processing.

Applications may include:

- Analog to Digital Conversion
  - Resolution determined by number of bits of AD converter
  - Amplify signal to maximum range for full resolution
- Noise reduction
  - Amplify signal to allow processing
  - Filter signal to reduce undesired aspects
- Feedback control
  - Feedback uses reference  $r(t)$  and measurement  $y(t)$
  - Compute difference  $e(t) = r(t) - y(t)$
  - Amplify, Integrate and or Differentiate  $e(t)$  (PID control)
- Signal generation
  - Create sinewave of proper frequency as carrier
  - Create blockwave of proper frequency for counter
  - etc. etc.

## Purpose of Lab Experiment

In this laboratory experiment we focus on a (relatively simple) signal conditioning algorithms: *amplification*, *adding/difference* and basic (at most 2nd order) *filtering*.

**Objective:** to model, build and debug op-amp based linear circuits that allow signal conditioning algorithms.

We apply this to an audio application, where the signal of a condenser microphone needs to be amplified, mixed and filtered.

**Challenge:** single source power supply of 5 Volt. Avoid clipping/distortion of amplified, mixed and filtered signal.

### Aim of the experiment:

- insight in op-amp based linear circuits
- build and debug (frustrating)
- compare theory (ideal op-amp) with practice (build and test)
- verify circuit behavior (simulation/PSPICE)

## Background Theory - op-amp

op-amp = operational amplifier

more precise definition:


DC-coupled high-gain electronic voltage amplifier with differential inputs and a single output.

- DC-coupled: constant (direct current) voltage at inputs results in a constant voltage at output
- differential inputs: two inputs  $V_-$  and  $V_+$  and the difference  $V_\delta = V_+ - V_-$  is only relevant
- high-gain:  $V_{out} = G(V_+ - V_-)$  where  $G \gg 1$ .

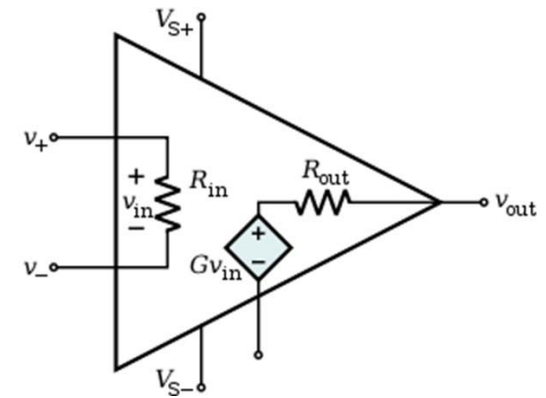
## Background Theory - op-amp

Ideal op-amp (equivalent circuit right):

- input impedance:  $R_{in} = \infty \Rightarrow i_{in} = 0$
- output impedance:  $R_{out} = 0$
- gain:  $V_{\delta} = (V_{+} - V_{-})$ ,  $V_{out} = GV_{\delta}$ ,  $G = \infty$
- rail-to-rail:  $V_{S-} \leq V_{out} \leq V_{S+}$



Ideal op-amp (block diagram below)

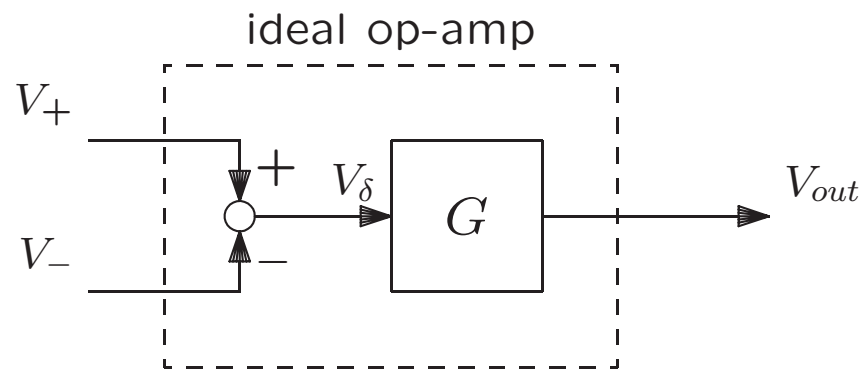

## Background Theory - op-amp

Infinite input impedance ( $R_{in} = \infty$ ) useful to minimize load on sensor/input.


Zero output impedance ( $R_{out} = 0$ ) useful to minimize load dependency and obtain maximum output power.

Rail-to-rail operation to maximize range of output  $V_{out}$  between negative source supply  $V_{S-}$  and positive source supply  $V_{S+}$ .

But **why (always) infinite gain  $G$** ? Obviously:

$$V_{out} = \begin{cases} V_{S+} & \text{if } V_+ > V_- \\ 0 & \text{if } V_+ = V_- \\ V_{S-} & \text{if } V_+ < V_- \end{cases}$$

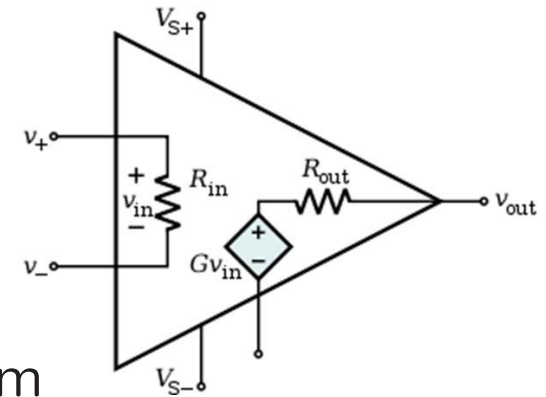not very useful with any (small) noise on  $V_+$  or  $V_-$ .





## Background Theory - op-amp

Usefulness of op-amp with high gain  $G$  only by **feedback!**

Consider open-loop behavior:

$$V_{out} = GV_{\delta}, \text{ where } V_{\delta} = V_{+} - V_{-}$$

and create a **feedback of  $V_{out}$**  by choosing

$$V_{-} = KV_{out}$$

to make

$$V_{\delta} = V_{+} - KV_{out}$$

Then


$$V_{out} = GV_{\delta} = GV_{+} - GK V_{out}$$

allowing us to write

$$V_{out} = \frac{G}{1 + GK} V_{+}$$
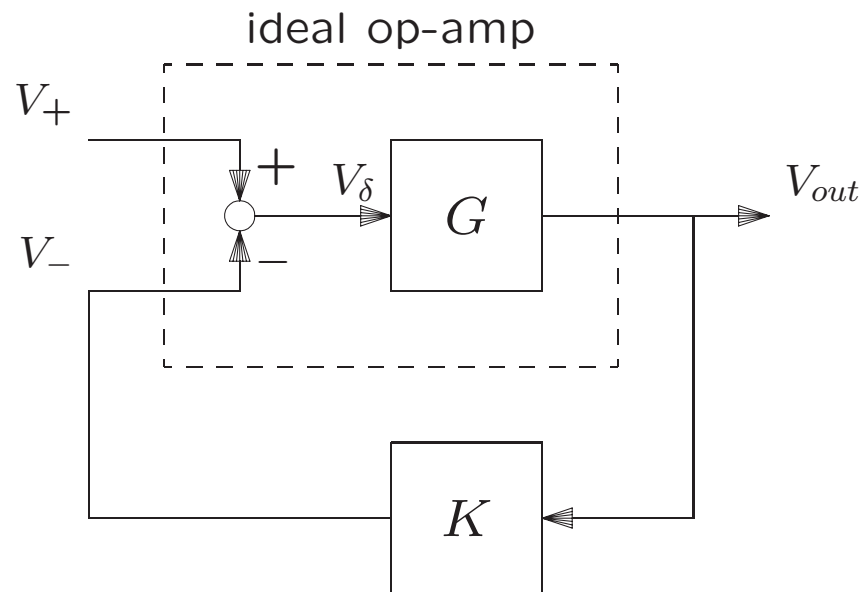
## Background Theory - op-amp

So, with the feedback  $V_- = KV_{out}$  we obtain  $V_{out} = \frac{G}{1 + GK}V_+$




In case  $G \rightarrow \infty$  we see:

$$V_{out} = \frac{1}{K}V_+$$

- Don't care what gain  $G$  is, as long as it is LARGE
- Make sure  $K$  is well-defined and accurate
- If  $0 < K < 1$  then  $V_+$  is nicely amplified to  $V_{out}$  by  $1/K$
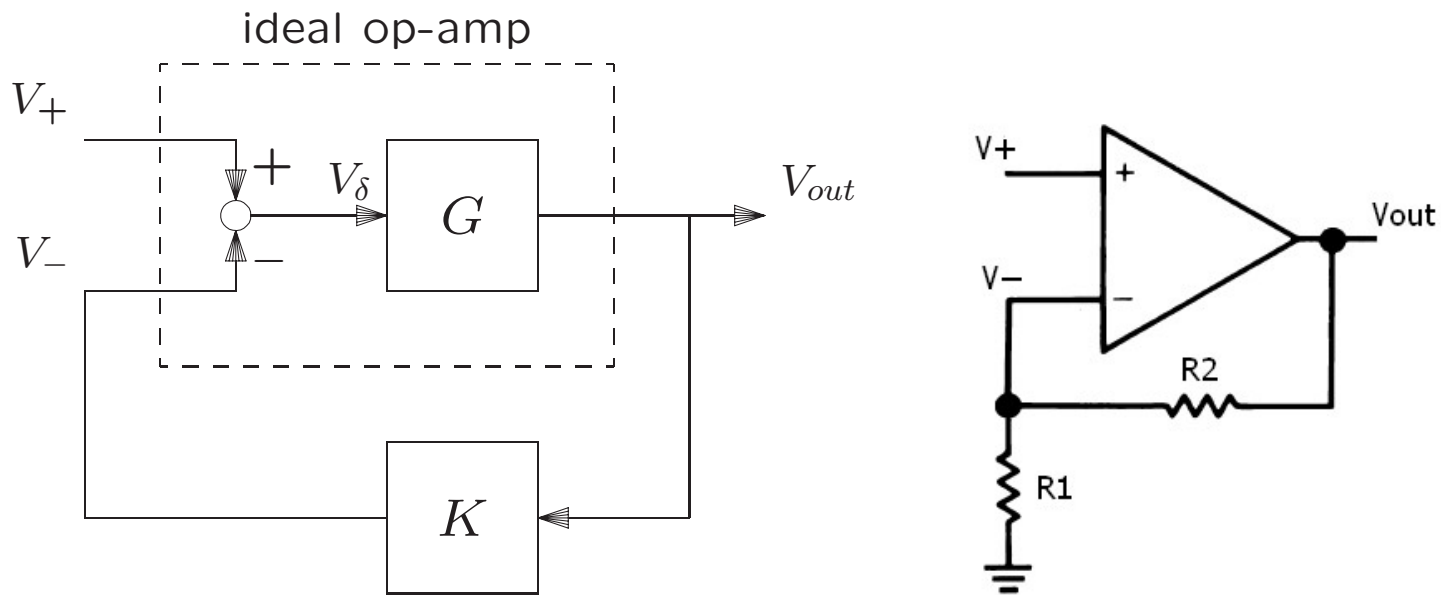
## Background Theory - op-amp

Amplification  $1/K$  by feedback  $K$  of ideal high gain op-amp:



Series of  $R_1$  and  $R_2$  leads to voltage divider on  $V_-$  given by:

$$V_- = \frac{R_1}{R_1 + R_2} V_{out} = K V_{out}, \quad 0 < K \leq 1$$

and with ideal high gain op-amp we get

$$\lim_{G \rightarrow \infty} V_{out} = \lim_{G \rightarrow \infty} \frac{G}{1 + GK} V_+ = \frac{1}{K} V_+ = \frac{R_1 + R_2}{R_1} V_+ = \left( 1 + \frac{R_2}{R_1} \right) V_+$$

## Background Theory - non-inverting amplifier (voltage follower)


Our first application circuitry:

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

So-called **voltage follower** in case

$$R_1 = \infty \text{ (not present) and } R_2 = 0$$

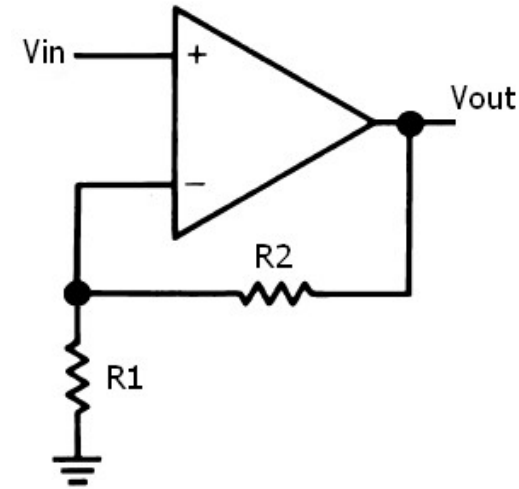where  $V_{out} = V_{in}$  but **improved output impedance!**



Quick (alternative) analysis based on  $V_+ = V_-$  and  $i_+ = i_- = 0$ :

- Since  $i_- = 0$  and series  $R_1, R_2$  we have  $V_- = \frac{R_1}{R_1 + R_2} V_{out}$
- Hence

$$V_{in} = V_+ = \frac{R_1}{R_1 + R_2} V_{out} \Rightarrow V_{out} = \frac{R_1 + R_2}{R_1} V_{in} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$

## Background Theory - inverting amplifier

Similar circuit but now negative sign:

$$V_{out} = -\frac{R_2}{R_1}V_{in}$$

Quick (alternative) analysis based on


$V_+ = V_-$  and  $i_+ = i_- = 0$ :

- With  $V_- = V_+ = 0$  and  $i_- = 0$ , Kirchhoff's Current Law indicates


$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$

- Hence

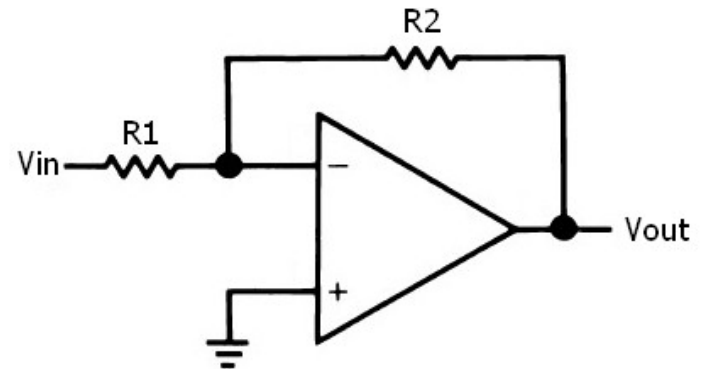
$$\frac{V_{out}}{R_2} = -\frac{V_{in}}{R_1} \Rightarrow V_{out} = -\frac{R_2}{R_1}V_{in}$$


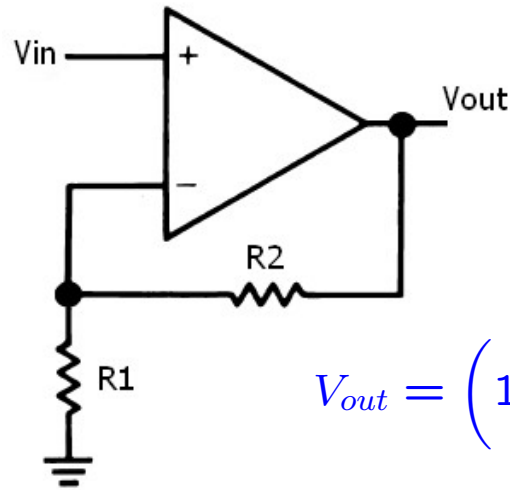
## Background Theory - effect of rail (source) voltages


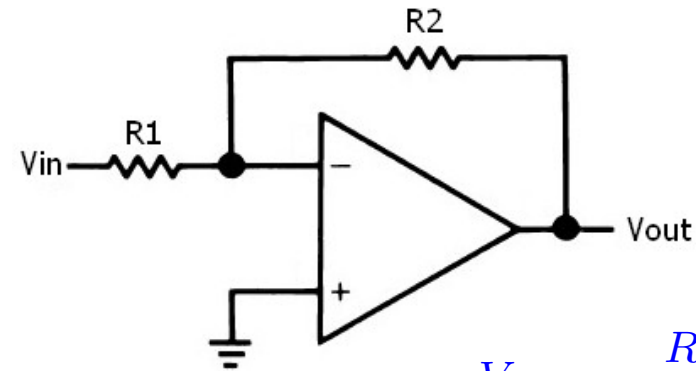
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$



$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Formulae are for ideal op-amp with **boundaries imposed by negative source supply  $V_{S-}$  and positive source supply  $V_{S+}$**


$$V_{S-} \leq V_{out} \leq V_{S+} \quad (\text{rail-to-rail op-amp})$$

**Single voltage power supply** with  $V_{S+} = V_{cc}$  and  $V_{S-} = 0$  (ground):


- Limits use of inverting amplifier ( $V_{out} < 0$  not possible)
- Limits use of large gain  $R_2/R_1$  ( $V_{out} > V_{cc}$  not possible)

**Design challenge:**  $0 < V_{out} < V_{cc}$  to **avoid 'clipping' of  $V_{out}$ .**
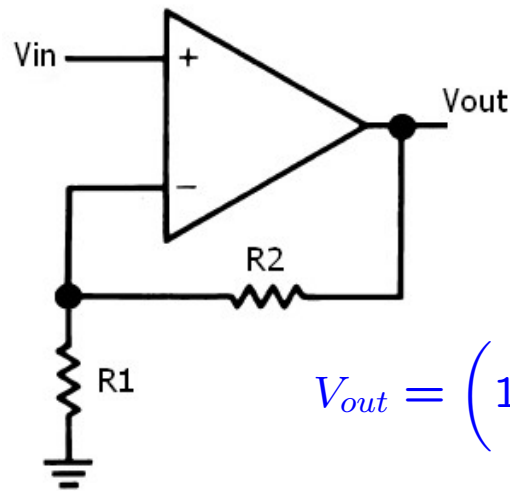
## Background Theory - effect of rail (source) voltages


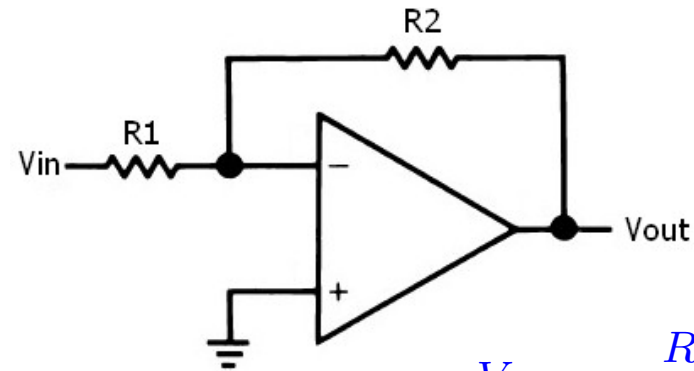
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$



$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

Single voltage power supply with  $V_{S+} = V_{cc}$  and  $V_{S-} = 0$  (ground) complicates amplification of

$$V_{in}(t) = a \sin(2\pi ft)$$

as  $-a < V_{in}(t) < a$  (both positive and negative w.r.t. ground).

**Example:** audio application (as in our experiment).

To ensure  $0 < V_{out} < V_{cc}$  provide **offset compensation**

$$V_{in}(t) = a \sin(2\pi ft) + a$$

to ensure  $V_{in}(t) > 0$  and use **non-inverting amplifier**.

## Background Theory - differential amplifier

Instead of amplifying one signal, amplify the difference:

$$V_{out} = \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} V_2 - \frac{R_2}{R_1} V_1$$

Difference or differential amplifier is found by inverting amplifier and adding signal to  $V_+$  via series connection of  $R_3$  and  $R_4$ . Analysis:

- With  $i_+ = 0$  the series of  $R_3$  and  $R_4$  leads to  $V_+ = \frac{R_4}{R_3 + R_4} V_2$
- With  $V_- = V_+$  and Kirchoff's Current Law we have


$$\frac{V_1 - \frac{R_4}{R_3 + R_4} V_2}{R_1} + \frac{V_{out} - \frac{R_4}{R_3 + R_4} V_2}{R_2} = 0$$

Hence

$$V_{out} = \frac{R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} V_2 + \frac{R_4}{R_3 + R_4} V_2 - \frac{R_2}{R_1} V_1$$

or
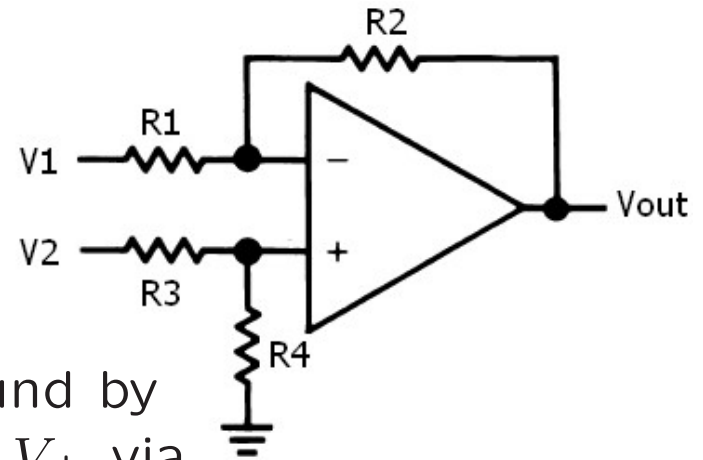
$$V_{out} = \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} V_2 - \frac{R_2}{R_1} V_1$$





## Background Theory - differential amplifier

Choice  $R_1 = R_3$  and  $R_2 = R_4$  reduces

$$V_{out} = \frac{R_1 + R_2}{R_3 + R_4} \cdot \frac{R_4}{R_1} V_2 - \frac{R_2}{R_1} V_1$$

to

$$V_{out} = \frac{R_2}{R_1} (V_2 - V_1)$$


create a difference/differential amplifier.

Further choice of  $R_1 = R_3$ ,  $R_2 = R_4$  and  $R_2 = R_1$  yields

$$V_{out} = V_2 - V_1$$



and computes the difference between input voltages  $V_1$  and  $V_2$ .

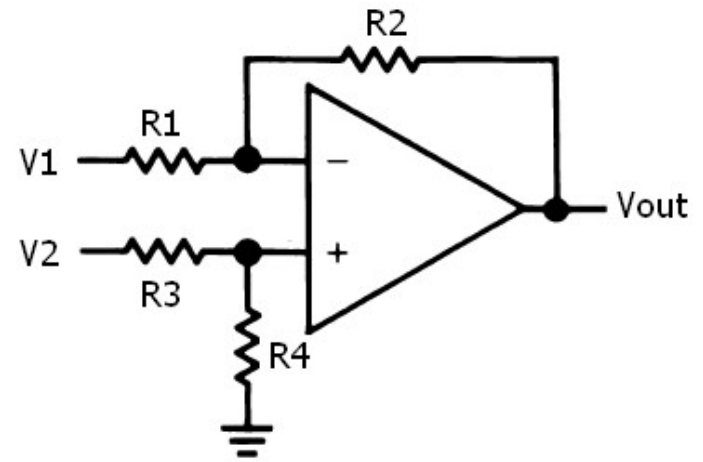**NOTE:**  $V_2 > V_1$  for a **single voltage power supply** with  $V_{S+} = V_{cc}$  and  $V_{S-} = 0$  (ground) to avoid clipping of  $V_{out}$  against ground.


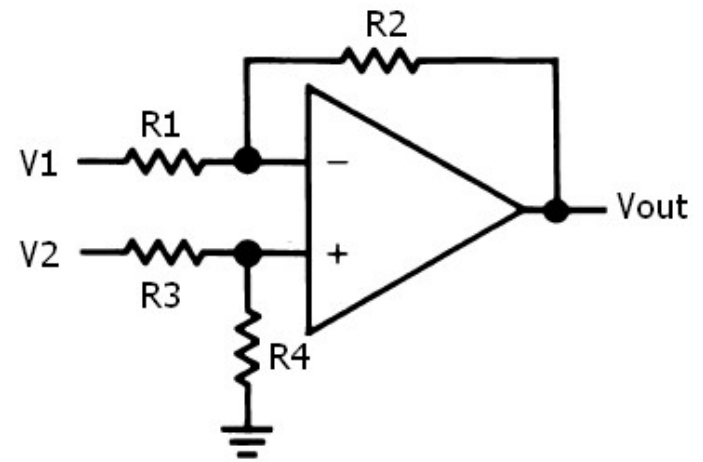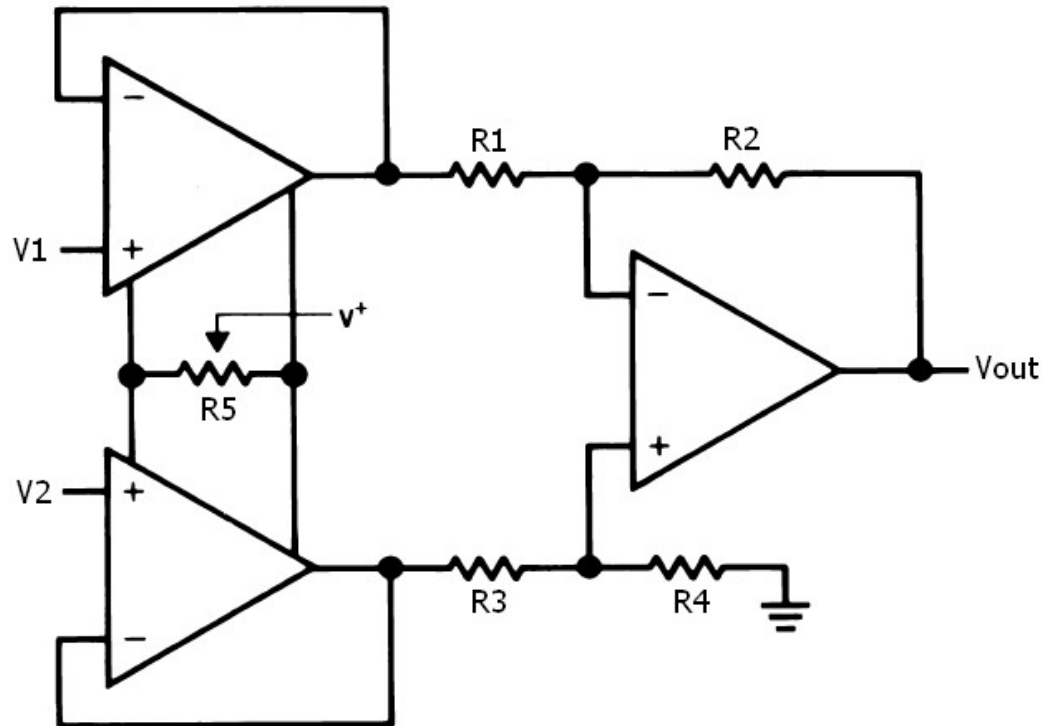
## Background Theory - more advanced differential amplifiers

Difference amplifier does not have high input impedance (loading of sensors).  
Better design with voltage followers:



With

$$\frac{R_2}{R_1} = \frac{R_4}{R_3}$$

we have

$$V_{out} = \frac{R_2}{R_1}(V_2 - V_1)$$

$R_5$  is used to adjust offset (balance)

## Background Theory - more advanced differential amplifiers

Even better differential amplifier that has a **variable gain** is a so-called **instrumentation amplifier**:


Setting all resistors

$$R_i = R, \quad i = 1, 2, \dots, 5$$

except  $R_{var}$ , makes

$$V_{out} = \left(1 + \frac{2R}{R_{var}}\right) (V_2 - V_1)$$

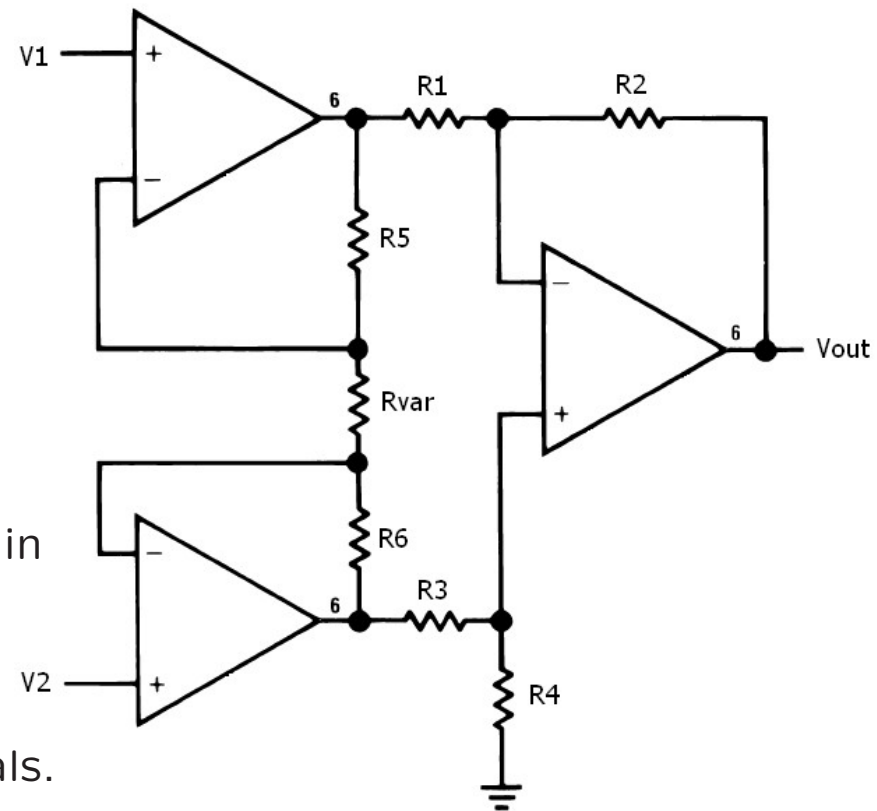High input impedance and variable gain via an (external) resistor  $R_{var}$  makes this ideal for the amplification of (non-grounded) instrumentation signals.



Instrumentation amplifiers are made & sold as a single chip.

## Background Theory - inverting summing amplifier

Inverting amplifier can also be extended to add signals:

$$V_{out} = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

Analysis follows from Kirchhoff's Current Law for the  $-$  input of the op-amp:


- With  $V_- = V_+$  we have  $V_- = 0$
- With  $i_- = 0$  we have

$$\frac{V_{out}}{R_4} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = 0$$

Hence

$$V_{out} = -R_4 \cdot \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

creating a weighted sum of signals.

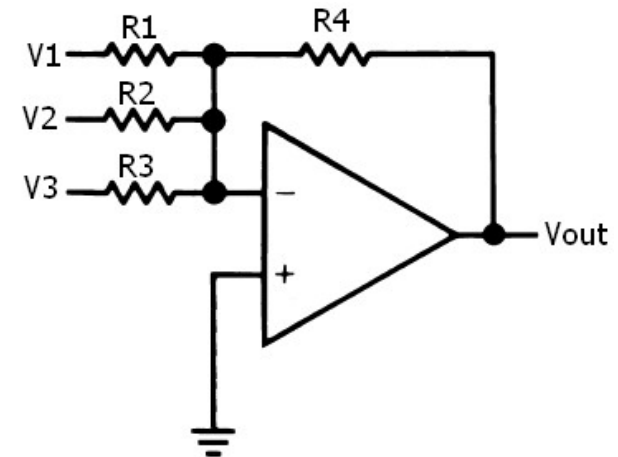

## Background Theory - inverting summing amplifier

The choice  $R_1 = R_2 = R_3$  reduces

$$V_{out} = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

to



$$V_{out} = -\frac{R_4}{R_1} (V_1 + V_2 + V_3)$$

simply amplifying the sum of the signals.

Oftentimes **extra resistor  $R_5$**  is added:

$$\frac{1}{R_5} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

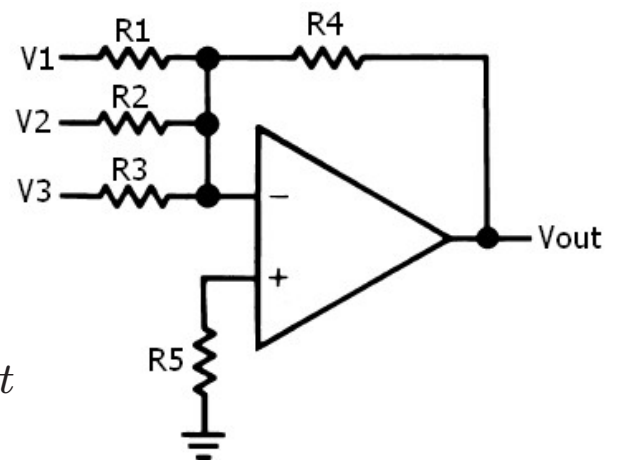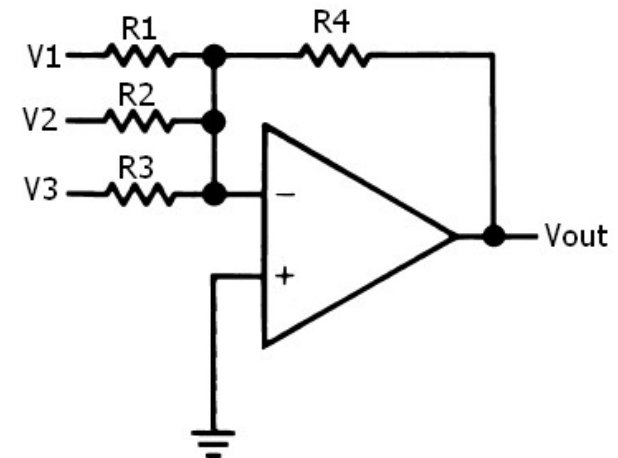to account for possible small (bias) input currents  $i_- \neq 0$ ,  $i_+ \neq 0$ . This ensures  $V_{out}$  remains sum, without bias/offset.




## Background Theory - inverting summing amplifier

Inverting summing amplifier:

$$V_{out} = -R_4 \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

and for  $R_1 = R_2 = R_3$ :
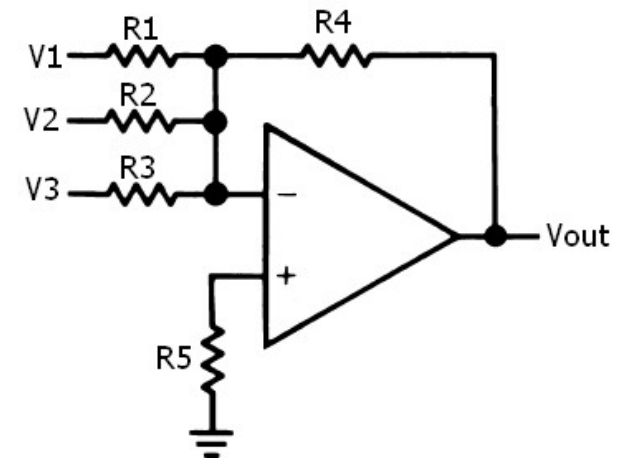
$$V_{out} = -\frac{R_4}{R_1} (V_1 + V_2 + V_3)$$



has a limitation for single source voltage supplies:

Single voltage power supply with  $V_{S+} = V_{cc}$  and  $V_{S-} = 0$ :


- Limits use of inverting summer ( $V_{out} < 0$  not possible)
- Limits use of large gain  $R_4/R_1$  ( $V_{out} > V_{cc}$  not possible)

'clipping' of  $V_{out}$  will occur if sum of input signals is positive.
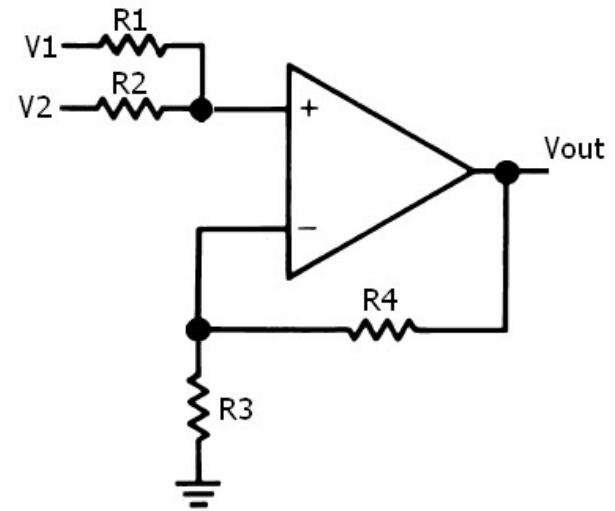
## Background Theory - non-inverting summing amplifier

Based on a non-inverting amplifier signals can also be summed:

$$V_{out} = \left(1 + \frac{R_4}{R_3}\right) \frac{R_1 R_2}{R_1 + R_2} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right)$$



Analysis:

- due to  $i_- = 0$  we have  $V_- = \frac{R_3}{R_3 + R_4} V_{out}$
- Due to  $V_+ = V_-$  and  $i_+ = 0$  with Kirchhoff's Current Law:

$$\frac{V_1 - \frac{R_3}{R_3 + R_4} V_{out}}{R_1} + \frac{V_2 - \frac{R_3}{R_3 + R_4} V_{out}}{R_2} = 0$$

Hence

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \frac{R_3}{R_3 + R_4} V_{out}$$

and

$$V_{out} = \left(1 + \frac{R_4}{R_3}\right) \frac{R_1 R_2}{R_1 + R_2} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right)$$

## Background Theory - non-inverting summing amplifier

The choice  $R_1 = R_2$  reduces

$$V_{out} = \left(1 + \frac{R_4}{R_3}\right) \frac{R_1 R_2}{R_1 + R_2} \left(\frac{V_1}{R_1} + \frac{V_2}{R_2}\right)$$

to

$$V_{out} = \left(1 + \frac{R_4}{R_3}\right) \frac{V_1 + V_2}{2}$$

indicating amplification of the sum  $V_1$  and  $V_2$  if  $R_4 \geq R_3$ .


Further choice of also  $R_1 = R_2 = R_3 = R_4$  leads to

$$V_{out} = V_1 + V_2$$

indicating a simple summation of  $V_1$  and  $V_2$ .

Unlike inverting summing amplifier, no extra resistor can be added to compensate for bias input current.

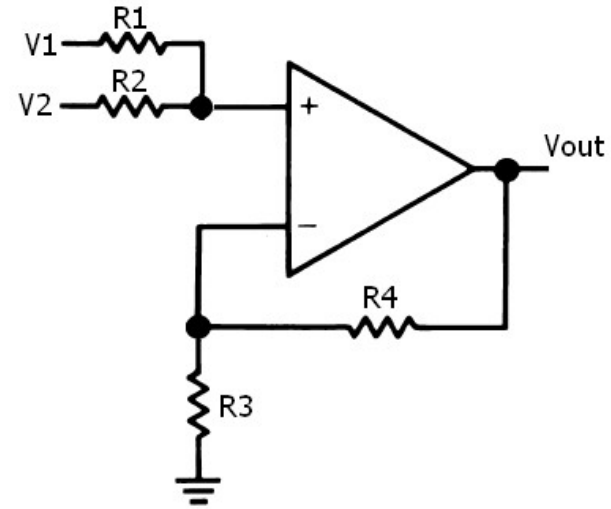Not desirable: source impedance part of gain calculation...





## Background Theory - filtering

So far, all circuits were build using op-amps and resistors.

When building filters, mostly **capacitors** are used as negative, positive or grounding elements.

Interesting phenomena: **resistor value of capacitor depends on frequency of signal.**

Analysis for capacitor: **capacitance  $C$  is ratio between charge  $Q$  and applied voltage  $V$ :**

$$C = \frac{Q}{V}$$

Since charge  $Q(t)$  at any time is found by flow of electrons:

$$Q(t) = \int_{\tau=0}^t i(\tau) d\tau$$

we have

$$V(t) = \frac{Q(t)}{C} = \frac{1}{C} \int_{\tau=0}^t i(\tau) d\tau$$

## Background Theory - filtering

Application of Laplace transform to

$$V(t) = \frac{Q(t)}{C} = \frac{1}{C} \int_{\tau=0}^t i(\tau) d\tau$$

yields

$$V(s) = \frac{1}{Cs} i(s)$$

Hence we can define the impedance/resistance of a capacitor as

$$R(s) = \frac{V(s)}{i(s)} = \frac{1}{Cs}$$

With Fourier analysis we use  $s = j\omega$  and we find the frequency dependent 'equivalent resistor value of a capacitor':

$$R(j\omega) = \frac{1}{jC\omega}$$

This value will allow analysis of op-amp circuits based on resistors (as we have done so far)

## Background Theory - filtering

Consider simple 1st order RC-filter with voltage follower op-amp.

Due to  $i_+ = 0$  we have


$$V_+(j\omega) = \frac{\frac{1}{C_1 j\omega}}{R_1 + \frac{1}{C_1 j\omega}} V_{in}(j\omega)$$

With  $V_{out} = V_- = V_+$  we have

$$V_{out}(j\omega) = \frac{1}{R_1 C_1 j\omega + 1} V_{in}(j\omega)$$

This is a 1st order low-pass filter with a cut-off frequency
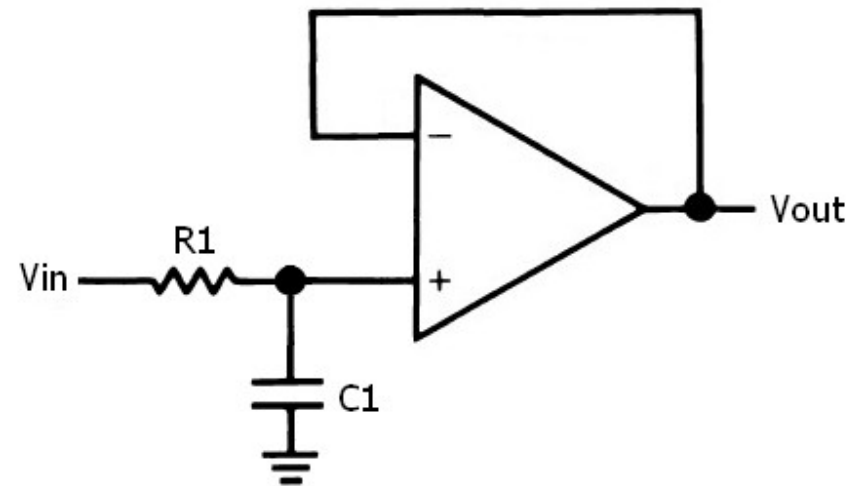
$$\omega_c = \frac{1}{R_1 C_1} \text{ rad/s or } f_c = \frac{1}{2\pi R_1 C_1} \text{ Hz}$$



## Background Theory - filtering

Consider circuit of non-inverting amplifier where  $R_1$  is now series of  $R_1$  and  $C_1$ . Equivalent series resistance is given by


$$R_1 + \frac{1}{jC_1\omega}$$

Application of gain formula for non-inverting amplifier yields:

$$V_{out}(j\omega) = \left( 1 + \frac{R_2}{R_1 + \frac{1}{jC_1\omega}} \right) V_{in}(j\omega)$$

We can directly see:

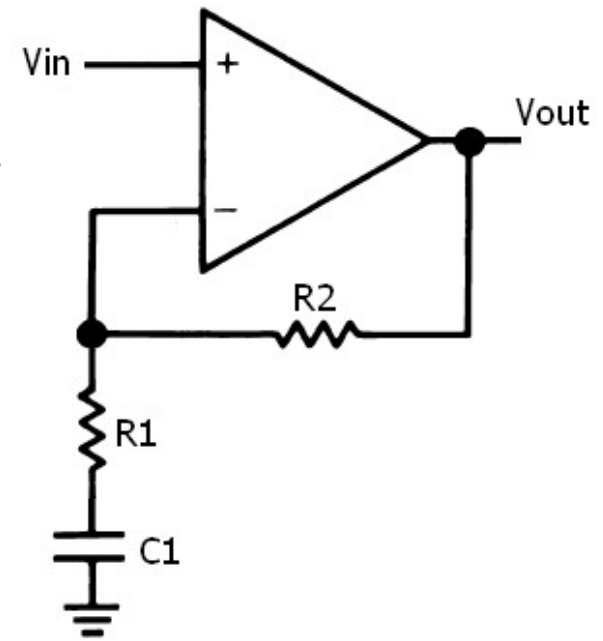- For low frequencies  $\omega \rightarrow 0$  we obtain a Voltage follower with  $V_{out} = V_{in}$
- For high frequencies  $\omega \rightarrow \infty$  we obtain our usual non-inverting amplifier  $V_{out}(j\omega) = \left( 1 + \frac{R_2}{R_1} \right) V_{in}(j\omega)$



## Background Theory - filtering

Transition between low and high frequency can be studied better by writing  $V_{out}(s) = G(s)V_{in}(s)$  where  $G(s)$  is a **transfer function**.

This allows us to write

$$V_{out}(s) = \left( 1 + \frac{R_2}{R_1 + \frac{1}{C_1 s}} \right) V_{in}(s)$$

as

$$V_{out}(s) = \left( 1 + \frac{R_2 C_1 s}{R_1 C_1 s + 1} \right) V_{in}(s) = \frac{(R_1 + R_2) C_1 s + 1}{R_1 C_1 s + 1} V_{in}(s)$$

making

$$G(s) = \frac{(R_1 + R_2) C_1 s + 1}{R_1 C_1 s + 1}$$

## Background Theory - filtering

The transfer function

$$G(s) = \frac{(R_1 + R_2)C_1s + 1}{R_1C_1s + 1}$$

has the following properties:

- single pole at  $p_1 = -\frac{1}{R_1C_1}$  and found by solving  $R_1C_1s + 1 = 0$ .
- single zero at  $z_1 = -\frac{1}{(R_1 + R_2)C_1}$  and found by solving  $(R_1 + R_2)C_1s + 1 = 0$ .
- DC-gain of 1 and found by substitution  $s = 0$  in  $G(s)$ . Related to the final value theorem for a step input signal  $v_{in}(t)$ :

$$\lim_{t \rightarrow \infty} V_{out}(t) = \lim_{s \rightarrow 0} s \cdot V_{out}(s) = \lim_{s \rightarrow 0} s \cdot G(s) \cdot \frac{1}{s} = \lim_{s \rightarrow 0} G(s)$$

where  $\frac{1}{s}$  is the Laplace transform of the step input  $v_{in}(t)$ .

- High frequency gain of  $\frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1}$  and found by computing  $s \rightarrow \infty$ .

## Background Theory - filtering


The transfer function

$$G(s) = \frac{(R_1 + R_2)C_1s + 1}{R_1C_1s + 1}$$

is a first order system where zero  $z_1 = -\frac{1}{(R_1+R_2)C_1} < p_1 = -\frac{1}{R_1C_1}$ .  
This indicates  $G(s)$  is a lead filter.

Easy to study in Matlab:
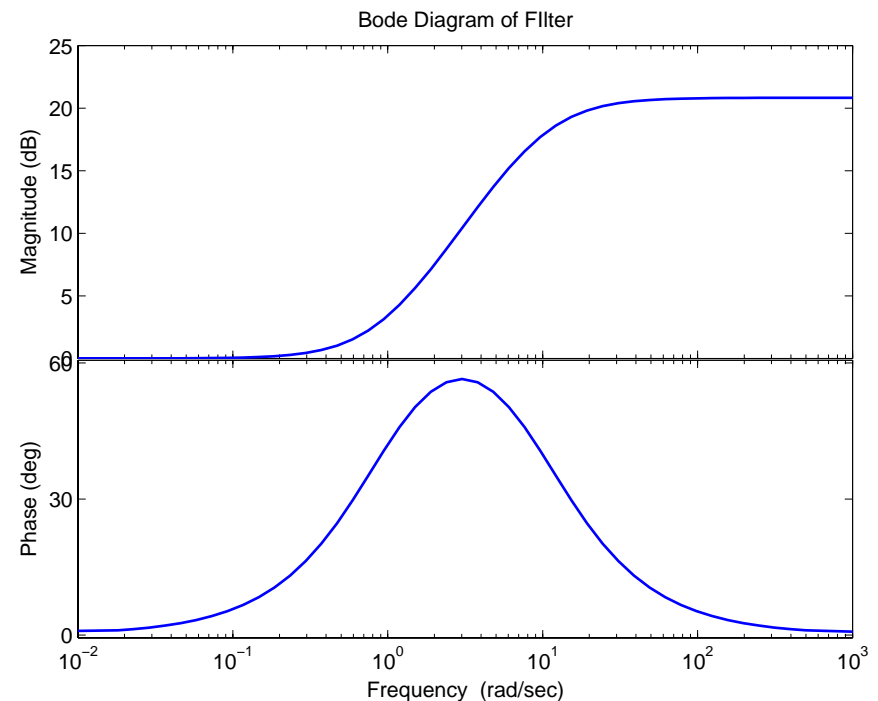
```
>> R2=100e3;R1=10e3;C1=10e-6;  
>> G=tf([(R1+R2)*C1 1],[R1*C1 1]);  
>> bode(G)
```




## Background Theory - filtering

Amplification lead filter circuit with

$$V_{out}(j\omega) = \left( 1 + \frac{R_2}{R_1 + \frac{1}{jC_1\omega}} \right) V_{in}(j\omega)$$

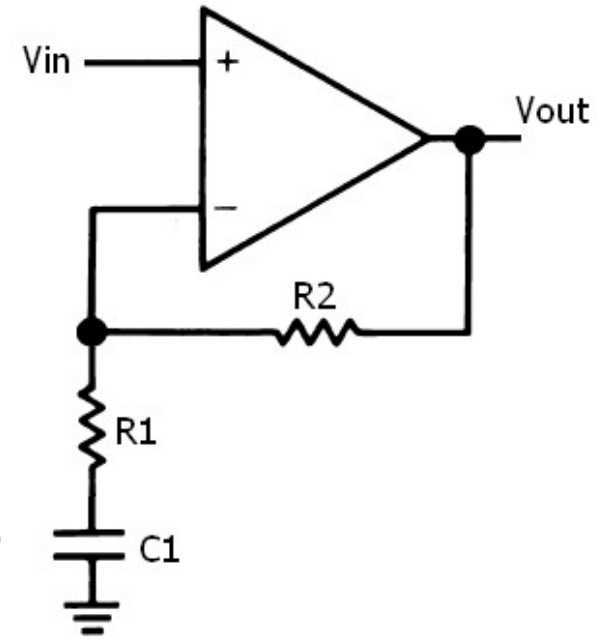will be used to strongly amplify a small high frequent signal but maintain (follow) the DC-offset.



From the previous analysis we see:


- Gain at DC ( $\omega = 0$ ) is simply 1.
- Gain at higher frequencies approaches  $1 + \frac{R_2}{R_1}$


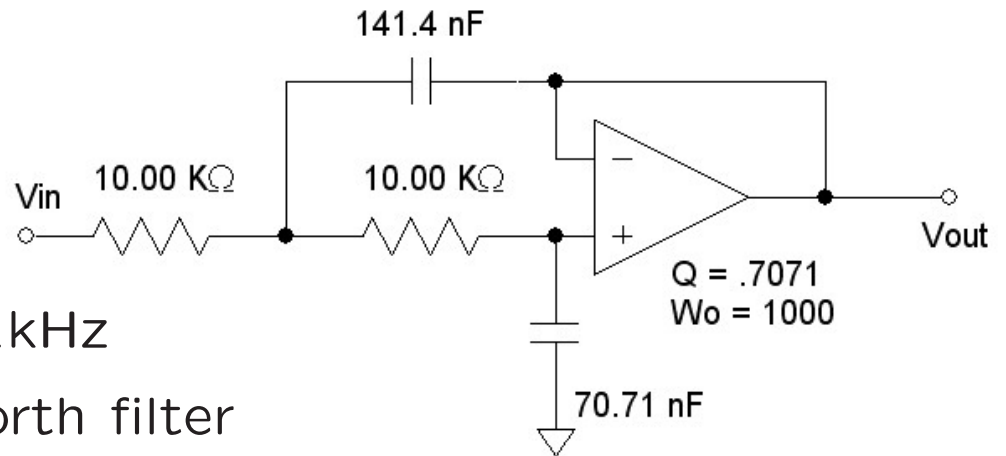
## Background Theory - filtering

Another fine filter:

- 2nd order low pass Butterworth filter
- Pass-band frequency of 1kHz
- 2nd order 1kHz Butterworth filter is a standard 2nd order system



$$V_{out}(s) = G(s)V_{in}(s)$$

where

$$G(s) = \frac{\omega_n^2}{s^2 + 2\beta\omega_n s + \omega_n^2}$$

with  $\omega_n = 2\pi \cdot 1000$ ,  $\beta = \sqrt{1/2} \approx 0.707$ .

## Background Theory - filtering

$$V_{out}(s) = G(s)V_{in}(s)$$

where



$$G(s) = \frac{\omega_n^2}{s^2 + 2\beta\omega_n s + \omega_n^2}$$

with  $\omega_n = 2\pi \cdot 1000$ ,  $\beta = \sqrt{1/2} \approx 0.707$

means:


- well damped filter
- -40dB/dec above 1kHz
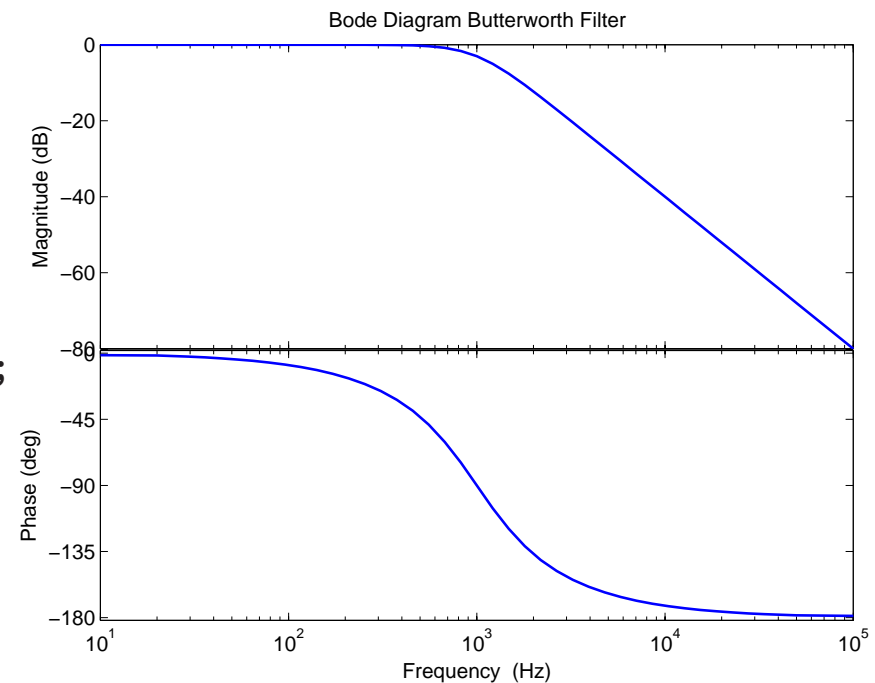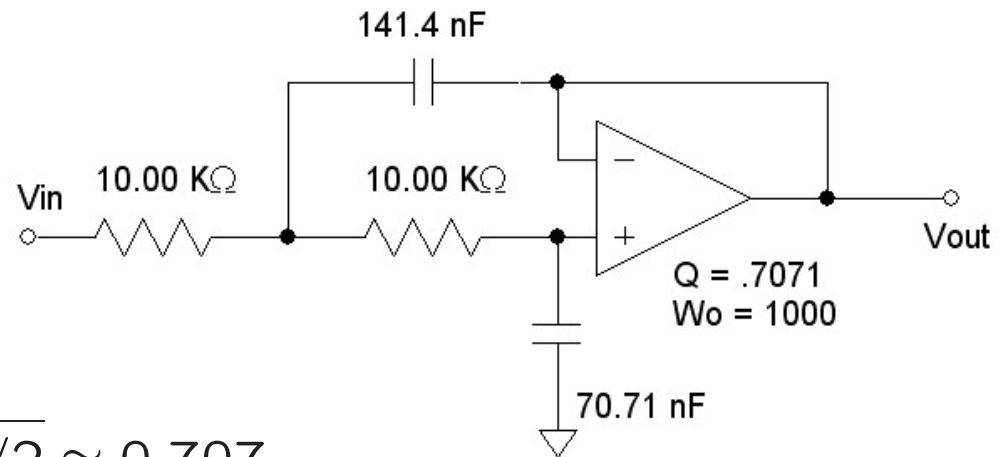
```
>> [num,den]=butter(2,2*pi*1000,'s');  
>> G=tf(num,den);  
>> bode(G)
```


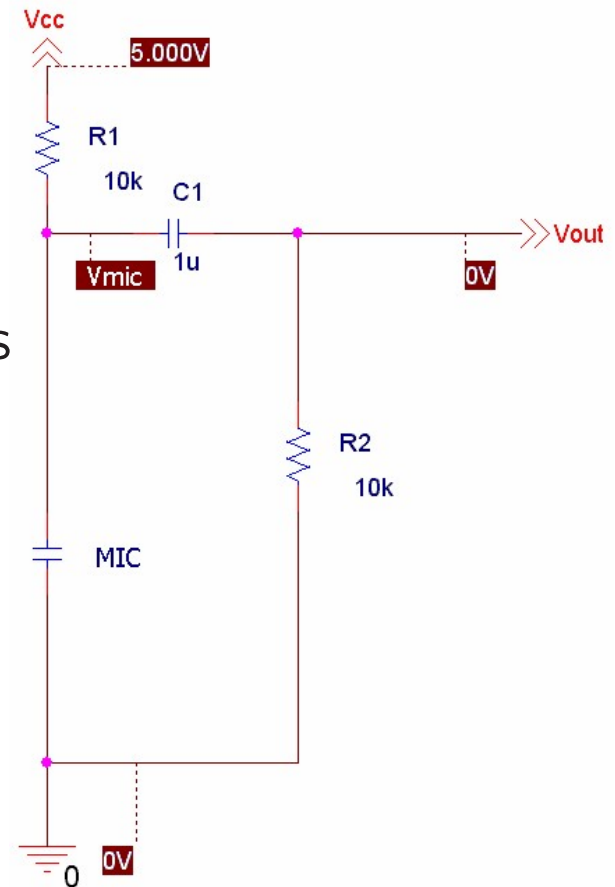
## Laboratory Work - week 1

- Audio application: generate input signal via MIKE-74 electret microphone
- build a DC-bias circuit for the microphone to measure (sound) pressure variations
- Measure the DC-bias (offset) voltages
- Display and analyse the time plots generated by the microphone




## Laboratory Work - week 1

- Build non-inverting amplifier using quad LM324 op-amp
- Measure bias voltages
- Experiments:  
determine gain for different resistor values and avoid clipping on output signal  $V_{out}$ .
- Measure the frequency response of your amplifier.


Connect amplifier to microphone

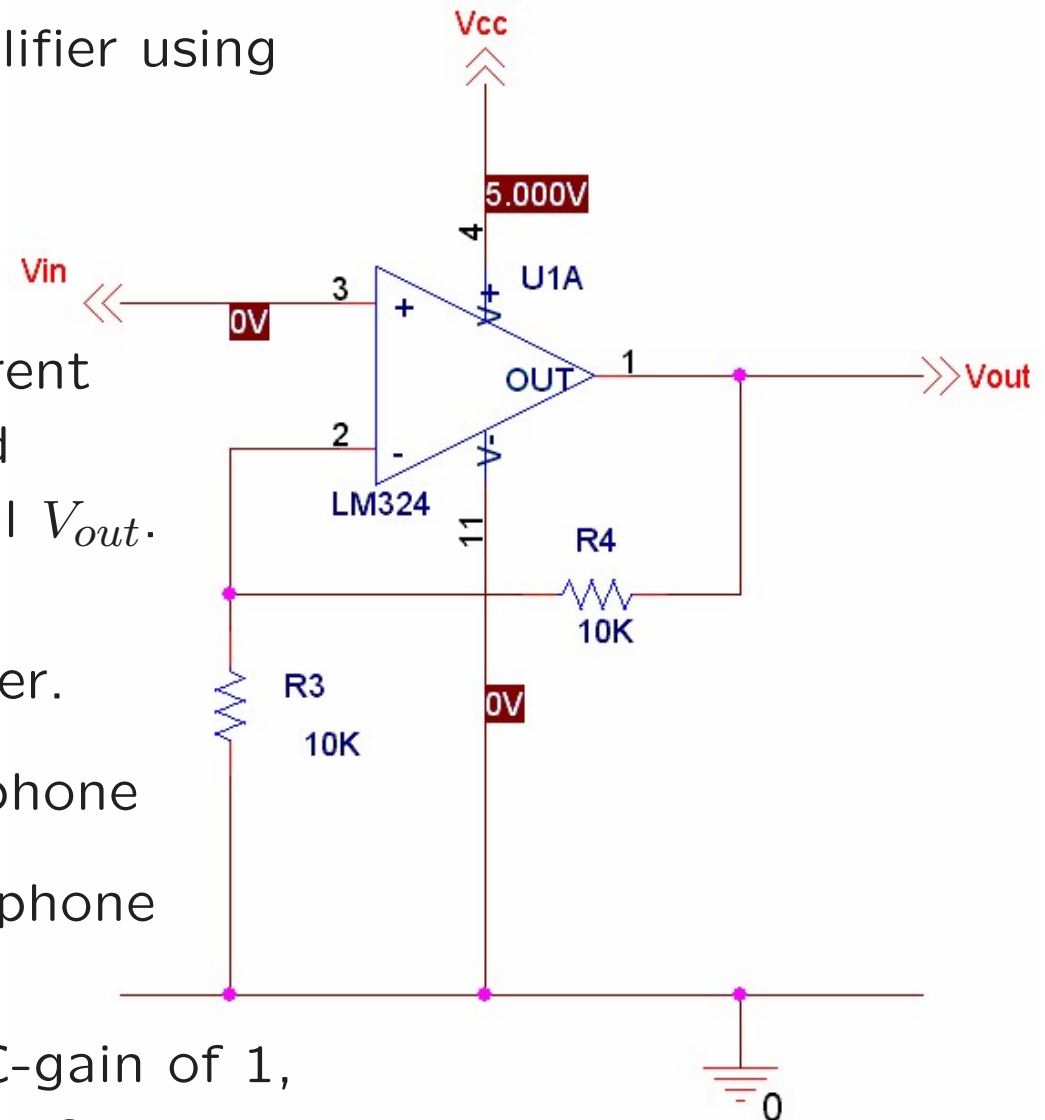- Provide off-set of microphone signal to avoid clipping
- Create lead filter for DC-gain of 1, and high frequency gain of 100.


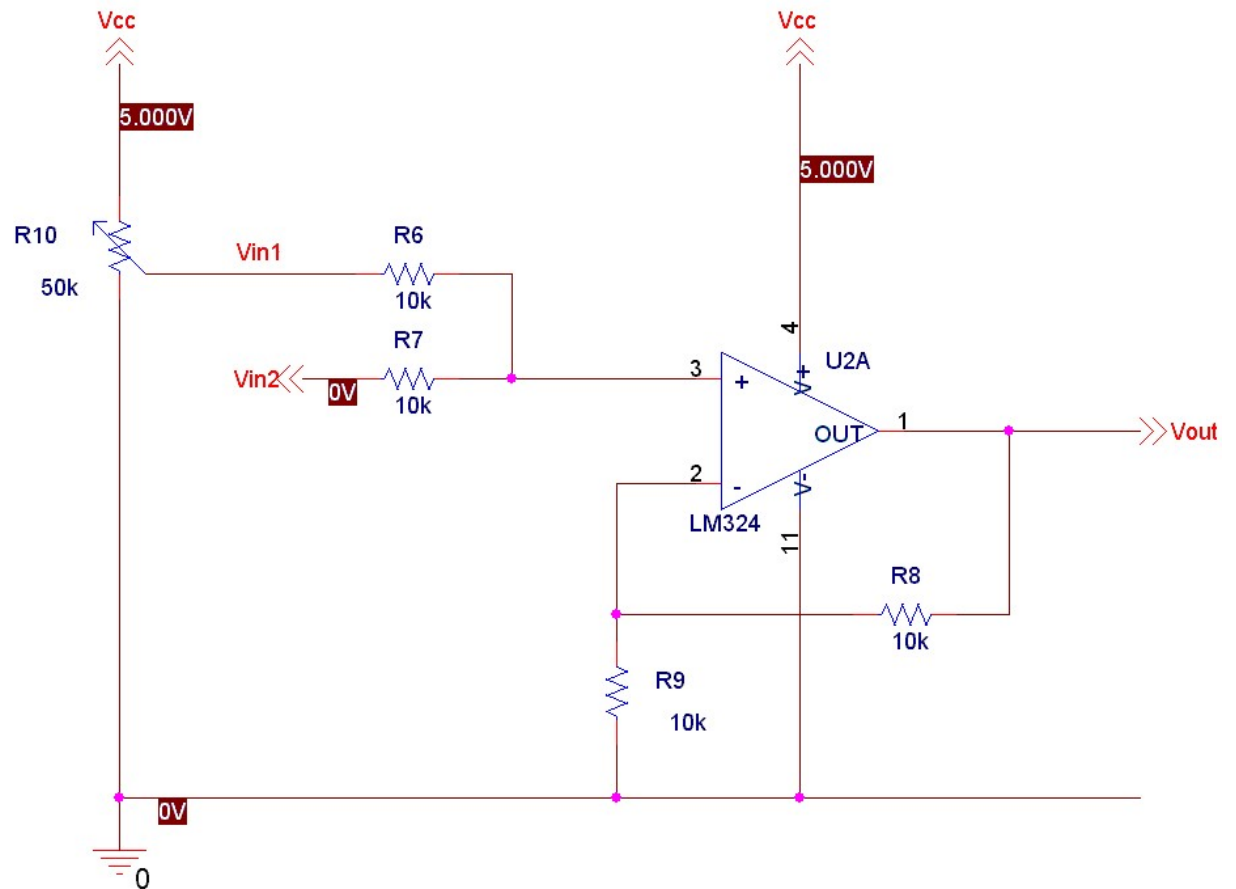
## Laboratory Work - week 2

- Build none inverting summing amplifier
- Experiments: verification of operation (adding of signals)
- Bias voltage adjustment
- Experimental verification of bias effects.




## Laboratory Work - week 2


- Build differential/difference amplifier
- Experiments: verification of operation (difference of signals)
- Bias voltage adjustment
- Gain adjustments and experimental verification

Combine microphone & amplifier circuit from week 1 with difference amplifier to allow mixing of signals.

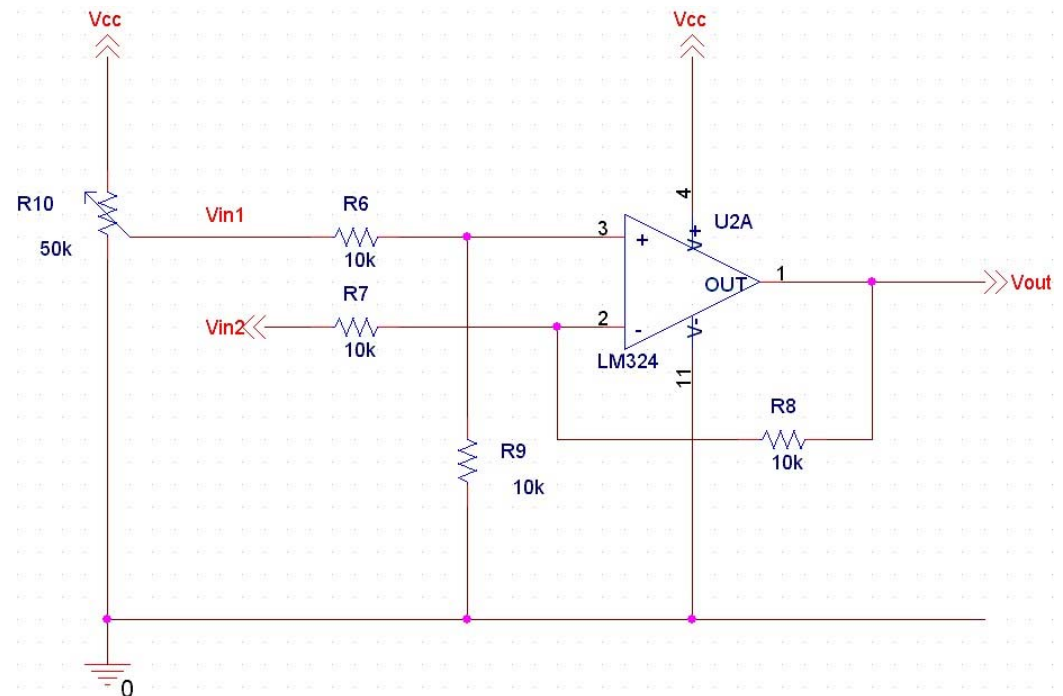- Measure bias voltages
- Demonstrate mixing of sine wave signal and microphone signal without distortions



## Laboratory Work - week 3

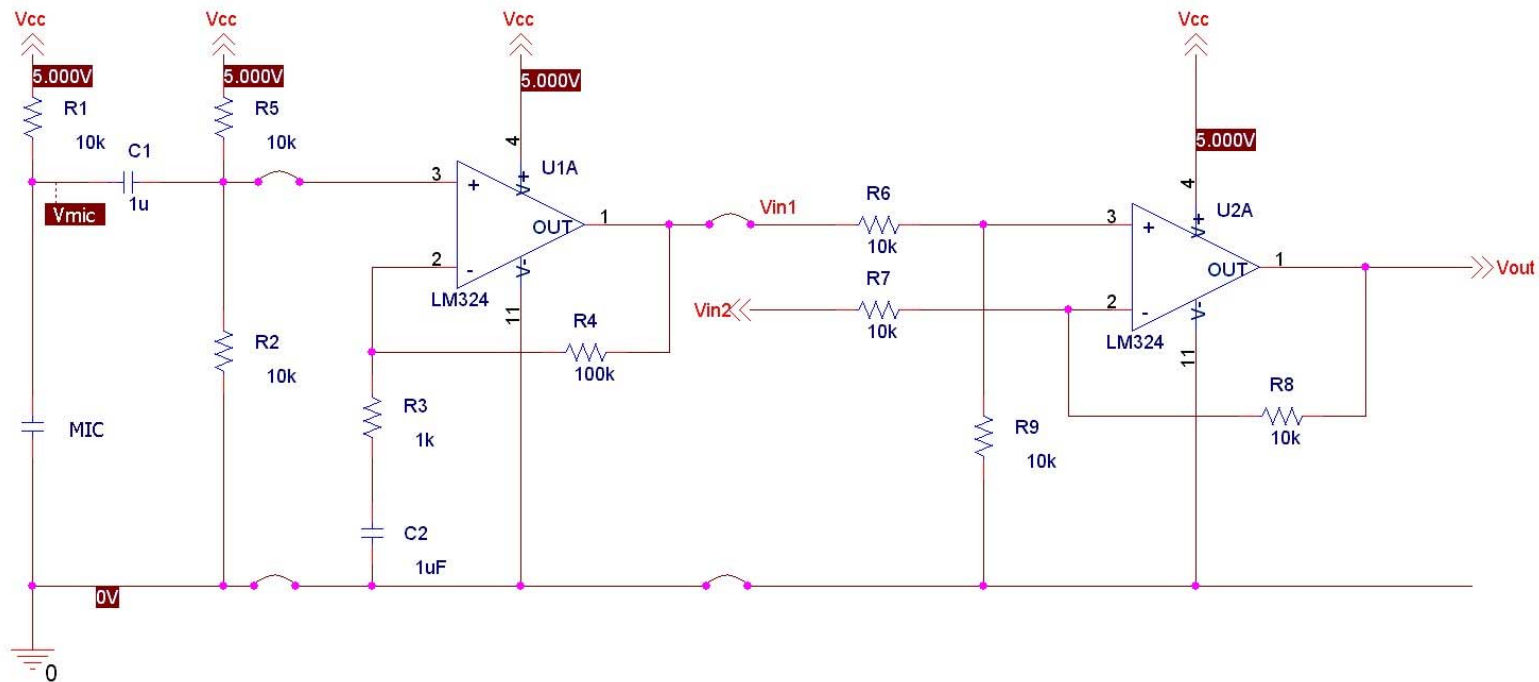

Starting point of week 3: completed amplified/mixed microphone signal.

$V_{out}$  will now be filtered and (optional) power boosted for speaker output.

## Laboratory Work - week 3

- Create active low pass filter with cutt-off frequency of 1kHz.
- Demonstrate filter by measuring amplitude of output signal for sine wave excitation of different frequencies
- Connect filter to circuit of week 2 (microphone, amplifier and differential amplifier for mixing)
- Demonstrate filter by measuring microphone and filtered microphone signal
- Optional: add power boost to circuitry and connect speaker.



## Summary

- (relatively simple) signal conditioning algorithms: *amplification*, *adding/difference* and basic (most 2nd order) *filtering*
- **Challenge:** single source power supply of 5 Volt. **Avoid clipping/distortion of amplified, mixed and filtered signal.**
- insight in op-amp based linear circuits by building and debugging
- compare theory (ideal op-amp) with practice (build and test)
- experimentally verify gain of circuitry
- for error/statistical analysis: measure gain for different resistor (of the same value)
- audio application on a single voltage power supply shows amplification of small signals and careful filter design to maintain DC (off-set)

GOOD LUCK