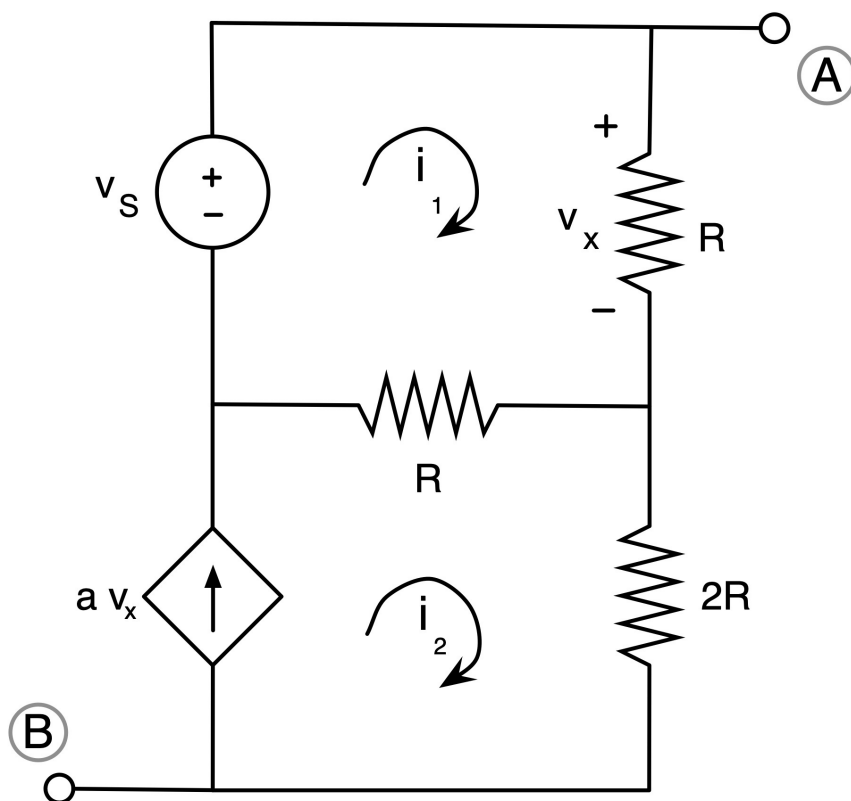


1. Part I



Looking at the circuit, we observe the presence of 1 current source, which is a problem we need to deal with to use mesh current analysis.

The current source belongs to one mesh, so we just use $i_2 = a v_x$ [method 2] [+1 point]

KVL for the top mesh reads

$$R i_1 + R(i_1 - i_2) - V_S = 0 \quad [+1 \text{ point}]$$

We also need to account for the presence of the dependent source. Looking at the circuit, we see that

$$v_x = R i_1 \quad [+1 \text{ point}]$$

This discussion leads to a total of 3 eqs on 3 unknowns i_1, i_2, V_x . We now solve them to find the unknowns.

$$i_2 = aV_x = aRi_1$$

Then

$$2Ri_2 - aR^2i_1 = V_S \Rightarrow R(2-aR)i_1 = V_S$$

$$i_1 = \frac{V_S}{R(2-aR)}$$

Therefore, the open circuit voltage as seen from terminals (A) and (B) is

$$V_{oc} = V_{AB} = Ri_1 + 2Ri_2 = Ri_1 + 2R^2ai_1 =$$

$$= \frac{R(1+2aR)}{R(2-aR)} V_S$$


[+1 point]

Part II

When we turn off the independent source, the dependent one also gets turned off. This can be seen in the expression for the mesh


[+0.5 point]

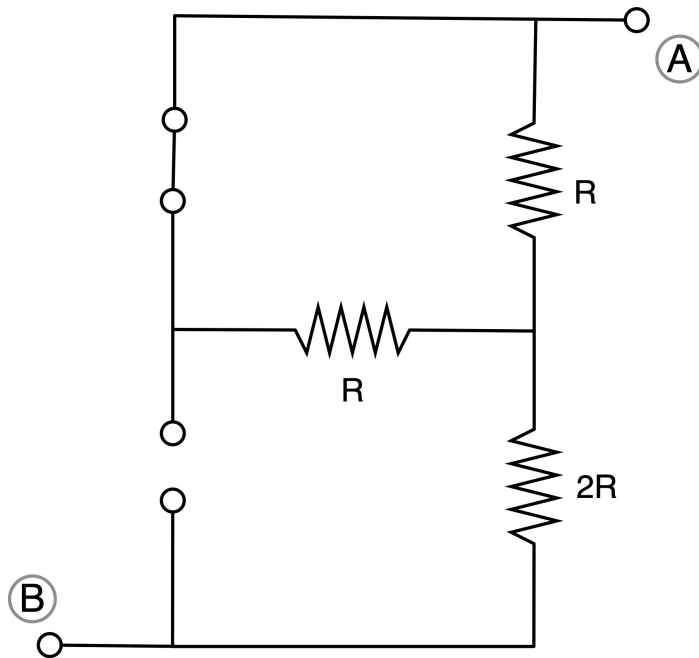currents in Part I: if $V_S = 0$, then both $i_1 = 0 = i_2$, and hence $V_X = 0$. With the sources off, the circuit looks like



[+0.5 point]

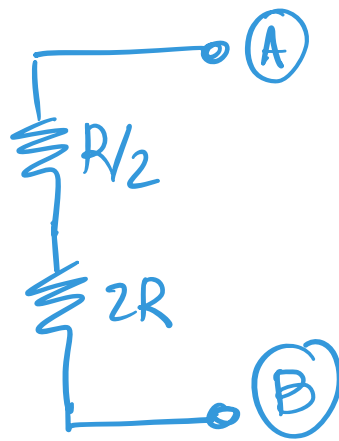Note that the two R resistors are in parallel, so we draw




Combining the resistors in series, we obtain

$$R_{EQ} = 2R + R/2 = \frac{5R}{2} \quad [+1 \text{ point}]$$

Part III

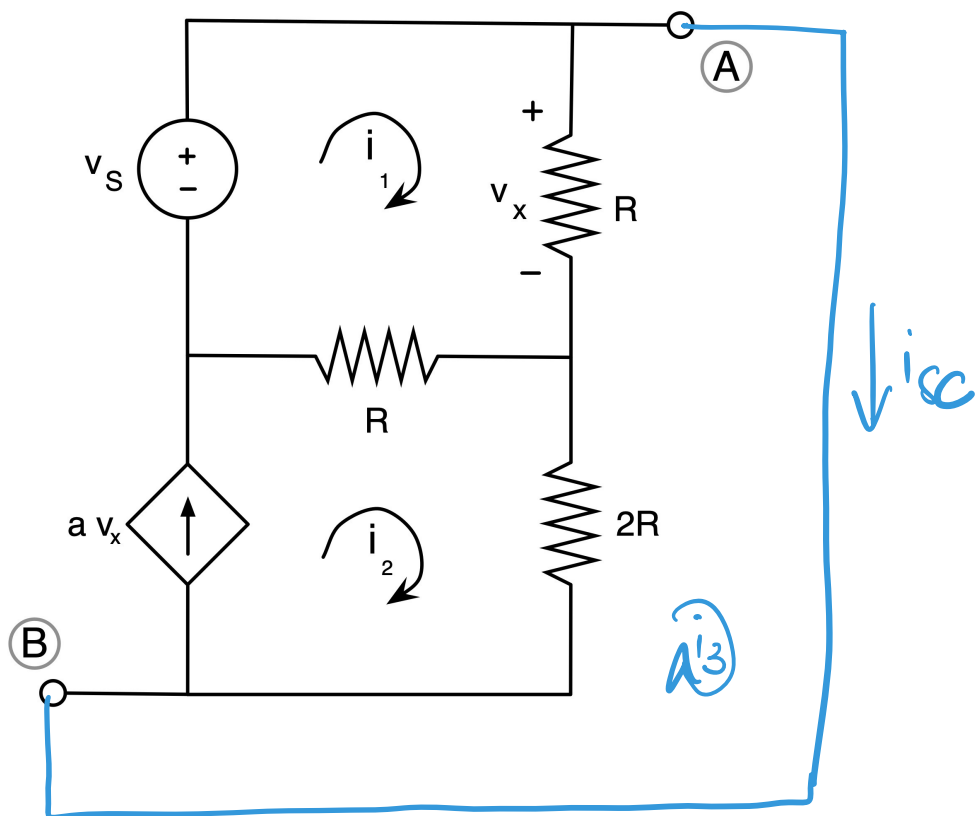We connect terminals (A) and (B) and find the short-circuit current as



The short-circuit current is $i_3 = i_{sc}$. We use mesh-current analysis to find i_1, i_2, i_3 (and v_x).

We deal with the current source by writing

$$i_2 = a v_x \quad (\text{method 2}) \quad [+0.5 \text{ point}]$$

We write KVL for meshes 1 & 3.

$$\text{KVL for mesh 1: } R(i_1 - i_3) + R(i_1 - i_2) - v_s = 0 \quad [+0.5 \text{ point}]$$

$$\text{KVL for mesh 3: } 2R(i_3 - i_2) + R(i_3 - i_1) = 0 \quad [+0.5 \text{ point}]$$

We account for the presence of the dependent source with

$$V_x = R(i_1 - i_3) \quad [+0.5 \text{ point}]$$

So we have 4 eqs in 4 unknowns (i_1, i_2, i_3, V_x). Solving,

$$3i_3 - 2i_2 - i_1 = 0 \quad (\text{from 3rd eq})$$

$$\text{So } i_1 = 3i_3 - 2i_2$$

Substituting in 2nd eq,

$$2R(i_3 - i_2) + 3R(i_3 - i_2) = V_S \Rightarrow 5R(i_3 - i_2) = V_S$$

And

$$i_2 = aV_x = aR(i_1 - i_3) = 2aR(i_3 - i_2)$$

$$\text{So } i_2 = \frac{2aR V_S}{5R} = \frac{2a}{5} V_S$$

$$\text{Therefore, } i_{sc} = i_3 = i_2 + \frac{V_S}{5R} = \frac{1+2aR}{5R} V_S \quad [+1 \text{ point}]$$

Part IV

With the answers to Parts I & II, we have

$$V_T = V_{AB} = \frac{1+2aR}{2-aR} V_S \quad [+0.25 \text{ point}]$$

$$R_T = R_N = \frac{V_T}{i_{sc}} = \frac{1+2aR}{2-aR} V_S \cdot \frac{5R}{1+2aR} \cdot \frac{1}{V_S} = \frac{5R}{2-aR} \quad [+0.5 \text{ point}]$$


$$i_N = i_{SC} = \frac{1+2aR}{5R} V_S$$

[+0.25 point]

The reason why $R_T = R_N$ is not equal to R_{EQ} computed in Part II is because, when we turn off the IVS, the dependent source also gets turned off and its effect is not taken into account.

Part V

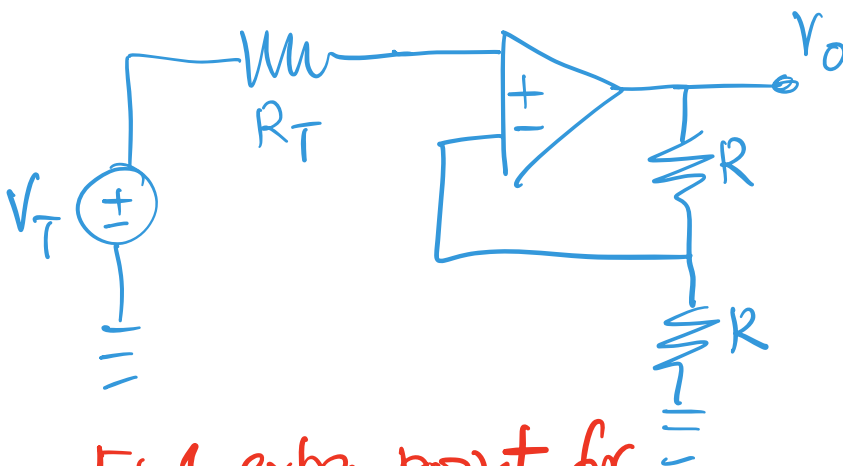Computing this directly would be quite involved. However, we have already done all the hard work computing the Thevenin equivalent. Connecting the circuits is the same as



This is a non-inverting op-amp, and therefore


$$V_O = \frac{R+R}{R} V_T =$$

$$= 2V_T = 2 \frac{1+2aR}{2-aR} V_S$$

[+1 extra point]

[+1 extra point for correctly articulating how to use Thevenin eqn. here]

2.-

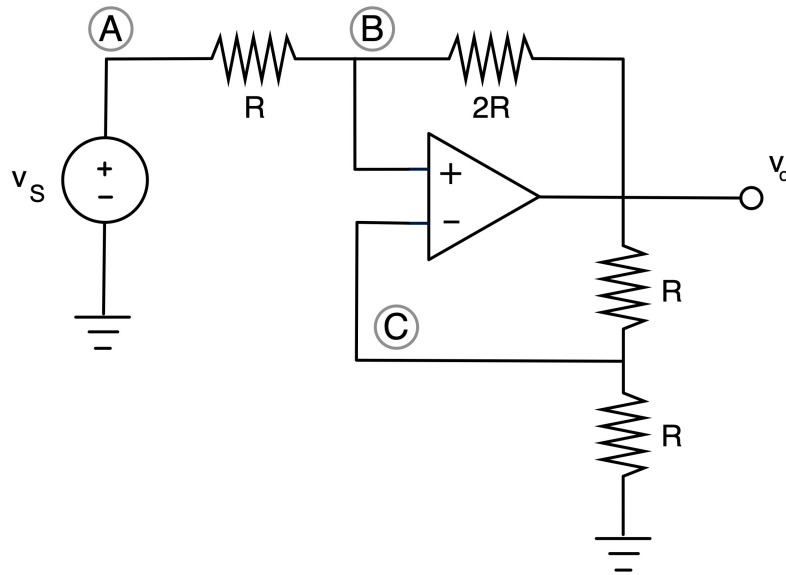

Part I

As instructed, we use nodal analysis to figure out the output voltage.

We know $v_A = v_s$.

[+ 1 point]

KCL at node (B) gives us (with $i_p = 0$)

$$\frac{1}{R}(v_B - v_s) + \frac{1}{2R}(v_B - v_o) = 0$$

[+ 1 point]

KCL at node (C) (with $i_n = 0$),

$$\frac{1}{R}(v_C - v_o) + \frac{1}{R}(v_C) = 0$$

[+ 1 point]

From ideal conditions, we have

$$v_B = v_C$$

[+ 1 point]

We have 3 eqs. in 3 unknowns V_B, V_C, V_O , so we can solve. From the 2nd equation,

$$V_O = 2V_C = 2V_B$$

Substituting into the 1st equation,

$$\frac{1}{R}(V_B - V_S) + \frac{1}{2R}(V_B - 2V_B) = 0 \Rightarrow V_B = 2V_S$$

Therefore

$$V_O = 2V_B = 4V_S$$

[+ 1 point]

Part II

When the engineer connects the load resistor $R_L = 10\Omega$, the voltage drop this resistor sees is V_O .

If the connected source is $V_S = 3V$, then $4 \cdot V_S = 4 \cdot 3 = 12 > 10V$, so the op-amp gets saturated and $V_O = 10V$. [+ 1 point]

Therefore, the power delivered to the load is $P_L = V_O^2 \cdot \frac{1}{R_L} = \frac{100}{10} = 10W$ [+ 1 point]

The range of values for the voltage source so that the op-amp operates linearly is

$$-10V < V_o = 4V_s < 10V$$


$$-2.5V < V_s < 2.5V$$

[+ 1 point]

Part III

Since we want to design a circuit with $V_o = 4V_s$, we use a non-inverting op-amp.

[+ 1 point]

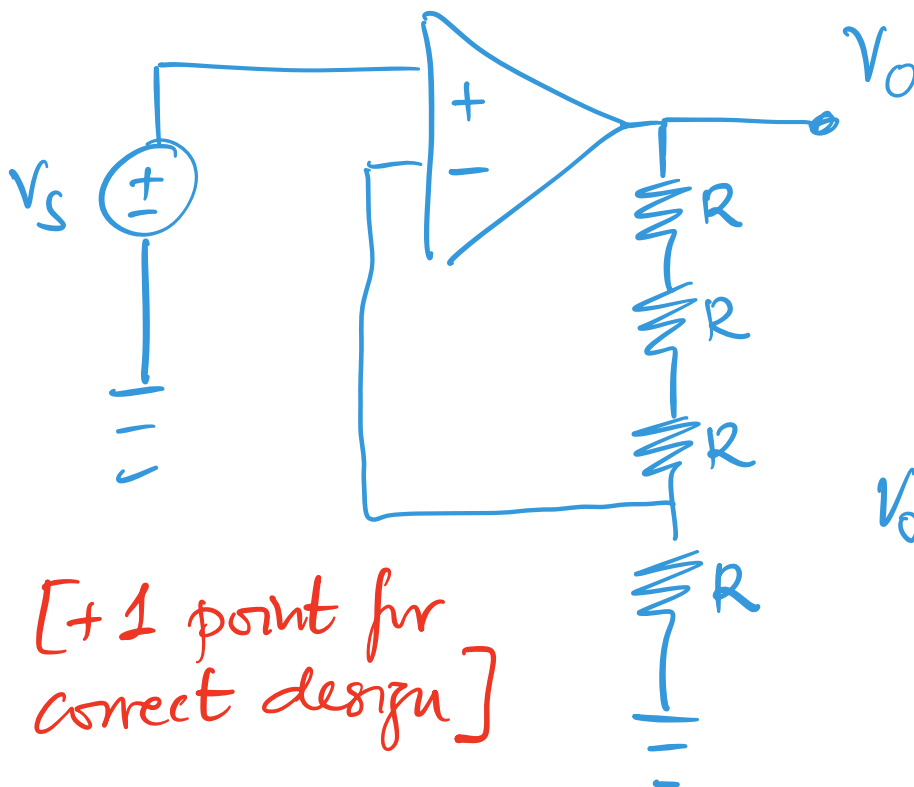

[+ 1 point for correct design]

With this, we have

$$V_o = \frac{3R+R}{R} V_s = 4V_s$$